

Reading Data from the ADS7862

Tom Hendrick

Data Acquisition Products

ABSTRACT

This application note presents a method for interfacing multiple ADS7862 12-bit SAR analog-to-digital converters (ADCs) to the parallel data bus of a host processor. Care must be taken when multiple devices share the data bus in order to maintain the integrity of channel sampling information.

Contents

1	Introduction	1
2	ADS7862 Design Problem	1
3	Parallel Interface of the ADS7862	2
4	Conclusion	2

1 Introduction

The ADS7862 is a 2+2 channel, 12-bit parallel version of the ADS7861. The device features two independent ADCs, each with a two-channel mux. Besides the parallel interface, a major difference between the devices is the output data format. The ADS7861 provides conversion channel information in a serial output data stream; the ADS7862, however, does not contain this information.

2 ADS7862 Design Problem

Assume three ADS7862 data converters share a common data bus. Each device can be independently **chip-selected** by means of a simple address decoding scheme. The start of conversion to all devices could be simultaneous or independent, but is controlled by an external source. We will also assume the BUSY signal from each ADC maps to an external interrupt pin of the host controller. The block diagram of [Figure 1](#) represents the basic interface and assumptions.

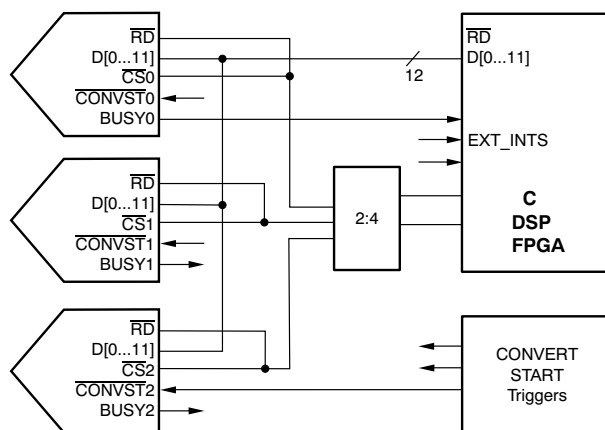


Figure 1. Hardware Interface Block Diagram

All trademarks are the property of their respective owners.

3 Parallel Interface of the ADS7862

Taking a closer look at [Figure 1](#), one might notice that the \overline{RD} pin on each device is connected to the device chip select (\overline{CS}) pin. The reason for this connection is to maintain data channel selection integrity.

Typically, a host processor such as a DSP will have an active-low read strobe (\overline{RD}) that is used for strobing the read pin of external devices; thus, one might ask, “Why can’t we use that for the ADS7862?” The reason for not using this option is because the ADS7862 does not internally validate the \overline{RD} strobe with the device \overline{CS} pin. If the configuration shown in [Figure 1](#) tied a common \overline{RD} strobe to all three devices, each part in the chain would increment its read pointer regardless of whether it was chip-selected or not.

The only way to ensure channel data integrity is to strobe \overline{RD} only while the device is chip-selected. The first read cycle will be from Channel 0 and the second from Channel 1. The channel pair (pair A or B) is determined by the state of the A0 pin. Since there is no set-up or hold time minimums for the relationship of \overline{RD} and \overline{CS} , the pins can be tied together as shown in [Figure 1](#), provided the signal is pulsed low for a minimum of 30ns.

The ADS7862 datasheet ([SBAS101](#)) shows several timing diagrams related to the individual control of the \overline{RD} and \overline{CS} pins, [Figure 2](#) shows two alternative methods of reading data from the ADS7862 when sharing a parallel data bus with additional peripherals. Option 1 depicts a standard \overline{RD} strobe logically *OR'd* with the device chip-select. Option 2 proposes a decoded address scheme that ties \overline{CS} and \overline{RD} together and feeds the signal to both pins simultaneously.

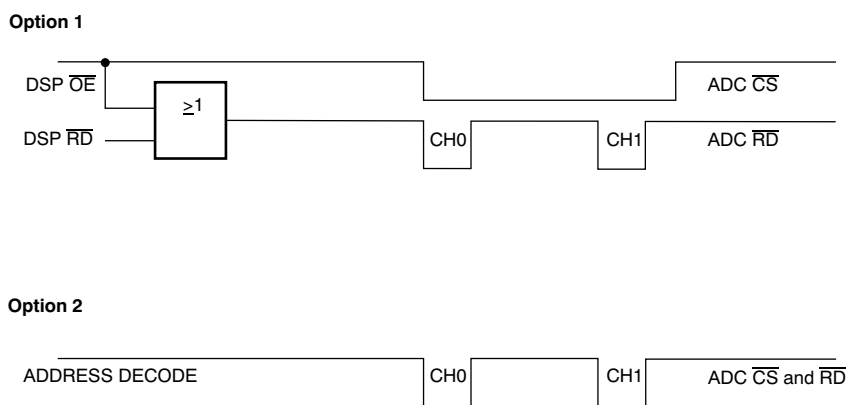


Figure 2. Alternate Control Options

4 Conclusion

Our simple design example above assumes multiple ADS7862 devices sharing a common data bus. In reality, this information pertains to any additional parallel device which might share common strobes such as an output or read enable. When sharing a common data bus and control signals with other peripherals, the ADS7862 should have its \overline{RD} pin connected to or gated by the device \overline{CS} pin.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265