

Application Note

TPLD Application in DC-DC Design



Nanxiao Zhong

ABSTRACT

TI programmable logic device (TPLD) family offers abundant logic resources, enabling flexible applications across consumer electronics, industrial systems, and data centers. This article proposes a method for utilizing TPLDs as PWM expanders in DC/DC power applications through graphical programming, thereby saving valuable DSP resources.

Table of Contents

1 Introduction	2
2 PCM Buck DC/DC Diagram	2
3 TPLD-Based DC/DC PWM Generation	3
3.1 TPLD-Based Topology PWM Generation	3
3.2 TPLD-Based PCM PWM Generation	5
3.3 TPLD-Based Multiphase Clock Generation	6
4 Summary	8
5 References	8

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

The TPLD family integrates a rich set of peripheral resources, including general-purpose logic gates, RS flip-flops, comparators, and timers, making it widely applicable across diverse scenarios with stringent logic and timing requirements. In multiphase DC/DC applications, the number of PWM channels, logic levels, and phase-shifted clocks pose significant challenges to both DSP resource utilization and software development. This paper presents a solution that utilizes TPLD as a PWM expander, effectively addressing the challenges of limited DSP resources and complex software development in single phase/interleaved parallel DC/DC converters.

2 PCM Buck DC/DC Diagram

 


Figure 2-1. Peak Current Mode Buck Diagram

This paper discusses TPLD applications based on Buck converter topology. As shown in [Figure 2-1](#), the architecture utilizes Peak Current Mode (PCM) control, which reduces the control-to-output small-signal transfer function to a first-order (single-pole) system. This significantly simplifies loop compensation network design and delivers fast load transient response. In multiphase power applications, interleaving technology is widely adopted; its primary advantage lies in shifting the phases of inductor currents across different phases to cancel output voltage ripples, thereby reducing the required output capacitance in high-current scenarios. Based on the level of DSP integration, this paper introduces three distinct implementation schemes: (1) The host DSP provides a single-phase base PWM signal, which TPLD then expands to support the target topologies, such as Buck, ACF, or PSFB; (2) The DSP provides the clock and error signals, while the TPLD handles the complete PWM signal generation; (3) TPLD independently manages both clock phase-shifting and PWM signal generation.

3 TPLD-Based DC/DC PWM Generation

3.1 TPLD-Based Topology PWM Generation

This section details the implementation scheme where the host DSP generates the initial PWM waveform, and TPLD handles the generation of the corresponding complementary PWM signals. As shown in Figure 2, the DSP or analog controller generates the initial closed-loop PWM signal. TPLD then processes the rising edge of this PWM signal using internal inverters and delay blocks to generate the complementary PWM waveforms with dead-time insertion.

 


Figure 3-1. Synchronous Buck PWM Logic Diagram

 


Figure 3-2. Synchronous Buck Simulation Waveforms

In practical applications, the GPIOs can be configured to operate in digital input mode with a Schmitt trigger to enhance the noise immunity of TPLD. For dead-time control, the configuration can also be offloaded to external RC circuits on the output GPIOs or implemented via the inherent dead-time design of the gate drivers, thereby simplifying TPLD internal logic design. The primary advantage of this scheme is its simple implementation; however, the disadvantage is that it only saves a single PWM channel in a standard Buck converter. In contrast, for more complex topologies, such as Synchronous Rectification Active Clamp Forward (SR-ACF) requiring 4 PWMs, or Phase-Shifted Full-Bridge (PSFB) requiring eight PWMs, this approach can offload a significantly higher number of host controller GPIO and PWM resources.

3.2 TPLD-Based PCM PWM Generation

This section introduces the implementation of Peak Current Mode (PCM) PWM signal generation in a Buck converter using TPLD. As shown in Figure 5, the host controller or an external operational amplifier provides the compensated error signal. TPLD utilizes its internal comparator to compare this error signal with the triangular inductor current waveform, generating an initial comparator output. This output is then processed by an RS flip-flop synchronized with the clock signal to establish the initial PWM waveform. Finally, the internal logic circuitry generates complementary PWM outputs.

 


Figure 3-3. PCM Buck PWM Logic Diagram

Figure 3-3 illustrates a simplified control block diagram. In practical designs, the overall performance and reliability of this implementation can be enhanced through the following methods:

1. When the duty cycle exceeds 50%, slope compensation must be introduced to the current sensing signal derived from the clock to prevent subharmonic oscillation
2. Internal comparators or additional logic circuitry can be utilized to construct maximum duty cycle limiting and cycle-by-cycle overcurrent protection circuits
3. For high-frequency applications, an external high-speed comparator can be employed to achieve faster transient response.

Clock and PWM generation for a buck converter can be implemented by TPLD. As shown in [Figure 3-4](#), the internal 2MHz oscillator is used as the source clock. A 50% duty-cycle Phase-1 clock is generated through the counter block and D flip-flops. Four interleaved phase clocks are then derived from the Phase-1 clock by using delay blocks, enabling interleaved multiphase operation.

 


Figure 3-4. Interleaved Phase-Clock Logic Diagram

 


Figure 3-5. Interleaved Phase-Clock Simulation Waveforms

Based on this config, TPLD can interface with the two mentioned PWM generation schemes to implement interleaved parallel DC/DC designs. In this implementation, TPLD can process nearly all functional tasks within the DC/DC converter circuitry except for loop compensation. This approach further reduces host controller resource requirements in multiphase power supply applications.

4 Summary

This paper utilizes TI's TPLD series as a graphical-programmed PWM expander in single /interleaved DC/DC converters. By processing the design of clock phase-shifting and complementary PWM generation, TPLD significantly offloads clock and PWM logic control resources from the host controller. This approach effectively conserves DSP resources, lowers software complexity, and facilitates hardware engineers in rapid development.

Learn more about TPLD with the [Engineer's guide to programmable logic](#).

5 References

1. Texas Instruments, [TPLD1202 Programmable Logic Device With I2 C/SPI and 10-GPIO](#) , datasheet.
2. Texas Instruments, [High-Speed Operation in TPLD](#), application brief.
3. Texas Instruments, [Power Sequencing With Feedback Using TI Programmable Logic Devices](#), application brief.
4. Texas Instruments, [使用 TI 可编程逻辑器件 \(TPLD\) 中的时序分量](#), application note.
5. Texas Instruments, [Parallel Operation of the Buck-Boost Converters Using LM5177 Buck-Boost Controller](#), application note.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025