

High-Performance Analog Products

Analog Applications Journal

First Quarter, 2012



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP™ Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E™ Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

SSZZ022C

Contents

Introduction	4
Power Management	
Turbo-boost charger supports CPU turbo mode	5
<p>High-performance mobile computers with turbo-mode CPUs have peak power demands that could require an AC adapter with a significantly higher power rating than standard CPUs. Instead of a higher-cost adapter, a high-efficiency, turbo-boost charger can be used to manage the power from the battery and adapter to meet the excessive power demands when the CPU operates in turbo mode. This article discusses the operation of a typical turbo-boost charger and presents efficiency analysis of its two modes of operation.</p>	
Benefits of a multiphase buck converter	8
<p>Single-phase, low-voltage buck converters work well at up to about 25 A; but at higher currents, multiphase buck converters offer several performance advantages. These include higher efficiency due to lower transitional losses; lower output ripple; better transient performance; and lower ripple-current-power dissipation in the input capacitor, FETs, and inductors. This article discusses these advantages, shows waveforms from a typical application, and provides a performance analysis and tips for board layout.</p>	
Downslope compensation for buck converters when the duty cycle exceeds 50%	14
<p>Current-mode control in a PWM forward converter with a duty cycle greater than 50% has the potential of going into subharmonic oscillations. This article presents as an example a three-switch forward converter that provides improved stability with downslope compensation and extends the maximum duty cycle to 67%. Included are typical waveforms and calculations to determine the value of the current-sensing resistor.</p>	
High-efficiency AC adapters for USB charging	18
<p>Battery chargers with USB outlets are becoming a universal standard for 10- to 25-W chargers. This article explores the advantages of using a synchronous rectifier to increase efficiency and satisfy the push towards high-density, small-form-factor adapters. Included are typical waveforms and efficiency plots comparing the performance of a Schottky diode to that of a synchronous rectifier.</p>	
Amplifiers: Op Amps	
Measuring op amp settling time by using sample-and-hold technique	21
<p>This article describes a new methodology that has proven to be effective in making settling-time measurements for modern op amps. Detailed is a relatively inexpensive and simple way to measure settling time that bases accuracy and precision on the relative speed of the waveform generator and the sample-and-hold circuit. Included with a description of the test setup are typical waveforms and settling-time plots.</p>	
Index of Articles	25
TI Worldwide Technical Support	31

To view past issues of the
***Analog Applications Journal*, visit the Web site**
www.ti.com/aaj

Introduction

Analog Applications Journal is a collection of analog application articles designed to give readers a basic understanding of TI products and to provide simple but practical examples for typical applications. Written not only for design engineers but also for engineering managers, technicians, system designers and marketing and sales personnel, the book emphasizes general application concepts over lengthy mathematical analyses.

These applications are not intended as “how-to” instructions for specific circuits but as examples of how devices could be used to solve specific design requirements. Readers will find tutorial information as well as practical engineering solutions on components from the following categories:

- Data Acquisition
- Power Management
- Interface (Data Transmission)
- Amplifiers: Audio
- Amplifiers: Op Amps
- Low-Power RF
- General Interest

Where applicable, readers will also find software routines and program structures. Finally, *Analog Applications Journal* includes helpful hints and rules of thumb to guide readers in preparing for their design.

Turbo-boost charger supports CPU turbo mode

By Jinrong Qian, *Product Line Manager*,
and Suheng Chen, *Design Engineer*

Introduction


To continuously improve a CPU's dynamic performance for fast processing of multiple complicated tasks in mobile computers, it is essential to increase the CPU frequency with full utilization of the CPU's thermal capability in a short time period. This could cause the total power required by the system to exceed the power delivered from a power source like an AC adapter, which may result in crashing the adapter. One possible solution is to increase the adapter's power rating, but at a higher cost. This article discusses the turbo-boost charger, which allows the adapter and battery to power the system simultaneously to meet instantaneous and excessive power demands from a notebook computer system operating in CPU turbo mode.

In traditional mobile computer systems, an AC adapter provides the power, and any power not needed by the system is used to charge the battery. When an AC adapter is not available, the battery provides power to the system by turning on switch S1 (see Figure 1). The adapter can be used to power the system and charge the battery simultaneously, which may require it to have a high power rating, increasing both its size and its cost without active control. Dynamic power management (DPM) typically is used to accurately monitor the total power drawn from the adapter, which gives high priority to powering the system.

Once the adapter's power limit is reached, the DPM control system regulates the input current (power) by reducing the charge current, providing power directly from the adapter to the system without power conversion for optimum efficiency. With the heaviest system load, all the adapter power is used to power the system without charging the battery at all. Therefore, the main design criterion is to make sure that the adapter's power rating is high enough to support peak CPU power and other system power.

To meet the increasing demand for improved system performance in processing complicated tasks fast with multiple CPU cores and enhanced graphics processor units (GPUs), Intel developed its turbo-boost technology in the Sandy Bridge processors. This technology allows processors to burst their power above the thermal design

Figure 1. Adapter and battery-charger system

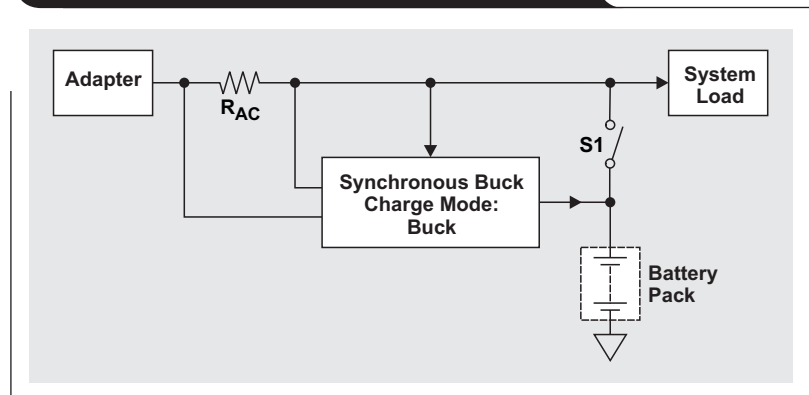

power (TDP) for a short time period in the range from a few tens of milliseconds to tens of seconds. However, an AC adapter is designed to provide the power just above the demand from the processors and platform at a TDP level considering the design tolerance. When a charger system detects that the adapter has reached its input power rating after its charge current has been reduced to zero through DPM, the simplest way to avoid crashing the AC adapter is to achieve CPU throttling by reducing the CPU frequency, which compromises system performance. How can the CPU be operated faster at above the TDP level for a short time period without crashing the adapter or increasing its power rating?

Turbo-boost battery charger


When the total power required by the system load and battery charger reaches the adapter's power limit, DPM starts to reduce the battery's charge current. The battery charger stops charging, and its charge current is reduced to zero when the system load alone reaches the AC adapter's power limit. As the system continues to increase its load during the CPU turbo mode, the battery charger, which is usually a synchronous buck converter, is idle, as no remaining power is available to charge the battery. The synchronous buck converter is actually a bidirectional DC/DC converter that can operate in either buck or boost mode, depending on the operating conditions. If the battery has enough capacity, the battery charger can operate in boost mode to provide power to the system in addition

to the power from the AC adapter. Figure 2 shows a block diagram of a turbo-boost battery charger.

When and how does the battery charger start to transition from buck charge mode to boost discharge mode? The system can enter CPU turbo mode at any time, and it is usually too late to inform the charger to initiate this transition through an SMBus. The charger should automatically detect which operating mode is needed. It is also critical that the system be designed to achieve a fast transition from buck to boost mode and vice versa. A DC/DC converter needs a soft-start time of a few hundred microseconds to a few milliseconds to minimize the inrush current. The adapter should have a strong overloading capability to support the whole system's peak power before the charger transitions into boost discharge mode. Most of the AC adapters currently available can hold their output voltage over a few milliseconds.


Figure 3 shows an application circuit for a turbo-boost battery charger supporting CPU turbo mode. The R_{AC} current-sense resistor is used to detect the AC adapter current for the DPM function and to determine whether the battery charger is operating in buck charge mode or boost discharge mode. Current-sense resistor R7 is used

Figure 2. Turbo-boost battery charger in CPU turbo mode

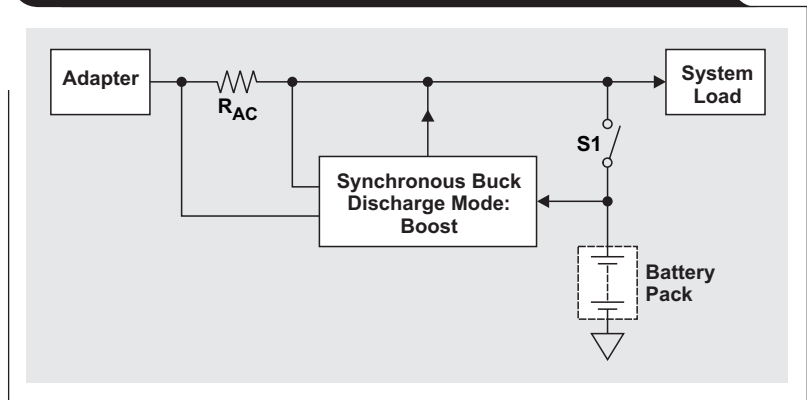

to sense the battery charge current programmed from the host through the SMBus based on the battery conditions. The total power drawn by both the charger and the system can be monitored through the I_{OUT} output, which is 20 times the voltage drop across sense resistor R_{AC} for achieving CPU throttling, if needed. Through SMBus control registers, the battery's boost discharge mode can be enabled or disabled based on the battery's state of charge and temperature conditions. In boost discharge mode, the circuit provides additional cycle-by-cycle current-limit protection by monitoring the voltage drop across the

Figure 3. Application circuit for turbo-boost battery charger

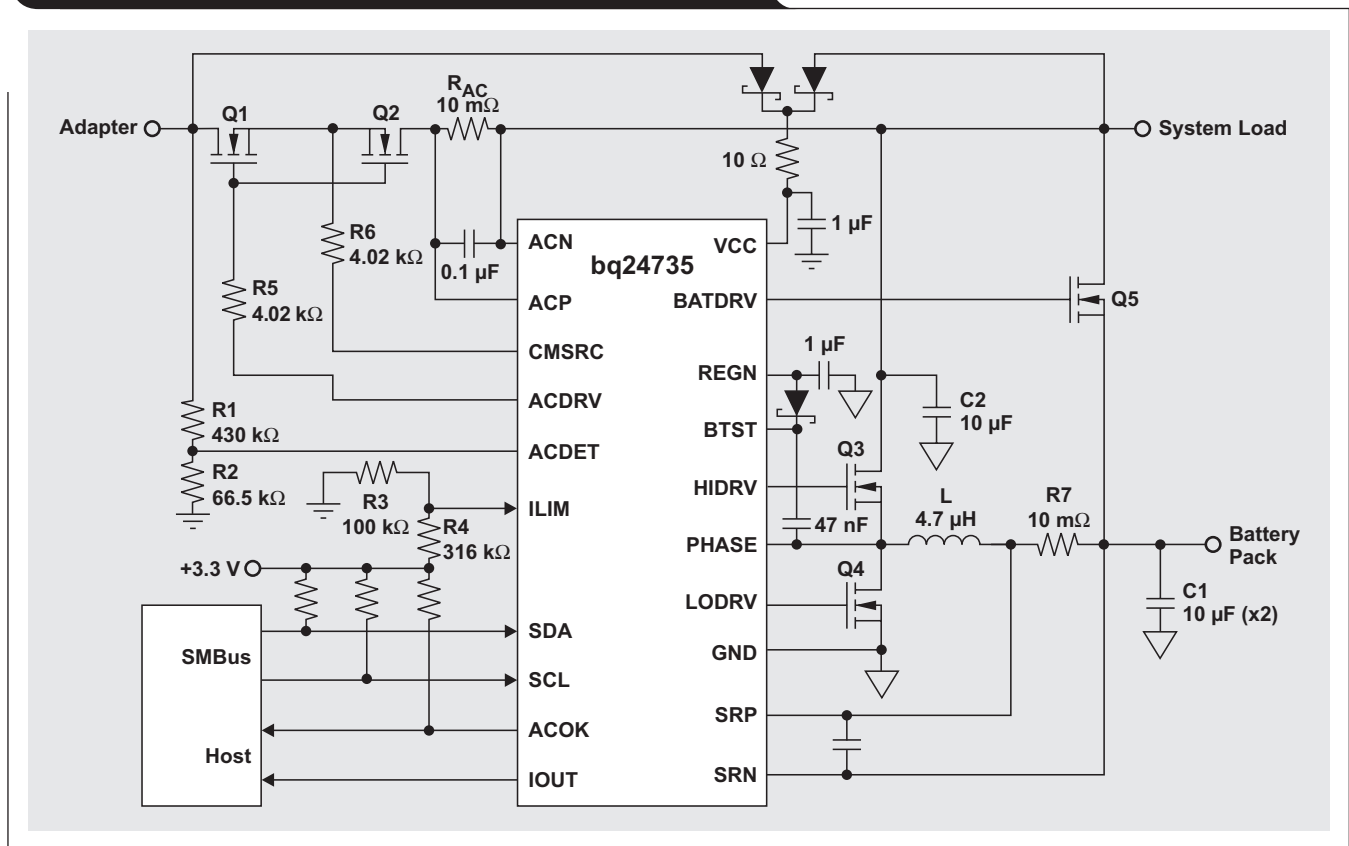

low-side MOSFET, Q4. To achieve a small form factor for a notebook computer like Intel's Ultrabook™, the switching frequency can be programmed at 615, 750, or 885 kHz. This minimizes the inductor size and the number of output capacitors. To further reduce the number of external components, the charger's controller chip fully integrates the loop compensators for the charge current, the charge voltage, and the input-current regulation loops. The power-source selector MOSFET controller is also integrated in the charger. Furthermore, the charger system uses all n-channel MOSFETs for cost reduction instead of the p-channel power MOSFETs used in traditional charge solutions. Another benefit of this turbo-boost charger system is that it can be used for either function without changing the bill of materials. System designers can do a quick system-performance evaluation without additional hardware-design effort.

Figure 4 shows the switching waveforms that occur during the transition from buck charge mode to boost discharge mode. When the input current reaches the adapter's maximum power limit due to a system-load increase, the battery charger stops charging and the battery transitions into boost mode to provide additional power to the system.

Figure 5 shows the efficiency of the turbo-boost charger. It can be seen that over 94% efficiency is achieved for charging and discharging a 3-cell or 4-cell battery pack. If the battery is removed or the battery's remaining capacity is not high enough, it is necessary to throttle the CPU to avoid the adapter crash.

Now the battery can be discharged even when the adapter is connected. However, one possible concern is the battery cycle life. Since the boost discharge mode lasts from only tens of milliseconds to tens of seconds, the impact on battery cycle life will be minimal. Battery degradation is proportional to the battery-cell voltage; so the higher this voltage is, the faster the battery will degrade and the shorter its cycle life will be. Discharging the battery in the boost discharge mode results in a lower battery-cell voltage, reducing the degradation of the battery and lengthening its cycle life.

Conclusion

A turbo-boost charger is a simple and cost-effective way for a battery to supplement AC adapter power for short periods when an AC adapter and battery simultaneously power the system. This topology supports CPU turbo mode while ensuring the lowest system cost without the need

Figure 4. Waveforms between buck charge mode and boost discharge mode


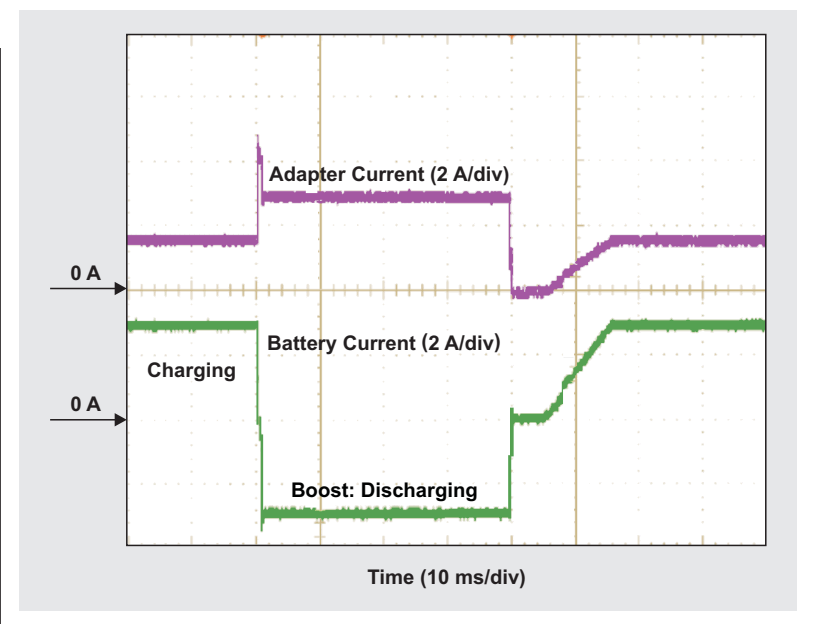


Figure 5. Efficiency of turbo-boost charger

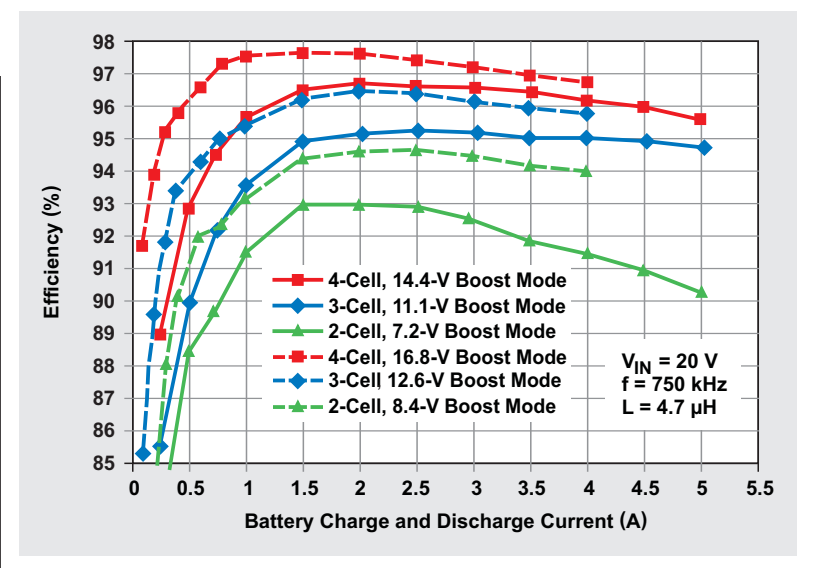

for upgrading to an AC adapter rated for peak system power. The test results show that the turbo-boost charger is a practical solution in real mobile-computer designs.

Related Web sites

power.ti.com

www.ti.com/product/bq24735

Benefits of a multiphase buck converter

By David Baba

Applications Engineering Manager

Introduction

Single-phase buck controllers work well for low-voltage converter applications with currents of up to approximately 25 A, but power dissipation and efficiency start to become an issue at higher currents. One suitable approach is to use a multiphase buck controller. This article briefly discusses the benefits of using a multiphase buck converter versus a single-phase converter and the value a multiphase buck converter can provide when implemented.

Figure 1 shows a two-phase circuit. From this circuit's waveforms, shown in Figure 2, it is clear that the phases are interleaved. Interleaving reduces ripple currents at the input and output. It also reduces hot spots on a printed circuit board or a particular component. In effect, a two-phase buck converter reduces the RMS-current power dissipation in the FETs and inductors by half. Interleaving also reduces transitional losses.

Output-filter consideration

The output-filter requirements decrease in a multiphase implementation due to the reduced current in the power stage for each phase. For a 40-A, two-phase solution, an average current of only 20 A is delivered to each inductor. Compared to a 40-A single-phase approach, the inductance and inductor size are drastically reduced because of lower average current and lower saturation current.

Output ripple voltage

Ripple-current cancellation in the output-filter stage results in a reduced ripple voltage across the output capacitor compared to a single-phase converter. This is another reason why a multiphase converter is preferred. Equations 1 and 2 calculate the percentage of ripple current canceled in each inductor.

$$m = D \times \text{Phases} \tag{1}$$

and

$$I_{\text{Rip_norm}}(D) = \text{Phases} \times \frac{\left[D - \frac{m \cdot D}{\text{Phases}} \right] \times \left[\frac{1 + m \cdot D}{\text{Phases}} - D \right]}{(1 - D) \times D}, \tag{2}$$

Figure 1. Two-phase buck converter


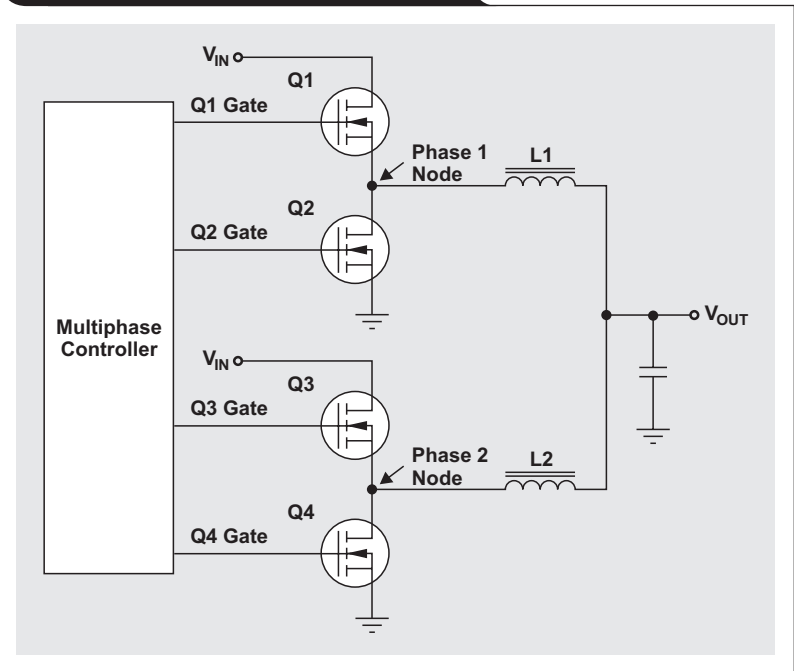


Figure 2. Node waveforms of phases 1 and 2

 


where D is the duty cycle, I_{Rip_norm} is the normalized ripple current as a function of D , and m_p is the integer of m . Figure 3 plots these equations. For example, using two phases at a 20% duty cycle (D) yields a 25% reduction in ripple current. The amount of ripple voltage the capacitor must tolerate is calculated by multiplying the ripple current by the capacitor's equivalent series resistance. Clearly, both maximum current and voltage requirements are reduced.

Figure 4 shows the simulation results for a two-phase buck converter at a duty cycle of 25%. The inductor ripple current is 2.2 A, but the output capacitor sees only 1.5 A due to ripple-current cancellation. With a duty cycle of 50% and two phases, the capacitor sees no ripple current at all.

Load-transient performance

Load-transient performance is improved due to the reduction of energy stored in each output inductor. The reduction in ripple voltage as a result of current cancellation contributes to minimal output-voltage overshoot and undershoot because many cycles will pass before the loop responds. The lower the ripple current is, the less the perturbation will be.

Figure 3. Normalized capacitor ripple current as a function of duty cycle

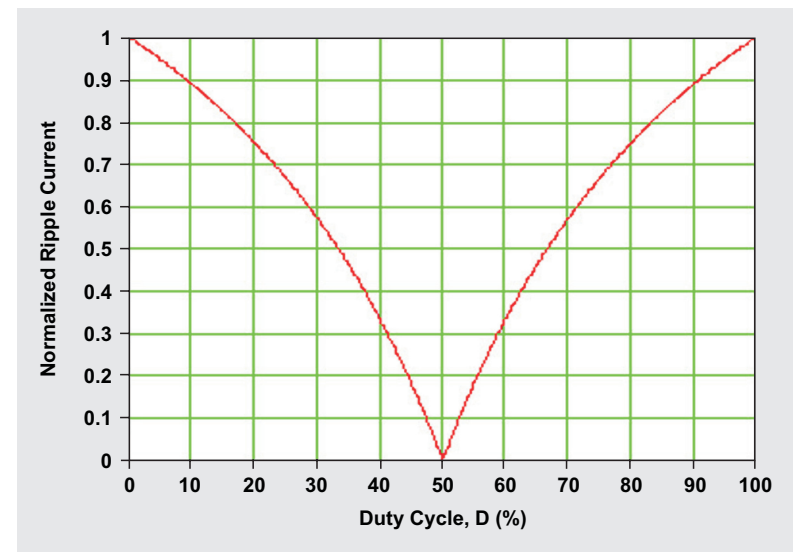

Cancellation of input RMS ripple current

The input capacitors supply all the input current to the buck converter if the input wire to the converter is inductive. These capacitors should be carefully selected to satisfy the RMS-ripple-current requirements to ensure that they

Figure 4. Cancellation of inductor ripple current with $D = 25\%$


 


Figure 5. Normalized input RMS ripple current as a function of duty cycle

 

do not overheat. It is well understood that, for a single-phase converter with a duty cycle of 50%, the worst-case input RMS ripple current is typically rated at 50% of the output current. Figure 5 and Equation 3 indicate that, for a two-phase solution, the worst-case RMS ripple current occurs at duty cycles of 25 and 75% and is only 25% of the output current.

$$I_{\text{Input_norm}}(D) = \sqrt{\left[D - \frac{mp(D)}{\text{Phases}} \right] \times \left[\frac{mp(D) + 1}{\text{Phases}} - D \right]} \quad (3)$$

The value of a multiphase solution as compared to a single-phase solution is clear. Less input capacitance can be used to satisfy the RMS-ripple-current demands of the buck stage.

Application example

The LM3754 high-power-density evaluation board delivers 1.2 V at 40 A from a 12-V input supply. The board is 2 × 2 inches, and the area covered by the components is 1.4 × 1.3 inches. The switching frequency of each phase is set to 300 kHz. Table 1 provides a summary of these and other operating conditions. The components are placed on a 4-layer board, with 1 oz. of copper on all layers. Additional pins are included on this board for remote sensing, and a pin is used for margining the output voltage.

Because the LM3754 evaluation board is designed to operate in high-power-density configurations, it utilizes the optimized input capacitors to provide the reduced RMS ripple current that is required. The evaluation board also has a low ripple voltage and good transient performance. The board layout shown in the LM3754 application note¹ should be followed as closely as possible. However, if this

Table 1. Operating conditions of LM3754 evaluation board

Input voltage	10.8 to 13.2 V
Output voltage	1.2 V ± 1%
Output current	40 A (max)
Switching frequency	300 kHz
Module size	2 × 2 inches
Circuit area	1.4 × 1.3 inches
Module height	0.5 inches
Air flow	200 LFM
Number of phases	2

is not possible, close attention should be paid to these considerations. Several more layout considerations will now be described, followed by the test results from a test board using the LM3754. These results are presented in Figures 6–11 on pages 12–13. They are typical of what one can expect to achieve or even improve upon in making the necessary modifications.

Layout considerations

High-current traces require enough copper to minimize voltage drops and temperature rises. The general rule of using a minimum of 7 mils per ampere was applied for the 2 oz. of copper used, and 14 mils per ampere for the inner layers for the 1 oz. of copper used. The input capacitors of each phase were placed as close as possible to the top MOSFET drain and the bottom MOSFET source to ensure minimal ground “bounce.”

Signal components connected to the IC

All small-signal components that connected to the IC were placed as close to it as possible. Decoupling capacitors for V_{REF} and V_{CC} were also placed as close as possible to the IC. The signal ground (SGND) was configured to ensure a low-impedance path from the ground of the signal components to the ground of the IC.

SGND and PGND connections

Good layout techniques include a dedicated ground plane; this board dedicated as much of inner-layer 2 as possible for the ground plane. Vias and signal lines were strategically placed to avoid high-impedance points that could pinch off wide copper areas. The power ground (PGND) and SGND were kept separate, only connected to each other at the ground plane (inner layer 2).

Gate drive

The designer should ensure that a differential pair of traces is connected from the high-gate output to the top MOSFET gate and the return, which is the switch node. The distance between the controller and the MOSFET should be as short as possible. The same procedure should be followed for the LG and GND pins when the traces for the low-side MOSFET are routed.

A differential pair of traces must also be routed from the CSM and CS2 pins to the RC network located across the output inductor. Notice in the layout in Reference 1 that, in order to provide additional noise suppression, the filter capacitor is split into two capacitors—one positioned by the inductor and the other close to the IC. These sense lines should not be run for long lengths in close proximity to the switch node. If possible, they should be shielded by using a ground plane.

Minimizing the switch node

To follow the common rules of keeping the switch-node area as small as possible but large enough to carry high currents, the switch node was built on multiple layers. Because the small evaluation board essentially folds back on itself from input to output, the switch node naturally sits on the outer layer, and the IC sits directly underneath the switch node. Therefore, it is essential to keep the switch node well away from the sense lines and also from the IC. Hence, the switch node was strategically placed facing outwards toward the edge of the board.

Conclusion

There are a number of benefits to using multiphase buck converters, such as higher efficiency from lower transitional losses; lower output ripple voltage; better transient performance; and lower ripple-current-rating requirements for the input capacitor. Some examples of multiphase buck converters that can deliver the full benefits described herein are the LM3754, LM5119, and LM25119 families.

Reference

1. Robert Sheehan and Michael Null, "LM3753/54 evaluation board," National Semiconductor Corp., Application Note 2021, Dec. 15, 2009 [Online]. Available: <http://www.national.com/an/AN/AN-2021.pdf>

Related Web sites

power.ti.com

www.ti.com/product/partnumber

Replace *partnumber* with LM3754, LM5119, or LM25119

Test results

Figure 6. Efficiency plot with 12-V input

 


Figure 7. Power loss with 12-V input

 


Figure 8. Switch-node voltages

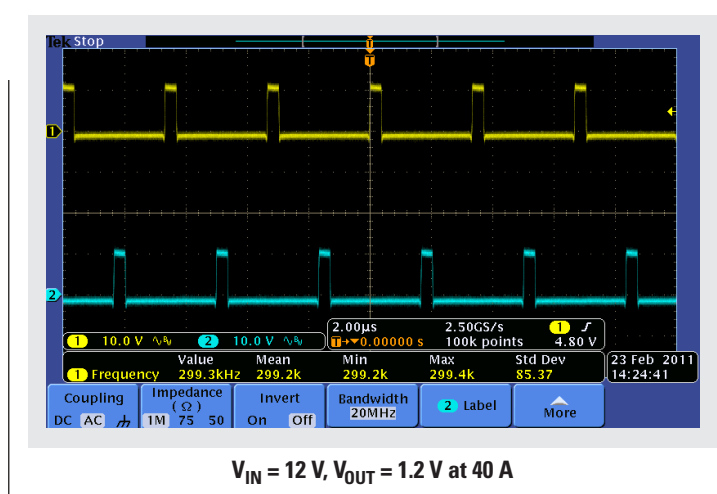


Figure 9. Output voltage ripple

 


Figure 10. Transient response: 20 µs with 10-A load step (undershoot/overshoot ~ 27 mV)


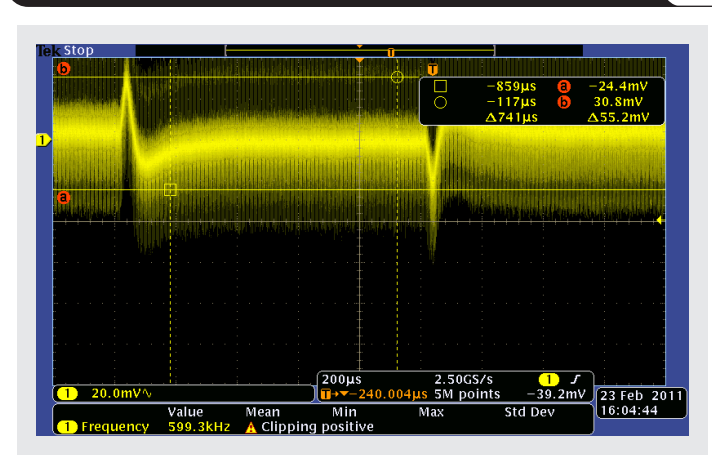


Figure 11. V_{OUT} start-up for 1.2-V output with 40-A load

 

Downslope compensation for buck converters when the duty cycle exceeds 50%

By John Bottrill

Senior Applications Engineer

Current-mode control (CMC) in a pulse-width-modulated (PWM) buck converter with a duty cycle greater than 50% has the potential of going into sub-harmonic oscillations. Lloyd H Dixon, Jr., discusses this in detail in Reference 1. According to Dixon, the solution is to add to the current-sensing signal a ramp that is equal to the downslope of the output inductor current. This additional voltage needs to be added into the required calculation in order to select the current-sensing resistor.


A push-pull converter, a phase-shifted full-bridge converter, or any forward converter with duty cycles greater than 50% at the output inductor are topologies that require this compensation. However, for demonstration purposes, the topology selected for this discussion is one that is relatively unknown: a three-switch forward converter. See a basic schematic of the power section in Figure 1. This topology, though patented by Texas Instruments (TI), is licensed to the public when a TI control IC is used in the circuit.

This topology has several advantages, particularly when the input-voltage range is that which is normally considered the telephone-battery range of 36 to 72 V. The topology limits the maximum duty cycle to 67%, which limits the design to a maximum duty cycle at a minimum input voltage of 67%. At the same time, the voltage on the main switches when they turn off is limited to the input voltage of the power rail. This means that low-voltage FETs can be used with their corresponding lower $R_{DS(on)}$ resistance. This topology also provides a means of recovering the magnetizing energy in the power transformer and in the primary-side leakage inductance, thereby removing the need for wasteful snubbers.

The converter design, in most other respects, is typical of any buck topology, with the exception that the duty cycle must be limited to 67% to avoid transformer saturation. This limit can be accomplished by selecting a control IC where the maximum duty cycle can be programmed, such as the UCC2807-1 (see Reference 2). Because this controller has the required duty-cycle-limiting feature, it is perfect for this application. Therefore, it was used in this study along with its characteristics for the analysis.

The following analysis assumes a theoretical switching supply with a 3.3-V output at 100 W. The supply has a maximum peak-to-peak ripple current through the output inductor equal to 10% of the maximum output DC load current of 30 A, and the input voltage is expected to be between 36 and 78 V. It is also assumed that synchronous rectifiers with a forward voltage drop, V_{fd} , of 0.5 V will be

Figure 1. Three-switch forward topology

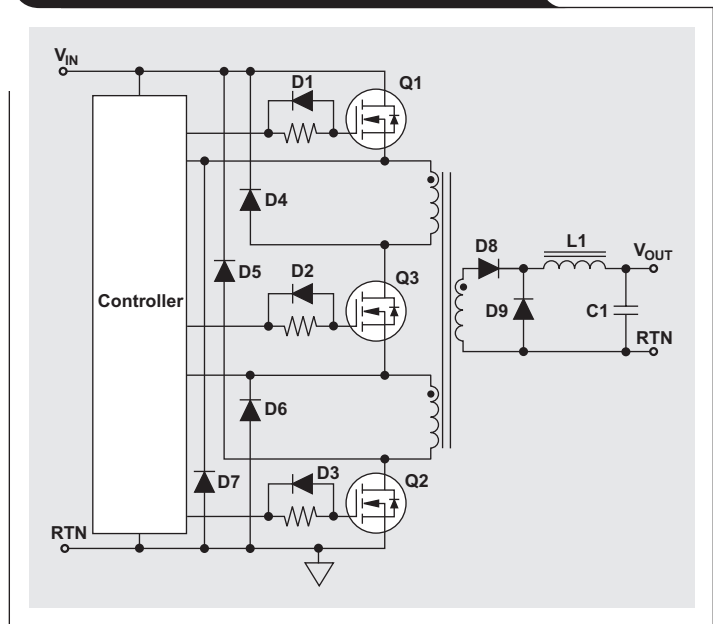

used for the output. The first step is to determine the turns ratio of the transformer. At the minimum input voltage, the duty cycle will be at the maximum limit (67%). The voltage needed at the output of the transformer can be determined by the equation

$$\frac{V_{OUT} + V_{fd}}{D_{max}} = \frac{3.3 \text{ V} + 0.5 \text{ V}}{0.67} = 5.672 \text{ V} \quad (1)$$

If 36 V across the transformer primary windings is assumed, the turns ratio (N_p) will be 6.147, so a primary with six turns will be used. The primary is divided into two sections of three turns each (see Figure 1). As is standard practice, the secondary is sandwiched between the two primary sections, and Q3 is placed between the two primary sections. With the input at 78 V, the transformer output voltage is 12.3 V, which will yield a minimum duty cycle, D_{min} , of about 31%. Therefore, the maximum OFF time equals

$$\frac{1 - D_{min}}{f_{sw}}$$

where f_{sw} is the planned switching frequency of 200 kHz. The minimum output inductance ($L1$ in Figure 1) to achieve the desired peak-to-peak ripple current of 10% is thus defined as

$$L_{OUT} = \frac{(V_{OUT} + V_{fd}) \times (1 - D_{min}) / f_{sw}}{I_{OUT} \times 0.1} \quad (2)$$

The output inductor in Equation 2 was determined to be 4.33 μH . For design purposes, 4.5 μH will be used. From this value, the current downslope, I_{ds} , of the output inductor can be calculated:

$$I_{ds} = \frac{V_{OUT} + V_{fd}}{L_{OUT}} \quad (3)$$

The inductor's downslope current (I_{ds}) is determined to be 0.844 A/ μs .

It can also be determined that the peak current through the output inductor at maximum input voltage is

$$I_{OUT} + 0.5 \times (I_{OUT} \times 0.1),$$

because the maximum peak-to-peak ripple current was defined as being 10% of the output current, and that current is balanced about the nominal DC output. The peak current that results is 31.884 A.

For the minimum input voltage, it is possible to determine the differential voltage across L_{OUT} . From that, the rate of change in the output inductor can be determined

to be 0.489 A/ μs . Knowing the duty cycle and frequency permits calculation of the time that the current is increasing in the output inductor, making it possible to determine the ripple current under these conditions. Finally, the peak current under the minimum input voltage is found to be 31.122 A. The waveforms are shown in Figure 2. These values are almost equal, but if the downslope is added, they change—and in a surprising way. The downslope current that must be added to the peak current for the maximum input voltage is

$$\frac{I_{ds} \times D_{min}}{f_{sw}} = 1.306 \text{ A},$$

and the downslope current that needs to be added to the peak current for the minimum input voltage is

$$\frac{I_{ds} \times D_{max}}{f_{sw}} = 2.829 \text{ A}.$$

See Figure 3, where the effective downslope current is added to the currents shown in Figure 2. The result is that

Figure 2. Output inductor ripple at maximum load for $V_{IN(min)}$ and $V_{IN(max)}$

 


Figure 3. Secondary currents plus effective downslope current


 


Figure 4. Circuit used to generate the desired current through R_{dsPRI}

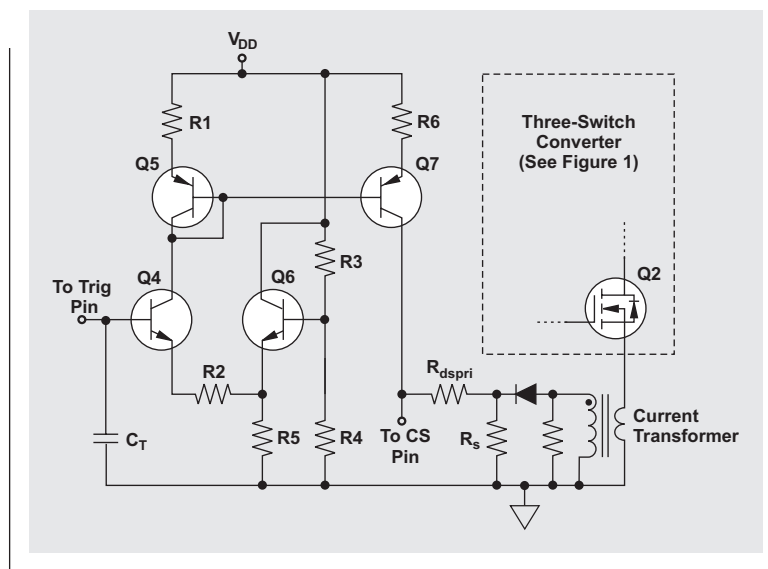

the effective peak current for the minimum input voltage is higher than the effective peak current for the maximum input voltage, even though the real peaks were the reverse. The effective maximum current, including downslope at the minimum input voltage, has a peak of 33.9 A, which is the value that must be used to set the current-sensing resistor, R_s . This current, including the downslope current translated to the primary, is 5.658 A.

The IC chosen as the controller has a typical current-trip level of 1.0 V, but the tolerance is between 0.9 and 1.1 V. To make certain that all units can provide the required power, the lower limit is used, and the value of R_s is set so that the voltage across it at 5.658 A will be 95% of the 0.9-V minimum. This gives a 5% safety margin for transients and sets R_s at 0.15 Ω . Of course, there will be about 5 W of power loss, which most likely would be replaced by a current transformer. With a 100:1 transformer, R_s would increase to 15 Ω . The remaining discussion assumes that such a transformer is used.

In reality, the downslope current (I_{ds}) does not go through either the current transformer or the power transformer, but the effect needs to be accounted for and added to the voltage on resistor R_s . To do this, a resistor R_{dsPRI} is added between resistor R_s and the IC's current-sensing pin. At the IC's current-sensing pin, a current ramp is injected into the circuit. This current ramp is such that the ramp voltage developed across resistor R_{dsPRI} between the IC's current-sensing pin and resistor R_s is equivalent to the voltage that would be developed across resistor R_s by the I_{ds} translated to the primary. It is assumed that an equivalent downslope current is flowing through resistor R_s , taking into account both the power-transformer and the current-transformer winding ratios. For this case,

resistor R_{dsPRI} is set at 1 k Ω for ease of calculation and because it is much larger than resistor R_s .

The next step is to determine the dv/dt required across R_{dsPRI} :

$$V_{dsPRI} = \frac{I_{ds} \times R_s}{N_p \times 100} = 21 \text{ V/ms} \quad (4)$$

From this result, the current ramp needed through the 1-k Ω resistor can be determined:

$$I_{dsPRI} = \frac{V_{dsPRI}}{R_{dsPRI}} = 21.1 \text{ } \mu\text{A}/\mu\text{s} \quad (5)$$

This current times the maximum ON time gives a peak current of 70.7 μA .

With a programmable, maximum-duty-cycle PWM controller like the UCC2807, it is relatively simple to set the maximum duty cycle to 67% by setting the two timing resistors to the same value, as shown in the datasheet. Also, the specification for the part states that the valley and peak voltages on the timing capacitor equal $\frac{1}{3} V_{CC}$ and $\frac{2}{3} V_{CC}$, respectively. This gives a voltage-ramp amplitude of $\frac{1}{3} V_{CC}$. With this information, a circuit can now be designed to generate a ramp current that can be injected into the current-sensing circuit to provide the current downslope to the current signal.

A circuit to generate the desired current is shown in Figure 4. This circuit is based on the UCC2807-1 control IC, with V_{DD} set at 11 V. The valley and peak voltages of the Trig ramp are 3.667 V minimum and 7.33 V maximum, and the time from minimum to maximum is equal to the maximum ON time. In this circuit, R3 is equal to twice R4. This sets the voltage at the base of Q6 equal to $\frac{1}{3} V_{CC}$,

which is the valley of the Trig voltage. As the voltage on the Trig pin swings from the valley to the peak ($\frac{2}{3} V_{CC}$), the voltage across R2 goes from 0 to $\frac{1}{3} V_{CC}$ in a linear manner. By choosing a value for R2 that gives a current of 70.7 μA with 3.667 V (51.8 k Ω) across it and then having the unity current mirror formed by Q5/R1 and Q7/R6, the designer can develop and add to the current-sensing signal the needed current with the correct shape and timing for the 1-k Ω resistor.

Conclusion

The three-switch forward converter offers unique advantages in energy recovery by returning the magnetizing energy and primary-side leakage energy to the source, preventing the need for snubbers and reducing the electromagnetic interference common with normal forward converters. It also offers the advantage over a two-switch forward topology of a duty cycle greater than 50%. This article has shown an example of the calculations necessary to determine the value of the current-sensing resistor and the impact of the downslope necessary for stability in a buck converter operating at a duty cycle greater than 50%. It has also shown a method of adding in the downslope in a converter.

References

For more information related to this article, you can download an Acrobat® Reader® file at www.ti.com/lit/litnumber and replace “*litnumber*” with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Lloyd H. Dixon, Jr., “Current-mode control of switching power supplies,” 1985 Texas Instruments Power Supply Design Seminar (SEM400)	SLUP075
2. “Programmable maximum duty cycle PWM controller,” UCC1807-x/2807-x/3807-x Datasheet	SLUS163

Related Web sites

power.ti.com

www.ti.com/product/UCC2807-1

High-efficiency AC adapters for USB charging

By Adnaan Lokhandwala

Product Manager

USB charging for electronic gadgets

Universal serial bus (USB) charging has become a common means for powering electronic gadgets. The AC power adapter/battery charger for many new consumer devices like smartphones, tablets, and e-readers is in the 5- to 25-W power range and presents a USB Standard-A receptacle. The adapter output voltage of 5 V has become the preferred choice for compatibility with PC/desktop-port charging and communication. The current dominant interface is via a standard (mini or Micro-B) USB cable or, in some cases, a nonstandard connector. With battery charging gaining consumer attention, the odd “wall wart” is transforming into a “cool,” light, sleek, green charger. Beyond meeting standard regulatory requirements, original equipment manufacturers are pushing the performance envelope on adapter efficiency and no-load power, which is also known as vampire power. For example, leading manufacturers of mobile-phone chargers have agreed to a five-star (<30 mW of no-load power) charger-rating system. This makes it easy for consumers to compare and choose the most energy-efficient chargers.

Recently, there has been much talk about standardizing the input to mobile phones and creating a universal charger to charge any cell phone. In 2006, China issued a new regulation aimed at standardizing the wall charger and its connecting cable. Similarly, the GSM Association (GSMA) is now leading the Universal Charging Solution adapter initiative for powering mobile phones with a micro USB connector. The common charger is required to provide 5 V \pm 5%, a minimum of 850 mA, and <150 mW of no-load


power. It must also comply with the USB Implementers Forum (USB-IF) Battery Charging Specification 1.1 (BC1.1).^{*} Besides providing ease of use for consumers, the standardized charger could potentially eliminate a multitude of duplicate chargers. Additionally, AC adapters with multiple USB outlets offer consumers the convenience of charging multiple devices without the need for a dedicated charger for each gadget. Chargers with higher output current also allow the possibility of fast battery charging, a key advantage over standard USB 2.0 ports that are limited to 500 mA. The increasing demand for these improvements, along with the continued push towards adapter designs with a smaller form factor, makes thermal management in this “black box” a huge challenge for power-supply designers.

Power-supply architecture

For the power levels under consideration here, the flyback topology shown in Figure 1 is the preferred choice today due to its simplicity and low cost. The conduction loss on the secondary-side Schottky-diode rectifier (Figure 1a) becomes a limiting factor in achieving high-efficiency, compact adapter designs. For instance, in a typical 5-V/3-A adapter, the power loss in the diode rectifier alone at full load can be 30 to 40% of the total system losses (neglecting the compounding effect of secondary losses on increased primary-side losses). Implementing a synchronous rectifier (SR) for the output (Figure 1b) can increase the overall efficiency of the converter and, because much less heat is generated (fundamentally important in adapter designs), ease system thermal management.

^{*}USB-IF BC1.2 extends the charging-current range from 1.5 A to 5 A.

Figure 1. Simplified flyback topology

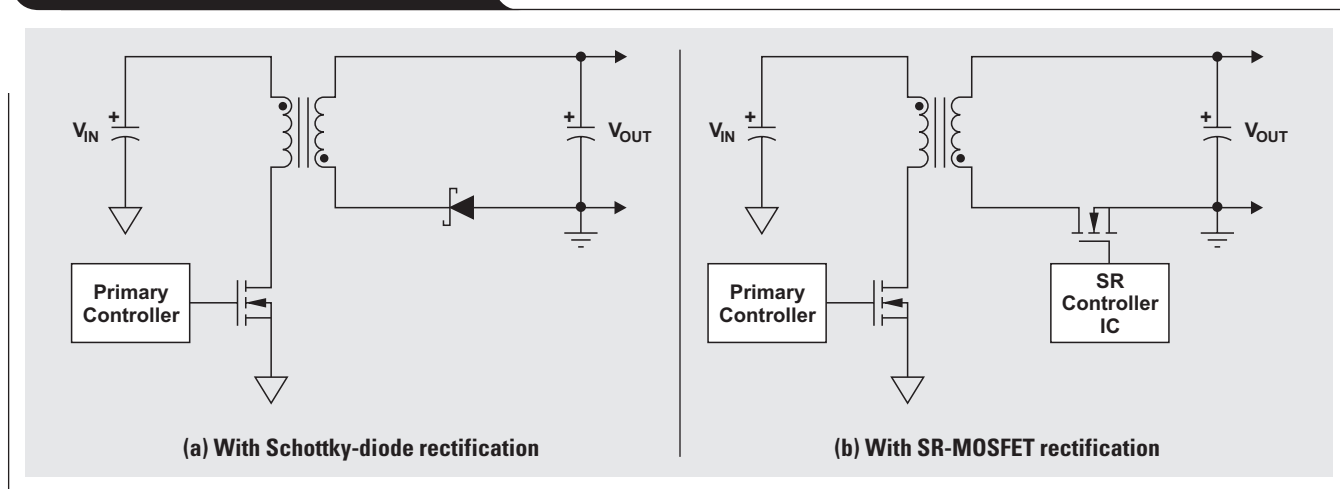

The conceptually simple change of adding an SR to the classic flyback topology can significantly reduce overall system power losses. The power level at which such a modification is practical has been decreasing with the rapid advancement in power MOSFET technology. Hence, synchronous rectification is now applicable to an ever-growing range of products. The lower power dissipation of an SR allows designers to take advantage of smaller components that have less heat sinking, thus increasing power density while lowering assembly costs, product size, and shipping weight.

Note that if the SR MOSFET is allowed to switch during no-load/standby conditions, the system power performance could be compromised. The SR-MOSFET switching losses, in addition to the quiescent power required by the SR controller IC, can be limiting factors in achieving the best possible system no-load performance.

Green output rectification: Full load to no load

This article will now discuss how an IC such as the Texas Instruments (TI) UCC24610 Green Rectifier™ controller can simplify USB charger designs and enable high system efficiency across the full load range. Simplified system waveforms for a flyback converter with and without synchronous rectification are shown in Figure 2. The waveforms are the results of a control scheme that directly senses the MOSFET drain-to-source voltage (V_{DS}). This control method is widely adopted today instead of other implementation choices such as primary-side synchronization or synchronous control from a secondary-side current transformer. Having the SR controller's turn-off threshold (V_{THOFF}) as close as possible to zero in this control scheme allows maximum conduction time in the MOSFET channel.

Flyback converters can be designed to operate in different modes depending on the end-application requirements. For designs operating in continuous-conduction mode (CCM), the current in the transformer secondary does not fall to zero before the primary-side MOSFET is turned on, which results in a period of cross-conduction. When synchronous rectification is implemented in such converters, it is imperative that the SR MOSFET be turned off as soon as the primary-side switch turns on. This prevents reverse conduction and limits additional power losses and device stresses. Instead of waiting for the V_{THOFF} threshold detection, the synchronizing function in the Green Rectifier detects the primary-side turn-on transition and turns off the SR MOSFET. Figure 3 illustrates how the SR-gate turn-off transition is now controlled by a synchronizing signal from the primary side and not by V_{DS} sensing.

Figure 2. Simplified flyback waveforms with Schottky-diode and SR-MOSFET output rectification


 


Figure 3. Typical CCM flyback waveforms with primary-side synchronization

 

As described earlier, implementing synchronous rectification could possibly compromise light-load efficiency and no-load power consumption. The major contributors to loss at light or no load are SR-MOSFET switching and SR controller-IC bias. The Green Rectifier overcomes these issues with (1) an automatic light-load-detection circuit that disables gate switching of the SR MOSFET when its conduction time falls below a certain threshold, and (2) an EN function to put the IC in sleep mode and disable

quiescent power loss. The light-load-detection circuit compares the SR conduction time and the programmed minimum ON time (MOT) for every switching cycle. When the load decreases, the secondary conduction time becomes shorter than the MOT, and the next SR gate pulse is disabled. Further reduction in no-load power can be achieved by using the EN function of the controller IC. A simple averaging circuit on the MOSFET drain voltage can be used to put the IC in sleep mode at a no-load condition that limits the IC's bias-current consumption to 100 μ A. An additional 10 mW of no-load power consumption can be saved with this approach. The last gasp in improving no-load performance is to add a low-current Schottky diode in parallel with the SR MOSFET.

As an example, a USB charger with a 3-A current rating was designed using two controller chipsets, TI's UCC28610 and UCC24610, for a tablet-PC end application. The reference design for this charger, the PMP4305, can be seen at the Web site listed at the end of this article. The UCC24610 is good for applications with a 5-V flyback switch-mode power supply and can operate within the specified USB voltage range of 4.75 to 5.25 V. Hence, this SR controller was biased directly from the converter output, eliminating the need for an auxiliary winding on the main power transformer. The controller also allowed external programming of two blanking timers to prevent SR false triggering from V_{DS} ringing sensed during the turn-on and turn-off transitions. Figure 4 shows typical power-stage waveforms of the PMP4305 at full load. The IC control scheme was not affected by the severe ringing on the V_{DS} signal at turn-on because the programmable MOT timer disabled the V_{THOFF} comparator during this period.

A comparison of the efficiency of SR-MOSFET versus Schottky-diode output rectification at 115- and 230-V AC line conditions is shown in Figure 5. Implementing synchronous rectification enables over 80% efficiency from full load down to about 25% of full load. Additionally, for this load range, an SR configuration can achieve a three- to five-point improvement in efficiency over Schottky-diode rectification.

Conclusion

USB power charging for consumer devices is gaining traction. A universal standard for 10- to 25-W chargers with USB outlets that power multiple devices eliminates the need for a new wall charger with every new gadget purchase. High-efficiency AC/DC converters are needed to satisfy the push towards high-density, small-form-factor adapters. Devices like the UCC24610 Green Rectifier can help improve AC/DC converter efficiency and enable the high-density USB-charger designs.

Figure 4. Full-load waveforms from PMP4305


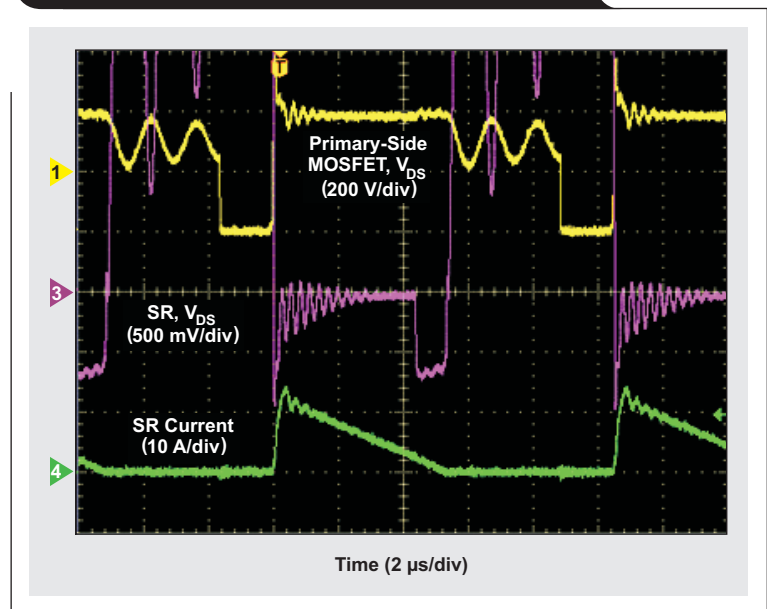


Figure 5. Comparison of system efficiency with Schottky diode versus synchronous rectifier (SR)

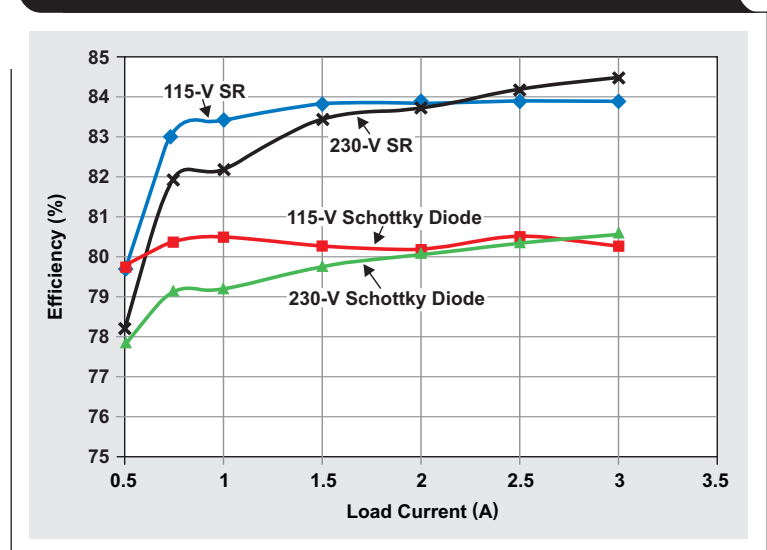

Related Web sites

power.ti.com
www.ti.com/product/UCC24610
www.ti.com/product/UCC28610

Reference design for tablet-PC charger:
www.ti.com/tool/PMP4305

Measuring op amp settling time by using sample-and-hold technique

By Roger Liang, *Systems Engineer*,
and Xavier Ramus, *System Engineer, High-Speed Amplifiers*

Introduction

Modern high-speed operational amplifiers (op amps) are designed with settling time in the range of nanoseconds. This time is so brief that measuring it within a reasonable error band presents a challenging task not only on automatic test equipment (ATE) but also on the bench. In today's op amp datasheets, settling time is usually given as a simulated value due to the cost and challenges associated with implementing additional hardware to test it on the bench. Traditional high-speed oscilloscopes have only a 10-bit analog-to-digital converter, which limits any measurement resolution to a maximum of 0.1%.

This article describes a new methodology that has proven to be effective in making these measurements. Detailed is a relatively inexpensive and simple way to measure settling time that bases accuracy and precision on the relative speed of the waveform generator and the sample-and-hold circuit.

Step input for the device under test


In this article, settling time refers to the time that elapses from the application of an ideal step input to the time at which the device under test (DUT) enters and remains within a specified error band that is symmetrical about the final value. An ideal step input is easily generated in simulation, but there are no instruments that can produce an ideal step waveform in any lab setting. Even under ideal conditions, the output of overdamped and critically damped instruments would take a few RC time constants to monotonically settle to within tenths of a percent of the final value.

For underdamped systems, a step waveform can overshoot the final value, and ringing may occur. In practice, even critically damped systems have underdamped behaviors. Generally, the faster the fall time of the step waveform, the more overshoot and ringing one observes. This non-ideality is then propagated into the measured output waveform of the DUT. Fortunately, with the aid of computer-logged records of input and output data, the output can be normalized by lining up the two and subtracting the input from the output (with the DUT in a non-inverting unity-gain configuration).

Flat-bottom pulse generator

When the falling edge of a waveform generator is used as the input to the DUT, a flat-bottom pulse generator (FBPG)

Figure 1. Flat-bottom pulse generator (FBPG)

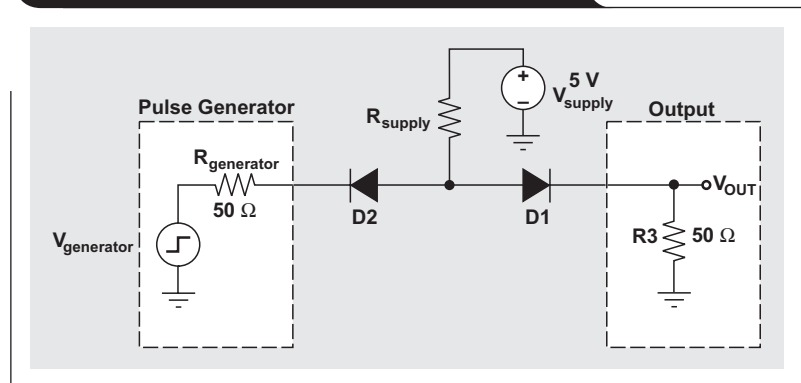

can be used to clean up the low-voltage level of the generated signal. The FBPG clamps the falling voltage to ground at the cost of a bigger overshoot. This gives test engineers some control over trade-offs in the test setup. Similarly, a flat-top pulse generator can be used to clean up the high-voltage level.

Figure 1 illustrates two back-to-back high-speed Zener diodes, each with a separate, adjustable power supply. As a rule of thumb, the setup should be started as follows: The R_{supply} should be adjusted to obtain 5 V at the D1/D2 connection, and the $V_{\text{generator}}$ output voltage should be adjusted to swing between a 2-V high and a -5-V low. This should bias the output at $2 V_{\text{PP}}$ and the low-voltage level at 0 V. When $V_{\text{generator}}$ is high, D2 is turned off and D1 is turned on. During this time, the output voltage becomes a function of D1's forward voltage (V_{supply}) and of the amount of current that flows through R_{supply} and D1. When the input is low, D1 is turned off and D2 is turned on. During this time, the output voltage swings to ground, and its slew rate is proportional to the amount of current that flows into the matching resistor, R3. The transient response is a function of the diode's capacitance, reverse recovery time, and forward recovery voltage.

Because of the diodes' nonlinearity, it does not make sense to derive rigorous equations to determine the DC levels and transient response of the FBPG. Instead, the equations can be simulated in software such as TINA-TI™ from Texas Instruments. Assuming that the pulse generator is very fast, the fall time and overshoot of the output waveform become functions of the diodes' speed and recovery time, as well as of the parasitic capacitance and inductance of the printed circuit board (PCB) on which the FBPG is built. In other words, the designer should pick the fastest, most robust diode and follow guidelines for


good PCB layout when using FBPG for generating high-speed waveforms.

Sample-and-hold methodology for measuring settling time

For the example presented here, the TI OPA615 (see Figure 2) was chosen to implement the sample-and-hold (S/H) functions of its wide-band operational transconductance amplifier (OTA), which is optimized for low input-bias current, and its fast and precise sampling OTA (SOTA), which also serves as a comparator and buffer. The analog input (V_{IN}) is sampled by the SOTA onto the capacitor (C_{HOLD}) when the Hold-Control pin is high. The voltage on C_{HOLD} is held and reflected at the output (V_{OUT}) when the Hold-Control pin swings low. During sampling, the voltage on C_{HOLD} is adjusted to the real-time voltage level on the input. If there is a large voltage difference between the input and C_{HOLD} and there are only a few nanoseconds of sampling time, then fast slewing is required. During holding, the voltage on C_{HOLD} invariably charges/discharges due to its leakage current and any biasing current needed for the OTA. The current-feedback loop ensures that the SOTA slews fast enough to capture the correct voltage level at V_{IN} .

Figure 3 shows an example of a S/H output of a 100-kHz sine-wave input. A waveform generator can be used to produce the input step function for the DUT and to synchronize a S/H signal to that step function. A S/H circuit can be used to capture points on the DUT's output waveform. Any

Figure 2. Sample-and-hold (S/H) circuit

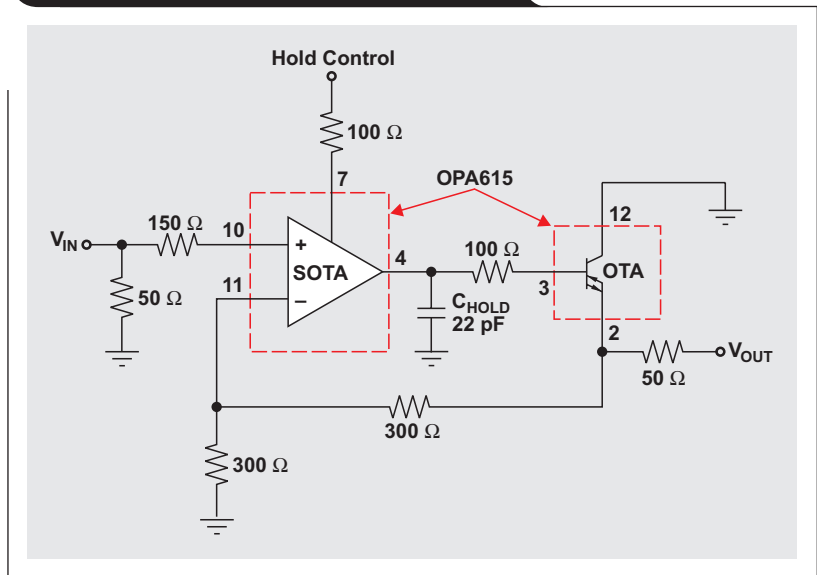

arbitrary waveform generator should work if it has a marker output that synchronizes with the output, thus creating a very convenient Hold-Control signal. The example test used a Tektronix AWG610, which has a sampling time of 2.6 Gbps and a minimum marker step of 100 ps, making it fast enough for most measurements of high-speed op amp settling time.

Figure 4 shows how to capture points on a curve by using a S/H circuit with the marker as the Hold-Control signal. The designer can capture sequential points on the curve by moving the marker position. After all the points

Figure 3. Example 1-MHz S/H output of a 100-kHz sine wave


 


Figure 4. Example of AWG610 output and marker synchronization

 

have been recorded, the S/H curve can be plotted and analyzed. Programming the waveform generator with software like MATLAB® or LabVIEW™ makes changing the marker and recording the results very simple. With the marker set in position 1, the S/H circuit tracks the V_{IN} voltage level when the marker is high and holds that value when the marker is low. At position 1, the output is held at 1 V. At position 2, the output is held at 0.2 V.

Figure 5 shows the test setup for measuring settling time where the AWG610 and OPA615 were used for the S/H functions. All signal lines were matched at 50 Ω . The output of the waveform generator was used as the test signal with two S/H circuits: One measured the input of the DUT (OPA656), and the other measured the DUT output. Digital multimeters (DMMs) were used to record the held values.

As an example of this method, take measuring a settling time of up to 100 ns. Assume that the waveform generator is programmed to continually output a square wave with a duty cycle of 50% and a period of 200 ns. The marker is initially set at the beginning of the falling edge of the waveform generator's output. The generator runs continually (executes many cycles of sampling and holding), and the S/H circuit integrates its output voltage to a steady DC value. This value is then recorded by the DMM, and the test engineer moves the marker to the next position, repeating this cycle until data for 100 ns has been recorded.

Figure 6 shows the plotted waveforms that resulted when the test setup in Figure 5 was used. To obtain a settling-time error waveform, the DC error was offset, and the output was normalized to the input. The result is shown in Figure 7.

Limitations and challenges

There are some limitations to the setup described here that should be kept in mind. When in doubt, the designer should always use the following equation:

$$I = C_{\text{HOLD}} \times dv/dt$$

For this equation, the size of the initial C_{HOLD} should be chosen based on three factors:

1. During the holding time, the OTA biasing current will flow in or out of the capacitor, thus affecting the accuracy of the voltage held.
2. Since a voltage droop will occur on the capacitor due to the biasing current, a delta voltage should be chosen based on the percentage of error within which the measurement should stay.
3. Delta time is the duration for which the sampled voltage is held and should be no longer than the planned settling time to be measured.

For example, C_{HOLD} should be no less than 50 pF under the following conditions: The biasing current of the OTA is 0.5 μA ; an error of less than 0.1% of a 1- V_{PP} signal is to be achieved; and the duration to be measured is 100 ns.

Figure 5. Test setup for measuring settling time

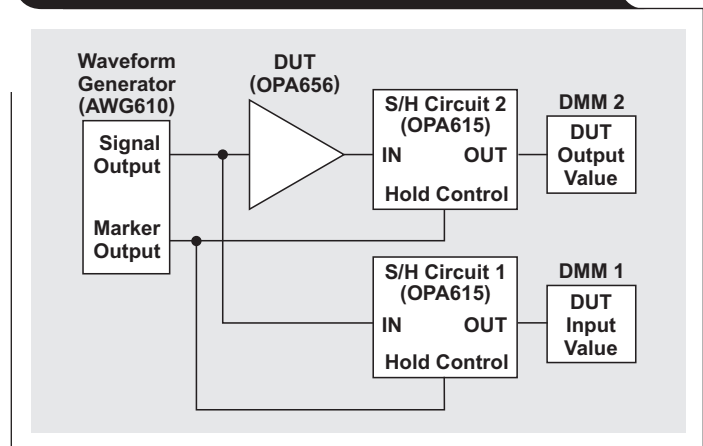


Figure 6. Step waveforms of op amp's input and output

 


Figure 7. Op amp's normalized settling error


 


Figure 8. Charge leakage on sampling capacitor

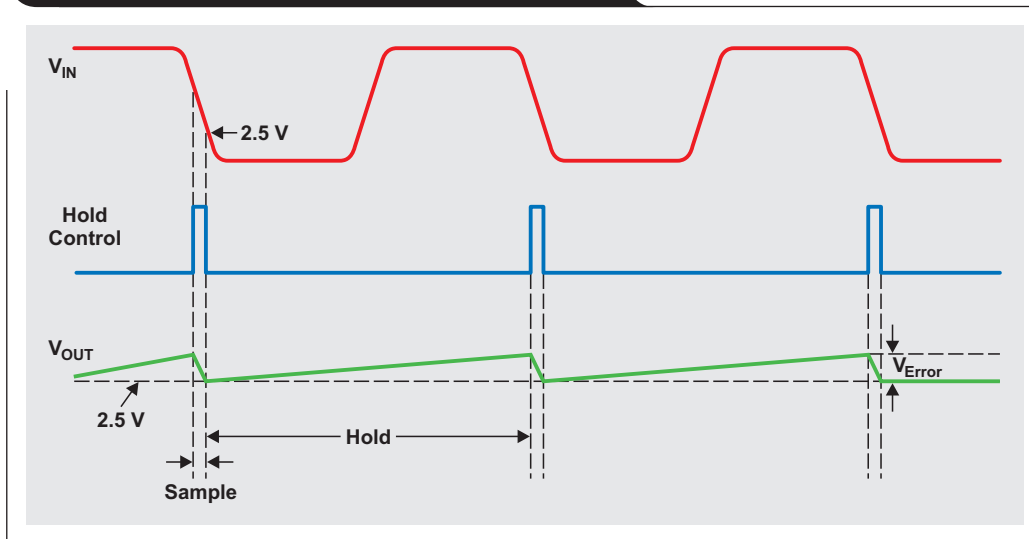

Other considerations

The duration of the sampling time could greatly affect the result of the measurement. During holding, the voltage on the sampling capacitor invariably strays from the supposed DC value because the OTA demands a biasing current. This voltage is then readjusted back to the expected DC value during sampling. The DMM that is reading the output of the S/H circuit is thus essentially taking an average value of this triangle waveform. This phenomenon is shown in Figure 8. To reduce this error, the holding time should be minimized and the capacitor size maximized. It should be kept in mind that the bigger the sampling capacitor is, the more S/H cycles (integration time) will be needed for the charges to integrate to a steady DC value.

Of course, increasing the sampling time does not mitigate the leakage problem. A minimum sampling time should be used that still guarantees the SOTA's holding-time delay and ensures enough time for the sampling capacitor's charge/discharge while it is tracking the S/H circuit's input. Figure 9 shows the recorded values of the op amp's settling time when different sampling times were used with the same holding and integration times. The results were measured against the same waveform taken from a 6-GHz, 10-bit oscilloscope, which showed a maximum overshoot of -60 mV. The measurement using a 20-ns sampling time matched that from the oscilloscope, but at the cost of applying a significant filter over the result. Conversely, the measurement using 6 ns applied a smaller filter but produced a bigger overshoot, which is an artifact of the measurement.


Conclusion

Numerous techniques exist for measuring settling time. This article has introduced a simple yet accurate technique that uses a relatively fast waveform generator and a S/H circuit. Knowing the limitations of this method, the user should be able to adjust any measurement parameters necessary to obtain the best results for a given settling-time range and expected accuracy.

Related Web sites

- amplifier.ti.com
- www.ti.com/product/OPA615
- www.ti.com/product/OPA656
- www.ti.com/tinati-ca

Figure 9. Settling time measured with different sampling times

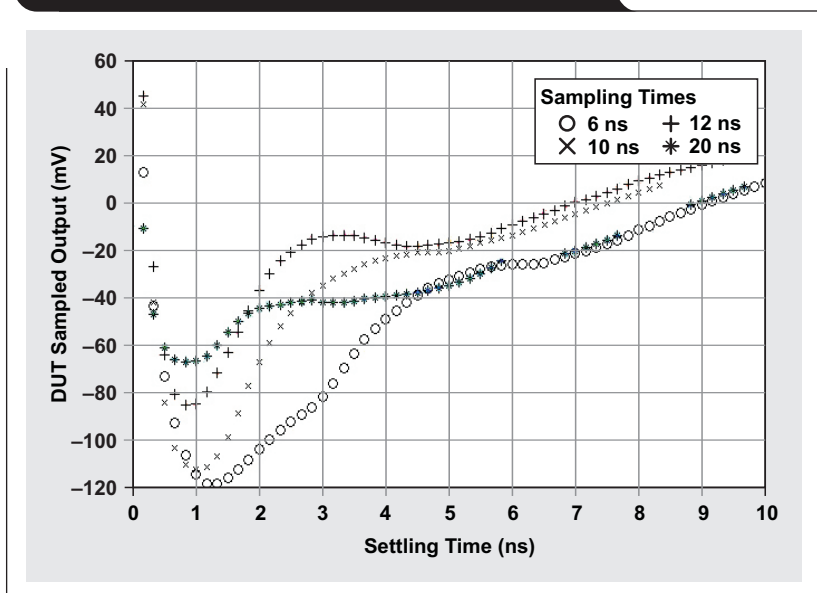

Index of Articles

Title	Issue	Page	Lit. No.
Data Acquisition			
Aspects of data acquisition system design	August 1999	1	SLYT191
Low-power data acquisition sub-system using the TI TLV1572	August 1999	4	SLYT192
Evaluating operational amplifiers as input amplifiers for A-to-D converters	August 1999	7	SLYT193
Precision voltage references	November 1999	1	SLYT183
Techniques for sampling high-speed graphics with lower-speed A/D converters	November 1999	5	SLYT184
A methodology of interfacing serial A-to-D converters to DSPs	February 2000	1	SLYT175
The operation of the SAR-ADC based on charge redistribution	February 2000	10	SLYT176
The design and performance of a precision voltage reference circuit for 14-bit and 16-bit A-to-D and D-to-A converters	May 2000	1	SLYT168
Introduction to phase-locked loop system modeling	May 2000	5	SLYT169
New DSP development environment includes data converter plug-ins	August 2000	1	SLYT158
Higher data throughput for DSP analog-to-digital converters	August 2000	5	SLYT159
Efficiently interfacing serial data converters to high-speed DSPs	August 2000	10	SLYT160
Smallest DSP-compatible ADC provides simplest DSP interface	November 2000	1	SLYT148
Hardware auto-identification and software auto-configuration for the TLV320AIC10 DSP Codec — a “plug-and-play” algorithm	November 2000	8	SLYT149
Using quad and octal ADCs in SPI mode	November 2000	15	SLYT150
Building a simple data acquisition system using the TMS320C31 DSP	February 2001	1	SLYT136
Using SPI synchronous communication with data converters — interfacing the MSP430F149 and TLV5616	February 2001	7	SLYT137
A/D and D/A conversion of PC graphics and component video signals, Part 1: Hardware	February 2001	11	SLYT138
A/D and D/A conversion of PC graphics and component video signals, Part 2: Software and control	July 2001	5	SLYT129
Intelligent sensor system maximizes battery life: Interfacing the MSP430F123 Flash MCU, ADS7822, and TPS60311	1Q, 2002	5	SLYT123
SHDSL AFE1230 application	2Q, 2002	5	SLYT114
Synchronizing non-FIFO variations of the THS1206	2Q, 2002	12	SLYT115
Adjusting the A/D voltage reference to provide gain	3Q, 2002	5	SLYT109
MSC1210 debugging strategies for high-precision smart sensors	3Q, 2002	7	SLYT110
Using direct data transfer to maximize data acquisition throughput	3Q, 2002	14	SLYT111
Interfacing op amps and analog-to-digital converters	4Q, 2002	5	SLYT104
ADS82x ADC with non-uniform sampling clock	4Q, 2003	5	SLYT089
Calculating noise figure and third-order intercept in ADCs	4Q, 2003	11	SLYT090
Evaluation criteria for ADSL analog front end	4Q, 2003	16	SLYT091
Two-channel, 500-kSPS operation of the ADS8361	1Q, 2004	5	SLYT082
ADS809 analog-to-digital converter with large input pulse signal	1Q, 2004	8	SLYT083
Streamlining the mixed-signal path with the signal-chain-on-chip MSP430F169	3Q, 2004	5	SLYT078
Supply voltage measurement and ADC PSRR improvement in MSC12xx devices	1Q, 2005	5	SLYT073
14-bit, 125-MSPS ADS5500 evaluation	1Q, 2005	13	SLYT074
Clocking high-speed data converters	1Q, 2005	20	SLYT075
Implementation of 12-bit delta-sigma DAC with MSC12xx controller	1Q, 2005	27	SLYT076
Using resistive touch screens for human/machine interface	3Q, 2005	5	SLYT209A
Simple DSP interface for ADS784x/834x ADCs	3Q, 2005	10	SLYT210
Operating multiple oversampling data converters	4Q, 2005	5	SLYT222
Low-power, high-intercept interface to the ADS5424 14-bit, 105-MSPS converter for undersampling applications	4Q, 2005	10	SLYT223
Understanding and comparing datasheets for high-speed ADCs	1Q, 2006	5	SLYT231
Matching the noise performance of the operational amplifier to the ADC	2Q, 2006	5	SLYT237
Using the ADS8361 with the MSP430™ USI port	3Q, 2006	5	SLYT244
Clamp function of high-speed ADC THS1041	4Q, 2006	5	SLYT253
Conversion latency in delta-sigma converters	2Q, 2007	5	SLYT264
Calibration in touch-screen systems	3Q, 2007	5	SLYT277
Using a touch-screen controller's auxiliary inputs	4Q, 2007	5	SLYT283

Title	Issue	Page	Lit. No.
Data Acquisition (Continued)			
Understanding the pen-interrupt (PENIRQ) operation of touch-screen controllers	2Q, 2008	5	SLYT292
A DAC for all precision occasions	3Q, 2008	5	SLYT300
Stop-band limitations of the Sallen-Key low-pass filter	4Q, 2008	5	SLYT306
How the voltage reference affects ADC performance, Part 1	2Q, 2009	5	SLYT331
Impact of sampling-clock spurs on ADC performance	3Q, 2009	5	SLYT338
How the voltage reference affects ADC performance, Part 2	3Q, 2009	13	SLYT339
How the voltage reference affects ADC performance, Part 3	4Q, 2009	5	SLYT355
How digital filters affect analog audio-signal levels	2Q, 2010	5	SLYT375
Clock jitter analyzed in the time domain, Part 1	3Q, 2010	5	SLYT379
Clock jitter analyzed in the time domain, Part 2	4Q, 2010	5	SLYT389
The IBIS model: A conduit into signal-integrity analysis, Part 1	4Q, 2010	11	SLYT390
The IBIS model, Part 2: Determining the total quality of an IBIS model	1Q, 2011	5	SLYT400
The IBIS model, Part 3: Using IBIS models to investigate signal-integrity issues	2Q, 2011	5	SLYT413
Clock jitter analyzed in the time domain, Part 3	3Q, 2011	5	SLYT422
How delta-sigma ADCs work, Part 1	3Q, 2011	13	SLYT423
How delta-sigma ADCs work, Part 2	4Q, 2011	5	SLYT438
Power Management			
Stability analysis of low-dropout linear regulators with a PMOS pass element	August 1999	10	SLYT194
Extended output voltage adjustment (0 V to 3.5 V) using the TI TPS5210	August 1999	13	SLYT195
Migrating from the TI TL770x to the TI TLC770x	August 1999	14	SLYT196
TI TPS5602 for powering TI's DSP	November 1999	8	SLYT185
Synchronous buck regulator design using the TI TPS5211 high-frequency hysteretic controller	November 1999	10	SLYT186
Understanding the stable range of equivalent series resistance of an LDO regulator	November 1999	14	SLYT187
Power supply solutions for TI DSPs using synchronous buck converters	February 2000	12	SLYT177
Powering Celeron-type microprocessors using TI's TPS5210 and TPS5211 controllers	February 2000	20	SLYT178
Simple design of an ultra-low-ripple DC/DC boost converter with TPS60100 charge pump	May 2000	11	SLYT170
Low-cost, minimum-size solution for powering future-generation Celeron™-type processors with peak currents up to 26 A	May 2000	14	SLYT171
Advantages of using PMOS-type low-dropout linear regulators in battery applications	August 2000	16	SLYT161
Optimal output filter design for microprocessor or DSP power supply	August 2000	22	SLYT162
Understanding the load-transient response of LDOs	November 2000	19	SLYT151
Comparison of different power supplies for portable DSP solutions working from a single-cell battery	November 2000	24	SLYT152
Optimal design for an interleaved synchronous buck converter under high-slew-rate, load-current transient conditions	February 2001	15	SLYT139
–48-V/+48-V hot-swap applications	February 2001	20	SLYT140
Power supply solution for DDR bus termination	July 2001	9	SLYT130
Runtime power control for DSPs using the TPS62000 buck converter	July 2001	15	SLYT131
Power control design key to realizing InfiniBand SM benefits	1Q, 2002	10	SLYT124
Comparing magnetic and piezoelectric transformer approaches in CCFL applications	1Q, 2002	12	SLYT125
Why use a wall adapter for ac input power?	1Q, 2002	18	SLYT126
SWIFT™ Designer power supply design program	2Q, 2002	15	SLYT116
Optimizing the switching frequency of ADSL power supplies	2Q, 2002	23	SLYT117
Powering electronics from the USB port	2Q, 2002	28	SLYT118
Using the UCC3580-1 controller for highly efficient 3.3-V/100-W isolated supply design	4Q, 2002	8	SLYT105
Power conservation options with dynamic voltage scaling in portable DSP designs	4Q, 2002	12	SLYT106
Understanding piezoelectric transformers in CCFL backlight applications	4Q, 2002	18	SLYT107
Load-sharing techniques: Paralleling power modules with overcurrent protection	1Q, 2003	5	SLYT100
Using the TPS61042 white-light LED driver as a boost converter	1Q, 2003	7	SLYT101
Auto-Track™ voltage sequencing simplifies simultaneous power-up and power-down	3Q, 2003	5	SLYT095
Soft-start circuits for LDO linear regulators	3Q, 2003	10	SLYT096
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1	3Q, 2003	13	SLYT097
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 2	4Q, 2003	21	SLYT092
LED-driver considerations	1Q, 2004	14	SLYT084
Tips for successful power-up of today's high-performance FPGAs	3Q, 2004	11	SLYT079

Title	Issue	Page	Lit. No.
Power Management (Continued)			
A better bootstrap/bias supply circuit	1Q, 2005	33	SLYT077
Understanding noise in linear regulators	2Q, 2005	5	SLYT201
Understanding power supply ripple rejection in linear regulators	2Q, 2005	8	SLYT202
Miniature solutions for voltage isolation	3Q, 2005	13	SLYT211
New power modules improve surface-mount manufacturability	3Q, 2005	18	SLYT212
Li-ion switching charger integrates power FETs	4Q, 2005	19	SLYT224
TLC5940 dot correction compensates for variations in LED brightness	4Q, 2005	21	SLYT225
Powering today's multi-rail FPGAs and DSPs, Part 1	1Q, 2006	9	SLYT232
TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)	1Q, 2006	14	SLYT233
Practical considerations when designing a power supply with the TPS6211x	1Q, 2006	17	SLYT234
TLC5940 PWM dimming provides superior color quality in LED video displays	2Q, 2006	10	SLYT238
Wide-input dc/dc modules offer maximum design flexibility	2Q, 2006	13	SLYT239
Powering today's multi-rail FPGAs and DSPs, Part 2	2Q, 2006	18	SLYT240
TPS61059 powers white-light LED as photoflash or movie light	3Q, 2006	8	SLYT245
TPS65552A powers portable photoflash	3Q, 2006	10	SLYT246
Single-chip bq2403x power-path manager charges battery while powering system	3Q, 2006	12	SLYT247
Complete battery-pack design for one- or two-cell portable applications	3Q, 2006	14	SLYT248
A 3-A, 1.2-V _{OUT} linear regulator with 80% efficiency and P _{LOST} < 1 W	4Q, 2006	10	SLYT254
bq25012 single-chip, Li-ion charger and dc/dc converter for <i>Bluetooth</i> ® headsets	4Q, 2006	13	SLYT255
Fully integrated TPS6300x buck-boost converter extends Li-ion battery life	4Q, 2006	15	SLYT256
Selecting the correct IC for power-supply applications	1Q, 2007	5	SLYT259
LDO white-LED driver TPS7510x provides incredibly small solution size	1Q, 2007	9	SLYT260
Power management for processor core voltage requirements	1Q, 2007	11	SLYT261
Enhanced-safety, linear Li-ion battery charger with thermal regulation and input overvoltage protection	2Q, 2007	8	SLYT269
Current balancing in four-pair, high-power PoE applications	2Q, 2007	11	SLYT270
Power-management solutions for telecom systems improve performance, cost, and size	3Q, 2007	10	SLYT278
TPS6108x: A boost converter with extreme versatility	3Q, 2007	14	SLYT279
Get low-noise, low-ripple, high-PSRR power with the TPS717xx	3Q, 2007	17	SLYT280
Simultaneous power-down sequencing with the TPS74x01 family of linear regulators	3Q, 2007	20	SLYT281
Driving a WLED does not always require 4 V	4Q, 2007	9	SLYT284
Host-side gas-gauge-system design considerations for single-cell handheld applications	4Q, 2007	12	SLYT285
Using a buck converter in an inverting buck-boost topology	4Q, 2007	16	SLYT286
Understanding output voltage limitations of DC/DC buck converters	2Q, 2008	11	SLYT293
Battery-charger front-end IC improves charging-system safety	2Q, 2008	14	SLYT294
New current-mode PWM controllers support boost, flyback, SEPIC, and LED-driver applications	3Q, 2008	9	SLYT302
Getting the most battery life from portable systems	4Q, 2008	8	SLYT307
Compensating and measuring the control loop of a high-power LED driver	4Q, 2008	14	SLYT308
Designing DC/DC converters based on SEPIC topology	4Q, 2008	18	SLYT309
Paralleling power modules for high-current applications	1Q, 2009	5	SLYT320
Improving battery safety, charging, and fuel gauging in portable media applications	1Q, 2009	9	SLYT321
Cell balancing buys extra run time and battery life	1Q, 2009	14	SLYT322
Using a portable-power boost converter in an isolated flyback application	1Q, 2009	19	SLYT323
Taming linear-regulator inrush currents	2Q, 2009	9	SLYT332
Designing a linear Li-Ion battery charger with power-path control	2Q, 2009	12	SLYT333
Selecting the right charge-management solution	2Q, 2009	18	SLYT334
Reducing radiated EMI in WLED drivers	3Q, 2009	17	SLYT340
Using power solutions to extend battery life in MSP430™ applications	4Q, 2009	10	SLYT356
Designing a multichemistry battery charger	4Q, 2009	13	SLYT357
Efficiency of synchronous versus nonsynchronous buck converters	4Q, 2009	15	SLYT358
Fuel-gauging considerations in battery backup storage systems	1Q, 2010	5	SLYT364
Li-ion battery-charger solutions for JEITA compliance	1Q, 2010	8	SLYT365
Power-supply design for high-speed ADCs	1Q, 2010	12	SLYT366
Discrete design of a low-cost isolated 3.3- to 5-V DC/DC converter	2Q, 2010	12	SLYT371
Designing DC/DC converters based on ZETA topology	2Q, 2010	16	SLYT372
Coupled inductors broaden DC/DC converter usage	3Q, 2010	10	SLYT380

Title	Issue	Page	Lit. No.
Power Management (Continued)			
Computing power going “Platinum”	3Q, 2010	13	SLYT382
A low-cost, non-isolated AC/DC buck converter with no transformer	4Q, 2010	16	SLYT391
Save power with a soft Zener clamp	4Q, 2010	19	SLYT392
An introduction to the Wireless Power Consortium standard and TI’s compliant solutions	1Q, 2011	10	SLYT401
Fine-tuning TI’s Impedance Track™ battery fuel gauge with LiFePO ₄ cells in shallow-discharge applications	1Q, 2011	13	SLYT402
Implementation of microprocessor-controlled, wide-input-voltage, SMBus smart battery charger	2Q, 2011	11	SLYT410
Benefits of a coupled-inductor SEPIC converter	2Q, 2011	14	SLYT411
I _Q : What it is, what it isn’t, and how to use it	2Q, 2011	18	SLYT412
Backlighting the tablet PC	2Q, 2011	23	SLYT414
Challenges of designing high-frequency, high-input-voltage DC/DC converters	2Q, 2011	28	SLYT415
A boost-topology battery charger powered from a solar panel	3Q, 2011	17	SLYT424
Solar charging solution provides narrow-voltage DC/DC system bus for multicell-battery applications	4Q, 2011	8	SLYT439
Solar lantern with dimming achieves 92% efficiency	4Q, 2011	12	SLYT440
Turbo-boost charger supports CPU turbo mode	1Q, 2012	5	SLYT448
Benefits of a multiphase buck converter	1Q, 2012	8	SLYT449
Downslope compensation for buck converters when the duty cycle exceeds 50%	1Q, 2012	14	SLYT450
High-efficiency AC adapters for USB charging	1Q, 2012	18	SLYT451
Interface (Data Transmission)			
TIA/EIA-568A Category 5 cables in low-voltage differential signaling (LVDS)	August 1999	16	SLYT197
Keep an eye on the LVDS input levels	November 1999	17	SLYT188
Skew definition and jitter analysis	February 2000	29	SLYT179
LVDS receivers solve problems in non-LVDS applications	February 2000	33	SLYT180
LVDS: The ribbon cable connection	May 2000	19	SLYT172
Performance of LVDS with different cables	August 2000	30	SLYT163
A statistical survey of common-mode noise	November 2000	30	SLYT153
The Active Fail-Safe feature of the SN65LVDS32A	November 2000	35	SLYT154
The SN65LVDS33/34 as an ECL-to-LVTTL converter	July 2001	19	SLYT132
Power consumption of LVPECL and LVDS	1Q, 2002	23	SLYT127
Estimating available application power for Power-over-Ethernet applications	1Q, 2004	18	SLYT085
The RS-485 unit load and maximum number of bus connections	1Q, 2004	21	SLYT086
Failsafe in RS-485 data buses	3Q, 2004	16	SLYT080
Maximizing signal integrity with M-LVDS backplanes	2Q, 2005	11	SLYT203
Device spacing on RS-485 buses	2Q, 2006	25	SLYT241
Improved CAN network security with TI’s SN65HVD1050 transceiver	3Q, 2006	17	SLYT249
Detection of RS-485 signal loss	4Q, 2006	18	SLYT257
Enabling high-speed USB OTG functionality on TI DSPs	2Q, 2007	18	SLYT271
When good grounds turn bad— isolate!	3Q, 2008	11	SLYT298
Cascading of input serializers boosts channel density for digital inputs	3Q, 2008	16	SLYT301
RS-485: Passive failsafe for an idle bus	1Q, 2009	22	SLYT324
Message priority inversion on a CAN bus	1Q, 2009	25	SLYT325
Designing with digital isolators	2Q, 2009	21	SLYT335
Magnetic-field immunity of digital capacitive isolators	3Q, 2010	19	SLYT381
Interfacing high-voltage applications to low-power controllers	4Q, 2010	20	SLYT393
Designing an isolated I ² C Bus® interface by using digital isolators	1Q, 2011	17	SLYT403
Isolated RS-485 transceivers support DMX512 stage lighting and special-effects applications	3Q, 2011	21	SLYT425
Industrial data-acquisition interfaces with digital isolators	3Q, 2011	24	SLYT426
Extending the SPI bus for long-distance communication	4Q, 2011	16	SLYT441

Title	Issue	Page	Lit. No.
Amplifiers: Audio			
Reducing the output filter of a Class-D amplifier	August 1999	19	SLYT198
Power supply decoupling and audio signal filtering for the Class-D audio power amplifier	August 1999	24	SLYT199
PCB layout for the TPA005D1x and TPA032D0x Class-D APAs	February 2000	39	SLYT182
An audio circuit collection, Part 1	November 2000	39	SLYT155
1.6- to 3.6-volt BTL speaker driver reference design	February 2001	23	SLYT141
Notebook computer upgrade path for audio power amplifiers	February 2001	27	SLYT142
An audio circuit collection, Part 2	February 2001	41	SLYT145
An audio circuit collection, Part 3	July 2001	34	SLYT134
Audio power amplifier measurements	July 2001	40	SLYT135
Audio power amplifier measurements, Part 2	1Q, 2002	26	SLYT128
Precautions for connecting APA outputs to other devices	2Q, 2010	22	SLYT373
Amplifiers: Op Amps			
Single-supply op amp design	November 1999	20	SLYT189
Reducing crosstalk of an op amp on a PCB	November 1999	23	SLYT190
Matching operational amplifier bandwidth with applications	February 2000	36	SLYT181
Sensor to ADC — analog interface design	May 2000	22	SLYT173
Using a decompensated op amp for improved performance	May 2000	26	SLYT174
Design of op amp sine wave oscillators	August 2000	33	SLYT164
Fully differential amplifiers	August 2000	38	SLYT165
The PCB is a component of op amp design	August 2000	42	SLYT166
Reducing PCB design costs: From schematic capture to PCB layout	August 2000	48	SLYT167
Thermistor temperature transducer-to-ADC application	November 2000	44	SLYT156
Analysis of fully differential amplifiers	November 2000	48	SLYT157
Fully differential amplifiers applications: Line termination, driving high-speed ADCs, and differential transmission lines	February 2001	32	SLYT143
Pressure transducer-to-ADC application	February 2001	38	SLYT144
Frequency response errors in voltage feedback op amps	February 2001	48	SLYT146
Designing for low distortion with high-speed op amps	July 2001	25	SLYT133
Fully differential amplifier design in high-speed data acquisition systems	2Q, 2002	35	SLYT119
Worst-case design of op amp circuits	2Q, 2002	42	SLYT120
Using high-speed op amps for high-performance RF design, Part 1	2Q, 2002	46	SLYT121
Using high-speed op amps for high-performance RF design, Part 2	3Q, 2002	21	SLYT112
FilterPro™ low-pass design tool	3Q, 2002	24	SLYT113
Active output impedance for ADSL line drivers	4Q, 2002	24	SLYT108
RF and IF amplifiers with op amps	1Q, 2003	9	SLYT102
Analyzing feedback loops containing secondary amplifiers	1Q, 2003	14	SLYT103
Video switcher using high-speed op amps	3Q, 2003	20	SLYT098
Expanding the usability of current-feedback amplifiers	3Q, 2003	23	SLYT099
Calculating noise figure in op amps	4Q, 2003	31	SLYT094
Op amp stability and input capacitance	1Q, 2004	24	SLYT087
Integrated logarithmic amplifiers for industrial applications	1Q, 2004	28	SLYT088
Active filters using current-feedback amplifiers	3Q, 2004	21	SLYT081
Auto-zero amplifiers ease the design of high-precision circuits	2Q, 2005	19	SLYT204
So many amplifiers to choose from: Matching amplifiers to applications	3Q, 2005	24	SLYT213
Getting the most out of your instrumentation amplifier design	4Q, 2005	25	SLYT226
High-speed notch filters	1Q, 2006	19	SLYT235
Low-cost current-shunt monitor IC revives moving-coil meter design	2Q, 2006	27	SLYT242
Accurately measuring ADC driving-circuit settling time	1Q, 2007	14	SLYT262
New zero-drift amplifier has an I_Q of 17 μ A	2Q, 2007	22	SLYT272
A new filter topology for analog high-pass filters	3Q, 2008	18	SLYT299
Input impedance matching with fully differential amplifiers	4Q, 2008	24	SLYT310
A dual-polarity, bidirectional current-shunt monitor	4Q, 2008	29	SLYT311
Output impedance matching with fully differential operational amplifiers	1Q, 2009	29	SLYT326
Using fully differential op amps as attenuators, Part 1: Differential bipolar input signals	2Q, 2009	33	SLYT336
Using fully differential op amps as attenuators, Part 2: Single-ended bipolar input signals	3Q, 2009	21	SLYT341
Interfacing op amps to high-speed DACs, Part 1: Current-sinking DACs	3Q, 2009	24	SLYT342

Title	Issue	Page	Lit. No.
Amplifiers: Op Amps (Continued)			
Using the infinite-gain, MFB filter topology in fully differential active filters	3Q, 2009	33	SLYT343
Using fully differential op amps as attenuators, Part 3: Single-ended unipolar input signals	4Q, 2009	19	SLYT359
Interfacing op amps to high-speed DACs, Part 2: Current-sourcing DACs	4Q, 2009	23	SLYT360
Operational amplifier gain stability, Part 1: General system analysis	1Q, 2010	20	SLYT367
Signal conditioning for piezoelectric sensors	1Q, 2010	24	SLYT369
Interfacing op amps to high-speed DACs, Part 3: Current-sourcing DACs simplified	1Q, 2010	32	SLYT368
Operational amplifier gain stability, Part 2: DC gain-error analysis	2Q, 2010	24	SLYT374
Operational amplifier gain stability, Part 3: AC gain-error analysis	3Q, 2010	23	SLYT383
Using single-supply fully differential amplifiers with negative input voltages to drive ADCs	4Q, 2010	26	SLYT394
Converting single-ended video to differential video in single-supply systems	3Q, 2011	29	SLYT427
Measuring op amp settling time by using sample-and-hold technique	1Q, 2012	21	SLYT452
Low-Power RF			
Using the CC2430 and TIMAC for low-power wireless sensor applications: A power-consumption study	2Q, 2008	17	SLYT295
Selecting antennas for low-power wireless applications	2Q, 2008	20	SLYT296
General Interest			
Synthesis and characterization of nickel manganite from different carboxylate precursors for thermistor sensors	February 2001	52	SLYT147
Analog design tools	2Q, 2002	50	SLYT122
Spreadsheet modeling tool helps analyze power- and ground-plane voltage drops to keep core voltages within tolerance	2Q, 2007	29	SLYT273
Analog linearization of resistance temperature detectors	4Q, 2011	21	SLYT442

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011012

DLP is a registered trademark and Auto-Track, E2E, FilterPro, Green Rectifier, Impedance Track, LabVIEW, MSP430, OMAP, SWIFT, and TINA-TI are trademarks of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. The Bluetooth word mark and logos are owned by the Bluetooth SIG, Inc., and any use of such marks by Texas Instruments is under license. Celeron is a trademark and StrataFlash is a registered trademark of Intel Corporation. I²C Bus is a registered trademark of NXP B.V. Corporation. InfiniBand is a service mark of the InfiniBand Trade Association. MATLAB is a registered trademark of The MathWorks, Inc. Ultrabook is a trademark of Intel Corporation. All other trademarks are the property of their respective owners.