

Automotive Qualified Isolated Wake for Digital Audio Bus Controllers

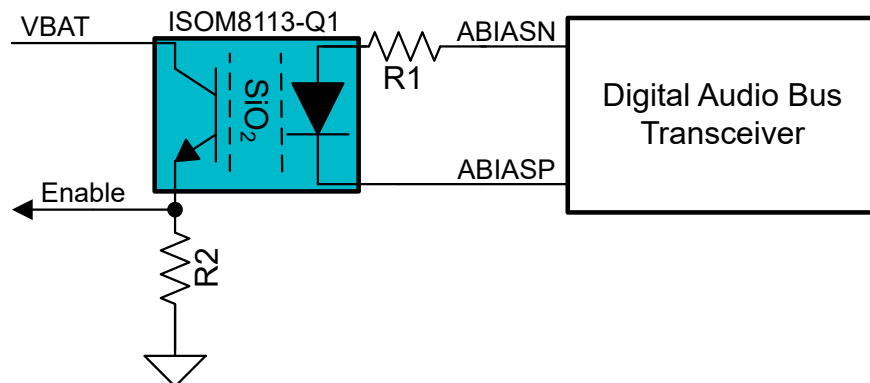


Figure 1. Isolated Wake Circuit for Automotive Digital Audio Bus Using ISOM8113-Q1

Design Considerations

- [\[FAQ\] What is an Opto-emulator?](#) | [\[FAQ\] Opto-Emulator FAQ's](#) | [\[FAQ\] What are the benefits?](#)
- Allows for low-cost, isolated, relay weld detection OBC systems
- Performance upgrade from traditional optocouplers; allows tight CTR performance with no LED aging.
- [Introduction to Opto-Emulators](#)
- [Opto-emulators explained: Why you should upgrade your optocoupler technology](#)
- [Upgrade photoMOS, SSR and Push-Pull, Totem-Pole, or Transistor Output Optocouplers With Opto-emulators](#)

Need additional assistance? Ask our engineers a question on the [TI E2E™ Isolation Support Forum](#).

Recommended Parts

Analog Output Opto-Emulators

Catalog Part Number	Automotive Part Number	Input Type	Output Type	V _F (MAX)	CTR
ISOM8110	ISOM8110-Q1	DC Input	Open-collector / transistor output	1.4V	100% to 155%
ISOM8111	ISOM8111-Q1			1.4V	150% to 230%
ISOM8112	ISOM8112-Q1			1.4V	255% to 380%
ISOM8113	ISOM8113-Q1			1.4V	375% to 560%

To find a pin-to-pin alternative to the optocouplers in your design, search TI's [cross reference tool](#). For more opto-emulators, browse through the [online parametric tool](#).

Resistor selection

R1 limits the amount of current flowing into the opto-emulator input and outputs a wake-up signal when the Digital Audio Bias Negative and Positive lines have an active signal (ABIASN and ABIASP). $I_{F \min}$ is 0.7mA, therefore the input current can be 1mA to allow for input sufficient margin. Therefore, R1 needs to satisfy:

$$R_1 < ((V_{ABIASP} - V_{ABIASN}) - V_F) \div I_{F \min} \quad (1)$$

R2 limits the maximum output current $I_{C \max}$ and is set according to the current and voltage needed at enable. For more information, please see [\[FAQ\] ISOM8110: How do I design ISOM8110 to have the best timing performance for switching applications?](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2025, Texas Instruments Incorporated

Last updated 10/2025