

Common Challenges When Choosing the Auxiliary Power Supply for Your Server PSU



Neha Nain

High-power converters used in server, telecom and industrial systems need auxiliary power supplies to support the housekeeping needs of the power-supply unit (PSU). Due to the ever-growing need for higher power density, these PSUs use an additional add-on card to support their auxiliary needs.



An auxiliary power supply commonly powers the internal control electronics, voltage and current feedback sensing electronics, system fans and biasing supply. It is an isolated DC/DC converter generating multiple isolated outputs to power primary- and secondary-side control devices ranging from 5W to 40W. [Figure 1](#) shows the typical usage of auxiliary power supply in server PSUs.

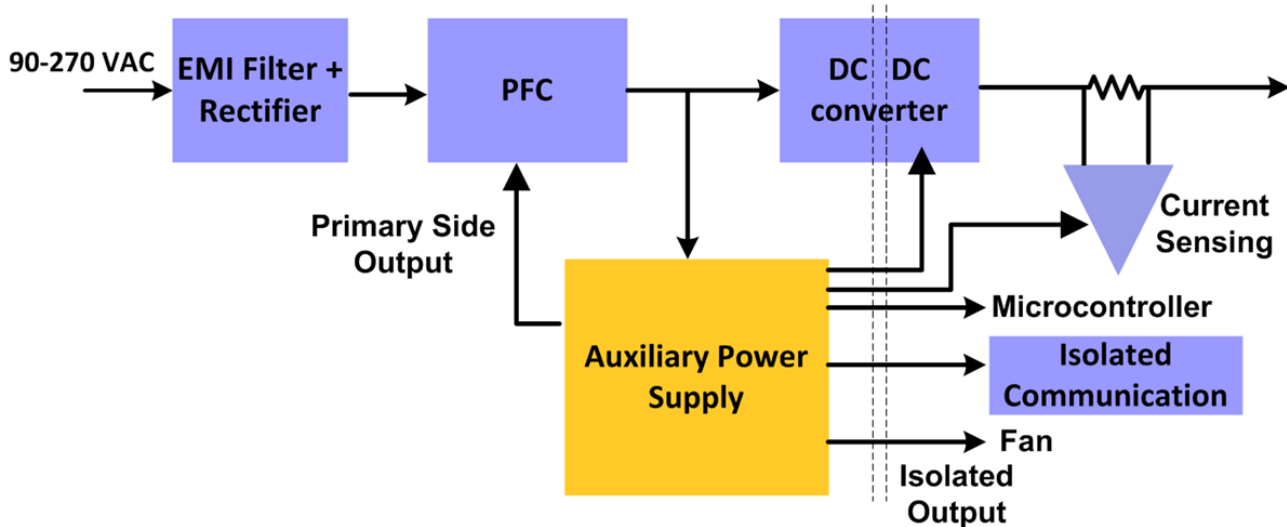


Figure 1. System Block Diagram of a Server PSU

The auxiliary power supplies are a part of a larger PSU which contains an electromagnetic interference (EMI) filter, diode bridge and bulk capacitor. The bulk capacitor gives us the rectified DC bus, making these supplies independent isolated DC/DC converter. The auxiliary power supplies must have high efficiency over a wide load range (10% load to full load) in order to help the server PSUs meet 80 PLUS platinum/titanium standards, tight regulation, low cost and low standby power, in sizes as small as possible to maintain high power density. The auxiliary power supply also needs to operate over a wide input range (from 100V to 400V_{DC}); have multiple isolated outputs; and keep the system electronics powered under all conditions to detect faults such as undervoltage, overvoltage and overcurrent.

Topology Selection

While selecting the topology of the DC/DC converter for an auxiliary power supply, keep in mind cost, efficiency, the reinforced isolation requirement for the outputs and the form factor. Since you need isolated outputs, your options are limited to flyback, forward, half /full bridge and push-pull converters.

The power level for the auxiliary power supply is usually low, varying from 5W to 40W. This low power-level requirement eliminates half/full-bridge and push-pull converters due to their expense, component requirements and greater losses. And although the efficiency of both flyback and forward converter topologies is comparable, the forward topology uses an extra inductor at the output, which makes it bulkier and more expensive when compared to a flyback converter.

Since a flyback transformer is really a coupled inductor through which power storage and transfer between the primary and secondary occurs, you do not need a separate inductor for storage. And because the other associated circuitry is simple, the flyback topology is thus a very popular topology for low-power-level converters requiring multiple outputs.

Realizing an Auxiliary Power Supply with Seven Outputs

The [25-W, 88% Efficiency, Multiple Isolated Output, Auxiliary Supply Reference Design for AC-DC Power Supply](#) demonstrates a fully equipped platform for a 25W auxiliary power supply, achieving high efficiency using quasi-resonant (QR) valley switching and primary-side regulation (PSR). This reference design provides 25W of continuous power over a wide DC input range from 120V to 425V_{DC}. It has a flyback power stage implemented using the [UCC28700](#) Valley Switched PSR CC-CV flyback controller to deliver seven outputs: three outputs referred to the primary ground of the transformer and four completely isolated outputs.

The UCC28700's valley-switching feature helps this design achieve high efficiency. The use of PSR eliminates the need for an optocoupler, which reduces component count and helps reduce the form factor. Another feature

that helps reduce the overall design size is the operating frequency. The UCC28700 can go up to a 130kHz switching frequency, which reduces the magnetics size and enables high power density. The form factor of this design is 35mm by 60mm with an EE20 transformer. The maximum efficiency achieved is >88% and the maximum no-load power consumed is ~80mW.

All things considered, the key challenges while building an auxiliary power supply is to provide safe and reliable power while delivering high performance with low power consumption and low bill-of-material (BOM) cost.

Additional resources

- Learn more about stimulating electromagnetic interference from our Power House blog
- Find out how GaN can help with electromagnetic interference
- Download the [25-W, 88% Efficiency, Multiple Isolated Output, Auxiliary Supply Reference Design for AC-DC Power Supply](#) Design Guide
- Learn more about TI's flyback solutions at www.ti.com/flyback

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated