

48-V Output Low-Noise Phantom Power Reference Design



1 Description

This reference design delivers a 48-V output, low-noise power supply for the phantom power application using the TPS61391 and TPS7A4101 devices. The TPS61391 is a 700-kHz PWM step-up converter that converts 3.3 V or 5 V to 48.5 V. The TPS7A4101 is a 50-V tolerant input and 0.29-V drop LDO that steps 48.5 V down to 48 V and minimizes the output ripple. The design supports 48-V, 20-mA output power at 5-V input. The output ripple is only around 8.4 mV, which is pretty low for phantom power applications.



Figure 1-1. Top Photo

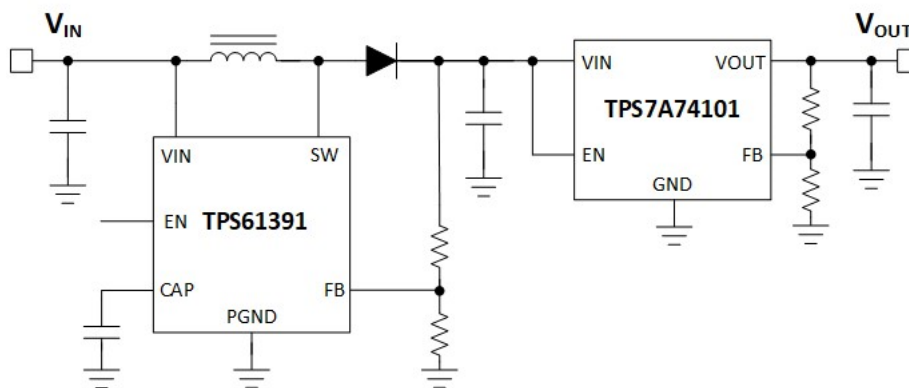


Figure 1-2. Block Diagram

2 Test Prerequisites

2.1 Voltage and Current Requirements

Table 2-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage	3.3-5 VDC
Output Voltage	48 VDC
Output Current	10-mA at 3.3-VDC input 20-mA at 5-VDC input

2.2 Required Equipment

- Multimeter (current): Fluke 287C
- Multimeter (voltage): Fluke 287C
- DC Source: Chroma MODEL 62012P-100-50
- E-Load: Chroma 63110A
- Oscilloscope: Tektronix DPO3054
- Electrical Thermography: Fluke TiS65

2.3 Dimensions

The board dimensions are 58.4 mm (length) × 30.5 mm (width) × 8.4 mm (height).

3 Testing and Results

3.1 Efficiency Graphs

Efficiency is shown in the following figure.

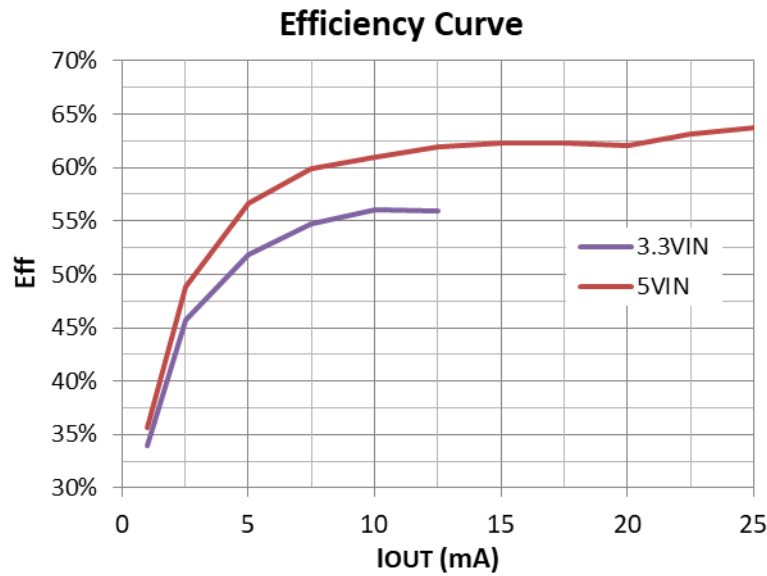


Figure 3-1. Efficiency Graph

3.2 Efficiency Data

Efficiency data is shown in the following table.

V _{IN} (V)	I _{IN} (mA)	P _{IN} (W)	Boost V _{OUT1} (V)	LDO V _{OUT} (V)	I _{OUT} (mA)	P _{OUT} (W)	P _{Loss} (W)	Eff.
3.3045	16.54	0.0547	48.239	47.636	0	0.0000	0.0547	
3.3013	43.5	0.1436	48.239	47.614	1.026	0.0489	0.0948	34.02%
3.2914	79.5	0.2617	48.239	47.604	2.516	0.1198	0.1419	45.77%
3.2923	140.3	0.4619	48.239	47.593	5.032	0.2395	0.2224	51.85%
3.2856	198.4	0.6519	48.24	47.586	7.504	0.3571	0.2948	54.78%
3.2968	257.7	0.8496	48.242	47.576	10.018	0.4766	0.3730	56.10%
3.2972	322.9	1.0647	48.242	47.571	12.530	0.5961	0.4686	55.99%
4.9943	10.64	0.0531	48.242	47.638	0	0.0000	0.0531	
4.997	27.34	0.1366	48.241	47.613	1.023	0.0487	0.0879	35.65%
4.9913	49.1	0.2451	48.241	47.603	2.515	0.1197	0.1254	48.85%
4.9936	84.6	0.4225	48.242	47.593	5.032	0.2395	0.1830	56.69%
4.9963	119.2	0.5956	48.242	47.584	7.503	0.3570	0.2385	59.95%
4.9926	156.7	0.7823	48.242	47.578	10.018	0.4766	0.3057	60.92%
4.9938	192.8	0.9628	48.242	47.57	12.531	0.5961	0.3667	61.91%
4.9924	230.1	1.1488	48.242	47.563	15.047	0.7157	0.4331	62.30%
4.9894	268.2	1.3382	48.242	47.555	17.519	0.8331	0.5050	62.26%
4.9937	307.5	1.5356	48.242	47.546	20.033	0.9525	0.5831	62.03%
4.9876	340	1.6958	48.239	47.537	22.505	1.0698	0.6260	63.09%
4.9855	371.5	1.8521	47.501	47.142	25.021	1.1795	0.6726	63.69%

3.3 Thermal Images

Thermal images are shown in the following figures.

Note

Testing was done after 20 minutes of operation, $T_a = 19.0^\circ\text{C}$.

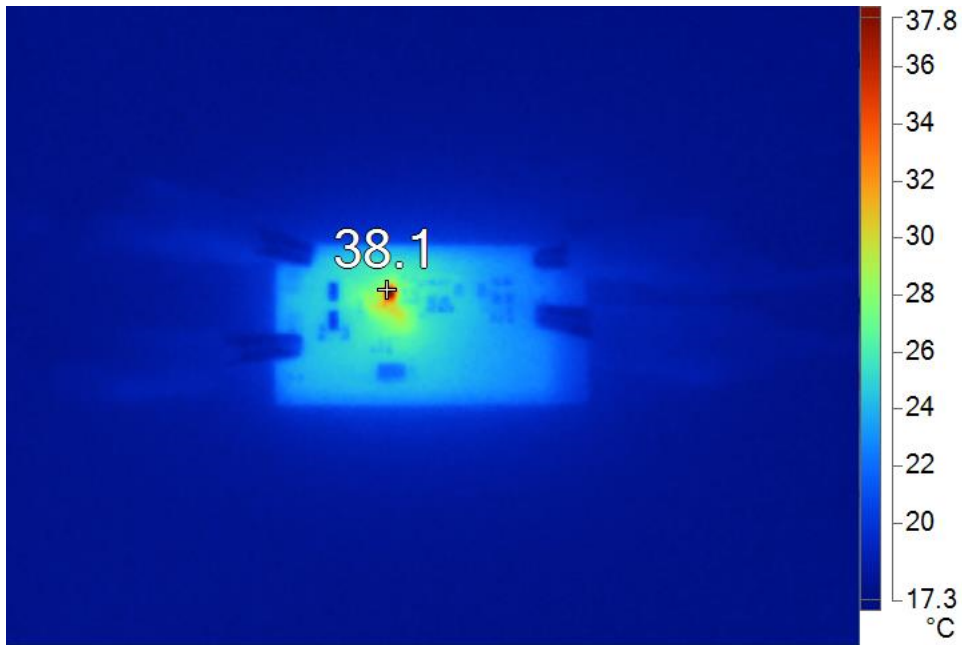


Figure 3-2. 3.3-V Input, 48-V, 10-mA Output, top Side

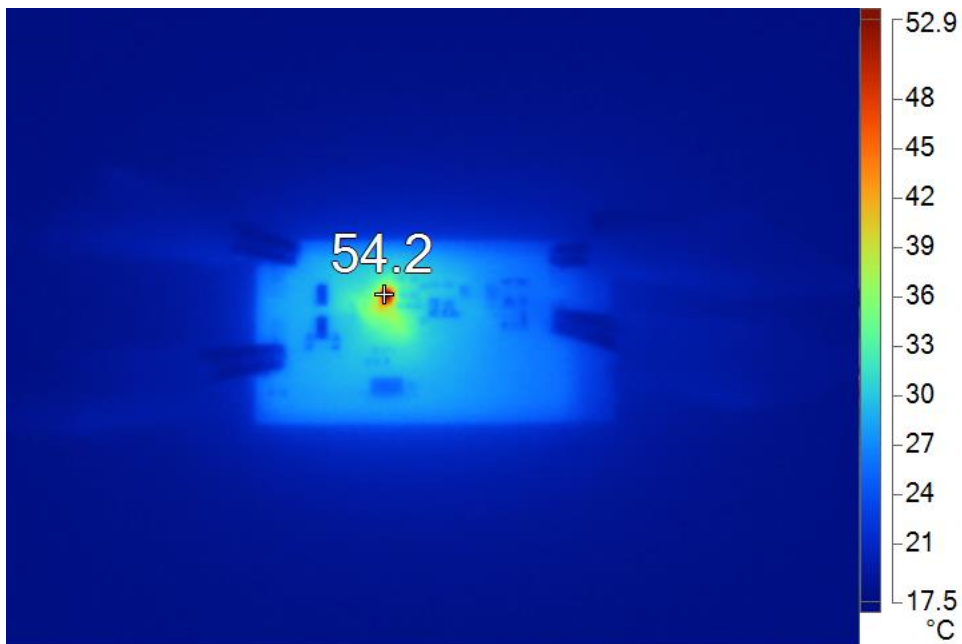


Figure 3-3. 5-V Input, 48-V, 20-mA Output, top Side

3.4 Load Regulation

Load regulation is shown in the following figure.


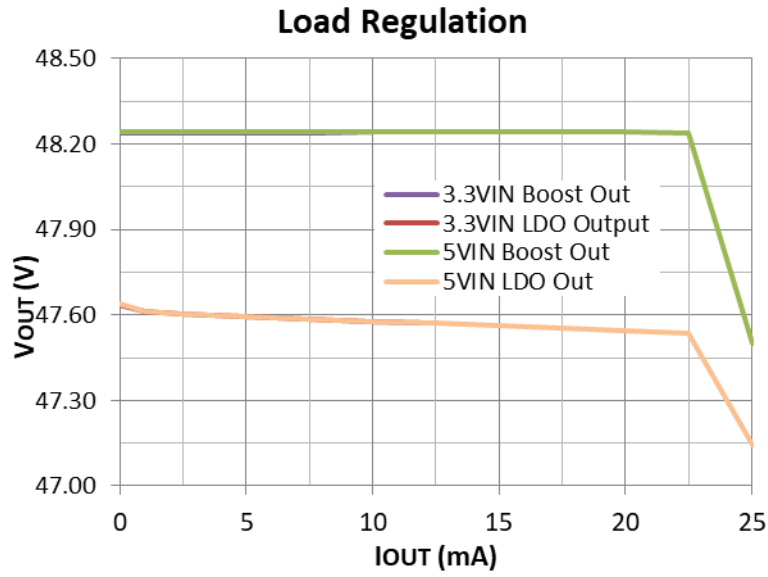


Figure 3-4. Load Regulation

4 Waveforms


4.1 Switching

Switching behavior of the TPS61391 is shown in the following figures.

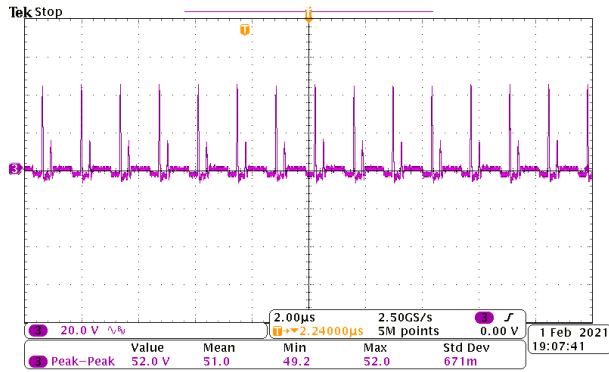


CH3: V_{SW}

Figure 4-1. 3.3-V input, 48-V no load

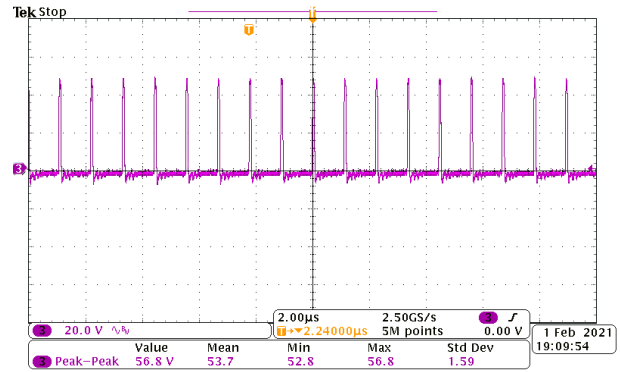


CH3: V_{SW}

Figure 4-2. 3.3-V Input, 48-V, 10-mA Load

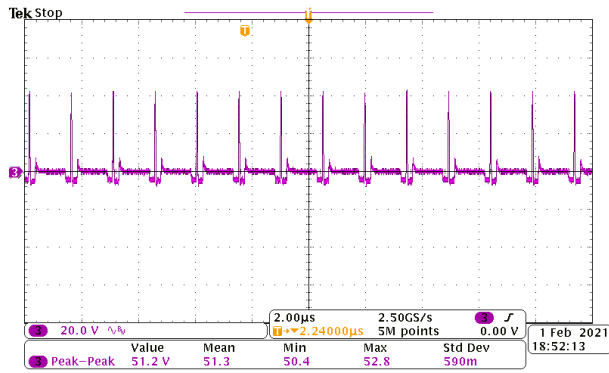

CH3: V_{SW}

Figure 4-3. 5-V Input, 48-V no Load

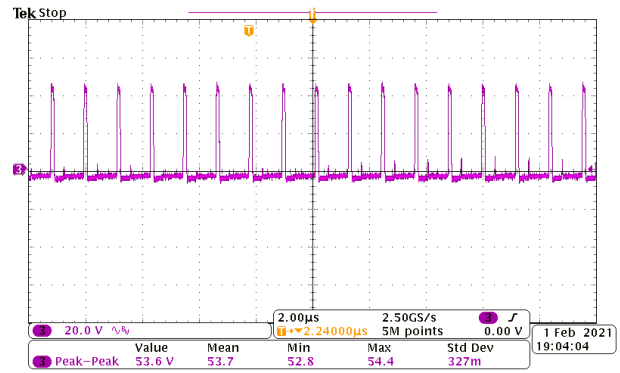


CH3: V_{SW}

Figure 4-4. 5-V Input, 48-V, 20-mA Load


4.2 Output Voltage Ripple

The output voltage ripple of the TPS61391 is shown in the following figures. It is also the input voltage ripple of the TPS7A4101.

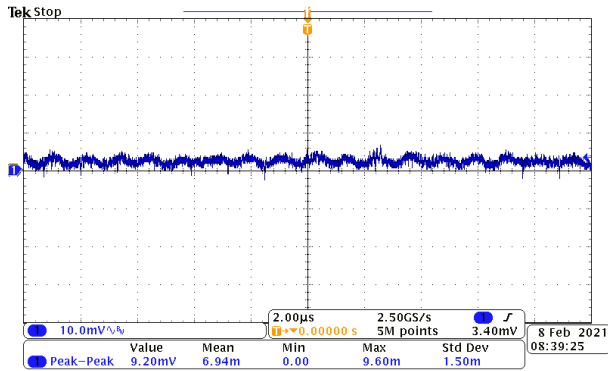


CH1: $V_{OUT(Boost)}$

Figure 4-5. 3.3-V Input, 48-V no Load

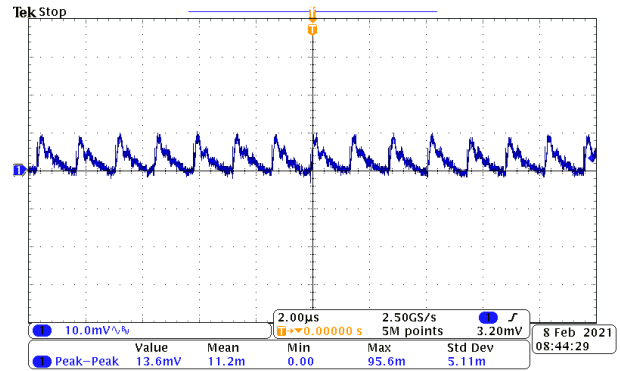


CH1: $V_{OUT(Boost)}$

Figure 4-6. 3.3-V Input, 48-V, 10-mA Load

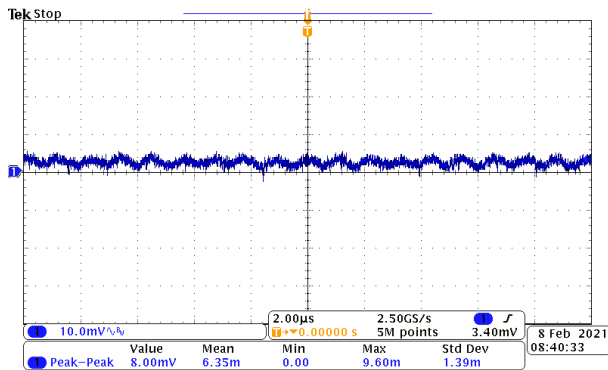

CH1: $V_{OUT(Boost)}$


Figure 4-7. 5-V Input, 48-V no Load

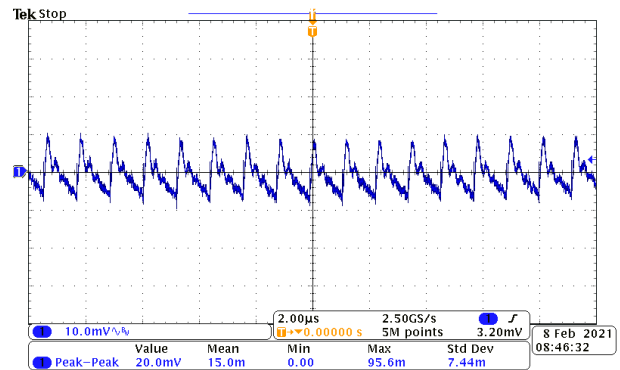

CH1: $V_{OUT(Boost)}$


Figure 4-8. 5-V Input, 48-V, 20-mA Load

The output voltage ripple of the LDO is shown in the following figures.

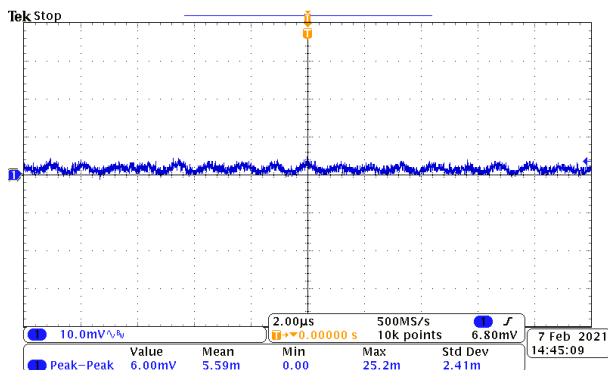


CH1: V_{OUT}

Figure 4-9. 3.3-V Input, 48-V no Load

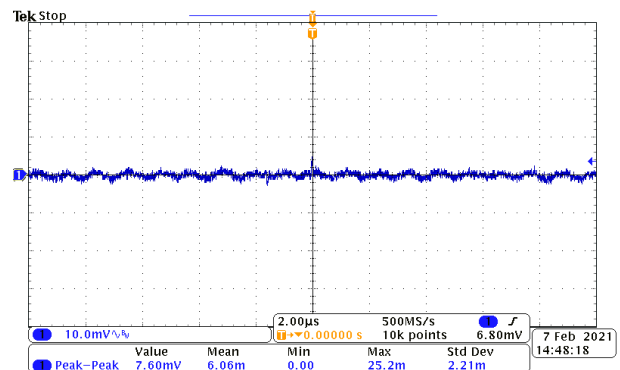


CH1: V_{OUT}

Figure 4-10. 3.3-V Input, 48-V, 10-mA Load

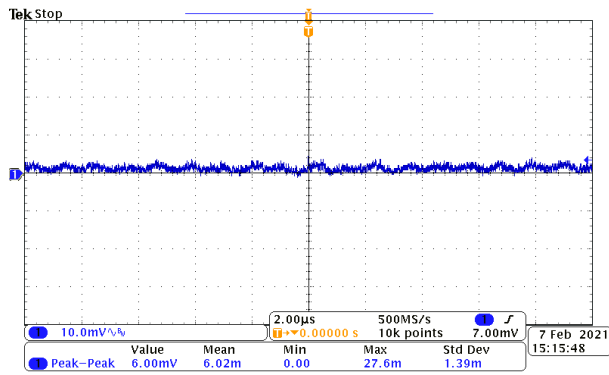

CH1: V_{OUT(Boost)}

Figure 4-11. 5-V Input, 48-V no Load

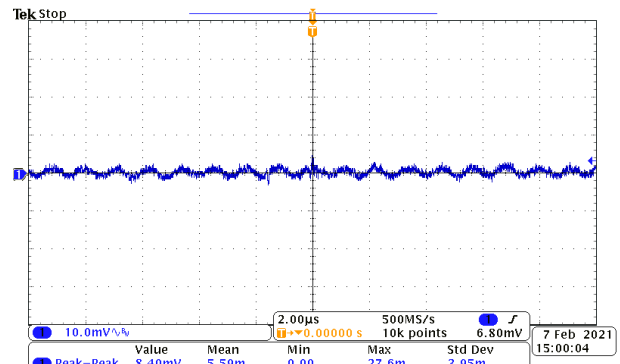


CH1: V_{OUT(Boost)}


Figure 4-12. 5-V Input, 48-V, 20-mA Load

4.3 Load Transients


The waveforms of output AC ripples at load transient (with 10-nF CBYP) are shown in following images.

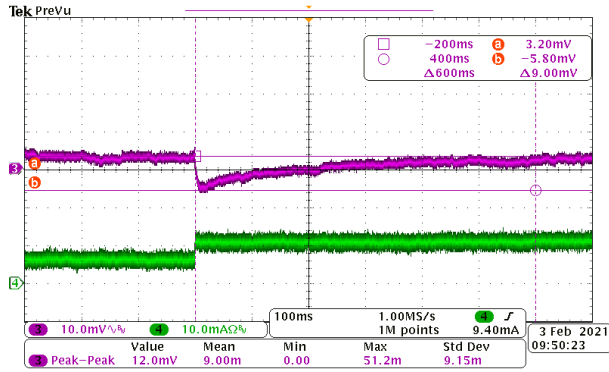


CH3: V_{OUT}, CH4: I_{OUT}
Figure 4-13. 3.3-V Input, 48 V, 5 mA to 10 mA

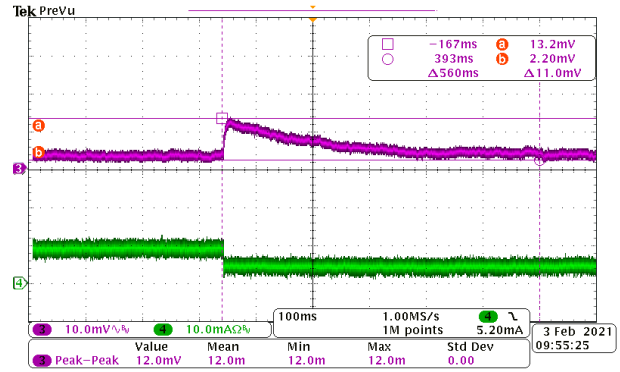

CH3: V_{OUT}, CH4: I_{OUT}
Figure 4-14. 3.3-V Input, 48 V, 10 mA to 5 mA

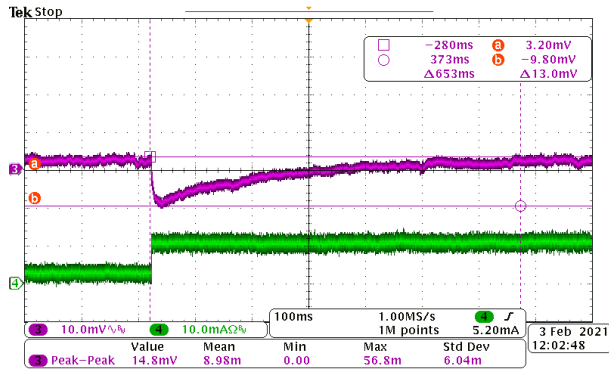


CH3: V_{OUT}, CH4: I_{OUT}
Figure 4-15. 5-V Input, 48 V, 10 mA to 20 mA

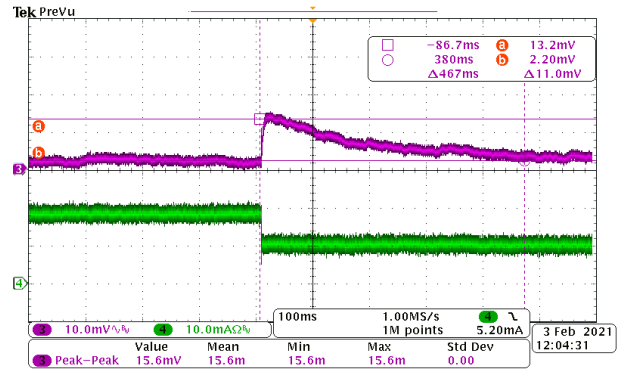

CH3: V_{OUT}, CH4: I_{OUT}
Figure 4-16. 5-V Input, 48 V, 20 mA to 10 mA


4.4 Start-up Sequence

Start-up behavior is shown in the following figures.

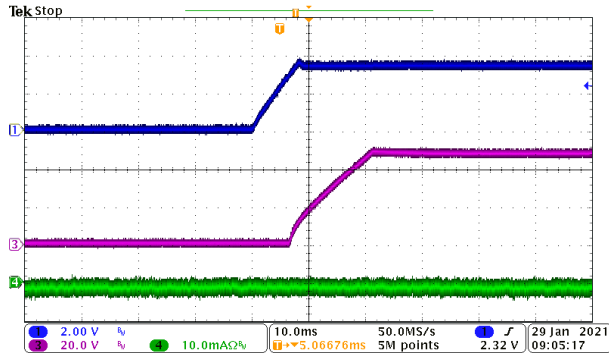


CH1: V_{IN} , CH3: V_{OUT} , CH4: I_{OUT}

Figure 4-17. 3.3-V Input, 48-V no Load

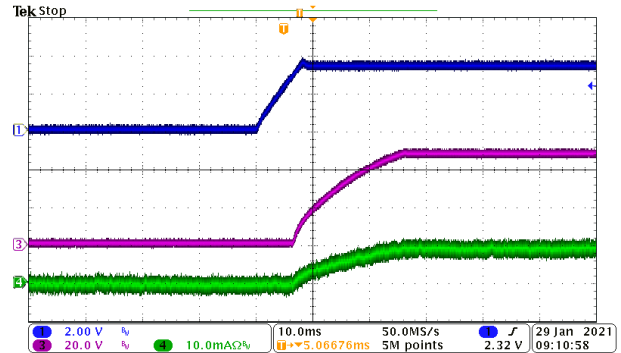


CH1: V_{IN} , CH3: V_{OUT} , CH4: I_{OUT}

Figure 4-18. 3.3-V Input, 48-V, 10-mA Load

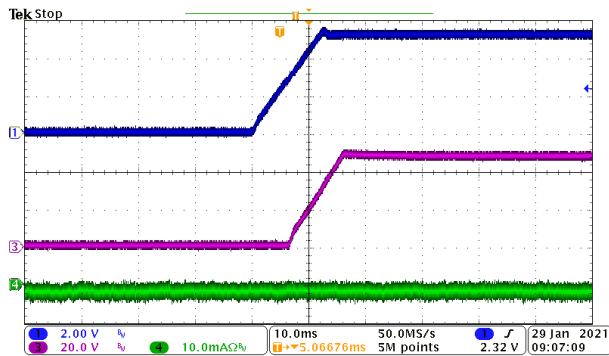

CH1: V_{IN} , CH3: V_{OUT} , CH4: I_{OUT}

Figure 4-19. 5-V Input, 48-V no Load

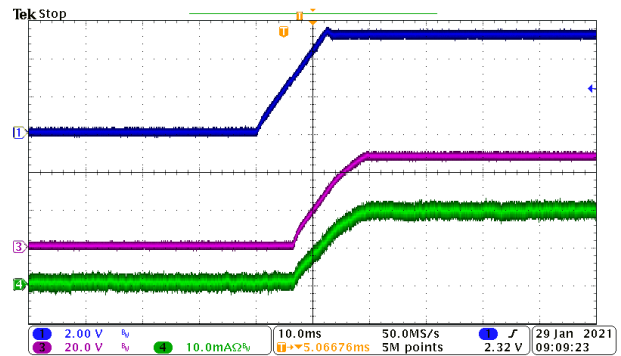

CH1: V_{IN} , CH3: V_{OUT} , CH4: I_{OUT}

Figure 4-20. 5-V Input, 48-V, 20-mA Load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated