

100W Automotive Infotainment Display Module Reference Design With Functional Safety Capabilities



Description

This reference design demonstrates a power supply system for infotainment display modules with common system requirements like cold crank, load dump, and Automotive Safety Integrity Level (ASIL). The LM74900-Q1 is the first stage of the design playing a role of protection for negative input voltage, undervoltage, locked output, and overcurrent protection. The LM5152-Q1 is the second stage to function as pre-boost controller which can boost up to a specific voltage if battery voltage is low when starting up. The device supports battery voltages down to 4.2V and 100W power output. At the third stage, the design uses LMQ644A2-Q1, TPS62813-Q1, and TPS745-Q1 to provide the desired voltage to the subsystem like local dimming backlight, TCON, and SerDes. Lastly the design uses voltage monitors to monitor each rail and to aid ISO 26262 system design to achieve the targeted ASIL.

Features


- LM74900-Q1 is the automotive ideal diode with circuit breaker, undervoltage (UV), and overvoltage (OV) protection with fault output
- LM5152-Q1 is the automotive low- I_Q synchronous boost controller for start-stop and backup battery power supply
- LMQ644A2-Q1 is the 3V to 36V, low- I_Q , dual 6A automotive buck converter optimized for power density and low EMI
- TPS37-Q1 is the wide V_{IN} , 65V dual channel OV and UV detector with programmable sense and reset delay function for automotive
- TPS3704-Q1 is the low V_{IN} automotive quad window or standard voltage supervisor
- Total 100W power rating with 4.2V battery voltage input
- Reference design aids ISO 26262 system design to achieve the targeted ASIL

Applications


- [Automotive display module](#)



Top of Board

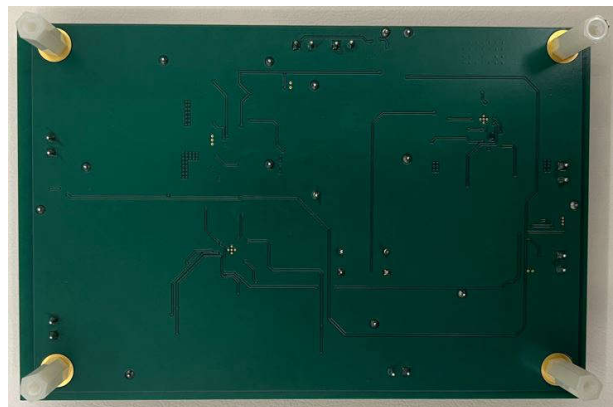

Bottom of Board

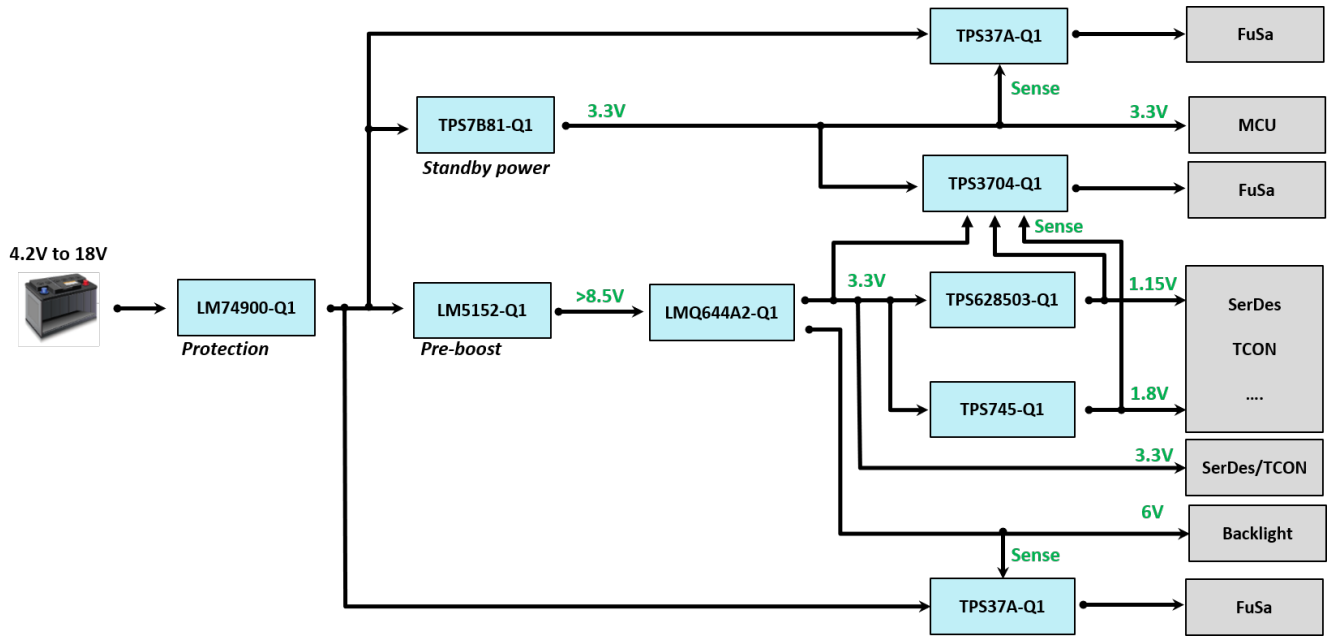

Block Diagram

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Key System Specifications

Device	Parameter	Value (MIN)	Value (TYP)	Value (MAX)	Unit
LM74900-Q1	Input voltage	4.2	13.5	18	Volt
	Output voltage	4.2	13.5	18	Volt
	Output current	24	7.4	5.55	Amp
LM5152-Q1	Input voltage	4.2	13.5	18	Volt
	Output voltage	8.5	13.5	18	Volt
	Output current	11.76	7.4	5.55	Amp
	Switching frequency	440			kHz
TPS7B8133-Q1	Input voltage	4.2	13.5	18	Volt
	Output voltage	3.3			Volt
	Output current	0.15			Amp
LMQ644A2-Q1	Input voltage	8.5	13.5	18	Volt
	Output voltage_1	3.3			Volt
	Output current_1	4			Amp
	Output voltage_2	6			Volt
	Output current_2	6			Amp
	Switching frequency	440			kHz
TPS628503-Q1	Input voltage	3.3			Volt
	Output voltage	1.15			Volt
	Output current	3			Amp
	Switching frequency	2200			kHz
TPS745-Q1	Input voltage	3.3			Volt
	Output voltage	1.8			Volt
	Output current	0.5			Amp

1.2 Required Equipment

- DC Source: Chroma 62006P-100-50
- DC electronic load: Chroma 6314A
- Oscilloscope: Tektronix DPO3054
- Electrical thermography: Fluke TiS55
- Digital Power meter: Yokogama WT310E
- Vector Network Analyzer: OMICRON Bode100
- Multimeter: Fluke 287C

1.3 Dimensions

The board dimensions are 137mm (length) × 90.7mm (width) × 15mm (height).

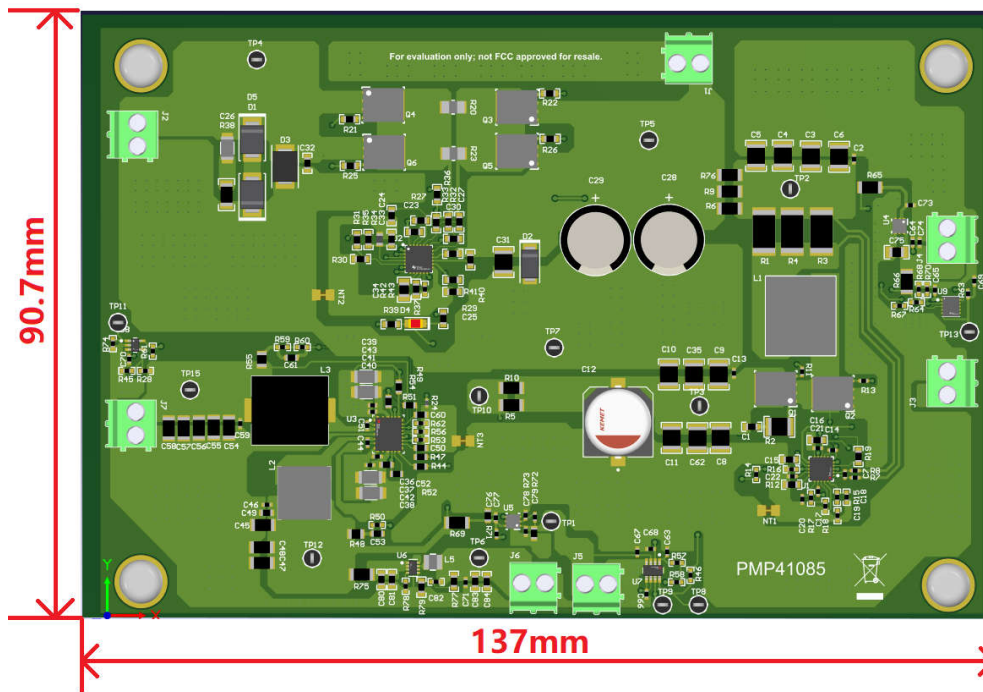


Figure 1-1. Board Dimension

2 Testing and Results

2.1 Thermal Images

LM5152-Q1 thermal images are shown in the following figures. The test conditions include room temperature with no airflow.

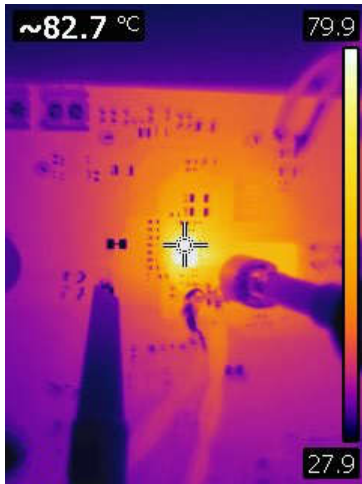


Figure 2-1. Thermal Image at 13.5 V_{IN}, 13.5 V_{OUT}, 7.4A I_{OUT}

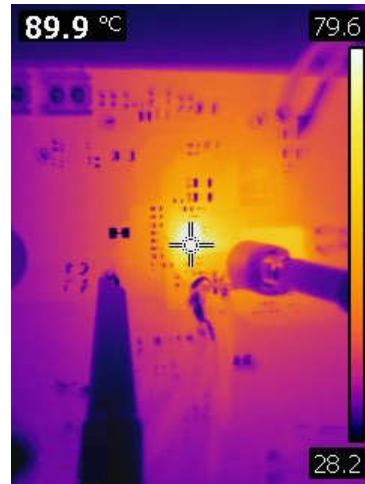


Figure 2-2. Thermal Image at 18 V_{IN}, 18 V_{OUT}, 5.55A I_{OUT}

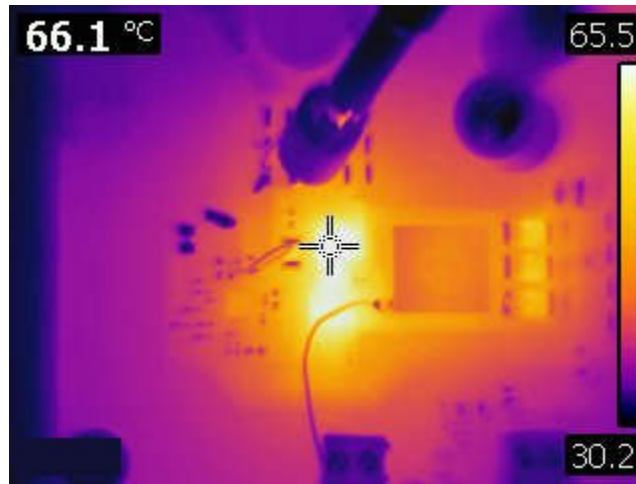


Figure 2-3. Thermal Image at 4.2 V_{IN}, 8.5 V_{OUT}, 11.76A I_{OUT}

LM74900-Q1 thermal images are shown in the following figures. The test conditions include room temperature, no airflow.

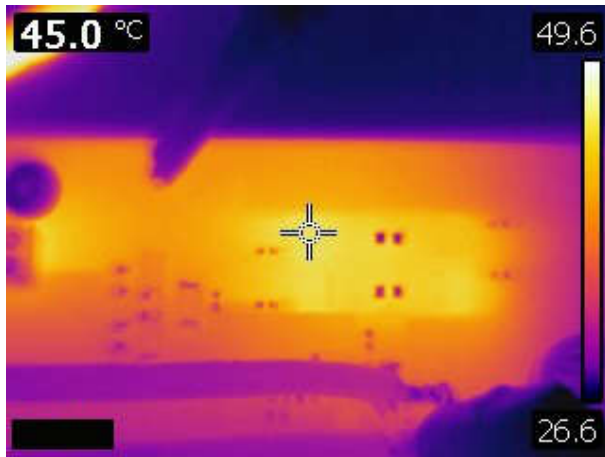


Figure 2-4. Thermal Image at 4.2 V_{IN}, 4.2 V_{OUT}, 24A I_{OUT}

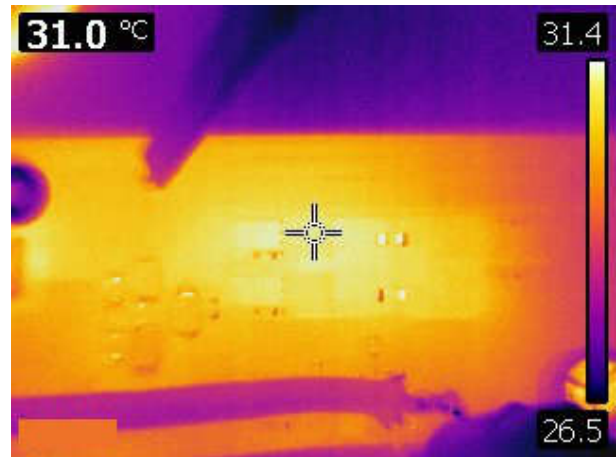


Figure 2-5. Thermal Image at 13.5 V_{IN}, 13.5 V_{OUT}, 7.48A I_{OUT}

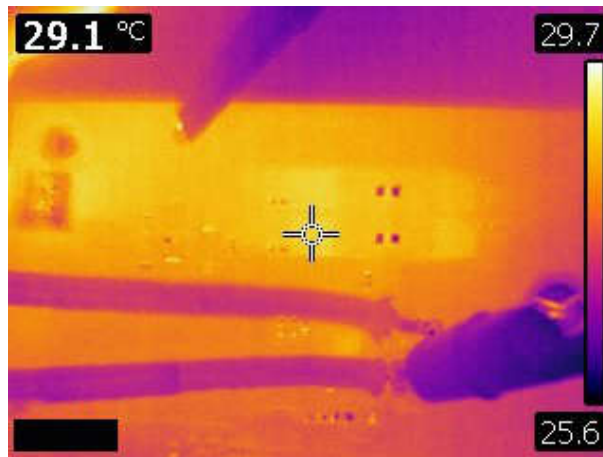


Figure 2-6. Thermal Image at 18 V_{IN}, 18 V_{OUT}, 5.55A I_{OUT}

LMQ644A2-Q1 thermal images are shown in the following figures. The test conditions include room temperature, output1 3.3V, 4A, output2 6V, 6A with no airflow.

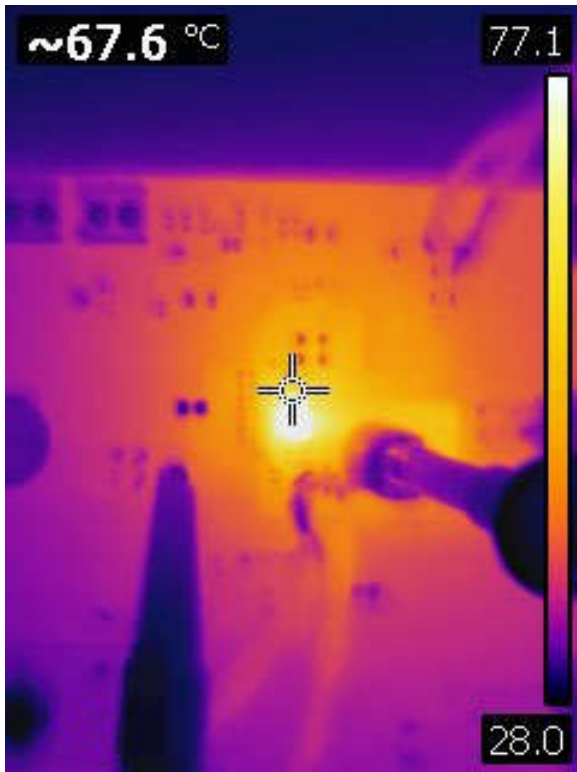


Figure 2-7. Thermal Image at 8.5 V_{IN}

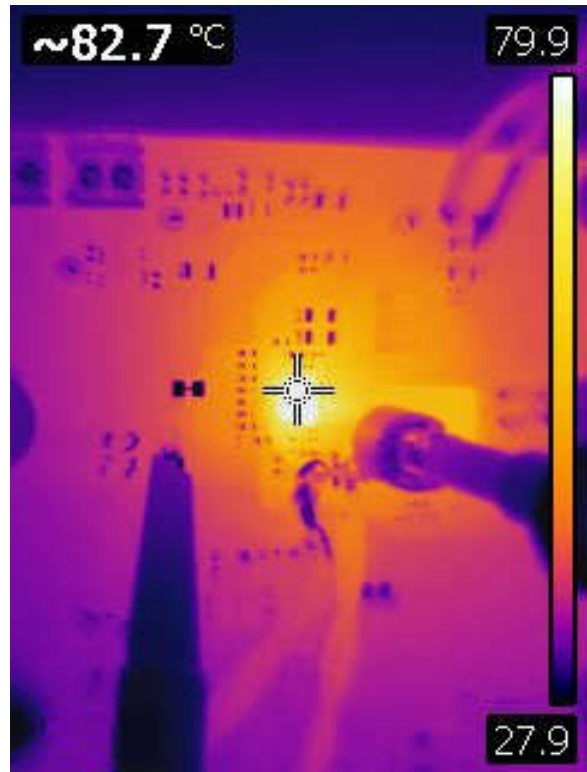


Figure 2-8. Thermal Image at 13.5 V_{IN}



Figure 2-9. Thermal Image at 18 V_{IN}

Thermal images of TPS7B81-Q1 are shown in the following figure. The test conditions include room temperature, no airflow.



Figure 2-10. Thermal Image at 4.2 V_{IN}, 3.3 V_{OUT}, 0.15A I_{OUT}

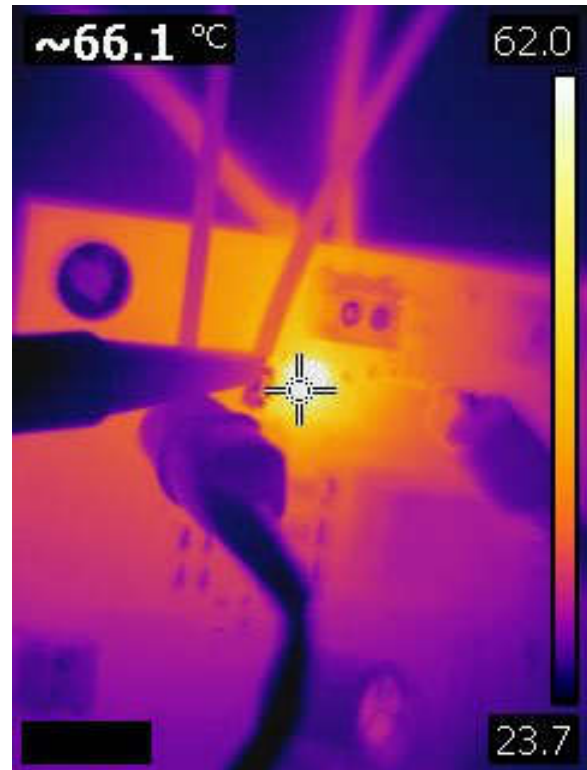


Figure 2-11. Thermal Image at 13.5 V_{IN}, 3.3 V_{OUT}, 0.15A I_{OUT}

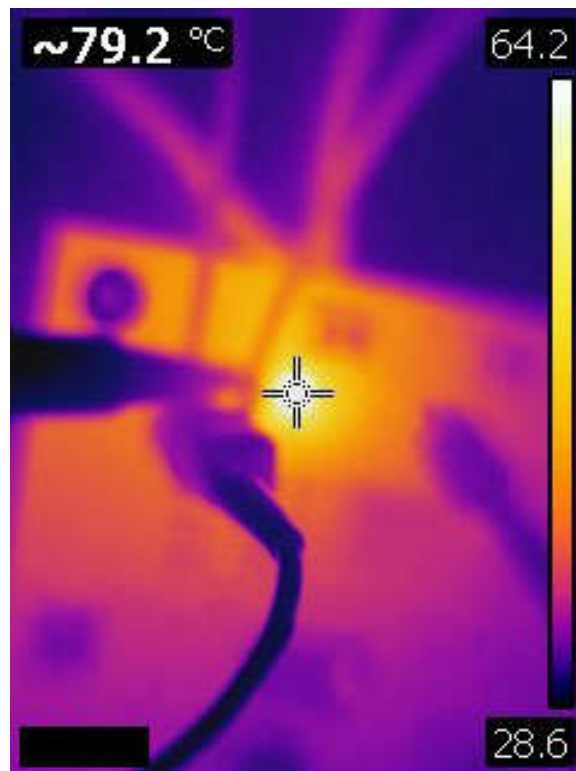


Figure 2-12. Thermal Image at 18 V_{IN}, 3.3 V_{OUT}, 0.15A I_{OUT}

Thermal images of TPS628503-Q1 are shown in the following figure. The test conditions include room temperature, no airflow.

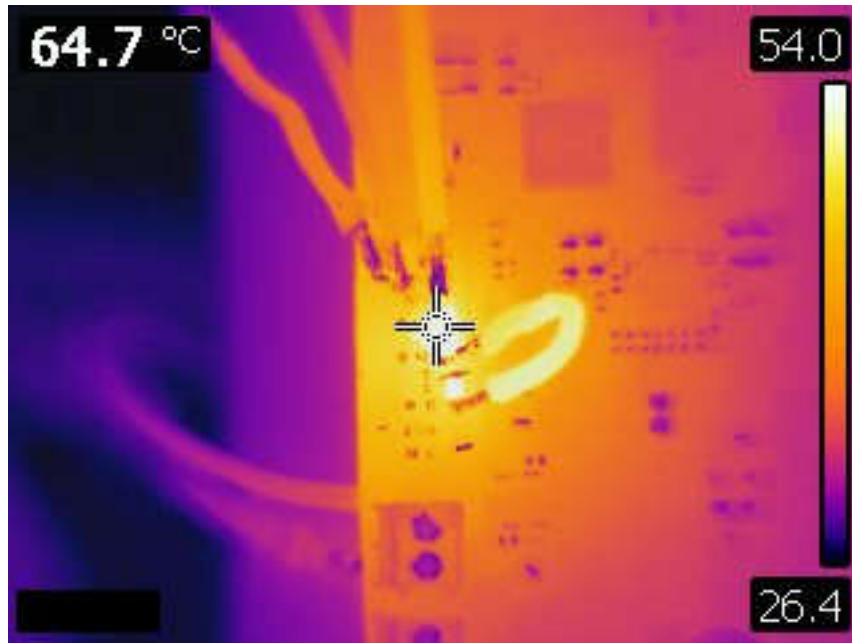


Figure 2-13. Thermal Image at 3.3 V_{IN}, 1.15 V_{OUT}, 3A I_{OUT}

2.2 Bode Plots

Bode plots of LMQ644A2-Q1 are shown in the following figures.

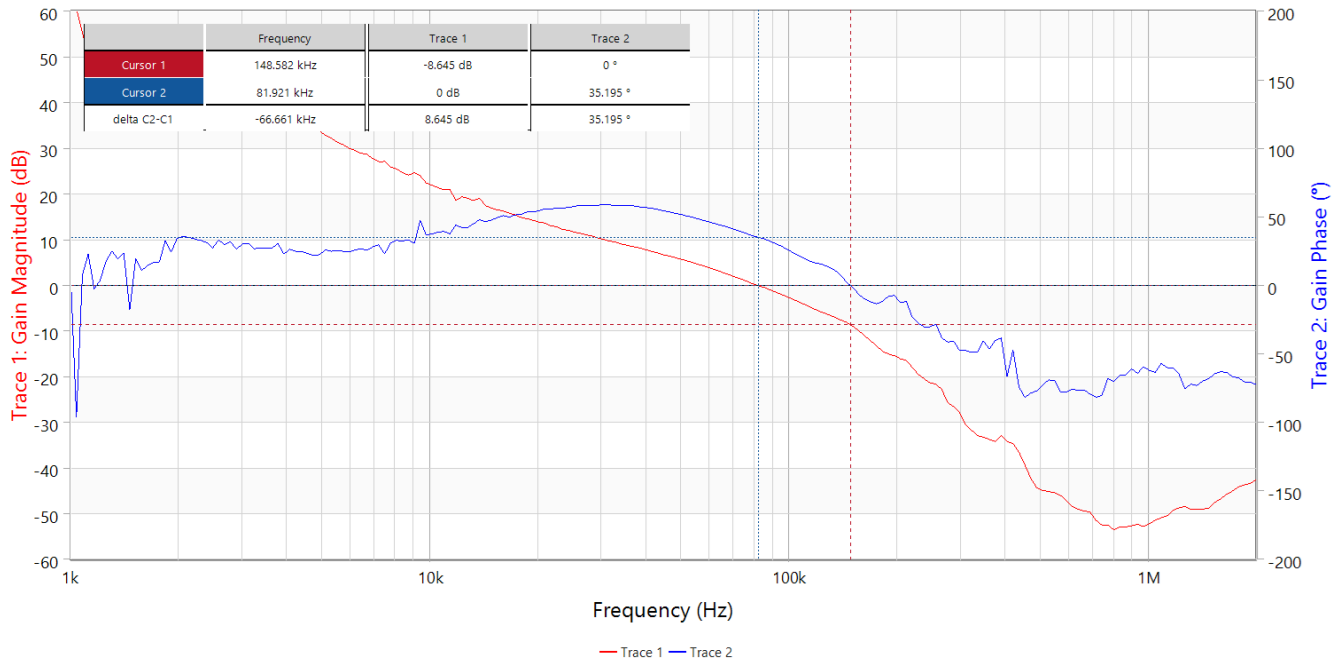


Figure 2-14. Bode Plot at 8.5 V_{IN}, 3.3 V_{OUT}, 0A I_{OUT}

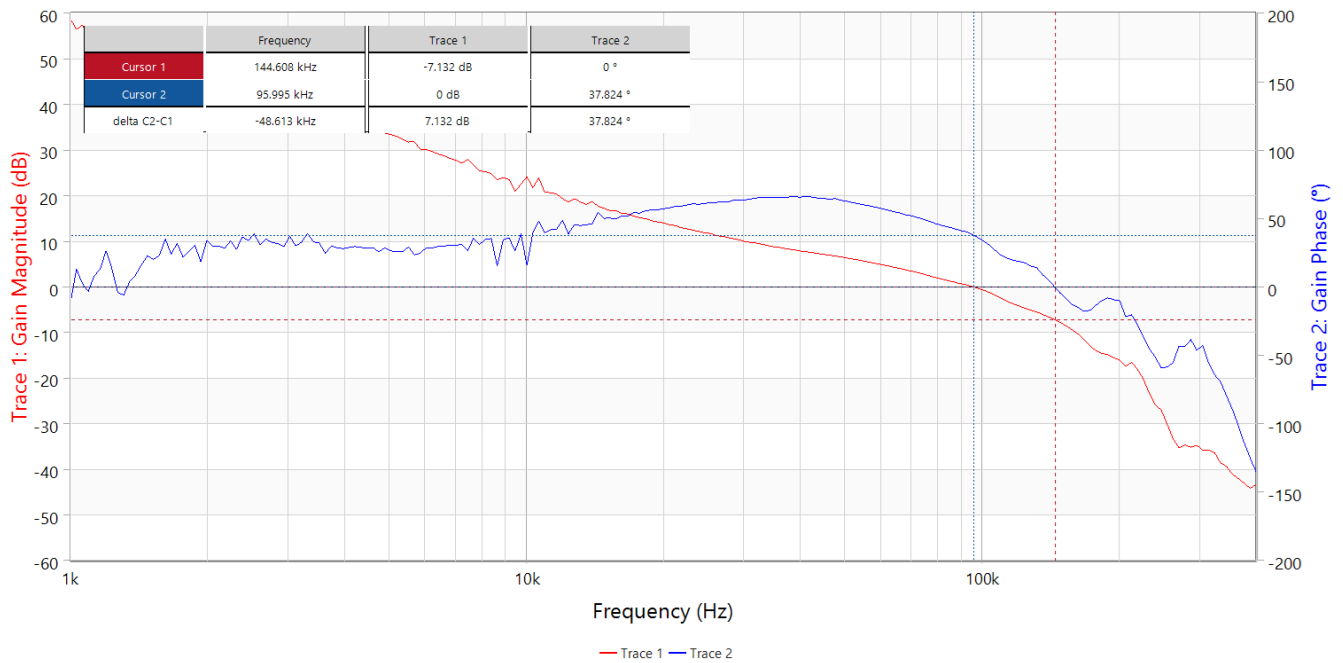


Figure 2-15. Bode Plot at 8.5 V_{IN}, 3.3 V_{OUT}, 4A I_{OUT}

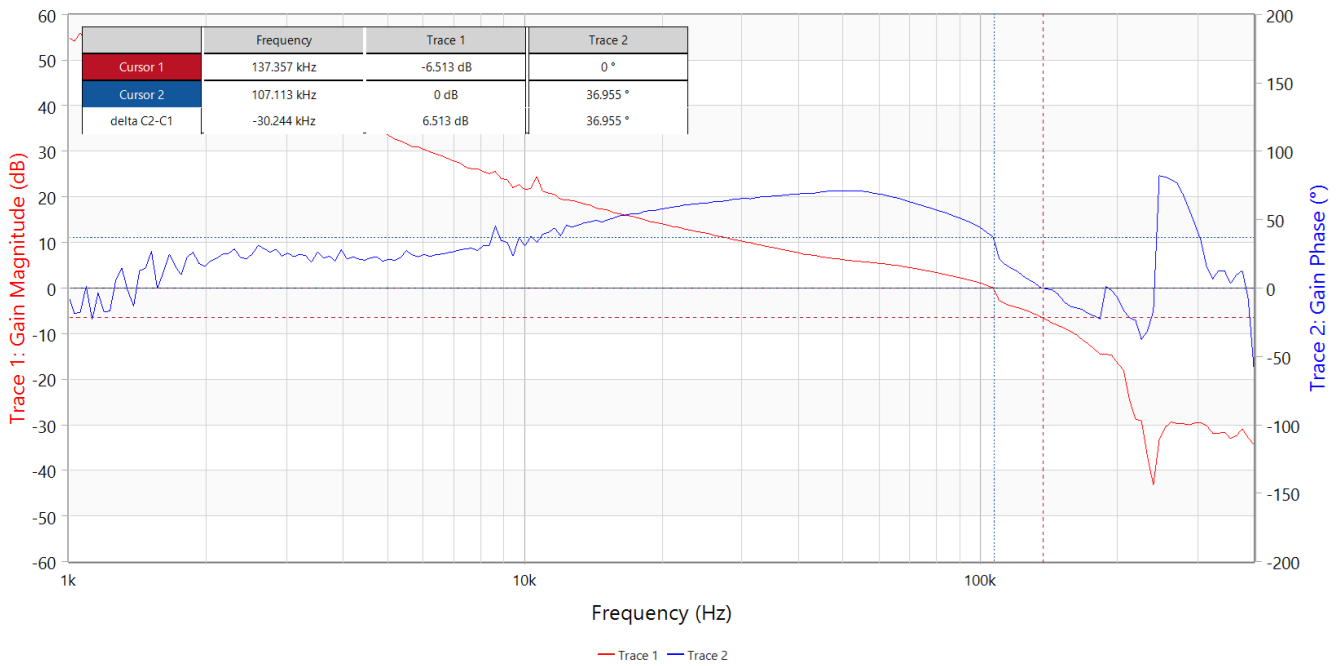


Figure 2-16. Bode Plot at 13.5 V_{IN}, 3.3 V_{OUT}, 4A I_{OUT}

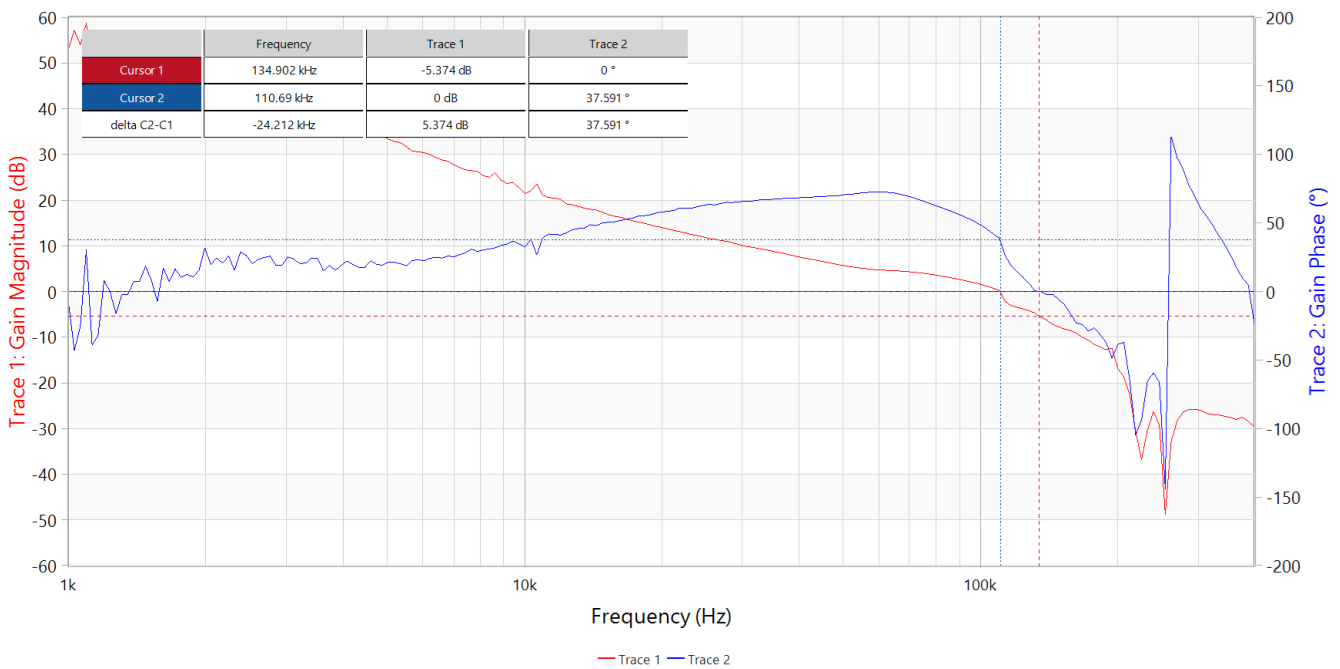


Figure 2-17. Bode Plot at 18 V_{IN}, 3.3 V_{OUT}, 4A I_{OUT}

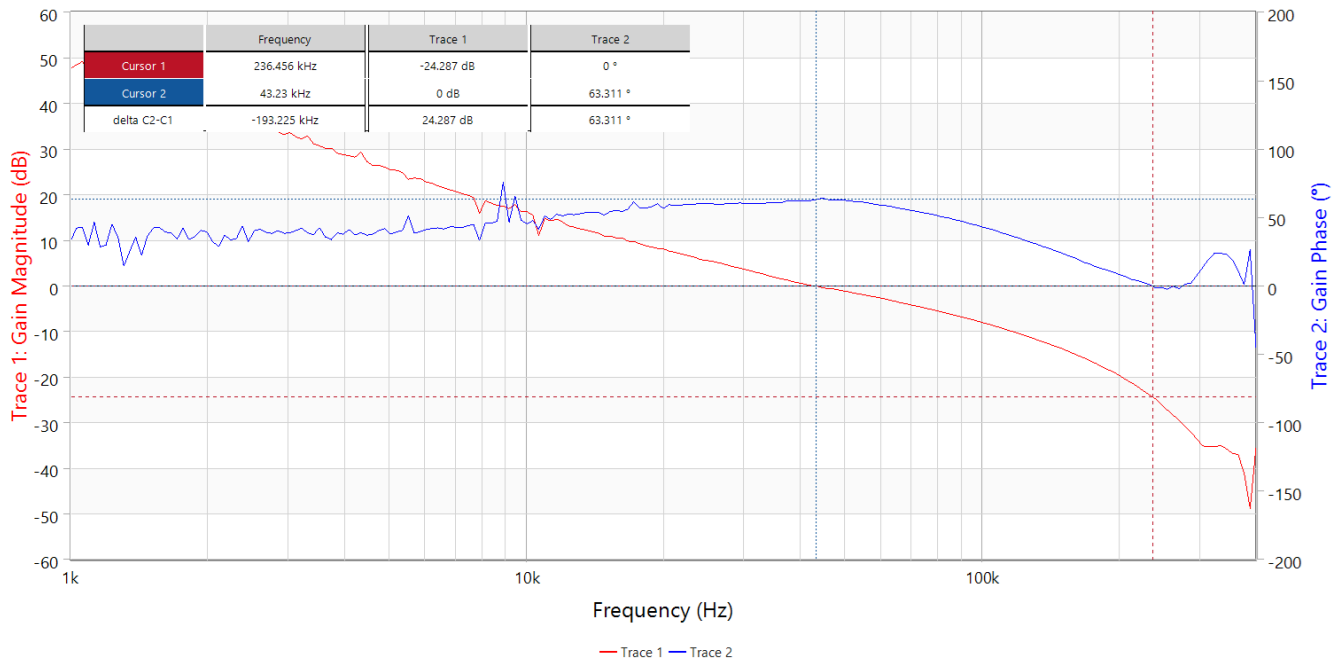


Figure 2-18. Bode Plot at 8.5 V_{IN}, 6 V_{OUT}, 6A I_{OUT}

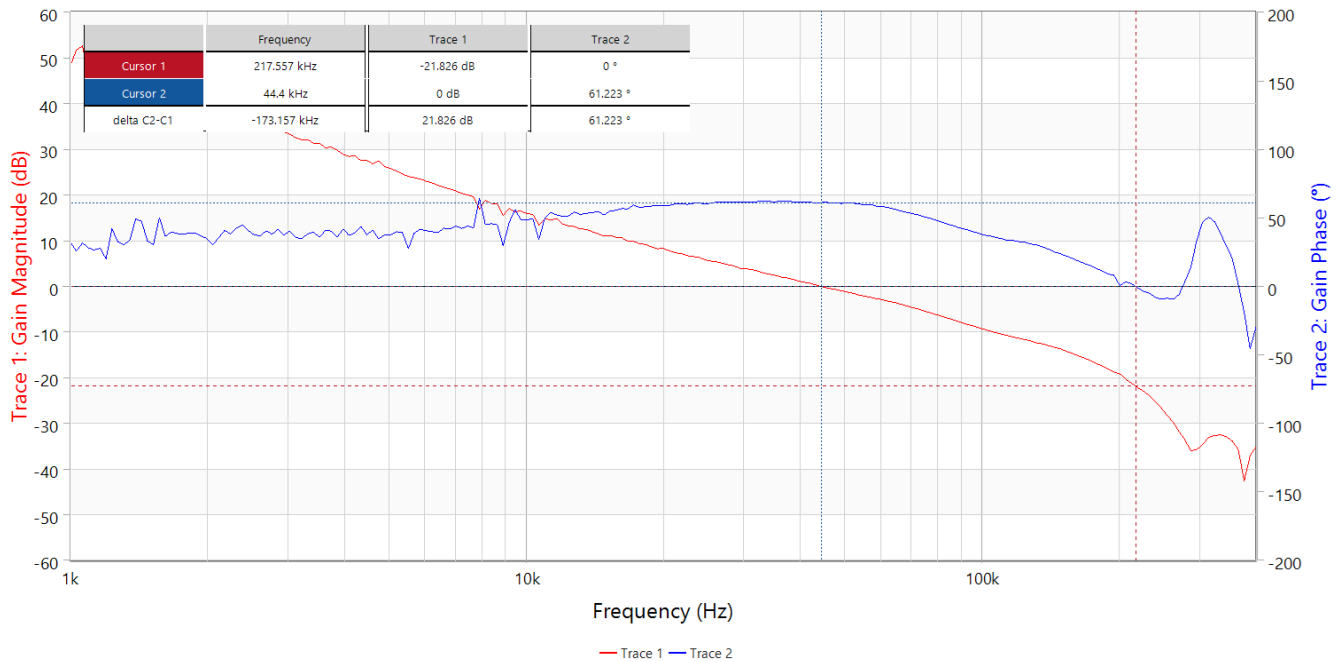


Figure 2-19. Bode Plot at 13.5 V_{IN}, 6 V_{OUT}, 6A I_{OUT}

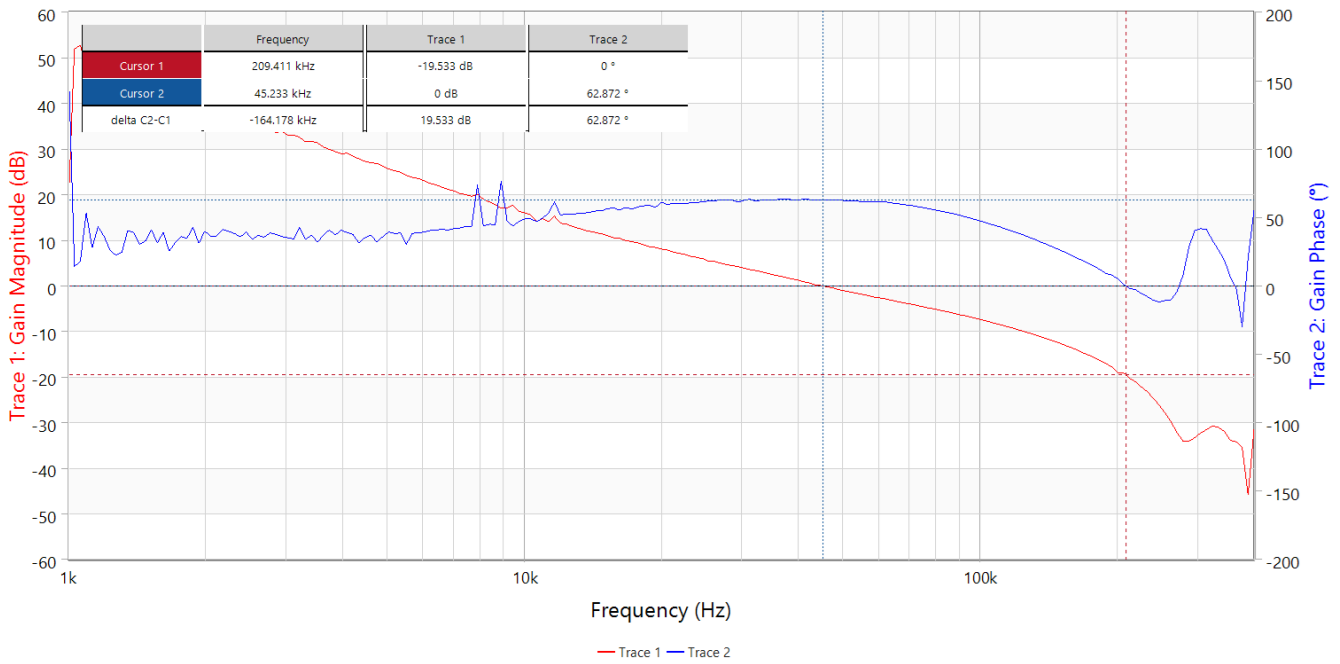


Figure 2-20. Bode Plot at 18 V_{IN}, 6 V_{OUT}, 6A I_{OUT}

Bode plots of TPS628503-Q1 are shown in the following figures.

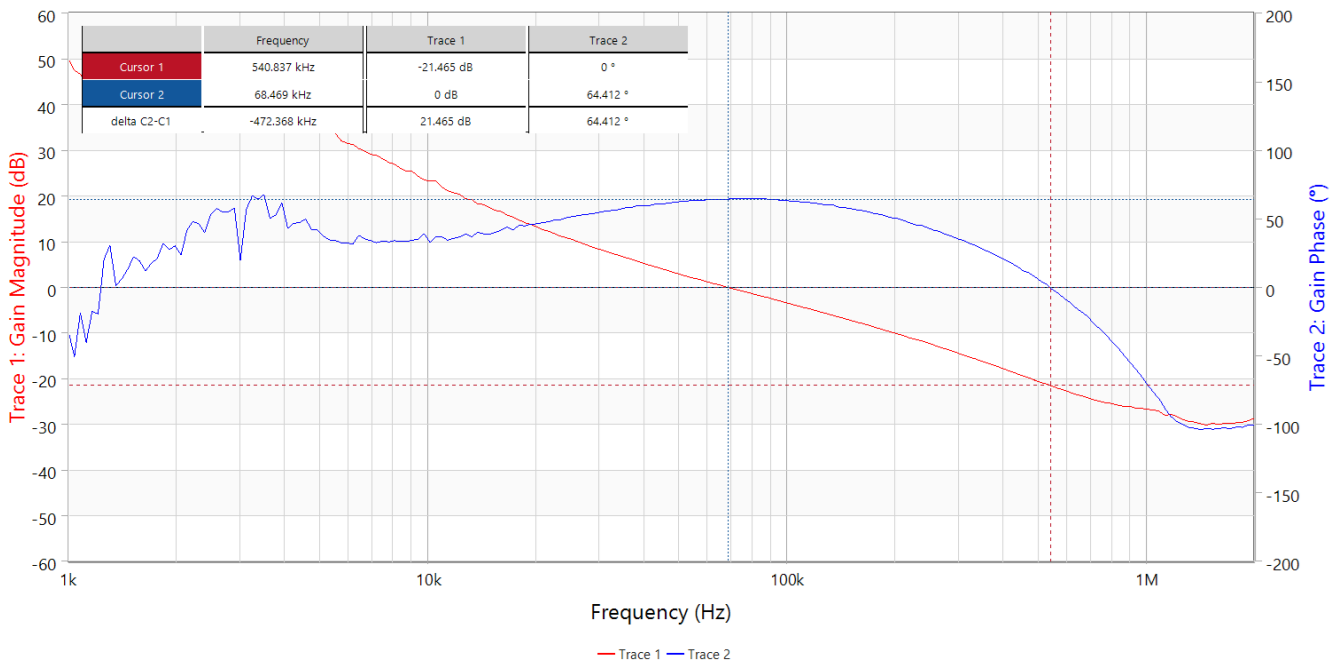


Figure 2-21. Bode Plot at 3.3 V_{IN}, 1.15 V_{OUT}, 0A I_{OUT}

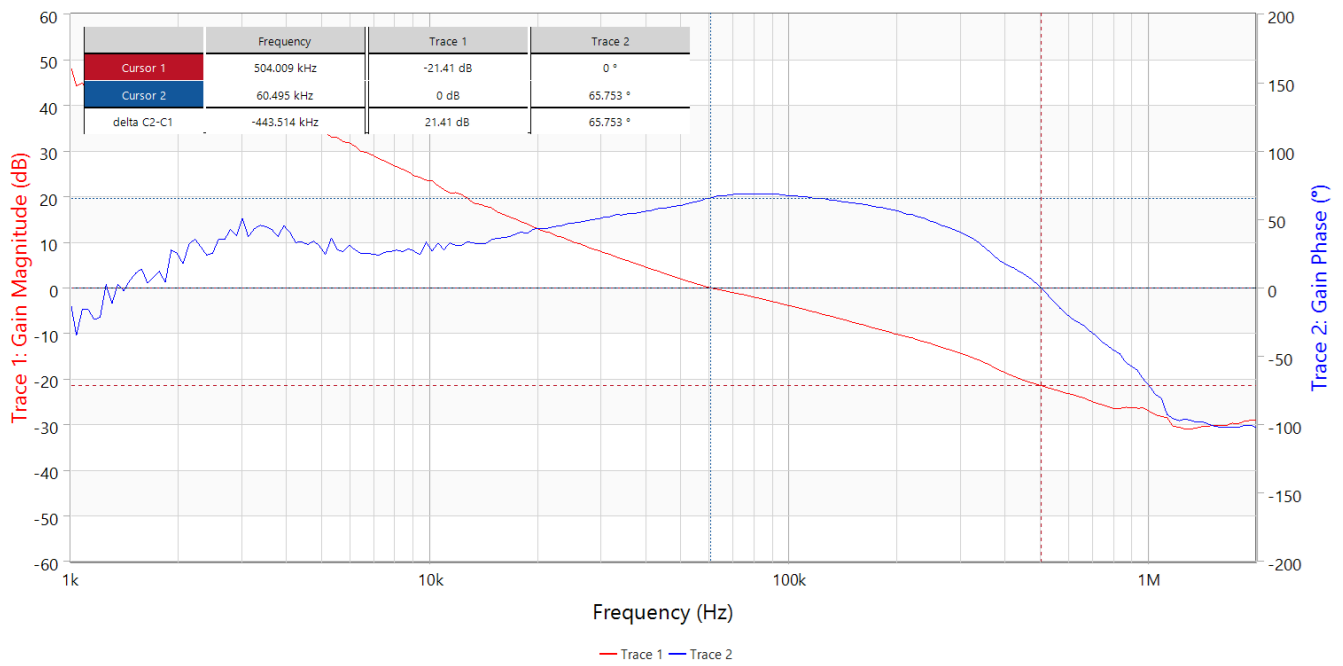


Figure 2-22. Bode Plot at 3.3 V_{IN}, 1.15 V_{OUT}, 3A I_{OUT}

3 Waveforms

3.1 Cold Crank

The cold crank waveform of the board is shown in the following figure by setting appropriate UVLO circuit.

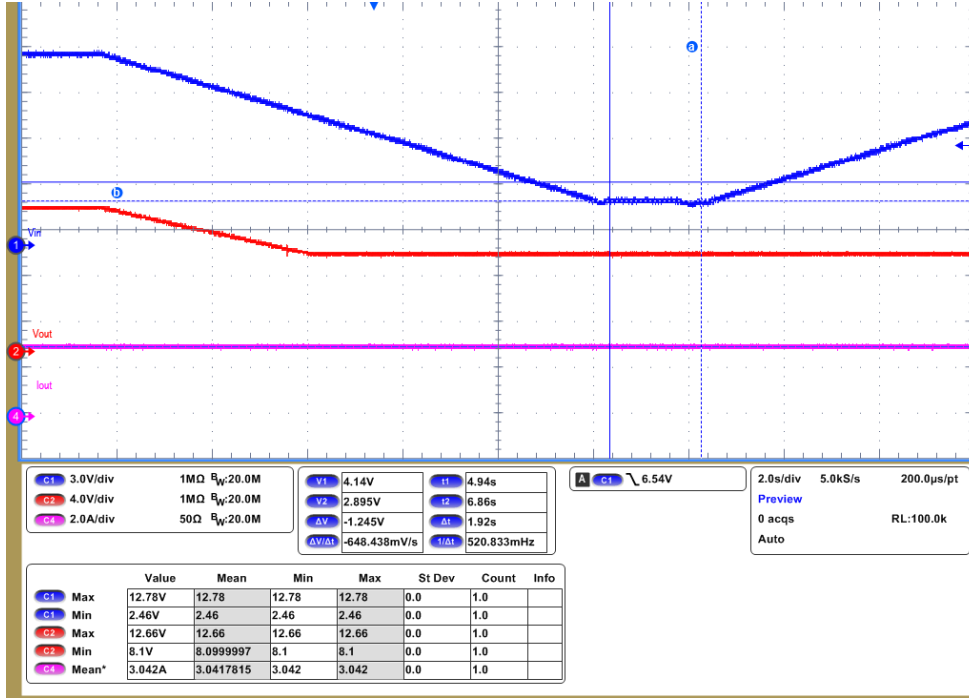


Figure 3-1. Cold Crank at 2.8V_{IN}, 8.5V_{OUT}, 3A I_{OUT}

3.2 Start-up

Start-up behaviors of the LM5152-Q1 are shown in the following figures.

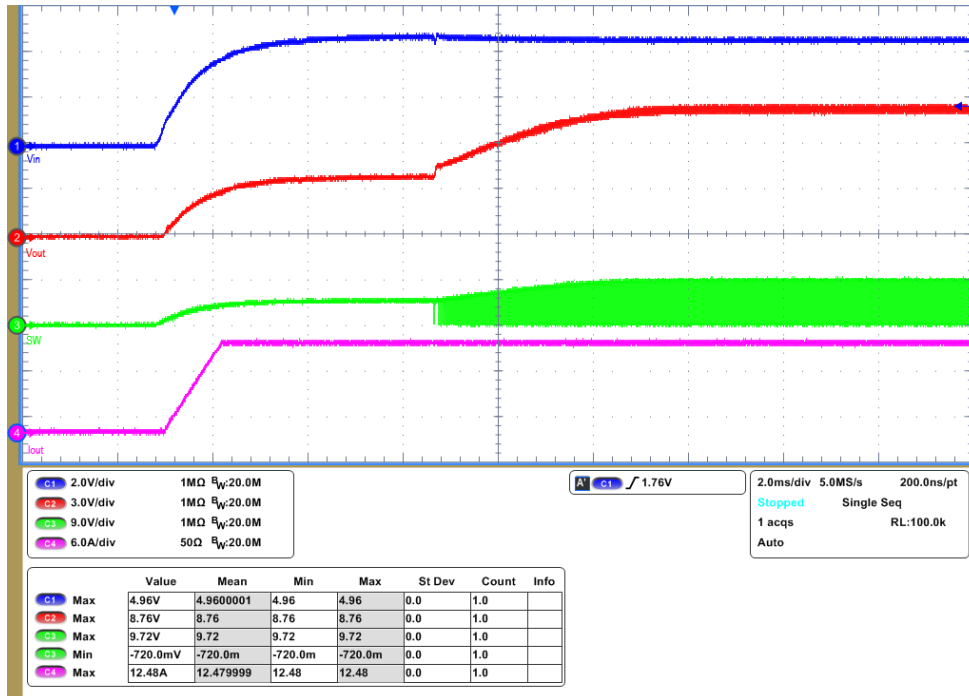


Figure 3-2. Start-up at 4.2 V_{IN}, 8.5 V_{OUT}, 11.76A I_{OUT}

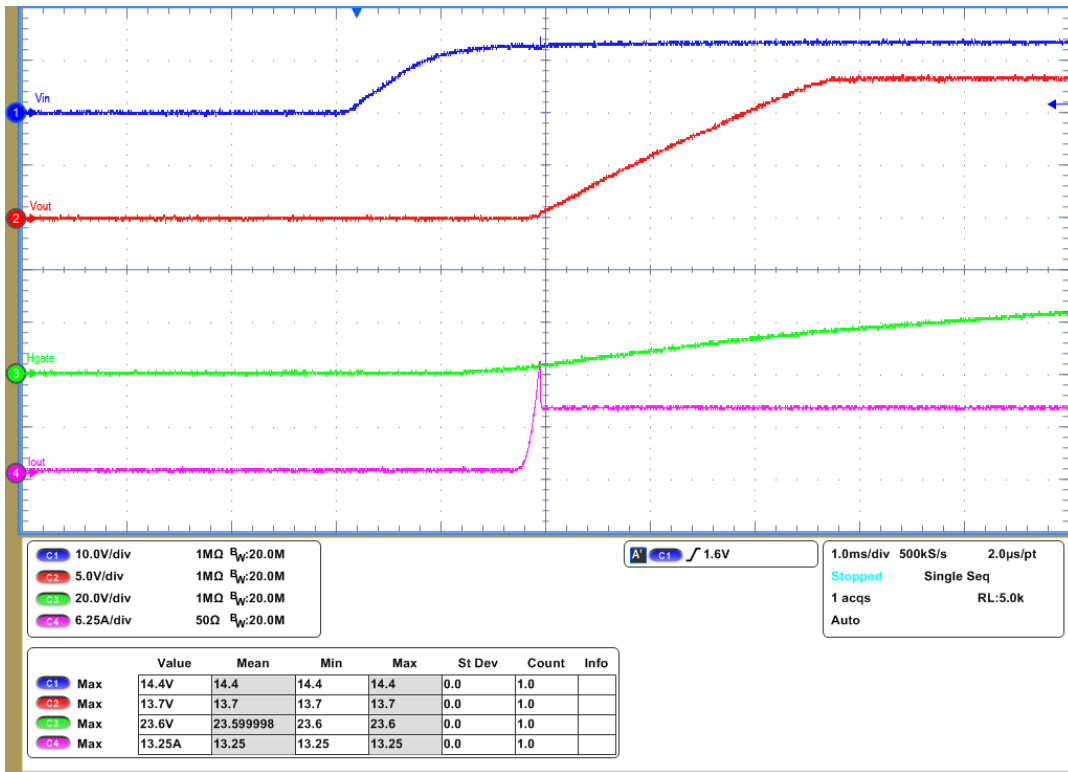


Figure 3-3. Start-up at 13.5 V_{IN}, 13.5 V_{OUT}, 7.48A I_{OUT}

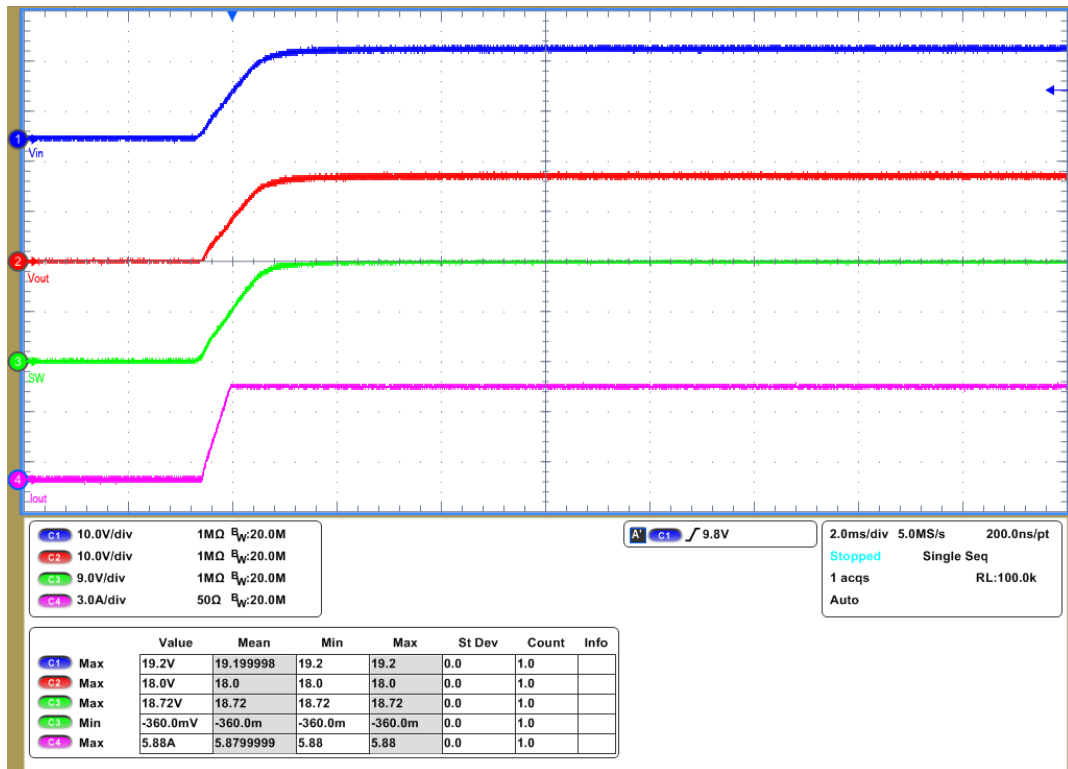


Figure 3-4. Start-up at 18 V_{IN}, 18 V_{OUT}, 5.55A I_{OUT}

Start-up behaviors of LM74900-Q1 are shown in the following figures.

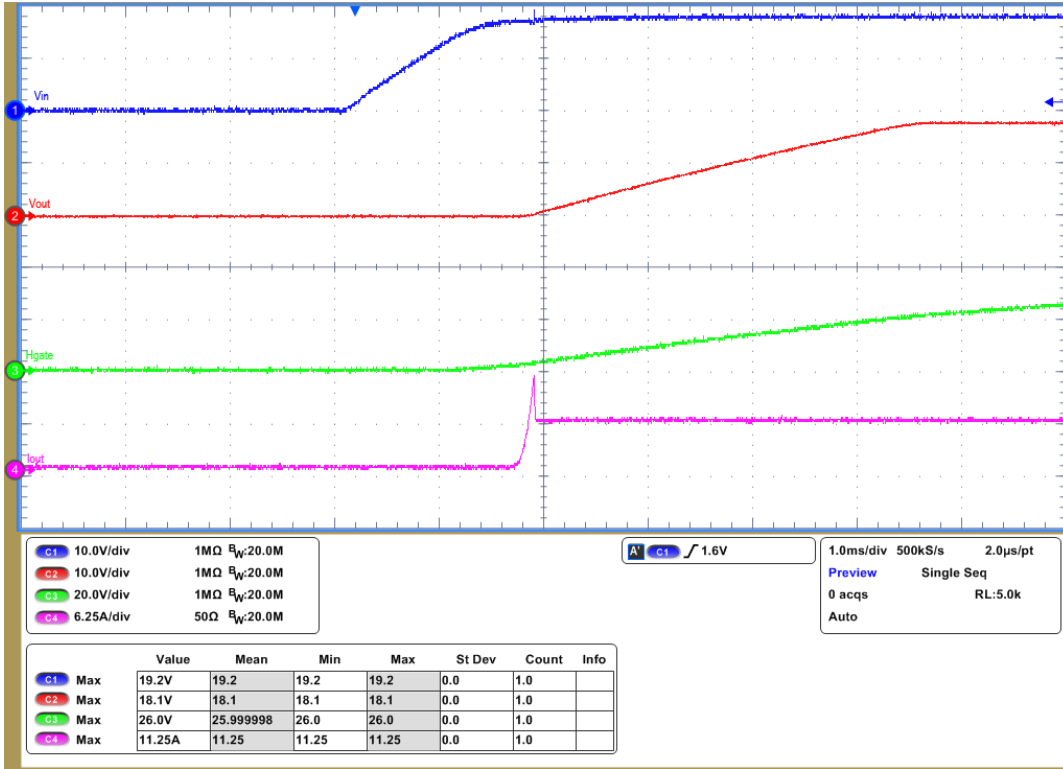


Figure 3-5. Start-up at 18 V_{IN}, 18 V_{OUT}, 5.78A I_{OUT}

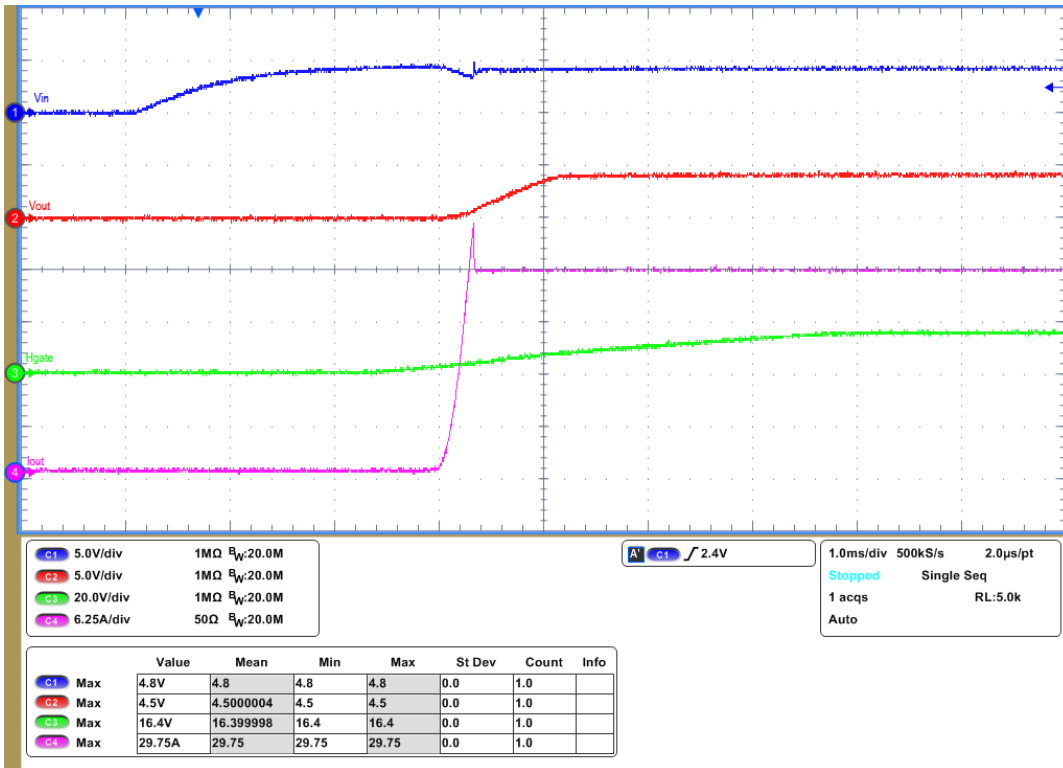


Figure 3-6. Start-up at 4.2 V_{IN}, 4.2 V_{OUT}, 24A I_{OUT}

Start-up behaviors of LMQ644A2-Q1 are shown in the following figures.

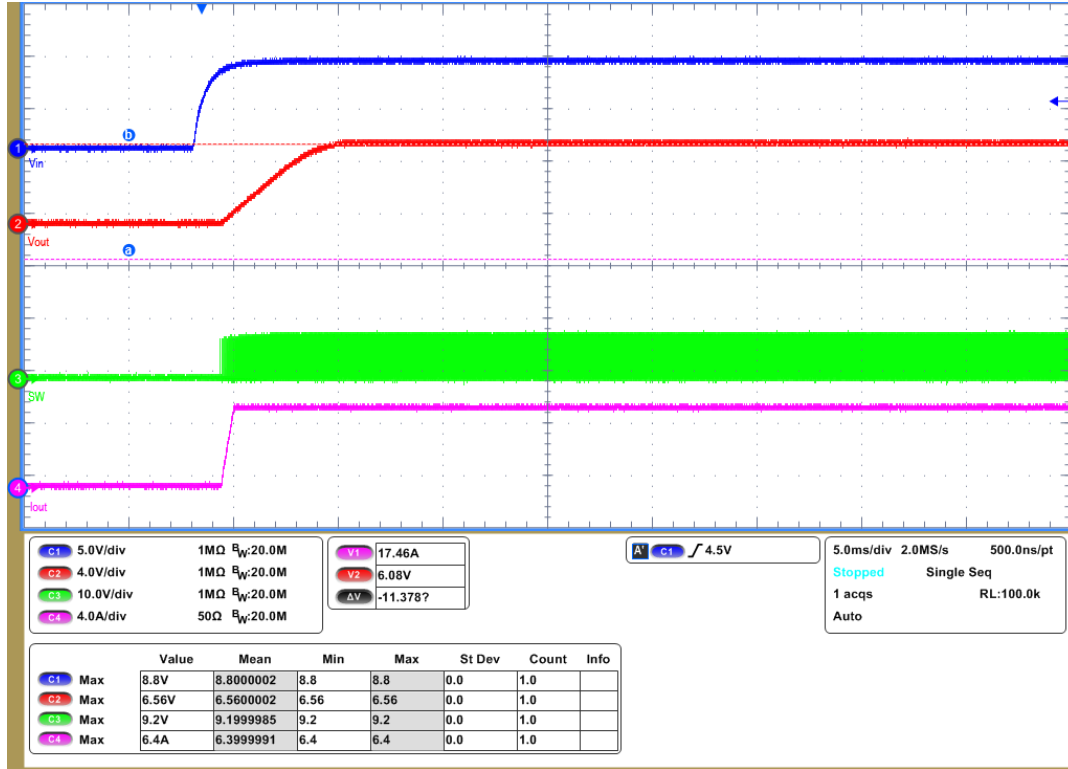


Figure 3-7. Start-up at 8.5 V_{IN}, 6 V_{OUT}, 6A I_{OUT}

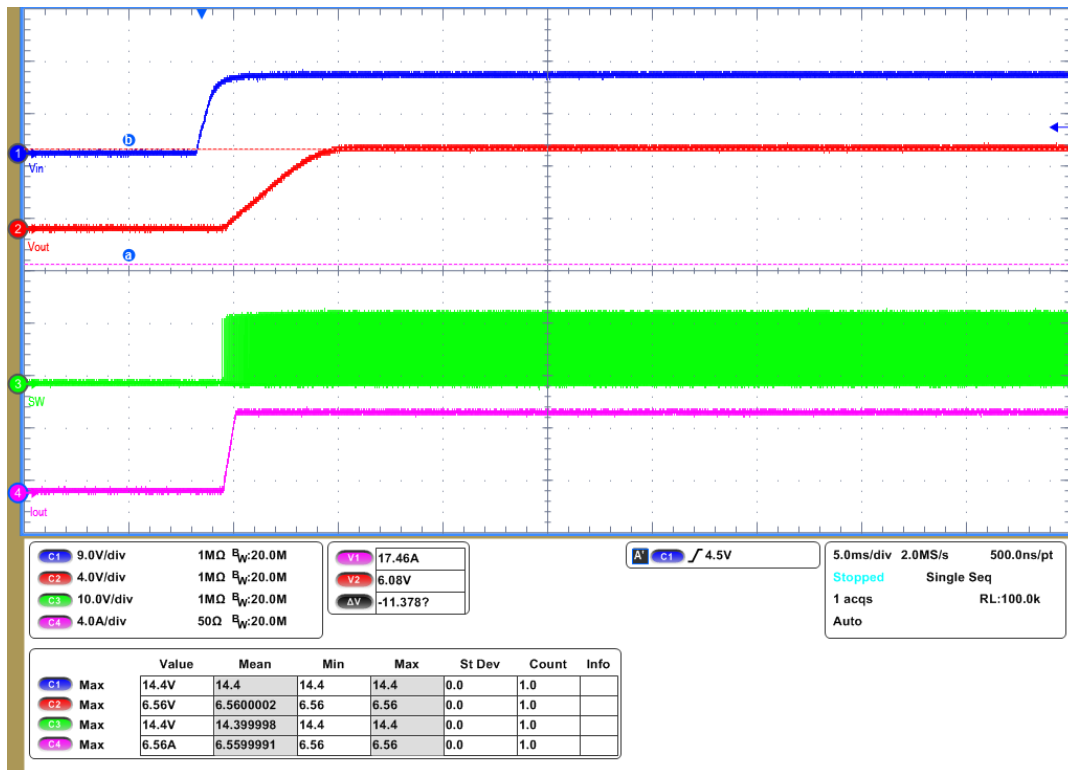


Figure 3-8. Start-up at 13.5 V_{IN}, 6 V_{OUT}, 6A I_{OUT}

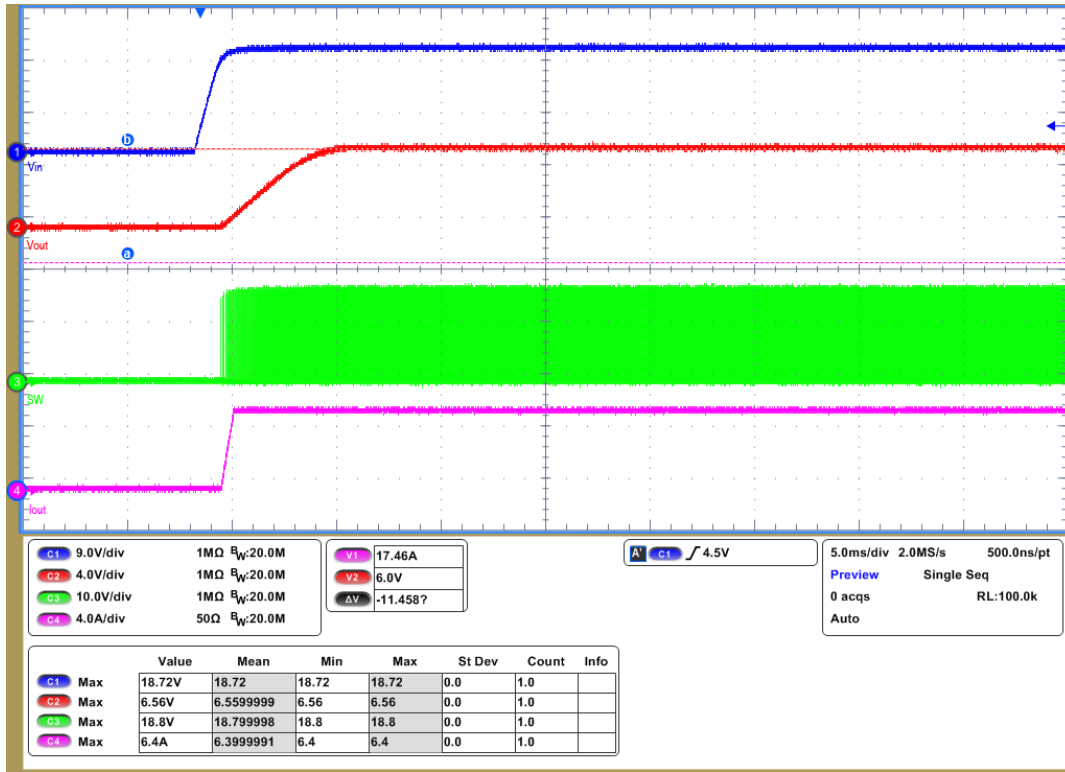


Figure 3-9. Start-up at 18 V_{IN}, 6 V_{OUT}, 6 A I_{OUT}

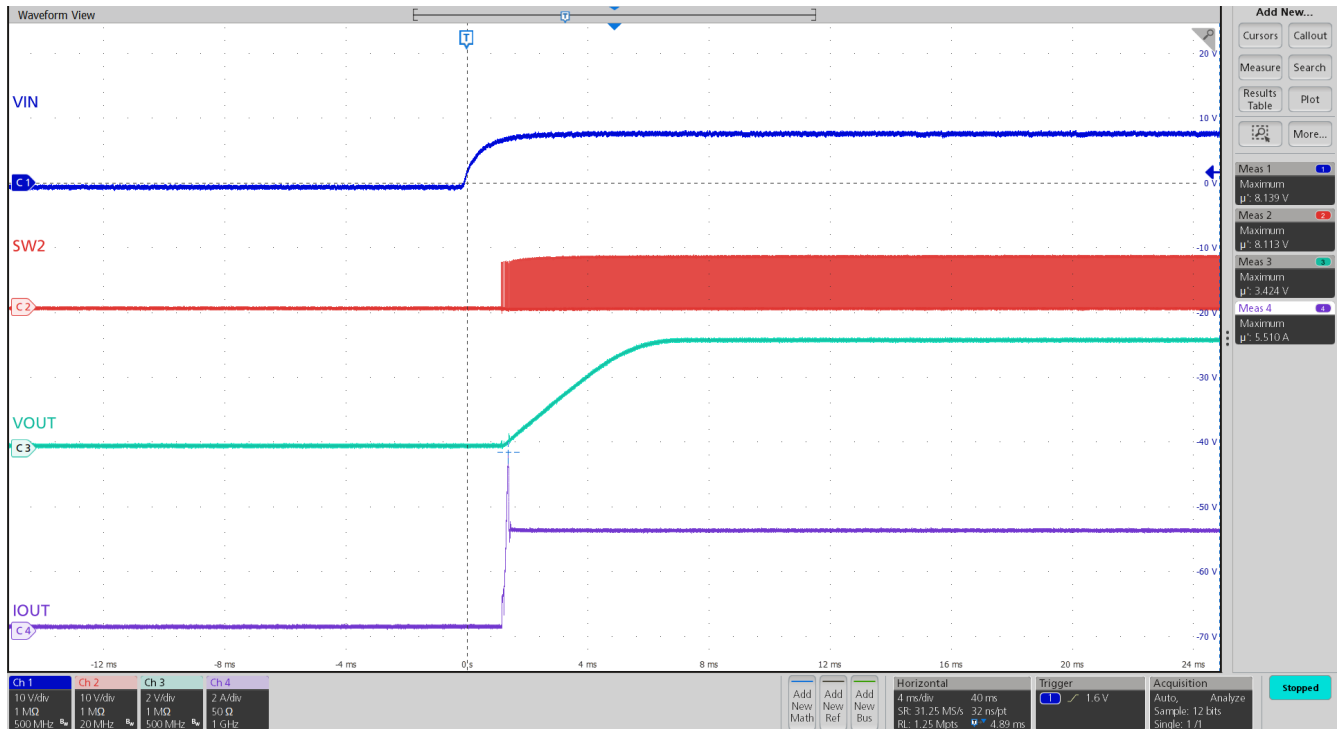


Figure 3-10. Start-up at 8.5 V_{IN}, 3.3 V_{OUT}, 3 A I_{OUT}

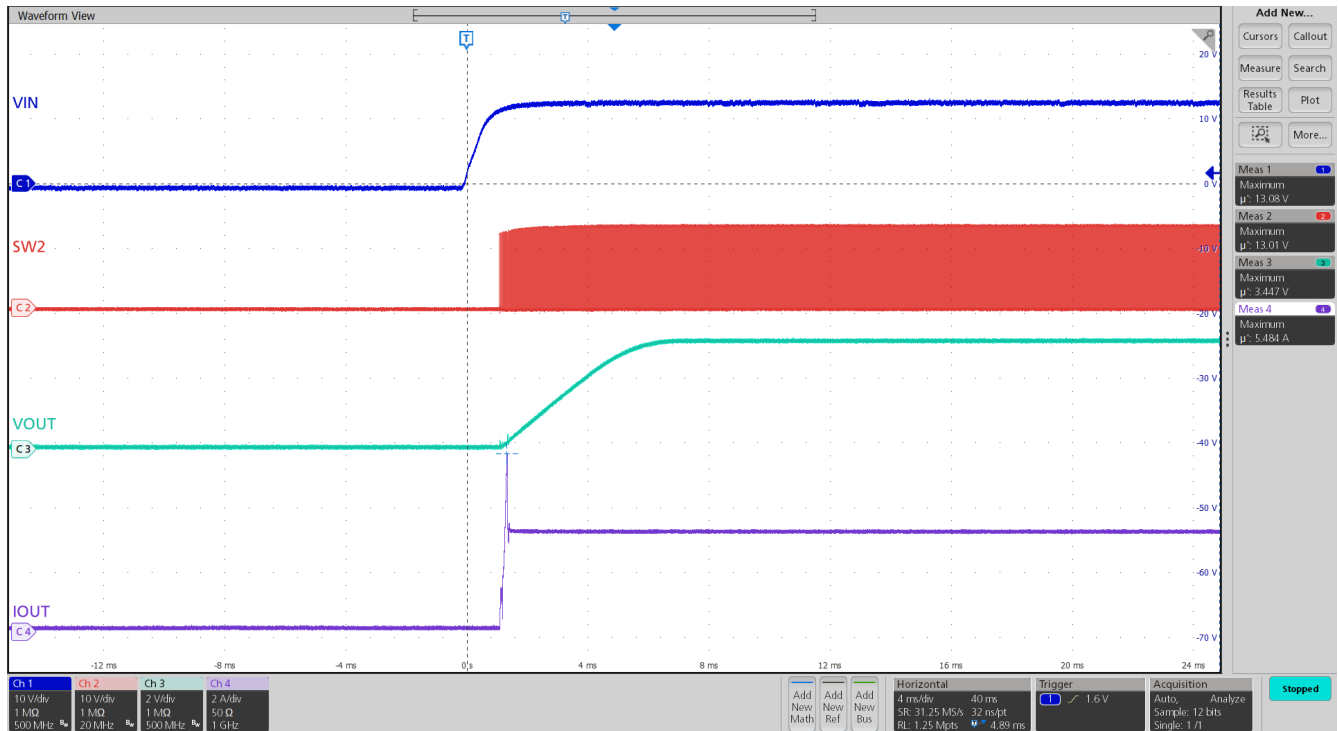


Figure 3-11. Start-up at 13.5 V_{IN}, 3.3 V_{OUT}, 3A I_{OUT}

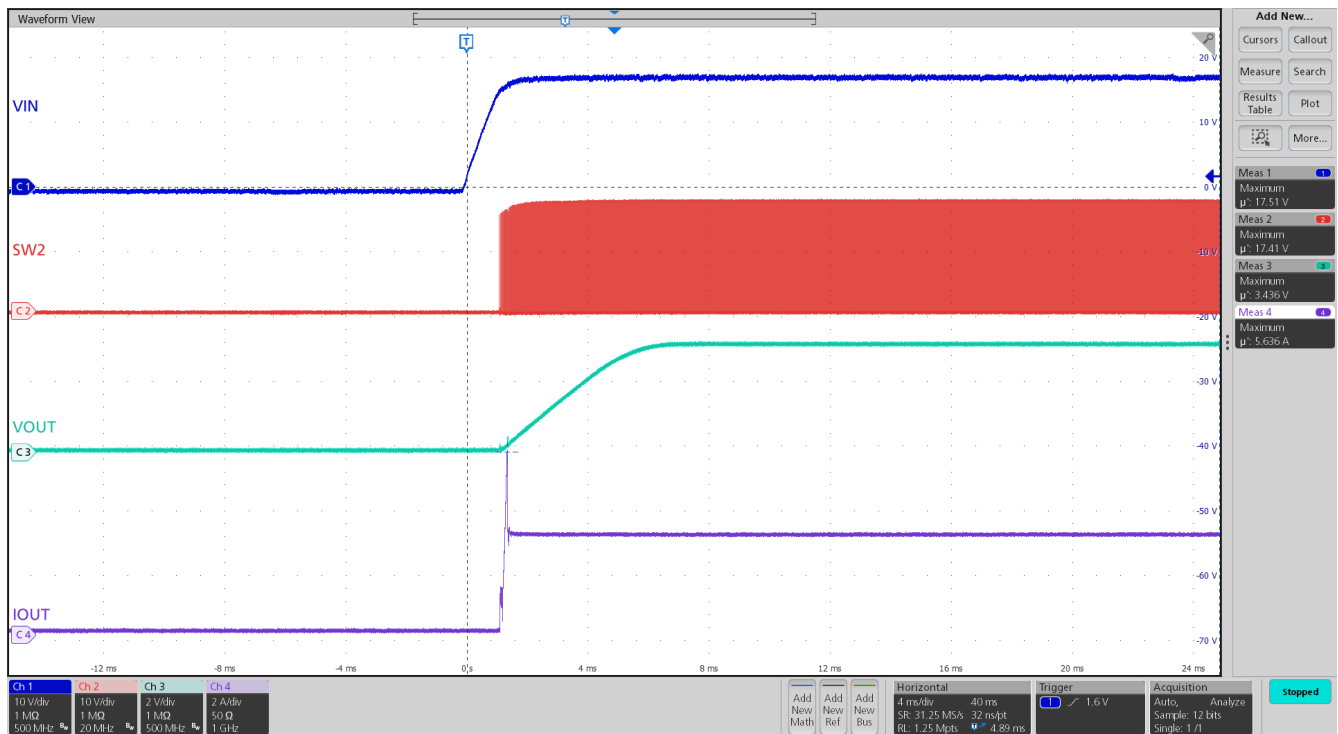


Figure 3-12. Start-up at 18 V_{IN}, 3.3 V_{OUT}, 3A I_{OUT}

Start-up behaviors of TPS7B81-Q1 are shown in the following figures.

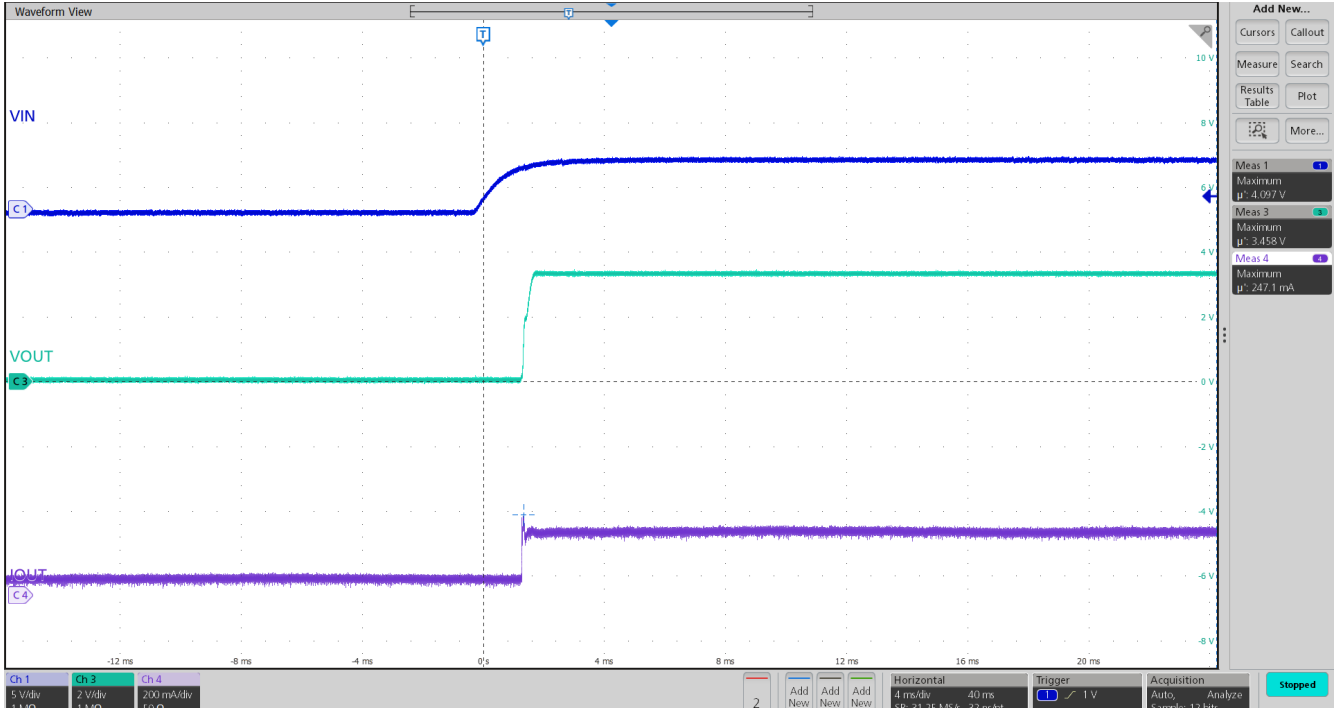


Figure 3-13. Start-up at 4.2 V_{IN}, 6 V_{OUT}, 0.15A I_{OUT}

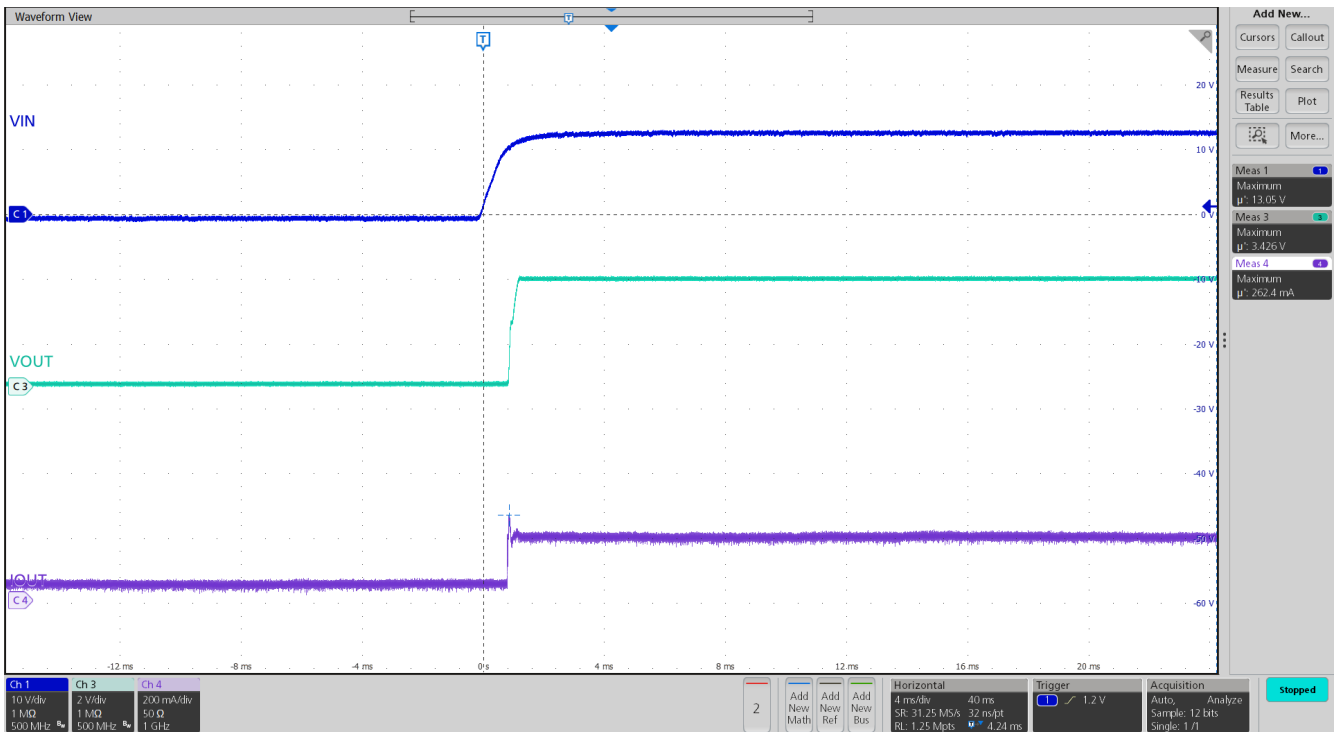


Figure 3-14. Start-up at 13.5 V_{IN}, 6 V_{OUT}, 0.15A I_{OUT}

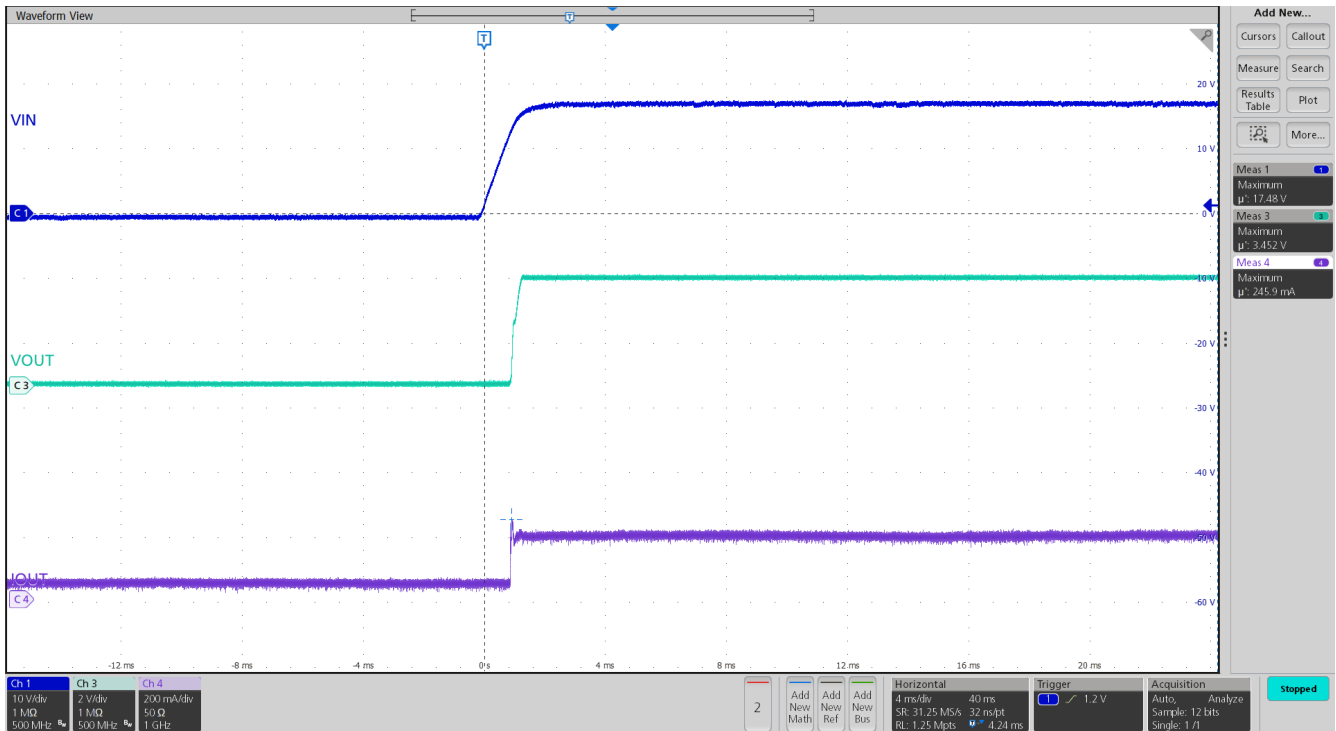


Figure 3-15. Start-up at 18 V_{IN}, 6 V_{OUT}, 0.15A I_{OUT}

Start-up behaviors of TPS745-Q1 are shown in the following figures.

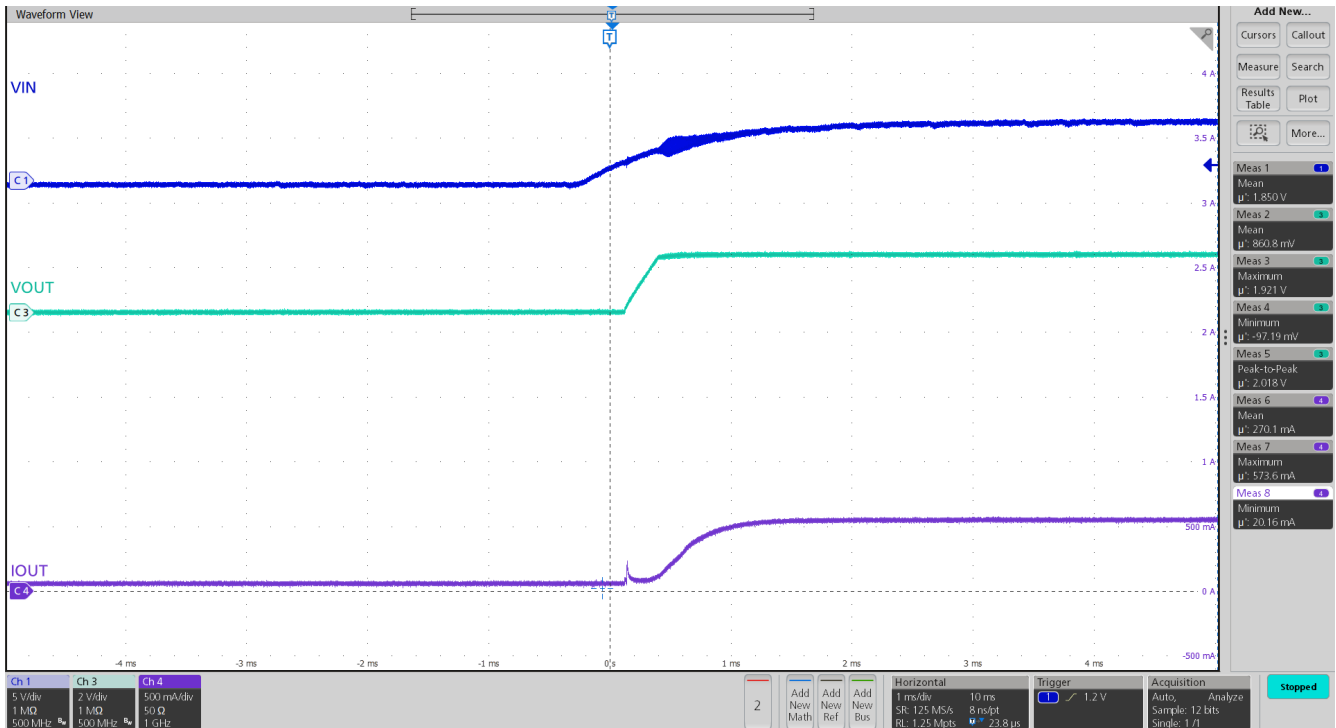


Figure 3-16. Start-up at 3.3 V_{IN}, 1.8 V_{OUT}, 0.5A I_{OUT}

Start-up behaviors of the TPS628503-Q1 are shown in the following figures.

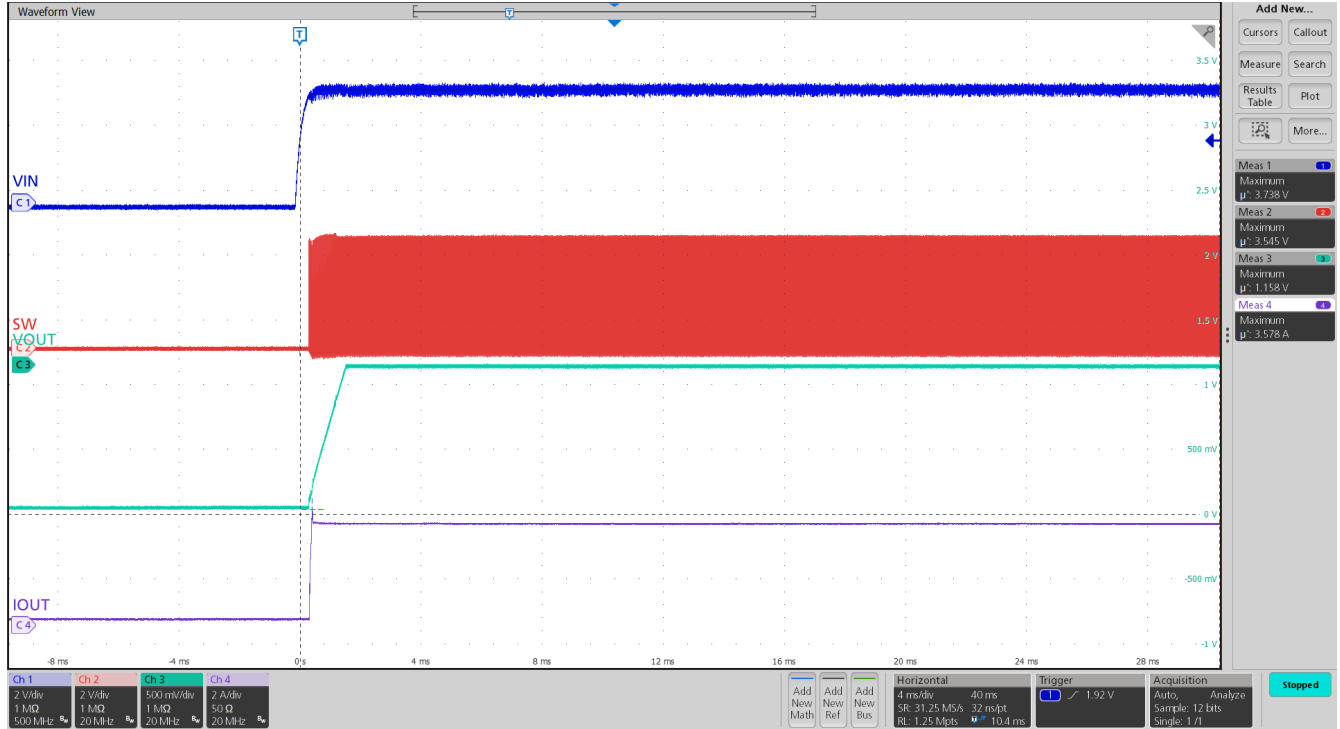


Figure 3-17. Start-up at 3.3 V_{IN}, 1.8 V_{OUT}, 3A I_{OUT}

3.3 Steady State

Steady state waveforms of LM5152-Q1 are shown in the following figures.

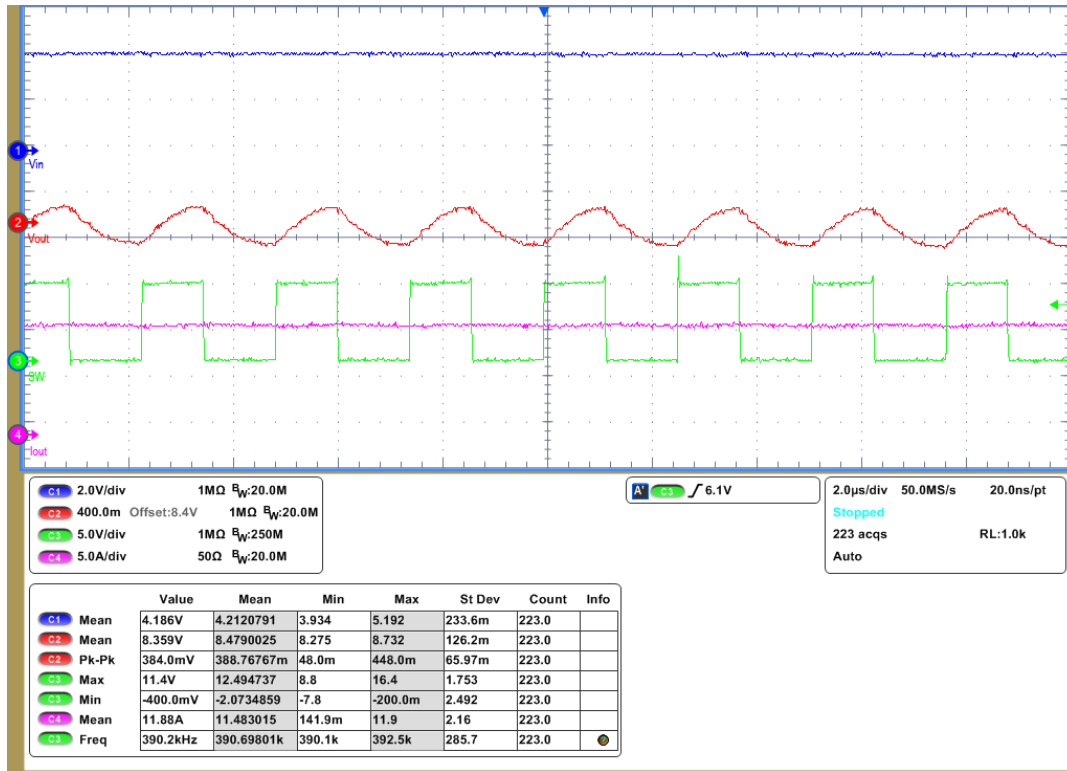


Figure 3-18. Steady State at 4.2 V_{IN} , 8.5 V_{OUT} , 11.76A I_{OUT}

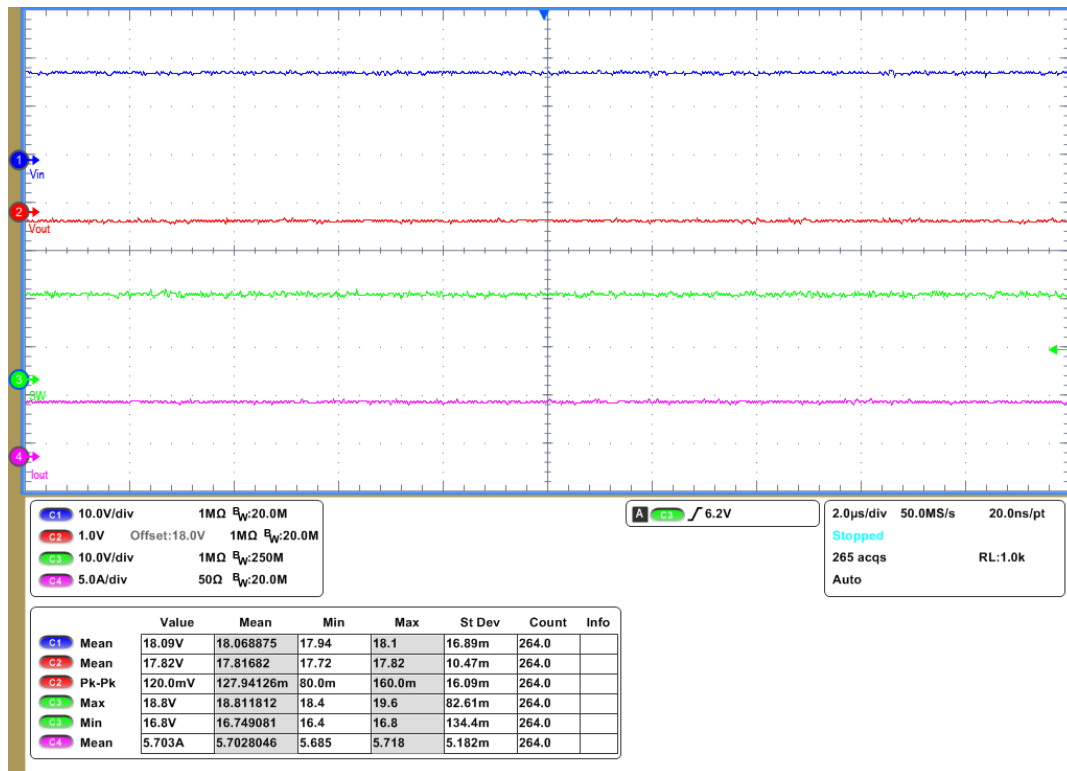


Figure 3-19. Steady State at 18 V_{IN} , 18 V_{OUT} , 5.5A I_{OUT}

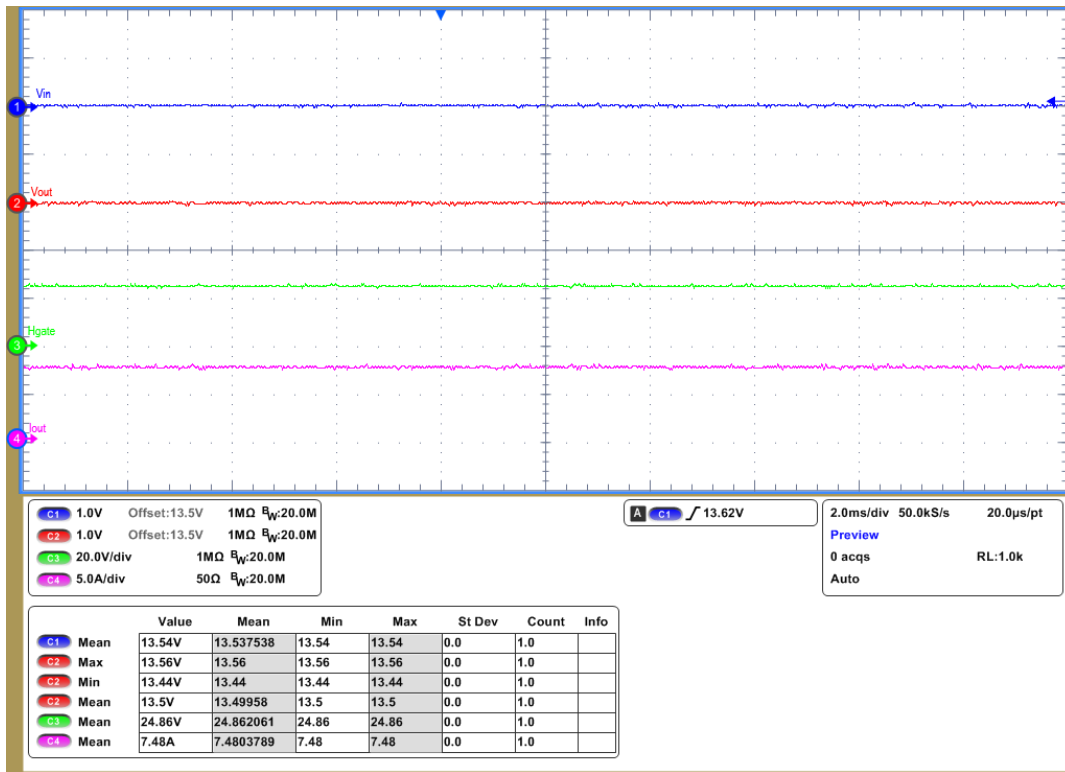


Figure 3-20. Steady State at 13.5 V_{IN}, 13.5 V_{OUT}, 7.48A I_{OUT}

Steady state waveforms of LM74900-Q1 are shown in the following figures.

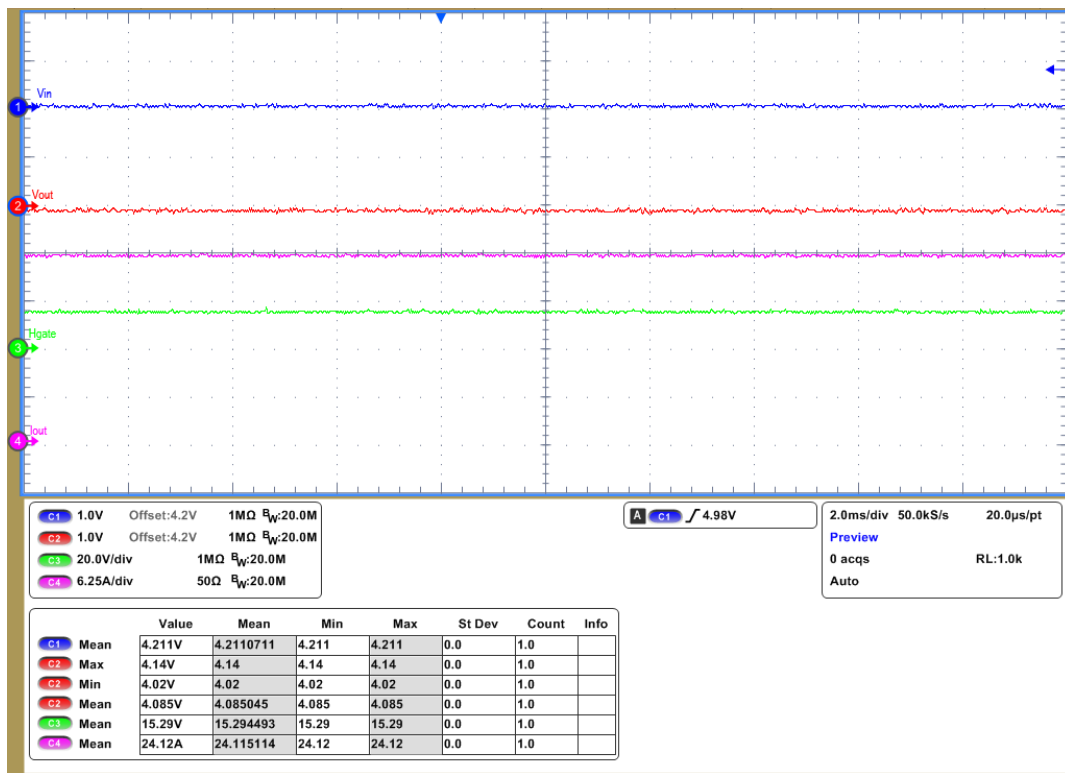


Figure 3-21. Steady State at 4.2 V_{IN}, 4.2 V_{OUT}, 24A I_{OUT}

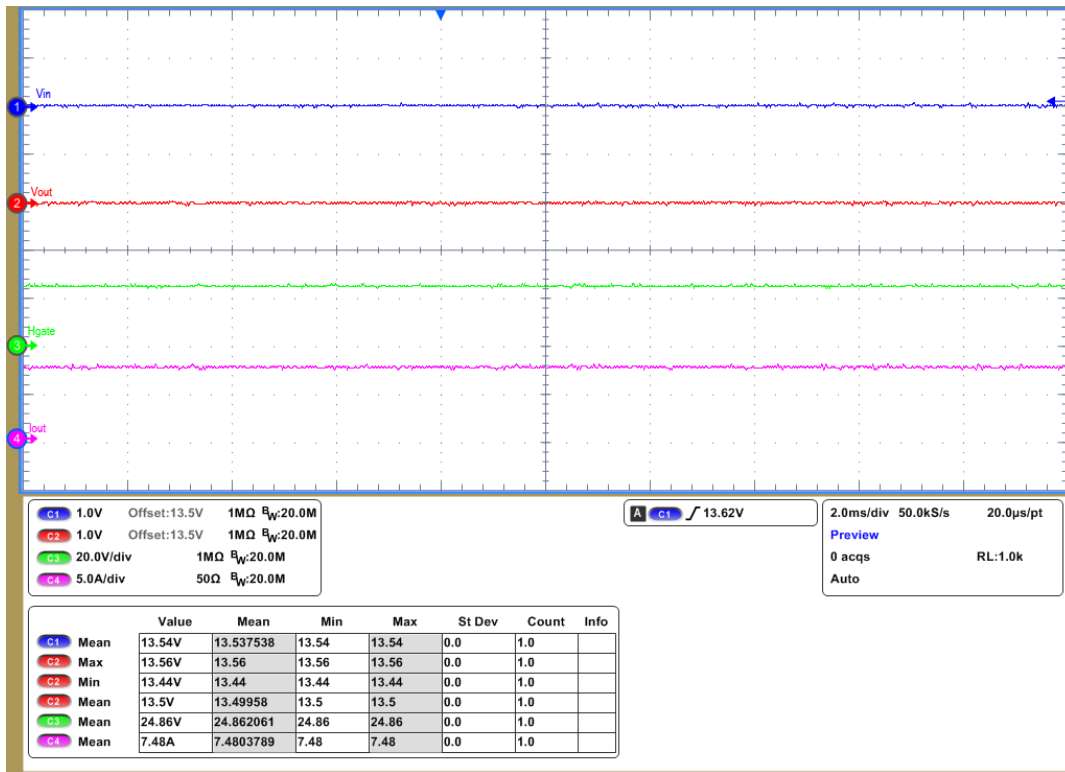


Figure 3-22. Steady State at 13.5 V_{IN}, 13.5 V_{OUT}, 7.48A I_{OUT}

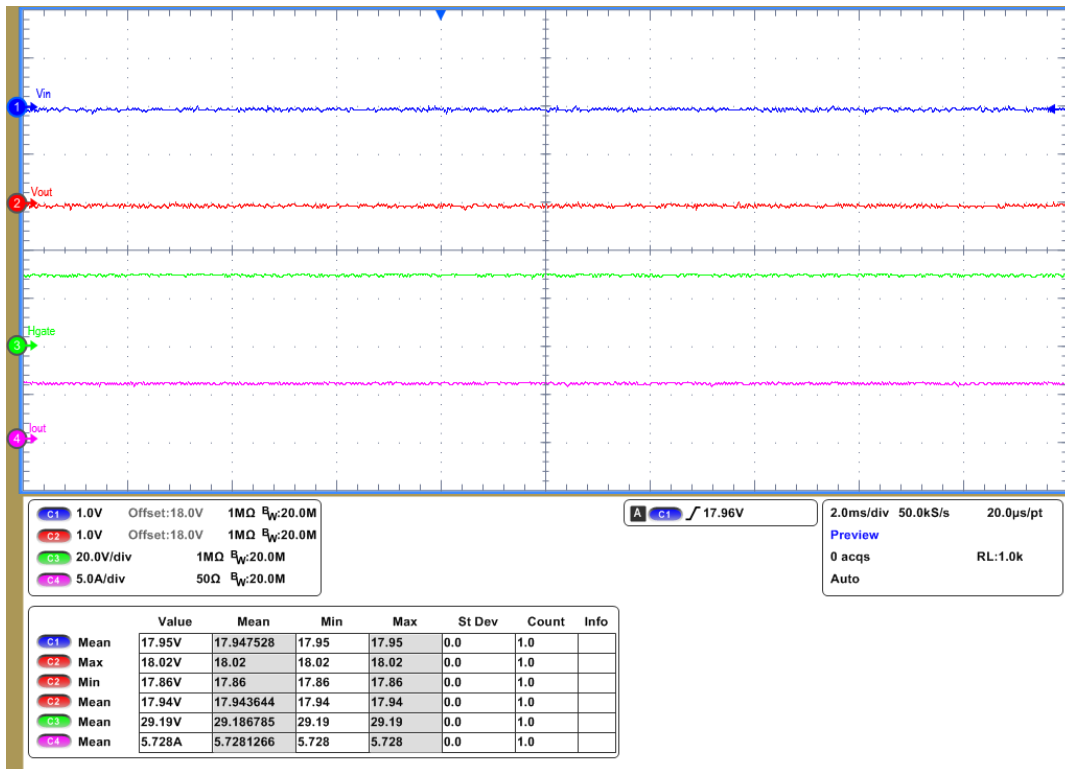


Figure 3-23. Steady State at 18 V_{IN}, 18 V_{OUT}, 5.5A I_{OUT}

Steady state waveforms of LMQ644A2-Q1 are shown in the following figures.

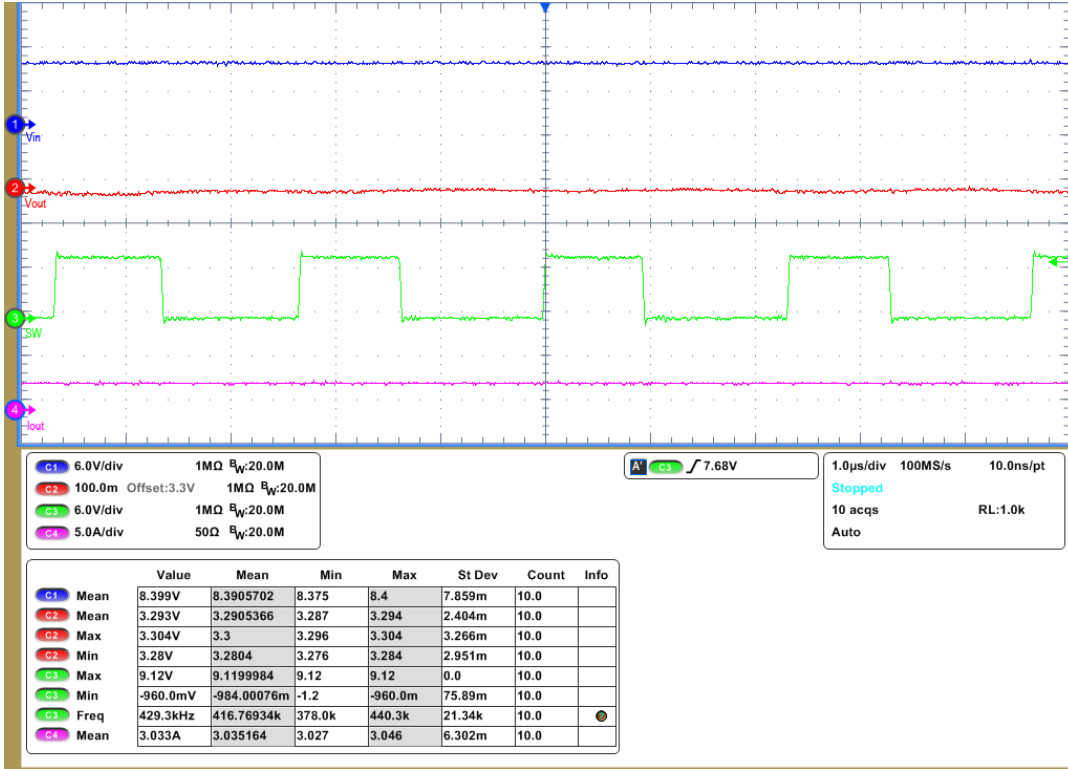


Figure 3-24. Steady State at 8.5 V_{IN}, 3.3 V_{OUT}, 3A I_{OUT}

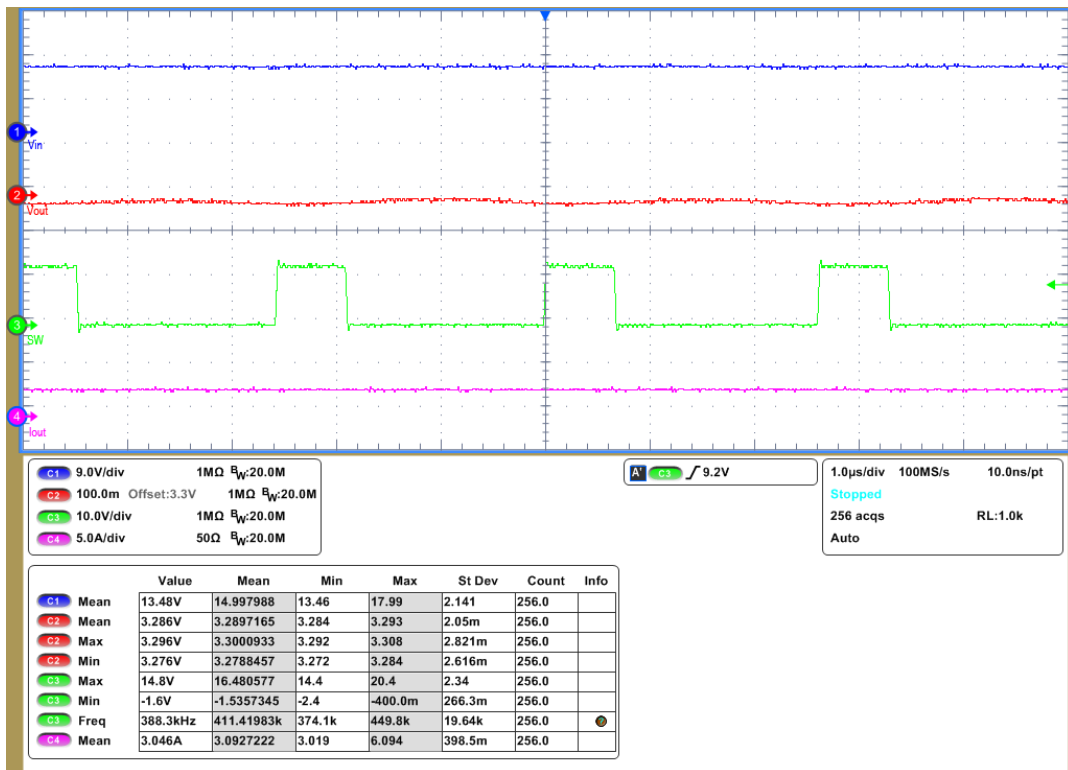


Figure 3-25. Steady State at 13.5 V_{IN}, 3.3 V_{OUT}, 3A I_{OUT}

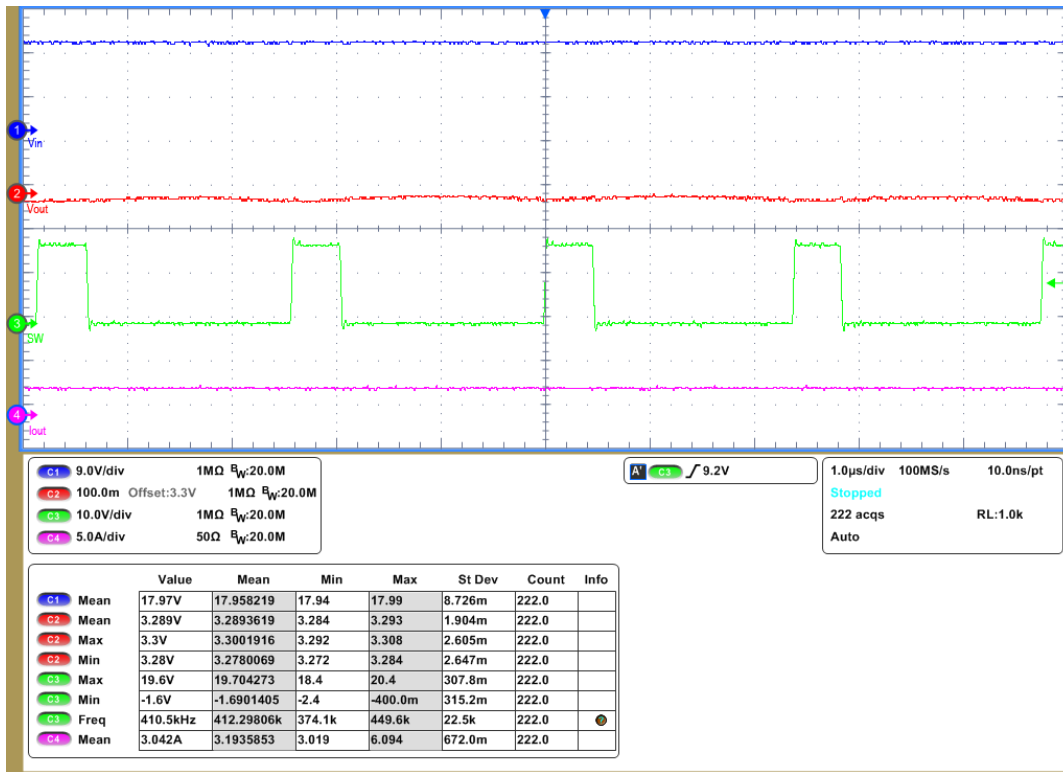


Figure 3-26. Steady State at 18 V_{IN}, 3.3 V_{OUT}, 3A I_{OUT}

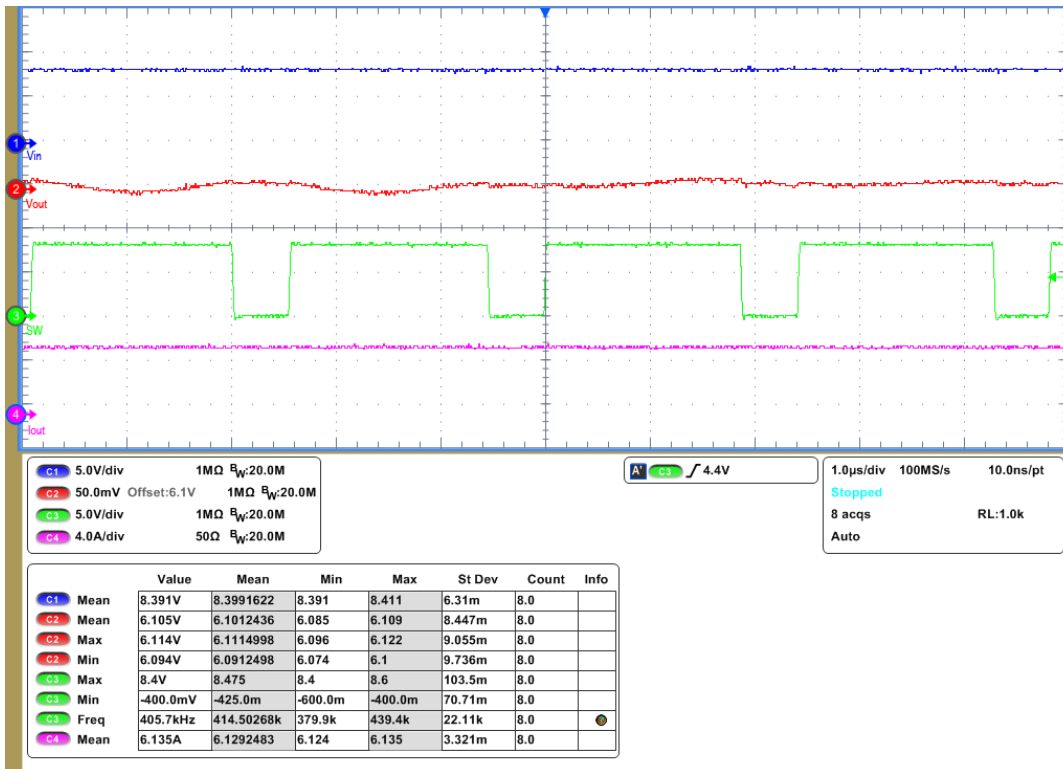


Figure 3-27. Steady State at 8.5 V_{IN}, 6 V_{OUT}, 6.13A I_{OUT}

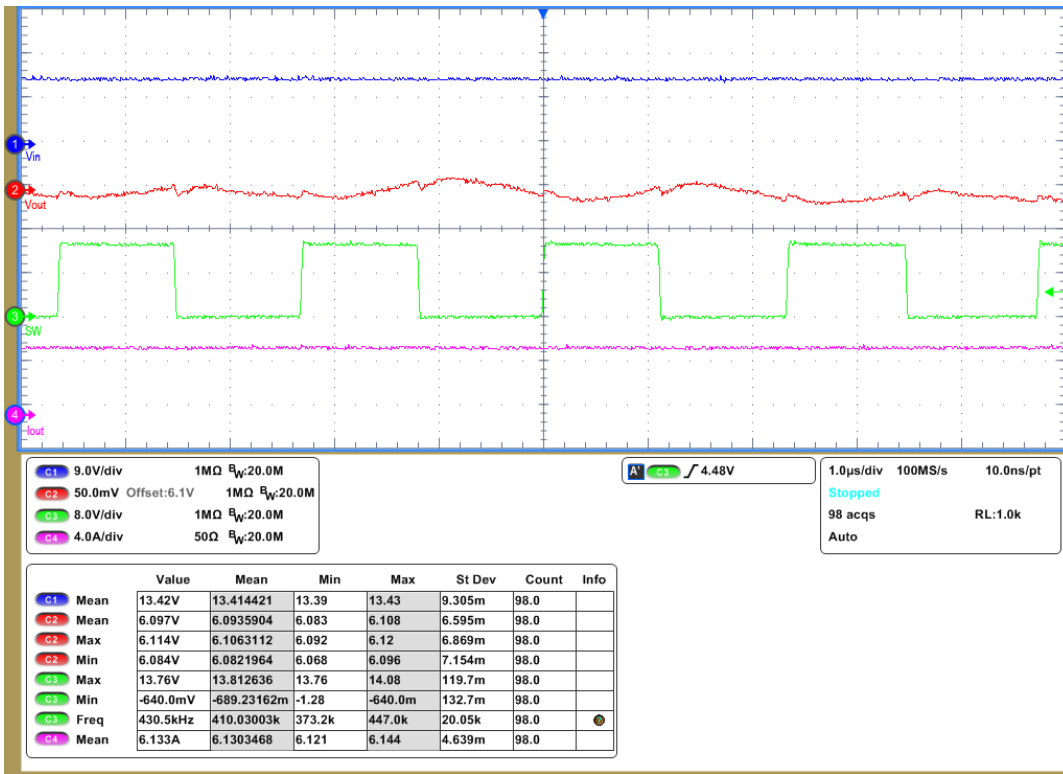


Figure 3-28. Steady State at 13.5 V_{IN}, 6 V_{OUT}, 6.13A I_{OUT}

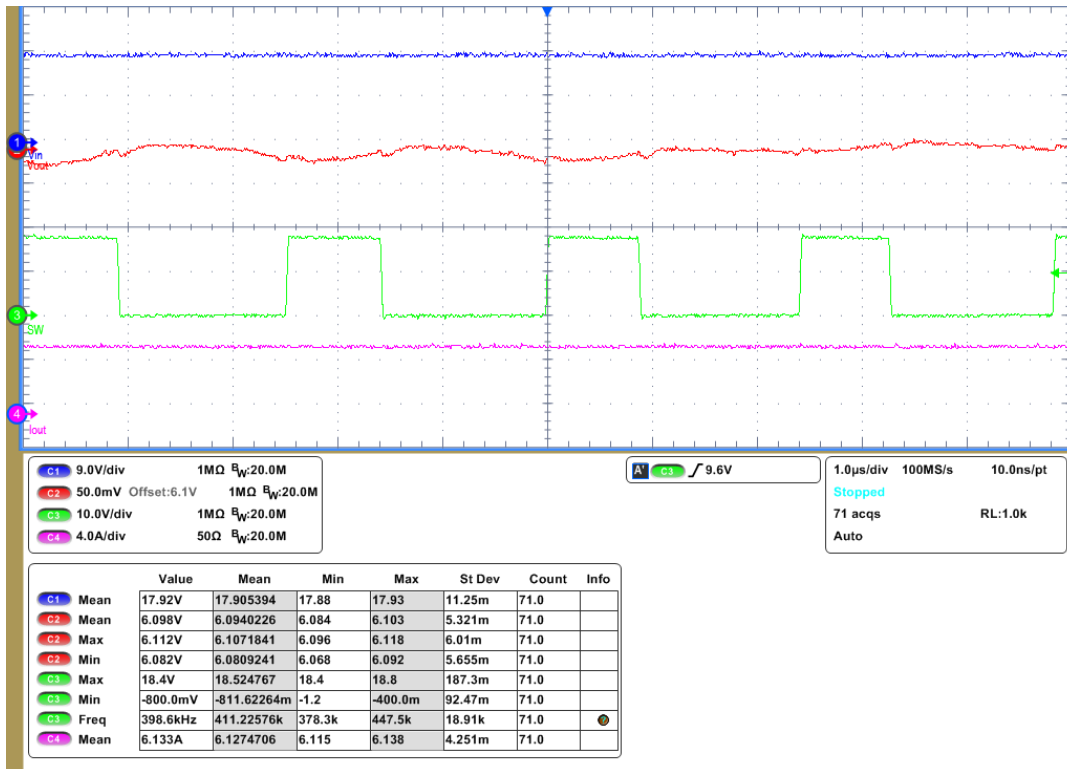


Figure 3-29. Steady State at 18 V_{IN}, 6 V_{OUT}, 6.13A I_{OUT}

Steady state waveforms of TPS7B81-Q1 are shown in the following figures.

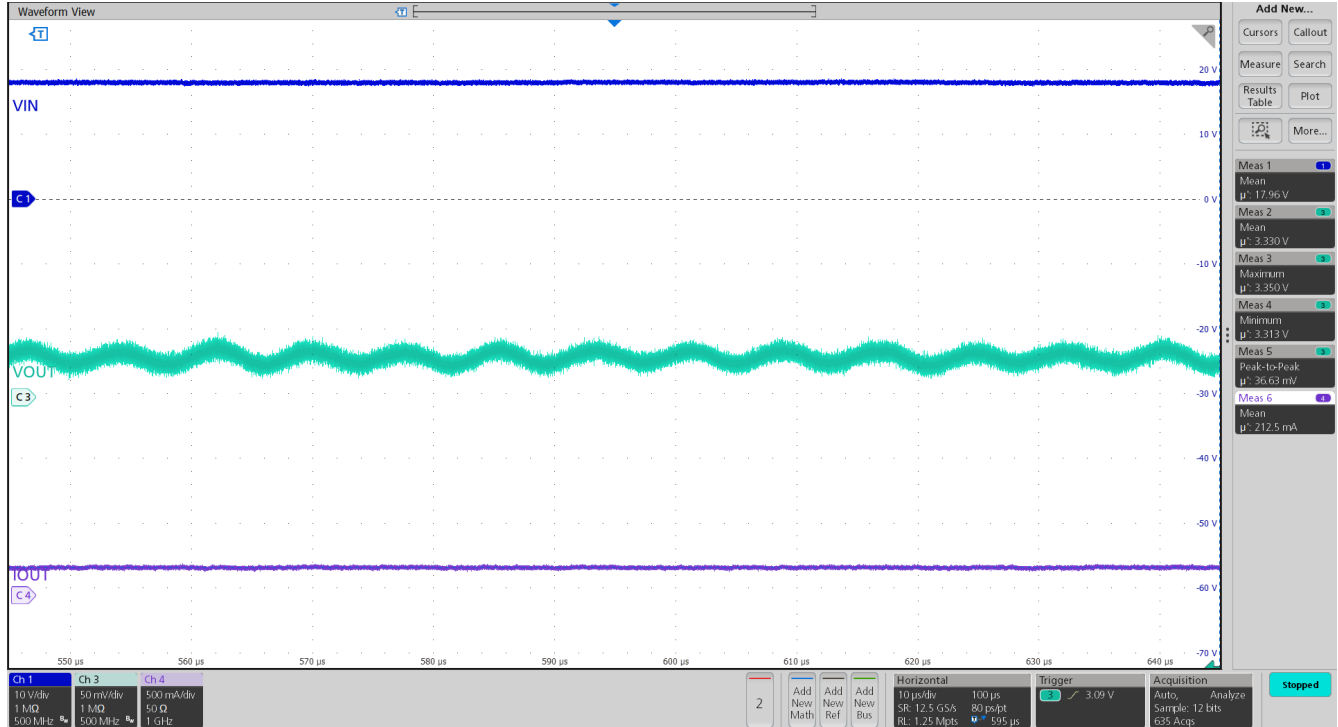


Figure 3-30. Steady State at 18 V_{IN}, 3.3 V_{OUT}, 0.15A I_{OUT}

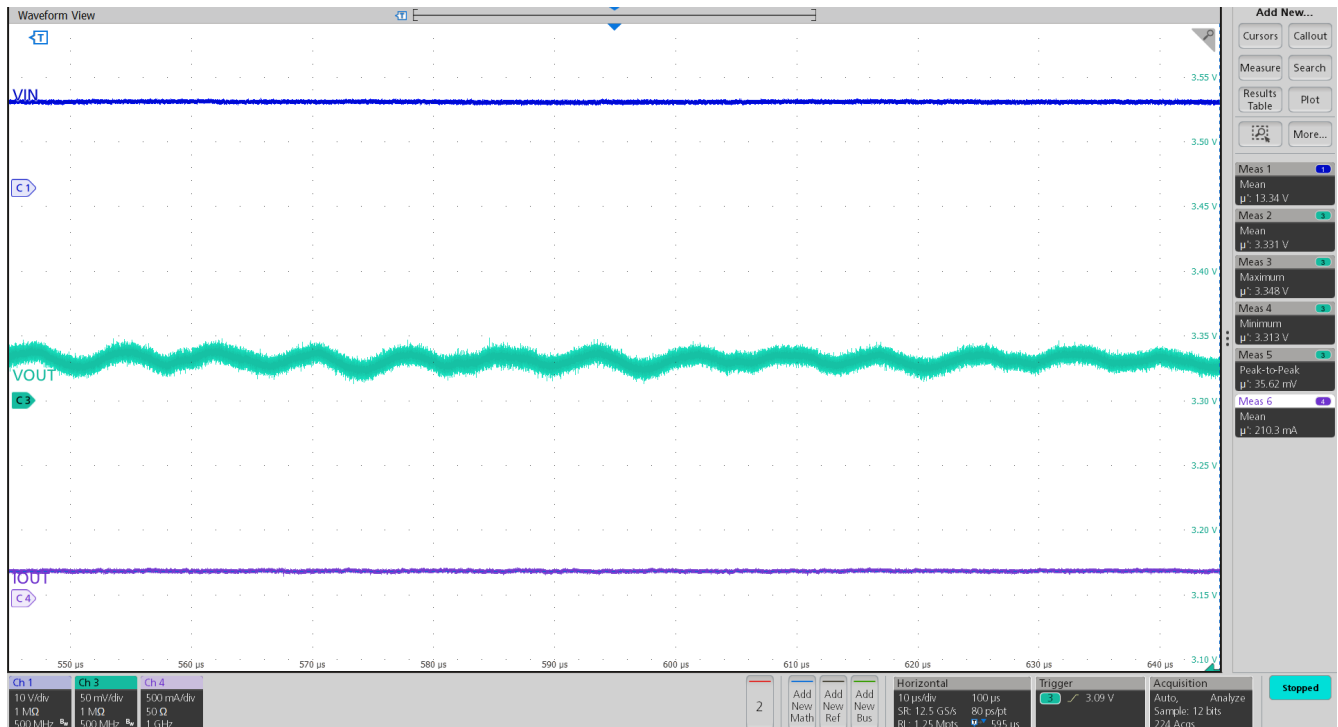


Figure 3-31. Steady State at 13.5 V_{IN}, 3.3 V_{OUT}, 0.15A I_{OUT}

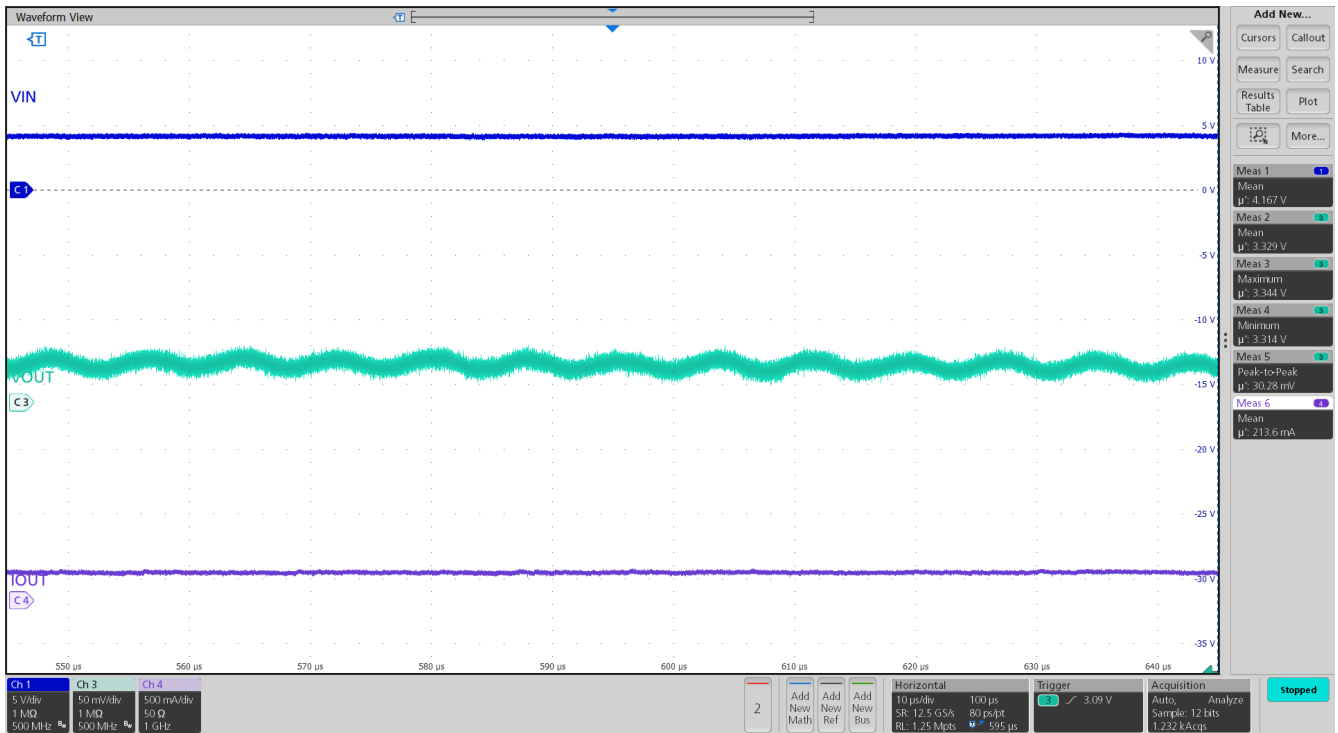


Figure 3-32. Steady State at 4.2 V_{IN}, 3.3 V_{OUT}, 0.15A I_{OUT}

Steady state waveforms of TPS745-Q1 are shown in the following figure.

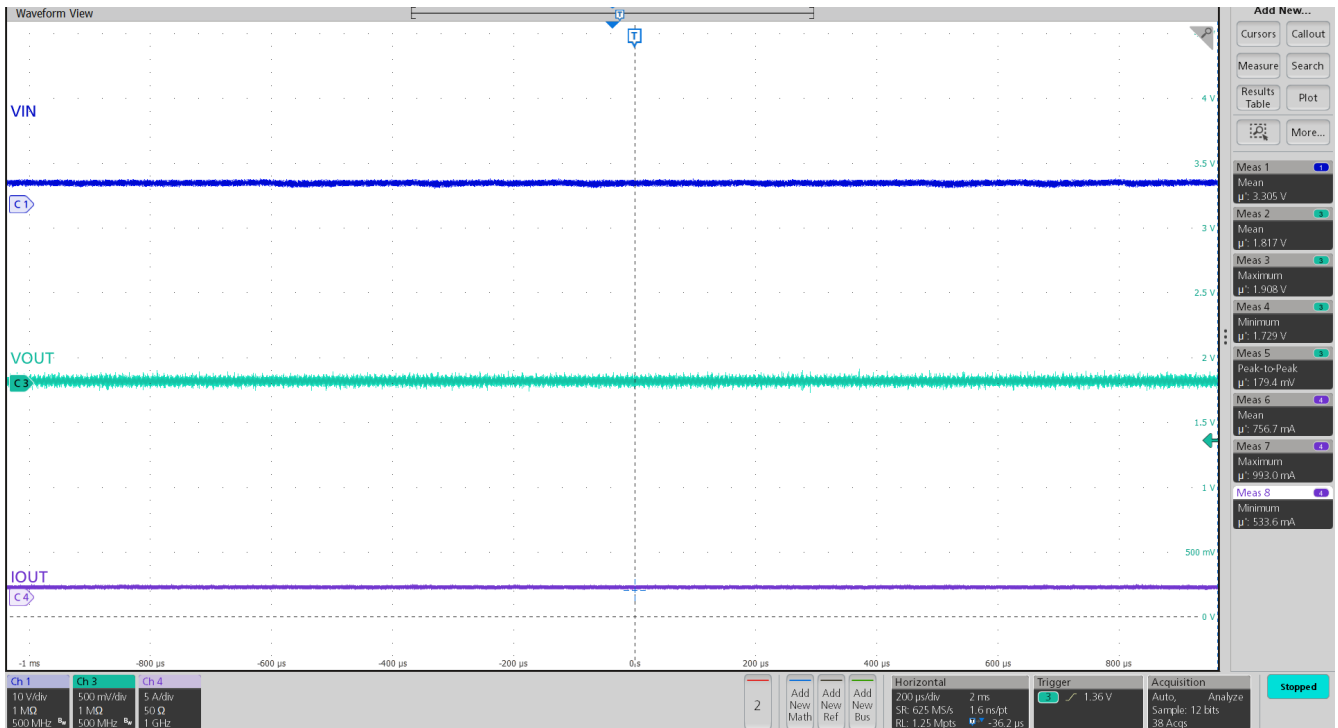


Figure 3-33. Steady State at 3.3 V_{IN}, 1.8 V_{OUT}, 0.5A I_{OUT}

Steady state waveforms of TPS628503-Q1 are shown in the following figure.

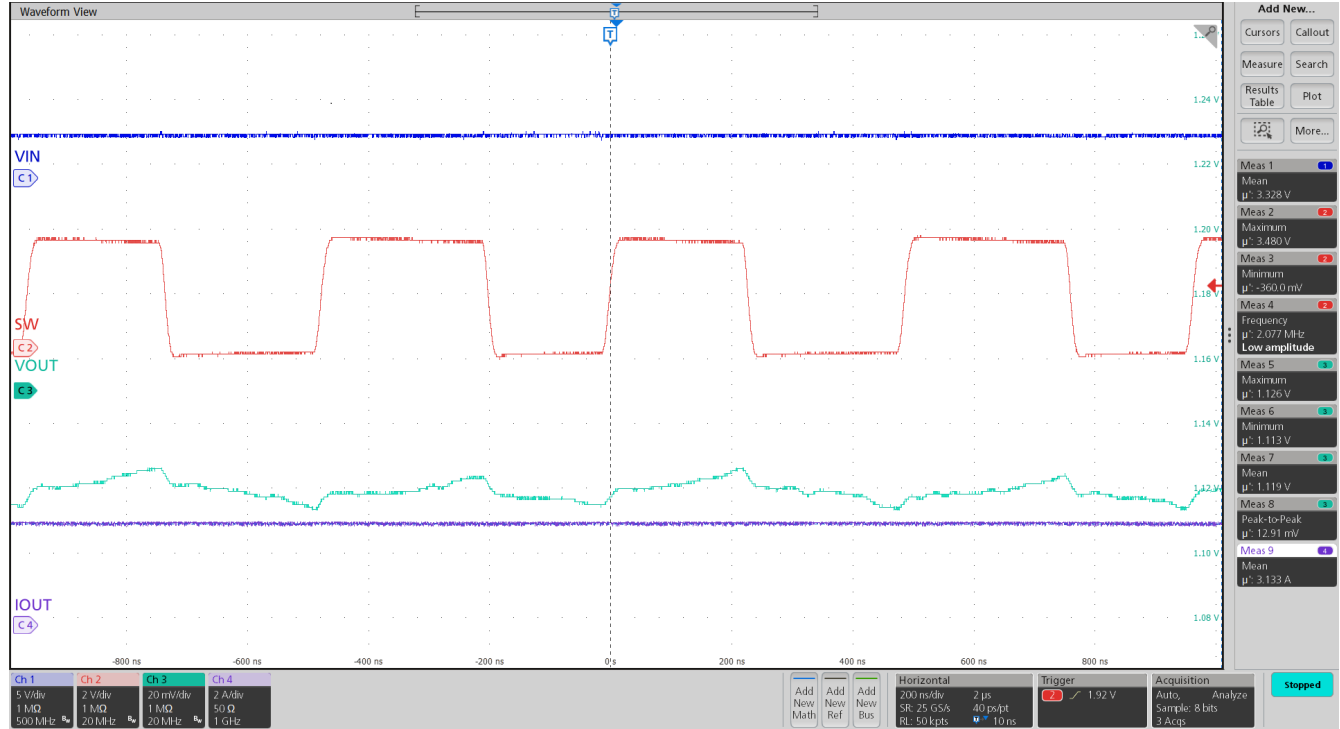


Figure 3-34. Steady State at 3.3 V_{IN}, 1.15 V_{OUT}, 3A I_{OUT}

3.4 Short-Circuit Protection

Short-circuit protection waveforms of LM74900-Q1 are shown in the following figure.

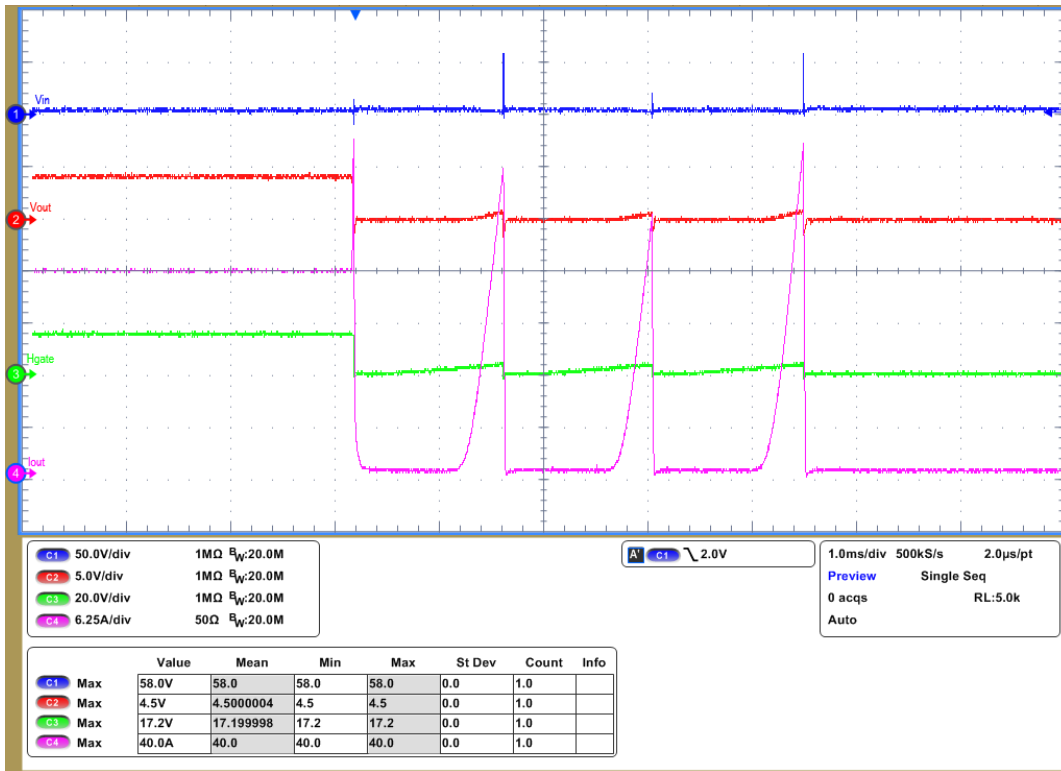


Figure 3-35. Short-Circuit Protection at 4.2 V_{IN}

Short-circuit protection waveforms of LMQ644A2-Q1 are shown in the following figures.

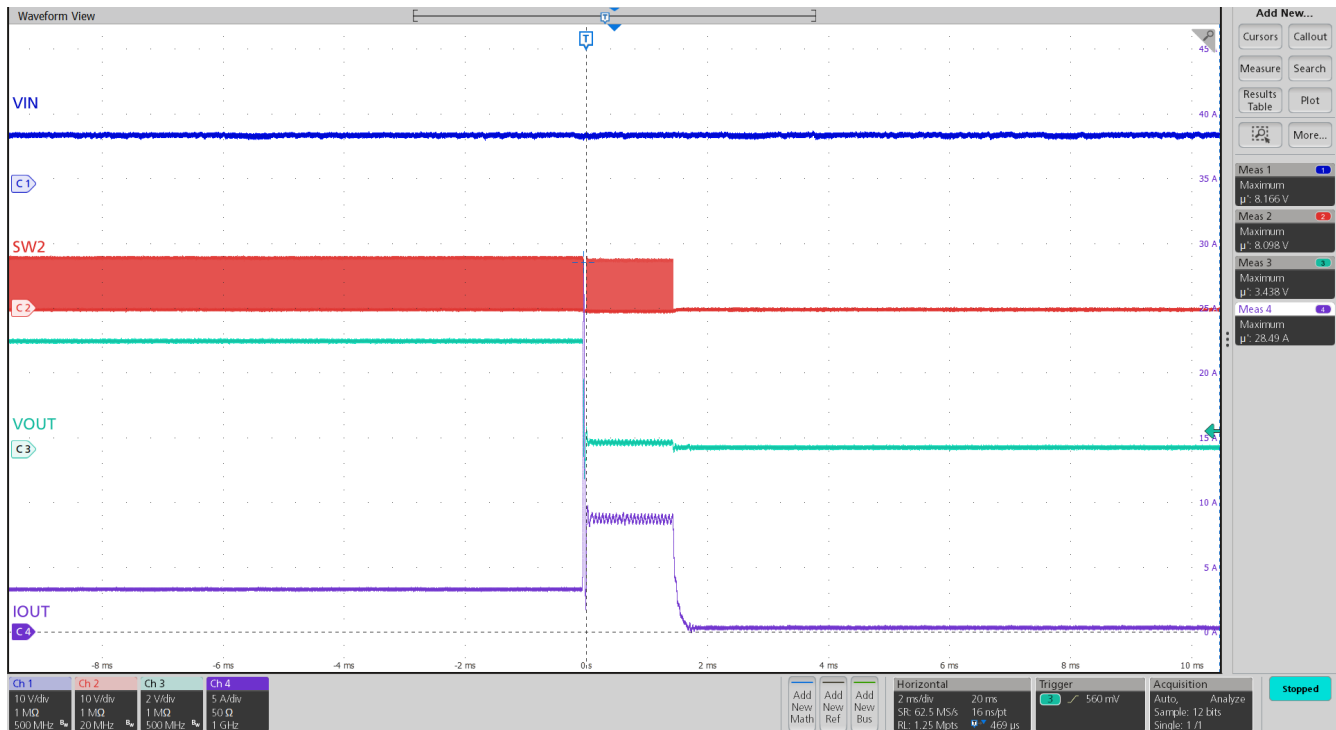


Figure 3-36. Short-Circuit Protection at 8.5 V_{IN}, 3.3 V_{OUT}

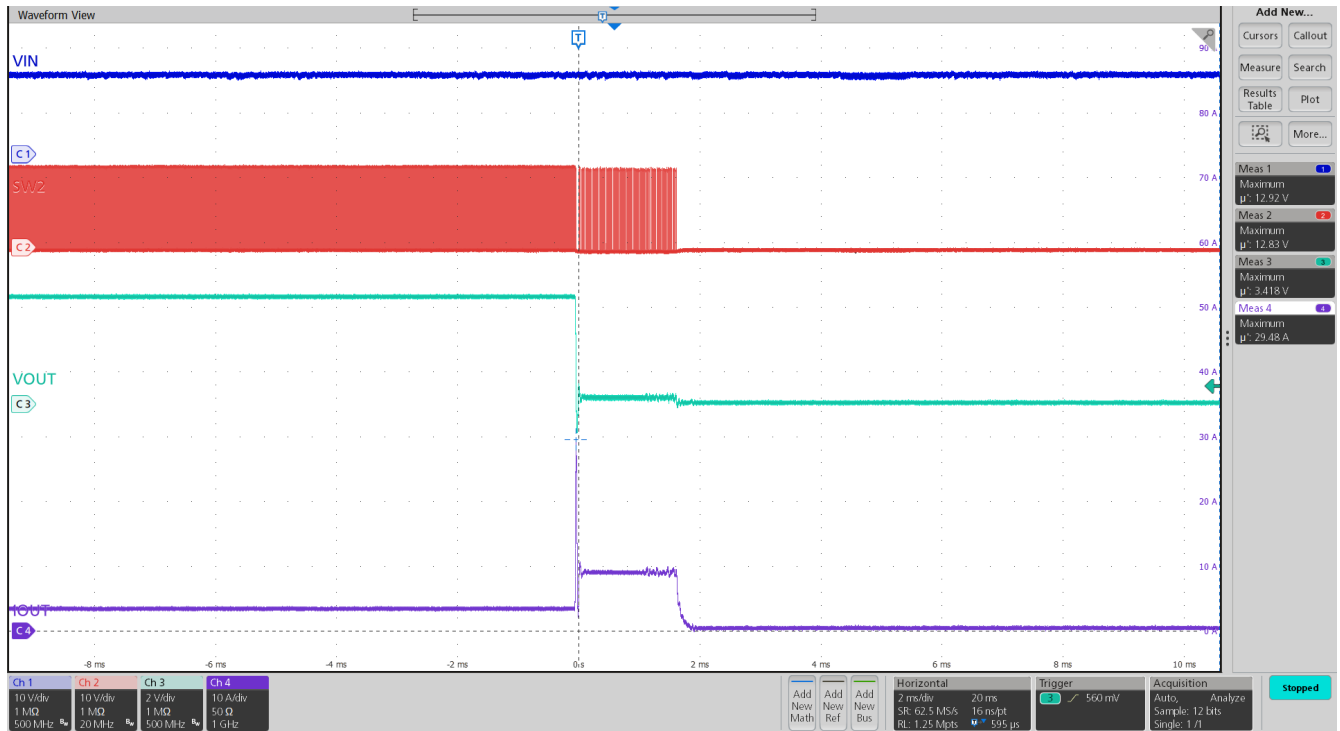


Figure 3-37. Short-Circuit Protection at 13.5 V_{IN}, 3.3 V_{OUT}

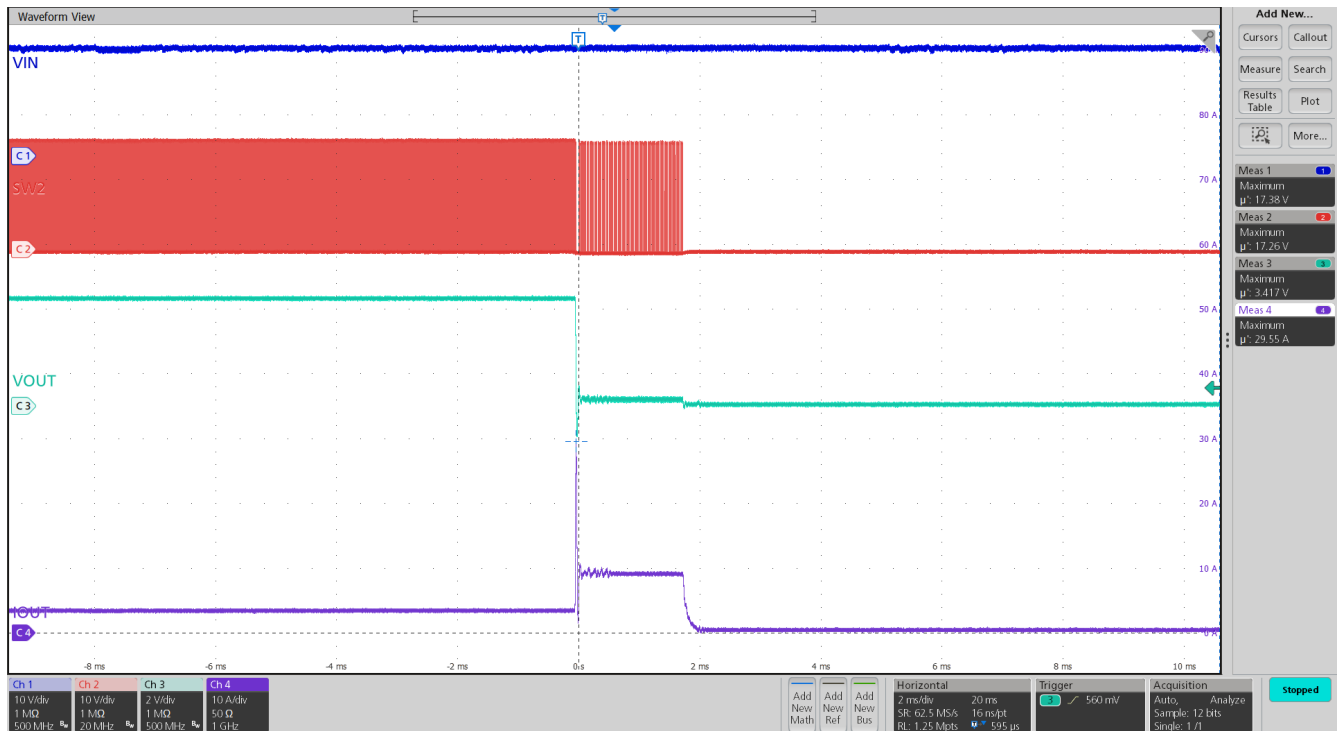


Figure 3-38. Short-Circuit Protection at 18 V_{IN}, 3.3 V_{OUT}

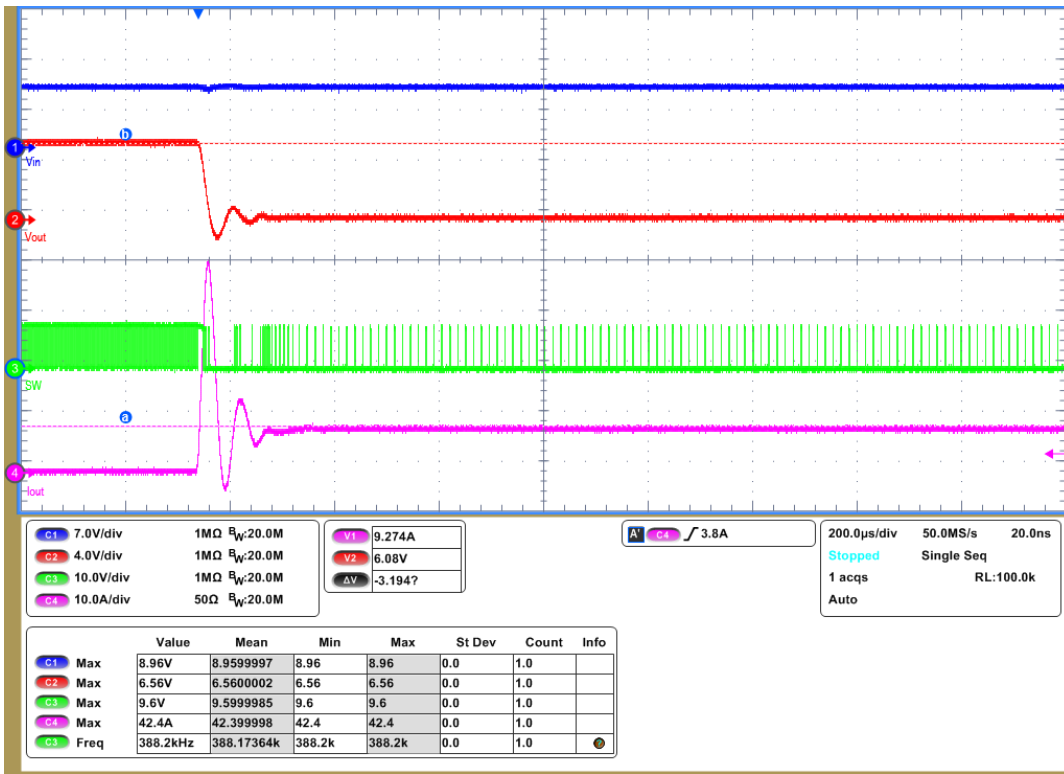


Figure 3-39. Short-Circuit Protection at 8.5 V_{IN}, 6 V_{OUT}

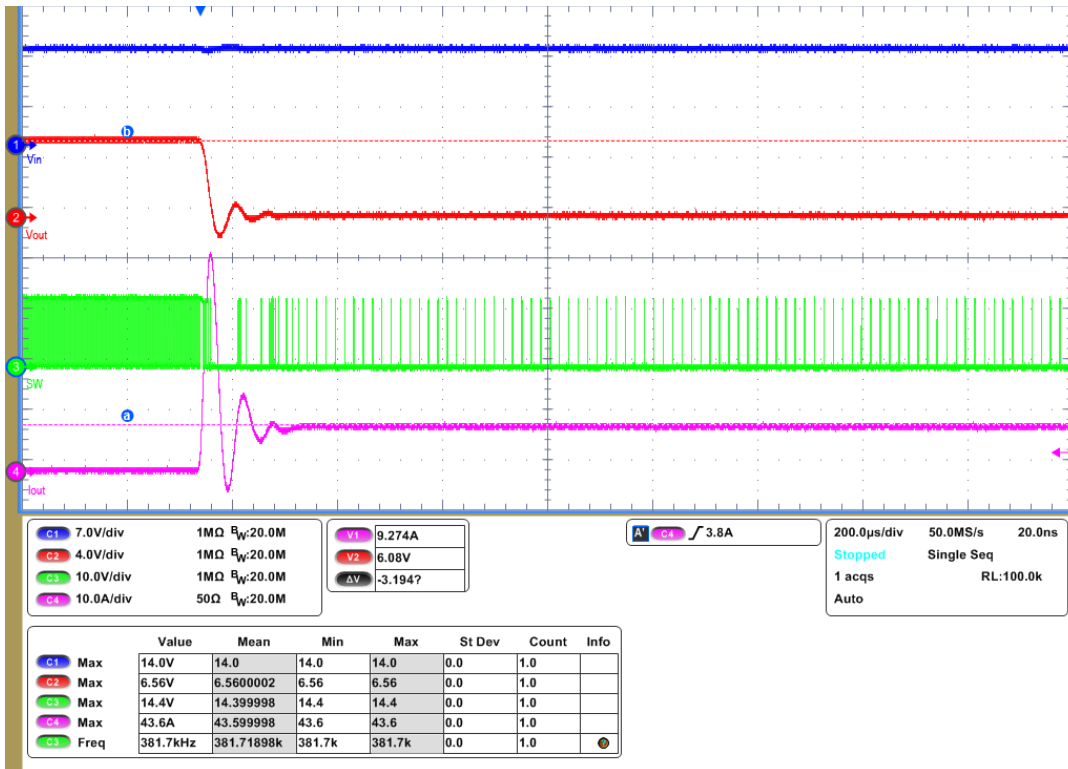


Figure 3-40. Short-Circuit Protection at 13.5 V_{IN}, 6 V_{OUT}

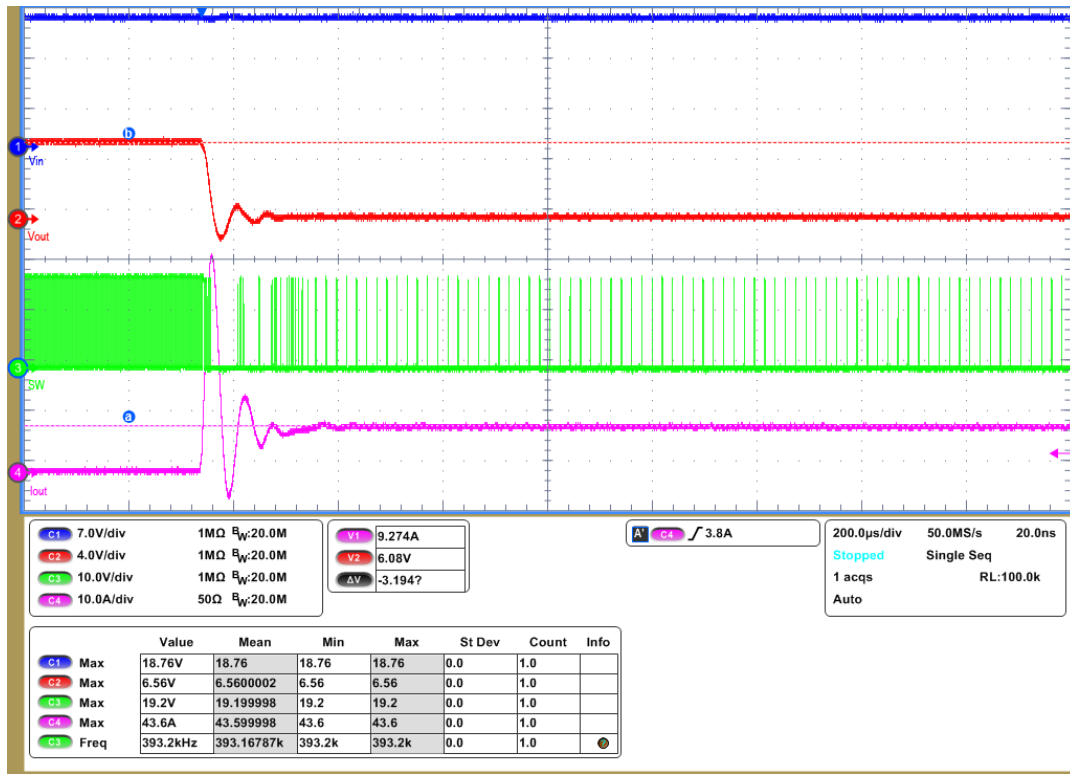


Figure 3-41. Short-Circuit Protection at 18 V_{IN}, 6 V_{OUT}

Short-circuit protection waveforms of TPS745-Q1 are shown in the following figure.

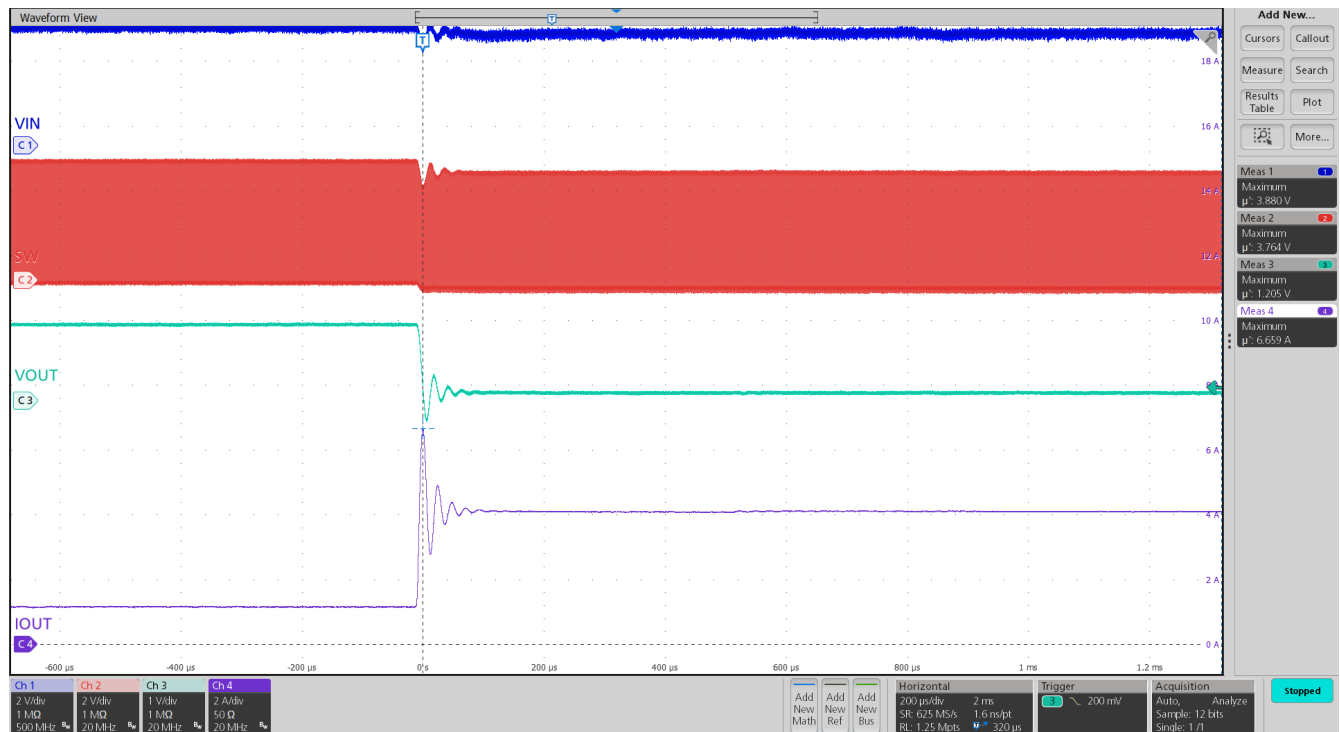


Figure 3-42. Short-Circuit Protection at 3.3 V_{IN}, 1.8 V_{OUT}

Short-circuit protection waveforms of TPS7B81-Q1 are shown in the following figures.

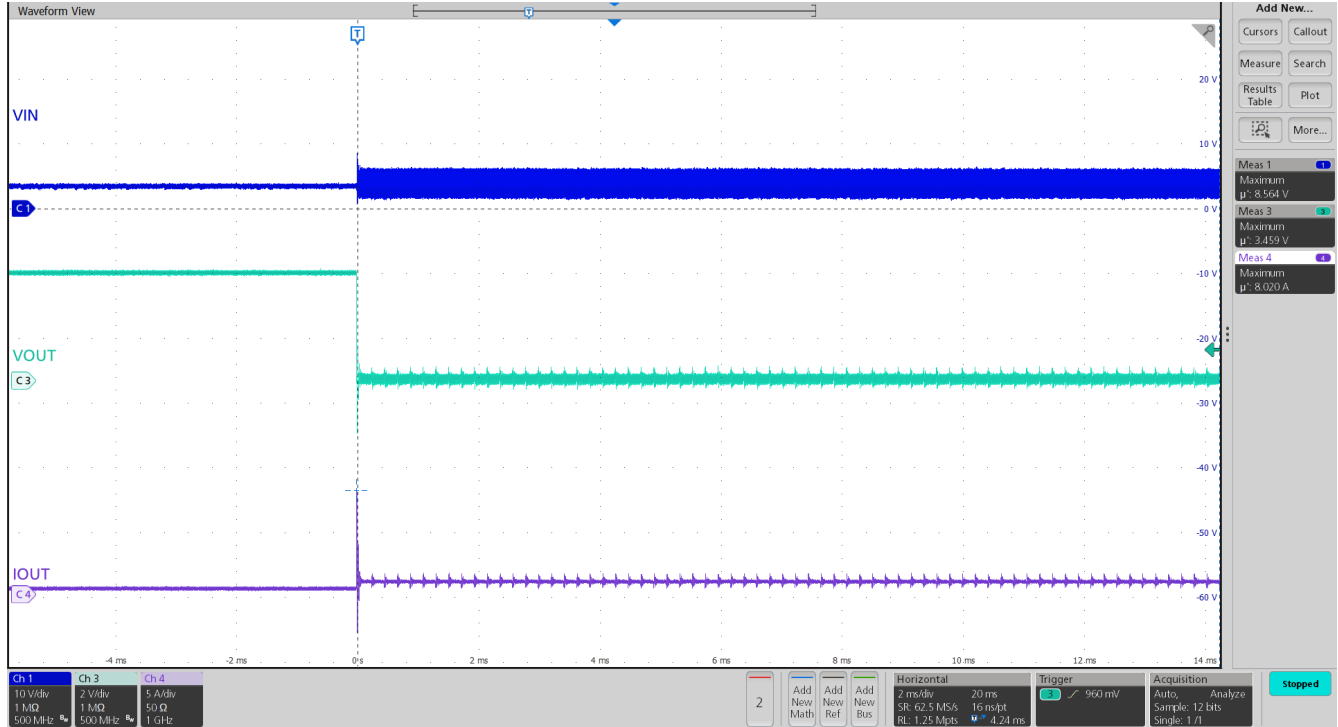


Figure 3-43. Short-Circuit Protection at 8.5 V_{IN} , 3.3 V_{OUT}

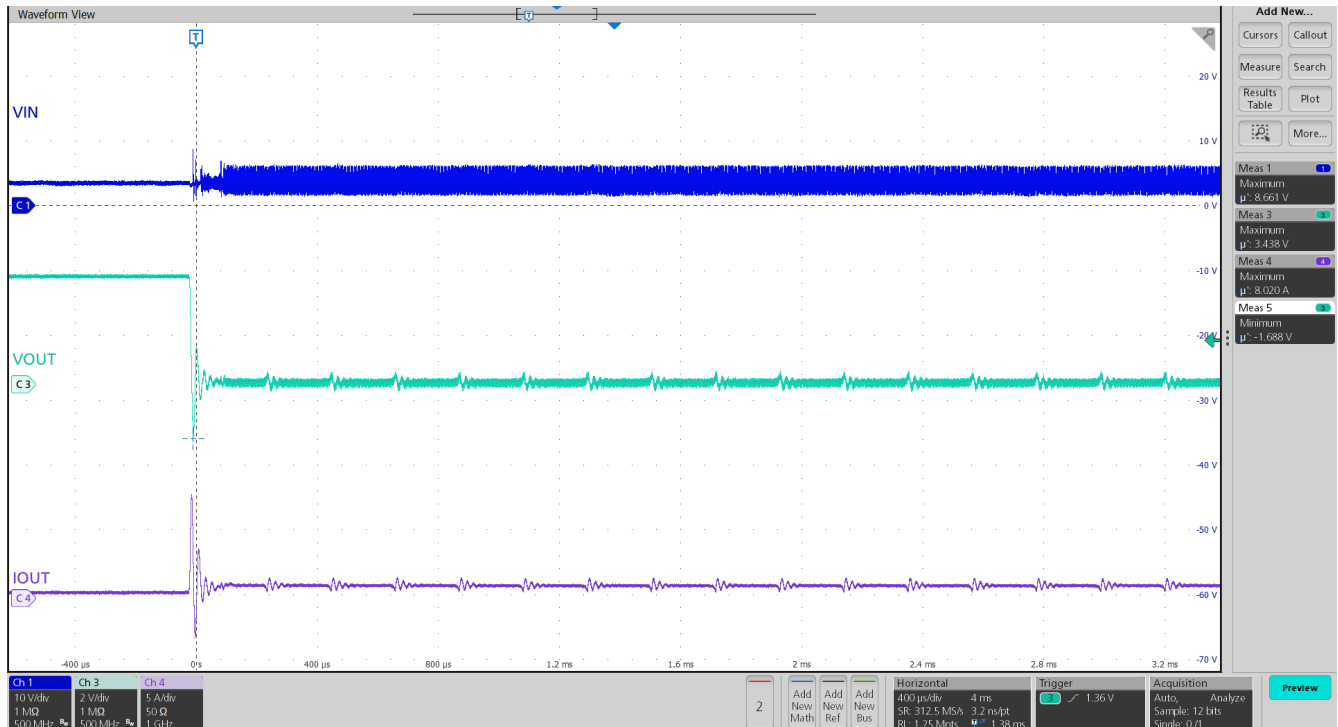


Figure 3-44. Short-Circuit Protection at 13.5 V_{IN} , 3.3 V_{OUT}

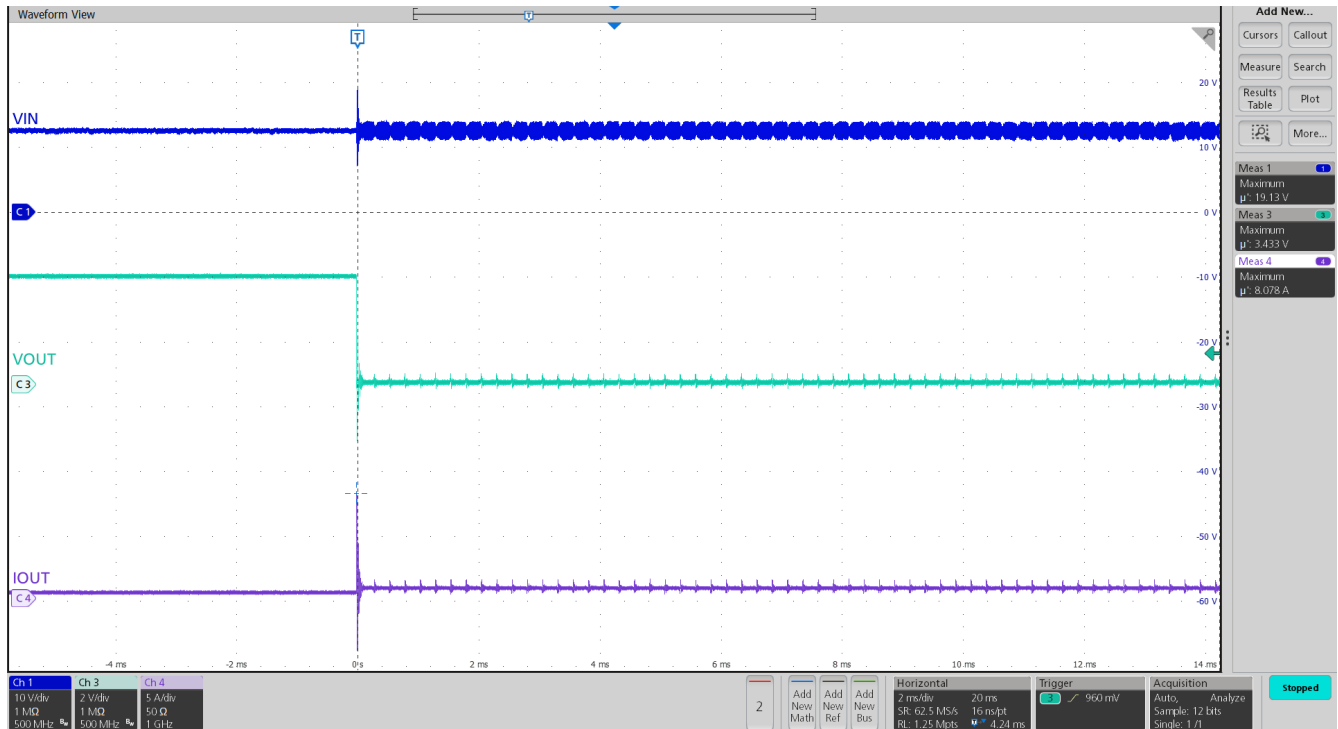


Figure 3-45. Short-Circuit Protection at 18 V_{IN}, 3.3 V_{OUT}

Short-circuit protection waveforms of TPS628503-Q1 are shown in the following figure.

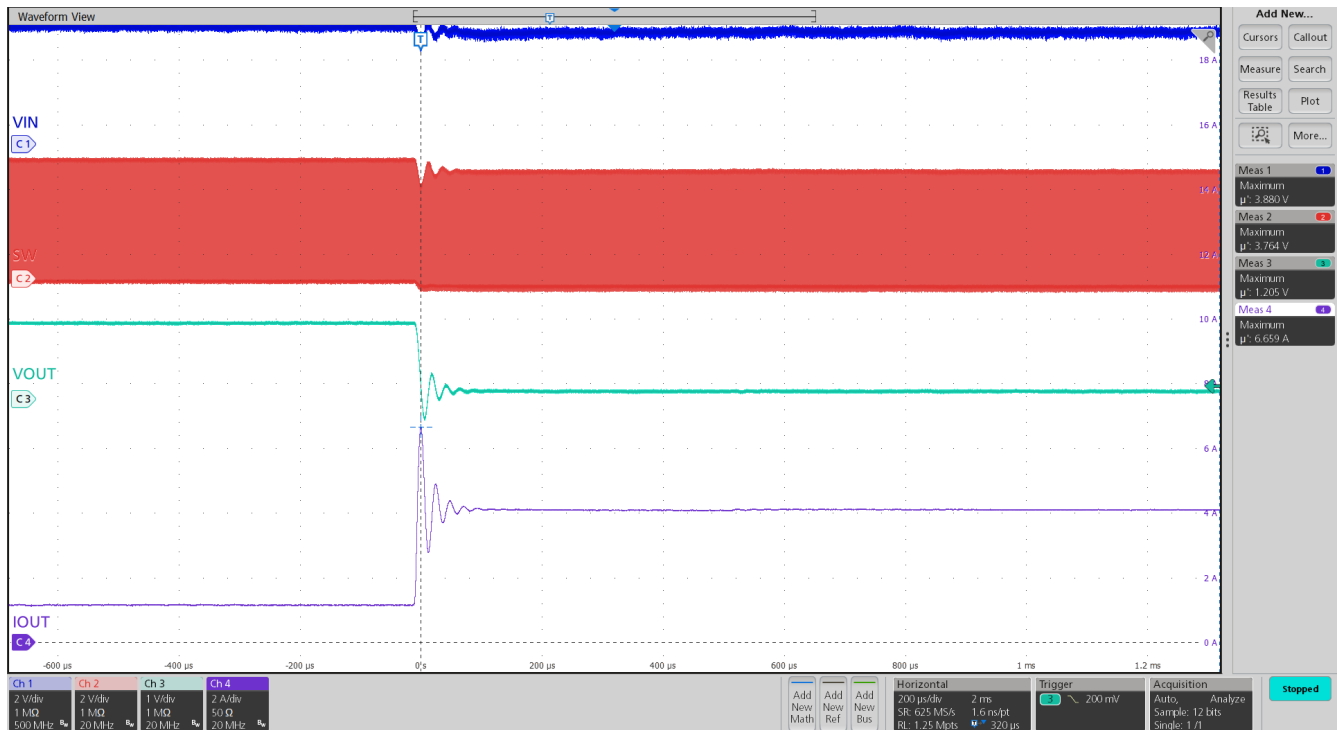


Figure 3-46. Short-Circuit Protection at 3.3 V_{IN}, 1.15 V_{OUT}

3.5 Load Transients

Load transient response waveforms of the LM5152-Q1 are shown in the following figures.

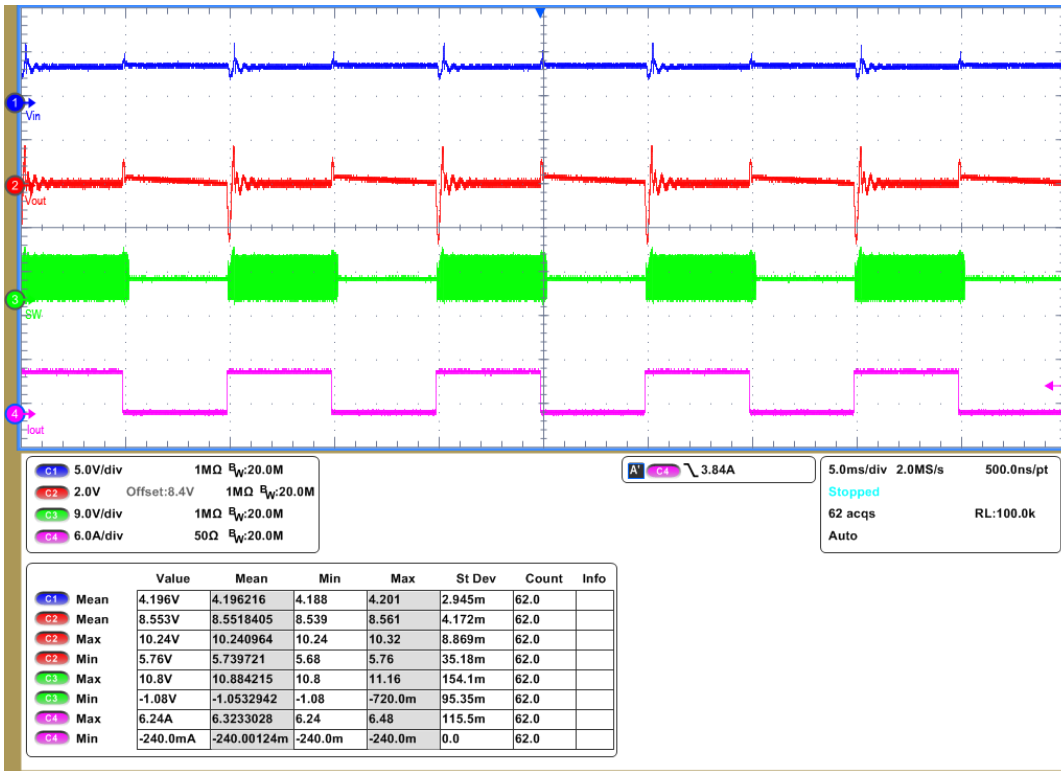


Figure 3-47. Load Transient at 4.2 V_{IN}, 8.5 V_{OUT}, 0A–5.88A

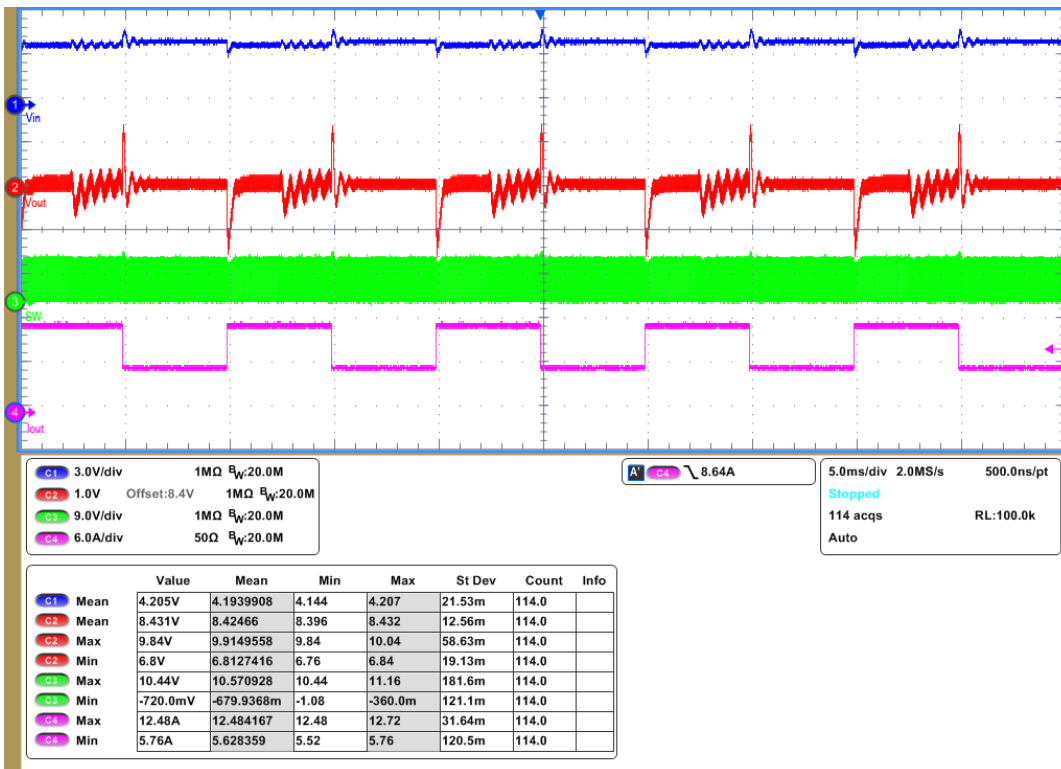


Figure 3-48. Load Transient at 4.2 V_{IN}, 8.5 V_{OUT}, 5.88A–11.48A

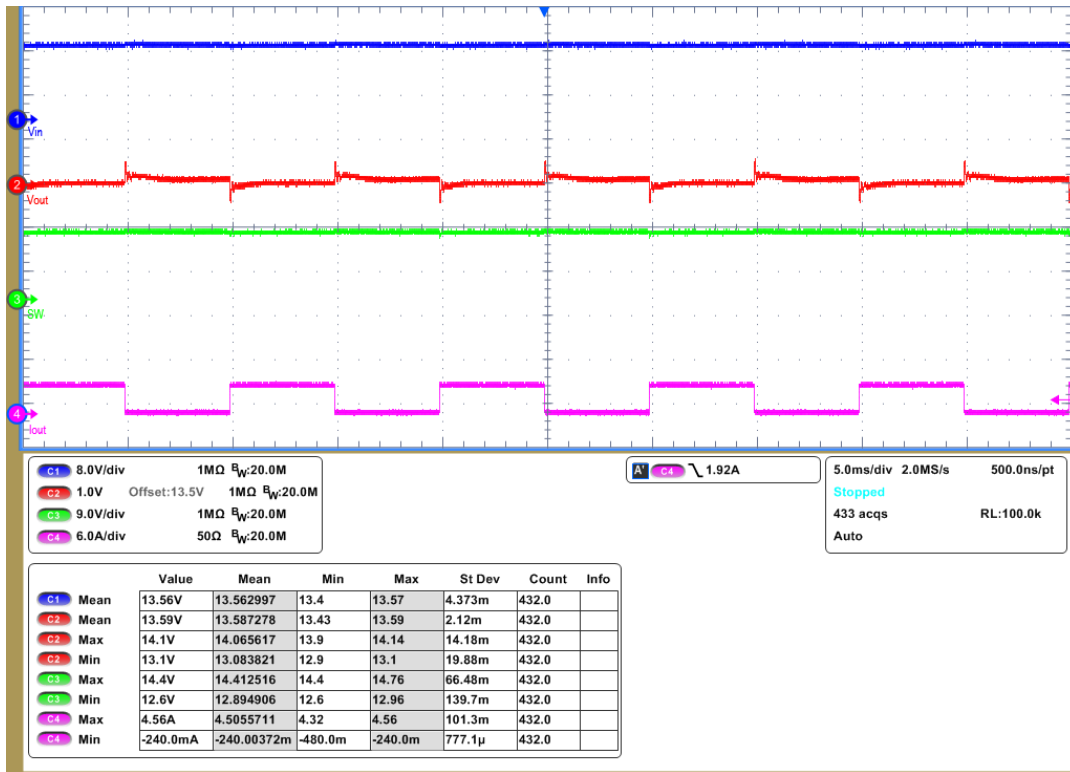


Figure 3-49. Load Transient at 13.5 V_{IN}, 13.5 V_{OUT}, 0A–3.74A

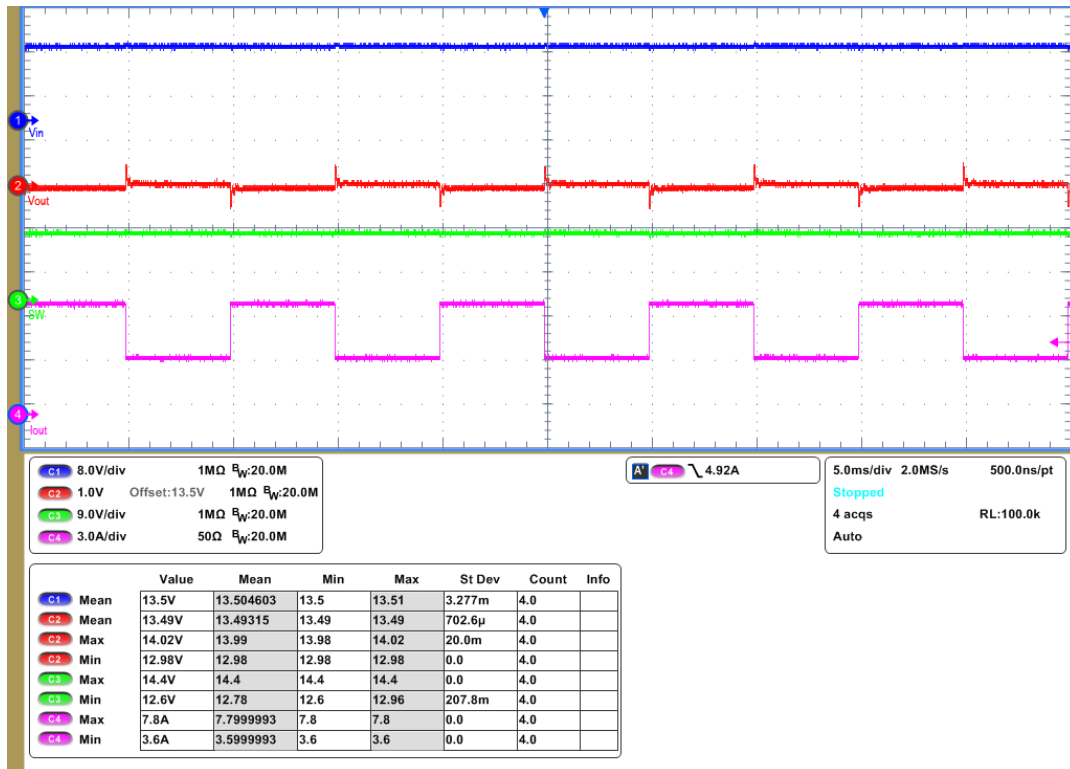


Figure 3-50. Load Transient at 13.5 V_{IN}, 13.5 V_{OUT}, 3.74A–7.48A

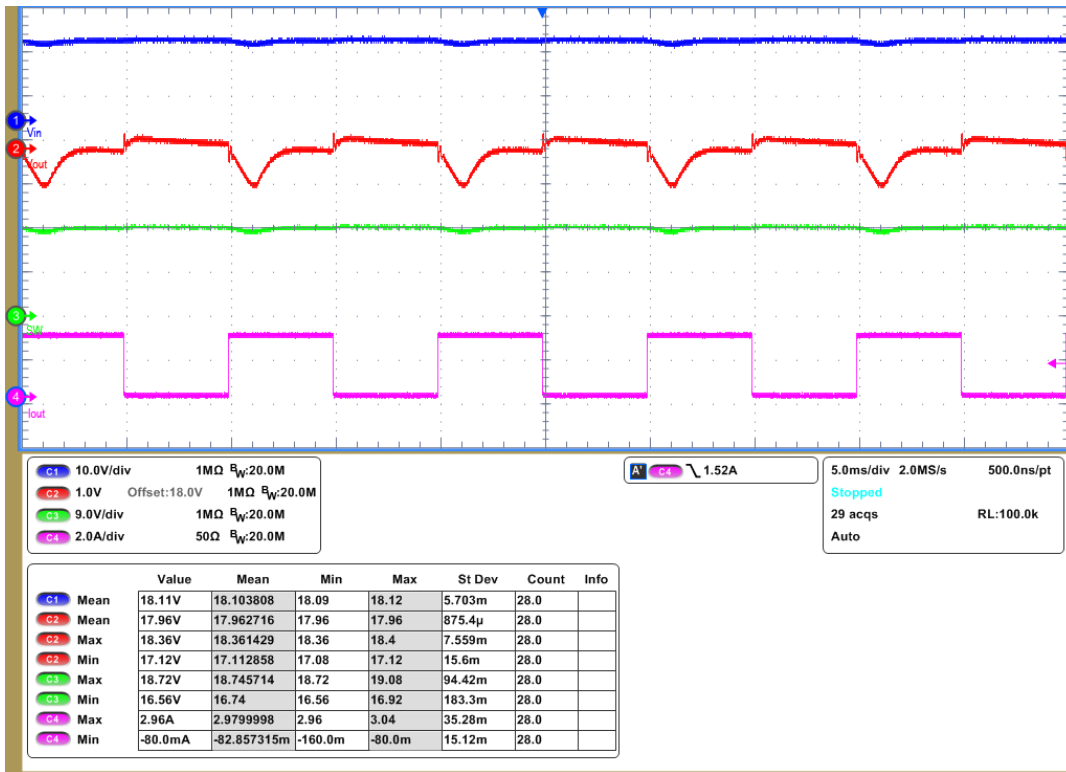


Figure 3-51. Load Transient at 18 V_{IN}, 18 V_{OUT}, 0A–2.78A

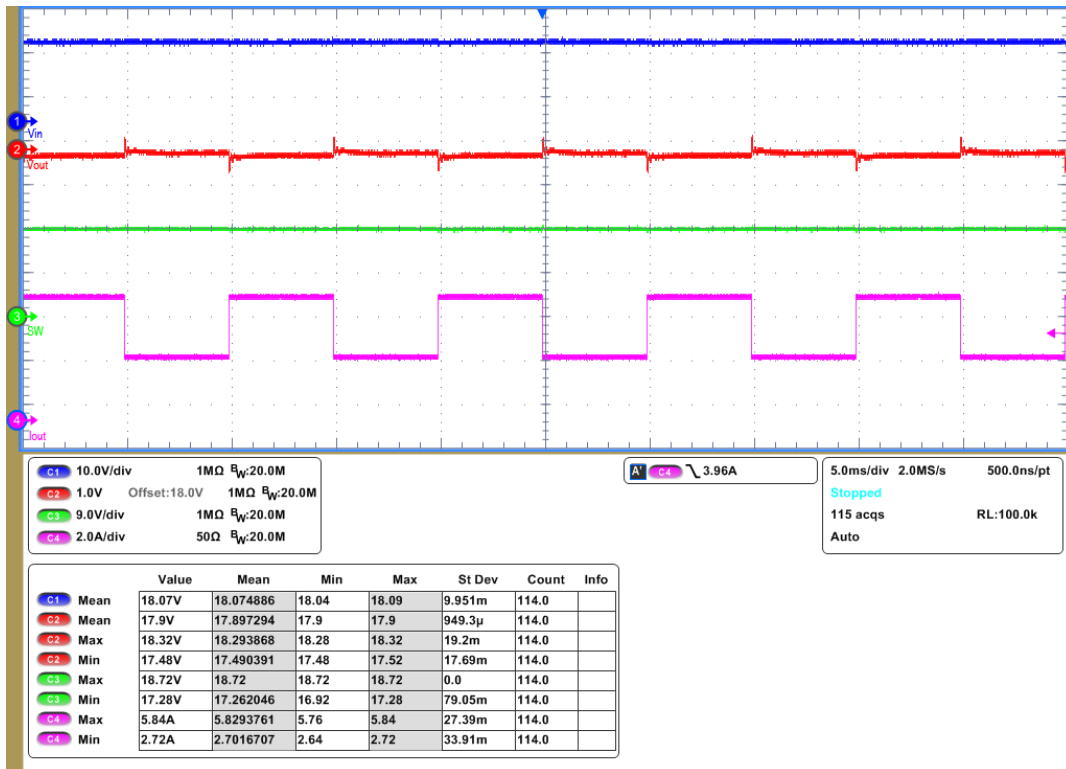


Figure 3-52. Load Transient at 18 V_{IN}, 18 V_{OUT}, 2.78A–5.55A

Load transient response waveforms of LM74900-Q1 are shown in the following figures.

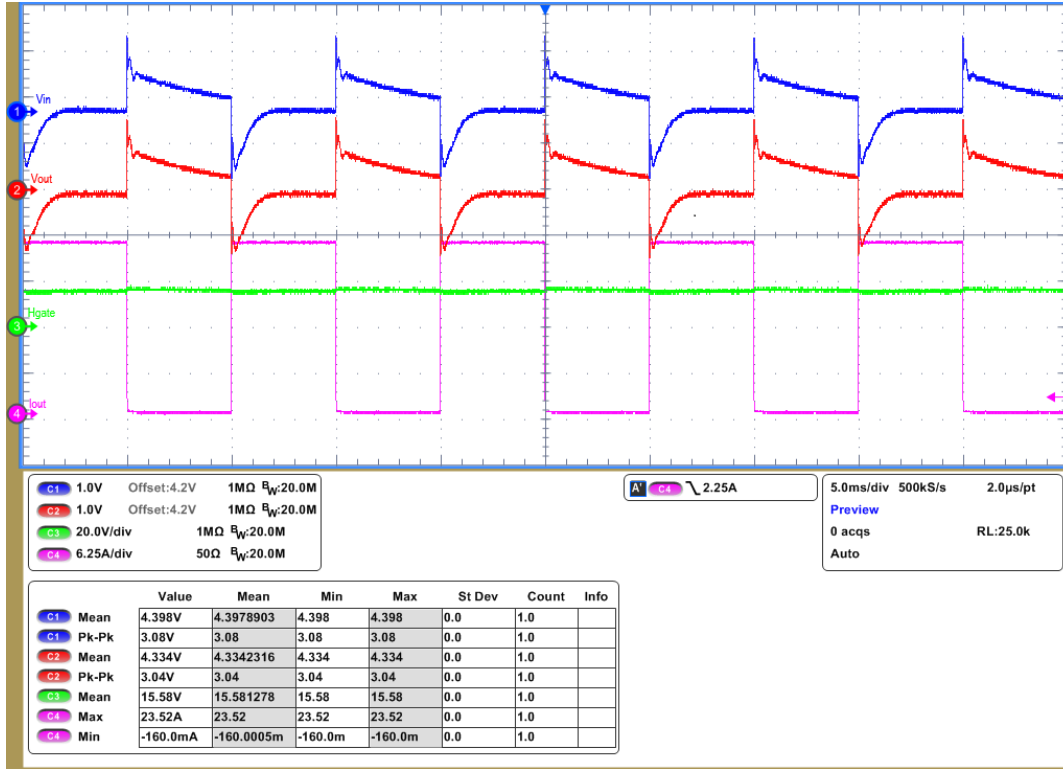


Figure 3-53. Load Transient at 4.2 V_{IN}, 4.2 V_{OUT}, 0A–24A

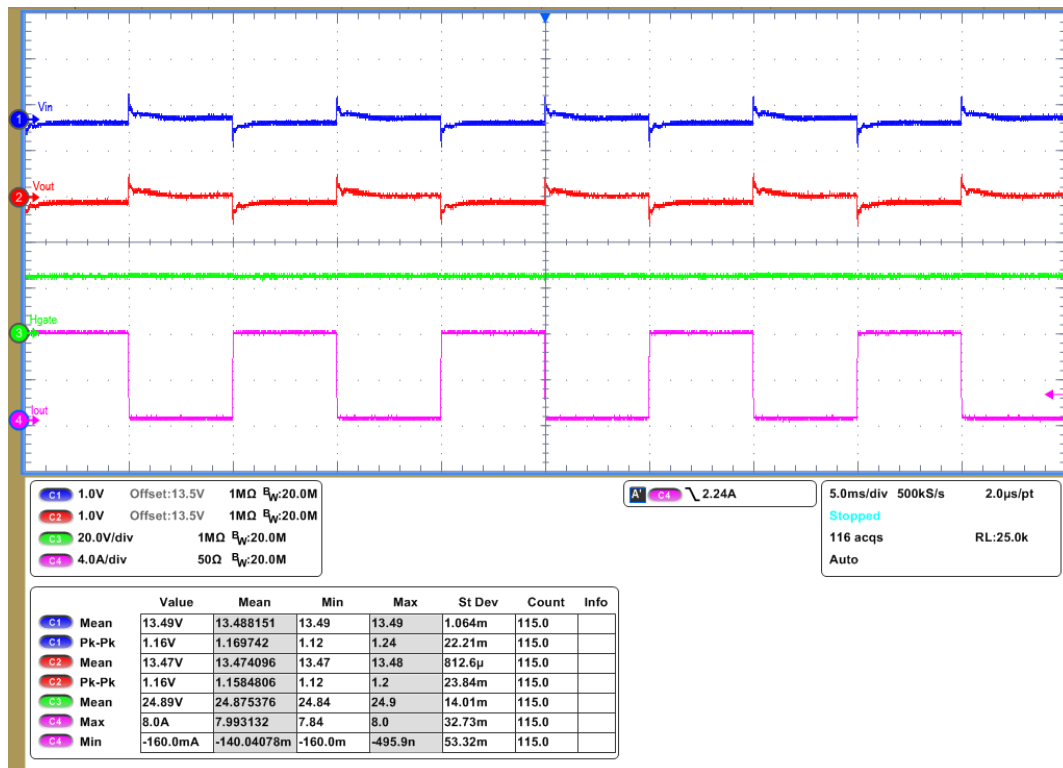


Figure 3-54. Load Transient at 13.5 V_{IN}, 13.5 V_{OUT}, 0A–7.48A

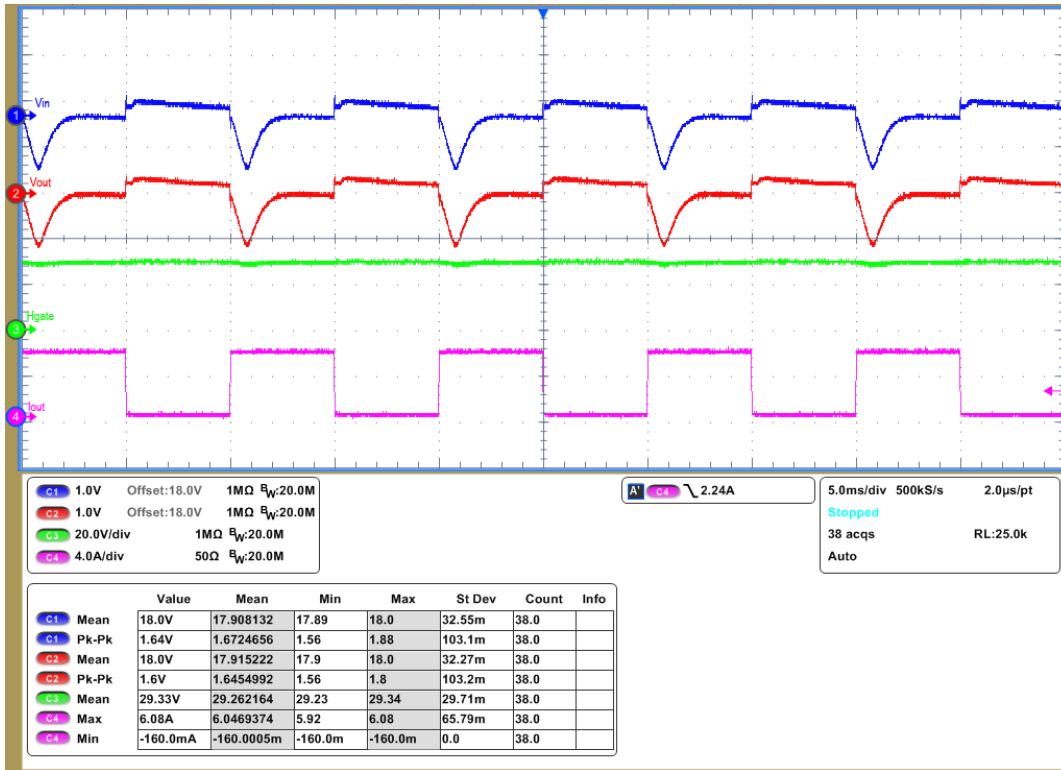


Figure 3-55. Load Transient at 18 V_{IN}, 18 V_{OUT}, 0A–6A

Load transient response waveforms of LMQ644A2-Q1 are shown in the following figures.

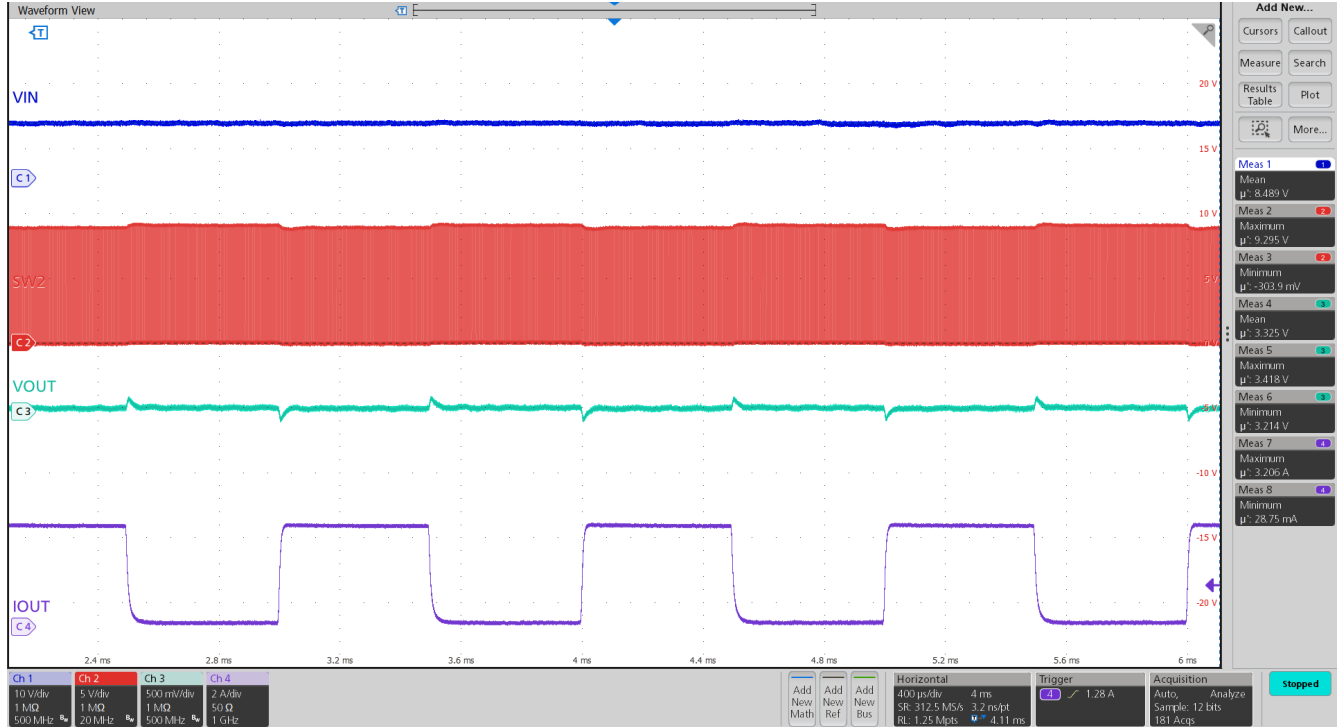


Figure 3-56. Load Transient at 8.5 V_{IN}, 3.3 V_{OUT}, 0A-3A

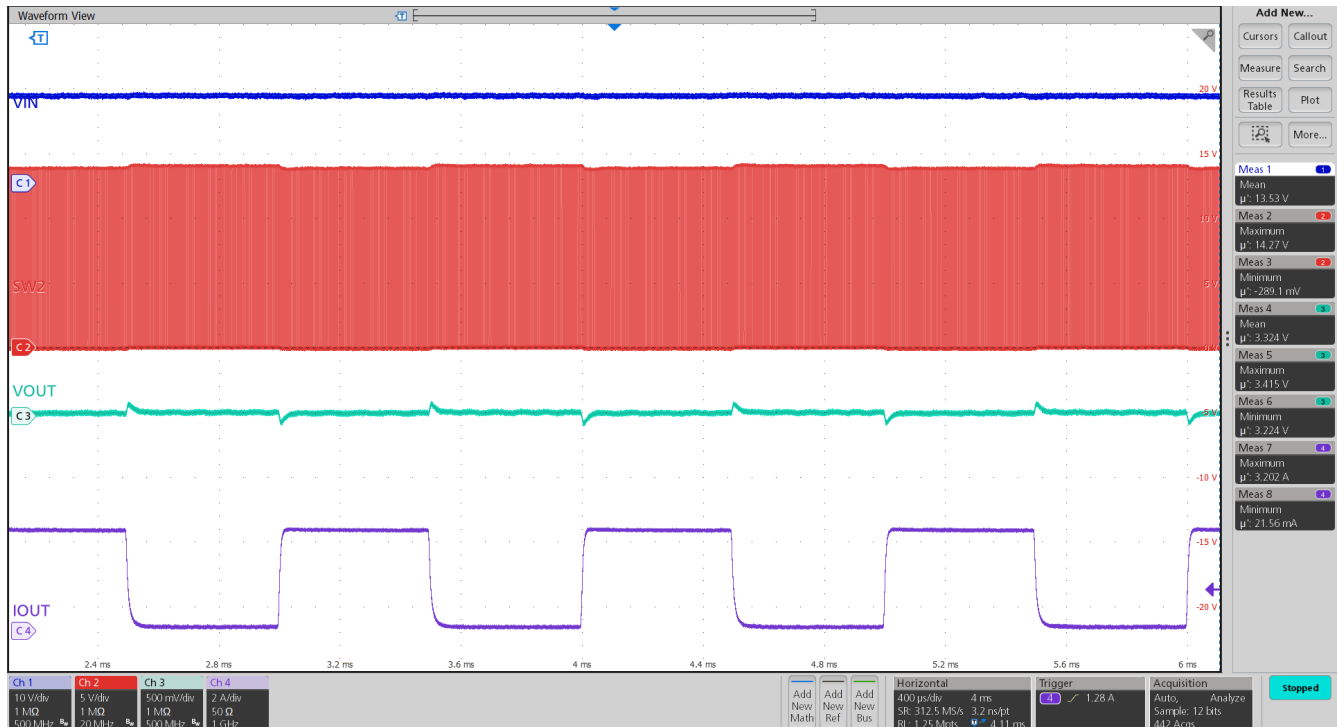


Figure 3-57. Load Transient at 13.5 V_{IN}, 3.3 V_{OUT}, 0A-3A

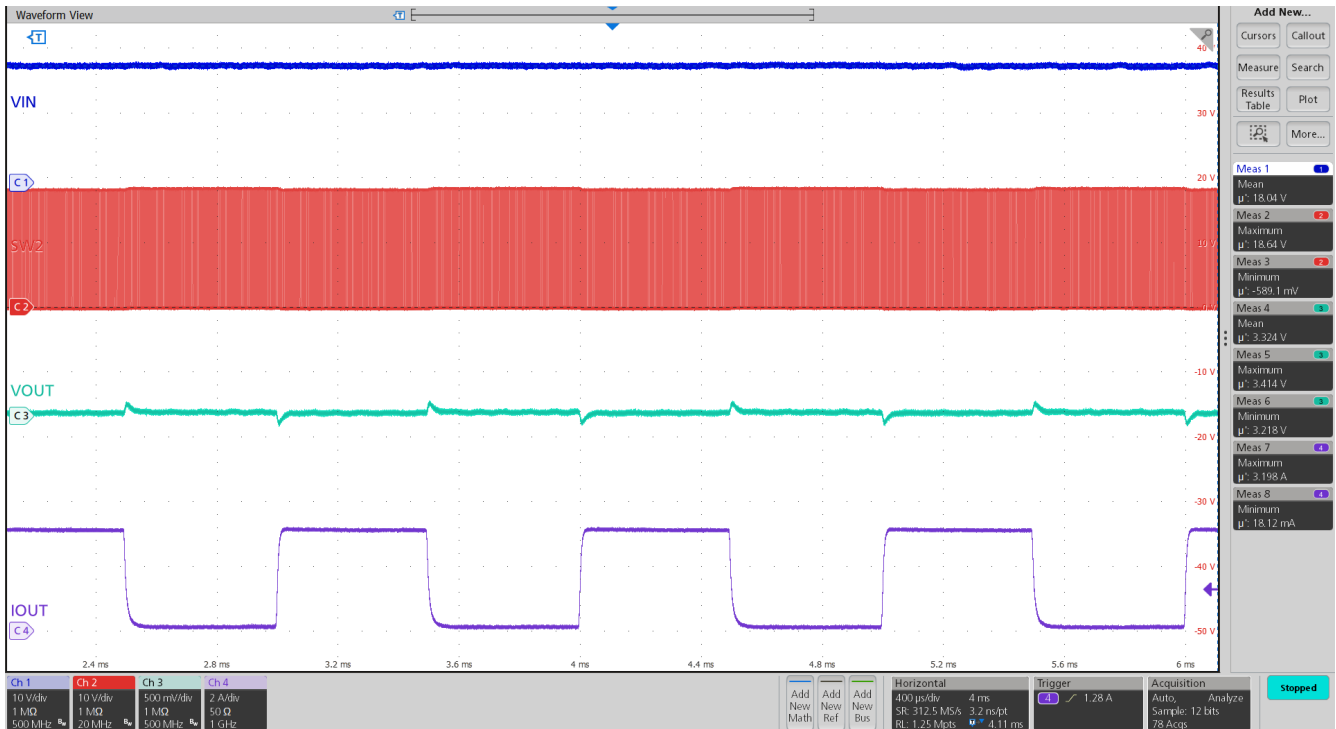


Figure 3-58. Load Transient at 18 V_{IN}, 3.3 V_{OUT}, 0A–3A

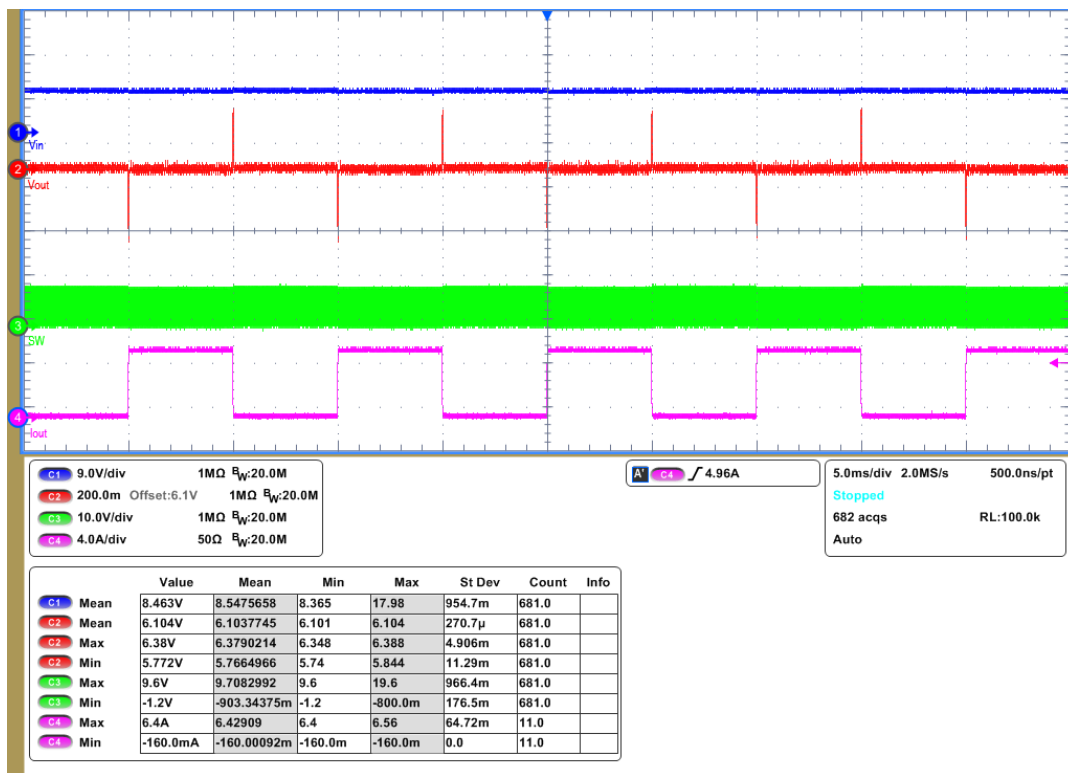


Figure 3-59. Load Transient at 8.5 V_{IN}, 6 V_{OUT}, 0A–6A

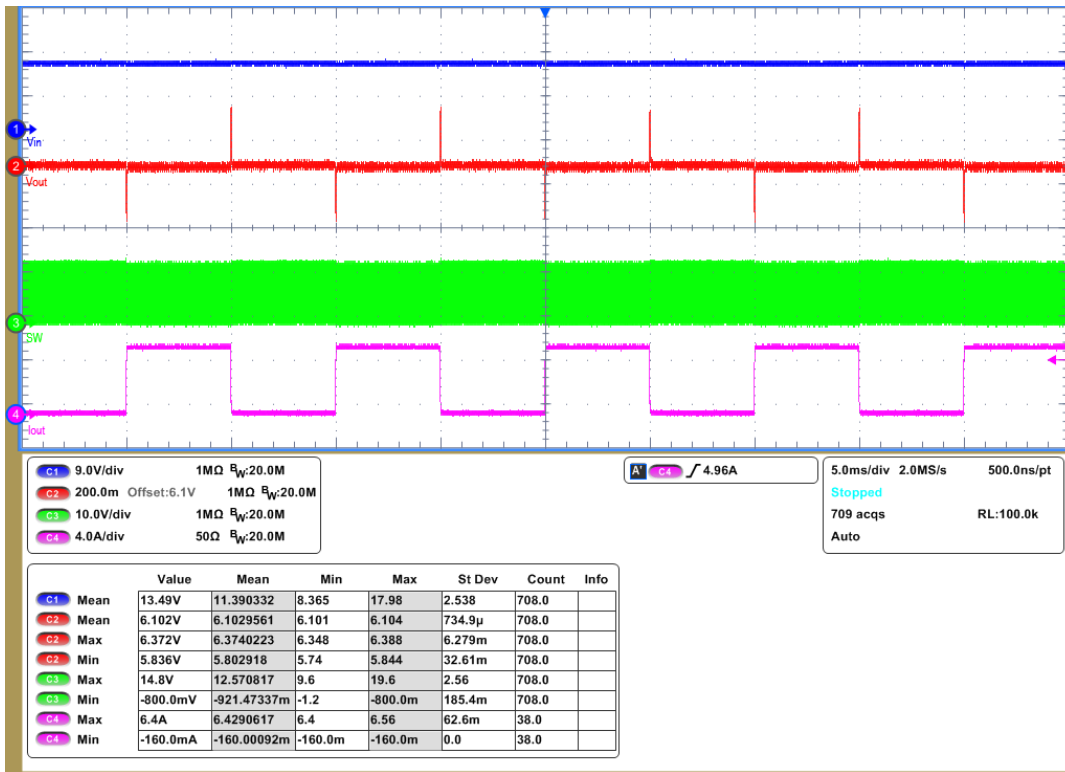


Figure 3-60. Load Transient at 13.5 V_{IN}, 6 V_{OUT}, 0A–6A

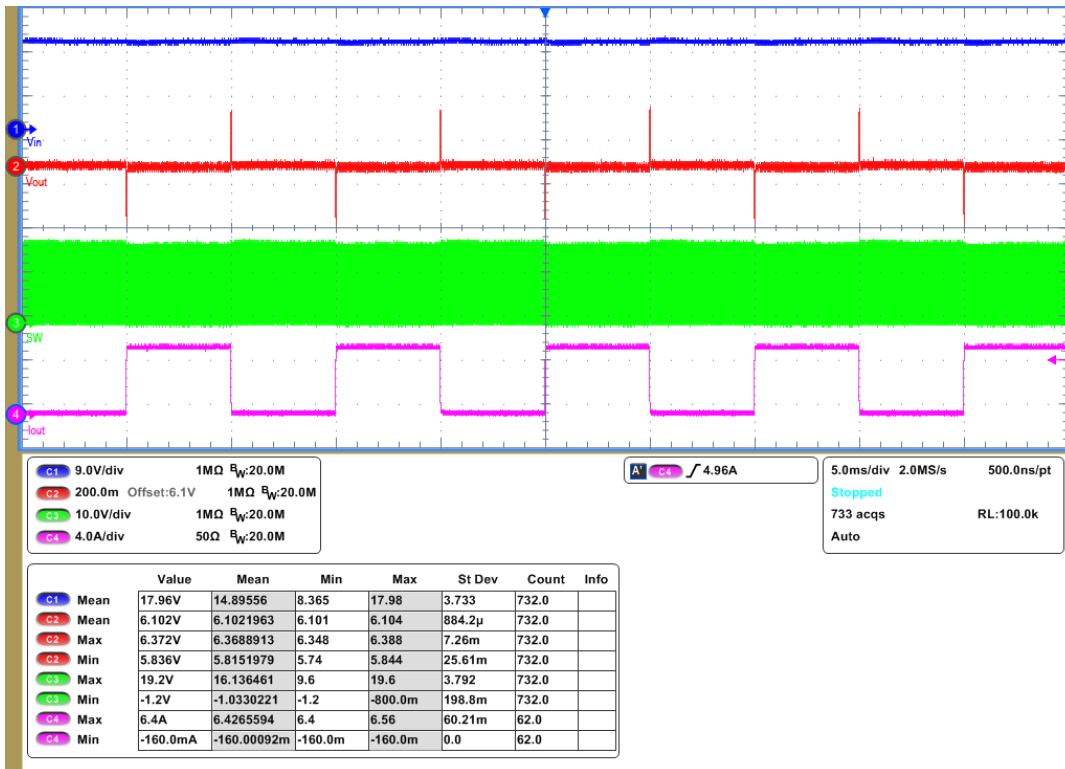


Figure 3-61. Load Transient at 18 V_{IN}, 6 V_{OUT}, 0A–6A

Load transient response waveforms of TPS628503-Q1 are shown in the following figure.

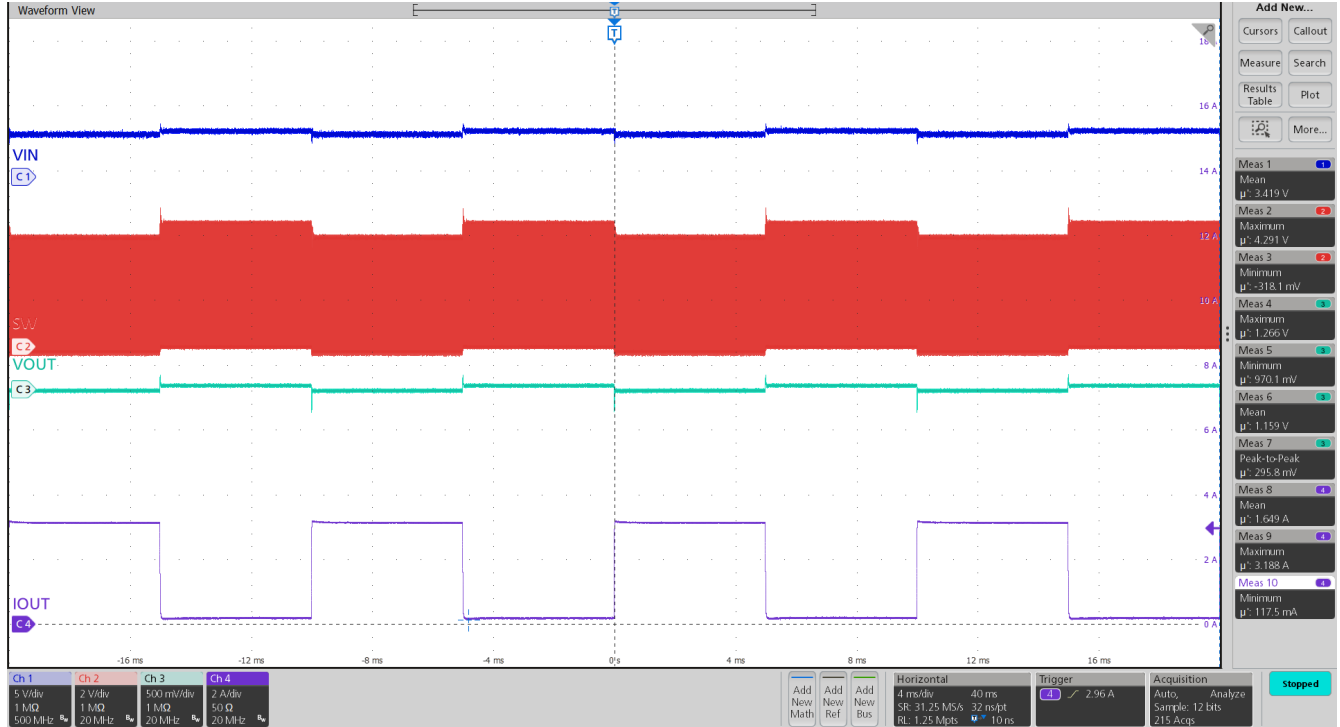


Figure 3-62. Load Transient at 3.3 V_{IN}, 1.15 V_{OUT}, 0A–3A

Load transient response waveforms of TPS745-Q1 are shown in the following figure.

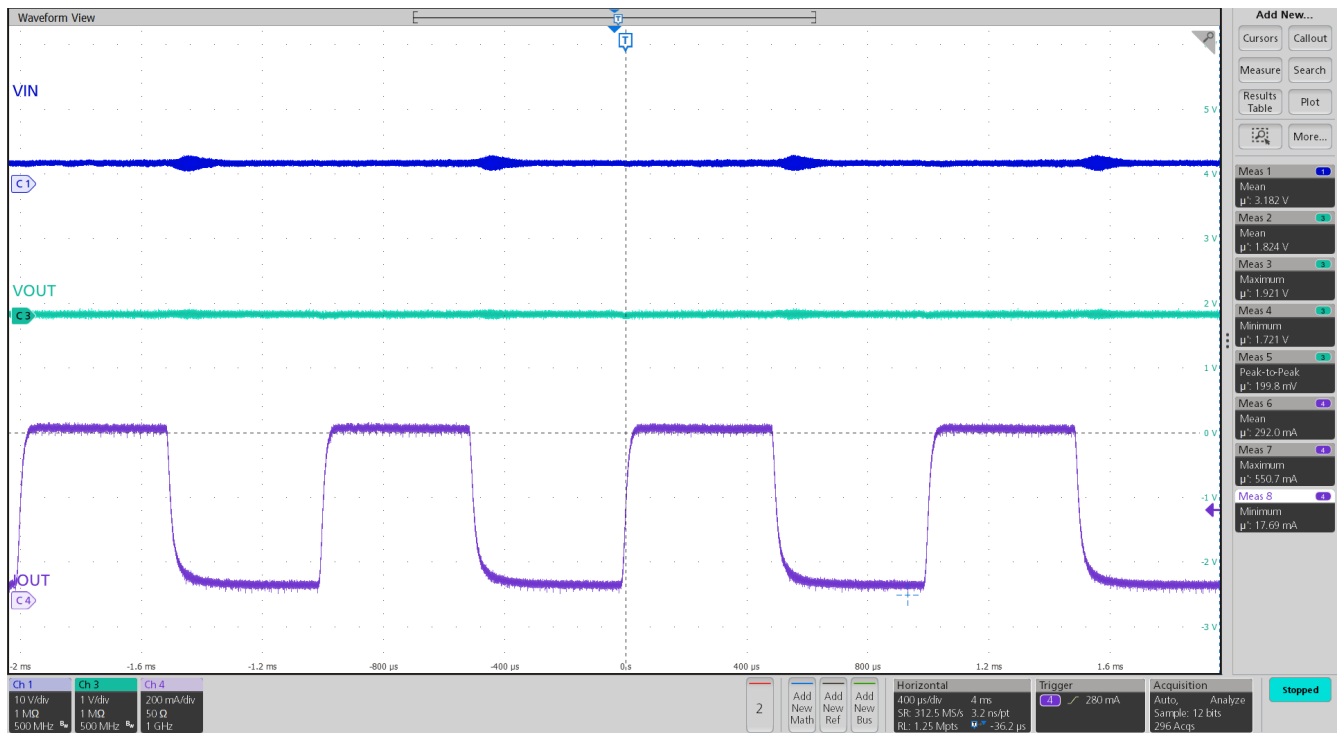


Figure 3-63. Load Transient at 3.3 V_{IN}, 1.8 V_{OUT}, 0A–0.5A

Load transient response waveforms of TPS7B81-Q1 are shown in the following figures.

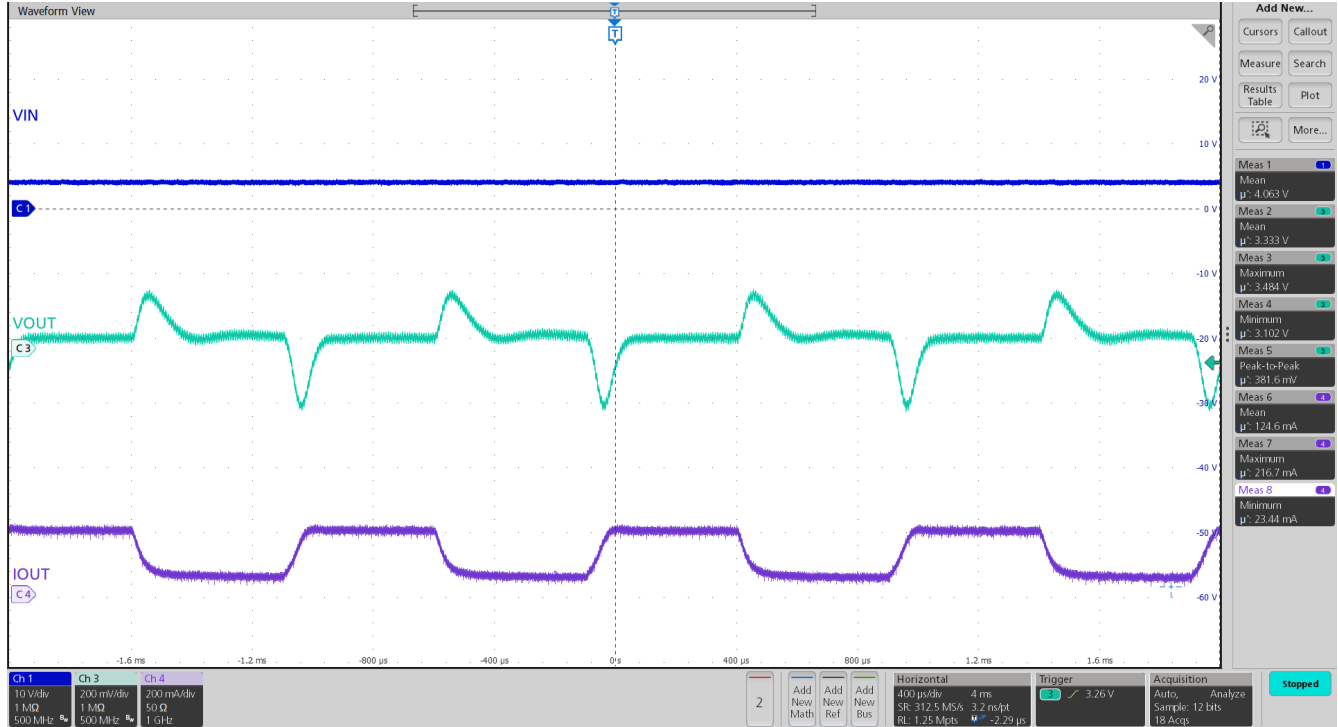


Figure 3-64. Load Transient at 4.5 V_{IN}, 3.3 V_{OUT}, 0A–0.15A

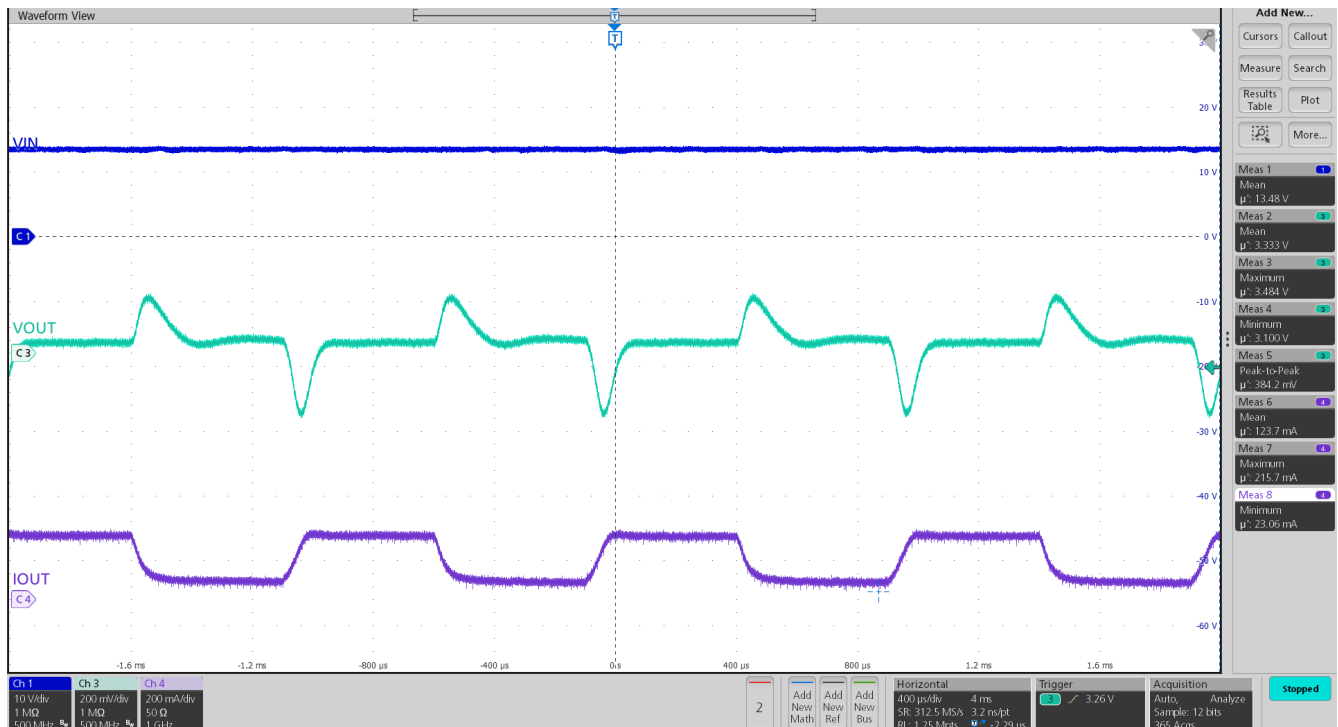


Figure 3-65. Load Transient at 13.5 V_{IN}, 3.3 V_{OUT}, 0A–0.15A

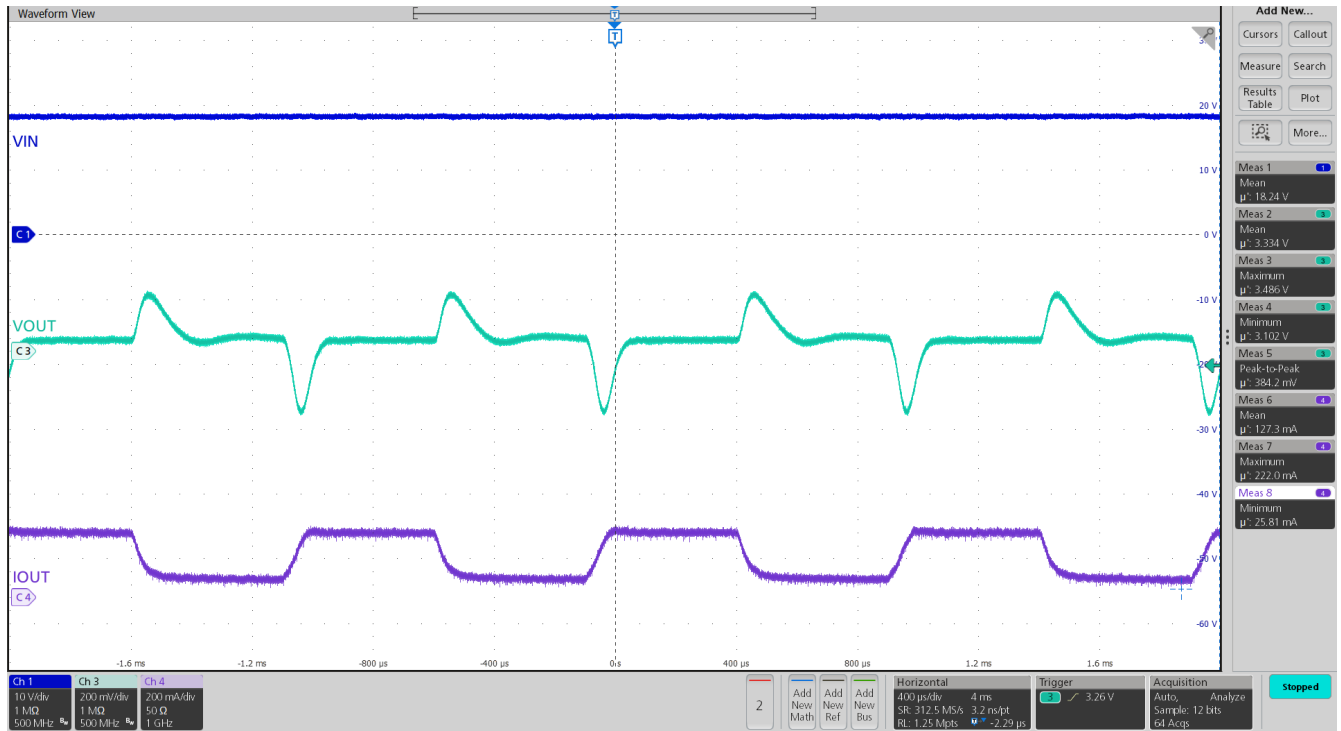


Figure 3-66. Load Transient at 18 V_{IN}, 3.3 V_{OUT}, 0A–0.15A

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated