

# LM5085

????P-FET????????????/?? (Zeta) ???



Literature Number: ZHCA413

## Designing Non-Inverting Buck-Boost (Zeta) Converters with a Buck P-FET Controller

— By Vijay Choudhary, Applications Engineer and Robert Bell, Design Center Director

### Introduction

Constant On-Time (COT) regulators provide a simple, cost-effective way of implementing step-down buck regulators with nearly fixed frequency, as shown in *Figure 1*. COT regulators do not require loop compensation and provide excellent transient performance with minimum design effort. Non-synchronous operation results in reduced switching frequency at a very light load which delivers higher efficiency than a comparable fixed frequency converter.

In many applications, the input voltage varies above and below the required output voltage. Many articles and application notes have shown how to configure a buck regulator to work as an inverting or non-inverting buck-boost regulator to accomplish the task. However, most of these methods are based on PWM buck controllers. While it is easy to configure the power

stage from buck to buck-boost topology, the compensation design remains a challenge as the power stage small signal model changes significantly. This means that the compensation design must be done from scratch. This approach also places limitations on the achievable bandwidth. Since COT topology does not require any compensation, significantly less effort is required to get a non-inverting buck-boost circuit working. This article explains how to use a COT P-FET buck controller to design a non-inverting buck-boost supply that achieves fast transient response without requiring a control loop design, as shown in *Figure 2*. Zeta converter implementation also has the added advantage of short-circuit protection over boost converters.

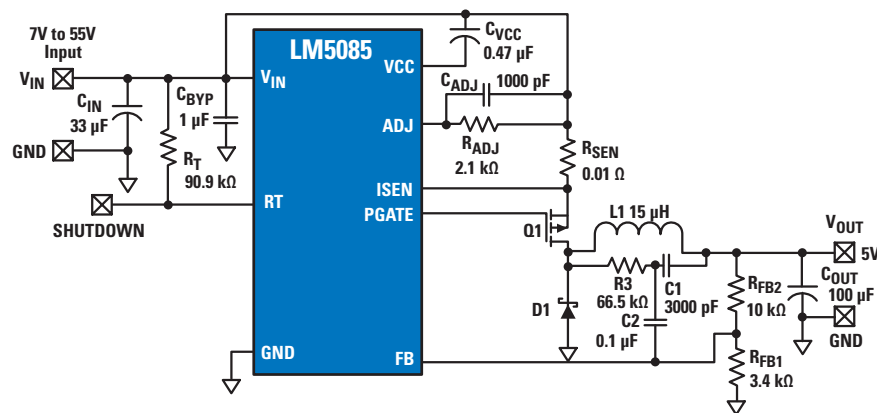


Figure 1. LM5085 Buck Application Circuit

## Designing Zeta Converters with a Buck P-FET Controller

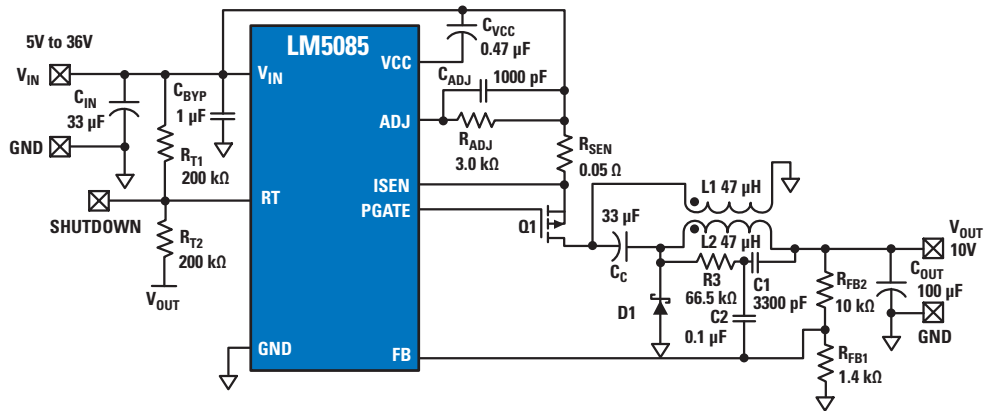


Figure 2. LM5085 Non-Inverting Buck-Boost (Inverse SEPIC or Zeta) Application Circuit

### Operation of LM5085-Based Non-Inverting Buck-Boost (Zeta) Converter

Zeta converter allows operation with  $V_{IN}$  varying below and above  $V_{OUT}$  while providing short circuit protection. The output capacitor has smaller ripple because of the series inductor at the output. **Figure 3** shows the simplified diagram of a Zeta converter. The coupling capacitor ( $C_C$ ) is charged to  $V_{OUT}$  in steady state. The blue lines show the direction of current during  $T_{ON}$  ( $Q1$  'on') and the dark red lines show the direction of current during  $T_{OFF}$  ( $D1$  conducting). Continuous conduction mode is assumed. **Figure 4** shows the ideal voltage waveforms for switch nodes ( $SW1$ ,  $SW2$ ) and ideal current waveforms in the inductors ( $I_{L1}$ ,  $I_{L2}$ ), switch ( $I_{Q1}$ ), and the coupling capacitor ( $I_{CC}$ ).

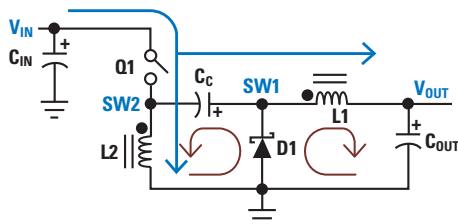


Figure 3. Zeta Converter Operation (Switching Intervals) (Blue: Q1 'on', Red: Q1 'off')

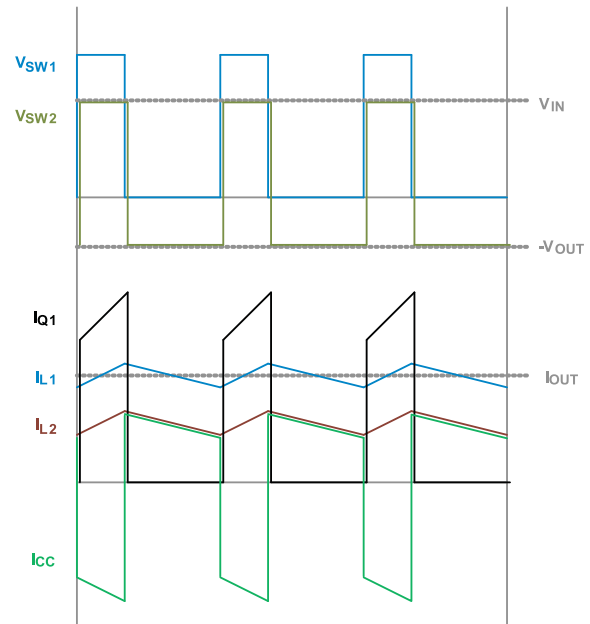


Figure 4. Zeta Converter Operating Waveforms

**Figure 3** shows  $L1$  and  $L2$  coupled inductors. Coupled inductors may reduce the footprint of the solution under some conditions but are not necessary for the proper operation of a Zeta converter. In applications where the  $V_{IN}$  varies much below  $V_{OUT}$ , the current rating on inductor  $L2$  is significantly higher than the current rating

of output inductor L1. In such cases, it may be easier to split the inductor in two and optimize each one separately. For tightly coupled inductors, the current ripple in the two windings may have some mismatch because the ripple voltage across the coupling capacitor appears across the small leakage inductance.

## Design Equations

In a Zeta converter, the input/output relationship—deduced by applying inductor voltage balance—is given by:

$$V_{OUT} = \frac{D}{1-D} V_{IN}$$

or

$$D = \frac{V_{OUT}}{V_{IN} + V_{OUT}}$$

L1 and L2 are given by:

$$L1 = L2 = \frac{V_{IN} T_{ON}}{\Delta I}$$

for uncoupled inductors and half as much for coupled inductors.  $\Delta I$  is the desired ripple current in L1 and L2 which is highest at the highest input voltage. The peak current in L1 is given by:

$$I_{L1(\text{peak})} = I_{OUT} + \frac{\Delta I}{2}$$

and the peak current in L2 is given by:

$$I_{L2(\text{peak})} = \frac{D}{1-D} I_{OUT} + \frac{\Delta I}{2}$$

D1—During  $T_{ON}$  the voltage across diode D1 is:

$$V_{D1} = V_{IN} + V_{OUT}$$

which is the same as the voltage across Q1 in  $T_{OFF}$ .

The average current through D1 is:

$$I_{D1(\text{avg})} = I_{OUT}$$

Q1—voltage rating of P-FET switch is:

$$V_{SW} = V_{IN} + V_{OUT}$$

Q1—average current is:

$$I_{SW(\text{avg})} = \frac{D}{1-D} I_{OUT}$$

however, the peak current through the switch is:

$$I_{SW(\text{peak})} = \frac{1}{1-D} I_{OUT} + \Delta I$$

which is important because it affects the current limit.

CC—The coupling capacitor handles the output voltage in steady state. The ripple current is given by:

$$I_{\text{Coup}(\text{rms})} = \sqrt{\frac{D}{1-D}} I_{OUT}$$

CIN—Input capacitor has the same ripple current as the coupling capacitor.

## Designing Zeta Converters with a Buck P-FET Controller

### Frequency of Operation

LM5085 is a COT controller optimized for buck operation with inverse relationship between  $V_{IN}$  and  $T_{ON}$ . In continuous conduction mode (CCM), this results in a nearly constant frequency operation as a buck converter. The inverse relationship between  $V_{IN}$  and  $T_{ON}$ , however, does not result in constant frequency operation when operating as a Zeta converter. In a buck-boost configuration

$$D = T_{ON}f = \frac{V_{OUT}}{V_{IN} + V_{OUT}}$$

and, therefore,  $T_{ON}$  should be made proportional to

$$\frac{1}{V_{IN} + V_{OUT}}$$

to achieve nearly constant frequency operation.

This is accomplished by connecting the  $R_T$  pin to  $V_{OUT}$  and  $V_{IN}$  with equal value resistors, as shown in **Figure 2**. The resulting  $T_{ON}$  is calculated by **Equation 3** in the LM5085 datasheet with  $V_{IN}$  replaced by  $V_{IN} + V_{OUT}$ .

### Performance

A Zeta converter was designed for input voltage range 5V-36V and maximum load current of 600 mA at 10V output. The complete schematic is shown in **Figure 2**. The frequency and maximum available  $I_{OUT}$  variation with  $V_{IN}$  are shown in **Figure 5** and **6**, and the efficiency for the  $I_{OUT}$  and  $V_{IN}$  design range is shown in **Figure 7**.

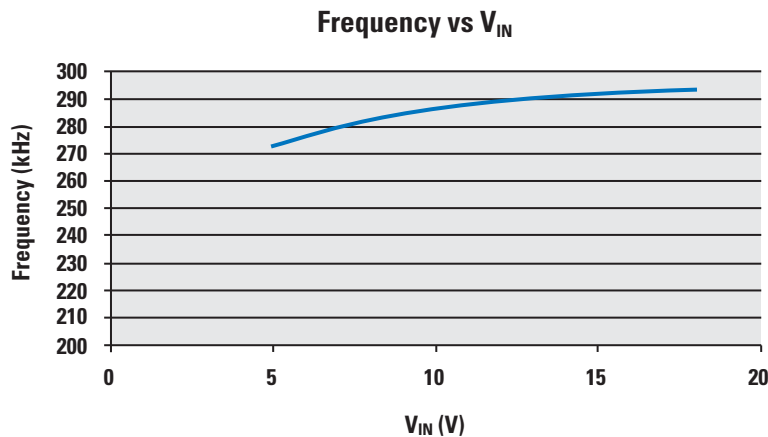


Figure 5. Frequency vs.  $V_{IN}$  in Zeta Configuration Based on LM5085

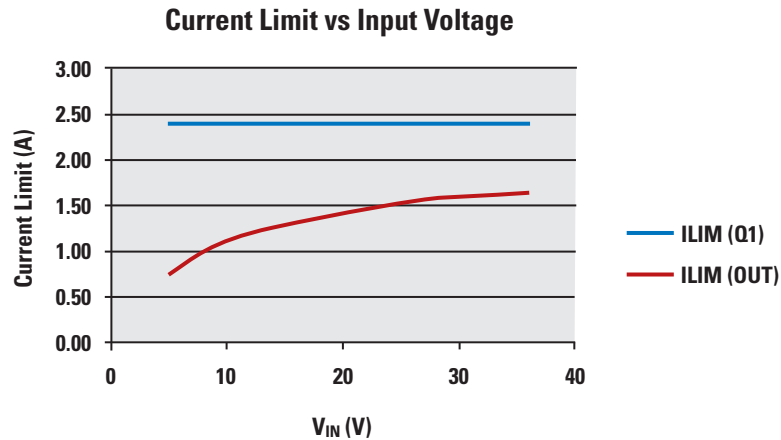


Figure 6. Peak Currents ( $I_{Q1}$  and  $I_{OUT}$ ) Variation with  $V_{IN}$ ,  $V_{OUT} = 10V$

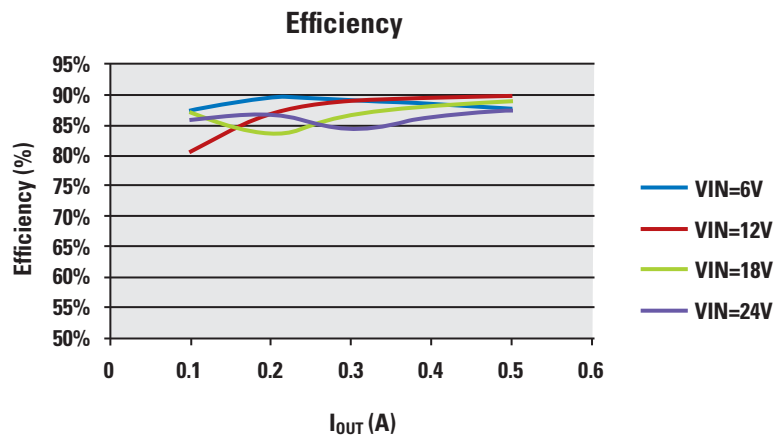


Figure 7. Efficiency of Zeta Converter,  $V_{OUT} = 10V$

## Conclusion

A non-inverting buck-boost with 10V regulated output voltage and 5-36V input voltage range with up to 600mA of guaranteed output current is presented based on the LM5085 COT P-FET buck controller. The operating principle of a Zeta converter is explained with the help of a simplified schematic and waveforms. The design equations and performance characteristics are also presented. LM5085 allows design of a non-inverting buck-boost converter based on a Zeta topology with

minimum effort, low solution cost, short circuit protection, and excellent transient response without any loop compensation design.

## References

- LM5085 Datasheet
- Application Note AN-1878
- LM5085 Evaluation Board
- LM(2)5085 Quick Start Calculator

# Power Design Tools

---



Design, build, and test analog circuits in this online design and prototyping environment.

[national.com/webench](http://national.com/webench)



Expand your knowledge and understanding of analog with our free online educational training tool.

[national.com/training](http://national.com/training)



National's monthly analog design technical journal.

[national.com/edge](http://national.com/edge)

## Tools for Energy-Efficient Designs

Access white papers, reference designs, and application notes on PowerWise® products and systems.

[national.com/powerwise](http://national.com/powerwise)

**National Semiconductor**  
2900 Semiconductor Drive  
Santa Clara, CA 95051  
1 800 272 9959

**Mailing address:**  
PO Box 58090  
Santa Clara, CA 95052

**Visit our website at:**  
[national.com](http://national.com)

**For more information,  
send email to:**  
[new.feedback@nsc.com](mailto:new.feedback@nsc.com)

## Don't miss a single issue!

Subscribe now to receive email alerts when new issues of Power Designer are available:

[national.com/powerdesigner](http://national.com/powerdesigner)

Read our Signal Path Designer® online today:

[national.com/spdesigner](http://national.com/spdesigner)



## 重要声明

德州仪器(TI) 及其下属子公司有权在不事先通知的情况下, 随时对所提供的产品和服务进行更正、修改、增强、改进或其它更改, 并有权随时中止提供任何产品和服务。客户在下订单前应获取最新的相关信息, 并验证这些信息是否完整且是最新的。所有产品的销售都遵循在订单确认时所提供的TI 销售条款与条件。

TI 保证其所销售的硬件产品的性能符合TI 标准保修的适用规范。仅在TI 保证的范围内, 且TI 认为有必要时才会使用测试或其它质量控制技术。除非政府做出了硬性规定, 否则没有必要对每种产品的所有参数进行测试。

TI 对应用帮助或客户产品设计不承担任何义务。客户应对其使用TI 组件的产品和应用自行负责。为尽量减小与客户产品和应用相关的风险, 客户应提供充分的设计与操作安全措施。

TI 不对任何TI 专利权、版权、屏蔽作品权或其它与使用了TI 产品或服务的组合设备、机器、流程相关的TI 知识产权中授予的直接或隐含权限作出任何保证或解释。TI 所发布的与第三方产品或服务有关的信息, 不能构成从TI 获得使用这些产品或服务的许可、授权、或认可。使用此类信息可能需要获得第三方的专利权或其它知识产权方面的许可, 或是TI 的专利权或其它知识产权方面的许可。

对于TI 的产品手册或数据表, 仅在没有对内容进行任何篡改且带有相关授权、条件、限制和声明的情况下才允许进行复制。在复制信息的过程中对内容的篡改属于非法的、欺诈性商业行为。TI 对此类篡改过的文件不承担任何责任。

在转售TI 产品或服务时, 如果存在对产品或服务参数的虚假陈述, 则会失去相关TI 产品或服务的明示或暗示授权, 且这是非法的、欺诈性商业行为。TI 对此类虚假陈述不承担任何责任。

TI 产品未获得用于关键的安全应用中的授权, 例如生命支持应用(在该类应用中一旦TI 产品故障将预计造成重大的人员伤亡), 除非各方官员已经达成了专门管控此类使用的协议。购买者的购买行为即表示, 他们具备有关其应用安全以及规章衍生所需的所有专业技术和知识, 并且认可和同意, 尽管任何应用相关信息或支持仍可能由TI 提供, 但他们将独力负责满足在关键安全应用中使用其产品及TI 产品所需的所有法律、法规和安全相关要求。此外, 购买者必须全额赔偿因在此类关键安全应用中使用TI 产品而对TI 及其代表造成的损失。

TI 产品并非设计或专门用于军事/航空应用, 以及环境方面的产品, 除非TI 特别注明该产品属于“军用”或“增强型塑料”产品。只有TI 指定的军用产品才满足军用规格。购买者认可并同意, 对TI 未指定军用的产品进行军事方面的应用, 风险由购买者单独承担, 并且独力负责在此类相关使用中满足所有法律和法规要求。

TI 产品并非设计或专门用于汽车应用以及环境方面的产品, 除非TI 特别注明该产品符合ISO/TS 16949 要求。购买者认可并同意, 如果他们在汽车应用中使用任何未被指定的产品, TI 对未能满足应用所需要求不承担任何责任。

可访问以下URL 地址以获取有关其它TI 产品和应用解决方案的信息:

	产品		应用
数字音频	<a href="http://www.ti.com.cn/audio">www.ti.com.cn/audio</a>	通信与电信	<a href="http://www.ti.com.cn/telecom">www.ti.com.cn/telecom</a>
放大器和线性器件	<a href="http://www.ti.com.cn/amplifiers">www.ti.com.cn/amplifiers</a>	计算机及周边	<a href="http://www.ti.com.cn/computer">www.ti.com.cn/computer</a>
数据转换器	<a href="http://www.ti.com.cn/dataconverters">www.ti.com.cn/dataconverters</a>	消费电子	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
DLP® 产品	<a href="http://www.dlp.com">www.dlp.com</a>	能源	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
DSP - 数字信号处理器	<a href="http://www.ti.com.cn/dsp">www.ti.com.cn/dsp</a>	工业应用	<a href="http://www.ti.com.cn/industrial">www.ti.com.cn/industrial</a>
时钟和计时器	<a href="http://www.ti.com.cn/clockandtimers">www.ti.com.cn/clockandtimers</a>	医疗电子	<a href="http://www.ti.com.cn/medical">www.ti.com.cn/medical</a>
接口	<a href="http://www.ti.com.cn/interface">www.ti.com.cn/interface</a>	安防应用	<a href="http://www.ti.com.cn/security">www.ti.com.cn/security</a>
逻辑	<a href="http://www.ti.com.cn/logic">www.ti.com.cn/logic</a>	汽车电子	<a href="http://www.ti.com.cn/automotive">www.ti.com.cn/automotive</a>
电源管理	<a href="http://www.ti.com.cn/power">www.ti.com.cn/power</a>	视频和影像	<a href="http://www.ti.com.cn/video">www.ti.com.cn/video</a>
微控制器 (MCU)	<a href="http://www.ti.com.cn/microcontrollers">www.ti.com.cn/microcontrollers</a>		
RFID 系统	<a href="http://www.ti.com.cn/rfidsys">www.ti.com.cn/rfidsys</a>		
OMAP 机动性处理器	<a href="http://www.ti.com/omap">www.ti.com/omap</a>		
无线连通性	<a href="http://www.ti.com.cn/wirelessconnectivity">www.ti.com.cn/wirelessconnectivity</a>		
	德州仪器在线技术支持社区		<a href="http://www.deyisupport.com">www.deyisupport.com</a>

邮寄地址: 上海市浦东新区世纪大道 1568 号, 中建大厦 32 楼 邮政编码: 200122  
Copyright © 2011 德州仪器 半导体技术 (上海) 有限公司