

## TI 设计: TIDA-01348

# 适用于汽车 LED 照明系统的 CISPR 25 5 类 7.5W 额定功率尾灯参考设计



### 说明

TIDA-01348 TI 设计详细展示了一款用于汽车尾灯应用的解决方案。该设计采用同步降压转换器 (LM53601-Q1) 供电的 TPS92638-Q1 线性 LED 驱动器, 该转换器直接通过汽车电池电压供电。该设计无需共模扼流线圈 (CMCC) 滤波器即可符合 CISPR 25 5 类传导发射和辐射发射标准, 且能够提高解决方案效率。

### 资源

<a href="#">TIDA-01348</a>	设计文件夹
<a href="#">LM53601-Q1</a>	产品文件夹
<a href="#">TPS92638-Q1</a>	产品文件夹
<a href="#">TLC2274A-Q1</a>	产品文件夹

### 特性



- 9V 至 36V 输入、八通道 LED 照明和 7.5W 总输出
- 具有频率为 2.1MHz 的同步降压转换器
- 符合 CISPR 25 5 类传导发射标准; 无需 CMCC 滤波器即可通过 AM 和 FM 无线电频带测试
- 具有方便易用的内置补偿
- 解决方案大小: 42.5mm x 32.6mm; 覆铜 1 盎司的四层电路板

### 应用

- [汽车 LED 照明](#)



咨询我们的 E2E 专家

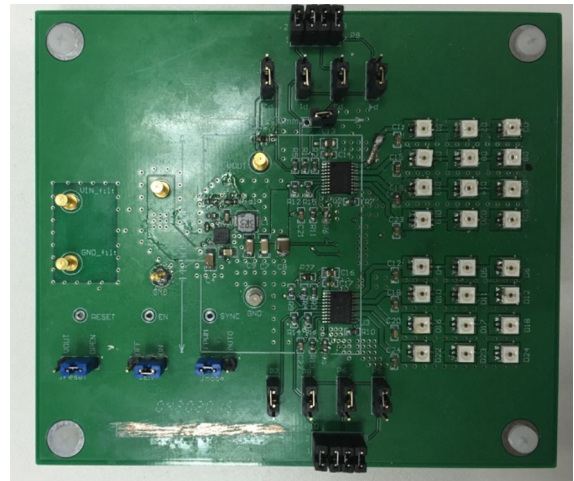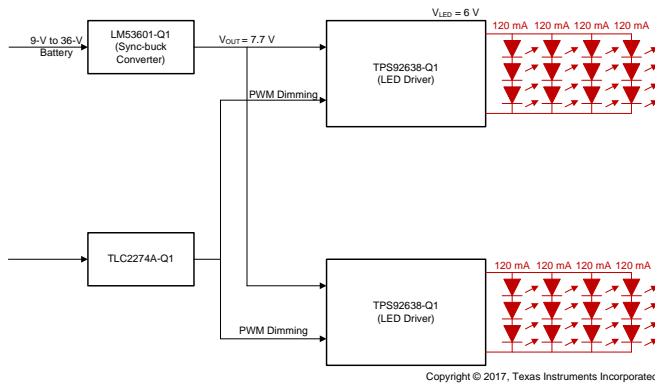

该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

## 1 System Description

The TIDA-01348 is a CISPR 25 Class-5 rated 7.5-W tail-light reference design which features the TPS92638-Q1 linear light-emitting diode (LED) driver powered by a synchronous buck converter (LM53601) that is directly supplied from the automotive-battery voltage. This design applies to automotive high-brightness lighting such as headlights and taillights and also interior LED lighting systems. This design passes CISPR 25 Class-5 conducted emissions and radiated emissions without a CMCC filter and also optimizes the solution efficiency.

### 1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	COMMENTS	SPECIFICATION
$V_{IN}$ minimum	Minimum input voltage	9-V DC
$V_{IN}$ maximum	Maximum input voltage	36-V DC
$V_{OUT\_Buck}$	Buck output voltage	7.7-V DC
$V_{OUT\_LED}$	LED output voltage	6 V (max)
$I_{OUT}$	Output current	1 A
$I_{LED}$	LED drive current (per channel)	120 mA
$f_s$ J5	Buck switching frequency	2.1 MHz
$I_{Dim}$ J7	LED dimming	0 mA to 120 mA

## 2 System Overview

### 2.1 Block Diagram

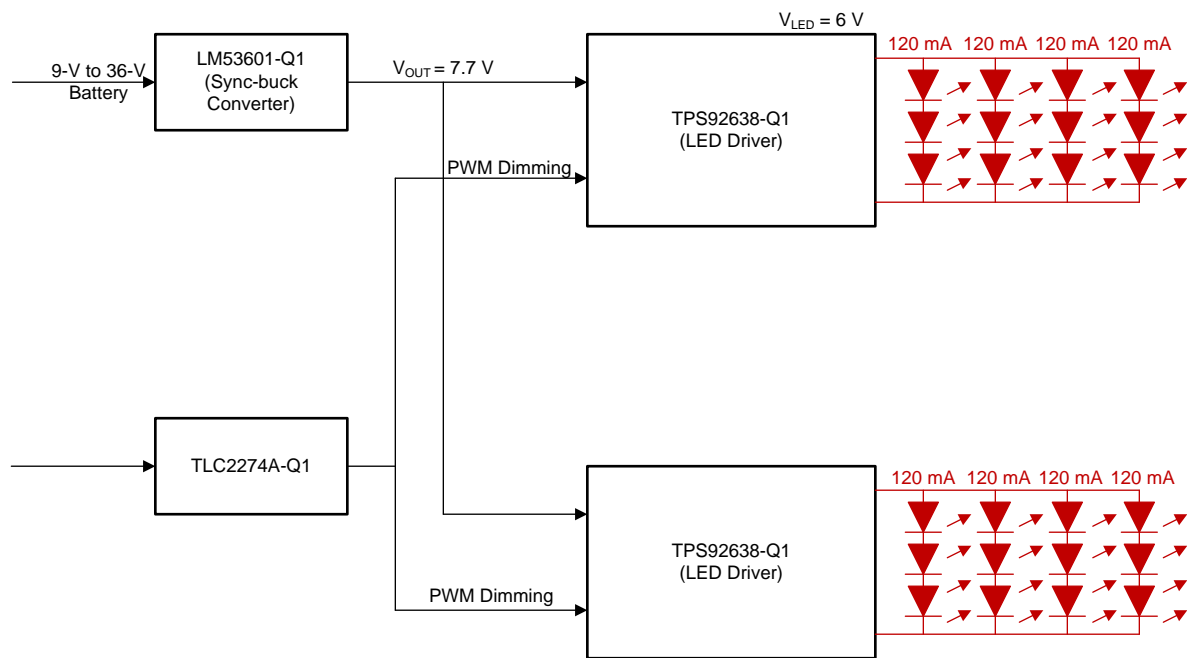


图 1. TIDA-01348 Block Diagram

## 2.2 Highlighted Products

### 2.2.1 LM53601-Q1

- AEC-Q100 qualified with  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  ambient operating temperature range
- Wide operating input voltage: 3.55 V to 36 V (with transient to 42 V)
- Spread spectrum option available
- 2.1-MHz fixed switching frequency
- Low output voltage noise:  $25\ \mu\text{V}_{\text{RMS}}$
- Pin-selectable forced pulse-width modulation (PWM) mode
- External frequency synchronization
- Internal compensation
- 10-lead, 3-mm x 3-mm SON package with wettable flanks

### 2.2.2 TPS92638-Q1

- AEC-Q100 qualified with  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  ambient operating temperature range
- Eight-channel LED driver with analog and PWM
- Four-bank PWM dimming to control eight channels
- Open- and shorted-LED detection with deglitch
- Single resistor for stop-current set point
- Single resistor for tail-current set point
- Package: 20-pin thermally enhanced PWP package (PDSO)

### 2.2.3 TLC2274A-Q1

- AEC-Q100 qualified with  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  ambient operating temperature range
- Output swing includes both supply rails
- Low noise:  $9\ \text{nV}/\sqrt{\text{Hz}}$  typical at  $f = 1\ \text{kHz}$
- Fully specified for both single-supply and split-supply operation
- Common-mode input voltage range includes negative rail
- High-gain bandwidth: 2.2 MHz typical
- High slew rate:  $3.6\ \text{V}/\mu\text{s}$  typical

### 3 System Design

#### 3.1 Buck Converter Design

The LM53601 is available in 3.3-V or 5.0-V fixed and adjustable versions, which can be programmed using a resistor divider and feedback voltage. With a red LED, each maximum drop voltage is about 2.0 V. A 1.5-V drop out between  $V_{IN}$  and  $V_{OUT}$  of LED driver is required to deliver 120 mA per channel.

When setting the output voltage of the LM53601 device at 7.7 V and  $R_{fb2} = 10 \text{ k}\Omega$ ,  $R_{fb1}$  can be derived using [公式 1](#).

$$R_{fb1} = \left( \frac{V_{OUT\_BUCK}}{V_{REF}} - 1 \right) \times R_{fb2} = 67 \text{ k}\Omega \quad (1)$$

where,


- $V_{REF}$  is the reference voltage of LM53601 and is equal to 2 V.

In the buck converter, the ripple of the inductor enlarges with the input voltage rising. During a 7.7- $V_{OUT}$  condition, the minimum ON time has not been triggered. Setting the ripple at a 36- $V_{IN}$  is an 80% ratio of the output current, for which the inductance can be calculated using [公式 2](#):

$$L_f = \frac{V_{OUT\_BUCK} \times \left( 1 - \frac{V_{OUT\_BUCK}}{V_{IN\_MAX}} \right)}{0.4 \times I_{OUT} \times f_s} = 3.6 \text{ }\mu\text{H} \quad (2)$$

Choose  $L_f = 4.7 \text{ }\mu\text{H}$ .

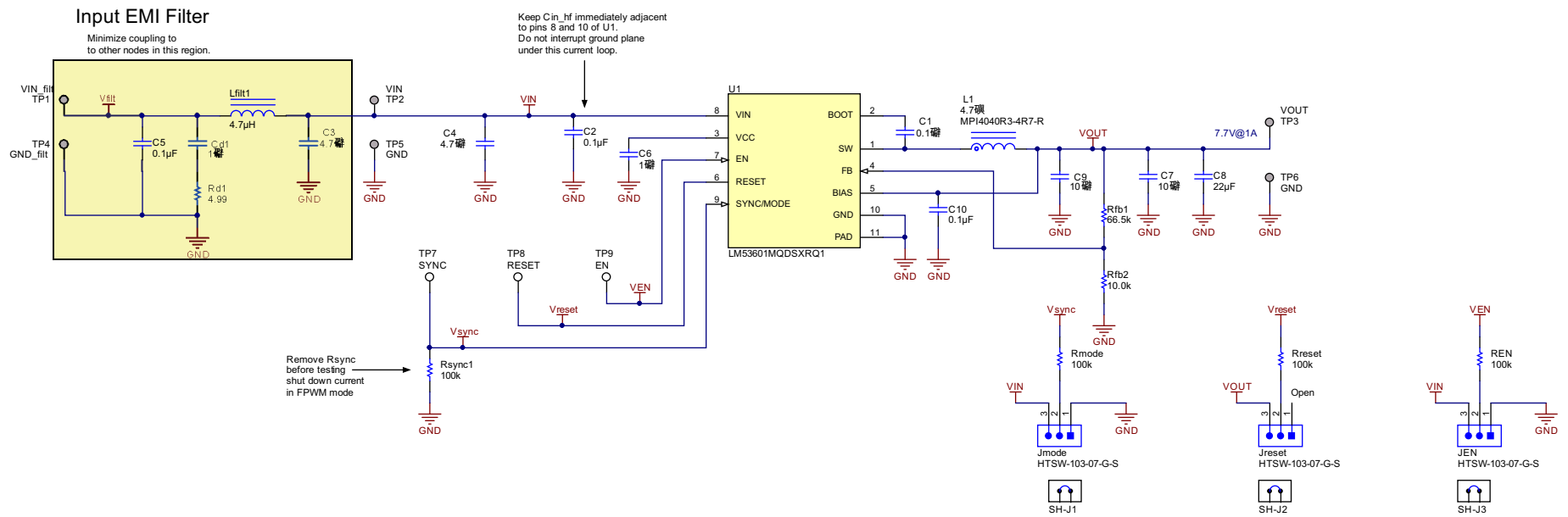[图 2](#) shows a schematic of the DC-DC converter.



Copyright © 2017, Texas Instruments Incorporated

图 2. Buck Converter LM53601 Schematic

### 3.2 LED Driver Design

The TPS92638-Q1 is an eight-channel linear LED driver with PWM dimming control. Independent linear current regulators control the eight LED output channels. Global external resistors set the current of each channel. The device also features two current levels, which are intended for stop and tail applications.

The internal current reference,  $I_{REF}$ , has two possible values depending on the state of the STOP input: When STOP is low, REF, which is the current drawn from the REF pin, controls the output current. When STOP is high, the sum of the currents drawn from the REFHI pin and REF pin controls the output current.

公式 3 和 公式 4 calculate values for the current-setting resistors.

**When STOP = low:**

$$I_{OUT\_TAIL} = \frac{V_{REF\_LED} \times G_{(I)}}{R_{REF}}$$

$$R_{REF} = \frac{V_{REF\_LED} \times G_{(I)}}{I_{OUT\_TAIL}} = 9.76 \text{ k}\Omega$$

where

- $V_{REF\_LED} = 1.222 \text{ V}$  is the internal reference voltage of TPS92638
- $G_{(I)} = 200$  is the ratio of output current to reference current
- $I_{OUT\_TAIL} = 25 \text{ mA}$  is the tail current of each channel.

(3)

**When STOP = high:**

$$I_{OUT\_STOP} = \frac{V_{REF\_LED} \times G_{(I)}}{R_{REF}} + \frac{V_{REF\_LED} \times G_{(I)}}{R_{REFHI}}$$


$$R_{REFHI} = \frac{V_{REF\_LED} \times G_{(I)}}{I_{OUT\_STOP} - \frac{V_{REF\_LED} \times G_{(I)}}{R_{REF}}} = 6.98 \text{ k}\Omega$$

where

- $I_{OUT\_STOP} = 60 \text{ mA}$  is the stop current of each channel.

(4)

图 3 shows the schematic of the LED driver part.

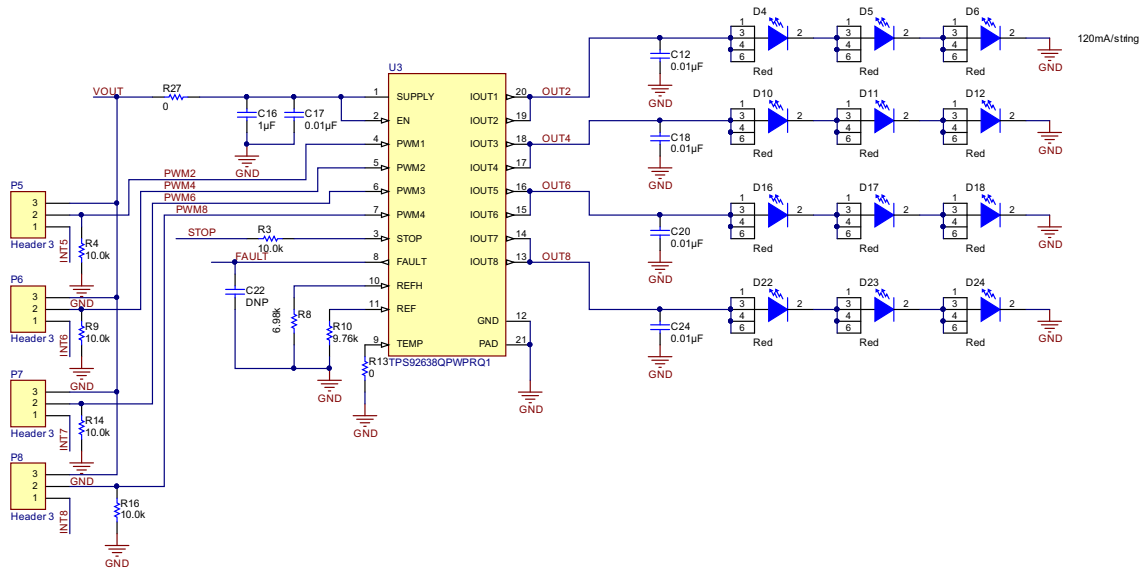

Copyright © 2017, Texas Instruments Incorporated


图 3. TPS92638 LED Driver Schematic

### 3.3 PWM Generation Design

This design uses the TLC2274A to generate PWM to control the LED driver dimming. 图 4 shows a schematic of the TLC2274A-Q1.

In this schematic, U4C works as an amplifier and is capable of generating a similar triangle waveform at pin 9. The minimum and maximum voltage is relatively  $V_{OUT} / 3$  and  $2V_{OUT} / 3$ . The period is:  $(2R_{23} \times C_{26} \times \ln 2)$ . U4B works as a comparator: When pin 3 voltage rises, pin 1 voltage also rises, which generates a larger duty cycle PWM through U4B. As R19 and C25 work as an RC filter, the crossover frequency must be smaller than one-tenth of the PWM frequency, which means that R23, C26, R19, and C25 must be calculated as shown in 公式 5.
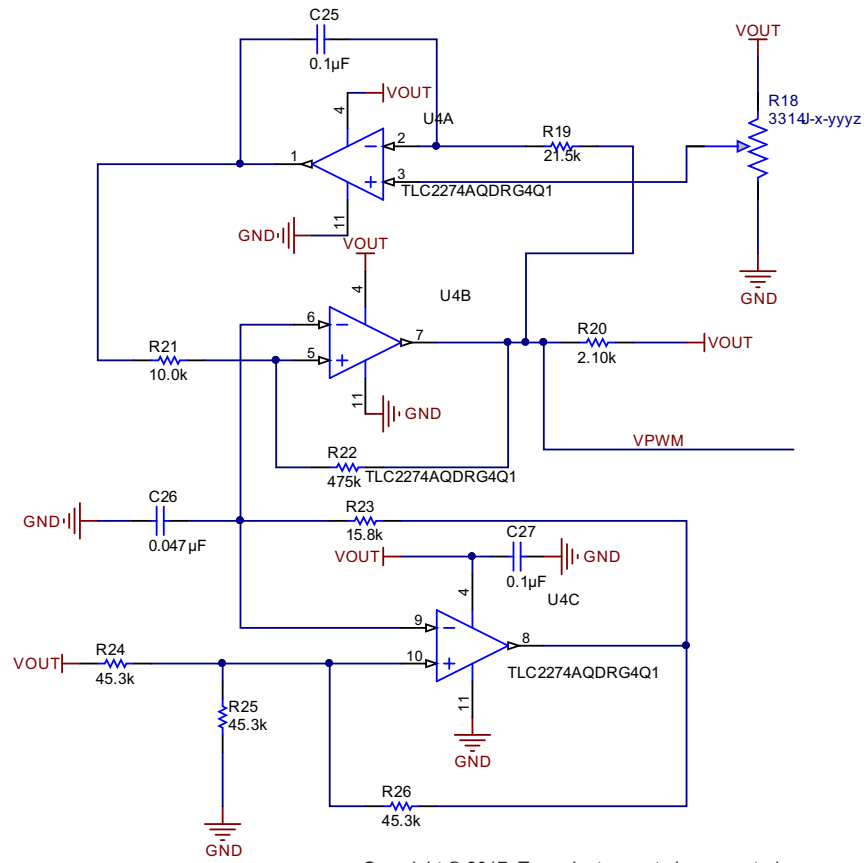
$$\frac{1}{2\pi \times R_{19} \times C_{25}} \leq \frac{1}{10} \times \frac{1}{2R_{23} \times C_{26} \times \ln 2} \quad (5)$$



Copyright © 2017, Texas Instruments Incorporated

图 4. TLC2274A-Q1 PWM Generation Schematic



## 4 Test Results

### 4.1 Thermal Data

The infrared thermal images in 图 5 and 图 6 were taken at a steady state at STOP = high, duty cycle = 100%, and  $V_{IN} = 9\text{ V}$  and  $24\text{ V}$  for two minutes with no airflow.

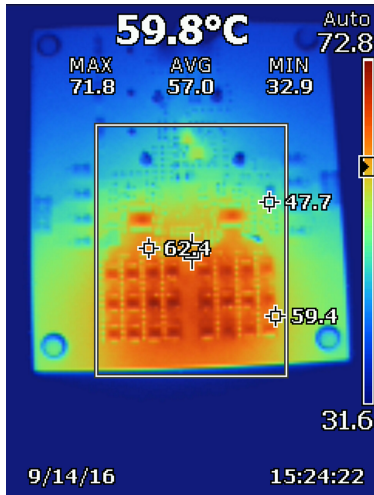


图 5. Thermal Data at  $9\text{ V}_{IN}$

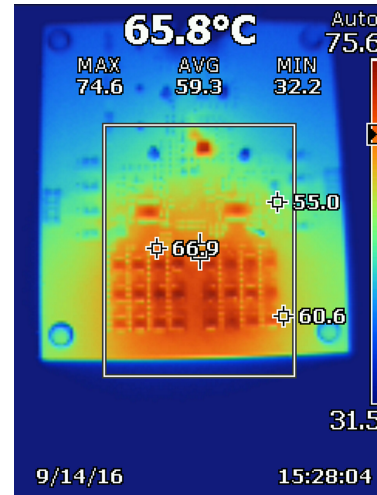


图 6. Thermal Data at  $24\text{ V}_{IN}$

### 4.2 Efficiency Data

图 7 shows the efficiency at various input conditions.

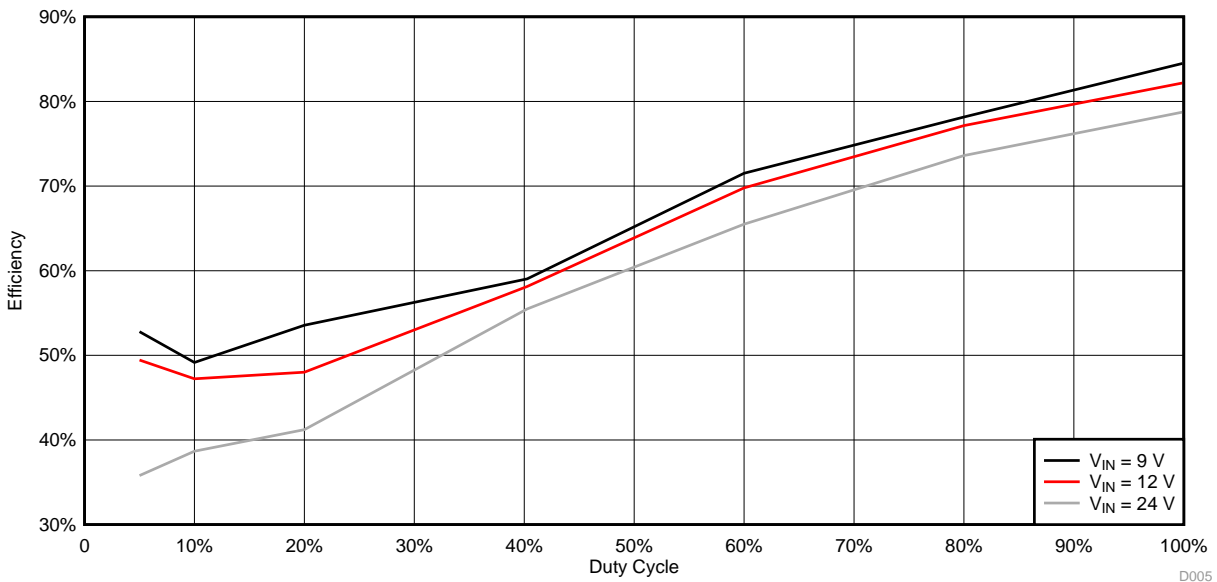


图 7. Efficiency versus Duty Cycle at Various Input Voltages

**表 2. Efficiency Data Table at 9 V<sub>IN</sub>**

V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	I <sub>o</sub> (mA)	DUTY	V <sub>o</sub> (V)	EFFICIENCY (%)
9.056	0.0693	17.7	0.05	2.34	52.80
9.045	0.1244	25.8	0.10	2.68	49.16
9.030	0.1834	36.0	0.20	3.08	53.56
9.098	0.3695	60.8	0.40	4.08	59.03
9.062	0.5472	89.8	0.60	4.94	71.51
9.029	0.7071	112.0	0.80	5.57	78.16
8.995	0.8701	139.0	1.00	5.95	84.52

**表 3. Efficiency Data Table at 12 V<sub>IN</sub>**

V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	I <sub>o</sub> (mA)	DUTY	V <sub>o</sub> (V)	EFFICIENCY (%)
12.012	0.0543	17.3	0.05	2.33	49.44
12.073	0.0974	26.0	0.10	2.67	47.23
12.063	0.1554	35.7	0.20	3.15	48.01
12.037	0.2852	61.2	0.40	4.08	58.13
12.011	0.4215	89.4	0.60	4.94	69.79
12.089	0.5403	113.0	0.80	5.57	77.15
12.065	0.6627	138.0	1.00	5.95	82.21

**表 4. Efficiency Data Table at 24 V<sub>IN</sub>**

V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	I <sub>o</sub> (mA)	DUTY	V <sub>o</sub> (V)	EFFICIENCY (%)
24.201	0.0382	17.6	0.05	2.35	35.79
24.197	0.0598	26.2	0.10	2.67	38.68
24.191	0.0885	35.1	0.20	3.14	41.22
24.180	0.1533	63.0	0.40	4.08	55.47
24.166	0.2210	88.4	0.60	4.95	65.49
24.154	0.2831	113.0	0.80	5.57	73.60
24.142	0.3462	138.0	1.00	5.96	78.77

## 5 Waveform

### 5.1 Start-Up

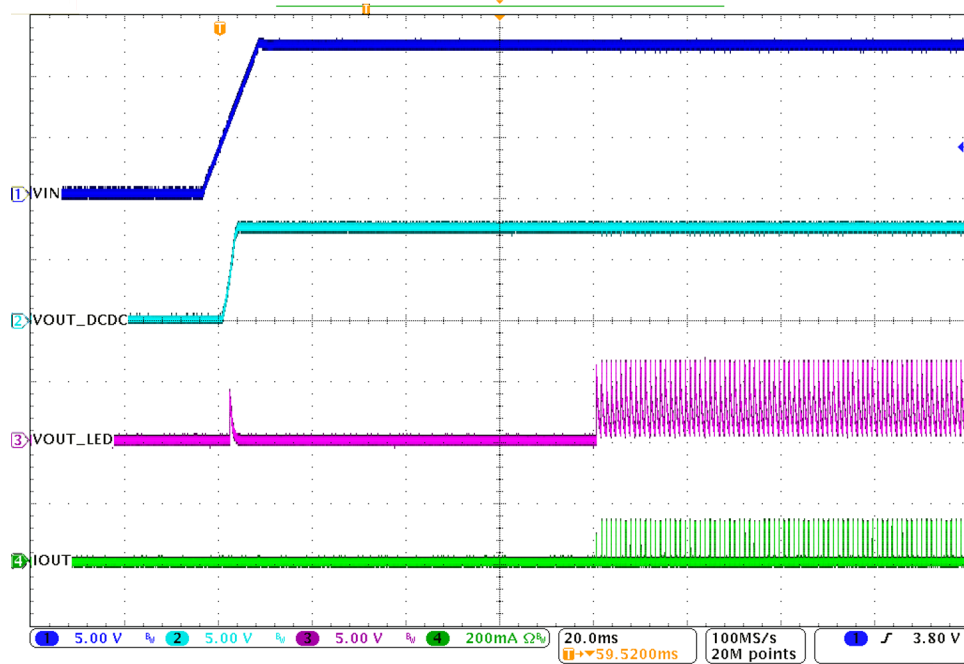


图 8. Start-Up:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 5%

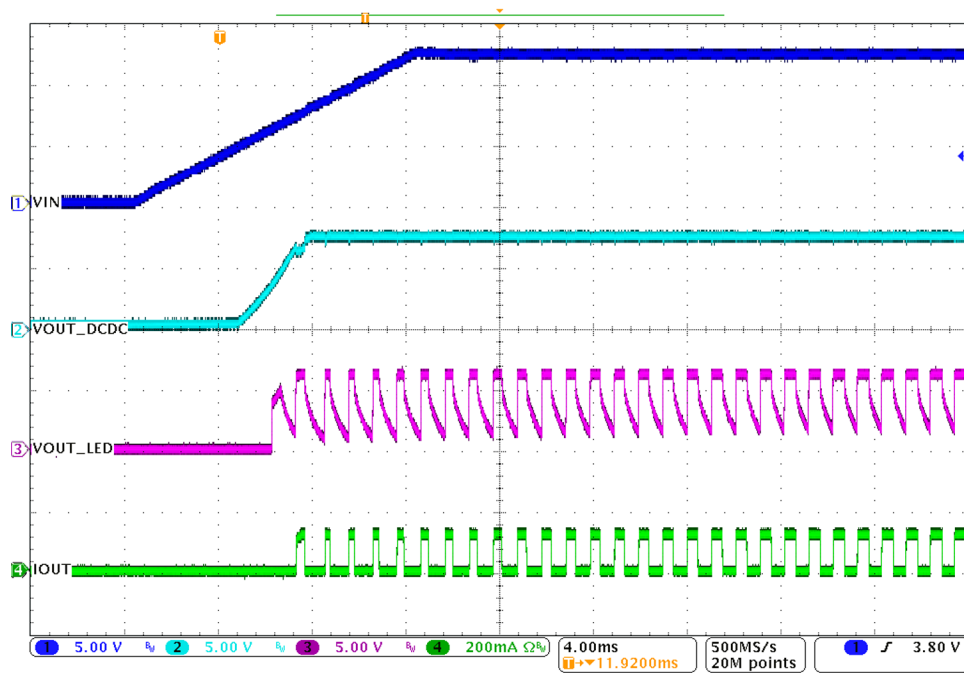


图 9. Start-Up:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 50%

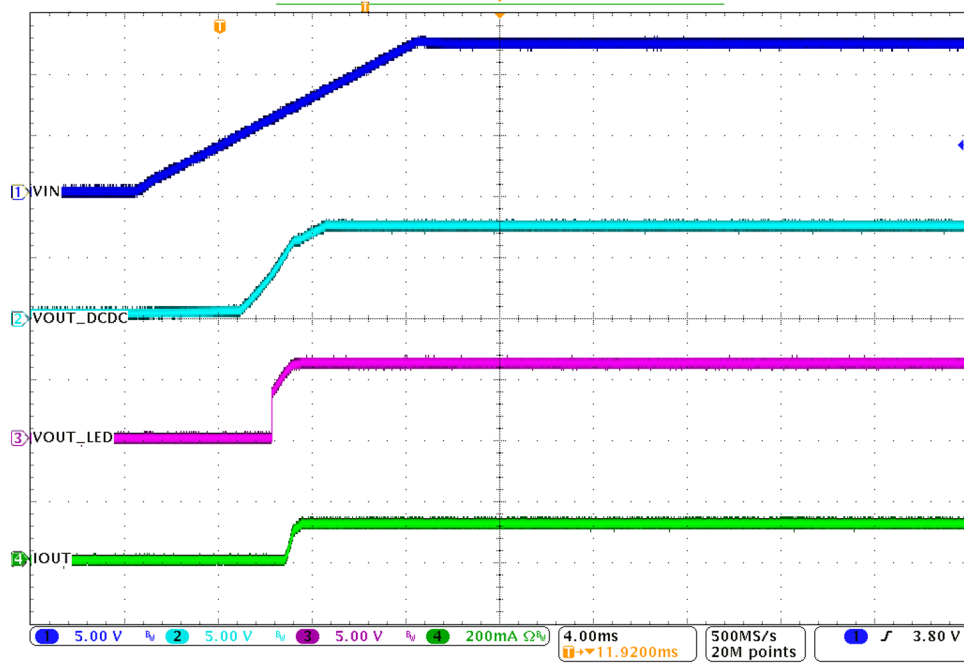


图 10. Start-Up:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 100%

## 5.2 Shut Down

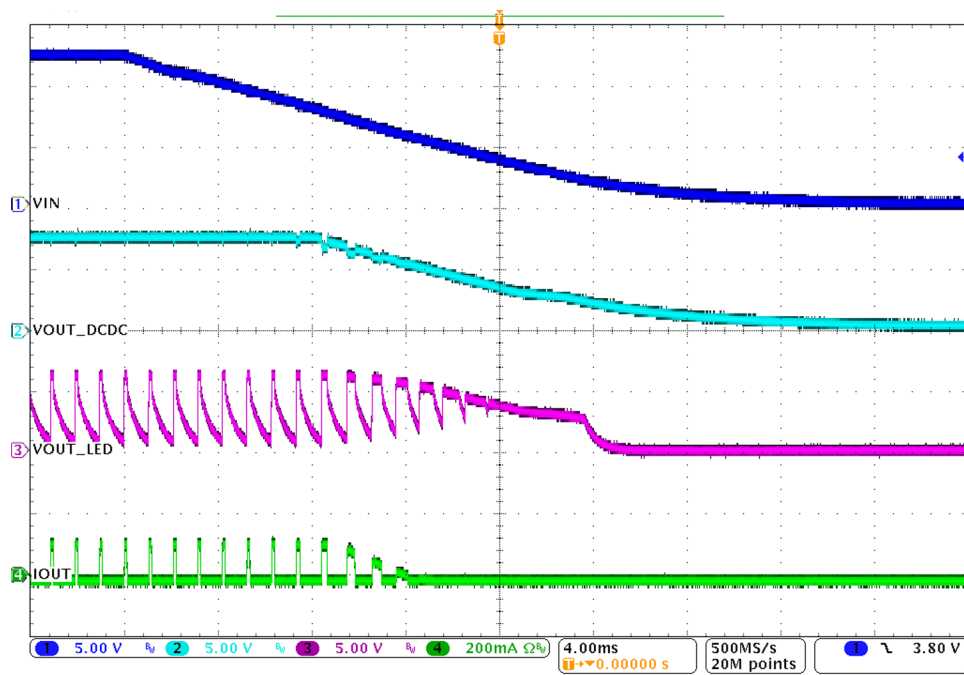


图 11. Shut Down:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 5%

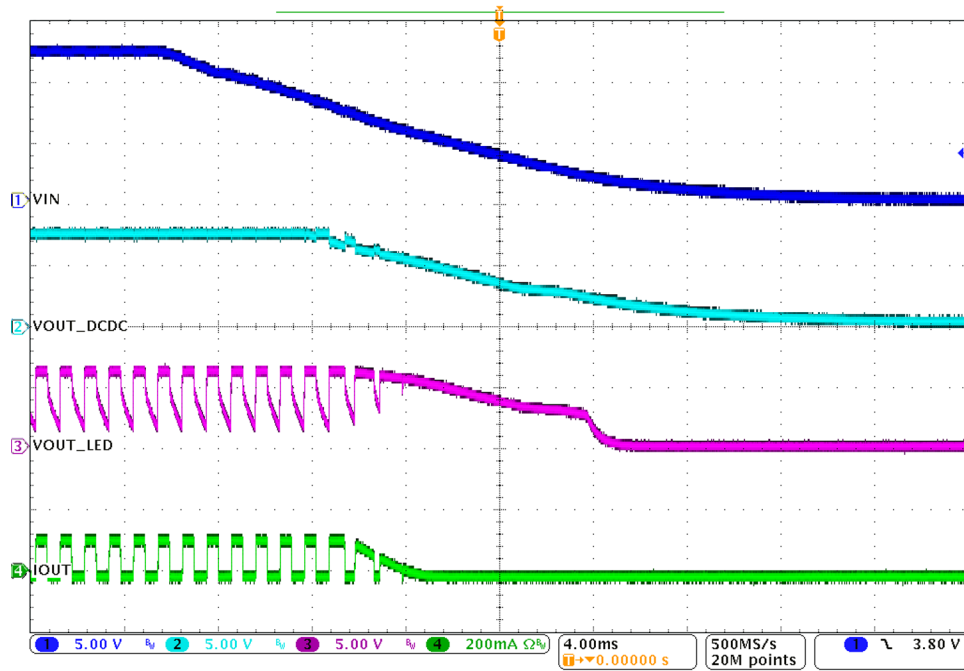


图 12. Shut Down:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 50%

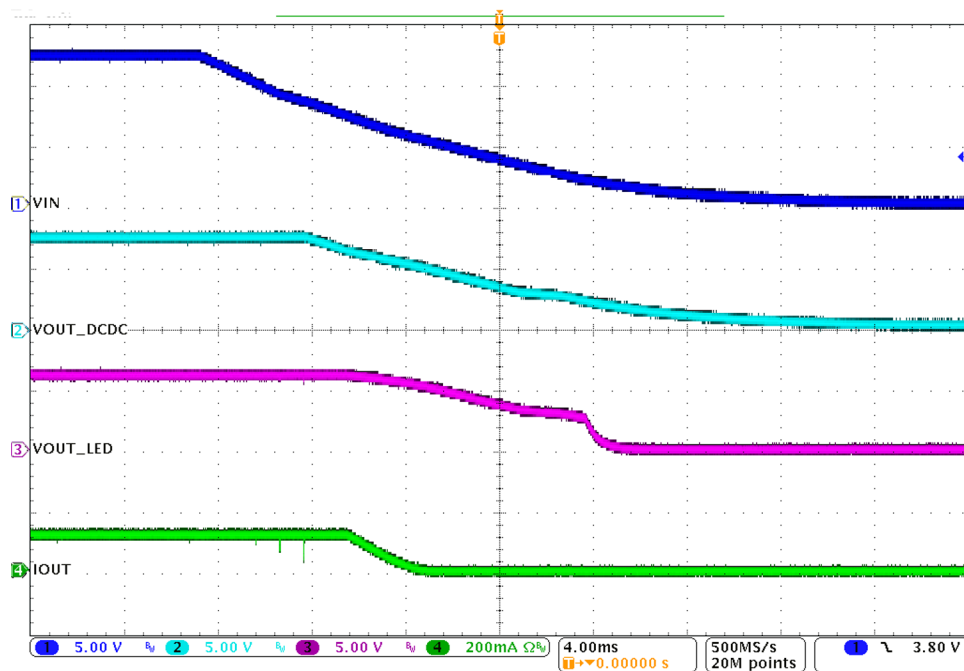


图 13. Shut Down:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 100%

### 5.3 Steady State

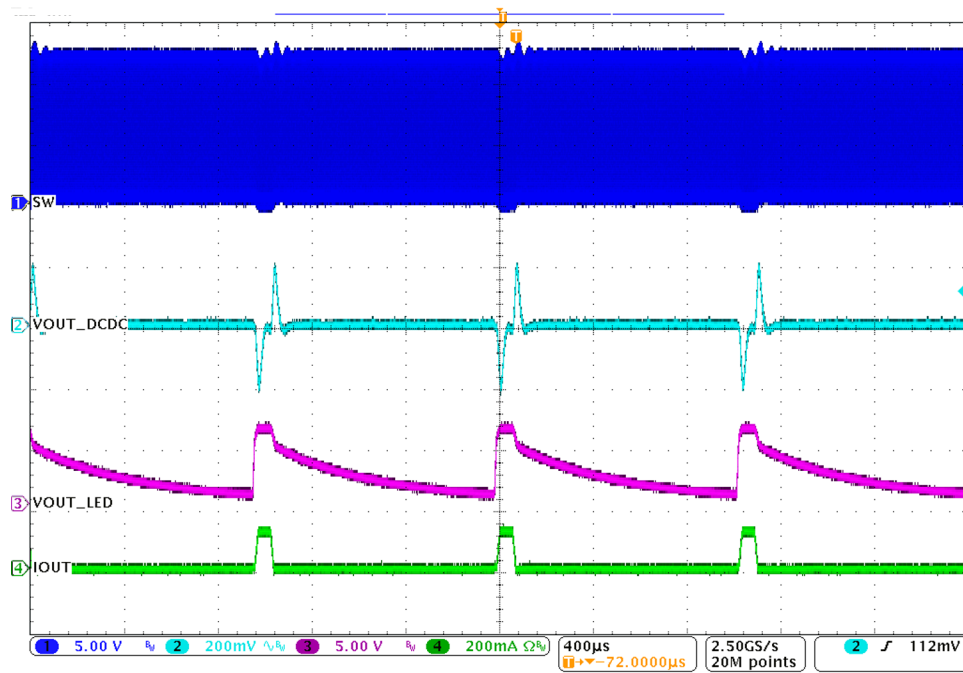


图 14. Steady State:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 5%

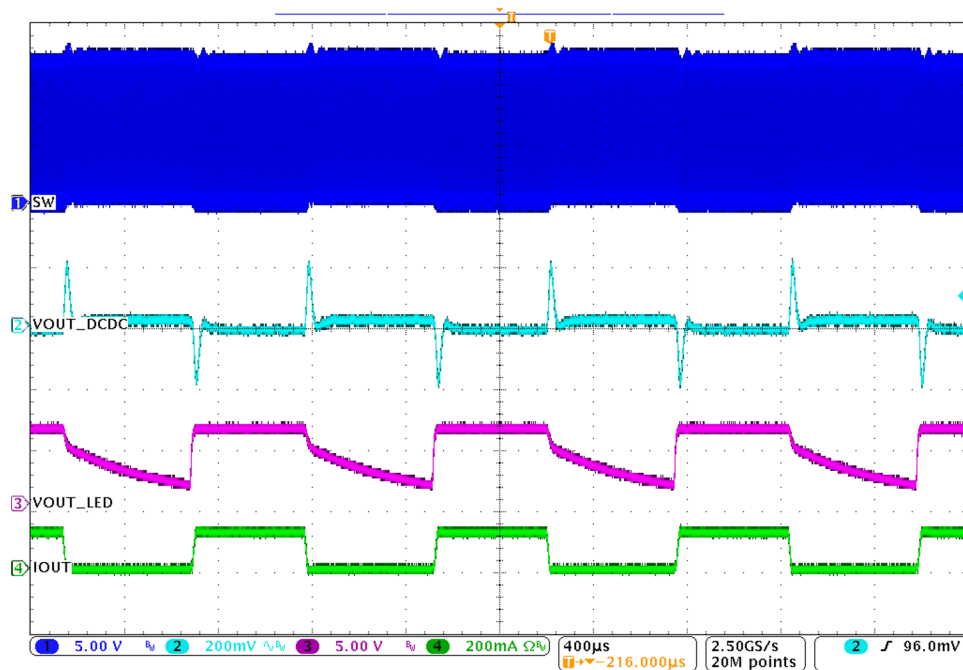


图 15. Steady State:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 50%

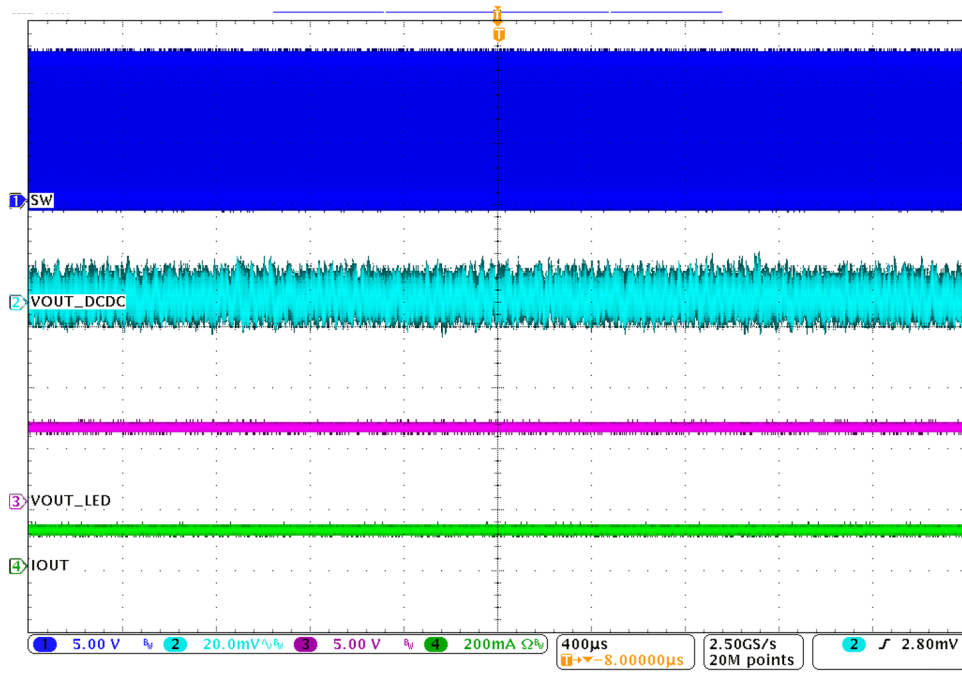


图 16. Steady State:  $V_{IN} = 12\text{ V}$ , Duty Cycle = 100%

## 6 EMI Test Results

CISPR 25-EMI testing is completed at a third-party facility. Both conducted and radiated emissions tests are completed. When viewing the results, the blue lines are Class-5 limits for the peak emissions limits and the green lines are the average emissions limits. The following graphs show that the TIDA-01348 design can pass CISPR 25 Class-5 specifications without requiring a CMCC filter.

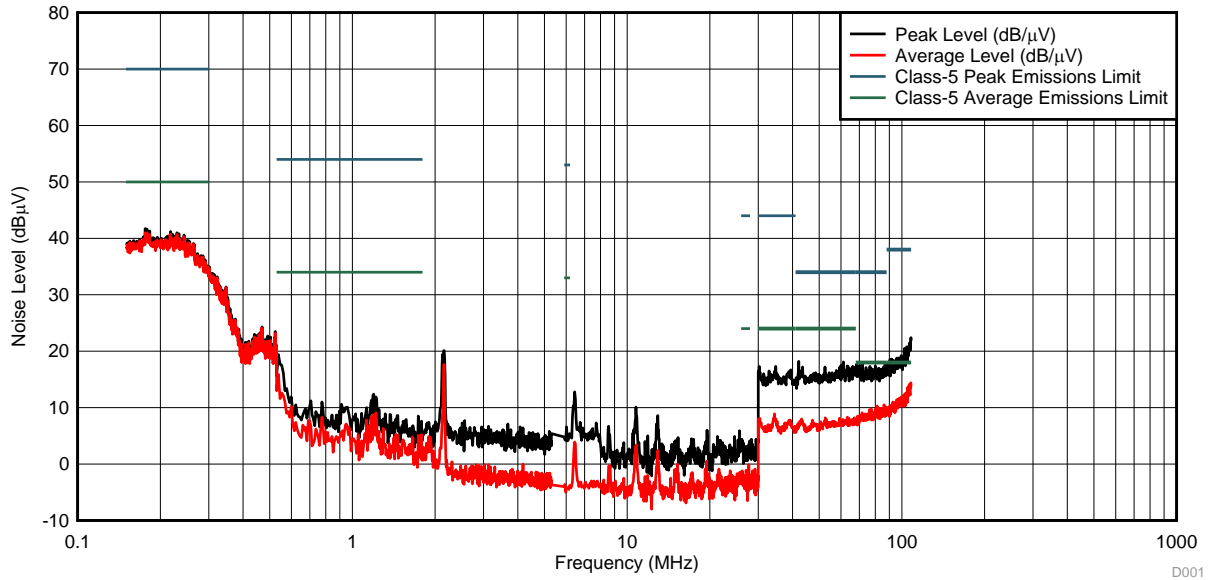


图 17. Conducted Emissions Positive

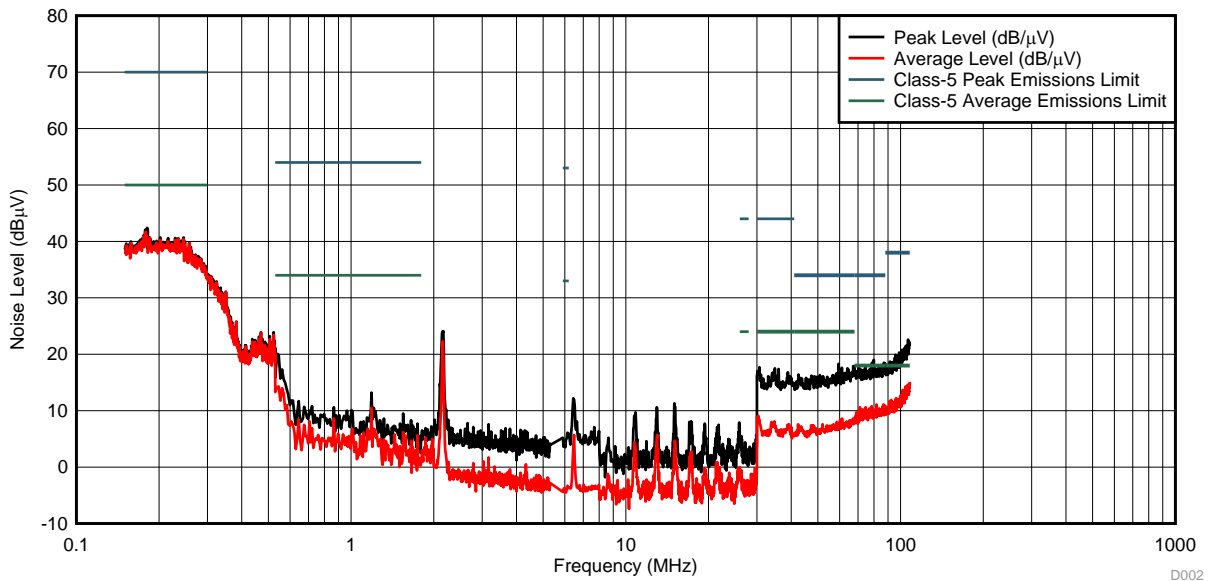


图 18. Conducted Emissions Negative



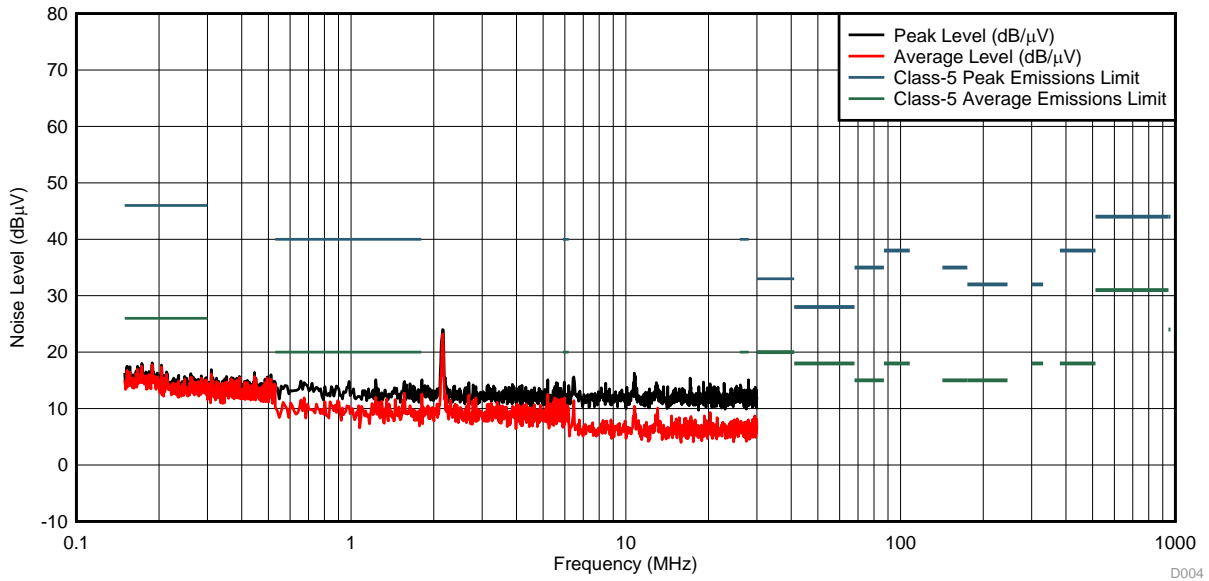


图 19. Radiated Emissions of 150 kHz to 30 MHz

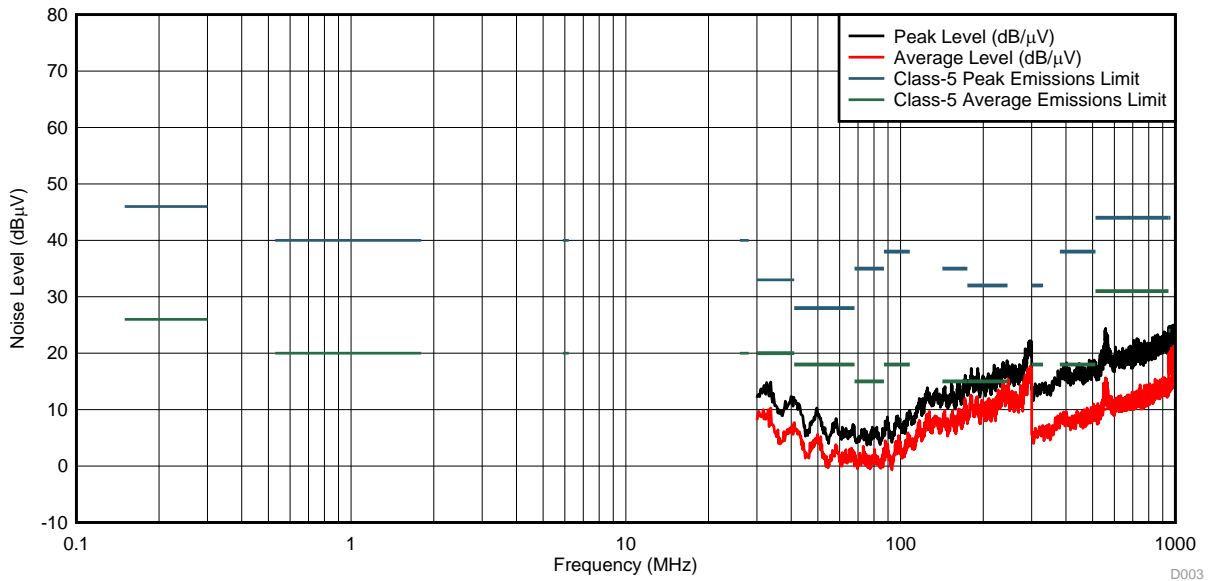


图 20. Radiated Emissions of 30 MHz to 1000 MHz

## 7 Design Files

### 7.1 Schematics

To download the schematics, see the design files at [TIDA-01348](#).

### 7.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01348](#).

### 7.3 PCB Layout Recommendations

#### 7.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01348](#).

### 7.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01348](#).

### 7.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01348](#).

### 7.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01348](#).

## 8 Related Documentation

1. Texas Instruments, [LM53600/01-Q1, 0.65A/1A, 36V Synchronous, 2.1MHz, Automotive Step Down DC-DC Converter](#), LM53600-Q1/LM53601-Q1 Data Sheet (SNAS660)
2. Texas Instruments, [TPS92638-Q1 8-Channel Linear LED Driver With PWM Dimming](#), TPS92638-Q1 Data Sheet (SLVSCK5)
3. Texas Instruments, [TLC227x-Q1 Advanced LinCMOS™ Rail-To-Rail Operational Amplifiers](#), TLC227x-Q1/TLC227xA-Q1 Data Sheet (SGLS007)

### 8.1 商标

All trademarks are the property of their respective owners.

## 有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。您就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等产权包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默认的保证或陈述，包括但不限于对准确性或完整性、产权保证、无复发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、[评估模块](http://www.ti.com/sc/docs/sampters.htm)和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2017 德州仪器半导体技术（上海）有限公司