

TI Designs: TIDA-01423

3V 至 4.5V 输入电压、400mA、-12V 反向降压/升压参考设计



说明

TIDA-01423 TI 设计演示了反相降压-升压转换器（电压反相器），用于在 3V 至 4.5V 的输入电压下生成 -12V 的电压轨（电流为 400mA）。许多通信设备系统和工业设备（如测试和测量）需要此类负电压。使用 TPS62136 降压转换器可以实现非常简单的负电压反相器（反相降压/升压）设计，以便在 400mA 的电流下生成 12V 的负输出电压。

资源

[TIDA-01423](#) 设计文件夹
[TPS62136](#) 产品文件夹




咨询我们的 E2E 专家

特性


- 高输出负电压，为 -12V
- 总体解决方案尺寸小于 65mm²
- 高输出电流，为 400mA
- 低输出电压波纹 (<0.5%)
- 输入电压范围为 3V 至 4.5V

应用

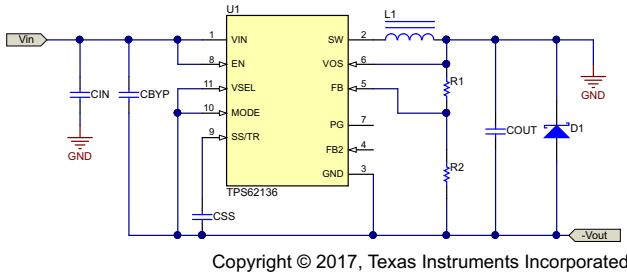- 电信基础设施
- 无线基础设施
- 光学模块
- 光纤网络: EPON
- 远程射频单元 (RRU)



 Copyright © 2017, Texas Instruments Incorporated



该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Description

A negative voltage in the range of -5 V to -12 V is frequently required in high-performance communications equipment systems, such as optical modules and remote radio units.

In an optical module, the negative voltage is required to supply modulators like the electroabsorption modulator (EAM) or Mach-Zehnder modulator (MZM). The high efficiency (low temperature rise) and small size is very important in such systems.

Such high negative voltages are also required for the new Gallium Nitride (GaN) technology (field-effect transistor (FET) and RF power amplifier) used in antenna systems and remote radio units.

The wide-output voltage range supports many of the different voltages required in such systems, which enables the same design to be reused for different systems that have different negative voltage rails.

1.1 Key System Specifications

表 1. Key System Specifications

PARAMETERS	SPECIFICATIONS	DETAILS
Input voltage range (V_{IN})	3 V to 4.5 V	—
Output voltage (V_{OUT})	-12 V	—
Output current	0.4 A	图 4

2 System Overview

2.1 Highlighted Products


2.1.1 TPS62136

The TPS62136 is a 4-A, step-down converter in a 2x3-mm QFN package based on a distributed control system (DCS). The device accepts up to a 17-V input voltage and supports up to 12 V on its output. This wide-input voltage range is ideally suited for an inverting converter, which, at a minimum, requires a voltage rating of the input voltage plus the output voltage.

2.2 Design Considerations

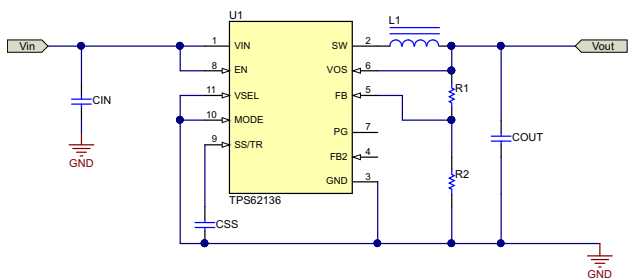
2.2.1 Inverting Buck-Boost Topology Concept

The inverting buck-boost topology is very similar to the buck topology. In the buck configuration that 图 1 shows: the positive connection (V_{OUT}) is connected to the inductor and the return connection is connected to the ground (GND) pin of the integrated circuit (IC). However, in the inverting buck-boost configuration that 图 2 shows, the IC ground is used as the negative output voltage pin (labeled as $-V_{OUT}$). The former positive output in the buck configuration is used as the ground. This inverting topology allows the output voltage to be inverted and always lower than the ground.



Copyright © 2017, Texas Instruments Incorporated

图 1. TPS62136 Buck Topology

 

Copyright © 2017, Texas Instruments Incorporated

图 2. TPS62136 Inverting Buck-Boost Topology

The circuit operation is different in the inverting buck-boost topology than in the buck topology. 图 3 (a) shows that the output voltage terminals are reversed, though the components are wired the same as a buck converter. As 图 3 (b) shows, during the ON-time of the control MOSFET, the inductor is charged with current while the output capacitor supplies the load current. The inductor does not provide current to the load during this time. During the OFF-time of the control MOSFET and the ON-time of the synchronous MOSFET shown in 图 3 (c), the inductor provides current to the load and the output capacitor. These changes affect many parameters, which the following subsections describe in further detail.

 


图 3. Inverting Buck-Boost Configuration

The average inductor current is affected in this topology. In the buck configuration, the average inductor current is equal to the average output current because the inductor always supplies current to the load during both the ON- and OFF-times of the control MOSFET. However, in the inverting buck-boost configuration, only the output capacitor supplies the load with current, while the load is completely disconnected from the inductor during the ON-time of the control MOSFET. During the OFF-time, the inductor connects to both the output capacitor and the load (see 图 3). Because the OFF-time is $1 - D$ of the switching period, the average inductor current in 公式 1 is calculated as:

$$I_{L(Avg)} = \left| \frac{I_{OUT}}{(1-D)} \right| \quad (1)$$

The duty cycle for the typical buck converter is simply V_{OUT} / V_{IN} , but the calculation of the ideal duty cycle in 公式 2 for an inverting buck-boost converter becomes:

$$D = \frac{V_{OUT}}{(V_{OUT} - V_{IN})} \quad (2)$$

公式 3 provides the peak-to-peak inductor ripple current:

$$\Delta I_L = \frac{V_{IN} D}{f_s L} \quad (3)$$

where,

- ΔI_L (A): Peak-to-peak inductor ripple current
- D: Duty cycle
- f_s (MHz): Switching frequency
- L (μ H): Inductor value
- V_{IN} (V): Input voltage with respect to ground, not with respect to the device ground or V_{OUT} .

公式 4 calculates the maximum inductor current:

$$I_L = I_{L(avg)} + \frac{\Delta I_L}{2} \quad (4)$$

2.2.2 V_{IN} and V_{OUT} Range

The input voltage that can be applied to an integrated circuit (IC) operating in the inverting buck-boost topology is less than the input voltage for the same IC operating in the buck topology. The reason for this difference is because the ground pin of the IC is connected to the (negative) output voltage. Therefore, the input voltage across the device is V_{IN} to V_{OUT} , not V_{IN} to ground. Thus, the input voltage range of the TPS62136 is 3 V to 17 V + V_{OUT} , where V_{OUT} is a negative value.

The output voltage range is the same as when configured as a buck converter, but negative. The output voltage for the inverting buck-boost topology must be set between -0.8 V and -12 V . The output voltage is set in the same way as the buck configuration, with two resistors connected to the FB pin. The TIDA-01423 design sets the output voltage at -12 V , which gives an input voltage range of 3 V to 5 V . However, TI does not recommend to use a 5-V input voltage because voltage tolerances on the input supply can violate the recommended operating range of TPS62136.

2.2.3 Capacitor Selection

An input capacitor, C_{IN} , is required to provide a low-impedance input voltage source to the inverter. A low equivalent series resistance (ESR) X5R or X7R ceramic capacitor is best for input voltage filtering and minimizing interference with other circuits. For most applications, a $10\text{-}\mu\text{F}$ ceramic capacitor is recommended from V_{IN} to ground (system ground, not $-V_{OUT}$). The C_{IN} capacitor value can be increased without any limit for better input voltage filtering.

On the output, the TIDA-01423 design uses a $22\text{-}\mu\text{F}$ output capacitor, which has an effective capacitance of about $10\text{ }\mu\text{F}$ at the -12-V output voltage. For maximum output current, a second output capacitor can help to increase the phase margin.

For the inverting buck-boost configuration of the TPS62136, installing a bypass capacitor, CBYP, to provide a low impedance source for the internal gate drivers is important. This capacitor is connected from V_{IN} to $-V_{OUT}$; therefore, it requires the highest voltage rating. For most applications, a $22\text{-}\mu\text{F}$ ceramic capacitor is recommended. The bypass capacitor provides an AC path from V_{IN} to $-V_{OUT}$. When V_{IN} is applied to the circuit, this dV/dt across a capacitor from V_{IN} to $-V_{OUT}$ creates a current that must return to ground (the return of the input supply) to complete its loop. This current may flow through the body diode of the internal low-side MOSFET and the inductor to return to ground. Flowing through the body diode pulls the VOUT pin below IC ground, which violates its absolute maximum rating. Such a condition may damage the TPS62136 device and is not recommended. For protective measure, a Schottky diode must be installed on the output, as the schematic in [图 2](#) shows.

To avoid excessive inrush current, a soft-start capacitor is installed on the SS/TR pin.

2.2.4 Maximum Output Current

In the inverting buck-boost topology, the maximum output current is reduced as compared to the buck topology. This reduction is a result of the peak inductor current being higher, as calculated in [公式 4](#).

For example, for an output voltage of -12 V , $1.5\text{-}\mu\text{H}$ inductor, and input voltage of 3.3 V , the following calculations produce the maximum allowable output current that can be ensured based on the TPS62136 minimum current limit value of 4.8 A . Due to increased duty cycles when operating at high load current, the duty cycle used for the following maximum output current calculation in [公式 5](#) must be increased by 5% for these conditions, which provides a more accurate maximum output current calculation.

$$D = \frac{V_{OUT}}{V_{OUT} - V_{IN}} \times 1.05 = \frac{-12}{-12 - 1.33} \times 1.05 = 0.82 \quad (5)$$

The switching frequency at maximum load is based on [图 9](#). Based on the inductor data sheet, the effective inductance value is approximately $1.1\text{ }\mu\text{H}$ at 3-A current (see [公式 6](#)).

$$\Delta I_L = \frac{V_{IN} \times D}{f_S \times L} = \frac{3.3 \times 0.82}{0.55\text{ MHz} \times 1.1\text{ }\mu\text{H}} = 4.5\text{ A} \quad (6)$$

Rearranging [公式 4](#) and setting $I_{L(max)}$ equal to the minimum value of I_{LIMF} , as specified in the data sheet, results in [公式 7](#):

$$I_{L(\text{avg})} = I_{L(\text{max})} - \frac{\Delta I_L}{2} = 4.8 - \frac{4.5}{2} = 2.5 \text{ A} \quad (7)$$

This result is then used in 公式 1 to calculate the maximum achievable output current in 公式 8:

$$I_{\text{OUT}} = I_{L(\text{avg})} \times (1 - D) = 2.5 \text{ A} \times (1 - 0.82) = 450 \text{ mA} \quad (8)$$

图 4 shows the maximum output current for the TIDA-01423 design.

 


图 4. Maximum Output Current ($V_{\text{OUT}} = -12 \text{ V}$)

2.2.5 Thermal Limits

With different conditions, thermal limits may become an issue as a result of the small size of the converter itself. As the output current increases, the absolute power loss (in mW) in the TPS62136 device also increases, which causes a higher temperature rise across the thermal impedance of the TPS62136 device.

The maximum allowed IC junction temperature is 125°C as stated in the TPS62136 data sheet. To calculate the IC temperature for different conditions, multiply the power loss of the TPS62136 device by the θ_{JA} , which is approximately 40°C/W for the TIDA-01423 printed-circuit board (PCB), and add this value to the ambient temperature.

To calculate the maximum output current at any ambient temperature, simply subtract the maximum ambient temperature from 125°C to obtain the allowable temperature rise. Divide the θ_{JA} of the PCB by this temperature rise to obtain the allowable IC power loss. Find this IC power loss for an input voltage of 3.3 V in 图 8 to determine the maximum output current under specific conditions. See 公式 9 for the calculation.


$$I_{\text{C}_{\text{Loss}}} \leq \frac{125 - T_{\text{A_MAX}}}{\theta_{\text{JA}}} \quad (9)$$

2.2.6 Enable Pin Configuration

The device is enabled when the voltage at the EN pin trips its threshold and the input voltage is above the undervoltage lockout (UVLO) threshold. The TPS62136 device stops operation when the voltage on the EN pin falls below its threshold or the input voltage falls below the UVLO threshold.

Because V_{OUT} is the IC ground in this configuration, the EN pin must be referenced to V_{OUT} instead of ground. In the buck configuration, 0.83 V is considered as high and less than 0.67 V is considered as low. However, in the inverting buck-boost configuration, the V_{OUT} voltage is the reference; therefore, the high threshold is $0.83\text{ V} + V_{OUT}$ and the low threshold is $0.67\text{ V} + V_{OUT}$. For example, if $V_{OUT} = -12\text{ V}$, then V_{EN} is considered at a high level for voltages above -11.17 V and a low level for voltages below -11.24 V .

This behavior can cause difficulties when enabling or disabling the part because, in some applications, the IC that provides the EN signal may not be able to produce negative voltages. The level-shifter circuit that 图 5 shows alleviates any difficulties associated with the offset EN threshold voltages by eliminating the requirement for negative EN signals. If disabling the TPS62136 is not desired, the EN pin may be directly connected to V_{IN} without this circuit.

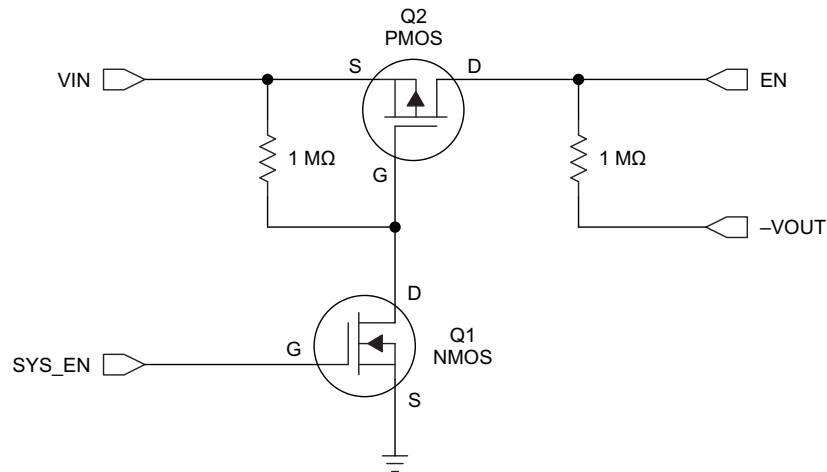

NOTE: V_{OUT} is the negative output voltage of the inverting buck-boost converter.

图 5. EN Pin Level Shifter

The positive signal that originally drives EN is instead tied to the gate of Q1 (SYS_EN). When Q1 is OFF (SYS_EN grounded), Q2 has 0 V across its V_{GS} and also remains OFF. In this state, the EN pin is at -12 V , which is below the low-level threshold, and disables the device.

When SYS_EN provides enough positive voltage to turn Q1 ON (V_{GS} threshold as specified in the MOSFET data sheet), the gate of Q2 is at ground potential through Q1. This action drives the V_{GS} of Q2 negative and turns Q2 ON. Then V_{IN} ties to EN through Q2 and the pin is above the high-level threshold, which turns the device ON. Be careful to ensure that the V_{GD} and V_{GS} of Q2 remain within the MOSFET ratings during both the enabled and disabled states. Failing to adhere to this constraint can result in damaged MOSFETs.

图 16 shows the enable sequence where the SYS_EN signal activates the enable circuit. This circuit has been tested with a 3.3-V SYS_EN signal and dual N/PFET Si1029X. The EN signal is the output of the circuit and goes from V_{IN} to V_{OUT} to properly enable and disable the device.


2.2.7 Mode Pin Configuration

The operation mode can be selected with the mode pin of the TPS62136. The device runs in automatic PFM or PWM mode when this pin is pulled low (IC ground which is $-V_{OUT}$), which results in a higher efficiency at a light load. When the pin is pulled high (V_{IN}), the device runs in forced PWM mode (for a constant frequency at a light load).

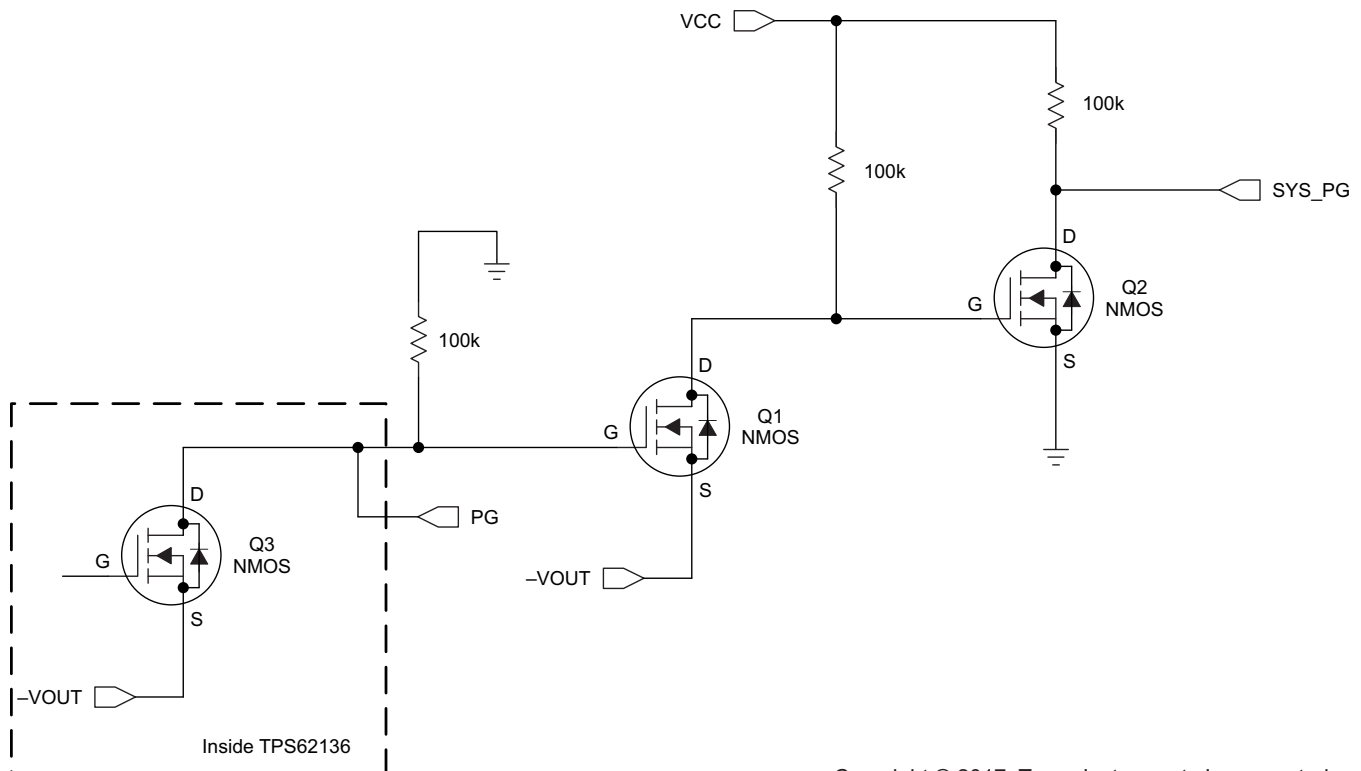2.2.8 Power Good Pin Configuration

The TPS62136 has a built-in power good (PG) function to indicate whether the output voltage has reached its appropriate level or not. The PG pin is an open-drain output that requires a pullup resistor. Because V_{OUT} is the IC ground in this configuration, the PG pin is referenced to V_{OUT} instead of ground, which means that the TPS62136 device pulls PG to V_{OUT} when it is low.

This behavior can cause difficulties in reading the state of the PG pin because, in some applications, the IC that detects the voltage level of the PG pin may not be able to withstand negative voltages. The level-shifter circuit shown in 图 6 alleviates any difficulties associated with the offset PG pin voltages by eliminating the negative output signals of the PG pin. If the PG pin functionality is not required, it may be left floating or connected to V_{OUT} without this circuit.



Copyright © 2017, Texas Instruments Incorporated

图 6. PG Pin Level Shifter

Inside the TPS62136, the PG pin is connected to an N-channel MOSFET (Q3). By tying the PG pin to the gate of Q1, when the PG pin is pulled low, Q1 is OFF and Q2 is ON because the V_{GS} of Q2 is at V_{CC} . SYS_PG is then pulled to ground.

When Q3 turns OFF, the gate of Q1 is pulled to ground potential, which turns Q1 ON. This sequence of events pulls the gate of Q2 below ground, which turns it OFF. SYS_PG is then pulled up to the V_{CC} voltage. Note that the V_{CC} voltage must be at an appropriate logic level for the circuitry connected to the SYS_PG net.

3 Getting Started Hardware

To test this TI Design, simply apply an input voltage on the J1 connector and the load to J2 connector. Then, connect a jumper between ON and EN on JP1. Set JP2 to the desired operating mode, PFM (for higher efficiency at light load) or PWM (for constant frequency at light load).

4 Testing and Results

All data in this section has been recorded using a 3.3-V V_{IN} , -12-V V_{OUT} unless otherwise noted.

4.1 Test Results

 


图 7. Thermal Performance (250-mA Load)

 


图 8. Efficiency Over Load (Mode = PFM)

 


图 9. Switching Frequency Over Load

 


图 10. Load Regulation (Mode = PFM)

 


图 11. Loop Gain (300 mA)

 


图 12. Transient Response (0-A to 250-mA Load Step, Mode = PWM)

 


图 13. Output Voltage Ripple (1-mA Load, Mode = PFM)

 


图 14. Output Voltage Ripple (1-mA Load, Mode = PWM)

 


图 15. Output Voltage Ripple (250-mA Load)

 


图 16. Start-Up on EN (No Load)

5 Design Files

5.1 Schematics

To download the schematics, see the design files at [TIDA-01423](#).

5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01423](#).

5.3 PCB Layout Recommendations

5.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01423](#).

5.4 Gerber Files

To download the Gerber files, see the design files at [TIDA-01423](#).

5.5 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01423](#).

6 Related Documentation

1. Texas Instruments, [Simplifying Stability Checks](#), Application Report (SLVA381)
2. Texas Instruments, [Using the TPS62125 in an Inverting Buck-Boost Topology](#), TPS62125 Application Report (SLVA514)
3. Texas Instruments, [TPS62136 1-MHz High Accuracy 3-V to 17-V 4-A Step-Down Converter](#), TPS62136 Data Sheet (SLVSDV2)

6.1 商标

All trademarks are the property of their respective owners.

有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。您就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等产权包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默示的保证或陈述，包括但不限于对准确性或完整性、产权保证、无复发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、[评估模块](http://www.ti.com/sc/docs/sampters.htm)和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122
Copyright © 2017 德州仪器半导体技术（上海）有限公司