

## TI Designs: TIDA-01464

# 具有可调输出电压且效率为 92% 的 200W、低 THD、10% 可调光交流/直流 LED 驱动器参考设计



### 说明

该参考设计是 200W、可调光、低 THD 交流/直流 LED 电源，具有 100V 至 200V 的可调输出电压，专为在街道照明、公路照明等户外照明应用而设计。该设计具有使用 UCC28180 CCM PFC 控制器设计的前端功率因数校正 (PFC) 电路，后跟使用 UCC28740 CC-CV 反激式控制器实现的准谐振 (QR) 反激式转换器，具有针对输出 LED 电流和电压的次级侧调节 (SSR) 的光耦合反馈。

该设计支持在 0 至 10V 模拟电压范围内进行调光，还通过了 IEC 61000-3-2 C 类照明设备电流 THD 调节测试。

### 资源

<a href="#">TIDA-01464</a>	设计文件夹
<a href="#">UCC28180</a>	产品文件夹
<a href="#">UCC28740</a>	产品文件夹
<a href="#">INA180</a>	产品文件夹
<a href="#">UCC28910</a>	产品文件夹
<a href="#">LM358M</a>	产品文件夹
<a href="#">LM4040</a>	产品文件夹

### 特性



- 支持 85 V 至 305V 的通用输入交流电压范围以及小于 350mW (230V) 的极低待机功率
- 对于不要求外部冷却的 196W 负载，具有很高的效率（在 120V 交流下接近 90%，在 230V、265V 交流下接近 92%）
- 对于 196W 负载，在 120V、230V 和 265V 交流下具有大于 0.98 的功率因数和小于 5% 的 THD
- 在 0 至 10V 模拟调光范围内具有小于 10% 的调光功能
- 在 100 至 200V 范围内进行可调直流输出运行，从而可以在不对性能造成很大影响的情况下支持不同的 LED 负载
- 对于不小于 196V 的 22% 和不小于 102V 的 36% 的 LED 负载，符合 IEC 61000-3-2 C 类电流 THD 调节标准

### 应用

- 街道照明
- 道路照明
- 室外照明



咨询我们的 E2E™ 专家

 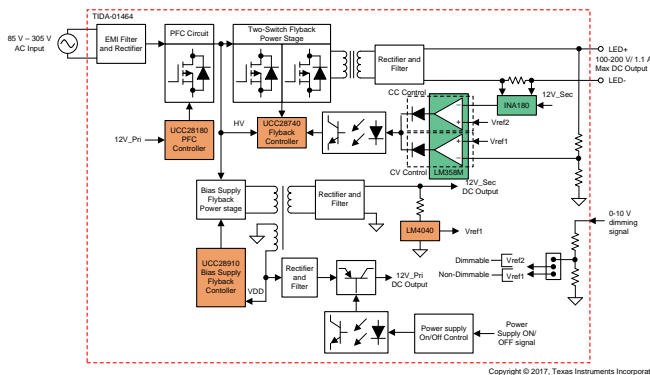

该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

## 1 System Description

High-power LED lighting applications such as road lighting, street lighting, and Flood lighting may need power levels above 75 W to 200 W. For such requirements, generally two stage power supplies are used to get higher efficiency, lower mains ripple at the output, higher power factor, and low total harmonic distortion (THD). Two-stage architectures have a PFC stage as a front end, and power architecture like flyback or resonant converters like LLC or LCC are used. While resonant converters can help achieving higher efficiency, generally they are tuned for specific load conditions. However, the LED power supplies that are sold as a separate unit needs to cater to different voltages of LED strings as the end user might use different numbers of LEDs or LED COBs in series. In such cases where the output voltage setting can change widely, the resonant converters efficiency are sacrificed. One of the architectures that can help to meet the cost, efficiency and design simplicity aspects of LED power supply with adjustable output voltage is the two switch flyback architecture. This 200-W LED power supply reference design has an output voltage that is adjustable from 100 V to 200 V. This design uses a CCM PFC front end to achieve low THD and high power factor. Following the PFC stage is a two-switch flyback architecture that converts DC/DC with isolation.

Due to its simplicity and low part count, flyback topology is often used in isolated switched-mode power supplies with an output power of 100 W or less. General operation principles of the flyback converter are used by power supply engineers for fast creation of new designs. Because of a low part count, designs can be made with low cost. Due to its versatility and simplicity, flyback topology can be called the 'work horse' of isolated topologies. Even though Flyback-topology is easily used with different applications, there are some drawbacks. The voltage stress of the primary-side transistor is high even in an ideal case, where the leakage effects of the transformer are not considered. When current flows on the secondary side, the drain voltage of the primary-side transistor rises to the sum of the input voltage and the reflected voltage.

When considering the parasitic ringing caused by transistor capacitances and the leakage inductance of the transformer, the voltage stress is even higher. Because the amplitude of the parasitic ringing is hard to predict, the designer must choose a transistor with a high voltage rating. High-voltage MOSFETs comes with higher on-state resistance compared to lower voltage MOSFETs. High on-state resistance increases conduction losses and leads to a reduction of efficiency. Different kinds of snubbers and clamping-circuits can reduce the transistor voltage stress. For voltage stress, snubbers and clamping-circuits are reasonable solutions, but the energy stored in the leakage inductance is dissipated in snubber and thus reducing efficiency.

The typical problems of flyback topology are overcome by using a two-switch flyback topology. When a second transistor is added between the input voltage and the transformer, the overall voltage stress is divided equally over both transistors. Instead of turning leakage energy into losses, it is now returned to the input supply through two diodes. Diodes also clamp drain-source voltages of both transistors to the input voltage, so the voltage rating of the transistors can be selected according to input voltage without a bigger margin. Due to these improvements, the two-switch flyback topology is an option over traditional flyback topology.

图 1 和 图 2 显示高功率 AC/DC LED 电源在户外照明应用中的示例。



图 1. Street Lighting



图 2. Flood Lighting


## 1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	TEST CONDITIONS	MIN	NOM	MAX	UNIT
<b>INPUT CONDITIONS</b>					
Input voltage ( $V_{INAC}$ )		85	120/230/265	305	VAC
Frequency ( $f_{LINE}$ )		47	50	60	Hz
Standby power				0.35	W
No load power (PNL)	$V_{INAC} = 230\text{ V}$ , $I_{OUT} = 0\text{ A}$			1.3	W
<b>OUTPUT CONDITIONS</b>					
Output voltage			198		V
Output current				1.1	A
Line regulation				0.5	%
Load regulation				0.5	%
Output voltage ripple			20	50	mV
Output power				200	W
THD	$V_{INAC} = 85 - 305\text{ V}$ , $P_{OUT} > 25\%$ of full load		< 20		%
Hold-up time ( $t_{HOLD}$ )	$V_{INAC} = 120\text{ V}$		> 30		ms
	$V_{INAC} = 230\text{ V}$		> 50		ms
Primary-to-secondary insulation				4	kV
<b>SYSTEM CHARACTERISTICS</b>					
Efficiency ( $\eta$ )	$V_{IN} = 265\text{-V AC}$ , $I_{OUT} = 1\text{ A}$			> 92	%
Protections	Output overvoltage (settable)				
	Output overcurrent				
	Thermal shutdown (temperature at the sense point)				
	Output open loop protection				
Operating ambient	Open frame	-40	25	60	°C
Power line harmonics	As per IEC 61000-3-2 Class-C Lighting Equipment				
Dimensions	Length x Breadth x Height	120 x 82 x 35			mm

## 2 System Overview

### 2.1 Block Diagram

 

Copyright © 2017, Texas Instruments Incorporated

图 3. TIDA-01464 Block Diagram

## 2.2 Highlighted Products

This reference design uses the following highlighted products. Key features for selecting the devices for this reference design are given in the following sections. Find complete details of the highlighted devices in their respective product data sheets.

### 2.2.1 UCC28180


To implement the low-cost, small form factor, PFC design to meet THD requirements at 200-W power, the UCC28180 is the preferred controller because it offers series of benefits to meet IEC 61000-3-2 Class C THD norms and achieve high power factor for wide input voltage range of operation.

The UCC28180 is a flexible and easy-to-use, 8-pin, active PFC controller that operates under Continuous Conduction Mode (CCM) to achieve a high PF, low current distortion, and excellent voltage regulation of boost pre-regulators in AC/DC front ends. The controller is suitable for universal AC input systems operating in 100-W to few-kW range with the switching frequency programmable between 18 to 250 kHz. This switching frequency allows the device to support both power MOSFET and IGBT switches. An integrated 1.5-A and 2-A (SRC-SNK) peak gate drive output, clamped internally at 15.2 V (typical), enables fast turnon, turnoff, and easy management of the external power switch without the need for buffer circuits.

Low-distortion wave shaping of the input current using average current mode control is achieved without input line sensing, reducing the external component count. In addition, the controller features reduced current sense thresholds to facilitate the use of small-value shunt resistors for reduced power dissipation. This reduced dissipation is especially important in high-power systems. To enable low current distortion, the controller also features trimmed internal current loop regulation circuits for eliminating associated inaccuracies.

Key features that make this device unique are:

- 8-pin solution (no AC line sensing needed)
- Wide range programmable switching frequency (18 to 250 kHz for MOSFET and IGBT-based PFC converters)
- Trimmed current loop circuits for low iTHD
- Reduced current sense threshold (minimizes power dissipation in shunt)
- Average current-mode control
- Soft overcurrent and cycle-by-cycle peak current limit protection
- Output overvoltage protection with hysteresis recovery
- Audible noise minimization circuitry
- Open loop detection
- Enhance dynamic response during output overvoltage and undervoltage conditions
- Maximum duty cycle of 96% (typ)
- Burst mode for no load regulation
- VCC UVLO, low ICC start-up (< 75  $\mu$ A)

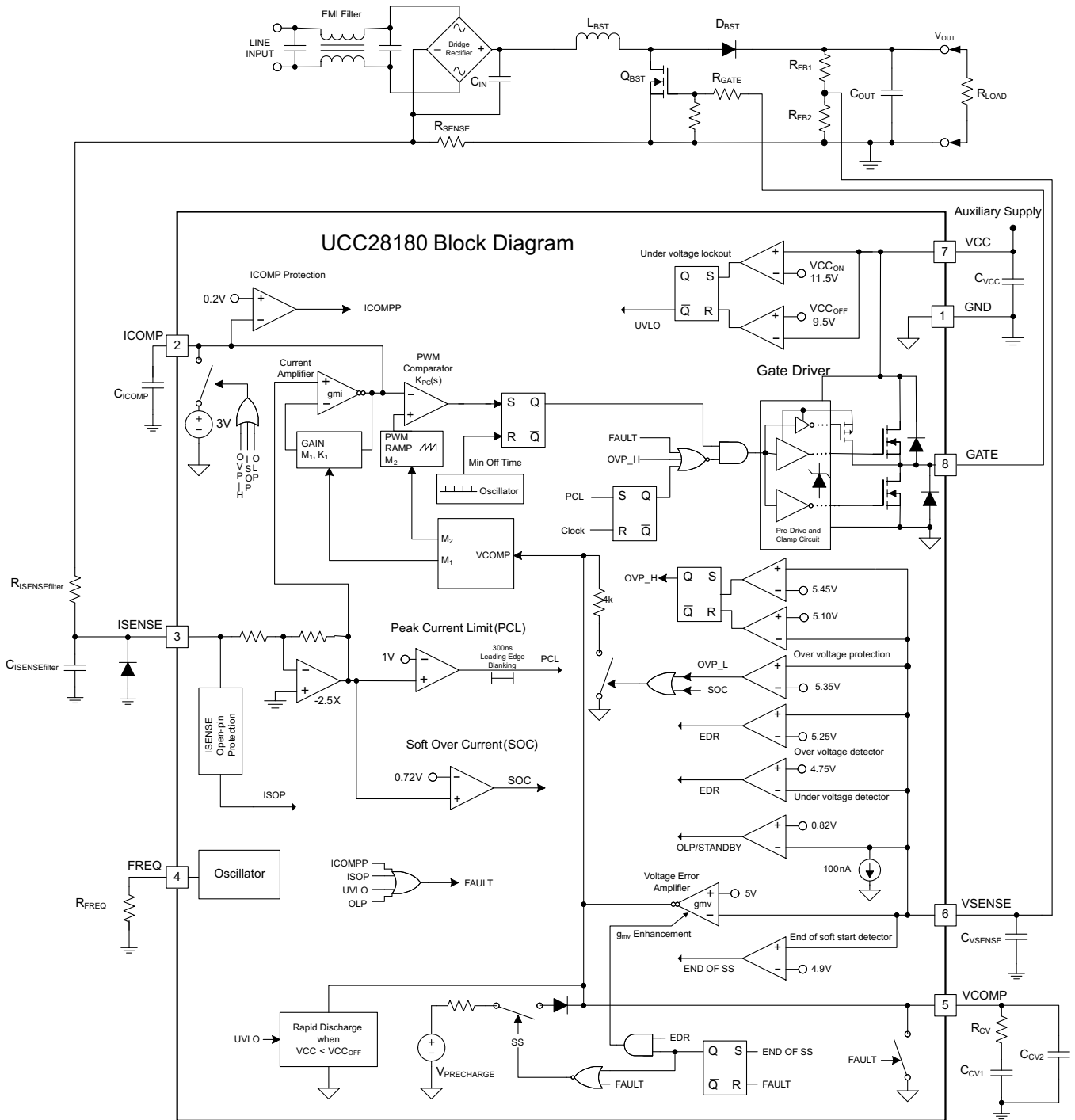

Copyright © 2016, Texas Instruments Incorporated

图 4. UCC28180 Functional Block Diagram



### 2.2.2 UCC28740


To implement the high-performance, small form factor, flyback design at 200-W power, the UCC28740 is preferred because it offers a series of benefits to address the needs of the next generation DIN rail power supply of low reduced feedback loops for precision current limit and power limit. This eliminates the need of external current sensing on the secondary side and multiple optocoupler feedback loops for open loop detection and power limiting.

The UCC28740 isolated-flyback power supply controller provides CV output regulation using an optical coupler to improve transient response to large load steps. CC regulation is accomplished through PSR techniques. This device processes information from optocoupled feedback and from an auxiliary flyback winding for precise high-performance control of output voltage and current. An internal 700-V startup switch, dynamically-controlled operating states, and a tailored modulation profile support ultra-low standby power without sacrificing startup time or output transient response. The drive output interfaces to a MOSFET power switch. Discontinuous conduction mode (DCM) with valley switching reduces switching losses. Modulating the switching frequency and primary current peak amplitude (FM and AM) keeps the conversion efficiency high across the entire load and line ranges.

Key features that make this device unique are:

- Optocoupled feedback regulation for CV and PSR for CC
- Enables  $\pm 1\%$  voltage regulation and  $\pm 5\%$  current regulation across line and load
- 100-kHz max switching frequency enables high power density charger designs
- QR valley switching operation for highest overall efficiency
- Frequency jitter scheme to ease EMI compliance
- Wide VDD range (35 V) allows small bias capacitor
- Drive output for MOSFET
- Enables  $<10$ -mW system standby and no load power
- Protection functions: Overvoltage, low line, and overcurrent
- SOIC-7 package



 

Copyright © 2017, Texas Instruments Incorporated

图 5. UCC28740 Functional Block Diagram

### 2.2.3 UCC28910

The UCC28910 is a high-voltage flyback switcher that provides output voltage and current regulation without the use of an optical coupler. This device incorporates a 700-V power FET and a controller that process operating information from the flyback auxiliary winding and power FET to provide a precise output voltage and current control. The integrated high-voltage current source for startup that is switched off during device operation, and the controller current consumption is dynamically adjusted with load. Both enable the very low standby power consumption.

Control algorithms in the UCC28910 that combining switching frequency and peak primary current modulation allow operating efficiencies to meet or exceed applicable standards. DCM with valley switching is used to reduce switching losses. Built-in protection features help to keep secondary and primary component stress levels in check across the operating range. The frequency jitter helps to reduce EMI filter cost.

Key features that make this device unique are:

- CV and CC output regulation without an optic coupler
- ±5% output voltage regulation accuracy
- ±5% output current regulation with AC line and primary inductance tolerance compensation
- 700-V start-up and smart power management enables <30-mW standby power

- 115-kHz maximum switching frequency design for high-power density
- Valley switching and frequency dithering to ease EMI compliance
- Thermal shutdown
- Low line and output overvoltage protection

 


图 6. UCC28910 Functional Block Diagram


## 2.2.4 INA180

The INA180 is a family of cost-optimized current sense amplifiers (also called current-shunt monitors) that sense voltage drops across current-sense resistors at common-mode voltages from  $-0.2$  to  $26$  V, independent of the supply voltage. The INA180 integrates a matched resistor gain network in four, fixed-gain device options:  $20$  V/V,  $50$  V/V,  $100$  V/V, or  $200$  V/V. This matched gain resistor network minimizes gain error and reduces the temperature drift.

The INA180 operates from a single  $2.7$ - to  $5.5$ -V power supply, drawing a maximum of  $260$   $\mu$ A of supply current. All device options are specified over the extended operating temperature range of  $-40^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  and are available in a 5-pin, SOT-23 package with two different pin configurations.

Key features that make this device unique are:

- Common-mode range ( $V_{\text{CM}}$ ):  $-0.2$  to  $26$  V
- High bandwidth:  $350$  kHz
- Offset voltage:
  - $\pm 150$   $\mu$ V (max) at  $V_{\text{CM}} = 0$  V
  - $\pm 500$   $\mu$ V (max) at  $V_{\text{CM}} = 12$  V
- Output slew rate:  $2$  V/ $\mu$ s
- Accuracy:
  - $\pm 1\%$  gain error (max)
  - $1$ - $\mu$ V/ $^{\circ}\text{C}$  offset drift (max)
- Gain options:
  - $20$  V/V (A1 devices)
  - $50$  V/V (A2 devices)
  - $100$  V/V (A3 devices)
  - $200$  V/V (A4 devices)
- Quiescent current:  $260$   $\mu$ A (max)

 

Copyright © 2017, Texas Instruments Incorporated

图 7. INA180 Functional Block Diagram

### 2.2.5 LM358

The LM358 device consist of two independent, high-gain, frequency-compensated operational amplifiers designed to operate from a single supply over a wide range of voltages. Operation from split supplies also is possible if the difference between the two supplies is 3 to 32 V (3 to 26 V for the LM2904 device), and VCC is at least 1.5 V more positive than the input common-mode voltage. The low supply-current drain is independent of the magnitude of the supply voltage.

Key features that make this device unique are:

- Wide supply ranges:
  - Single supply: 3 to 32 V
  - Dual supplies:  $\pm 1.5$  to  $\pm 16$  V
- Low supply-current drain, independent of supply voltage: 0.7 mA (typ)
- Wide unity gain bandwidth: 0.7 MHz
- Common-mode input voltage range includes ground, allowing direct sensing near ground
- Low input bias and offset parameters:
  - Input offset voltage: 3 mV (typ)  
A versions: 2 mV (typ)
  - Input offset current: 2 nA (typ)
  - Input bias current: 20 nA (typ)  
A versions: 15 nA (typ)
- Differential input voltage range equal to maximum-rated supply voltage: 32 V
- Open-loop differential voltage gain: 100 dB (typ)
- Internal frequency compensation
- On products compliant to MIL-PRF-38535, all parameters are tested unless otherwise noted. On all other products, production processing does not necessarily include testing of all parameters.

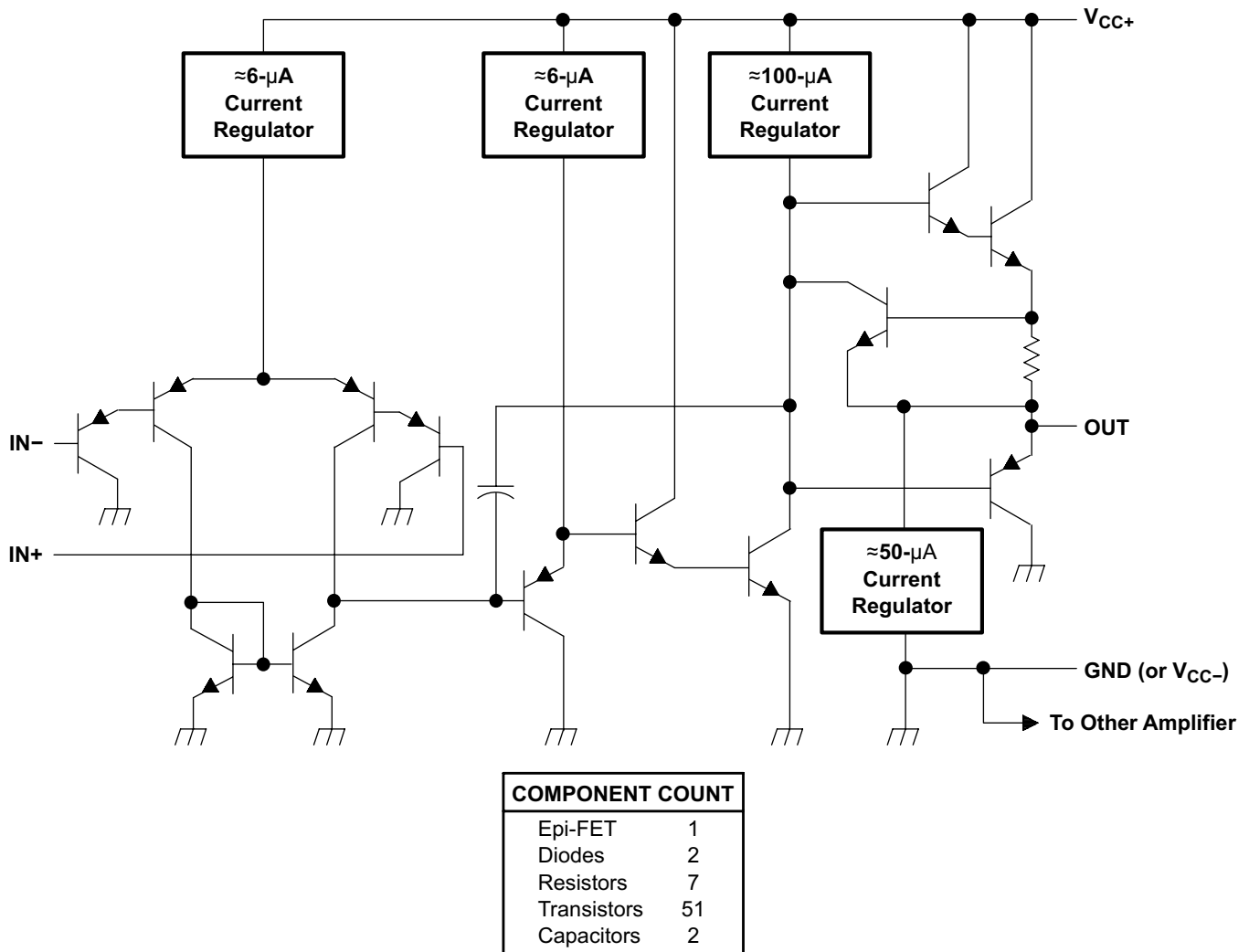


图 8. LM358 Functional Block Diagram

### 2.2.6 LM4040

The LM4040-N is a precision micropower, curvature-corrected, band-gap shunt voltage reference. For space critical applications, the LM4040-N is available in the sub-miniature SOT-23 and SC70 surface-mount package. The LM4040-N is designed for stable operation without the need of an external capacitor connected between the + pin and the - pin. If, however, a bypass capacitor is used, the LM4040-N remains stable. Reducing design effort is the availability of several fixed reverse breakdown voltages: 2.048 V, 2.5 V, 3 V, 4.096 V, 5 V, 8.192 V, and 10 V. The minimum operating current increases from 60  $\mu$ A for the LM4040-N-2.048 and LM4040-N-2.5 to 100  $\mu$ A for the 10-V LM4040-N. All versions have a maximum operating current of 15 mA.

Key features that make this device unique are:

- Fixed reverse breakdown voltages of 2.048 V, 2.5 V, 3 V, 4.096 V, 5 V, 8.192 V, and 10 V
- Wide operating current range: 45  $\mu$ A (typ) to 15 mA
- Stable with all capacitive loads; no output capacitor required
- Available in extended temperature range:  $-40^{\circ}\text{C}$  packages to  $+125^{\circ}\text{C}$

- Low output noise:  $35 \mu V_{RMS}$  (typ)
- Small packages: SOT-23, TO-92, and SC70

 


图 9. LM4040 Functional Block Diagram

## 2.3 System Design Theory

This reference design provides 200 W of continuous power over a wide AC input range from 85- to 305-V AC with power factor correction. The UCC28180 controls a PFC boost front-end power stage to generate DC output voltage, while the UCC28740 QR flyback controller converts the PFC output to isolated 198 V and 1.1 A. The total system efficiency is over 92% with a 265-V AC input and over 90% with a 120-V AC input under full load conditions. The design has a precise current limit and limits the power to less than 200 W under all fault conditions. In addition, several protections are embedded into this reference design, which includes output over-voltage and output over-current protection. High efficiency, high PF, low THD, and low standby power are the main focuses of this reference design.

### 2.3.1 PFC Circuit Component Design

表 2. Design Goal Parameters for PFC

PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
<b>INPUT CHARACTERISTICS</b>						
$V_{IN}$	Input voltage		85		305	VAC
$f_{LINE}$	Input frequency		47		63	Hz
$I_{IN(peak)}$	Peak input current	$V_{IN} = V_{IN(min)}$ , $I_{OUT} = I_{OUT(max)}$			3.8	A
<b>OUTPUT CHARACTERISTICS</b>						
$V_{OUT}$	Output voltage	$I_{OUT} \leq I_{OUT(max)}$ , $f_{LINE(min)} \leq f_{LINE} \leq f_{LINE(max)}$ , $V_{IN(min)} \leq V_{IN} \leq V_{IN(max)}$	431	434	444	VDC
	Line regulation	$I_{OUT} = I_{OUT(max)}$ , $V_{IN(min)} \leq V_{IN} \leq V_{IN(max)}$			5	
	Load regulation	$V_{IN} = 85\text{-V AC}$ , $f_{LINE} = 60\text{ Hz}$ , $I_{OUT(min)} \leq I_{OUT} \leq I_{OUT(max)}$			5	%
		$V_{IN} = 230\text{-V AC}$ , $f_{LINE} = 60\text{ Hz}$ , $I_{OUT(min)} \leq I_{OUT} \leq I_{OUT(max)}$			5	%
$I_{OUT}$	Output load current	$V_{IN(min)} \leq V_{IN} \leq V_{IN(max)}$ , $f_{LINE(min)} \leq f_{LINE} \leq f_{LINE(max)}$	0		0.507	A
$P_{OUT}$	Output power	$V_{IN(min)} \leq V_{IN} \leq V_{IN(max)}$ , $f_{LINE(min)} \leq f_{LINE} \leq f_{LINE(max)}$	0		220	W
$V_{OUT(OVP)}$	Output overvoltage protection	$V_{IN} = 85\text{-V AC}$		477		VDC
$V_{OUT(UVP)}$	Output undervoltage protection			416		VDC
THD	$V_{INAC} = 85\text{ to }305\text{ V}$ , $P_{OUT} > 25\%$ of full load			< 20		%
<b>CONTROL LOOP CHARACTERISTICS</b>						
$f_{SW}$	Switching frequency	$T_J = 25^\circ\text{C}$		130		kHz
$f_{CO}$	Voltage loop bandwidth	$V_{IN} = 162\text{-V DC}$ , $I_{OUT} = 0.466\text{ A}$		8		Hz
	Voltage loop phase margin	$V_{IN} = 162\text{-V DC}$ , $I_{OUT} = 0.466\text{ A}$		68		°
PF	Power factor	$V_{IN} = 115\text{-V AC}$ , $I_{OUT} = I_{OUT(max)}$		0.994		
$\eta$	Full load efficiency	$V_{IN} = 85\text{-V AC}$ , $f_{LINE} = 60\text{ Hz}$ , $I_{OUT} = I_{OUT(max)}$		90		%
	Ambient temperature			25		°C



### 2.3.1.1 Current Calculations

The input fuse, bridge rectifier, and input capacitor are selected based upon the input current calculations. First, determine the maximum average output current,  $I_{OUT(max)}$ :

$$I_{OUT(max)} = \frac{P_{OUT(max)}}{V_{OUT}} \quad (1)$$

$$I_{OUT(max)} = \frac{220 \text{ W}}{434 \text{ V}} = 0.507 \text{ A}$$

The maximum input RMS line current,  $I_{IN\_RMS(max)}$ , is calculated using the parameters from 表 2 such as the initial assumptions of efficiency and PF:

$$I_{IN\_RMS(max)} = \frac{P_{OUT(max)}}{\eta \times V_{IN(min)} \times PF} \quad (2)$$

$$I_{IN\_RMS(max)} = \frac{220}{0.9 \times 85 \times 0.994} = 2.893 \text{ A}$$

Based upon the calculated RMS value and assuming the waveform is sinusoidal, the maximum input current,  $I_{IN(max)}$ , and the maximum average input current,  $I_{IN\_AVG(max)}$  can be determined.

$$I_{IN(max)} = \sqrt{2} \times I_{IN\_RMS(max)}$$

$$I_{IN(max)} = \sqrt{2} \times 2.893 = 4.09 \text{ A}$$

$$I_{IN\_AVG(max)} = \frac{2 \times I_{IN(max)}}{\pi} \quad (3)$$

$$I_{IN\_AVG(max)} = \frac{2 \times 4.09 \text{ A}}{3.14} = 2.60 \text{ A}$$

In this reference design, a fuse and bridge rectifier with a 4-A rating is used at the input.

### 2.3.1.2 Switching Frequency

The UCC28180 switching frequency is user programmable with a single resistor on the FREQ pin (4<sup>th</sup> pin) to ground. For this reference design, the switching frequency,  $f_{SW}$ , is chosen to be 130 kHz. 图 10 can be used to select the suitable resistor to program the switching frequency, or the value can be calculated using constant scaling values of  $f_{TYP}$  and  $R_{TYP}$ . In all cases,  $f_{TYP}$  is a constant that is equal to 65 kHz,  $R_{INT}$  is a constant that is equal to 1 M $\Omega$ , and  $R_{TYP}$  is a constant that is equal to 32.7 k $\Omega$ . Simply applying these to 公式 4 yields the appropriate resistor that must be placed between FREQ and GND:

$$R_{FREQ} = \frac{f_{TYP} \times R_{TYP} \times T_{INT}}{(f_{SW} \times R_{INT}) + (R_{TYP} \times f_{SW}) - (R_{TYP} \times f_{TYP})} \quad (4)$$

$$R_{FREQ} = \frac{65 \text{ kHz} \times 32.7 \text{ k}\Omega \times 1 \text{ M}\Omega}{(130 \text{ kHz} \times 1 \text{ M}\Omega) + (32.7 \text{ k}\Omega \times 130 \text{ kHz}) - (32.7 \text{ k}\Omega \times 65 \text{ kHz})} = 16.2 \text{ k}\Omega$$

A standard resistor of 16.2 k $\Omega$  is used for setting a switching frequency around 130 kHz.

 


图 10. Frequency versus R<sub>FREQ</sub>

### 2.3.1.3 Bridge Rectifier

The input bridge rectifier must have an average current capability that exceeds the input average current. Assuming a forward voltage drop,  $V_{F\_BRIDGE}$ , of 1 V across the rectifier diodes, the power loss in the input bridge,  $P_{BRIDGE}$ , can be calculated as:

$$P_{BRIDGE} = 2 \times V_{F\_BRIDGE} \times I_{IN\_AVG(max)}$$

$$P_{BRIDGE} = 2 \times 1 \times 2.42 = 5.21 \text{ W}$$

Heat sinking is required to maintain operation within the safe operating area of the bridge rectifier.

### 2.3.1.4 Inductor Ripple Current

The UCC28180 is a CCM controller, but if the chosen inductor allows relatively high-ripple current, the converter is forced to operate in DCM at light loads and at the higher input voltage range. High-inductor ripple current has an impact on the CCM and DCM boundary and results in higher light-load THD, and also affects the choices for the input capacitor,  $R_{SENSE}$  and  $C_{ICOMP}$  values. Allowing an inductor ripple current,  $\Delta I_{RIPPLE}$ , of 20% or less results in CCM operation over the majority of the operating range but requires a boost inductor that has a higher inductance value and the inductor itself will be physically large. As with all converter designs, decisions must be made at the onset to optimize performance with size and cost. For this reference design, inductor ripple current is chosen to be 20%.

### 2.3.1.5 Input Capacitor

The input capacitor must be selected based upon the input ripple current and an acceptable high-frequency input voltage ripple. Allowing an inductor ripple current,  $\Delta I_{\text{RIPPLE}}$ , of 20% and a high-frequency voltage ripple factor,  $\Delta V_{\text{RIPPLE\_IN}}$ , of 7%, the maximum input capacitor value,  $C_{\text{IN}}$ , is calculated by first determining the input ripple current,  $I_{\text{RIPPLE}}$ , and the input voltage ripple,  $V_{\text{IN\_RIPPLE}}$ :

$$I_{\text{RIPPLE}} = \Delta I_{\text{RIPPLE}} \times I_{\text{IN(max)}}$$

$$I_{\text{RIPPLE}} = 0.2 \times 4.09 = 0.818 \text{ A}$$

$$V_{\text{IN\_RIPPLE}} = \Delta V_{\text{RIPPLE\_IN}} \times V_{\text{IN\_RECTIFIED(min)}}$$

where:

- $V_{\text{IN\_RECTIFIED(min)}} = \sqrt{2} \times V_{\text{IN(min)}} = \sqrt{2} \times 85 = 120 \text{ V}$
- $V_{\text{IN\_RIPPLE}} = 0.07 \times 120 = 8.415 \text{ V}$

The recommended value for the input x-capacitor can now be calculated using [公式 5](#):

$$C_{\text{IN}} = \frac{I_{\text{RIPPLE}}}{8 \times f_{\text{SW}} \times V_{\text{IN\_RIPPLE}}} \quad (5)$$

$$C_{\text{IN}} = \frac{0.818}{8 \times 130 \times 8.415} = 0.936 \mu\text{F}$$

Two standard value 0.22- $\mu\text{F}$  and 0.47- $\mu\text{F}$  Y2/X2 film capacitors are used at the input of the PFC stage.

### 2.3.1.6 Boost Inductor

Based upon the inductor ripple current allowed, the boost inductor,  $L_{\text{BST}}$ , is selected after determining the maximum inductor peak current,  $I_{\text{LPEAK}}$ :

$$I_{\text{LPEAK(max)}} = I_{\text{IN(max)}} + \frac{I_{\text{RIPPLE}}}{2} \quad (6)$$

$$I_{\text{LPEAK(max)}} = 4.09 + \frac{0.818}{2} = 4.499 \text{ A}$$

The minimum value of the boost inductor is calculated based upon the acceptable ripple current,  $I_{\text{RIPPLE}}$ , at a worst case duty cycle of 0.5:

$$L_{\text{BST(min)}} = \frac{V_{\text{OUT}} \times D \times (1-D)}{f_{\text{SW}} \times I_{\text{RIPPLE}}} \quad (7)$$

$$L_{\text{BST(min)}} = \frac{434 \times 0.5 \times 0.5}{130 \text{ kHz} \times 0.818} = 1.02 \text{ mH}$$

The actual value of the boost inductor that will be used is 1.6 mH. With this actual value used, the actual resultant inductor current ripple will be:

$$I_{\text{RIPPLE}} = \frac{V_{\text{OUT}} \times D \times (1-D)}{f_{\text{SW}} \times L_{\text{BST}}} \quad (8)$$

$$I_{\text{RIPPLE}} = \frac{V_{\text{OUT}} \times D \times (1-D)}{f_{\text{SW}} \times L_{\text{BST}}} = 0.52 \text{ A}$$

$$I_{\text{LPEAK(max)}} = I_{\text{IN(max)}} + \frac{I_{\text{RIPPLE}}}{2} = 4.09 + \frac{0.52}{2} = 4.35 \text{ A} \quad (9)$$

The duty cycle is a function of the rectified input voltage and will be continuously changing over the half line cycle. The duty cycle,  $D_{\text{MAX}}$ , can be calculated at the peak of the minimum input voltage:

$$D_{MAX} = \frac{V_{OUT} - V_{IN\_RECTIFIED(min)}}{V_{OUT}} \quad (10)$$

$$D_{MAX} = \frac{434 - 120}{434} = 0.723$$

### 2.3.1.7 Boost Diode

The diode losses are estimated based upon the forward voltage drop,  $V_F$ , at 125°C and the reverse recovery charge,  $Q_{RR}$ , of the diode. Although the silicon carbide diode is more expensive, using this as a schottky diode essentially eliminates the reverse recovery losses and results in less power dissipation:

$$P_{DIODE} = V_{F\_125C} \times I_{OUT(max)} + 0.5 \times f_{SW} \times V_{OUT} \times Q_{RR} \quad (11)$$

where:

- $V_{F\_125C} = 1 \text{ V}$
- $Q_{RR} = 0 \text{ nC}$
- $P_{DIODE} = (1 \times 0.507) = 0.507 \text{ W}$

This output diode must have a blocking voltage that exceeds the output overvoltage of the converter and be attached to an appropriately sized heat sink.

### 2.3.1.8 Boost MOSFET Selection

The MOSFET switch is driven by a gate output that is clamped at 15.2 V for VCC bias voltages greater than 15.2 V. An external gate drive resistor is recommended to limit the rise time and to dampen any ringing caused by the parasitic inductances and capacitances of the gate drive circuit. This external resistor also helps in meeting any EMI requirements of the converter. This design example uses a 10-Ω as gate resistor. To facilitate a fast turnoff, a standard 100-V, 0.2-A Schottky diode is placed anti-parallel with the gate drive resistor. A 20-kΩ resistor is placed between the gate of the MOSFET and ground to discharge the gate capacitance and protect from inadvertent dV/dt triggered turnon.

For this reference design, a MOSFET with 600-V voltage and 13-A current rating is used. The conduction losses of the switch MOSFET in this reference design are estimated using the  $R_{DS(on)}$  at 125°C, found in the device data sheet, and the calculated drain-to-source RMS current,  $I_{DS\_RMS}$ :

$$P_{COND} = I_{DS\_RMS}^2 \times R_{DS(on)125C}$$

where:

- $R_{DS(on)125C} = 0.346 \text{ } \Omega$

$$I_{DS\_RMS} = \frac{P_{OUT(max)}}{V_{IN\_RECTIFIED(min)}} \times \sqrt{2 - \frac{16 \times V_{IN\_RECTIFIED(min)}}{3\pi \times V_{OUT}}} = \frac{220}{120} \times \sqrt{2 - \frac{16 \times 120}{3\pi \times 2.26 \text{ A}}} \quad (12)$$

$$P_{COND} = 2.267^2 \times 0.346 = 1.778 \text{ W}$$

The switching losses are estimated using the rise time,  $t_r$ , and fall time,  $t_f$ , of the MOSFET gate and the output capacitance losses using 公式 13:

$$P_{SW} = f_{SW} \left( 0.5 \times V_{OUT} \times I_{IN(max)} (t_r + t_f) + 0.5 \times C_{OSS} \times V_{OUT}^2 \right) \quad (13)$$

where:

- $t_r = 7 \text{ ns}$
- $t_f = 6 \text{ ns}$

- $C_{OSS} = 34 \text{ pF}$

$$P_{SW} = 130 \text{ kHz} \left( 0.5 \times 434 \text{ V} \times 4.09 \times (7 \text{ ns} + 6 \text{ ns}) + 0.5 \times 34 \text{ pF} \times 434^2 \right) = 1.8 \text{ W} \quad (14)$$

$$\text{Total FET losses} = P_{COND} + P_{SW} = 1.778 + 1.8 \text{ W} = 3.57 \text{ W}$$

The MOSFET requires an appropriately sized heat sink.

### 2.3.1.9 Sense Resistor

To accommodate the gain of the non-linear power limit, the sense resistor,  $R_{\text{SENSE}}$ , is sized such that it triggers the soft overcurrent at 10% higher than the maximum peak inductor current using the minimum soft overcurrent threshold of the  $I_{\text{SENSE}}$  pin,  $V_{\text{SOC}}$ , of  $I_{\text{SENSE}}$  equal to 0.265 V.

$$R_{\text{SENSE}} = \frac{V_{\text{SOC}(\text{min})}}{I_{\text{L\_PEAK}(\text{max})} \times 1.1} \quad (15)$$

$$R_{\text{SENSE}} = \frac{0.259}{4.35 \times 1.1} = 0.054 \Omega$$

The peak current limit, PCL, protection feature is triggered when current through the sense resistor results in the voltage across  $R_{\text{SENSE}}$  to be equal to the  $V_{\text{PCL}}$  threshold. For a worst case analysis, the maximum  $V_{\text{PCL}}$  threshold is used:

$$I_{\text{PCL}} = \frac{V_{\text{PCL}(\text{max})}}{R_{\text{SENSE}}} \quad (16)$$

$$I_{\text{PCL}} = \frac{0.438}{0.054} = 8.11 \text{ A}$$

To protect the device from inrush current, a standard 221- $\Omega$  resistor,  $R_{\text{ISENSE}}$ , is placed in series with the  $I_{\text{SENSE}}$  pin. A 1000-pF capacitor is placed close to the device to improve noise immunity on the  $I_{\text{SENSE}}$  pin.

### 2.3.1.10 Output Capacitor

The output capacitor,  $C_{\text{OUT}}$ , is sized to meet holdup requirements of the converter. Assuming the downstream converters require the output of the PFC stage to never fall below 300 V,  $V_{\text{OUT\_HOLDUP}(\text{min})}$ , during one and half line cycle.

$$t_{\text{HOLDUP}} = \frac{0.5}{f_{\text{LINE}(\text{min})}} = \frac{0.5}{47} = 10.6 \text{ ms} \quad (17)$$

The minimum calculated value for the capacitor is:

$$C_{\text{OUT}(\text{min})} \geq \frac{2 \times P_{\text{OUT}(\text{max})} \times t_{\text{HOLDUP}}}{V_{\text{OUT}}^2 - V_{\text{OUT\_HOLDUP}(\text{min})}^2} \quad (18)$$

$$C_{\text{OUT}(\text{min})} \geq \frac{2 \times 220 \times 10.6 \text{ ms}}{434^2 - 300^2} \geq 44.7 \mu\text{F}$$

De-rate this capacitor value by 10%; the actual capacitor used is 47  $\mu\text{F}$ .

Verify that the maximum peak-to-peak output ripple voltage will be less than 5% of the output voltage. This ensures that the ripple voltage will not trigger the output overvoltage or output undervoltage protection features of the controller. If the output ripple voltage is greater than 5% of the regulated output voltage, a larger output capacitor is required. The maximum peak-to-peak ripple voltage, occurring at twice the line frequency, and the ripple current of the output capacitor is calculated:

$$V_{\text{OUT\_RIPPLE}(\text{pp})} < 0.05 \times V_{\text{OUT}}$$

$$V_{\text{OUT\_RIPPLE}(\text{pp})} < 0.05 \times 434 \text{ V} = 21.7 \text{ V}_{\text{PP}}$$

$$V_{\text{OUT\_RIPPLE}(\text{pp})} = \frac{I_{\text{OUT}}}{2\pi \times 2 \times f_{\text{LINE}(\text{min})} \times C_{\text{OUT}}} \quad (19)$$

$$V_{\text{OUT\_RIPPLE}(\text{pp})} = \frac{0.507}{2\pi \times 2 \times 47 \times 47 \mu\text{F}} = 18.27 \text{ V}$$

The required ripple current rating at twice the line frequency is equal to 公式 20:

$$I_{\text{COUT\_2fline}} = \frac{I_{\text{OUT(max)}}}{\sqrt{2}} \quad (20)$$

$$I_{\text{COUT\_2fline}} = \frac{0.507}{\sqrt{2}} = 0.358 \text{ A}$$

There is a high-frequency ripple current through the output capacitor:

$$I_{\text{COUT\_HF}} = I_{\text{OUT(max)}} \times \sqrt{\frac{16 \times V_{\text{OUT}}}{3\pi \times V_{\text{IN\_RECTIFIED(min)}}} - 1.5} \quad (21)$$

$$I_{\text{COUT\_HF}} = 0.507 \times \sqrt{\frac{16 \times 434}{3\pi \times 120} - 1.5} = 1.09 \text{ A}$$

The total ripple current in the output capacitor is the combination of both, and the output capacitor must be selected accordingly:

$$I_{\text{COUT\_RMS(total)}} = \sqrt{I_{\text{COUT\_2fline}}^2 + I_{\text{COUT\_HF}}^2} \quad (22)$$

$$I_{\text{COUT\_RMS(total)}} = \sqrt{0.358^2 + 1.09^2} = 1.14 \text{ A}$$

### 2.3.1.11 Output Voltage Set Point

For low-power dissipation and minimal contribution to the voltage set point, it is recommended to use 1 M $\Omega$  for the top voltage feedback divider resistor,  $R_{\text{FB1}}$ . Multiple resistors in series are used due to the maximum allowable voltage across each. Using the internal 5-V reference,  $V_{\text{REF}}$ , the bottom divider resistor,  $R_{\text{FB2}}$ , is selected to meet the output voltage design goals.

$$R_{\text{FB2}} = \frac{V_{\text{REF}} \times R_{\text{FB1}}}{V_{\text{OUT}} - V_{\text{REF}}} \quad (23)$$

$$R_{\text{FB2}} = \frac{5 \text{ V} \times 0.996 \text{ M}\Omega}{434 - 5} = 11.6 \text{ k}\Omega$$

A standard value 11-k $\Omega$  resistor for  $R_{\text{FB2}}$  results in a nominal output voltage set point of 434 V. A small capacitor on  $V_{\text{SENSE}}$  must be added to filter out noise. Limit the value of the filter capacitor such that the RC time constant is limited to approximately 10  $\mu\text{s}$  so as not to significantly reduce the control response time to output voltage deviations.

$$C_{\text{VSENSE}} = \frac{10 \mu\text{s}}{R_{\text{FB2}}} = 909 \text{ pF} \quad (24)$$

The closest standard value of 820 pF is used on  $V_{\text{SENSE}}$  for a time constant of 10.66  $\mu\text{s}$ .

### 2.3.1.12 Loop Compensation

The voltage error amplifier is compensated with a zero,  $f_{\text{ZERO}}$ , at the  $f_{\text{PWM\_PS}}$  pole and a pole,  $f_{\text{POLE}}$ , placed at 20 Hz to reject high-frequency noise and roll off the gain amplitude. The overall voltage loop crossover,  $f_{\text{V}}$ , is desired to be at 10 Hz. The compensation components of the voltage error amplifier are selected accordingly. The design spreadsheet has all relevant equations for characterization of the compensation of the UCC28180 device (see 4.7 节).



### 2.3.2 Circuit Design of Dual Switch Flyback

The UCC28740 is a quasi-resonant flyback controller that provides CV mode control and CC mode control for precise output regulation. In this design, the controller uses an optocoupler for tight output voltage and current regulation and also for improved transient response to large load steps. The UCC28740 uses frequency modulation, peak primary current modulation, valley switching, and valley hopping in its control algorithm to maximize efficiency over the entire operating range.

表 3. Design Goal Parameters for Dual Switch Flyback Stage

PARAMETER		MIN	TYP	MAX	UNIT
<b>INPUT</b>					
$V_{\text{INDC}}$	DC input voltage range (from PFC output)	300		460	VAC
<b>OUTPUT</b>					
$V_{\text{OUT}}$	Output voltage	199.6	200	201	VDC
$I_{\text{OUT}}$	Output current		1	1.1	ADC
$I_{\text{OCC}}$	Output overcurrent			1.1	ADC
$P_{\text{OUT}}$	Output power (max)		200		W
	Line regulation			< 1%	
	Load regulation			< 1%	
$f_{\text{MAX}}$	Maximum desired switching frequency			60	kHz
$\eta$	Targeted efficiency		90%		

#### 2.3.2.1 Input Bulk Capacitance and Minimum Bulk Voltage

Because a PFC front-end is used in this reference design, the PFC output capacitor is the input capacitance for the flyback converter ( $C = 47 \mu\text{F}$ ).

The minimum voltage operation of flyback is defined by the holdup voltage of the PFC converter during brownout conditions ( $V_{\text{HOLD\_UP(min)}} = 300 \text{ V}$ ).

Considering a maximum of 20-V ripple voltage on the capacitor:

$$V_{\text{BULK(min)}} = V_{\text{HOLD\_UP(min)}} - 20 \text{ V} = 280 \text{ V}$$

#### 2.3.2.2 Transformer Parameter Calculations: Turns Ratio, Primary Inductance, and Peak Primary Current

The target maximum switching frequency at full load, the minimum input-capacitor bulk voltage, and the estimated DCM  $Q_R$  time determine the maximum primary-to-secondary turns ratio of the transformer. Initially determine the maximum-available total duty cycle of the on-time and secondary conduction time based on the target switching frequency,  $f_{\text{MAX}}$ , and DCM resonant time. For DCM resonant frequency, assume 500 kHz if an estimate from previous designs is not available. At the TM operation limit of DCM, the interval required from the end of secondary current conduction to the first valley of the  $V_{\text{DS}}$  voltage is  $\frac{1}{2}$  of the DCM resonant period ( $t_R$ ), or  $1 \mu\text{s}$  assuming a 500-kHz resonant frequency. The maximum allowable MOSFET on-time  $D_{\text{MAX}}$  is determined using 公式 25.

$$D_{\text{MAX}} = 1 - D_{\text{MAGCC}} - f_{\text{MAX}} \frac{t_R}{2} \quad (25)$$

where:

- $t_R$  is the estimated period of the LC resonant frequency at the switch node
- $D_{\text{MAGCC}}$  is defined as the duty cycle of the secondary-diode conduction during CC operation and is fixed

internally by the UCC28740 at 0.425

$$D_{\text{MAX}} = 1 - 0.425 - 60 \text{ kHz} \times \frac{2 \mu\text{s}}{2} = 0.51$$

When  $D_{MAX}$  is known, the maximum primary-to-secondary turns ratio is determined with [公式 26](#). The total voltage on the secondary winding must be determined, which is the sum of  $V_{OCV}$ ,  $V_F$ , and  $V_{OCBC}$ .

$$N_{PS(max)} = \frac{D_{MAX} \times V_{BULK(min)}}{D_{MAGCC} \times (V_{OCV} + V_F + V_{OCBC})} \quad (26)$$

$V_{OCBC}$  is the additional voltage drop of post filter inductor and any other target cable-compensation voltage added to  $V_{OCV}$  (provided by an external adjustment circuit applied to the shunt regulator).

Assuming  $V_{OCBC} = 0$  and  $V_F = 0.6$  V:

$$N_{PS(max)} = \frac{0.51 \times 300}{0.425 \times (200 + 0.6)} = 1.794$$

A higher turns ratio generally improves efficiency, but may limit operation at a low input voltage. The transformer turns ratio selected affects the MOSFET  $V_{DS}$  and secondary rectifier reverse voltage, so these must be reviewed. The UCC28740 controller requires a minimum on time of the MOSFET ( $t_{ON(min)}$ ) and minimum secondary rectifier conduction time ( $t_{DM(min)}$ ) in the high line and minimum load condition. The selection of  $f_{MAX}$ ,  $L_P$ , and  $R_{CS}$  affects  $t_{ON(min)}$  and  $t_{DM(min)}$ . The secondary rectifier and MOSFET voltage stress can be determined by [公式 27](#).

$$V_{REV} = \frac{V_{IN(max)} \times \sqrt{2}}{N_{PS}} + V_{OCV} + V_{OCBC} \quad (27)$$

For the MOSFET  $V_{DS}$  voltage stress, include an estimated leakage inductance voltage spike ( $V_{LK}$ ).

$$V_{DSPK} = (V_{IN(max)} \times \sqrt{2}) + (V_{OCV} + V_F + V_{OCBC}) \times N_{PS} + V_{LK} \quad (28)$$

[公式 29](#) determines if  $t_{ON(min)}$  exceeds the minimum  $t_{ON}$  target of 280 ns (maximum  $t_{CSLEB}$ ). [公式 30](#) verifies that  $t_{DM(min)}$  exceeds the minimum  $t_{DM}$  target of 1.2  $\mu$ s.

$$t_{ON(min)} = \frac{L_P}{V_{IN(max)} \times \sqrt{2}} \times \frac{I_{PP(max)}}{K_{AM}} \quad (29)$$

$$T_{DM(min)} = \frac{t_{ON(min)} \times V_{IN(max)} \times \sqrt{2}}{N_{PS} \times (V_{OCV} + V_F)} \quad (30)$$

To determine the optimum turns ratio,  $N_{PS}$ , design iterations are generally necessary to optimize and evaluate system-level performance trade-offs and parameters mentioned in [公式 27](#) to [公式 30](#).

When the optimum turns ratio  $N_{PS}$  is determined from a detailed transformer design, use this ratio for the following parameters. For this reference design,  $N_{PS} = 1.5$  is selected on optimization.

The UCC28740 CC regulation is achieved by maintaining  $D_{MAGCC}$  at the maximum primary peak current setting. The product of  $D_{MAGCC}$  and  $V_{CST(max)}$  defines a CC-regulating voltage factor,  $V_{CCR}$ , which is used with  $N_{PS}$  to determine the current-sense resistor value necessary to achieve the regulated CC target,  $I_{OCC}$  (see [公式 31](#)).

$$I_{PP(max)} = \frac{0.81}{0.21} = 3.85 \text{ A} \quad (31)$$

Because a small portion of the energy stored in the transformer does not transfer to the output, a transformer efficiency term is included in 公式 31. This efficiency number includes the core and winding losses, the leakage-inductance ratio, and a bias-power to maximum-output-power ratio. For example, an overall transformer efficiency of 0.9 is a good estimate based on 3.5% leakage inductance, 5% core and winding loss, and 0.5% bias power. Adjust these estimates appropriately based on each specific application.

$$I_{PP(nom)} = \frac{0.773}{0.21} = 3.68 \text{ A}$$

$V_{CCR(min)}$  is the minimum CC regulation factor and device parameter = 0.33 V. The standard value of current sense resistor selected is  $R_{CS} = 0.21 \Omega$ . Two parallel resistors to  $R_{CS}$  are added in the schematic to adjust values easily.

To calculate primary inductance, first determine the transformer primary peak current using 公式 32. Peak primary current is the maximum current-sense threshold divided by the current-sense resistance:

$$I_{PP(max)} = \frac{V_{CST(max)}}{R_{CS}} \quad (32)$$

$$R_{LED\_SNS} = \frac{V_{TH}}{I_{OUT(max)} \times INA_{gain}} = \frac{1}{1 \times 50} = 0.02 \Omega$$

$$V_{TH} = \frac{V_{OUT} \times R_{FB2}}{R_{FB1} + R_{FB2}} \quad (33)$$

The primary transformer inductance is calculated using the standard energy storage equation for flyback transformers. Primary current, maximum switching frequency, output voltage and current targets, and transformer power losses are included in 公式 34:

$$L_P = \frac{2 \times (V_{OCV} + V_F + V_{OCBC}) \times I_{OCC}}{\eta \times FMR \times I_{PP(max)}^2 \times f_{MAX}} \quad (34)$$

$$L_P = \frac{2 \times (200 + 0.6) \times 1.1}{0.9 \times 3.85^2 \times 60 \text{ kHz}} = 551 \mu\text{H}$$

The actual primary inductance selected is  $L_P = 600 \mu\text{H}$ .

$N_{AS}$  is determined by the lowest target operating output voltage while in CC regulation and by the  $V_{DD}$  UVLO turnoff threshold of the UCC28740. Additional energy is supplied to  $V_{DD}$  from the transformer leakage-inductance, which allows a lower turns ratio to be used in many designs.

$$N_{AS} = \frac{V_{DD(off)} + V_{FA}}{V_{OCC} + V_F} = \frac{8.15 + 0.9}{8.5 + 0.4} = 0.925 \quad (35)$$

### 2.3.2.3 Transformer Parameter Calculations: Primary and Secondary RMS Currents

With the primary inductance of 600  $\mu\text{H}$ , the absolute maximum switching frequency is calculated from 公式 36:

$$f_{MAX} = \frac{2 \times (200 + 0.6) \times 1.1}{0.9 \times 3.85^2 \times 600 \mu\text{H}} = 55.1 \text{ kHz} \quad (36)$$

The maximum switching period is:

$$t_{SW} = \frac{1}{f_{MAX}} = \frac{1}{55.1 \text{ kHz}} = 18.14 \mu\text{s} \quad (37)$$

The actual maximum on-time is given by 公式 38:

$$t_{\text{ON(max)}} = \frac{I_{\text{PP(nom)}} \times L_{\text{P}}}{V_{\text{BULK(min)}}} = \frac{3.68 \times 600 \mu\text{H}}{300} = 7.36 \mu\text{s} \quad (38)$$

The maximum duty cycle of operation ( $D_{\text{MAX}}$ ) is:

$$D_{\text{MAX}} = \frac{t_{\text{ON(max)}}}{t_{\text{SW}}} = \frac{7.36 \mu\text{s}}{18.14 \mu\text{s}} = 0.405 \quad (39)$$

The transformer primary RMS current ( $I_{\text{PRMS}}$ ) is:

$$I_{\text{PRMS}} = I_{\text{PP(nom)}} \sqrt{\frac{D_{\text{MAX}}}{3}} = 3.68 \times \sqrt{\frac{0.405}{3}} = 1.35 \text{ A} \quad (40)$$

The transformer secondary peak current RMS current ( $I_{\text{SEC(max)}}$ ) is:

$$I_{\text{SEC(max)}} = I_{\text{PP(max)}} \times N_{\text{PS}} = 3.85 \times 1.5 = 5.77 \text{ A}$$

The transformer secondary RMS current ( $I_{\text{SEC\_RMS}}$ ) is:

$$I_{\text{SEC\_RMS}} = I_{\text{SEC(max)}} \sqrt{\frac{D_{\text{MAX}}}{3}} = 5.77 \times \sqrt{\frac{0.425}{3}} = 2.17 \text{ A} \quad (41)$$

Based on these calculations, a Minntronix transformer was designed for this application (part number 4815839), which has the following specifications:

- $N_{\text{PS}} = 1.5$
- $N_{\text{PA}} = 15$
- $L_{\text{P}} = 600 \mu\text{H}$
- $L_{\text{LK}} = 3.5 \mu\text{H}$  (which denotes the primary leakage inductance)

#### 2.3.2.4 Main Switching Power MOSFET Selection

The drain-to-source RMS current,  $I_{\text{DS\_RMS}}$ , through switching FET is calculated using 公式 42:

$$I_{\text{DS\_RMS}} = I_{\text{PP(max)}} \times \sqrt{\frac{D_{\text{MAX}}}{3}} = 3.85 \times \sqrt{\frac{0.405}{3}} = 1.41 \text{ A} \quad (42)$$

Select a MOSFET with five times the  $I_{\text{DS\_RMS}}$  calculated. The maximum voltage across the FET can be estimated using 公式 28. Considering a de-rating of 25% and leakage spike of around 250 V, the voltage rating of the MOSFET in a dual switch flyback must be around 1200-V DC. Two STF18N65M2 MOSFETs of 650 V and 11 A at 25°C / 8 A at 100°C are selected for this reference design.

#### 2.3.2.5 Rectifying Diode Selection

Calculate the secondary output diode or synchronous rectifier FET reverse voltage or blocking voltage needed ( $V_{\text{DIODE\_BLOCKING}}$ ):

$$V_{\text{DIODE\_BLOCKING}} = \frac{V_{\text{IN\_DC(max)}}}{N_{\text{PS}}} + V_{\text{OUT\_OVP}} + V_{\text{OCBC}} \quad (43)$$

$$V_{\text{DIODE\_BLOCKING}} = \frac{460}{1.5} + 200 = 506.6 \text{ V}$$

The required minimum average rectified output current is:

$$I_{\text{DOUT}} = I_{\text{SEC\_RMS}} = 2.17 \text{ A}$$

A silicon carbide Schottky diode is recommended for low power loss and high-efficiency needs. For this reference design, the silicon carbide Schottky diode (C3D04060A) with a 600-V voltage and 4-A forward current rating is selected to optimize the on-state losses.

### 2.3.2.6 Output Capacitor Selection

For this reference design, the output capacitor ( $C_{OUT}$ ) for output is selected to prevent  $V_{OUT}$  (= 200 V) from dropping below the minimum output voltage ( $V_{OTRM}$ ) during transients up to 0.36 V and ripple voltage less than 100 mV.

$$C_{OUT} \geq \frac{\frac{I_{OUT}}{2} \times (t)}{V_{OUT} - V_{OTRM}} \quad (44)$$

where:

- $V_{OTRM} = 199.64$  V

$$C_{OUT} \geq \frac{\frac{1.1}{2} \times (3.33 \mu\text{s})}{200 - 199.64} \geq 50.8 \mu\text{F}$$

Considering the allowable output ripple voltage of 120 mV (5%), the ESR of the capacitor must be:

$$\text{ESR} = \frac{V_{OUT\_RIPPLE}}{I_{SEC(max)}} = \frac{120 \text{ mV}}{5.77 \text{ A}} = 20.7 \text{ m}\Omega \quad (45)$$

$$I_{COUT\_RMS} = \sqrt{(I_{SEC\_RMS})^2 - (I_{OUT})^2} = \sqrt{(2.17)^2 - (1.1)^2} = 1.87 \text{ A} \quad (46)$$

Two 47- $\mu\text{F}$ , 250-V capacitors are selected for the output.

### 2.3.2.7 Capacitance on VDD Pin

The capacitance on VDD needs to supply the device operating current until the output of the converter reaches the target minimum operating voltage in CC regulation.

The capacitance on VDD must supply the primary-side operating current used during startup and between low-frequency switching pulses. The largest result of two independent calculations denoted in [公式 47](#) determines the value of  $C_{VDD}$ .

At start-up, when  $V_{VDD(on)}$  is reached,  $C_{VDD}$  alone supplies the device operating current and MOSFET gate current until the output of the converter reaches the target minimum operating voltage in CC regulation,  $V_{OCC}$ . Now the auxiliary winding sustains VDD for the UCC28740 above UVLO. The total output current available to the load and to charge the output capacitors is the CC-regulation target,  $I_{OCC}$ . [公式 47](#) assumes that all of the output current of the converter is available to charge the output capacitance until  $V_{OCC}$  is achieved. For typical applications, [公式 47](#) includes an estimated  $q_G \times f_{SW(max)}$  of average gate drive current and a 1-V margin added to  $V_{VDD}$ .

$$C_{VDD} \geq \frac{(I_{RUN} + q_G \times f_{SW(max)}) \times \frac{C_{OUT} \times V_{OCC}}{I_{OCC}}}{V_{DD(on)} - (V_{DD(off)} + 1 \text{ V})} \quad (47)$$

$$C_{VDD} \geq \frac{(2 \text{ mA} + 9.9 \text{ nC} \times 60 \text{ kHz}) \times \frac{94 \mu\text{F} \times 201 \text{ V}}{1.1}}{21 - (8.5 + 1 \text{ V})} \geq 3.87 \mu\text{F}$$

During a worst-case un-load transient event from full load to no load,  $C_{OUT}$  overcharges above the normal regulation level for a duration of  $t_{OV}$  until the output shunt regulator loading is able to drain  $V_{OUT}$  back to regulation. During  $t_{OV}$ , the voltage feedback loop and optocoupler are saturated, driving maximum  $I_{FB}$  and temporarily switching at  $f_{SW(min)}$ . The auxiliary bias current expended during this situation exceeds that normally required during the steady-state no-load condition.



The current design uses 10- $\mu$ F and 2.2- $\mu$ F capacitors.

### 2.3.2.8 Open-Loop Voltage Regulation versus Pin Resistor Divider, Line Compensation Resistor

The resistor divider at the  $V_S$  pin determines the output voltage regulation point of the flyback converter. Also, the high-side divider resistor ( $R_{S1}$ ) determines the line voltage at which the controller enables continuous DRV operation.  $R_{S1}$  is initially determined based on transformer auxiliary-to-primary turns ratio and desired input voltage operating threshold.

$$R_{S1} = \frac{V_{IN(run)} \times \sqrt{2}}{N_{PA} \times I_{VSL(min)}} \quad (48)$$

where:

- $N_{PA}$  is the transformer primary-to-auxiliary turns ratio
- $V_{IN(run)}$  is the AC RMS voltage to enable turnon of the controller (run); in case of DC input, leave out the  $\sqrt{2}$  term in the equation
- $I_{VSL(run)}$  is the run threshold for the current pulled out of the VS pin during the switch on-time (see the Electrical Characteristics section of the [UCC28740 data sheet](#))

$$R_{S1} = \frac{390 \text{ V}}{15 \times 275 \mu\text{A}} = 110 \text{ k}\Omega$$

A standard resistor of 110 k $\Omega$  is selected.

The low-side VS pin resistor is selected based on the desired  $V_{OUT}$  regulation voltage in open-loop conditions and sets maximum allowable voltage during open-loop conditions.

$$R_{S2} = \frac{R_{S1} \times V_{OVPTH}}{N_{AS} \times (V_{OV} - V_F) - V_{OVPTH}} \quad (49)$$

where:

- $V_{OV}$  is the maximum allowable peak voltage at the converter output
- $V_F$  is the output-rectifier forward drop at near-zero current
- $N_{AS}$  is the transformer auxiliary-to-secondary turns ratio
- $R_{S1}$  is the VS divider high-side resistance
- $V_{OVPTH}$  is the overvoltage detection threshold at the VS input (see the Electrical Characteristics section of the [UCC28740 data sheet](#))

$$R_{S2} = \frac{110 \text{ k}\Omega \times 4.6}{0.1 \times (201 - 0.6) - 4.6} = 32.77 \text{ k}\Omega$$

A standard resistor of 33.2 k $\Omega$  is selected.

The UCC28740 maintains tight CC regulation over varying input line by using the line-compensation feature. The line-compensation resistor ( $R_{LC}$ ) value is determined by current flowing in  $R_{S1}$  and the total internal gate drive and external MOSFET turnoff delay. Assuming an internal delay of 50 ns in the UCC28740:

$$R_{LC} = \frac{K_{LC} \times R_{S1} \times R_{CS} \times t_D \times N_{PA}}{L_P} \quad (50)$$

where:

- $R_{CS}$  is the current-sense resistor value

- $t_D$  is the current-sense delay including MOSFET turnoff delay
- $N_{PA}$  is the transformer primary-to-auxiliary turns ratio
- $L_P$  is the transformer primary inductance
- $K_{LC}$  is a current-scaling constant (see the Electrical Characteristics section of the [UCC28740 data sheet](#))

$$R_{LC} = \frac{25 \times 71.5 \text{ k}\Omega \times 0.21 \times 46 \text{ ns} \times 15}{600 \text{ }\mu\text{H}} = 720 \text{ }\Omega$$

A standard resistor of 590  $\Omega$  is selected.

### 2.3.2.9 Feedback Elements

In this reference design, the secondary side CC-CV control is implemented using two op amps where LED current regulation is achieved using the [INA180](#), which is used for sensing output LED current through sensing voltage across sense resistor. Output voltage regulation is achieved using feedback based on the resistor divider (R221, R223, and R225). The value of the LED current sensing resistor can be calculated using [公式 51](#) based on INA180 gain (50 V/V), reference voltage setting (1 V), and full-load LED current (1 A).

$$R_{LED\_SNS} = \frac{V_{TH}}{I_{OUT(max)} \times INA_{GAIN}} = \frac{1}{1 \times 50} = 0.02 \text{ }\Omega \quad (51)$$

The output voltage is set through the sense network resistors  $R_{FB1}$  and  $R_{FB2}$ . The value of feedback resistor can be chosen based on desired output voltage by [公式 52](#).

$$V_{TH} = \frac{V_{OUT} \times R_{FB2}}{R_{FB1} + R_{FB2}} \quad (52)$$

where:

- $V_{TH} = 1 \text{ V}$

Assuming  $R_{FB1} = 224 \text{ k}\Omega$  and setting  $V_{OUT} = 200 \text{ V}$ , the value of  $R_{FB2}$  as calculated per [公式 52](#) is 1.23 k $\Omega$ .

The op amp compensation network,  $Z_{FB}$ , is determined using well-established design techniques for control-loop stability. Typically, a type-II compensation network is used.

### 3 Hardware, Testing Requirements, and Test Results

#### 3.1 Required Hardware

- Isolated AC source (0- to 305-V AC / 3 A)
- Single-phase power analyzer
- DC power supply (0- to 10-V DC / 0.3 A)
- Digital oscilloscope
- Digital multimeter
- High-wattage LED load

#### 3.2 Testing and Results


##### 3.2.1 Test Setup

###### 3.2.1.1 Test Conditions

- Input voltage range: The AC source must be capable of varying a  $V_{INAC}$  between 85- and 305-V AC. Set input current limit to 3 A.
- Output: Connect an LED load capable of 200 V and a load variable in range from 0 to 1 A.
- External DC input voltage: External DC signal up to 10 V is required to turn on or off the PFC stage in the power supply reference design.

3.2.1.2 Test Procedure

图 11 shows the flow followed to test the reference design PCB and perform 0- to 10-V dimming.

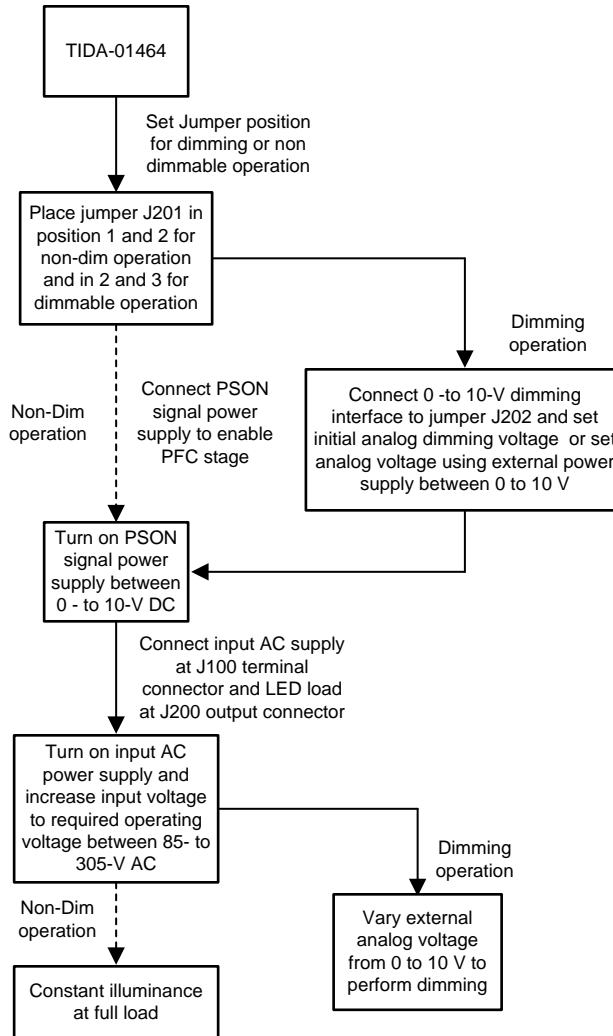

NOTE: PSON signal can be pulled low to turn off TIDA-01464 LED power supply

Copyright © 2017, Texas Instruments Incorporated

图 11. Test Flow for TIDA-01464

### 3.2.2 Test Results

The test results are divided into multiple sections that cover the steady state performance measurements, current harmonics measurements, functional performance waveforms and test data, transient performance waveforms, and thermal measurements.

#### 3.2.2.1 Performance Data With 196-V and 102-V LED Loads With Input Line Voltage Variation at Full Load

表 4. Test Data With 102-V LED Load at Full Load

V <sub>IN</sub> (V)	FREQ (Hz)	V <sub>RMS</sub> (V)	I <sub>RMS</sub> (A)	P <sub>IN</sub> (W)	PF	A <sub>THD</sub>	V <sub>OUT</sub> (V)	I <sub>LED</sub> (A)	P <sub>OUT</sub> (W)	EFFICIENCY
85	50	84.07	1.39	116.9	0.998	3.36%	102	1	102	87.25%
100	50	109.09	1.06	115.8	0.997	3.40%	102	1	102	88.08%
120	50	120	0.964	114.9	0.997	3.60%	102	1	102	88.77%
180	50	179.5	0.636	112.8	0.989	4.31%	102	1	102	90.43%
230	50	230.05	0.502	113.2	0.976	4.47%	102.1	1.01	103.121	91.10%
265	50	265.61	0.443	112.7	0.963	4.53%	102.2	1.01	103.222	91.59%

表 5. Test Data With 196-V LED Load at Full Load

V <sub>IN</sub> (V)	FREQ (Hz)	V <sub>RMS</sub> (V)	I <sub>RMS</sub> (A)	P <sub>IN</sub> (W)	PF	A <sub>THD</sub>	V <sub>OUT</sub> (V)	I <sub>LED</sub> (A)	P <sub>OUT</sub> (W)	EFFICIENCY
85	50	83.92	2.69	225.2	0.995	11.18%	195.9	1	195.9	86.99%
100	50	98.9	2.23	220.8	0.997	7.20%	196	1	196	88.77%
120	50	118.97	1.86	218.5	0.998	4.30%	196	1	196	89.70%
180	50	179.5	1.19	214.8	0.995	3.50%	196	1	196	91.25%
230	50	230.1	0.936	213.2	0.991	3.80%	196	1	196	91.93%
265	50	265	0.811	212.5	0.986	3.90%	196.2	1	196.2	92.33%

#### 3.2.2.1.1 Functional Performance Graphs With Input Line Voltage Variation at Full Load

 


图 12. Line Voltage versus V<sub>OUT</sub> at Full Load

 


图 13. Line Voltage versus Efficiency at Full Load

 


图 14. Line Voltage versus LED Current at Full Load

 


图 15. Line Voltage versus THD at Full Load

 


图 16. Line Voltage versus Power Factor at Full Load

### 3.2.2.2 Dimming Data for 196-V and 102-V LED Loads

#### 3.2.2.2.1 Dimming Data With 196-V LED Load at Different Operating Line Voltages

表 6. Performance Data With Dimming at 120-V/50-Hz Input AC Voltage

I <sub>ADJ</sub> (V)	I <sub>RMS</sub> (A)	P <sub>IN</sub> (W)	PF	A <sub>THD</sub>	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	P <sub>OUT</sub> (W)	EFFICIENCY
10	1.848	218.5	0.997	4.26	196	1	196	89.70%
9	1.62	192.6	0.997	3.69	193.9	0.891	172.7649	89.70%
8	1.425	169.3	0.997	3.36	192.3	0.79	151.917	89.73%
7	1.236	146.8	0.997	3.26	190.6	0.691	131.7046	89.72%
6	1.05	125.1	0.997	3.45	188.7	0.594	112.0878	89.60%
5	0.874	103.8	0.996	4.03	186.7	0.496	92.6032	89.21%
4	0.698	82.9	0.995	4.8	184.2	0.399	73.4958	88.66%
3	0.525	62.25	0.991	6.87	181.1	0.301	54.5111	87.57%
2	0.356	41.9	0.983	9.87	176.8	0.202	35.7136	85.24%
1	0.193	21.96	0.951	15.88	170.7	0.101	17.2407	78.51%
0.8	0.158	17.74	0.935	16	169.1	0.081	13.6971	77.21%

表 7. Performance Data With Dimming at 230-V/50-Hz Input AC Voltage

I <sub>ADJ</sub> (V)	I <sub>RMS</sub> (mA)	P <sub>IN</sub> (W)	PF	A <sub>THD</sub>	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	P <sub>OUT</sub> (W)	EFFICIENCY
10	937.8	213.2	0.99	3.87	196	1	196	91.93%
9	826.4	187.9	0.989	3.76	194.1	0.889	172.5549	91.83%
8	729.2	165.5	0.987	3.76	192.5	0.789	151.8825	91.77%
7	635.9	143.9	0.984	3.92	190.8	0.691	131.8428	91.62%
6	545.4	122.9	0.979	4.29	189	0.593	112.077	91.19%
5	456.6	102.2	0.972	4.86	186.9	0.496	92.7024	90.71%
4	369.9	81.76	0.96	5.86	184.4	0.399	73.5756	89.99%
3	284.2	61.42	0.935	7.22	181.2	0.301	54.5412	88.80%
2	198.8	41.8	0.891	11.36	177.1	0.203	35.9513	86.01%
1	126.1	21.3	0.733	20.5	170.9	0.101	17.2609	81.04%
0.8	109.1	17.33	0.689	20.75	169.2	0.081	13.7052	79.08%

表 8. Performance Data With Dimming at 265-V/50-Hz Input AC Voltage

I <sub>ADJ</sub> (V)	I <sub>RMS</sub> (mA)	P <sub>IN</sub> (W)	PF	A <sub>THD</sub>	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	P <sub>OUT</sub> (W)	EFFICIENCY
10	802.2	212.5	0.985	3.96	196.2	1	196.2	92.33%
9	711.2	185.6	0.982	3.85	193.5	0.885	171.2475	92.27%
8	629.6	163.7	0.979	3.86	191.9	0.786	150.8334	92.14%
7	550.8	142.5	0.974	4.02	190.2	0.689	131.0478	91.96%
6	474	121.8	0.966	4.36	188.4	0.592	111.5328	91.57%
5	399.2	101.3	0.955	4.97	186.4	0.495	92.268	91.08%
4	326.1	81	0.935	5.7	183.9	0.398	73.1922	90.36%
3	252.5	60.7	0.904	8.77	180.9	0.301	54.4509	89.70%
2	182.8	40.4	0.832	16.24	176.6	0.202	35.6732	88.30%
1	118.3	20.8	0.665	23.4	170.4	0.101	17.2104	82.74%
0.8	106.6	17.1	0.604	28.4	168.8	0.081	13.6728	79.96%

3.2.2.2.1.1 Performance Graphs With 196-V LED Load

 


图 17. Output Power versus Efficiency at Different Line Voltages

 


图 18. Output Power versus Power Factor at Different Line Voltages

 


图 19. Output Power versus THD at Different Line Voltages

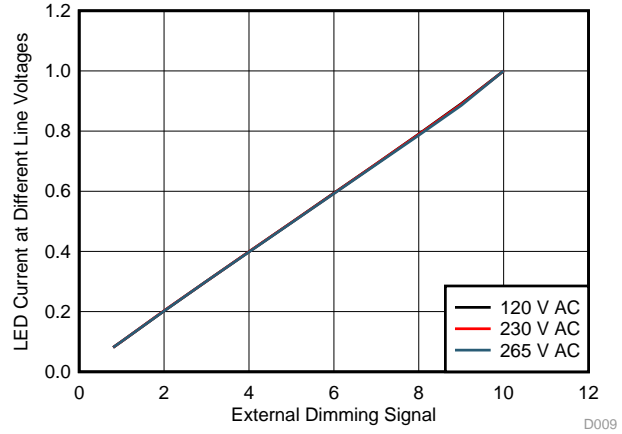


图 20. External Dimming Signal versus LED Current at Different Line Voltages

3.2.2.2.2 Dimming Data With 102-V LED Load at Different Operating Line Voltages

表 9. Performance Data With Dimming at 120-V/50-Hz Input AC Voltage

I <sub>ADJ</sub> (V)	I <sub>RMS</sub> (mA)	P <sub>IN</sub> (W)	PF	A <sub>THD</sub>	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	P <sub>OUT</sub> (W)	EFFICIENCY
10	964	114.9	0.997	3.60%	102	1	102	88.77%
9	857.6	101.8	0.996	4.02%	101.3	0.891	90.2583	88.66%
8	753.4	89.4	0.995	4.61%	100.4	0.785	78.814	88.16%
7	655.7	77.7	0.994	5.35%	99.5	0.686	68.257	87.85%
6	561.8	66.5	0.992	6.32%	98.6	0.59	58.174	87.48%
5	470.6	55.5	0.989	7.59%	97.6	0.494	48.2144	86.87%
4	380.9	44.7	0.985	9.23%	96.4	0.398	38.3672	85.83%
3	292.7	34.1	0.976	11.50%	95.08	0.301	28.61908	83.93%
2	205.4	23.4	0.956	15.10%	93.24	0.203	18.92772	80.89%
1	104.6	12.4	0.913	18.70%	90.62	0.101	9.15262	73.81%
0.8	91	9.6	0.888	20.18%	89.9	0.082	7.3718	76.79%

表 10. Performance Data With Dimming at 230-V/50-Hz Input AC Voltage

I <sub>ADJ</sub> (V)	I <sub>RMS</sub> (mA)	P <sub>IN</sub> (W)	PF	A <sub>THD</sub>	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	P <sub>OUT</sub> (W)	EFFICIENCY
10	502	113.2	0.976	4.47%	102.1	1.01	103.121	91.10%
9	449.5	100.5	0.971	4.88%	101.4	0.893	90.5502	90.10%
8	397.4	88.2	0.965	5.47%	100.5	0.786	78.993	89.56%
7	348.8	76.7	0.955	6.04%	99.6	0.686	68.3256	89.08%
6	302.3	65.6	0.942	6.85%	98.6	0.589	58.0754	88.53%
5	257.5	54.6	0.922	7.17%	97.6	0.494	48.2144	88.30%
4	210.9	43.6	0.899	9.69%	96.5	0.397	38.3105	87.87%
3	166.4	32.6	0.851	15.50%	95.1	0.301	28.6251	87.81%
2	131	22.6	0.752	20.20%	93.28	0.203	18.93584	83.79%
1	89.7	11.8	0.573	25.20%	90.6	0.101	9.1506	77.55%
0.8	79.4	9.7	0.531	31.80%	89.96	0.081	7.28676	75.12%



表 11. Performance Data With Dimming at 265-V/50-Hz Input AC Voltage

$I_{ADJ}$ (V)	$I_{RMS}$ (mA)	$P_{IN}$ (W)	PF	$A_{THD}$	$V_{OUT}$ (V)	$I_{OUT}$ (A)	$P_{OUT}$ (W)	EFFICIENCY
10	443	112.7	0.963	4.53%	102.2	1.01	103.222	91.59%
9	397	100.68	0.954	4.97%	101.2	0.897	90.7764	90.16%
8	348	87.33	0.942	5.49%	100.2	0.783	78.4566	89.84%
7	308.1	75.9	0.927	5.85%	99.39	0.685	68.08215	89.70%
6	268	64.8	0.91	6.69%	98.47	0.588	57.90036	89.35%
5	228.5	53.9	0.888	9.68%	97.48	0.493	48.05764	89.16%
4	191.5	43.2	0.849	16.60%	96.34	0.397	38.24698	88.53%
3	160	32.9	0.775	20.80%	95	0.301	28.595	86.91%
2	123.7	22.5	0.684	25.40%	93.2	0.203	18.9196	84.09%
1	89.1	11.6	0.494	38.60%	90.57	0.101	9.14757	78.86%
0.8	84	9.5	0.425	45.00%	89.89	0.081	7.28109	76.64%

3.2.2.2.1 Performance Graphs With 102-V LED Load

 


图 21. Output Power versus Efficiency at Different Line Voltages

 


图 22. Output Power versus Power Factor at Different Line Voltages

 


图 23. Output Power versus THD at Different Line Voltages

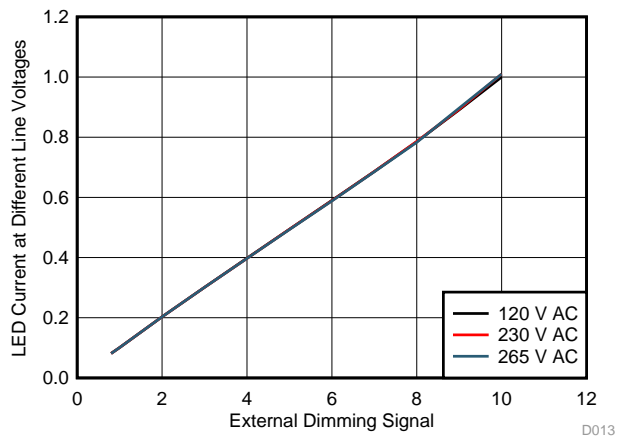


图 24. External Dimming Signal versus LED Current at Different Line Voltages

3.2.2.3 Input Harmonic Currents Tested as per IEC 6100-3-2

表 12. EN 61000-3-2 Class C Limits for System Power > 25 W

HARMONICS ORDER n	MAXIMUM VALUE EXPRESSED AS A PERCENTAGE OF THE FUNDAMENTAL INPUT CURRENT
2	< 2%
3	< 30 λ% <sup>(1)</sup>
5	10%
7	< 7%
9	< 5%
11 ≤ n ≤ 39	< 3%

(1) λ = Power factor

3.2.2.3.1 Input Current Harmonics Tested at 22% Load With 196-V LED Load

表 13. Test Conditions for 22% Load With 196-V LED Load

I <sub>ADJ</sub> (V)	V <sub>IN</sub> (V)	FREQ (Hz)	I <sub>IN</sub> (mA)	P <sub>IN</sub> (W)	PF	A <sub>THD</sub>	P <sub>OUT</sub> (W)
2.2	230	50	216.79	45.043	0.902	8.10%	39.54

 


图 25. Harmonic Test Results at 230-V AC and 22% Load

### 3.2.2.3.2 Input Current Harmonics Tested at 100% Load With 196-V LED Load

表 14. Test Conditions for 100% Load With 196-V LED Load

$I_{ADJ}$ (V)	$V_{IN}$ (V)	FREQ (Hz)	$I_{IN}$ (mA)	$P_{IN}$ (W)	PF	$A_{THD}$	$P_{OUT}$ (W)
10	230	50	936.71	213.2	0.99	3.87%	196

 


图 26. Harmonic Test Results at 230-V AC and 100% Load

### 3.2.2.3.3 Input Current Harmonics Tested at 36% Load With 102-V LED Load

表 15. Test Conditions for 36% Load With 102-V LED Load

$I_{ADJ}$ (V)	$V_{IN}$ (V)	FREQ (Hz)	$I_{IN}$ (mA)	$P_{IN}$ (W)	PF	$A_{THD}$	$P_{OUT}$ (W)
3.8	230	50	202.68	41.65	0.893	9.62%	36.56

 


图 27. Harmonic Test Results at 230-V AC and 36% Load

### 3.2.2.4 Functional Waveforms

This section comprises of various functional waveforms such as the PFC output ripple, output current, and voltage ripple waveforms at various input line voltages.

#### 3.2.2.4.1 PFC Output Ripple

 


图 28. PFC Output Ripple at 120-V AC With 196-W LED Load

 


图 29. PFC Output Ripple at 120-V AC With 196-W LED Load

#### 3.2.2.4.2 Output Voltage and Current Ripple

 


图 30. Output Voltage and Current Ripple With 196-W LED Load at 120-V AC

 


图 31. Output Voltage and Current Ripple With 196-W LED Load at 230-V AC

 


图 32. Output Voltage and Current Ripple With 196-W LED Load at 265-V AC

### 3.2.2.5 Transient Waveforms

This section presents transient waveforms such as start-up and turnoff waveforms at various input line voltages.

#### 3.2.2.5.1 Start-up Waveforms at No Load and Full Load

 


图 33. Start-up at 120-V AC With No Load at Output

 


图 34. Start-up at 120-V AC With 196-W LED Load at Output

 


图 35. Start-up at 230-V AC With No Load at Output

 


图 36. Start-up at 230-V AC With 196-W LED Load at Output

 


图 37. Start-up at 265-V AC With No Load at Output

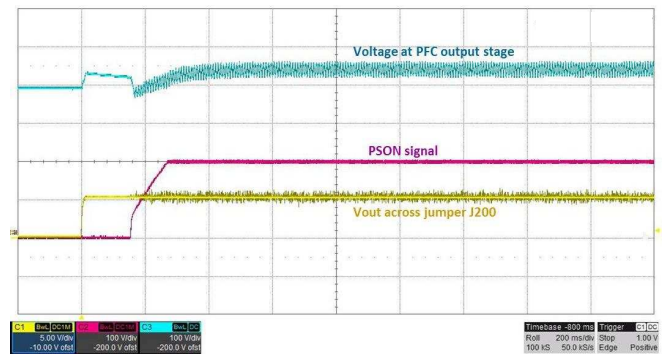


图 38. Start-up at 265-V AC With 196-W LED Load at Output

3.2.2.5.2 Turnoff Waveforms

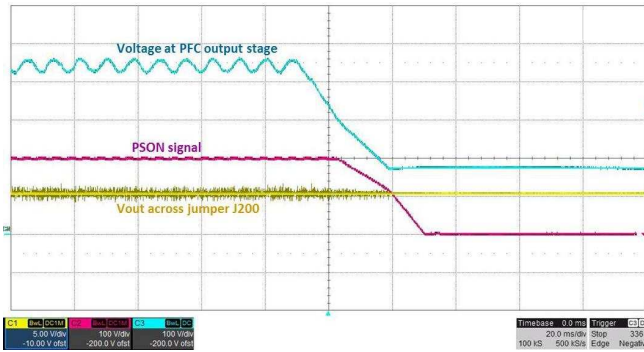


图 39. Turnoff at 120-V AC With 196-W LED Load at Output

 


图 40. Turnoff at 230-V AC With 196-W LED Load at Output

 


图 41. Turnoff at 265-V AC With 196-W LED Load at Output



3.2.2.6 Thermal Images at Full Load

 


图 42. Thermal Image of Top View of TIDA-01464 PCB With 196-W Load at 230-V Input AC Voltage

表 16. Max Temperature for PCB Components Highlighted in 图 42

MAX TEMPERATURE (°C)	DEVICE NAME
74.5	NTC at the input (RT100)
48.6	Bridge rectifier, PFC MOSFET, and diode (D102, Q100, and D100)
33.4	PFC inductor
38.9	Two-switch flyback MOSFETs
39.9	Flyback transformer
46.5	Secondary-side rectifier diode



 


图 43. Thermal Image of Bottom View of TIDA-01464 PCB With 196-W Load at 230-V Input AC Voltage

表 17. Max Temperature for PCB Components Highlighted in 图 43

MAX TEMPERATURE (°C)	DEVICE NAME
45.7	RT100 bottom
51.1	D102 bottom
44.3	UCC28180
38.9	UCC28740
35.9	LM358
55.7	Q207

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-01464](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01464](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01464](#).

### 4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01464](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01464](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01464](#).

### 4.7 Design Calculator Spreadsheet

To download the design calculator spreadsheet for PFC stage, see the design files at [TIDA-01464](#).

## 5 Related Documentation

1. Texas Instruments, [Improving the Performance of Traditional Flyback Topology With Two-Switch –Approach Application Report](#)

### 5.1 商标

E2E is a trademark of Texas Instruments.

All other trademarks are the property of their respective owners.

## 6 About the Authors

**SEETHARAMAN DEVENDRAN** is a systems architect at Texas Instruments, where he is responsible for developing reference design solutions for the industrial segment. Seetharaman brings to this role his extensive experience in analog and mixed signal system-level design expertise. Seetharaman earned his bachelor's degree in electrical engineering (BE, EEE) from Thiagarajar College of Engineering, Madurai, India

**SHENG-YANG YU** is an application engineer at Texas Instruments where he is responsible for developing power supply reference design solutions for strategic customers. Sheng-Yang earned his PhD degree from The University of Texas at Austin.

**SURYA MISHRA** is a systems designer at Texas Instruments, where he is responsible for developing reference design solutions for the Lighting, Industrial Segment. Surya earned his bachelor of electronics and communication engineering from the Motilal Nehru National Institute of Technology (MNNIT), Allahabad.

## 有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。您就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等产权包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默认的保证或陈述，包括但不限于对准确性或完整性、产权保证、无复发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、[评估模块](http://www.ti.com/sc/docs/sampters.htm)和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2017 德州仪器半导体技术（上海）有限公司