

TI Designs: TIDA-01527

带有 C2000™ 微控制器且精度为 $\pm 0.1^\circ$ 的分立式旋转变压器前端参考设计



说明

该参考设计是适用于旋转变压器传感器的励磁放大器和模拟前端。该设计在尺寸大小仅为 1 平方英寸的印刷电路板 (PCB) 上实施分立式组件和标准运算放大器。提供的算法和代码示例使用了 C2000™ 微控制器 (MCU) LaunchPad™ 开发套件, 通过 TMS320F28069M MCU 来进行信号处理和角度计算。该参考设计使用了创新的散射信号处理方法 (参见 3 节)。该方法将系统精度提高了 250%, 同时还将硬件成本和复杂性保持在合理水平。

TIDA-01527 是 TIDA-00796 和 TIDA-00363 参考设计的低成本配套设计。这些设计均基于 PGA411-Q1 且能够提供先进的特性, 例如保护和诊断特性。

资源

TIDA-01527	设计文件夹
TLV4171	产品文件夹
TLV431B-Q1	产品文件夹
TMS320F28069M	产品文件夹

特性



- 在 1 平方英寸的四层 PCB 上进行极简的部署
- 行业标准化组件
- 低成本
- TMS320F28069M C2000™ MCU 的示例固件包含源代码
- 通过欠采样算法来计算角度
- 支持性能升级
- $\pm 0.25^\circ$ 的角度读取精度, 使用创新的散射信号处理方法时精度为 $\pm 0.1^\circ$

应用

- 交流驱动器位置反馈
- HEV/EV - 逆变器和电机控制
- 电动自行车
- 伺服驱动器位置反馈



咨询我们的 E2E 专家

 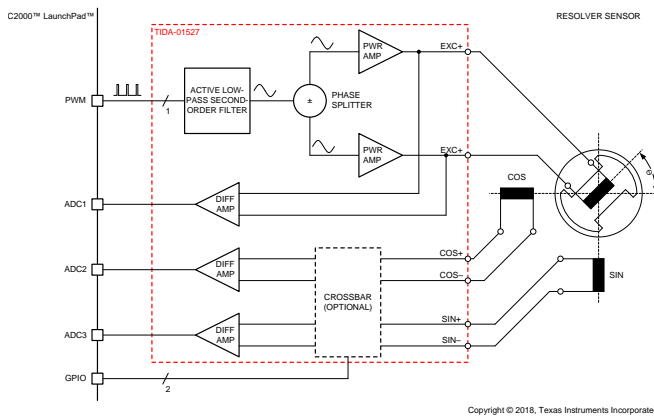

该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Description

High-performance motor control applications traditionally require a speed or position sensor for the control loop feedback. Various methods and new algorithms are available which may eliminate the requirement for a physical sensor; however, many applications cannot achieve the required performance and reliability through sensorless control. Examples include traction inverters for hybrid-electric vehicles (HEV) and electric vehicles (EV), electric power steering, motor drives and servos in industrial applications. A resolver is one of the most popular angular sensors due to its reliability (even in an harsh environment) and the ratiometric output, which suppresses common-mode noise.

This discrete resolver front-end reference design provides a simple implementation of a resolver interface. The design uses a small PCB which implements an excitation amplifier for the primary winding and the analog signal front end for the feedback windings. The PCB connects to the [C2000 LaunchPad with the TMS320F28069M MCU](#) over a flat ribbon cable or by using a small PCB adapter. The provided code example for the MCU uses the undersampling algorithm for readback signals demodulation and the arc tangent goniometric function for the angle calculation.

Components used in this design have been rated for automotive applications or have an automotive-qualified alternative. The guide also suggests more customized components with higher integration for performance upgrade.

注: The TIDA-01527 reference design has not been tested for any automotive or industrial requirements (for example, functional safety or electromagnetic compatibility). The design serves as a practical guidance and inspiration for the customer's system implementation.

1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Resolver excitation voltage	Typically 4 V _{RMS} or 7 V _{RMS}
Input voltage	12 V to 15 V
Resolver excitation frequency	Scalable, optimized for 5 kHz
PCB dimensions	25.4 mm × 25.4 mm
Output signal levels	0 V to 2.54 V
Supported excitation current	< 80 mA, upgrade possible
Protection mechanisms (e.g. current, voltage, temperature, electrostatic discharge (ESD))	None
Excitation amplifier modulation	Sine-wave-modulated pulse width modulation (PWM), fixed frequency $f = 312.5$ kHz, variable duty cycle
Accuracy	$\pm 0.25^\circ$ angle readout accuracy or $\pm 0.1^\circ$ using the innovative scattering signal processing method (see Test Results)
Resolution	12 b

2 System Overview

The TIDA-01527 reference design consists of a host MCU and resolver sensor. The host MCU generates a pulse-width modulated (PWM) signal with a variable duty cycle. The duty-cycle modulation matches the desired resolver excitation frequency. The second-order active low-pass filter only preserves the excitation frequency and converts the PWM signal into a harmonic signal. The analog phase-splitter circuit splits the harmonic signal into two complementary harmonic signals. Two power amplifiers boost these harmonic signals to match the resolver excitation voltage levels. A set of difference amplifiers monitor all resolver windings and interface to the analog-to-digital converter (ADC) in the host MCU. The system uses an optional analog crossbar circuit for advanced analog processing techniques, system calibration, and basic diagnostics. For details on the scattered signal processing method, see 3 节.

图 1 shows the reference design from the top and the bottom side.


 


图 1. TIDA-01527 Board (Top and Bottom)

2.1 Block Diagram

图 2 shows a block diagram of the TIDA-01527 reference design, host MCU, and resolver sensor.

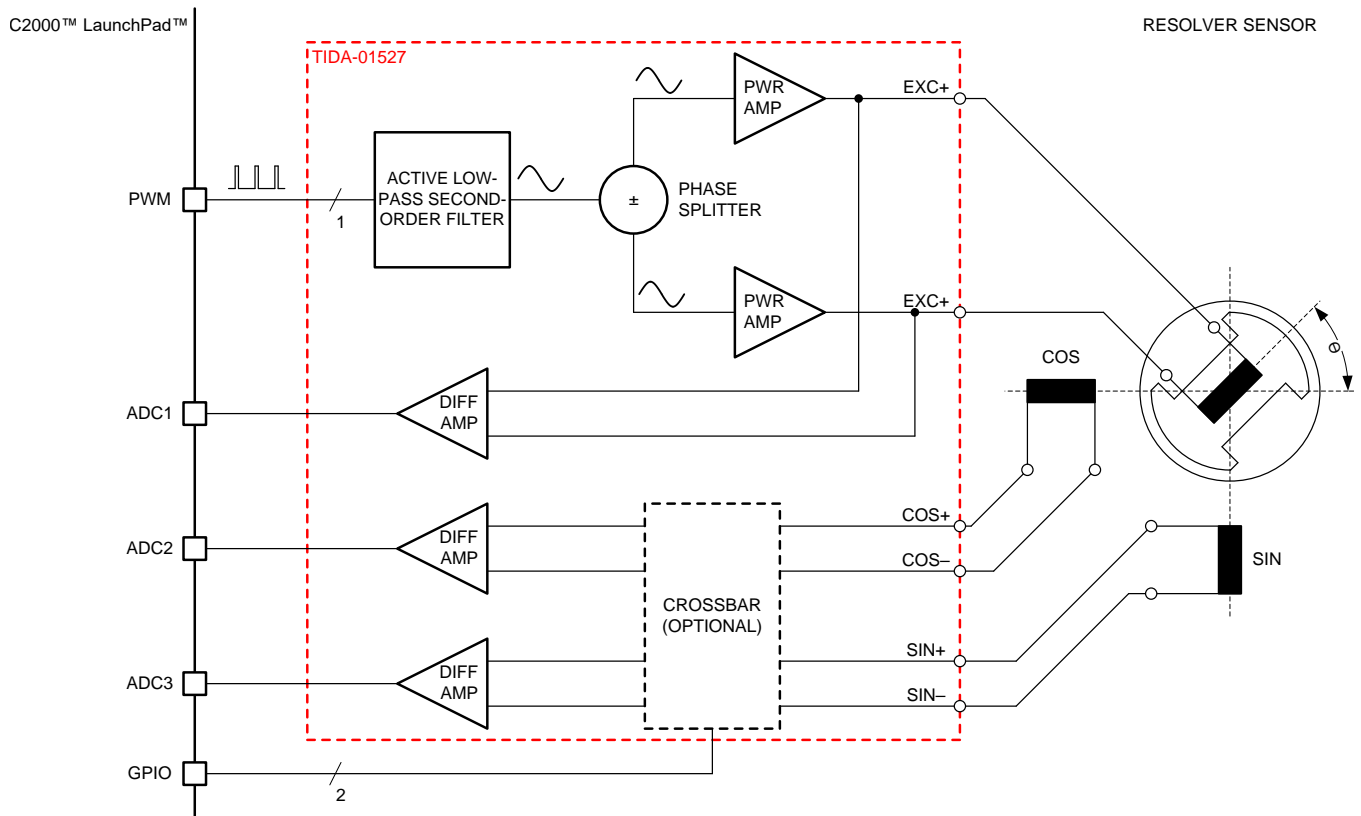

Copyright © 2018, Texas Instruments Incorporated

图 2. TIDA-01527 Block Diagram

2.2 Highlighted Products

2.2.1 TLV4171

The TLVx171 family of devices is a 36-V, single-supply, low-noise operational amplifier (op amp) with the ability to operate on supplies ranging from 2.7 V (± 1.35 V) to 36 V (± 18 V). This series is available in multiple packages and offers low offset, drift, and low quiescent current. The single, dual, and quad versions all have identical specifications for maximum design flexibility.

Unlike most op amps, which are specified at only one supply voltage, the TLVx171 family of devices is specified from 2.7 V to 36 V. Input signals beyond the supply rails do not cause phase reversal.

The TLVx171 family of devices is stable with capacitive loads up to 200 pF. The input can operate 100 mV below the negative rail and within 2 V of the top rail during normal operation. The device can operate with full rail-to-rail input 100 mV beyond the top rail, but with reduced performance within 2 V of the top rail.

The TLVx171 op amp family is specified from -40°C to $+125^{\circ}\text{C}$.

2.2.2 TLV431x-Q1

The TLV431x-Q1 device is a low-voltage three-terminal adjustable voltage reference with specified thermal stability over applicable industrial, automotive, and commercial temperature ranges. The output voltage can be set to 1.24 V on stand-alone mode or any value between V_{REF} (1.24 V) and 6 V with two external resistors. These devices operate from a lower voltage (1.24 V) than the widely-used TL431 and TL1431 shunt-regulator references. When used with an optocoupler, the TLV431 device is an ideal voltage reference in isolated feedback circuits for 3-V to 3.3-V switching-mode power supplies. These devices have a typical output impedance of 0.25 Ω . Active output circuitry provides a very-sharp turnon characteristic, making them excellent replacements for low-voltage Zener diodes in many applications, including onboard regulation and adjustable power supplies.

2.2.3 C2000™ TMS320F28069M MCU

The F2806x Piccolo™ family of microcontrollers (MCUs) provides the power of the C28x core and control law accelerator (CLA) coupled with highly-integrated control peripherals in low pin-count devices. This family is code-compatible with previous C28x-based code, and also provides a high level of analog integration.

An internal voltage regulator allows for single-rail operation. Enhancements have been made to the high-resolution pulse width modulator (HRPWM) module to allow for dual-edge control (frequency modulation). Analog comparators with internal 10-bit references have been added and can be routed directly to control the ePWM outputs. The ADC converts from a 0- to 3.3-V fixed full-scale range and supports ratio-metric V_{REFHI}/V_{REFLO} references. The ADC interface has been optimized for low overhead and latency.

2.3 System Design Theory

The following chapters describe the system design in the order which corresponds to the signal flow.

- *PWM Generation* (C2000, software)
- *Active Low-Pass Second-Order Filter and Phase Splitter* (hardware)
- *Power (Excitation) Amplifiers* (hardware)
- *Resolver Sensor* (hardware)
- *Crossbar—Optional* (hardware)
- *Analog Front-End Difference Amplifiers* (hardware)
- *A/D Conversion and Signal Processing* (C2000, software)

2.3.1 PWM Generation

The C2000 MCU generates a PWM signal with a fixed frequency and variable duty cycle. The PWM period is significantly higher than the period of the resolver excitation signal. 图 3 shows the PWM stream (not in scale).

 


图 3. PWM Generation From MCU

Every new period of the PWM triggers an interrupt service routine where the controller calculates a new duty cycle using the sinus function. The period of the PWM modulator is set as per 公式 1.

$$T_{\text{PWM}} = 2^n \times T_{\text{SYSCLK}} \quad (1)$$

This method allows conversion of the excitation signal into a discrete time signal with an n -bit resolution. An internal variable-counter counts every interrupt from 0 to $2^n - 1$ and automatically resets when it reaches 2^n . The software example uses the IQ math library. After casting the internal variable-counter to IQ n number, the result takes the value between 0..1, which corresponds to 0.. 2π angle on the unity circle. For this reason, the internal variable-counter is called the excitation angle, or *ExcAngle*. This variable is very important because all signal processing refers to it.

The designer can also adjust the PWM duty-cycle modulation index (depth). Typically, the modulation index is 1.0, which corresponds to a duty cycle from 0% to 100%. When set to 0.5, the duty cycle varies from 25% to 75%. This variation reduces the output amplitude of the excitation signal. For this reason, the modulation index variable is called *ExcGain* and may be used to fine-tune the output amplitude. Note that lowering the modulation index reduces the effective resolution and increases harmonic distortion of the excitation signal.

Another important aspect to understand is that the required bit-resolution n and the system clock period T_{SYSCLK} define the period T_{PWM} of the generated PWM signal, as per 公式 2. A lower resolution increases the total harmonic distortion (THD) while a lower operating frequency requires a higher-order low-pass filter.

$$T_{\text{PWM}} = \frac{T_{\text{EXC}}}{2^n} \quad (2)$$

Finally, the MCU sets the duty cycle, as per 公式 3:

$$\text{duty} = 0.5 \times \left[1 + \left(\sin(\text{ExcAngle}) \times \text{ExcGain} \right) \right] \quad (3)$$

where,

- duty = 0...1,
- ExcAngle = 0... 2π ,
- ExcGain = 0...1.

Adding 1 ensures that the duty cycle is always positive with the center at 0.5.

Example calculation for TIDA-01527:

Desired excitation frequency $f_{\text{EXC}} = 5 \text{ kHz} \rightarrow T_{\text{EXC}} = 200 \mu\text{s}$

System clock $f_{\text{SYSCLK}} = 80 \text{ MHz} \rightarrow T_{\text{SYSCLK}} = 12.5 \text{ ns}$

Choosing PWM resolution = 8 b

PWM period as per 公式 4:


$$T_{\text{PWM}} = 2^8 \times 12.5 \text{ ns} = 3.2 \mu\text{s} \quad (4)$$

The excitation angle variable resolution per 公式 1 then turns into 公式 5

$$T_{\text{PWM}} = \frac{T_{\text{EXC}}}{2^n} \rightarrow n = \frac{\log\left(\frac{T_{\text{EXC}}}{T_{\text{PWM}}}\right)}{\log 2} = \frac{\log\left(\frac{200\text{e} - 6}{3.2\text{e} - 6}\right)}{\log 2} = 5.96 \Rightarrow 6 \text{ bit} \quad (5)$$

2.3.2 Active Low-Pass Second-Order Filter and Phase Splitter


图 4 shows a simplified magnitude spectrum of the generated PWM signal described in 节 2.3.1.

 

Note: X-axis is not in scale

图 4. Magnitude Spectrum of Generated PWM Signal

A properly-set low-pass filter suppresses the PWM carrier and harmonics to a minimum but passes the resolver excitation signal content, as 图 5 shows. This process converts the modulated PWM stream to a sine wave. Note that increasing the difference between f_{EXC} and f_{PWM} lowers the requirement for filter rolloff (filter order). Setting the DC gain and the rolloff point is worth the practical experiment. The DC gain compensates for the excitation frequency attenuation and different combinations provide different results. Matching the -3 -dB cutoff to the excitation frequency is the starting point when designing the filter.

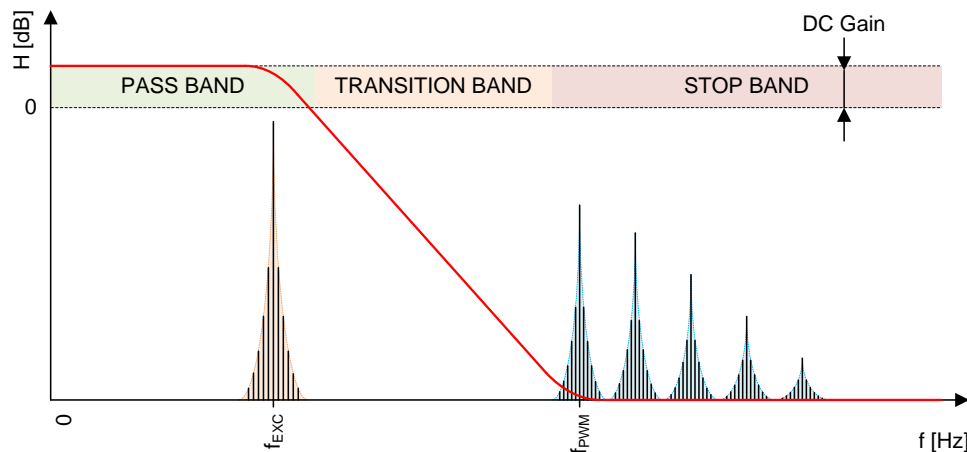

Note: X-axis is not in scale

图 5. Suggested Low-Pass Filter Response for PWM Signal Filtering

The reference design uses a second-order low-pass active filter with a multiple feedback topology, as 图 6 shows.

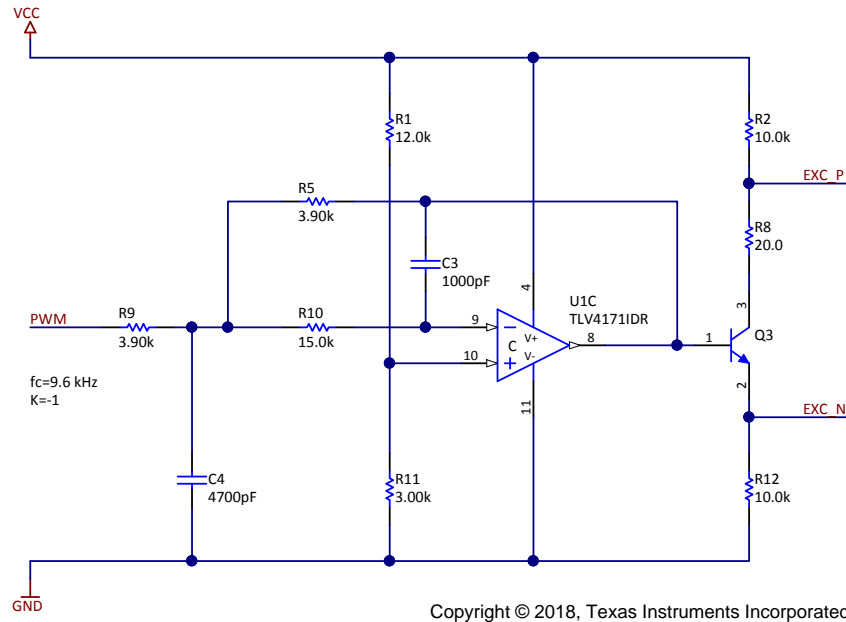


图 6. Multiple-Feedback Filter (MFB) in TIDA-01527

During development, this topology was proven to be a better solution rather than the popular Sallen-Key topology. Another benefit is that the resistor divider (R1, R11), which sets the DC offset, connects to the high-impedance non-inverting input of the op amp. The Sallen-Key filter requires buffering for floating ground (DC offset), which adds to the circuit complexity. R5 and R9 set the DC gain of the filter as per 公式 6.

$$A_{DC} = -\frac{R5}{R9} = -\frac{3900}{3900} = -1 \tag{6}$$

公式 7 calculates the -6-dB cutoff frequency of the filter.

$$f_{c-6\text{ dB}} = \frac{1}{2\pi\sqrt{R5 \times R10 \times C4 \times C3}}$$

$$f_{c-6\text{ dB}} = \frac{1}{2\pi\sqrt{3900 \times 15000 \times 4.7 \times 10^{-9} \times 1 \times 10^{-9}}}$$

$$f_{c-6\text{ dB}} = 9589 \text{ Hz} \tag{7}$$

公式 8 calculates the more-common approximation of a -3-dB cutoff from the -6-dB point.

$$f_{c-3\text{ dB}} = f_{c-6\text{ dB}} \sqrt{2^{\left(\frac{1}{n}\right)} - 1} = 9589 \sqrt{2^{\left(\frac{1}{2}\right)} - 1} = 6171 \text{ Hz} \tag{8}$$

注: The cutoff frequency is typically identified as the point where the transfer function of a filter drops by -3 dB. This drop corresponds to approximately half of the power transfer. However, higher-order filters have a steeper rolloff (for example: -40 dB/dek for a second-order filter) and the cutoff frequency is defined as $n(-3\text{ dB})$ where n is the filter order. This definition often causes confusion because some technical articles or [online calculators](#) use formulas referring to the -3-dB point whereas others use $n(-3\text{ dB})$. TI recommends checking the calculation using a simulation tool.

As 节 2.3.4 describes, a resolver is a transformer. Eliminating any DC current through the primary winding is important to avoid magnetic circuit saturation. For this reason, the system uses differential excitation with two output amplifiers with a phase shift of 180°. The resolver then registers only the differential voltage V_R as per 公式 9:

$$V_R = (V_{EXC+} + V_{DC}) - (V_{EXC-} + V_{DC}) \tag{9}$$

where,

$$V_{EXC+} = -V_{EXC-} \tag{10}$$

and then,

$$V_R = 2 \times V_{EXC} \tag{11}$$

A simple analog phase splitter using the transistor Q3 and resistors (R2, R12) creates well-matched complementary sine waves, as per 公式 10. The resistor R8 compensates for the intrinsic emitter resistance of Q3. This compensation helps to roughly match output impedances between the collector and emitter node.

2.3.3 Power (Excitation) Amplifiers

A pair of excitation amplifiers directly drive the primary winding of the resolver sensor. Both amplifiers are identical, so this documentation only describes the first one. The amplifier is practically a single-supply audio amplifier with a band-pass filter response. 图 7 shows the circuit diagram.

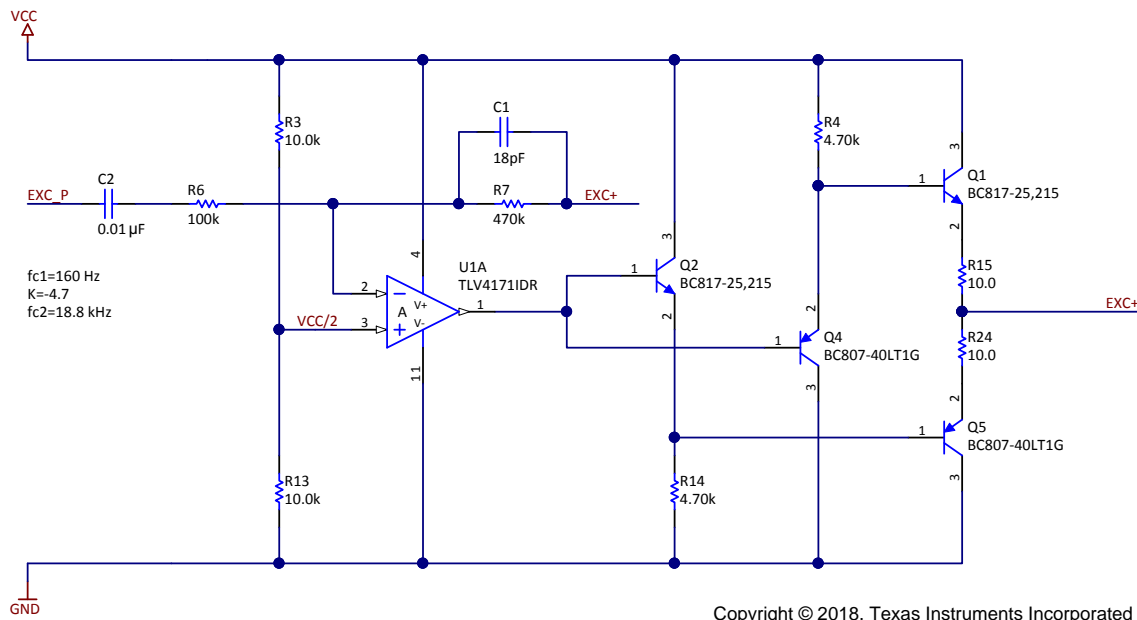


图 7. TIDA-01527 Excitation Amplifier—Single Channel

Resistors R3 and R13 create a virtual ground and set the DC offset to the middle of the operating voltage range. Resistors R6 and R7 set the pass-band gain as per 公式 12 . Note that keeping these resistors reasonably high is important because R6 also defines the input impedance of the power stage.

$$A_{PASS-BAND} = -\frac{R7}{R6} = -\frac{470e3}{100e3} = -4.7 \tag{12}$$

The power stage is AC-coupled because the virtual ground (DC offset) of the power stage does not match the EXC_P, EXC_N outputs of the phase splitter. The capacitor C2 and resistor R6 set the lower cutoff frequency as per 公式 13. The cutoff frequency is set significantly lower than the excitation frequency to prevent signal of interest attenuation.

$$f_{\text{low-3 dB}} = \frac{1}{2\pi \times R6 \times C2} = \frac{1}{2\pi \times 100\text{e}3 \times 10\text{e-}9} = 159.2 \text{ Hz} \quad (13)$$

公式 14 defines the upper cutoff frequency of the amplifier. Similar to the low-pass filter in 节 2.3.2, the designer must set the cutoff frequency as low as possible to further reduce the PWM spectral content but high enough to pass the excitation frequency without attenuation.

$$f_{\text{high-3dB}} = \frac{1}{2\pi \times C1 \times R7}$$

$$f_{\text{high-3dB}} = \frac{1}{2\pi \times 18\text{e-}12 \times 470\text{e}3}$$

$$f_{\text{high-3dB}} = 18.81 \text{ kHz} \quad (14)$$

Texas Instruments offers integrated power amplifiers that fit this application. An integrated solution solves many problems, such as:

- Output stage biasing
- Crossover distortion
- Overcurrent protection
- Temperature protection
- Temperature (runaway) stability

Adding these features by using discrete components usually results in very complex circuits which are typically known for their use in high-end audio amplifiers.

Recommended parts: ALM2402, OPA564-Q1

Verifying the minimal slew rate for the excitation amplifier is also very important. 公式 15 defines the minimal slew-rate SR.

$$SR_{\text{min}} \geq f_{\text{EXC}} \times 2\pi \times V_{\text{amp}} \quad (15)$$

where,

- V_{amp} is the amplitude (single-ended) of the generated sine wave.

图 8 shows the relationship between excitation frequency, resolver excitation voltage, and the amplifier slew rate for applications using the differential type of an excitation amplifier.


 


图 8. Minimum Required Slew Rate per Amplifier (Single-Ended) for 4-V_{RMS} and 7-V_{RMS} Resolvers

 2.3.4 Resolver Sensor

A resolver uses the principle of a rotating transformer with a single primary winding and two secondary windings positioned in a right angle from each other (see 图 9). The generated sine wave V_R excites the primary winding and creates the magnetic flux Φ , which is distributed through secondary windings with respect to the rotor angle Θ . 公式 16 then calculates the rotor angle Θ from the ratio of voltages V_S , V_C on the secondary windings.



Copyright © 2017, Texas Instruments Incorporated

图 9. Resolver as Rotating Transformer

$$V_S = \sin\theta \times V_R \times TS$$

$$V_C = \cos\theta \times V_R \times TS$$

$$\frac{\sin\theta \times V_R \times TS}{\cos\theta \times V_R \times TS} = \frac{\sin\theta}{\cos\theta} = \frac{V_S}{V_C}$$

$$\tan \Theta = \frac{V_S}{V_C} \rightarrow \Theta = \arctan \frac{V_S}{V_C} \quad (16)$$

Understanding the spectral content of a resolver sensor is important. The signal that each resolver winding produces is amplitude modulated with a modulation index of $m = 2$ (overmodulation). When a resolver is steady and at a fixed angle (highlighted by the green color in [图 10](#)), then the output spectrum only has a single spectral line at the excitation frequency f_{EXC} , unless the output signal has zero amplitude (every 180°). When a resolver spins with angular frequency $f_{VELOCITY}$ (highlighted by red color in [图 10](#)), then the effect of overmodulation ($m = 2$) completely suppresses the carrier (excitation) frequency f_{EXC} . This effect is important to consider when designing a signal processing algorithm.


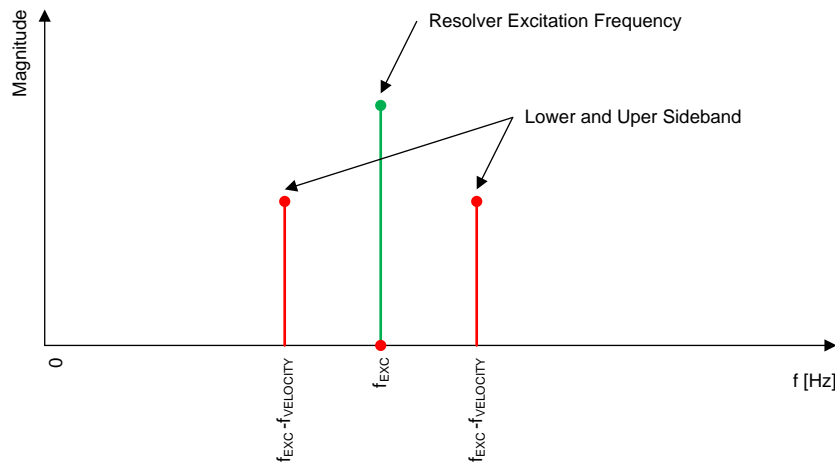


图 10. Magnitude Spectrum of Resolver Sensor Output Signal

For further details on resolvers, see [EMC Compliant Single-Chip Resolver-to-Digital Converter \(RDC\) Reference Design](#) or [Synchro and Resolver Engineering Handbook](#).

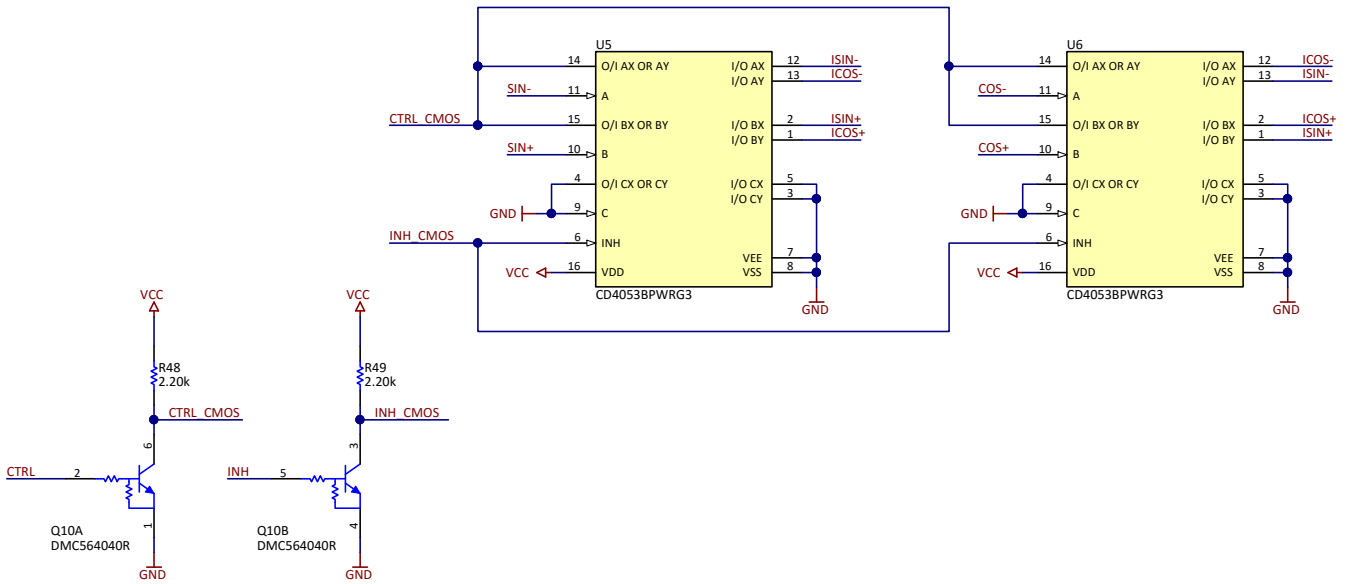2.3.5 Crossbar—Optional

A pair of CMOS multiplexers (U5, U6) form an analog crossbar, as [图 11](#) shows. This crossbar is an experimental circuitry further used in the signal processing algorithm. This circuit also allows for swapping input signals between each difference amplifier or the complete disconnection of resolver windings. This circuitry, together with an advanced algorithm in the MCU, reduces system error and enables basic diagnostics features. Transistors Q10A, Q10B and resistors R48, R48 convert logic levels from the MCU.



Copyright © 2018, Texas Instruments Incorporated

图 11. Analog Crossbar (Experimental)

2.3.6 Analog Front-End Difference Amplifiers

The system uses three difference amplifiers for the feedback.

图 12 shows the first amplifier, which monitors the excitation outputs. Monitoring the excitation amplifier is extremely useful because a diagnostic routine in the MCU can compensate the tolerances of parts and precisely adjust the output voltage using the *ExcGain* variable. Additionally, this monitoring enables the system to measure the phase lag of the active filter and excitation amplifier or detect a faulty excitation amplifier. Set the DC gain of the difference amplifier per 公式 17.

$$A = \frac{R19}{R20} = \frac{10k}{100k} = 0.1 \text{ when } R19 = R23 \text{ and } R20 = R22 \quad (17)$$

The resistor R21 and capacitor C7 form a charge bucket filter for the ADC. The difference amplifier uses the DC offset (VREF1/2) to match the bidirectional signal from the resolver with the single-ended ADC input.


 


图 12. Excitation Amplifier Output Monitoring

 The other two difference amplifiers monitor the sinus and cosinus windings from the resolver sensor. Because both amplifiers are identical, this documentation only describes the first one (see 图 13).



Copyright © 2018, Texas Instruments Incorporated

图 13. Resolver Feedback Winding Monitoring

Set the DC gain of the difference amplifier per 公式 18. The resistor R32 and capacitor C15 form a charge bucket filter for the ADC. The difference amplifier uses the DC offset (VREF1/2) to match the bidirectional signal from the resolver with the single-ended ADC input.

$$A = \frac{R28}{R29} = \frac{10k}{51k} = 0.196 \text{ when } R28 = R35 \text{ and } R29 = R33 \tag{18}$$

The signal from the resolver secondary winding is floating. Resistors R26, R31, and R36 provide the appropriate DC biasing. Keeping the inputs of the op amps within the specified common mode range is important. C12 is an optional filtering capacitor (do not assemble). The 0-Ω resistors R30, R34 must be populated when the analog crossbar circuitry is not in use.

Two inexpensive voltage references U2, U4 create a 1.24 V and 2.48 V for the ADC. Resistor R27 provides biasing and capacitors C13, C14 provide basic filtering.

注: Always check the stability boundary conditions and minimal bias current for the x431 series of shunt references. The criteria is subject to change between manufacturers.

Texas Instruments recommends the use of integrated difference amplifiers such as the INA1650-Q1 as a potential performance upgrade. An integrated multichannel solution provides better channel matching and precise gain setting without the requirement of expensive precision resistors.

2.3.7 A/D Conversion and Signal Processing

The system uses the undersampling method for demodulating the signals from the resolver sensor. This technique is one of the simplest, yet very effective. An example of another method is to use a digital envelope detector and various digital filters. Such a solution is also effective, especially in a noisy environment; however, every filter causes phase lag and a delay in the system, which is often undesirable in high-performance feedback control loops.

图 14 shows the typical waveforms of a resolver spinning at angular speed as per 公式 19.

$$\omega = \frac{2 \times \pi}{T_{\text{VELOCITY}}} \tag{19}$$

 


图 14. Typical Resolver Waveforms

The physical placement of the secondary windings defines the phase shift between the sine and cosine signal, which is ideally 90°.

Sampling V_S and V_C with period $T_{\text{SAMPL}} = T_{\text{EXC}}$ demodulates the signal and preserves only the signal envelope that is required for angle calculation, as per the previous 公式 16. The ADC converter is set in such a way that it always samples the signal when the amplitude reaches the maximum. This setting increases the signal-to-noise ratio and delivers the best results. The ADC sampling time derives from the *ExcAngle* parameter described in 节 2.3.1. For this reason, the code uses the name *SamplAngle*. Ideally, the sampling time *SamplAngle* occurs when *ExcAngle* is 0.25, 0.75, or both. However, two sources of phase lag exist for which the system must compensate. The first source of phase lag is on the active low-pass filter and the excitation amplifier. Resolver impedance, which varies with every model, defines the

second source of phase lag. A diagnostic routine, which sweeps the *SamplAngle* variable during the start-up and picks the time point when either V_C or V_S is highest, makes the system compatible with various resolvers with different impedance. The ADC samples both resolver signals ideally at the same time. The MCU offers two independent sample-and-hold circuits which enable this simultaneous sampling. For this reason, V_C and V_S connect to ADCINA0 and ADCINB0, respectively.

3 Scattered Signal Processing Method

A typical resolver system uses a difference amplifier, which interfaces with the ADC for each output (V_S , V_C), as 图 15 shows.

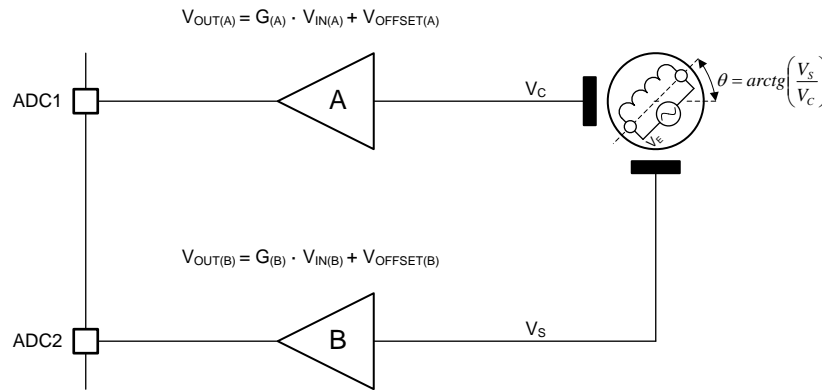


图 15. Typical Resolver-to-Digital Signal Chain

Matching the transfer function of the difference amplifiers is critical for system accuracy. Any difference between the gain or DC offset creates a non-linear error in angle measurement, as per 公式 20.

$$\Theta = \text{arctg}\left(\frac{V_S}{V_C}\right) = \text{arctg}\left(\frac{G_{(B)} \times V_S + V_{\text{OFFSET}(B)}}{G_{(A)} \times V_C + V_{\text{OFFSET}(A)}}\right) \tag{20}$$

The blue trace in 图 16 shows how a 1% gain imbalance between the amplifiers contributes to the angle error. The red trace shows the effect of the DC offset on the angle error when $V_{\text{OFFSET}(A)} = 0.05 \times V_{S(\text{MAX})}$.

 


图 16. Effect of DC Offset and Gain Imbalance on Angle Error

Higher accuracy systems require precision components for the difference amplifiers and system calibration, which increases system and manufacturing costs. This consideration is valid for discrete as well as integrated circuits.

The reference design implements a novel method called *scattered signal processing*. The method uses the analog crossbar described in 节 2.3.5 and a modified algorithm in the firmware.

The scattered signal processing method adds an inexpensive analog multiplexer with an inhibit function (for example, the CD4053) between each resolver output and difference amplifier. This analog multiplexer allows disconnecting the resolver outputs or swapping them between the difference amplifiers on-the-fly when the system is running. Swapping resolver outputs *scatters* the signal between two signal paths, which is the key action of this concept.

The system operates in the following three steps, which repeat periodically:

1. DC offset calibration with disconnected resolver sensor
2. Sampling the output of both differential amplifiers with the normally-connected resolver outputs V_s , V_c (direct mode)
3. Sampling the output of both differential amplifiers with swapped resolver outputs V_s , V_c (inversed mode)

图 17 shows the first step, which is DC offset calibration. The resolver sensor is completely disconnected and the output of each difference amplifier corresponds to the DC offset $V_{\text{OFFSET(A,B)}}$.

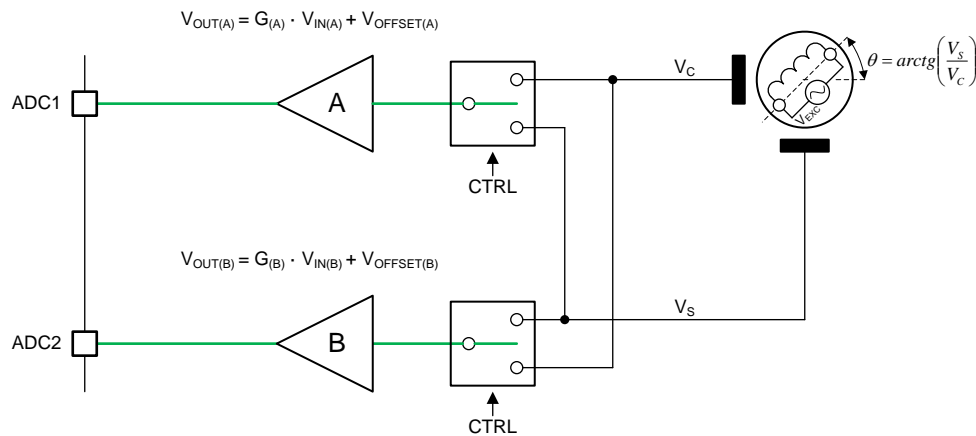


图 17. Scattered Signal Processing Method—Step 1:DC Offset Calibration

In the next step, the ADC samples the output of both differential amplifiers in direct mode (see 图 18).

 


图 18. Scattered Signal Processing Method—Step 2: Direct Mode

In the last step, the ADC samples the output of both differential amplifiers in inversed mode (see 图 19).

 


图 19. Scattered Signal Processing Method—Step 3: Inversed Mode

表 2 lists the values that the ADC reads during all three steps.

表 2. ADC Samples Taken During Steps 1 Through 3

ADC INPUT	STEP 1	STEP 2	STEP 3
ADC1	$V_{\text{OFFSET}(A)}$	$G_{(A)} \times V_C + V_{\text{OFFSET}(A)}$	$G_{(A)} \times V_S + V_{\text{OFFSET}(A)}$
ADC2	$V_{\text{OFFSET}(B)}$	$G_{(B)} \times V_S + V_{\text{OFFSET}(B)}$	$G_{(B)} \times V_C + V_{\text{OFFSET}(B)}$

The angle calculation algorithm uses all three results for gain imbalance and DC offset elimination. First, the algorithm adds the results from step 2 and step 3, as per 公式 21.

$$\Theta = \text{arctg}\left(\frac{V_S}{V_C}\right) = \text{arctg}\left(\frac{G_{(B)} \times V_S + V_{\text{OFFSET}(B)} + G_{(A)} \times V_S + V_{\text{OFFSET}(A)}}{G_{(A)} \times V_C + V_{\text{OFFSET}(A)} + G_{(B)} \times V_C + V_{\text{OFFSET}(B)}}\right) \quad (21)$$

The system obtains the DC offset information for both channels from step 1 and compensates it. This compensation results in the simplified formula as per 公式 22.

$$\Theta = \text{arctg}\left(\frac{V_S}{V_C}\right) = \text{arctg}\left(\frac{G_{(B)} \times V_S + G_{(A)} \times V_S}{G_{(A)} \times V_C + G_{(B)} \times V_C}\right) \quad (22)$$

Mathematical manipulation eliminates the gain variables from the formula as per 公式 23.

$$\Theta = \text{arctg}\left(\frac{V_S}{V_C}\right) = \text{arctg}\left(\frac{V_S \times (G_{(B)} + G_{(A)})}{V_C \times (G_{(A)} + G_{(B)})}\right) \rightarrow \Theta = \text{arctg}\left(\frac{V_S}{V_C}\right) \quad (23)$$

At this point note that the gain imbalance and DC offset no longer contribute to the error calculation. Also note that the method compensates for any imperfections in the ADC transfer function (gain or offset).

注:

- Embedded algorithms typically use Atan2 function which is defined at $\pm\pi$ radians.
- The scattered-signal processing method is effective for signals with a significantly lower bandwidth than the ADC sampling and algorithm execution frequency.
- The current firmware implementation only performs step 1 during the system start-up.

The scattered-signal processing technique has additional positive side effects. The system allows for "limp mode" operation due to the redundant signal path and allows for additional diagnostics, the process for which is as follows:

1. The hardware engineer calculates the worst-case tolerances for the DC offset and gain imbalance and parametrizes the system (for example, a 1.5% tolerance span).
2. The algorithm then periodically checks if readout data are within the given tolerance boundaries, typically for:
 - DC offset for both channels
 - Maximum acceptable difference between ADC samples taken in step 2 and step 3
 - V_S and V_C amplitude
3. If one of the diagnostic results fails, the system is able to detect the defective channel and eventually work in the "limp mode" with reduced performance, using only one analog front-end channel. This measure is important and beneficial in robust systems and in safety-critical applications (SIL/ASIL).

4 Hardware, Software, Testing Requirements, and Test Results

4.1 Required Hardware and Software

4.1.1 Hardware

The following hardware is necessary for exploring the TIDA-01507 reference design:

- The TIDA-01527 discrete resolver front-end board
- The [LAUNCHXL-F28069M](#) LaunchPad development board (or similar)
- The adapter board or a custom ribbon cable for interfacing the TIDA-01527 with the LaunchPad
- A resolver sensor matching the system specification
- Laboratory power supply specified at 0 V to 15 V, 0 mA to 200 mA, preferably with current limitation or overcurrent protection
- A computer capable of running Code Composer Studio™ (CCS) software

图 20 shows the reference design pinout and 表 3 lists the connections to the LaunchPad and the pin mapping. To access the quick start guide for the LAUNCHXL-F28069M including a pins overview, see [TMS320F28069M LaunchPad Development Kit Quick Start Guide](#).

 


图 20. TIDA-01527 Pinout

图 21 shows a properly-assembled TIDA-01527 reference design with the LaunchPad adapter and LAUNCHXL-F28069M development board.

 


图 21. LAUNCHXL-F28069M Development Board With TIDA-01527 and LaunchPad™ Adapter

表 3. TMS320F28069M Pin Mapping for TIDA-15027 Reference Design

SIGNAL	DESCRIPTION	TMS320F28069M (LAUNCHXL PIN)
PWM	Sine-modulated PWM	EPWM1A (J4 pin 40)
GND	Common ground	GND (J2 pin 20, J3 pin 22)
VCC	Power supply 12 V to 15 V	Provided externally
OSIN	Sinus difference amplifier output	ADCINA0 (J3 pin 27)
INH	Analog crossbar inhibit	GPIO02 (J4 pin 38)
OCOS	Cosinus difference amplifier output	ADCINB0 (J3 pin 28)
OEXC	Excitation amplifier monitoring output	ADCINA1 (J3 pin 29)
CTRL	Analog crossbar control	GPIO01 (J4 pin 39)
VREF1/2	Voltage reference 1.24 V	(Optional) ADCINB2 (J3 pin 26)
VREF	Voltage reference 2.48 V	(Optional) ADCINA2 (J3 pin 25)

4.1.2 Software

This reference design comes with a complete example software package with a precompiled binary file and source codes. The following software tools were used during development with the LAUNCHXL-F28069M development board.

1. [Code Composer Studio](#) v7 with C2000 compiler TI v16.9.1 LTS
2. [controlSUITE™](#) software (optional) – Provides extensive database of schematics, libraries, code examples, and manuals for C2000-based solutions
3. [C2000Ware](#) (optional) – A lightweight version of the controlSUITE package

Texas Instruments also offers a set of free-of-charge online development tools at dev.ti.com that can be used for programming the MCU or code modifications.

注: For detailed tutorials on how to program, compile, and debug using TI's MCUS, see processors.wiki.ti.com. Alternatively, TI also offers live support within the [E2E™](#) online community.

4.1.3 Quick-Start With TIDA-01527

Software:

1. Install the CCS software and import the TIDA-01527 project files using the *File* → *Import* menu and then select the *CCS Project*.

2. Connect the C2000 LaunchPad to the PC and make sure that the device drivers have been properly installed.
3. Compile the TIDA-01527 code. The compilation process proceeds with no errors or warnings.
4. Run the code using the *Run*→*Debug* menu, then click the *Resume* button. The binary code loads to the MCU. The code then executes, even without the TIDA-01527 connected.
5. Add system variables to the *Expressions* window and activate an automatic refresh. This action enables real-time monitoring and allows for modifications to system variables.

Hardware:

1. Connect the TIDA-01527 board to the LaunchPad using either a flat ribbon cable or the provided adapter board.
2. Connect a resolver to the TIDA-01527 board.
3. Set the laboratory power supply to 14 V with the current limitation set to 100 mA and power the TIDA-01527 board.
4. The light-emitting diode (LED) on the TIDA-01527 board illuminates.
5. Run the software from CCS. Check the resolver waveforms and compare them with the results from [Test Results](#).

4.2 Testing and Results

4.2.1 Test Setup

图 22 shows the test setup used during the TIDA-01527 reference design development. The test bench uses the following:

- Keithley 2230-30-1 multiple-output laboratory power supply
- R&S®RTB2004 (Rohde & Schwarz) or Tektronix TDS5054B oscilloscope
- TIDA-00176 reference design with ROD480-1024 Sin/Cos encoder as the reference encoder
- TIDA-01527 reference design (test subject) with LTN58 (R58CURE151B04-021-07AX) resolver


 



图 22. TIDA-01527 Test Setup Used for Development and Measurements

4.2.2 Test Results

 


D0 – Input PWM from the C2000 MCU; D1, D2 – Control (CTRL) and Inhibit (INH) signals for the analog crossbar; CH1, CH2 – Generated sine wave after the analog phase-splitter (EXC_N, EXC_P); CH3, CH4 – Excitation amplifier outputs (EXC+, EXC–)

图 23. Active Low-Pass Filter and Excitation Amplifier Waveforms

 


D0 – Input PWM from the C2000 MCU; D1, D2 – Control (CTRL) and Inhibit (INH) signals for the analog crossbar;
 CH1 – Exciter voltage monitoring (OEXC), CH2 – Sine-winding voltage monitoring (OSIN), CH3 – Cosine winding
 voltage monitoring (OCOS)

图 24. Analog Front-End Waveforms (Steady Operation)

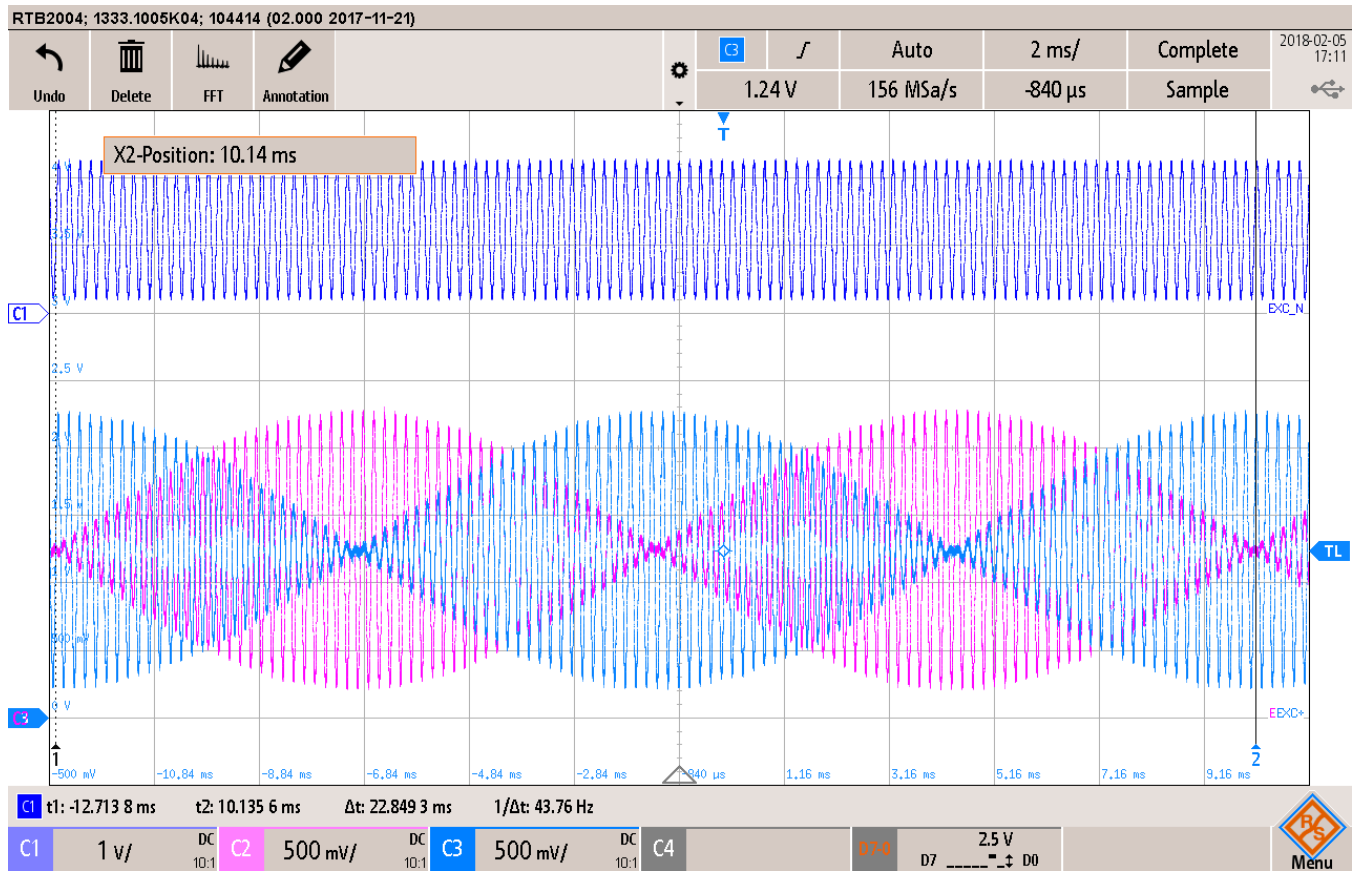


CH1 – Exciter voltage monitoring (OEXC); CH2 – Sine-winding voltage monitoring (OSIN); CH3 – Cosine-winding voltage monitoring (OCOS)

图 25. Analog Front-End Waveforms (Resolver Spins at ≈ 2625 RPM)

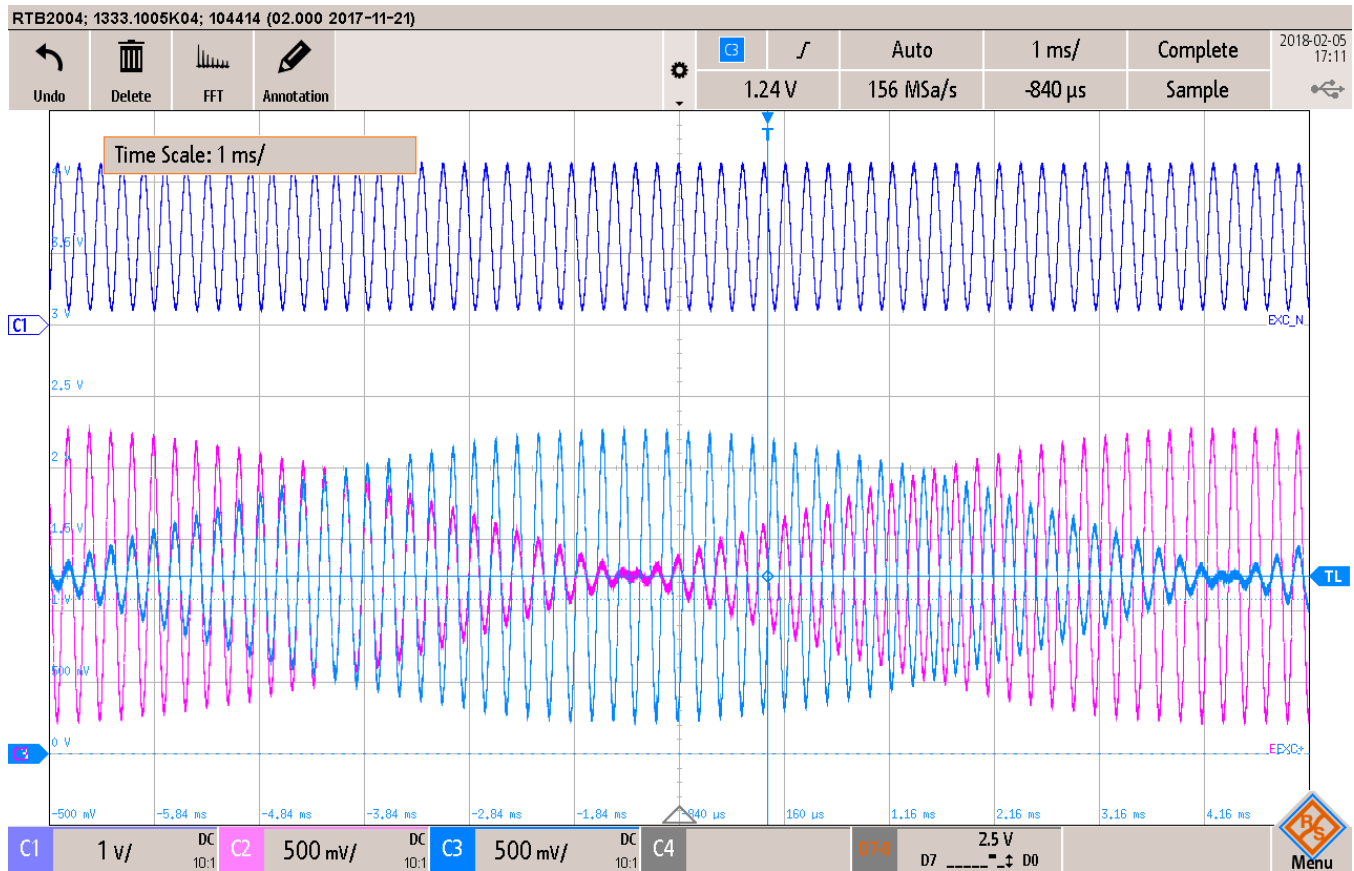

CH1 – Exciter voltage monitoring (OEXC); CH2 – Sine-winding voltage monitoring (OSIN); CH3 – Cosine-winding voltage monitoring (OCOS)

图 26. Analog Front-End Waveforms (Resolver Spins at ≈ 2625 RPM With Detail)

 

D0 – Input PWM from the C2000 MCU; D1, D2 - Control (CTRL) and Inhibit (INH) signals for the analog crossbar; CH1 – Exciter voltage monitoring (OEXC), CH2 – Sine-winding voltage monitoring (OSIN); CH3 – Cosine-winding voltage monitoring (OCOS).

Note that the provided example performs offset calibration (step 1) during the start-up and then alternates only to step 2 and step 3.

图 27. Analog Front-End Waveforms With Scattered Signal Processing Enabled

图 28 显示了诊断例程的结果，该例程在 2.3.7 节中描述，用于找到包络检测器的正确采样时间。GPIO3 引脚上的上升沿表示 OSIN 和 OCOS 采样，而下降沿表示 OEXC 信号的采样。

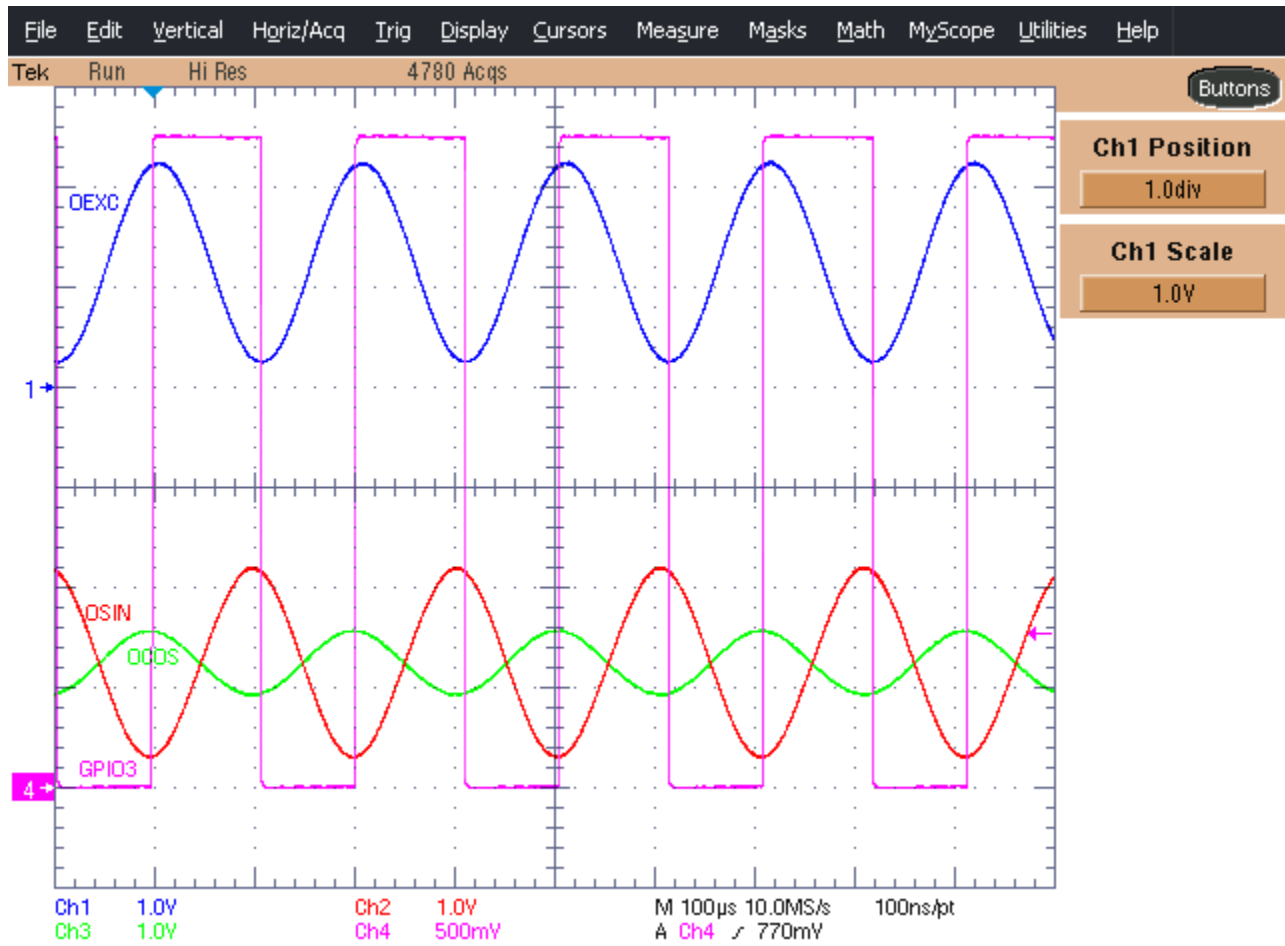


图 28. OSIN、OCOS 和 OEXC 信号的采样时间

图 29 shows the accuracy plot. 图 30 and 图 31 show the same data in a different format.

 


图 29. TIDA-01527 Accuracy Plot

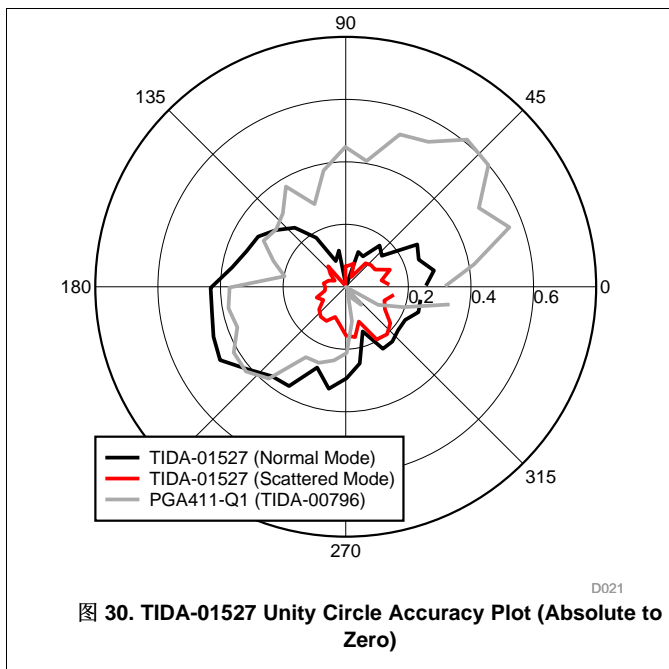


图 30. TIDA-01527 Unity Circle Accuracy Plot (Absolute to Zero)

 


图 31. TIDA-01527 Unity Circle Accuracy Plot

As mentioned in 节 2.3.1, the system uses the IQ math library in the angle calculation routine. The plot in 图 32 shows the calculation error due to the finite Q-number resolution. The reference data use RAW results from the ADC with post processing (calculation) in the PC using Microsoft® Excel. The error is negligible and significantly below the system resolution.

 


图 32. Effect of Fixed Point IQ-Math Library on Error

图 33 shows a photo from the thermal imaging camera when the TIDA-01527 reference design drives the LTN58 resolver at 5 kHz with a 7- V_{RMS} excitation at a 22°C ambient temperature. Not many options are available for reducing the dissipation of an AB-class amplifier other than lowering voltage drop across and current through the power stage.

 


图 33. TIDA-01527 Thermal Imaging Camera Picture

5 Design Files

5.1 Schematics

To download the schematics, see the design files at [TIDA-01527](#).

5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01527](#).

5.3 PCB Layout Recommendations

The design does not require any special PCB layout considerations. The TIDA-01527 uses a four-layer PCB with double-side component placement. The top side (图 34) primarily carries circuitry for the excitation amplifier and voltage references. Signal conditioning amplifiers for the resolver secondary windings and the system connector are located on the bottom side (图 35). The other two internal layers (图 36 and 图 37) carry the power, ground, and signals, too.

 


图 34. Top PCB Side and Components Placement

 


图 35. Bottom PCB Side and Components Placement

 


图 36. Internal Layer 1 With Common Ground GND and Signals

 


图 37. Internal Layer 2 With Power Rail VCC and Signals

5.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01527](#).

5.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01527](#).

5.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01527](#).

5.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01527](#).

6 Software Files

To download the software files, see the design files at [TIDA-01527](#).

7 Related Documentation

1. Texas Instruments, [TLVx171-Q1 36-V, Single-Supply, General-Purpose Operational Amplifier for Cost-Sensitive Automotive Systems Data Sheet](#)
2. Texas Instruments, [TLV431x-Q1 Low-Voltage Adjustable Precision Shunt Regulator Data Sheet](#)
3. Texas Instruments, [TMS320F2806x Piccolo™ Microcontrollers Data Manual](#)
4. Texas Instruments, [Automotive Resolver-to-Digital Converter for Safety Applications Design Guide](#)
5. Texas Instruments, [EMC Compliant Single-Chip Resolver-to-Digital Converter \(RDC\) Reference Design](#)
6. Texas Instruments, [Reduce system costs with resolver-to-digital conversion implementation on C2000™ microcontrollers \(white paper\)](#)
7. Texas Instruments, [TMS320F240 DSP Solution for Obtaining Resolver Angular Position and Speed Application Note](#)
8. Texas Instruments, [C28x IQmath Library Module User's Guide](#)
9. (2004) [Synchro and Resolver Engineering Handbook](#). Moog Components Group. Retrieved from <http://www.moog.com/literature/MCG/synchrohbook.pdf>

7.1 商标

C2000, LaunchPad, Piccolo, Code Composer Studio, controlSUITE, E2E are trademarks of Texas Instruments.

Microsoft is a registered trademark of Microsoft Corporation.

R&S is a registered trademark of Rohde & Schwarz USA, Inc..

All other trademarks are the property of their respective owners.

8 Glossary

ADC— Analog-to-digital converter

CCS— Code Composer Studio™

CLA— Control law accelerator

ESD— Electrostatic discharge

EV— Electric vehicle

HEV— Hybrid-electric vehicle

HRPWM— High-resolution pulse width modulator

LED— Light-emitting diode

MCU— Microcontroller

Op Amp— Operational amplifier

PCB— Printed-circuit board

PWM— Pulse-width modulation

RMS— Root mean square

9 About the Author

JIRI PANACEK is a systems engineer in the Powertrain Automotive Systems team at Texas Instruments where he develops reference designs. Jiri has five years of field experience in the industrial automation and most recently the EV/HEV automotive segment. Jiri earned his master's degree in microelectronics from the Brno University of Technology in the Czech Republic.

有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能而设计。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等许可包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默示的保证或陈述，包括但不限于对准确性或完整性、产权保证、无屡发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、[评估模块](http://www.ti.com/sc/docs/sampters.htm)和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122
Copyright © 2018 德州仪器半导体技术（上海）有限公司