



说明

此参考设计是一种汽车电源解决方案，具备额外的高精度电压监控功能和窗口看门狗，可用于高级驾驶员辅助系统 (ADAS) 中的安全 MCU。这些系统可以控制驾驶功能，例如自动紧急刹车、车道保持辅助和自适应巡航控制。高精度电压探测器会同时监控每条电压轨，监控能力更强，可以帮助客户实现功能性安全目标。此设计不但可以支持高达 5A 的系统电源电流（电压为 3.3V），还能利用汽车电池供电运行、承受电池反向情况，并支持低至 3.5V 输入的启停和冷启动操作。该解决方案中的所有开关频率均固定不变，且都高于 2MHz（不在 AM 无线电频带内）。此参考设计还提供了 CISPR 25 5 类传导发射测试结果。

资源

<a href="#">TIDA-050008</a>	设计文件夹
<a href="#">TPS3703-Q1</a>	产品文件夹
<a href="#">TPS3850-Q1</a>	产品文件夹
<a href="#">TPS3890-Q1</a>	产品文件夹
<a href="#">LM4132-Q1</a>	产品文件夹
<a href="#">TLV1805-Q1</a>	产品文件夹
<a href="#">LM73605-Q1</a>	产品文件夹
<a href="#">TPS62065-Q1</a>	产品文件夹
<a href="#">TPS61240-Q1</a>	产品文件夹
<a href="#">AutoCrankSim-EVM</a>	工具文件夹

特性



- 准确地监控（最大值 1%，-40°C 至 +125°C），可用于监控过压和欠压
- 可编程复位延迟，适用于所有电源轨
- 可编程窗口看门狗计时器，可以与安全 MCU 连接
- 高精度电压基准，可精确地执行 ADC 诊断和监控
- 由汽车电池供电，提供 5V、3.3V 和 1.2V 电源轨
- 5A 集成式 2.2MHz 同步宽输入电压降压直流/直流转换器
- 提供反向电池保护，具有低压降 (~20 mV)
- 3.5V 至 24V 工作范围，支持高达 42V 瞬态电压的宽电池电压范围
- 通过了 CISPR 25 5 类发射测试

应用

- [前置摄像头](#)
- [驾驶员监控系统](#)
- [视镜更换](#)
- [前置远距离雷达](#)
- [ADAS 域控制器](#)



咨询我们的 E2E 专家

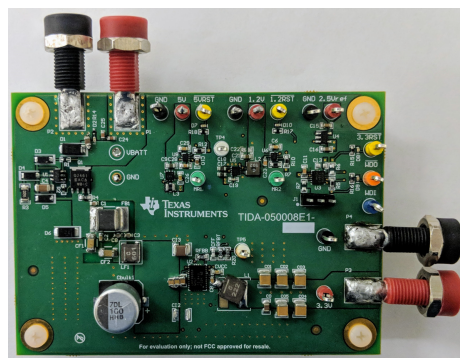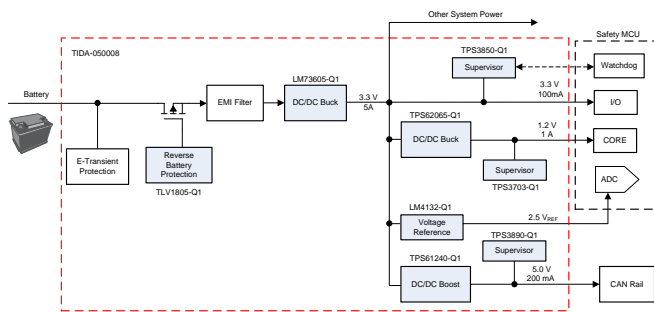



该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

## 1 System Description

ADAS systems process and analyze data from local or remote sensor such as camera, radar, or lidar to either output video or use machine-vision algorithms to perceive the environment in and around the car. For systems that have to achieve higher levels of functional safety (for example systems that control steering or braking functions), an MCU for functional safety applications and precision voltage monitoring of the processor's supply rails (and other critical system rails) may be used. This design focuses on applications up to 15 W.

图 1 显示了一个单前摄像头系统的示例。系统可以根据应用的不同，在传感器的数量和摄像头方面有所差异。

图 1. Example of Mono Front Camera Block Diagram


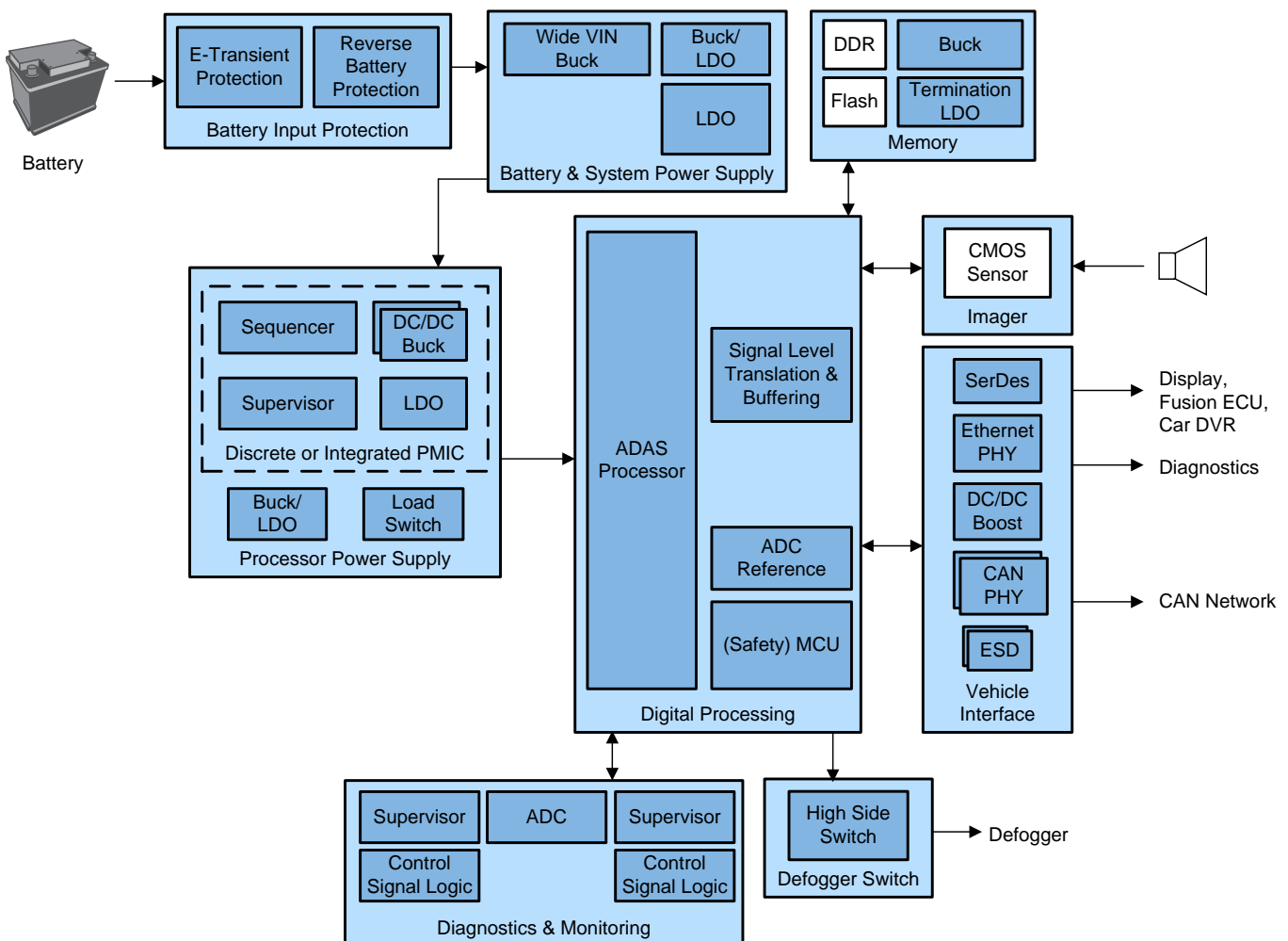


图 2 shows each subsystem and block on the actual TIDA-050008 board. The red blocks are all components located on the TIDA-050008 board and cover the power requirements for a typical safety MCU and CAN PHY. Functionality such as voltage supervision and watchdog timing are done with supervisor ICs. They provide features such as overvoltage and undervoltage monitoring, manual reset, programmable RESET delays, and programmable window watchdog timers.

图 2. TIDA-050008 Subsystems Highlight

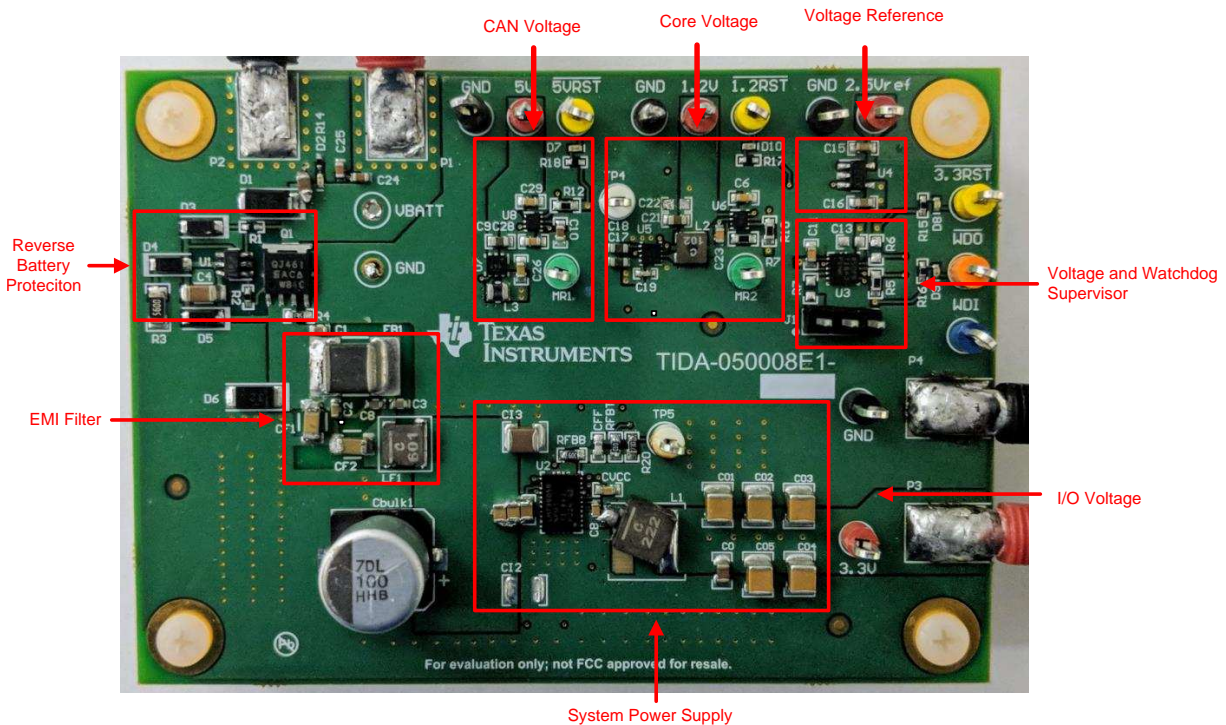

### 1.1 Key System Specifications


表 1. Key System Specifications

PARAMETER	COMMENTS	MIN	TYP	MAX	UNIT		
<b>SYSTEM INPUT</b>							
$V_{IN}$	Input voltage	Battery voltage range (DC)		3.5	13.5	24	V
$V_{SYS}$	System supply output voltage	—	3.3	—	—	V	
$I_{SYS}$	System supply output current	—	—	5	—	A	
$V_{CORE}$	Core-voltage supply output voltage	—	1.2	—	—	V	
$I_{CORE}$	Core-voltage supply output current	—	—	1	—	A	
$V_{I/O}$	I/O supply voltage	—	3.3	—	—	V	
$I_{I/O}$	I/O supply output current	—	—	0.1	—	A	
$V_{CAN}$	CAN supply voltage	—	5.0	—	—	V	
$I_{CAN}$	CAN supply output current	—	—	0.2	—	A	
$V_{REF}$	ADC Voltage Reference	—	2.5	—	—	V	
$F_{SYS\_SW}$	Switching frequency	Switching frequency of all supplies in system		2.2	—	3.5	MHz
$V_{IT}$	Voltage Supervisor Error	Error of threshold voltage in undervoltage and overvoltage conditions		—	—	1	%

## 2 System Overview

### 2.1 Block Diagram

图 3. TIDA-050008 Functional Block Diagram

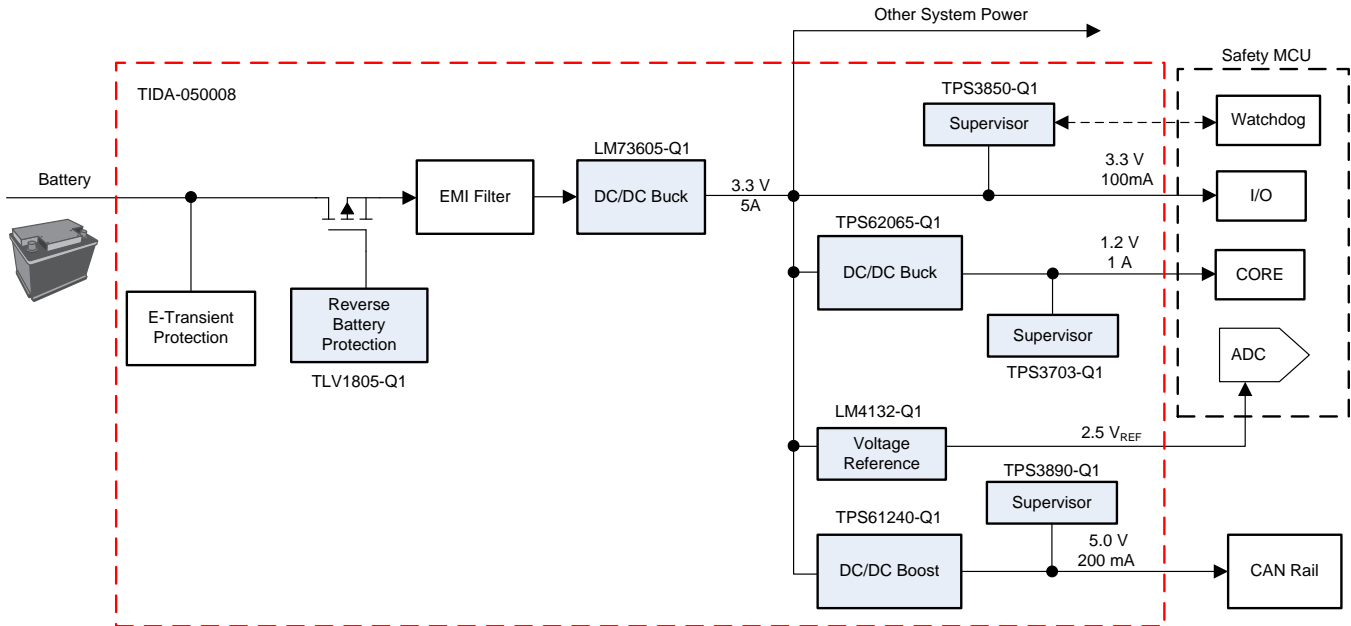

### 2.2 Design Consideration

This design has been created with the following considerations in mind:

- Precision voltage supervision for processor rails and watchdog monitoring for the MCU
- Provide precision voltage reference for voltage monitoring and diagnostics ADC
- Provide system supply currents up to 5 A at 3.3 V.
- Minimize electromagnetic interference (EMI) and solution size.
- Reduce conducted emissions below CISPR 25 Class 5 conducted emissions limits
- Withstand reverse battery condition
- Operate through start-stop and cold-crank down to 3.5 V
- Optimize the individual blocks for smallest possible solution size
- Provide power for CAN PHY and Safety MCU

## 2.3 Highlighted Products

This reference design uses the following TI products:

- TLV1805-Q1: 40 V Push-pull Comparator for reverse battery protection. This is a low voltage drop alternative to discrete diodes.
- LM73605-Q1: 5-A synchronous buck converter with a wide input voltage range from 3.5 V to 36 V (42-V transients), enabling the device to work directly from an automotive battery.
- TPS62065-Q1: Highly-efficient 3-MHz synchronous buck converter. Has power-save mode operation at light load conditions to maintain high efficiency over load current ranges.
- TPS61240-Q1: Fixed 5 V output 3.5-MHz boost converter. TPS61240-Q1 allows the use of small inductor and capacitors to achieve a small solution size.
- TPS3850-Q1: Precision voltage supervisor with under and voltage monitoring. The TPS3850-Q1 doubles as a programmable window watchdog timer.
- TPS3703-Q1: Small form factor precision window supervisor. Does not require any external resistors for setting overvoltage and undervoltage thresholds, which further increases overall accuracy and reduces solution size and cost.
- TPS3890-Q1: Low-quiescent current precision voltage supervisor. Available in a small 1.5-mm x 1.5-mm package, making the device well-suited for space constrained applications
- LM4132-Q1: Precision series voltage reference. This device has 0.05% output initial voltage accuracy and a low temperature coefficient of 10 ppm/°C.

The following subsections detail each device and explain their selection for this application.

### 2.3.1 TLV1805-Q1

The TLV1805-Q1 is a comparator that is used to sense the battery voltage for reverse battery conditions. The unique combination of wide supply range, push-pull output, rail-to-rail inputs, low quiescent current, and fast output response makes this device an easy choice for reverse battery applications.

### 2.3.2 LM73605-Q1

The LM73605-Q1 is the main system supply in this reference design. The wide input voltage range, high integration, and fast switching at 5-A make this device a top choice for the wide input, voltage power front end. The switching frequency of the device is adjustable between 350 kHz to 2.2 MHz. The switching frequency is selected to be 2.2 MHz because there should be minimal interference in the AM band (530 kHz to 1.8 MHz) for automotive applications. The benefit to switching above the AM band rather than below is that the faster switching frequency reduces the physical size of the output inductor and decreases the total solution size.

Though not used in this reference design, this switcher supports external clock synchronization to avoid beat frequencies between multiple converters or to allow a master to dither the clock signal. This feature can be very useful for optimizing systems for EMI performance.

### 2.3.3 TPS62065-Q1

The TPS62065-Q1 provides 1.2 V for the core voltage supply of a typical MCU in this design. Its high efficiency and 2-A current capabilities makes it a great fit to provide the core supply. The switching frequency is a fixed 3-MHz to provide minimal interference to the AM band. The TPS62065-Q1 is optimized for operation with a tiny 1- $\mu$ H inductor and a small output capacitor to achieve smallest solution size and high regulation performance.

### 2.3.4 TPS61240-Q1

The TPS61240-Q1 is 3.5-MHz boost converter. Its fixed 5 V output lowers the amount of external components required for low cost, low size solutions. The device has 450 mA output current capabilities to support single or dual CAN transceivers at 200-mA maximum current each. During light load conditions the device will automatically pulse skip allowing maximum efficiency.

### 2.3.5 TPS3850-Q1

The TPS3850-Q1 is a voltage supervisor that achieves 0.8% accuracy maximum across operating temperature. The overvoltage and undervoltage monitoring and built-in window watchdog timer makes this device an easy choice to monitor the I/O voltage rail of the MCU and provide watchdog diagnostic for the MCU as well. The device comes in set threshold for overvoltage and undervoltage monitoring so external resistors are not required. The TPS3850-Q1 has user-programmable reset delay and window watchdog timeouts.

### 2.3.6 TPS3703-Q1

The TPS3703-Q1 is a small-sized precision window voltage supervisor. Like the TPS3850-Q1, this device has integrated overvoltage and undervoltage monitoring with set thresholds and tolerances. With many fixed options, the TPS3703-Q1 does not require many external components which can reduce solution size and BOM cost. Because of its high performance and features, the TPS3703-Q1 is perfect to provide supervision to the main core rail of the MCU while keeping a small board footprint.

### 2.3.7 TPS3890-Q1

The TPS3890-Q1 is a low-quiescent current, under voltage supervisor. Similar to the TPS3703-Q1, the TPS3890-Q1 comes in a fixed voltage version and small WSON 1.5-mm x 1.5-mm package which makes it capable in size constrained applications. The device has adjustable reset delays for proper sequencing in multi-rail systems such as ADAS applications.

### 2.3.8 LM4132-Q1

The LM4132-Q1 is a family automotive grade precision voltage reference. Available in multiple fixed voltage options and accuracy grades, the LM4132-Q1 provides great flexibility and performance. For systems that require voltage monitoring more than the ones this design covers, a precision voltage reference is critical for an ADC to provide accurate diagnostic.

## 2.4 System Design Theory

### 2.4.1 Printed-Circuit Board (PCB) and Form Factor

This design does not have any specific requirements for the board shape or size. The main objective is to have as small of a solution size as possible for each power supply sub-system. 图 4 shows a three-dimensional (3-D) rendering of the PCB, followed by a labeled photograph of the actual board in 图 5.

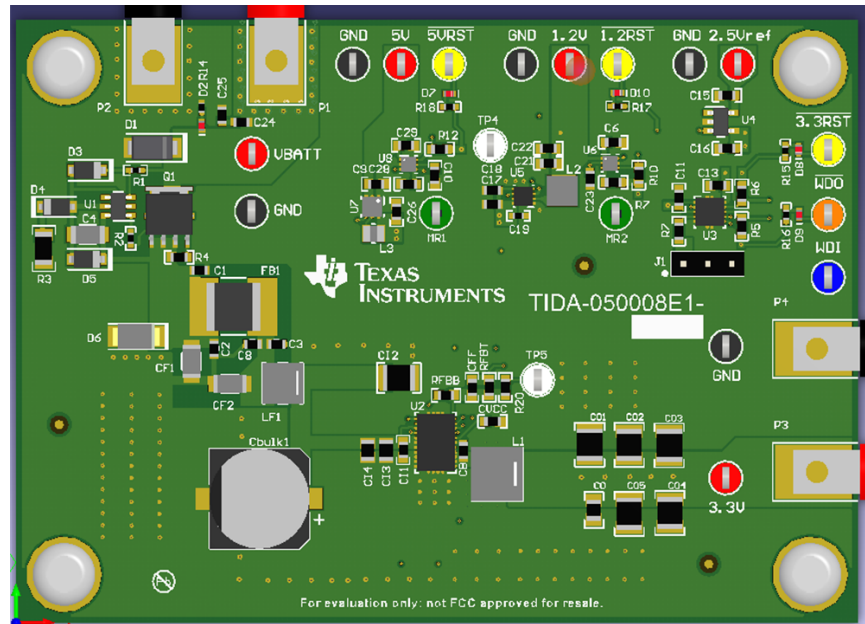


图 4. TIDA-050008 PCB Render

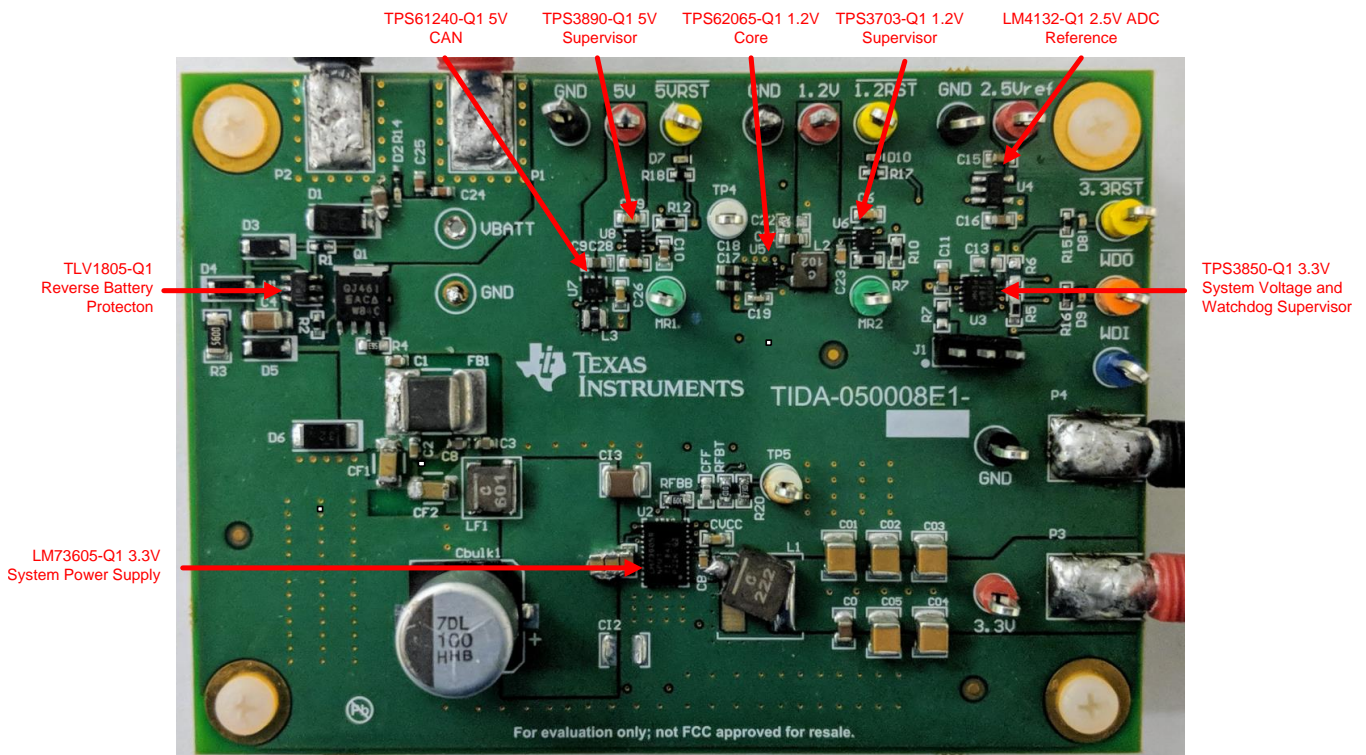


图 5. TIDA-050008 Labeled Supplies and Components

## 2.4.2 Input Protection and Wide- $V_{IN}$ DC-DC

### 2.4.2.1 TVS Diodes

Transient voltage suppression (TVS) diodes are required on the supply input of the system to protect against both positive and negative going transients. The transients of concern are detailed in ISO 7637-2:2004, pulses 1 and 2a. Many systems in a car can simply shut down during these transients until the condition passes; alternatively, many ADAS applications require continuous operation. For this reason, the transients must be shunted instead of using an over voltage shutdown scheme.

图 6 shows a schematic of the input transient protection.

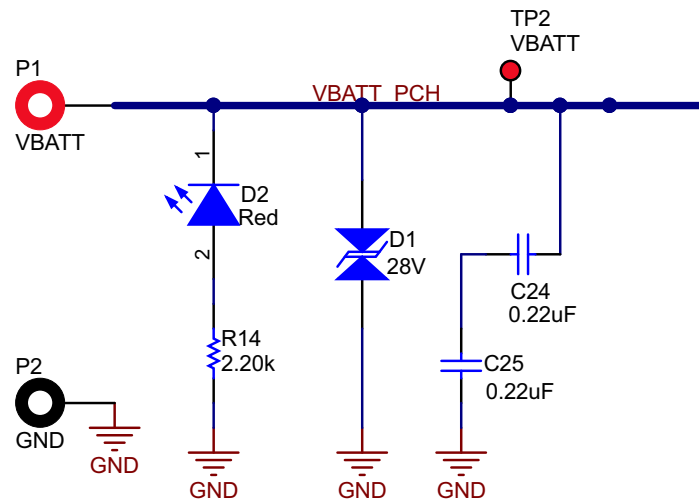


图 6. Input Transient Protection

The diode breakdown voltages have been chosen such that transients are clamped at voltages that protect the MOSFET and the rest of the system. The positive clamping device must clamp above a double-battery (jump-start) and clamped load dump voltages, but lower than the maximum operating voltage of the downstream devices. In this case, the requirement is to clamp around 28 V but have a maximum clamping voltage below 40 V. Ideally, the best choice is to specify 36 V as the approximate maximum clamping voltage. The reverse clamping device must clamp negative voltages greater than the battery voltage so that it does not short out during a reverse-battery condition.

The two series capacitors should be mounted at right angles to each other. Placing ceramic SMT capacitors in series-angle is common practice in automotive applications. The most common failure modes for ceramic SMT capacitors is a short or open. The series connection is for if one of the capacitors short-out it will not short the bus and the other capacitor will still be functional. The right-angle reason is so that if the board flexes and damages one of the capacitors, the other capacitor should survive since it was at the opposite angle. The capacitors should also be closest to the input connectors since they will be handling the high voltage, high frequency transients. The current path needs to be as short as possible between the jacks.



### 2.4.2.2 Reverse Battery Protection

Reverse battery protection is a requirement for nearly every electronic module in a vehicle, both by original equipment manufacturer (OEM) standards as well as ISO 16750-2, an international standard that pertains to supply quality. The TLV1805-Q1 circuitry has been subjected to selected ISO 16750-2 and ISO 6737-2 waveforms for 12 V systems. The circuits survived with no performance degradation, and the load voltage did not exceed design limits. The circuit was tested on an evaluation module and does not imply full ISO certification of the board, or that the use of these circuits implies ISO certification of users end equipment. For more information, check the [TLV1805-Q1](#) product page and datasheet.

图 7 shows a schematic of the reverse battery input protection.

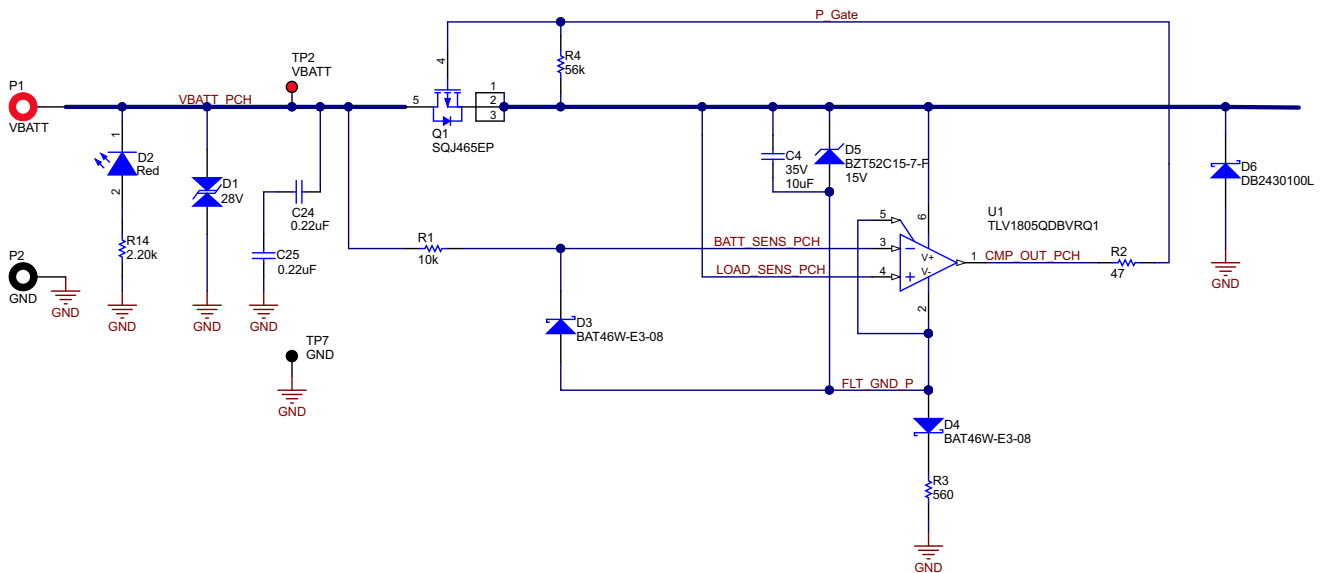


图 7. Reverse Battery Input Protection

This implementation of reverse battery protection uses a P-channel MOSFET controlled by the TLV1805-Q1 device. The TLV1805-Q1 is a low-power comparator that is used to sense the voltage between the P-FET. In reverse battery conditions, the TLV1805 will disable the FET to protect the devices on the board. The power dissipation of a traditional diode rectifier solution is significantly higher due to the typical 600-mV to 700-mV forward drop. A very-low forward voltage drop can be achieved using low  $R_{DS(ON)}$  external P-channel MOSFETs. This low forward voltage drop from the supply to the system yields much higher efficiency, less heat, and a lower input voltage operating range while protecting the system from a reverse polarity condition.

The FET must have a rating which is at least as high as the clamped input voltage. This reference design uses a -60-V, -30A P-FET with a -2-V gate-source threshold voltage.

### 2.4.2.3 Input EMI Filter

The schematic in 图 8 shows the EMI filter at the system supply input, after the reverse battery protection.

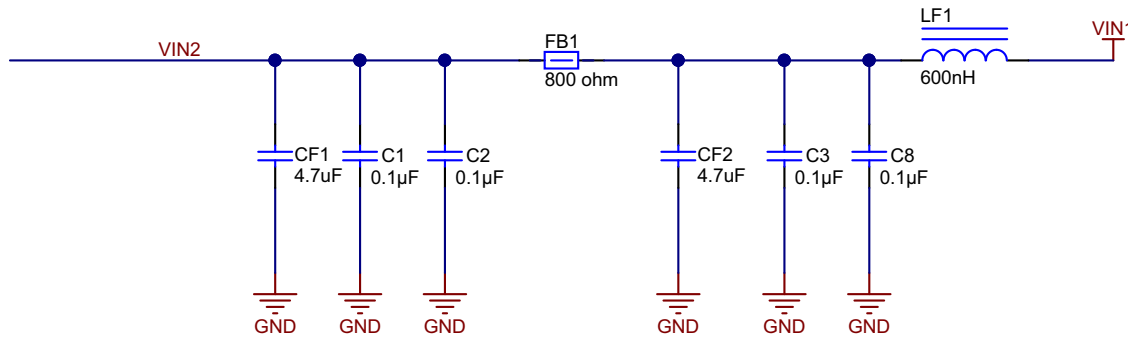


图 8. Input EMI Filter Schematic

The switching frequency of the system power supply is 2.2 MHz. The EMI filter inductor requirement can be eased since filtering out frequencies below the AM band typically requires larger inductors with more inductance, usually 10  $\mu\text{H}$  or more, as more inductance provides more impedance at lower frequencies. Decoupling capacitors C3 and C8 filter out the high-frequency noise that the inductor LF1 cannot attenuate.

The ferrite bead FB1 has a higher resonant frequency than inductor LF1, around 100 MHz. The impedance due to the higher resonant frequency attenuates any unfiltered noise around this 100-MHz band that has been conducted upstream from the LF1-CF2 node to VIN2 and acts as a high-frequency current choke by increasing the impedance for higher-frequency currents from the larger upstream loop, from VIN2 to downstream components after VIN1. Similar to capacitors C3 and C8 after LF1, the decoupling capacitors C1 and C2 provide a low impedance path for high-frequency currents to ground.

When selecting and adding decoupling capacitors, it may seem attractive to simply add more capacitors. No matter how much decoupling is used, designers must take careful consideration to avoid parallel resonances resulting from the unseen parasitics of the passives. Parallel resonances can cause EMI problems that may be difficult to pinpoint and address.

While it is critical to select the right components for the EMI filter, strategically laying out these components is equally critical for an effective EMI filter.

### 2.4.2.4 Wide Input Voltage Buck Converter

The LM73605-Q1 is an AEC-Q100 qualified, wide-input voltage buck regulator used as a front-end supply to provide a 3.3-V system voltage and I/O voltage of the MCU. With a nominal input voltage range of 3.5 V to 36 V and transients up to 42 V, the device can continue operation through most battery conditions such as start-stop, cold-crank, and load dump.

图 9 shows a schematic of the wide input voltage buck.

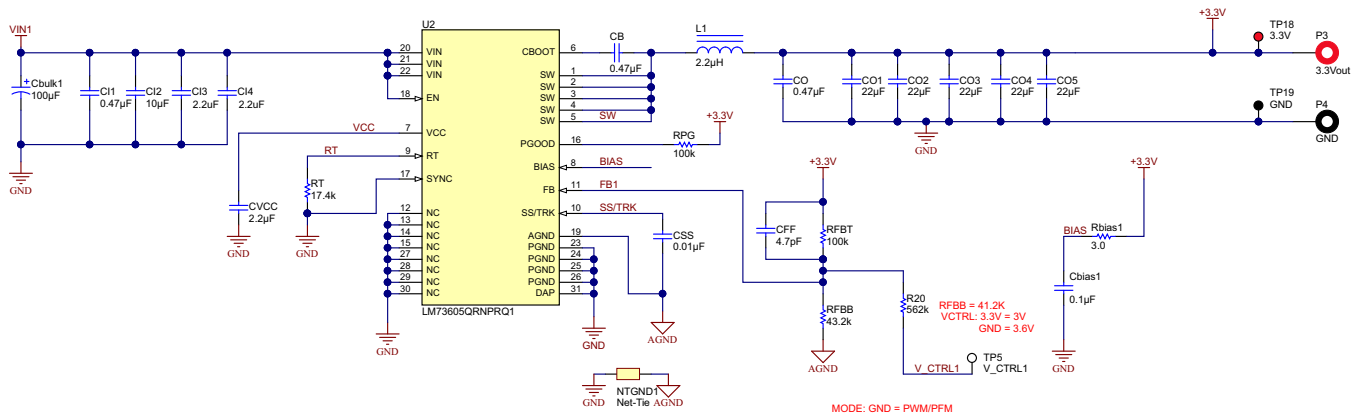


图 9. Wide Input Voltage Buck

The LM73605-Q1 delivers 5 A and configures for a 2.2-MHz switching frequency and a light load architecture (PFM), which means that the device lowers its switching frequency for lower current loads. V\_CTRL1 is used to apply voltage to the FB to test overvoltage and undervoltage conditions.

### 2.4.3 Power Supply Design Considerations

For this power supply, choose inductors such that:

- The ripple current is between 20% to 40% of the load current  $I_{LOAD}$  with the given switching frequency, input voltage, and output voltage. This reference design uses 40%.
- The temperature ratings are appropriate for automotive applications, typically  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  for ADAS applications.
- Saturation current is chosen per 公式 1 for peak current, plus additional margin.

$$I_{SAT} (I_{LOAD} + 0.5 \times I_{RIPPLE}) \times 1.2 \quad (1)$$

An important recommendation for ADAS applications is selecting ceramic capacitors that use X7R dielectric material, which ensures minimum capacitance variation over the full temperature range. The voltage rating of the capacitors must be greater than the maximum voltage and twice the typical voltage across its terminals to avoid DC bias effects. The amount of output capacitance used depends on output ripple and transient response requirements, for which there are many equations and tools available online to help estimate. The supplies in this solution have been designed for a  $\pm 2.5\%$  total transient response. Low equivalent series resistance (ESR) ceramic capacitors have been used exclusively for the purpose of reducing ripple. For internally-compensated supplies, see the device-specific data sheets, as they may have limitations on acceptable LC output filter values.

ICs must always be qualified per AECQ100. TI parts that are qualified typically have part numbers ending in "-Q1".

For improved accuracy, all feedback resistor dividers must use components with 1% tolerance.

### 2.4.3.1 TPS62065-Q1 Core-Voltage Supply

The TPS62065-Q1 is a 2-A, buck converter switching at a fixed 3-MHz. The TPS62065-Q1 is optimized for operation with a tiny 1- $\mu$ H inductor and a small output capacitor to achieve smallest solution size and high regulation performance. This device also has the ability to operate in a power save mode to maintain efficiency in light-load conditions with pulse-frequency modulation (PFM). V\_CTRL2 is used to apply voltage on the feedback to test overvoltage and undervoltage conditions.

图 10 shows the schematic for the device.

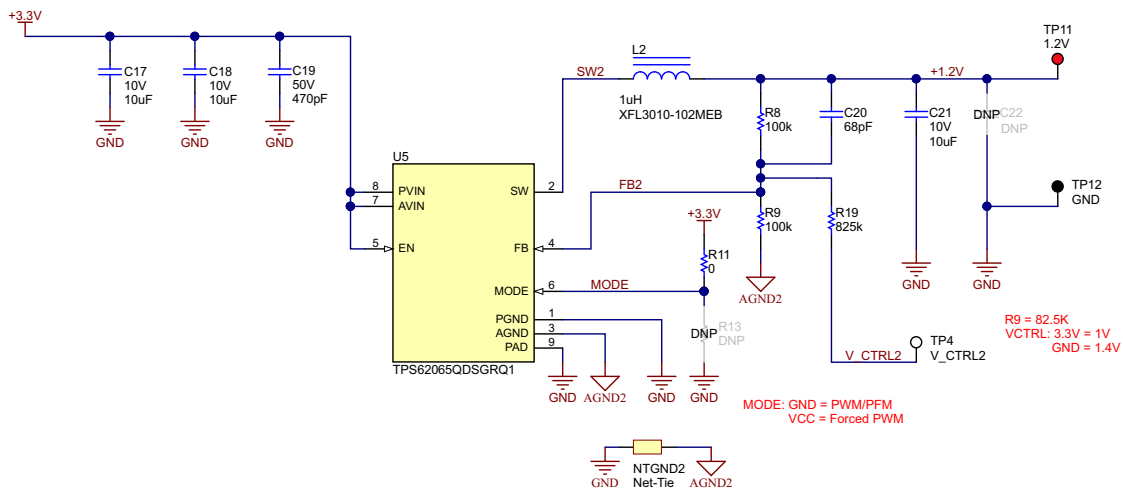


图 10. Core-Voltage Supply Schematic

### 2.4.3.2 TPS61240-Q1 CAN-Voltage Supply

The TPS61240-Q1 device provides the 5-V output voltage required for a CAN bus (see 图 11). The TPS61240-Q1 is a fixed 5V, 3.5-MHz boost converter that requires minimal external components for low cost and size solutions. The device has 450 mA output current capabilities to support single or dual CAN transceivers at 200-mA maximum current each. During light load conditions the device will automatically pulse skip to achieve maximum efficiency.

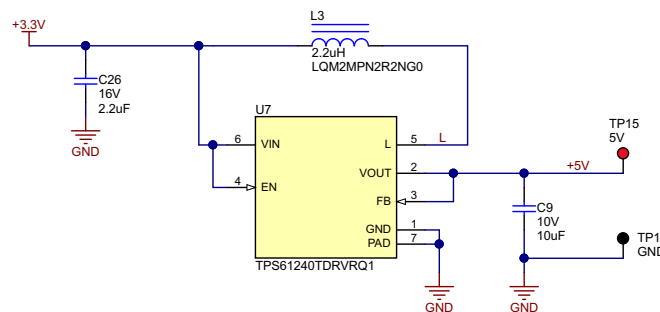


图 11. 5-V CAN Supply Schematic

### 2.4.4 Watchdog, Voltage Supervision, and Reference

Diagnostics and monitoring subsystems play a key role in ADAS systems. In this reference design, each supply voltage is monitored by a dedicated voltage supervisor with different features and specifications to meet the requirements. Features such as watchdog monitoring, window voltage supervision, and programmable reset delays allows for multiple layers of security that can help customers achieve their functional safety goals. Over-voltage monitoring is required for processor applications because high temperatures may affect DC-DC converters nominal values. This may cause the output voltage to drift higher than a processor's tight voltage tolerance. A series voltage reference is also added to provide precision reference to an ADC (internal or external) for accurate diagnostics and monitoring in case other system rails or sensors need to be monitored.

### 2.4.5 TPS3850-Q1 Watchdog and System-Voltage Monitoring

The TPS3850-Q1 combines a precision voltage supervisor with a precision programmable window watchdog timer. The TPS3850-Q1 window comparator achieves 0.8% accuracy (−40°C to +125°C) for both overvoltage and undervoltage thresholds. This device is an easy choice to monitor the I/O voltage rail of the MCU and provide watchdog diagnostic for the MCU as well. The programmability of the TPS3850-Q1 allows adjustable reset delay and window watchdog timeouts, watchdog ratios, and watchdog disable. **RESET** and **WDO** are open-drain outputs that require pull-up resistors to a logic-high voltage. An LED is added in parallel for physical indications of a reset occurring. **图 12** shows the schematic of the TPS3850-Q1 voltage and watchdog monitoring design. The variant of the TPS3850-Q1 in this design is a 7% tolerance, 3.3 V threshold monitor.

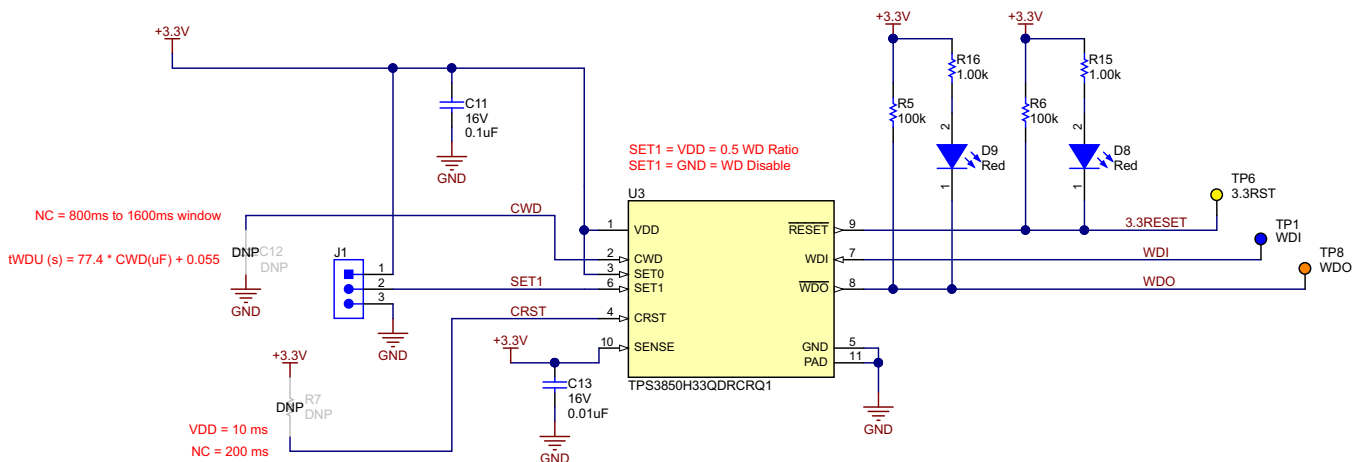


图 12. System-Voltage and Watchdog Monitoring Schematic

### 2.4.6 TPS3703-Q1 Core-Voltage Window Monitoring

The TPS3703-Q1 is a 6-pin WSON precision window voltage supervisor for overvoltage and undervoltage monitoring. TPS3703-Q1 requires minimum passive components because of its various one-time programmable options. The TPS3703-Q1 has 50 mV threshold steps from 500 mV to 1.3V with popular voltage options from 1.5 V to 5.0 V. Tolerances are available from 3% to 7% in 1% steps. Seven fixed time delay options with a programmable delay option with a capacitor. Combined with internal glitch immunity and latch feature, the TPS3703-Q1 is a perfect fit to provide voltage supervision to the core-voltage of the MCU. 图 13 shows the schematic of the TPS3703-Q1 window voltage monitoring design. The variant of the TPS3703-Q1 in this design is a 4% tolerance, 1.2V threshold monitor with a fixed option of 10 ms or 200 ms reset delay.

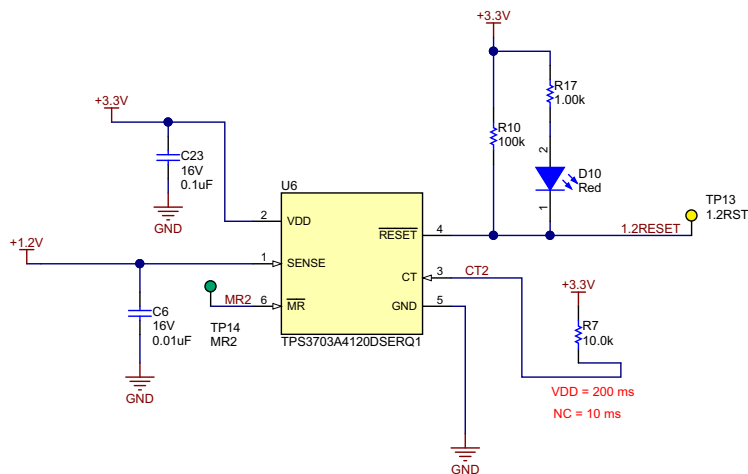


图 13. Core-Voltage Window Monitoring Schematic

### 2.4.7 TPS3890-Q1 CAN Undervoltage Monitoring

The TPS3890-Q1 is a low-quiescent current, under voltage supervisor. Similar to the TPS3703-Q1, the TPS3890-Q1 comes in small WSON 1.5-mm x 1.5-mm package and multiple fixed options in threshold voltage monitoring and tolerance options. The device provides programmable reset delays using an external capacitor. If window voltage monitoring is required for the CAN voltage rail, using the TPS3703-Q1 would be great replacement. 图 14 shows the schematic of the TPS3890-Q1 undervoltage monitoring design. The variant of the TPS3890-Q1 in this design is a 7% tolerance, 5.0 V threshold monitor.

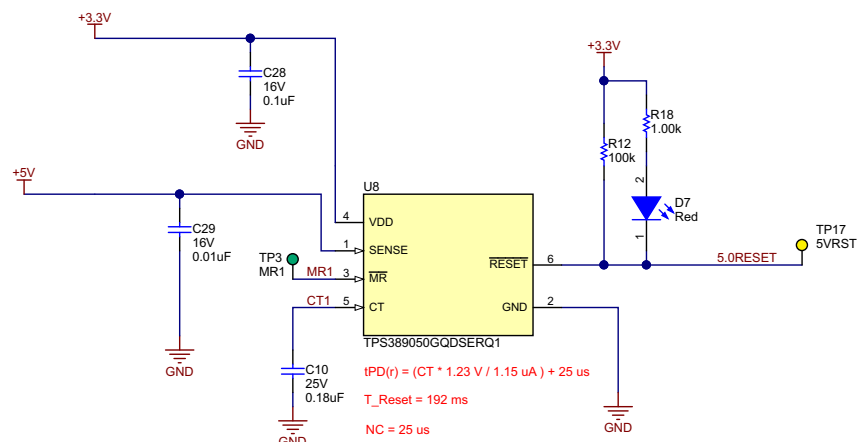


图 14. CAN Undervoltage Monitoring

### 2.4.8 LM4132-Q1 Precision ADC Reference

The LM4132-Q1 is a family of automotive grade precision voltage references. Available in multiple fixed voltage options and accuracy grades, the LM4132-Q1 provides flexibility and performance. With a maximum of 10 ppm/°C temperature coefficient and 60 uA low-Iq, the LM4132-Q1 is a great fit for an ADC reference. For systems that require monitoring on other system voltages, a precision voltage reference is critical for an ADC to provide accurate diagnostic.

图 15 shows the schematic of the LM4132-Q1 precision ADC reference design. The variant of the LM4132-Q1 has initial output accuracy of 0.05% and 10 ppm/°C temperature coefficient. Depending on the application's specifications and accuracy requirements, the LM4128-Q1 or REF34-Q1 may be a better fit for the ADC.

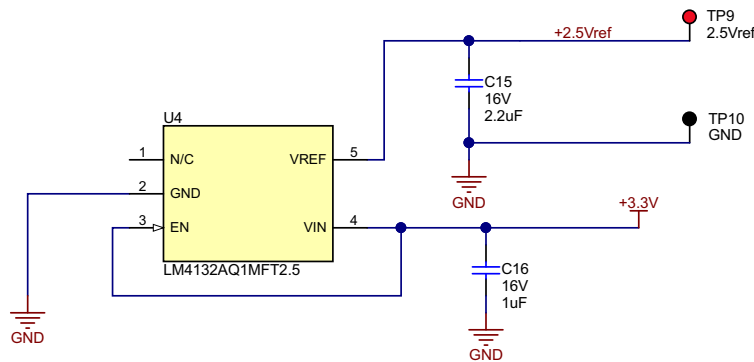


图 15. Precision ADC Reference Schematic

### 3 Hardware and Testing Requirements

#### 3.1 Hardware

To get started with the TIDA-050008 board, simply connect the leads to the banana jack on the top-left corner of the board. The screw terminals are labeled VBATT and GND and color-coded red and black respectively to indicate the correct polarity of the supply (see [图 16](#)). The system voltage supply also has output terminals with banana jacks on the bottom-right corner of the board labeled 3.3V and GND. Connect a power supply that is capable of at least 13.5 V and 2 A to the leads to supply power.

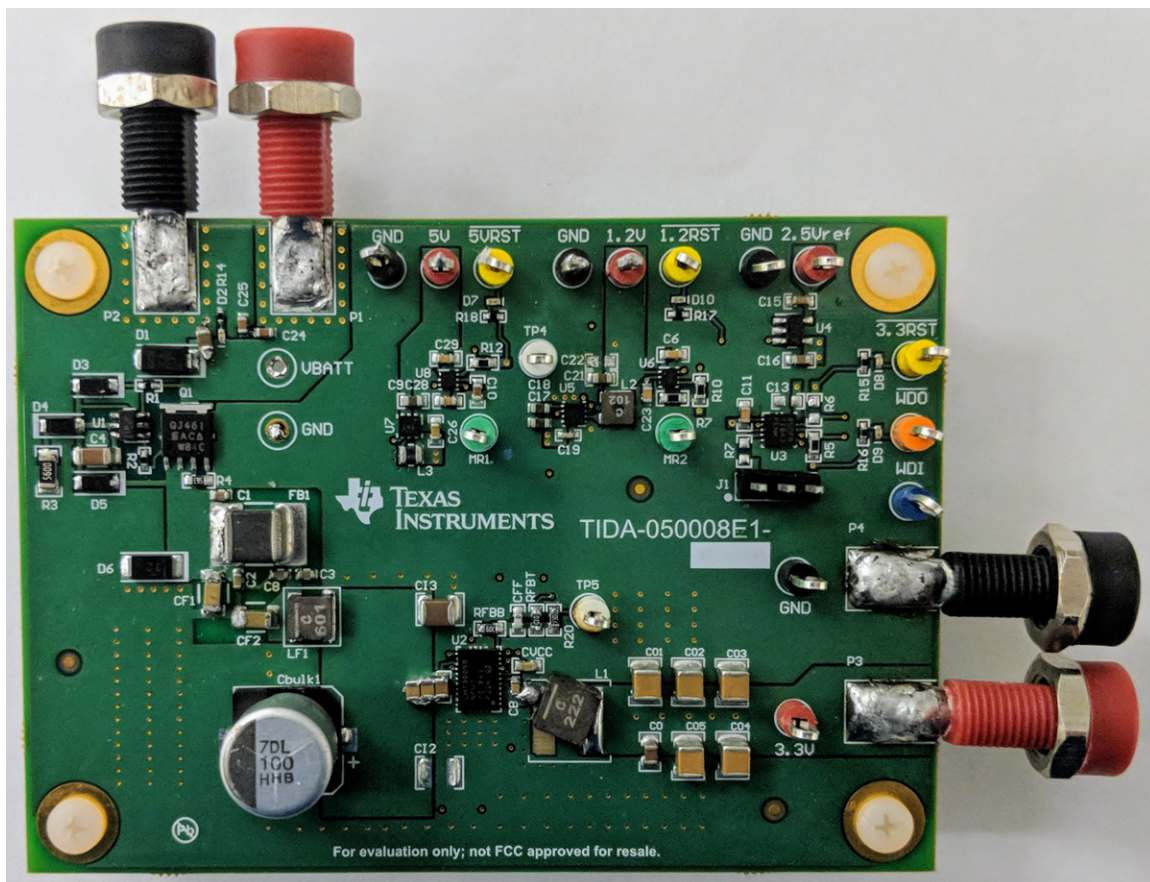


图 16. Board Input Terminals



## 3.2 Testing and Results

The following information shows how to set up for the various tests performed on this design.

To perform pulse testing, this design used the AutoCrankSim-EVM: Simulator for Automotive Cranking Pulses Evaluation Module Board. This board is available for purchase at: [AUTOCRANKSIM\\_EVM: Simulator for Automotive Cranking Pulses Evaluation Module Board](#). If the designer wishes to build the board or simply view the design files, use the power design files from: [PMP7233 Cranking Simulator Reference Design for Automotive Applications](#).

The following subsections show the test data from characterizing the switching power supplies, voltage supervisors, and voltage reference in the system.

### 3.2.1 Load Regulation and Efficiency

This section presents and discusses the 3.3V system-voltage supply load regulation and system-level power efficiency test results of the Wide-Vin LM73605-Q1 buck regulator. 图 17 shows the output voltage variation of the 3.3-V system-voltage supply with varying load current, from no load to full load.

A close examination of 图 17 shows low deviation from typical voltage supply across various loads. The input voltage is measured from the banana jack terminals, so there is a voltage drop from the reverse battery protection pass FET and EMI filter when it arrives to the LM73605-Q1. At full load, the device does not regulate well at 3.50 V input voltage due to the forward voltages and dropout voltage of the device.

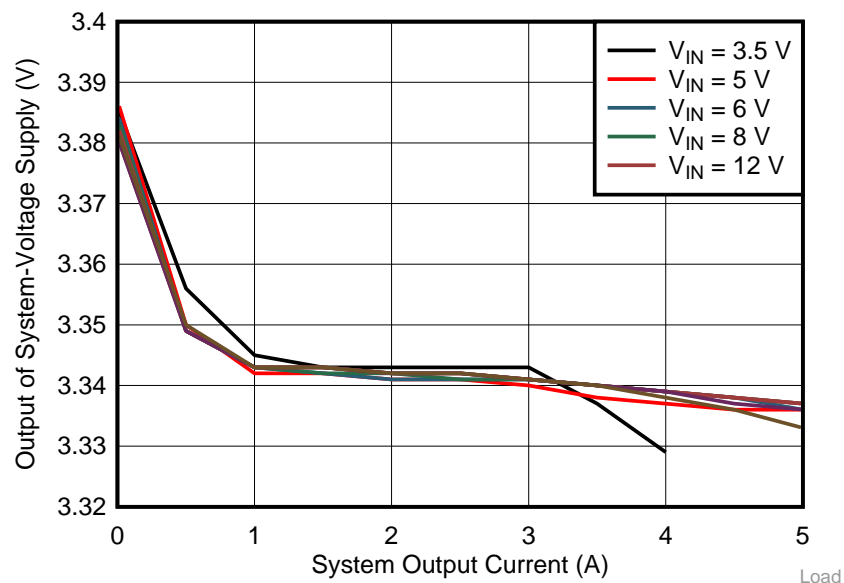


图 17. Load Regulation of 3.3V System-Voltage Supply

The following [图 18](#) shows the efficiency of the system-voltage supply that supports a 15 W design. The system supply consists of the LM73605-Q1 supplying power to the rest of the system outside of TIDA-050008 at a max load of 5A at 3.3 V output. Output voltage and current measurements were taken across an input voltage range of 3.5 V to 24 V.

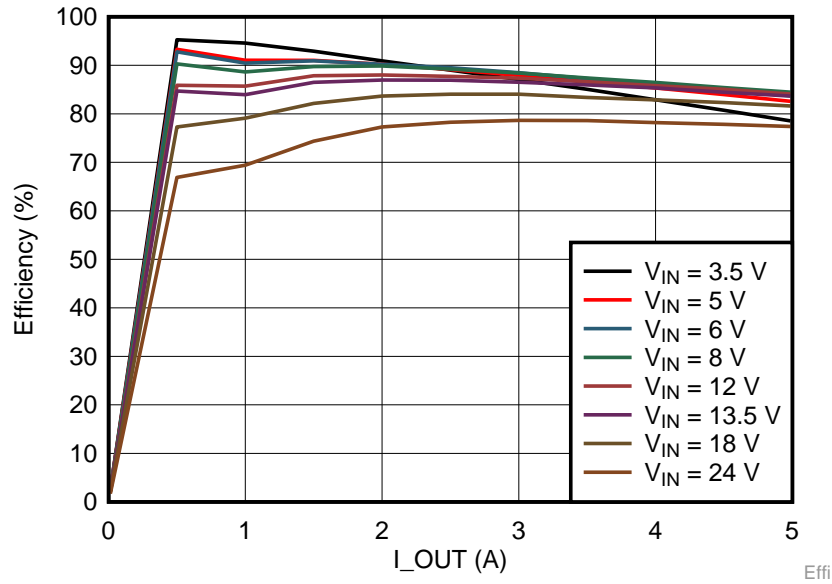


图 18. LM73605-Q1 3.3 V System-level Efficiency

[图 19](#) shows the efficiency with varying input voltage and the full 5-A load. As expected, the measured peak efficiency appears to be around 8 V, with the efficiency dropping off as the input voltage increases.

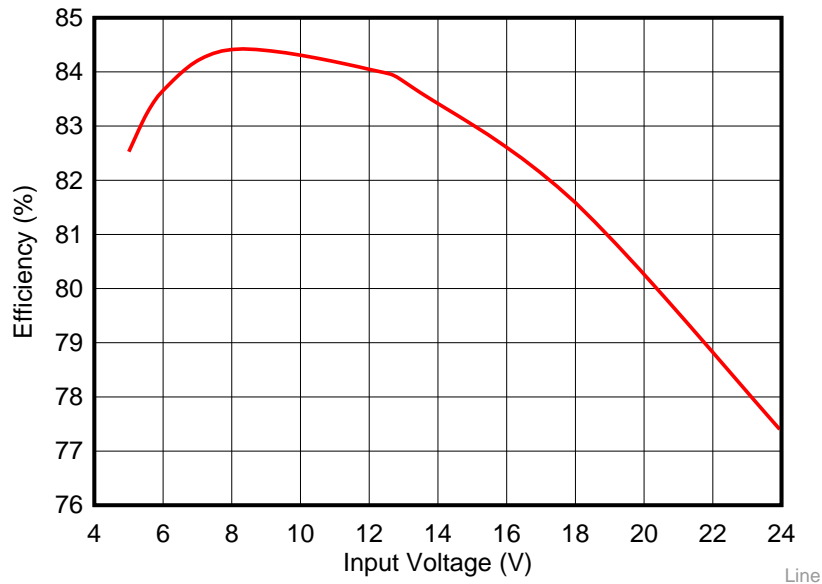


图 19. Full Load Efficiency for Varying Input Voltage

### 3.2.2 Switch Node Waveforms and Output Voltage Ripple

The following oscilloscope waveforms show the switch nodes and output voltage ripples of the various power supplies in the reference design. They are measured using the tip and barrel method. The switch nodes are measured from the SW pin to the power ground of the DC-DC converter. Output voltage ripple are measured closely between the output capacitor. 图 20 and shows the switch node and output voltage ripple at the full load of the LM73605-Q1 buck converter. Channel 1 (blue) shows the switch node waveform and channel 2 (red) shows the output voltage ripple. The output voltage ripple measurements are AC coupled.

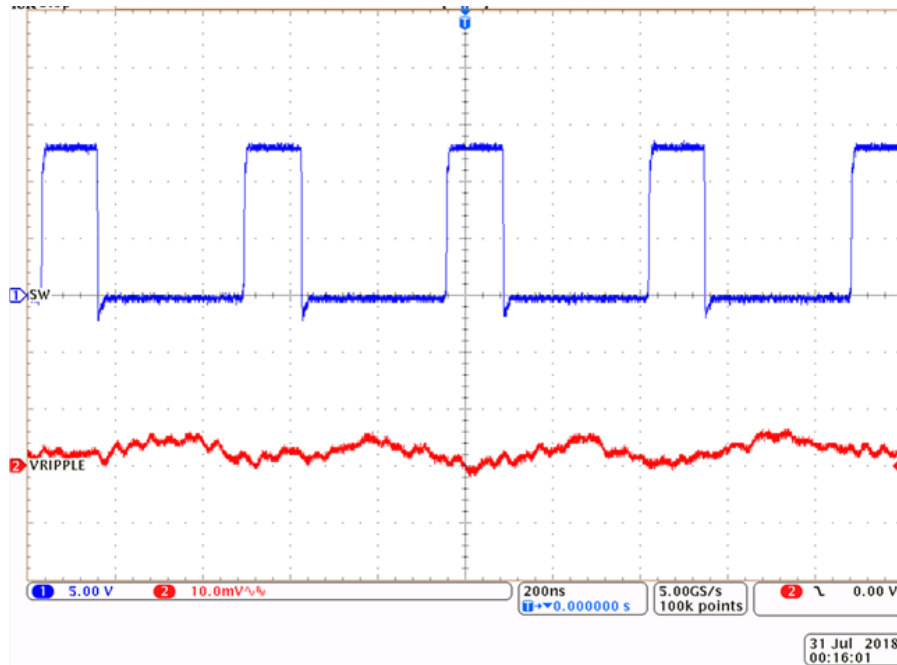


图 20. LM73605-Q1 Switch Node and Output Voltage Ripple, 13.5-V Input at 5-A Full Load

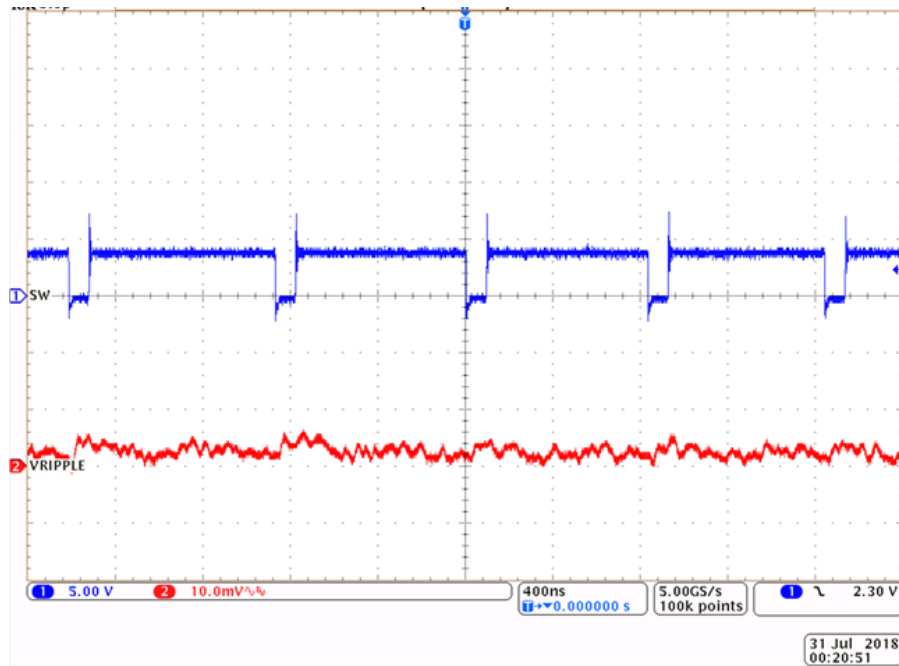


图 21. LM73605-Q1 Switch Node and Output Voltage Ripple, 4.5-V Input at 5-A Full Load

图 22 和 图 23 显示核心电压和 CAN 电压电源的开关节点和输出电压纹波。第一个示波器截图显示了 TPS62065-Q1 1.2-V 输出，然后是 TPS61240-Q1 5-V 输出。这是在 13.5 V 输入电压和满载规格下。

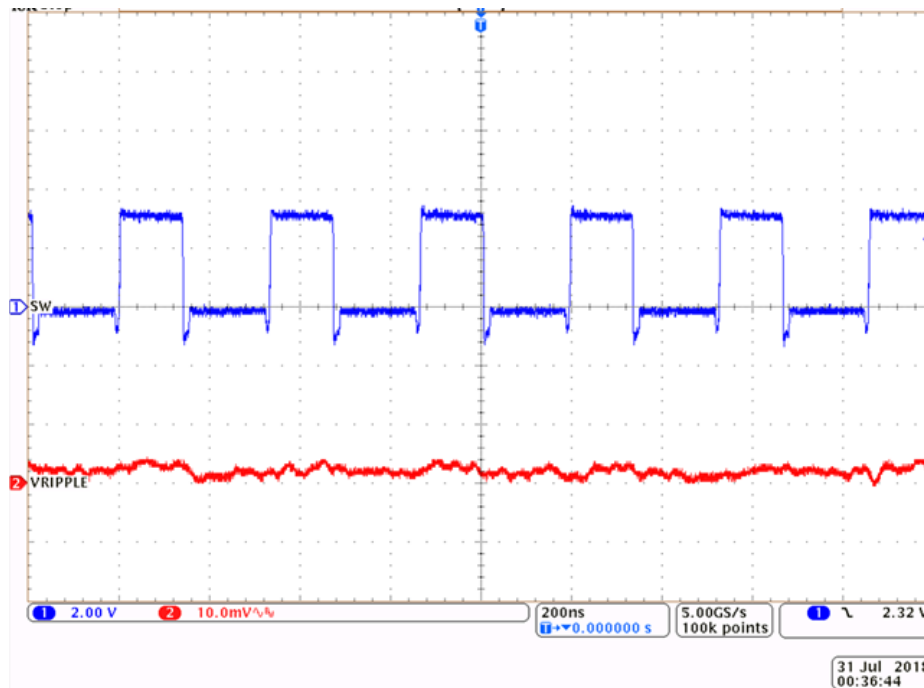


图 22. TPS62065-Q1 开关节点和输出电压纹波, 1.2-V 输出在 1-A 满载

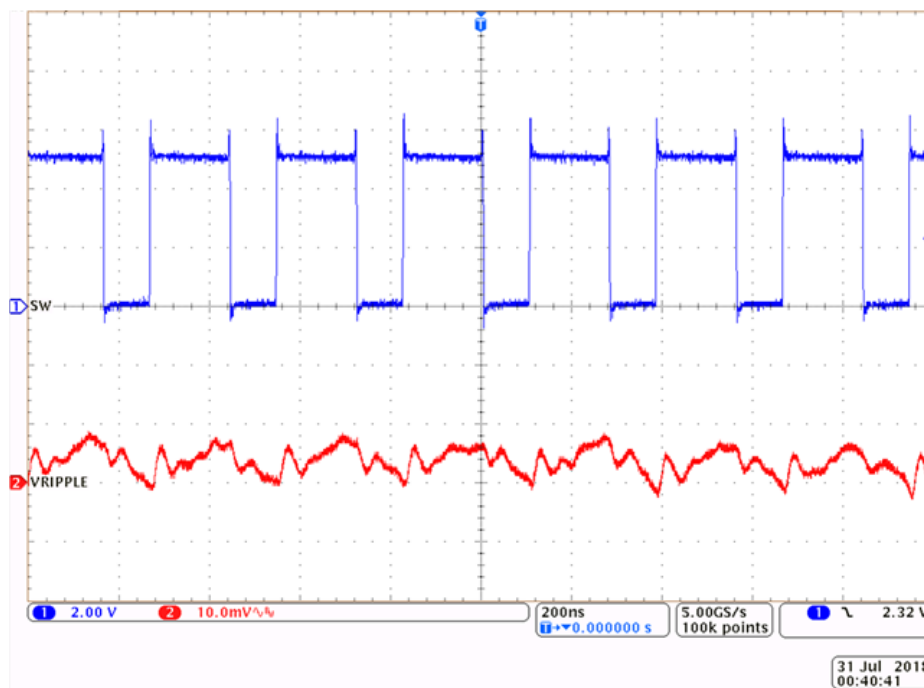


图 23. TPS61240-Q1 开关节点和输出电压纹波, 5.0-V 输出在 200-mA 满载

### 3.2.3 Load Transients

图 24 through 图 27 shows the transient responses for system and core supplies. Channel 2 (pink) measures the AC-coupled output voltage and channel 4 (green) measures the current of the load transient

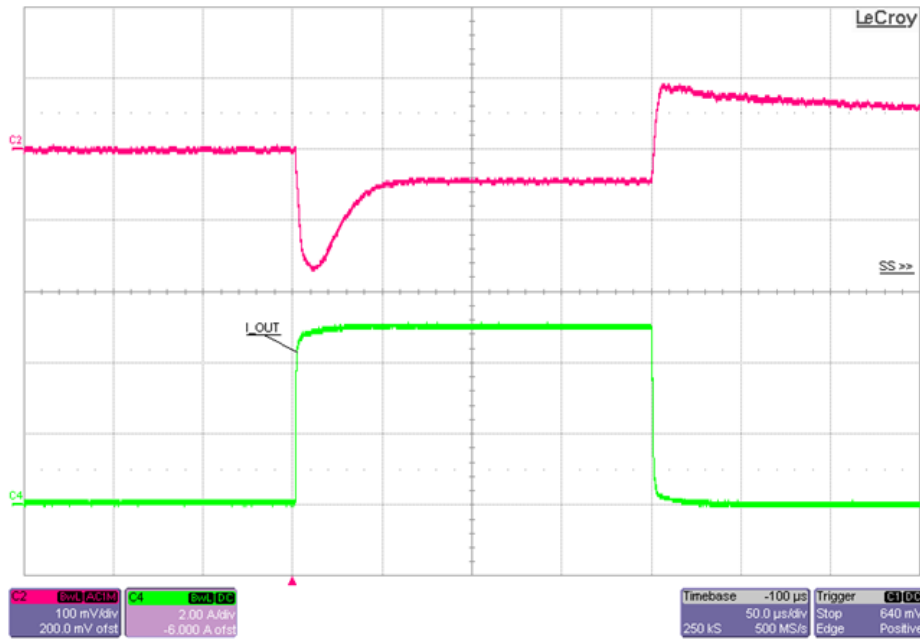


图 24. LM73605-Q1 0-100%, 0 A - 5 A Load Transient

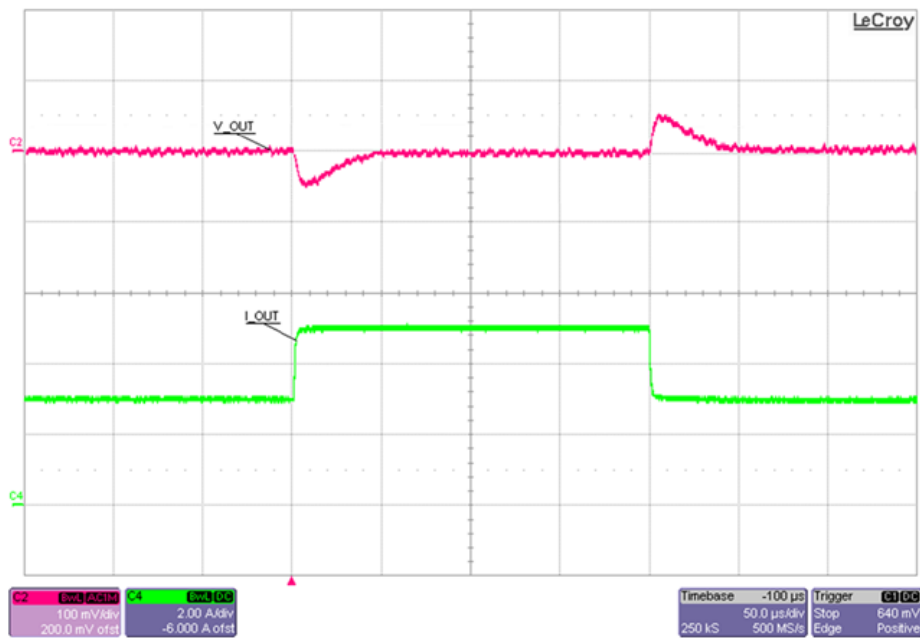


图 25. LM73605-Q1 50-100%, 2.5 A - 5 A Load Transient

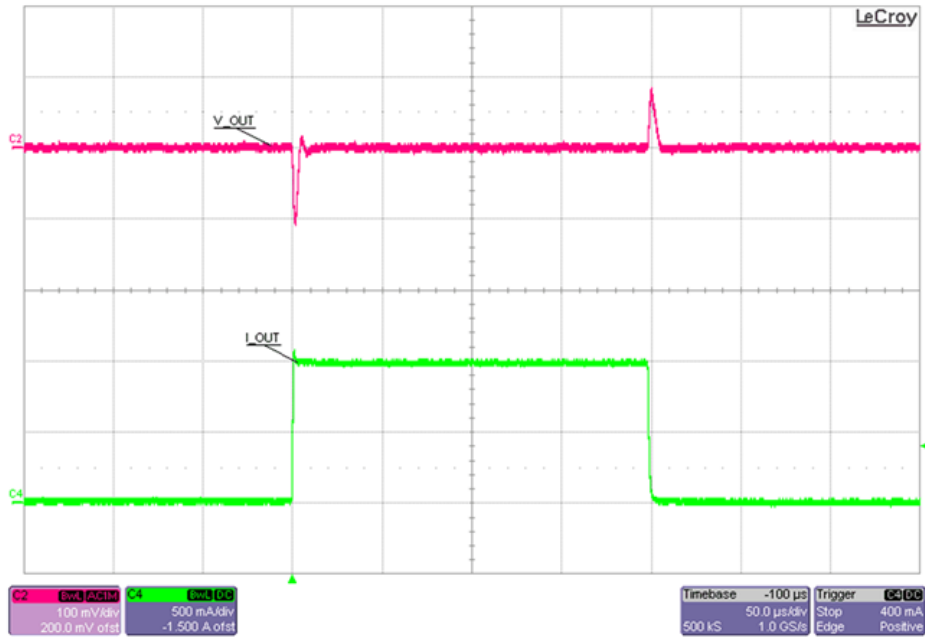


图 26. TPS62065-Q1 0-100%, 0 A - 1 A Load Transient

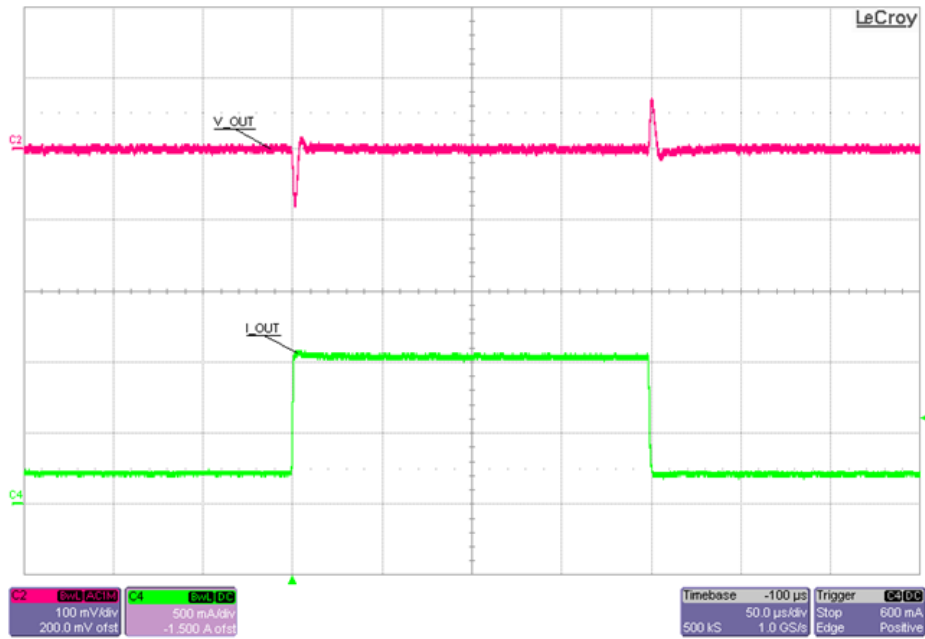


图 27. TPS62065-Q1 25-100%, 250 mA - 1 A Load Transient

### 3.2.4 Voltage Supervisor and Watchdog

图 28 到 图 35 展示了系统电压、核心电压和 CAN 电压电源的电压监督。监督器在过电压和欠电压条件下进行测试。传播延迟和复位时间延迟也被测量。通道 1 (蓝色) 测量电压供应，通道 2 (红色) 测量监督器监测相应电压供应的  $\overline{\text{RESET}}$  引脚。

图 28 和 图 29 展示了 TPS3890-Q1 监督器监测 CAN 电压轨。该器件变体监测典型的 5V 轨，具有 7% 的欠电压容差。这意味着当典型电压低于 4.65 V 时， $\overline{\text{RESET}}$  引脚将触发主动低电压。当 sensed 电压回到容差加上一些迟滞电压时，存在一个复位延迟，该延迟由外部电容器到地编程。

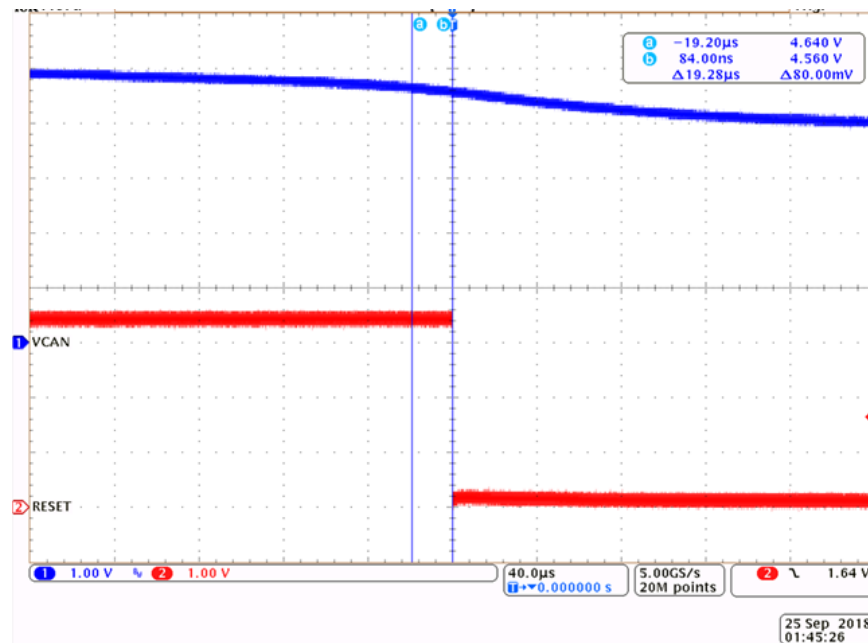


图 28. TPS3890-Q1 欠电压和传播延迟



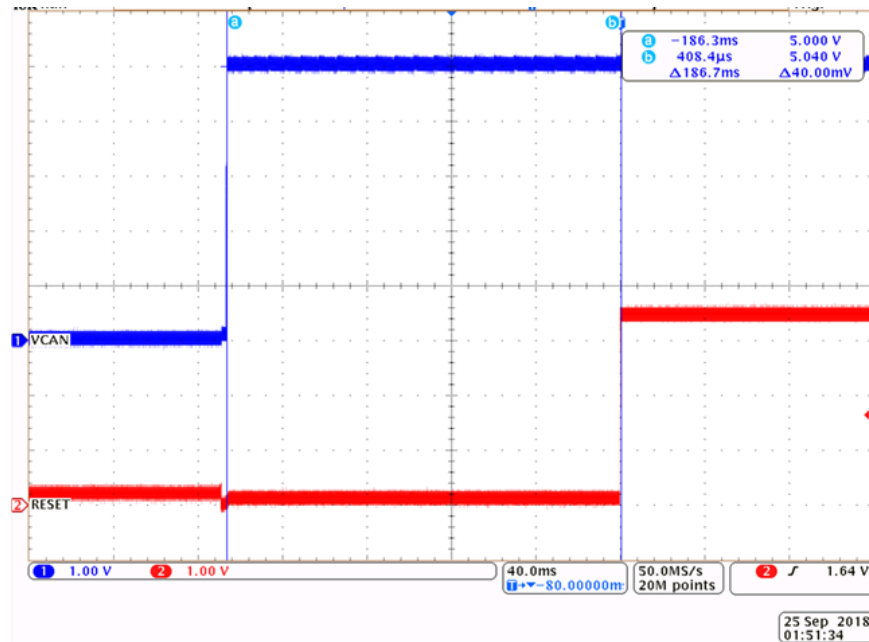


图 29. TPS3890-Q1 Start-Up and Reset Delay

图 30 through 图 32 shows the TPS3703-Q1 window supervisor monitoring the core voltage rail. This device variant monitors a typical 1.2V rail with a 4% undervoltage and overvoltage tolerance. This means when the typical voltage fall below 1.152 V and above 1.248 V , the  $\overline{\text{RESET}}$  pin will trigger an active-low voltage. When the sensed voltage comes back within the tolerance plus some hysteresis voltage, there is a reset delay which is programmed by pulling the CT pin up to VDD. The TPS3703-Q1 has also another fixed time delay option by leaving the CT pin open, or can be adjusted with an external capacitor.

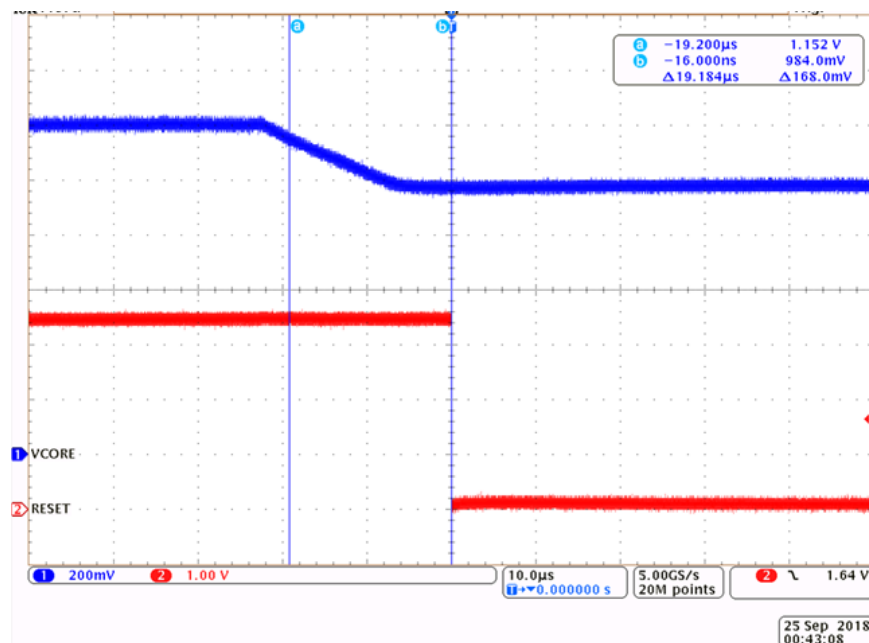


图 30. TPS3703-Q1 Undervoltage and Propagation Delay

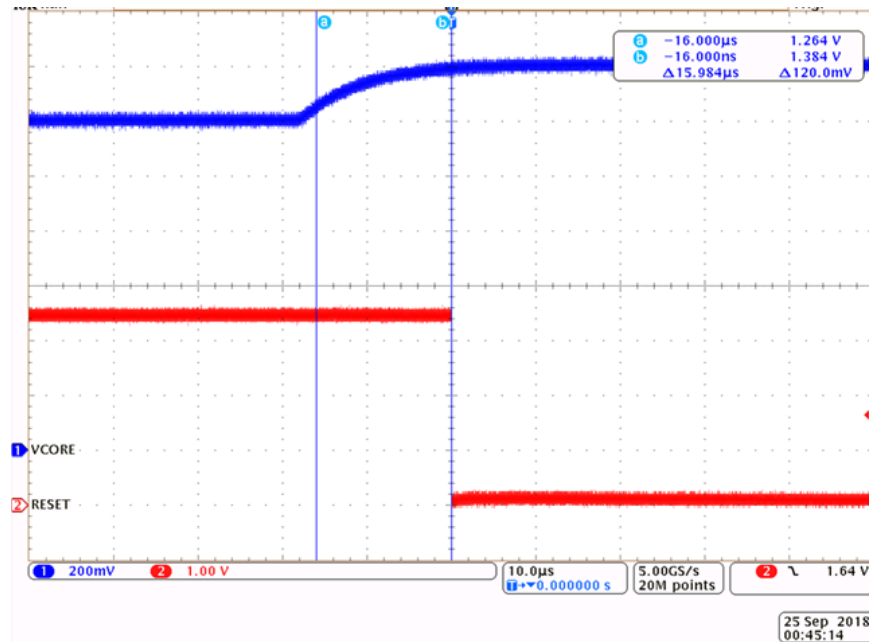


图 31. TPS3703-Q1 Overvoltage and Propagation Delay

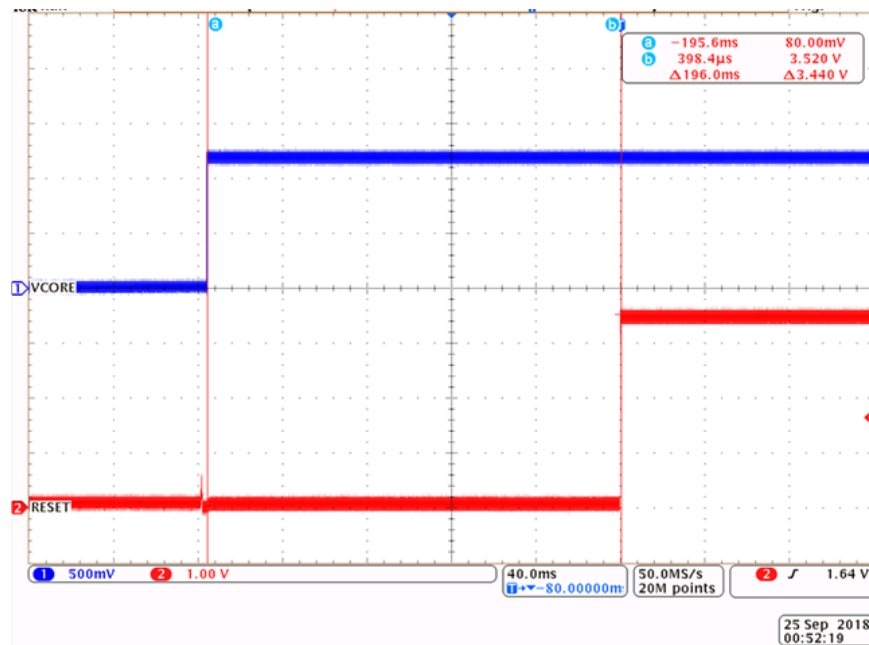


图 32. TPS3703-Q1 Start-Up and Reset Delay

图 33 through 图 35 shows the TPS3850-Q1 window supervisor monitoring the system-power and I/O voltage rail. This device variant monitors a typical 3.3V rail with a 7% undervoltage and overvoltage tolerance. This means when the typical voltage fall below 3.069 V and above 3.531 V , the  $\overline{\text{RESET}}$  pin will trigger an active-low voltage. When the sensed voltage comes back within the tolerance plus some hysteresis voltage, there is a reset delay which is programmed by leaving the CT pin open. The TPS3850-Q1 has also another fixed time delay by connected the pin to VDD, or can be adjusted with an external capacitor..

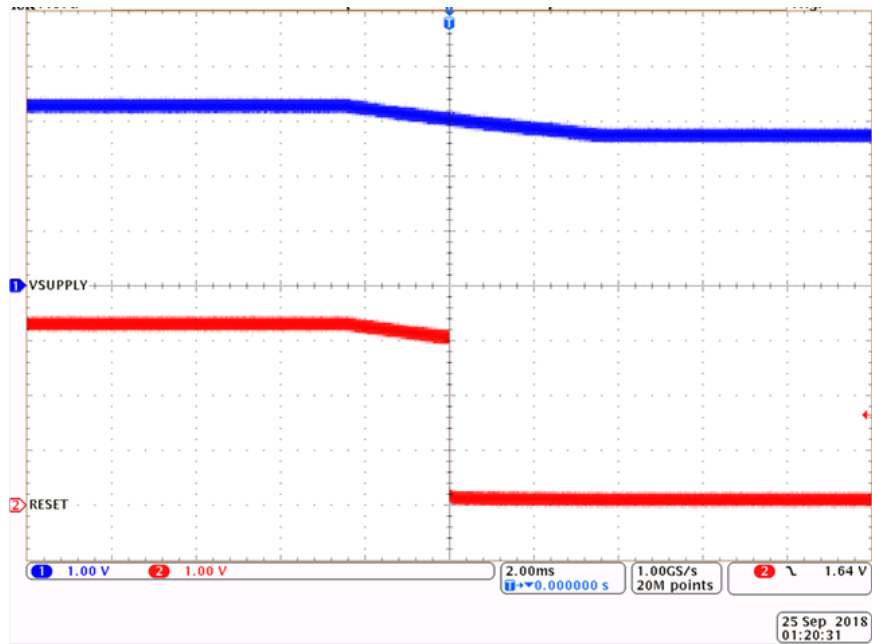


图 33. TPS3850-Q1 Undervoltage and Propagation Delay

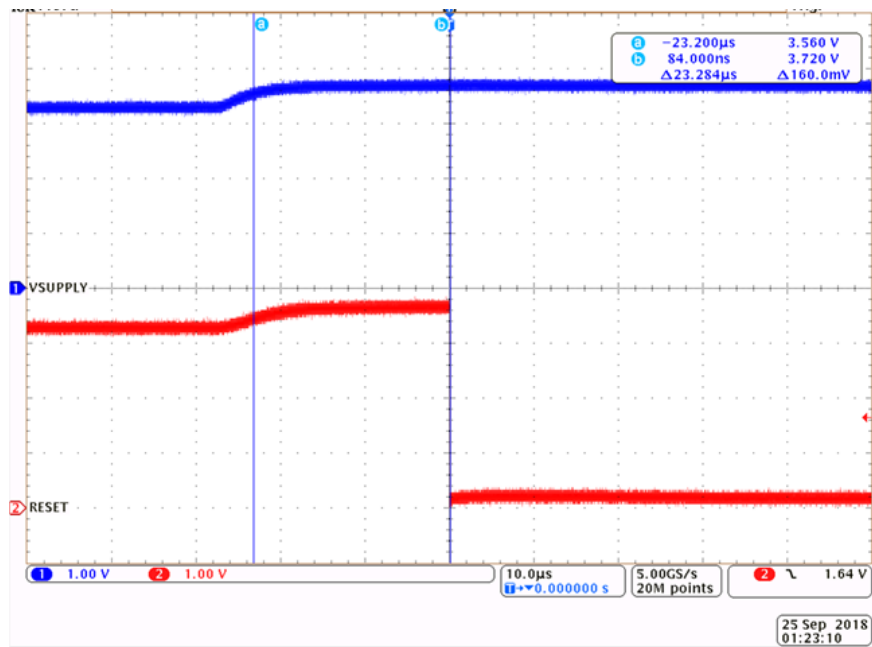


图 34. TPS3850-Q1 Overvoltage and Propagation Delay

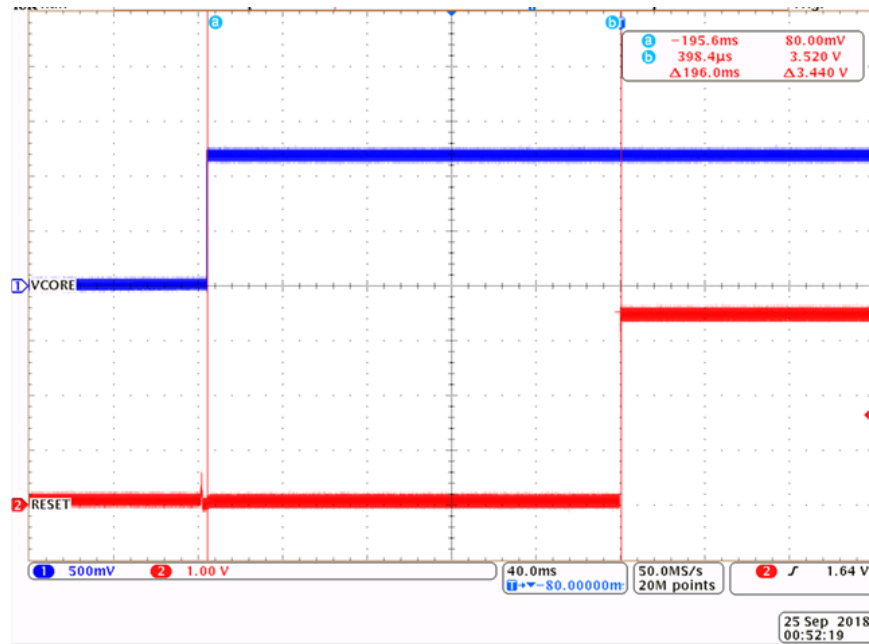


图 35. TPS3850-Q1 Start-Up and Reset Delay

The TPS3850-Q1 has an integrated window watchdog timer with adjustable window ratios and multiple fixed watching timing options. In this reference design, the TPS3850-Q1 utilizes a fixed watching timing option with a 1/2 window watchdog ratio. This means if the upper boundary of the watchdog timer is 1600 ms, then the lower boundary will be 800 ms.

图 36 through 图 39 shows the TPS3850-Q1 watchdog timer monitoring a WDI input waveform input at different frequencies. 图 36 shows a situation where the watchdog input waveform is absent. The watchdog timer output, WDO, stays at a logic-high voltage until the upper boundary limit (1600 ms). Afterwards it is asserted to a logic-low voltage for a reset timeout period (200 ms). When it rises again to a logic-high voltage it will try to detect a falling edge on the watchdog timer input, WDI.

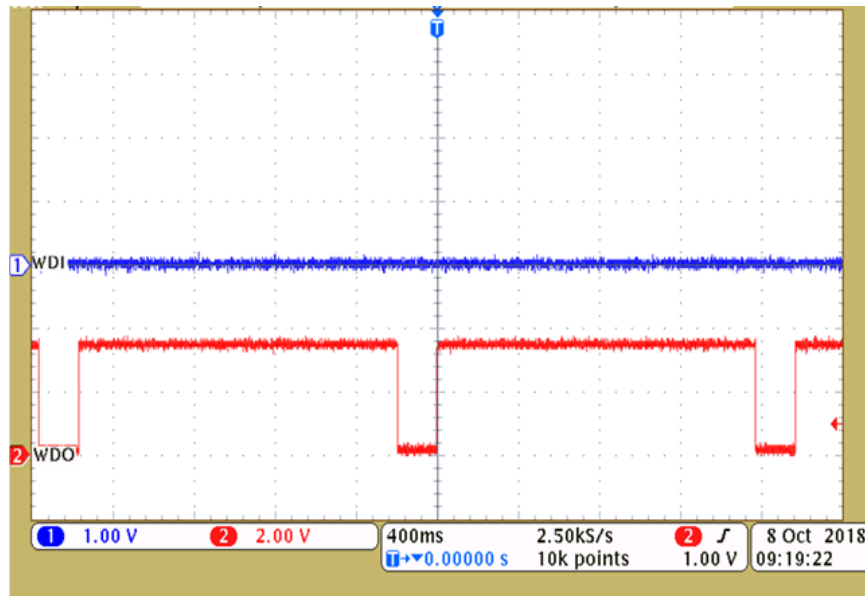


图 36. TPS3850-Q1 Watcher Timer 0 ms Period

图 37 shows the WDO signal when an acceptable input waveform is present on the WDI pin. The WDO pin stays high when the recurring falling edges fall between 800 ms and 1600 ms of the previous falling edge.

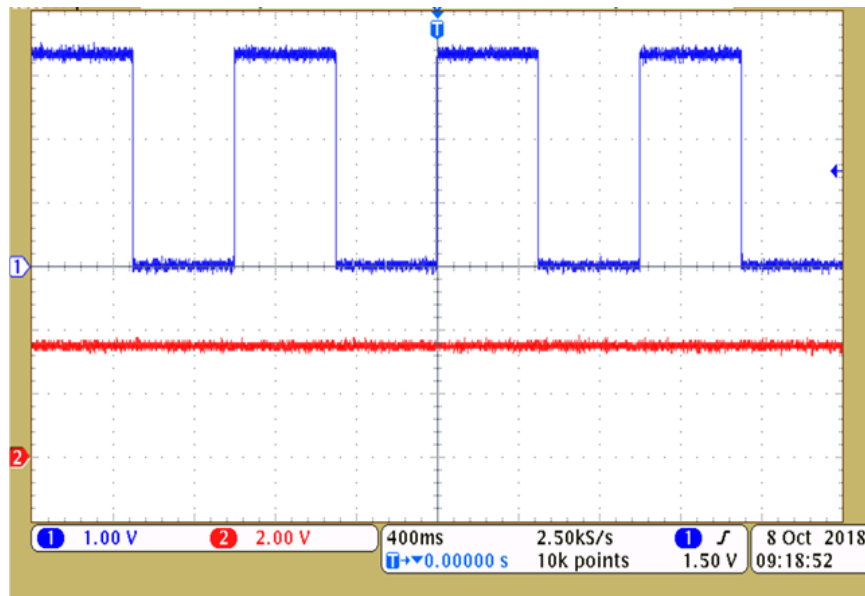


图 37. TPS3850-Q1 Watchdog Timer 1000 ms Period

图 38 shows an early detection fault found on the WDI input waveform. After the device reset timeout period (200 ms), it is asserted logic-high to detect the next falling edge. After detecting a falling edge, if another falling edge is found before the window lower boundary (800 ms), WDO will trigger to a logic-low voltage.

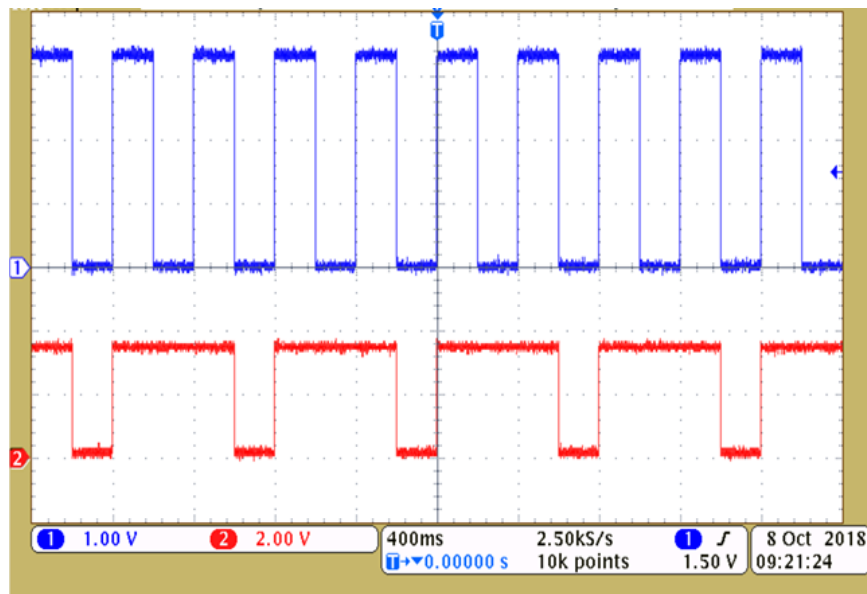


图 38. TPS3850-Q1 Watchdog Timer Early Detection 400 ms Period

图 39 shows an late detection fault found on the WDI input waveform. After the device reset timeout period (200 ms), it is asserted logic-high to detect the next falling edge. After detecting a falling edge, if another falling edge is not found within the window upper boundary (1600 ms), WDO will trigger to a logic-low voltage.

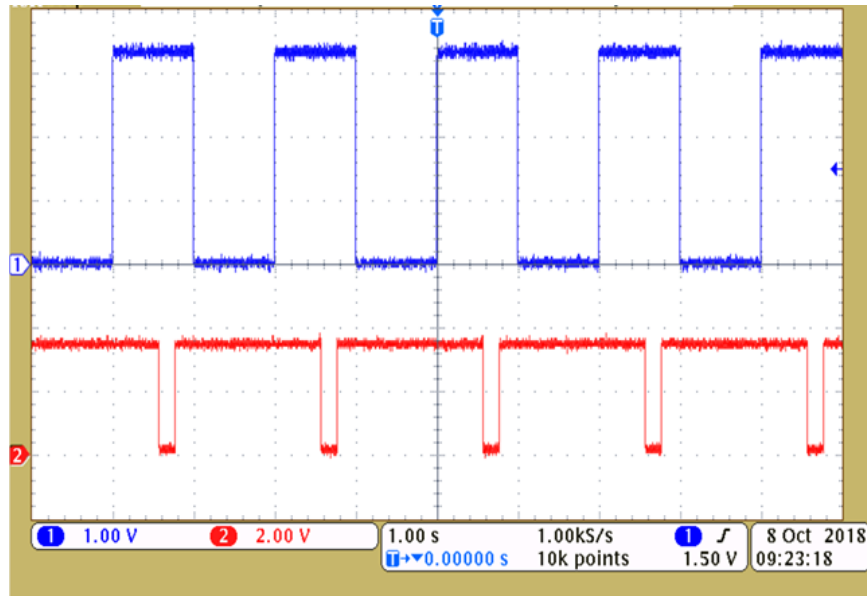


图 39. TPS3850-Q1 Watchdog Timer Late Detection 2000 ms Period

### 3.2.5 Voltage Reference Temperature Drift

Figure X shows the temperature drift of the LM4132-Q1 series voltage reference. See the [LM4132-Q1](#) datasheet for more information and bench characteristics. Depending on the ADC specifications and accuracy requirements, the [LM4128-Q1](#) or [REF34-Q1](#) may be a better fit.

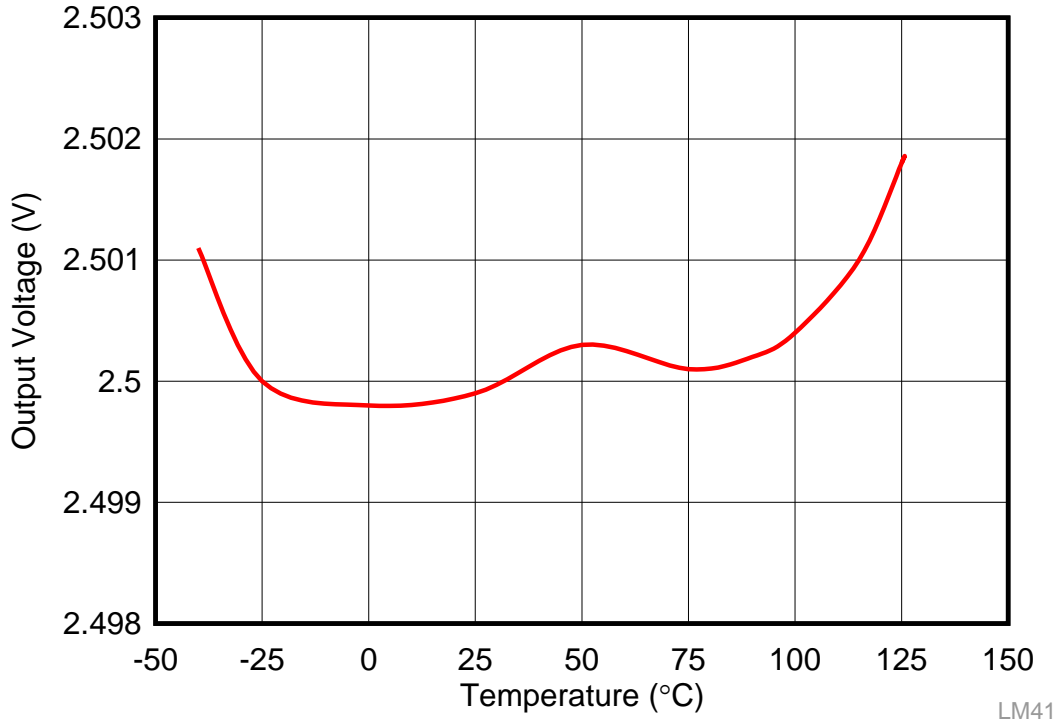


图 40. LM4132-Q1 Reference Voltage Temperature Drift



### 3.2.6 Thermal Images

图 41 through 图 44 shows the temperature rise of each supply on the board under full load conditions and with a 13.5-V input voltage after 10 minutes.

注: Board temperatures can exceed 55°C during operation.

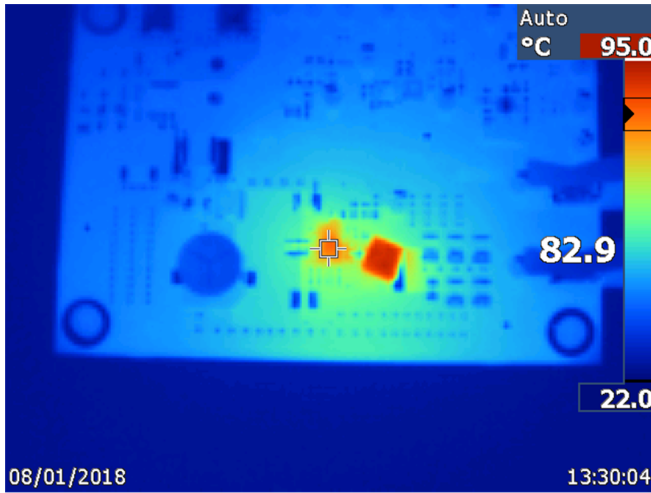


图 41. Thermal of LM73605-Q1 at 5-A Load

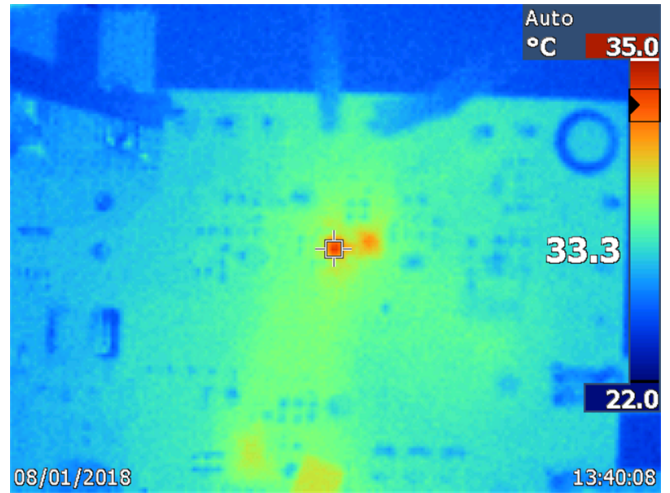


图 42. Thermal of TPS62065-Q1 at 1-A Load

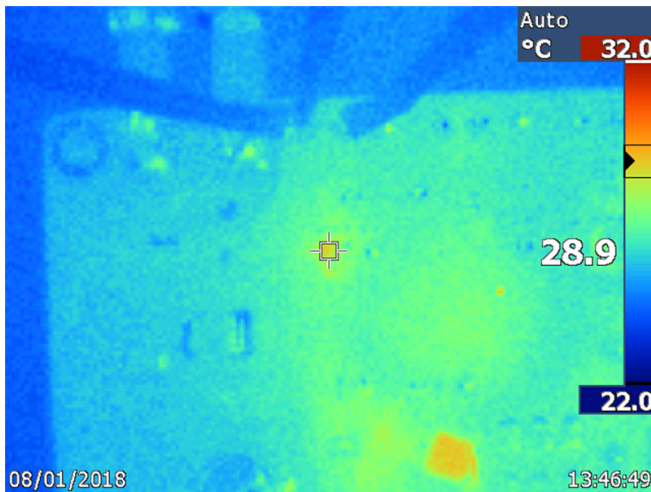


图 43. Thermal of TPS61240-Q1 at 200-mA Load

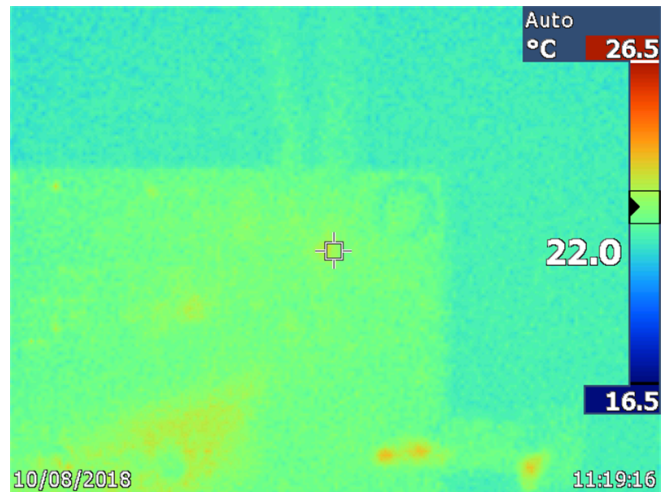


图 44. LM4132-Q1 at 20-mA Load

### 3.2.7 Electrical Transient Testing

The following transients were tested:

- Reverse battery
- Cold crank
- Warm crank
- Start-stop
- Start-up and shutdown

The following subsections show the waveforms of each rail during each condition.

#### 3.2.7.1 Reverse Battery

The following [图 45](#) shows that the input is disconnected during the reverse battery input voltage condition. Channel 1 (blue) is the input battery voltage that is connected to the source of the p-channel MOSFET and channel 2 (red) is connected to the drain of the P-FET and leads to the system EMI input filter and voltage input of the LM73605-Q1 wide vin buck converter.

The TLV1805-Q1 circuitry has been subjected to selected ISO 16750-2 and ISO 6737-2 waveforms for 12 V systems. The circuits survived with no performance degradation, and the load voltage did not exceed design limits. The circuit was tested on an evaluation module and does not imply full ISO certification of the board, or that the use of these circuits implies ISO certification of users end equipment. For more information, check the [TLV1805-Q1](#) product page and datasheet.

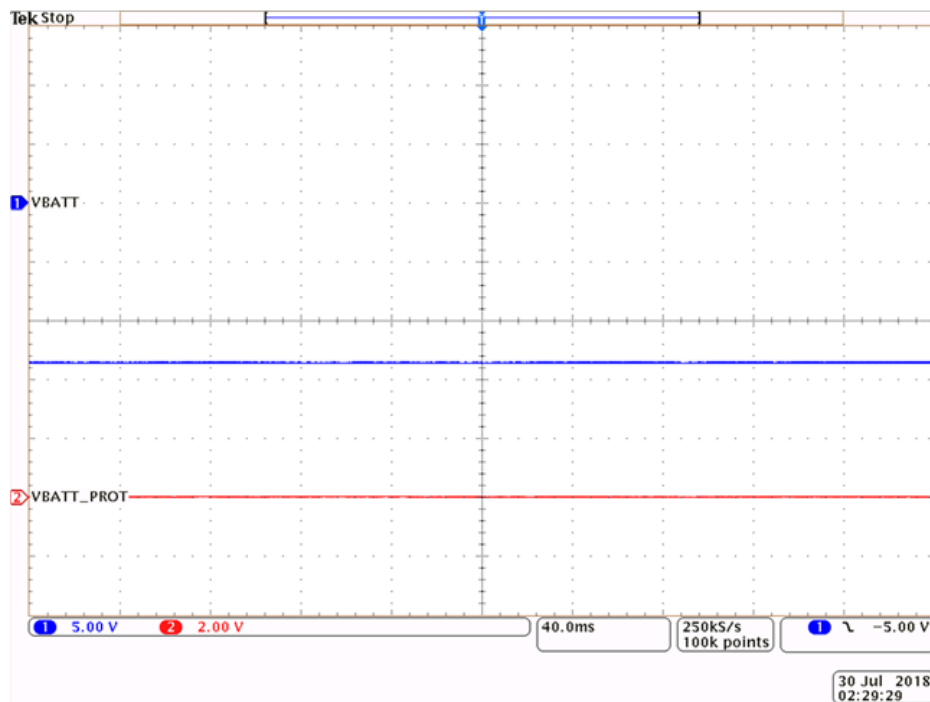


图 45. Continuous Reverse Voltage at Input

This behavior is expected from the TLV1805-Q1 comparator, where, upon a reverse voltage condition, the TLV1805-Q1 disconnects the MOSFET and prevents the reverse battery voltage from damaging the system components and board. 图 46 shows the transition to reverse input voltage. The input voltage after the P-FET remains undisturbed as the voltage at the input becomes increasingly negative.

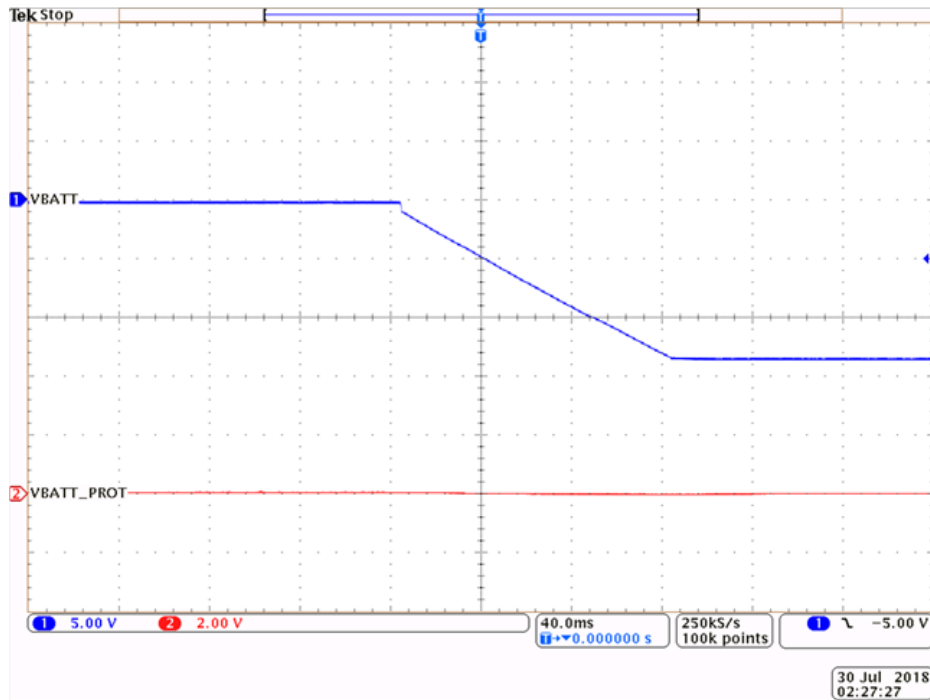


图 46. Transition to Reverse Voltage at Input

### 3.2.7.2 Cold Crank

Testing this design for a severe cold-crank condition was a key objective. This test was accomplished without using a pre-boost.

For the cold-crank test, the input voltage was allowed to fall to 3.5 V from the nominal 13.5 V. 图 47 shows the cold-crank waveform.

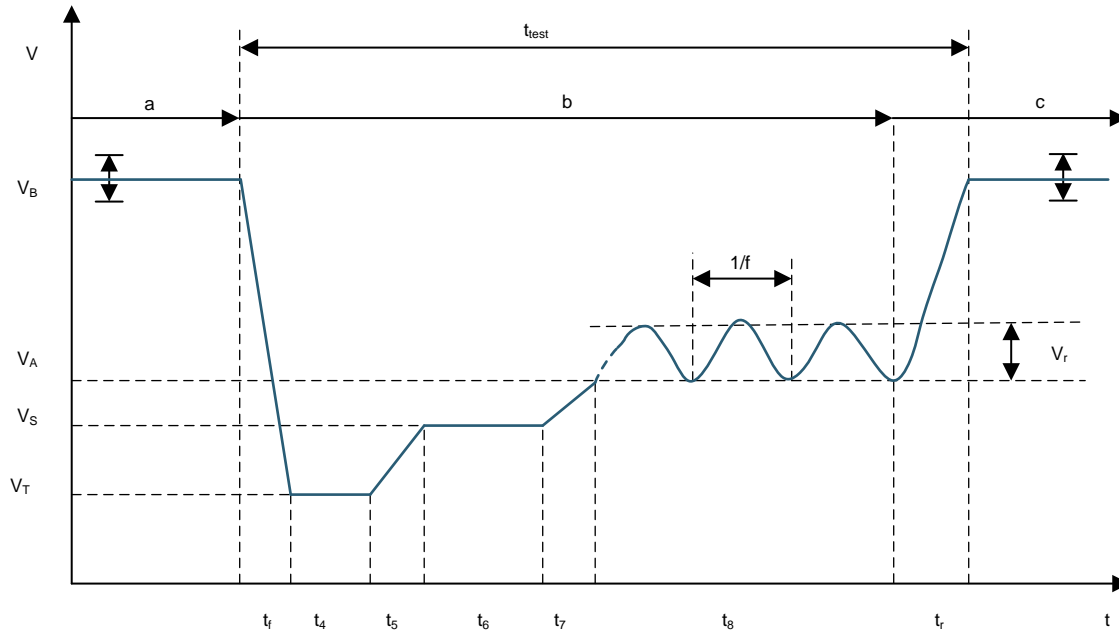


图 47. Cold-Crank Waveform and Parameters

表 2 list the cold-crank test pulse parameters.

表 2. Cold-Crank Test Pulse Parameters

PARAMETER	"NORMAL" TEST PULSE	"SEVERE" TEST PULSE
$V_B$	11.0 V	11.0 V
$V_T$	4.5 (0%, -4%)	3.2 V (0%, -4%)
$V_S$	4.5 (0%, -4%)	5.0 V (0%, -4%)
$V_A$	6.5 V (0%, -4%)	6.0 V (0%, -4%)
$V_R$	2 V	2 V
$t_f$	$\leq 1$ ms	$\leq 1$ ms
$t_4$	0 ms	19 ms
$t_5$	0 ms	$\leq 1$ ms
$t_6$	19 ms	329 ms
$t_7$	50 ms	50 ms
$t_8$	10 s	10 s
$t_r$	100 ms	100 ms
f	2 Hz	2 Hz

Only the severe test pulse was tested. The cold-crank condition lasts roughly 3s, after which it repeats. In 图 48, channel 1 (blue) shows the cold-crank input voltage waveform, channel 2 (red) shows the 3.3-V system-supply voltage output.

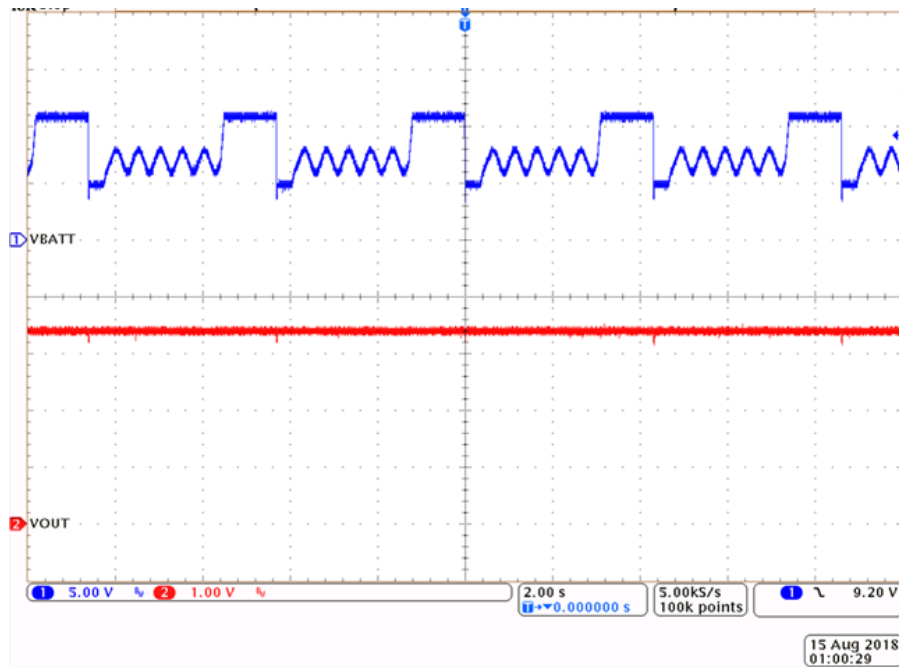


图 48. Cold Crank LM73605-Q1: 3.3 V at 5-A Output

图 49 shows the initial drop from 13.5 V to 3.5 V in a shorter timescale. The waveform shows the output voltage dips slightly, but is still within an operable voltage range. The dip is due to the forward voltage of the P-FET and EMI filter and dropout voltage of the LM73605-Q1.

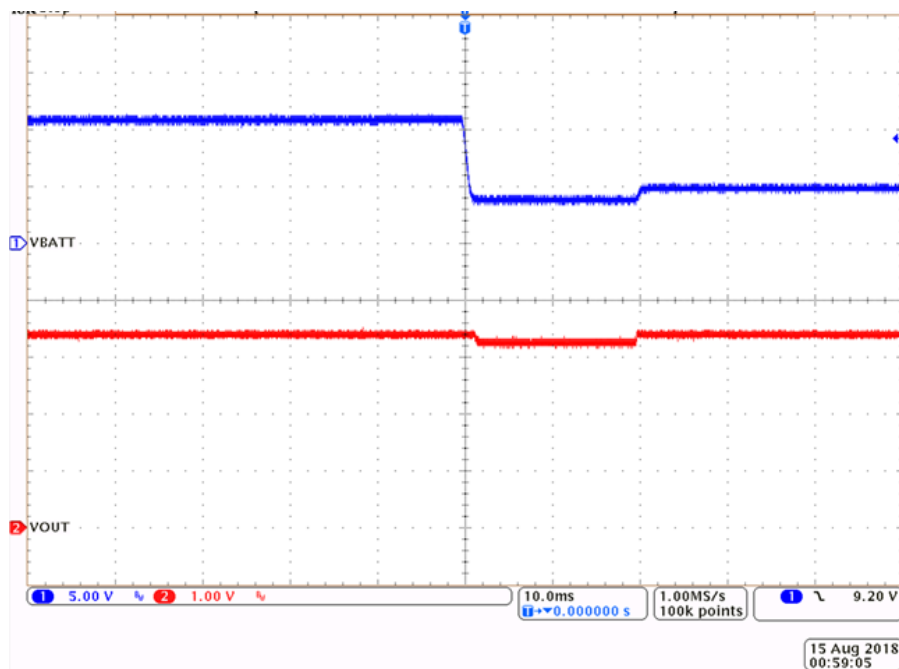


图 49. Cold Crank 10-ms Timescale, 3.3 V at 5-A Output

### 3.2.7.3 Warm Crank

This subsection provides test data for the main system supply during warm-crank conditions. In 图 50 and 图 51, channel 1 (blue) measures the warm-crank input voltage waveform, channel 2 (red) measures the 3.3-V main system supply.

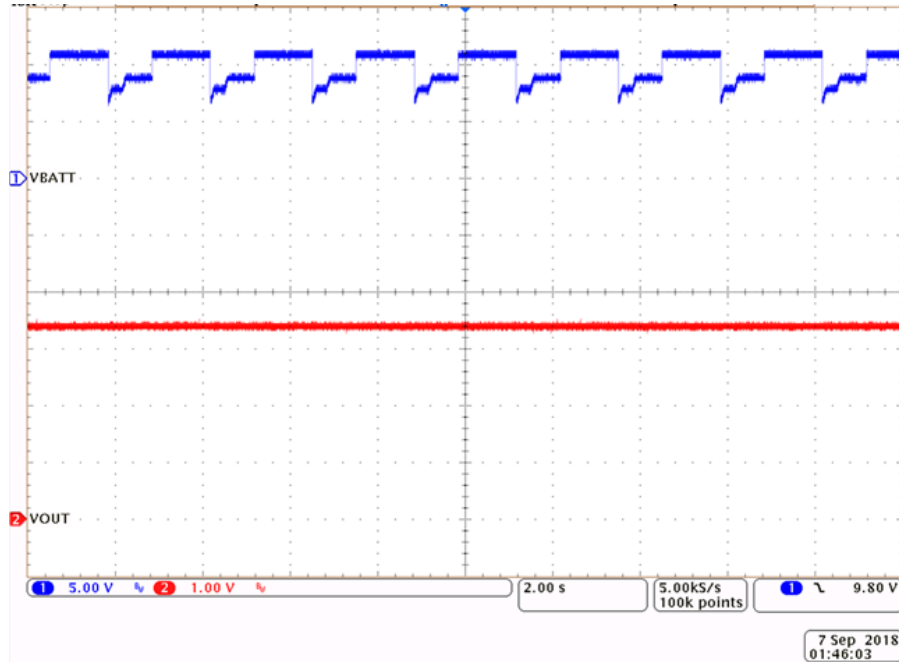


图 50. Warm Crank LM73605–Q1: 3.3 V at 5-A Output



图 51. Warm Crank 40-ms Timescale, 3.3 V at 5-A Output

### 3.2.7.4 Start-Stop

This subsection provides test data for the main system supply rail during start-stop conditions. In [图 52](#) and [图 53](#), channel 1 (blue) measures the start-stop input voltage waveform, channel 2 (red) measures the 3.3-V main system supply.

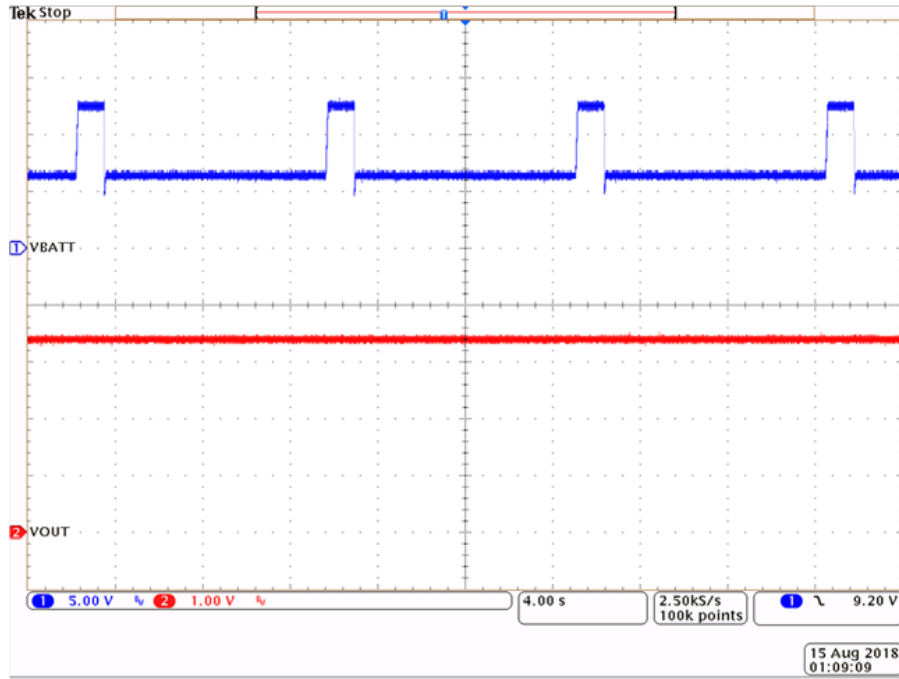


图 52. Start-Stop LM73605-Q1: 3.3 V at 5-A Output

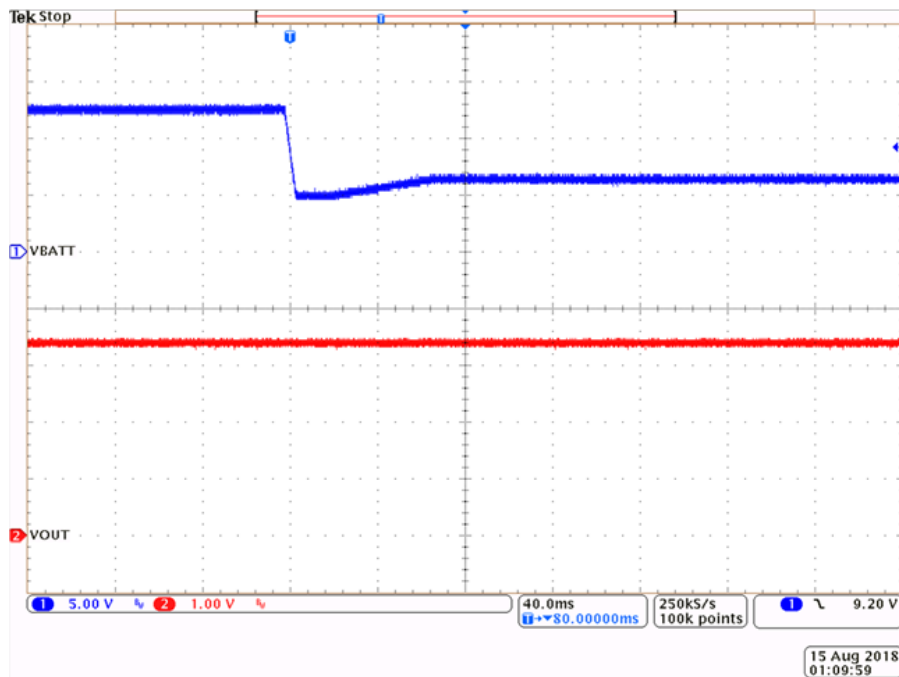


图 53. Start-Stop 40-ms Timescale, 3.3 V at 5-A Output

### 3.2.7.5 Start-Up and Shutdown

This subsection provides test data for the system-voltage (I/O), core-voltage, and CAN during system start-up and shutdown. Measurements were taken at full and no loads of the LM73605-Q1. Waveforms in 图 54 and 图 55 shows start-up behaviors. Waveforms in 图 56 and 图 57 shows shutdown behaviors.

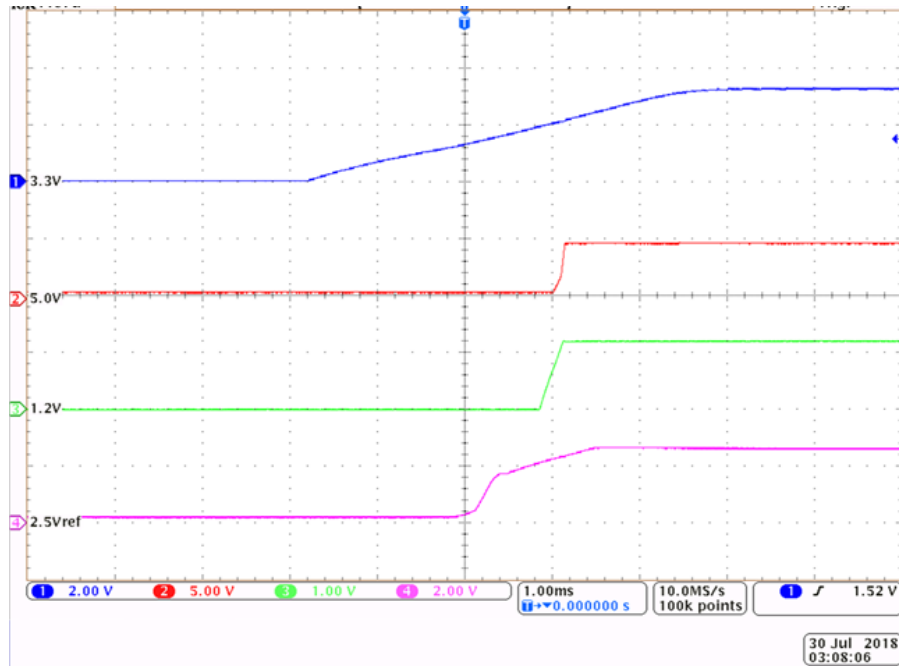


图 54. No Load Start-Up

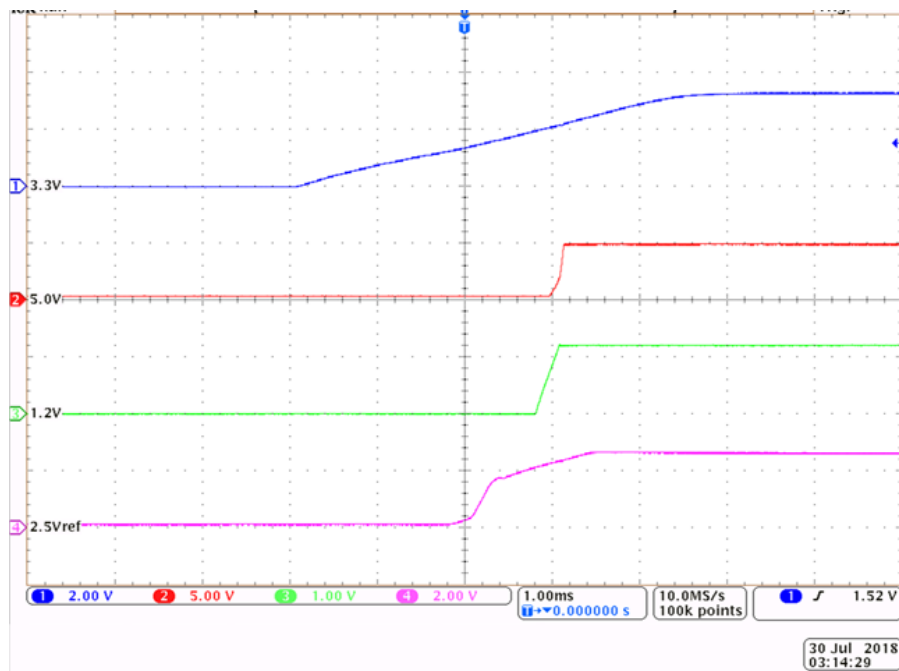


图 55. Full Load Start-Up



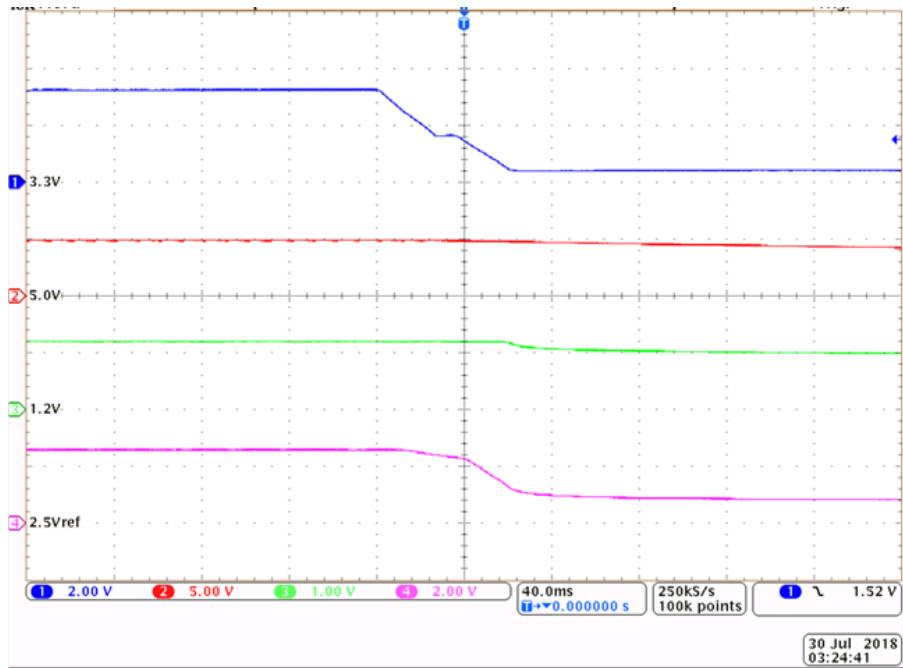


图 56. No Load Shutdown

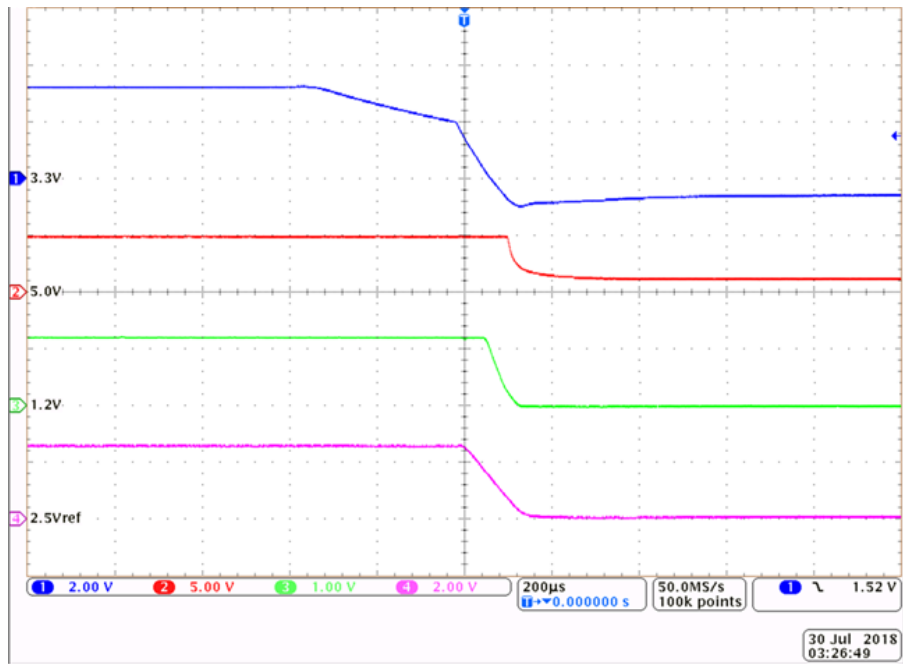


图 57. Full Load Shutdown

### 3.2.8 Conducted Emissions

The conducted emissions of the TIDA-050008 have been tested according to CISPR 25 Class 5 limit lines. The examined frequency band spans from 150 kHz to 108 MHz covering the AM-FM radio bands, very-high-frequency (VHF) band, and TV band specified in CISPR 25.

图 58 和 图 59 显示测试结果。限制线（显示为红色）是 CISPR 25 中规定的 Class 5 传导骚扰限值。黄色迹线（峰值检测器测量）和蓝色迹线（平均检测器测量）是测量结果。


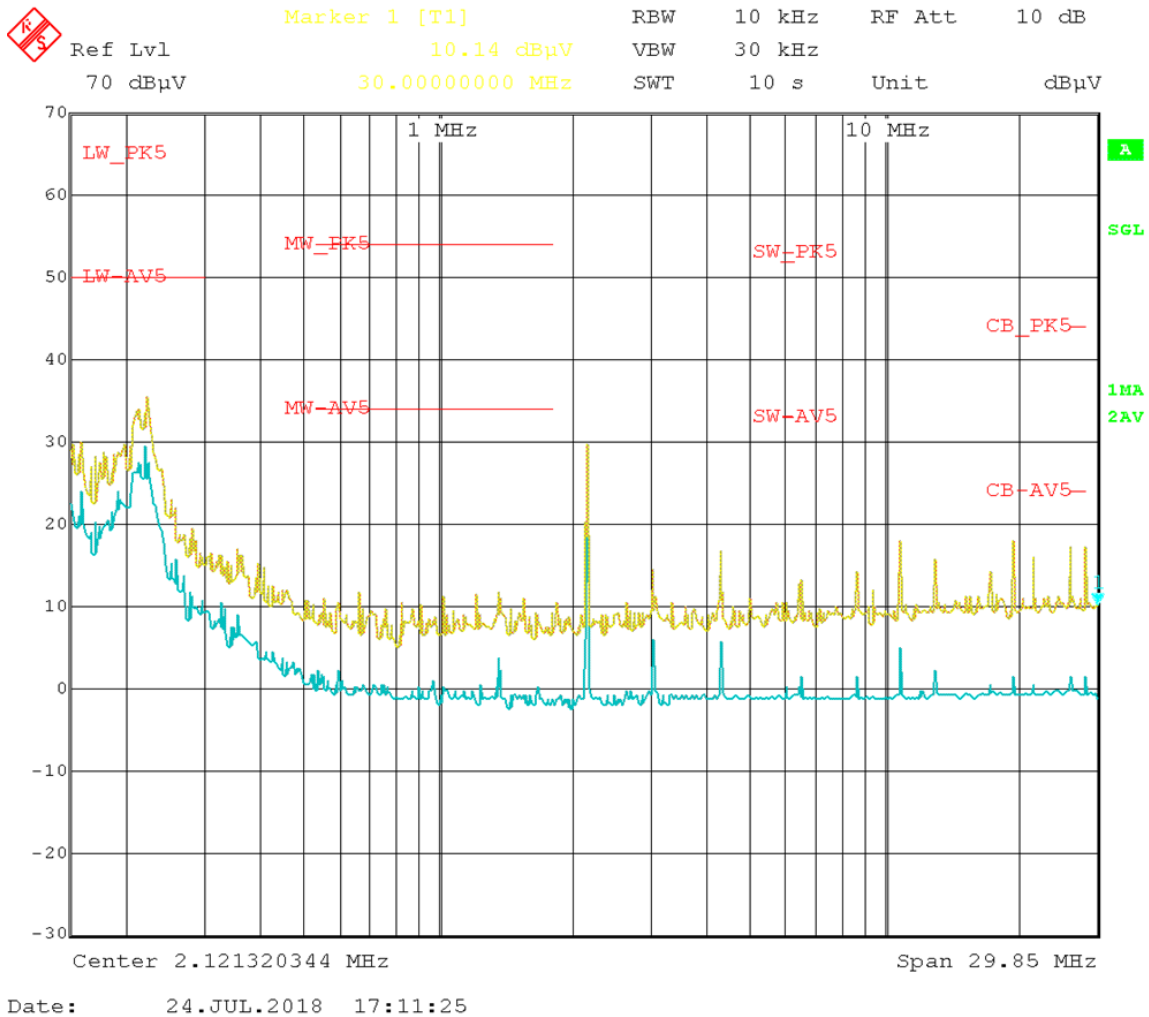


图 58. 150-kHz 到 30-MHz 传导发射—峰值和平均检测

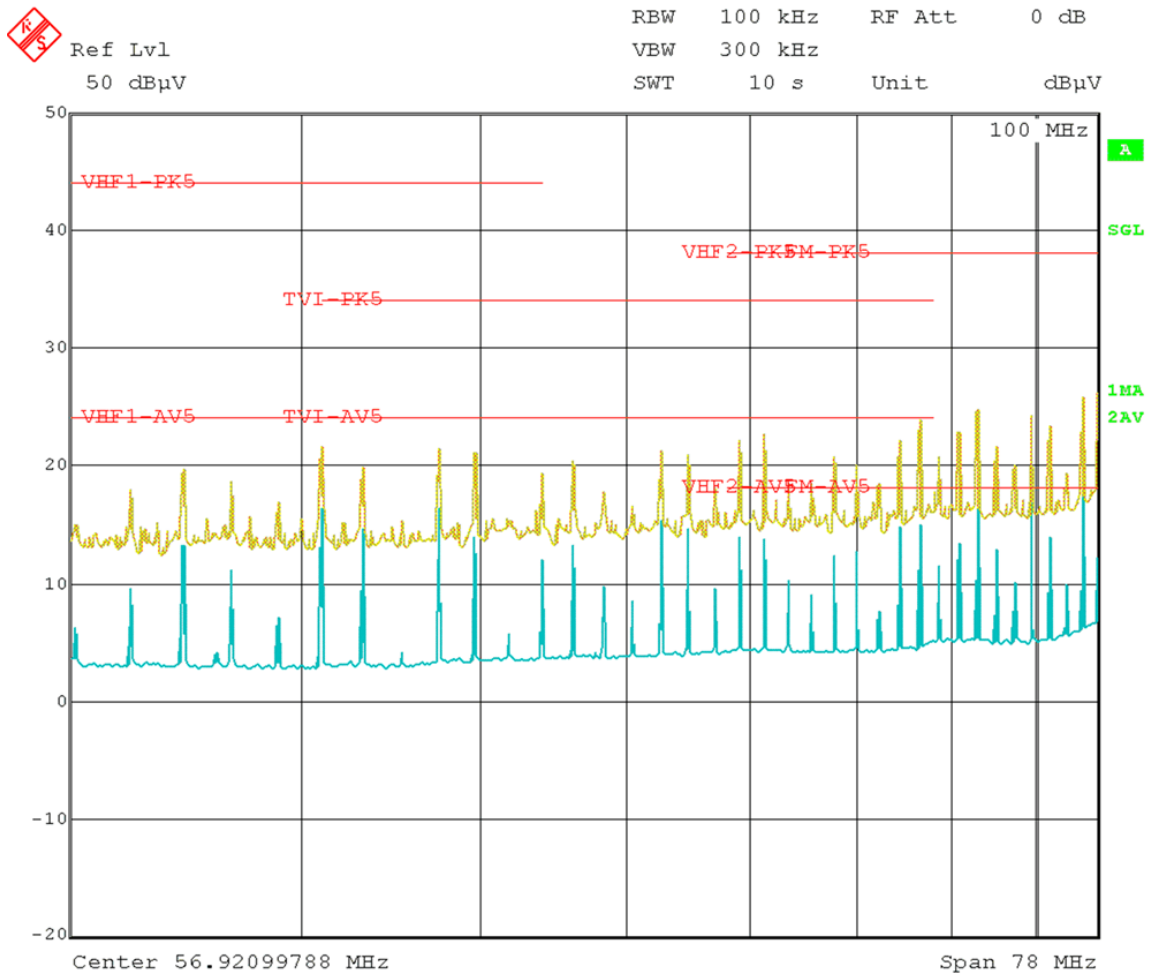

Date: 24.JUL.2018 17:14:33

图 59. 30-MHz to 108-MHz Conducted Emissions—Peak and Average Detection

The conducted emissions were tested using the setup shown in 图 60. The test setup uses 3, 2- $\Omega$  load resistors in parallel and covered with copper tape. The load resistors are directly connected to the output terminal copper pads of the LM73605-Q1 device.

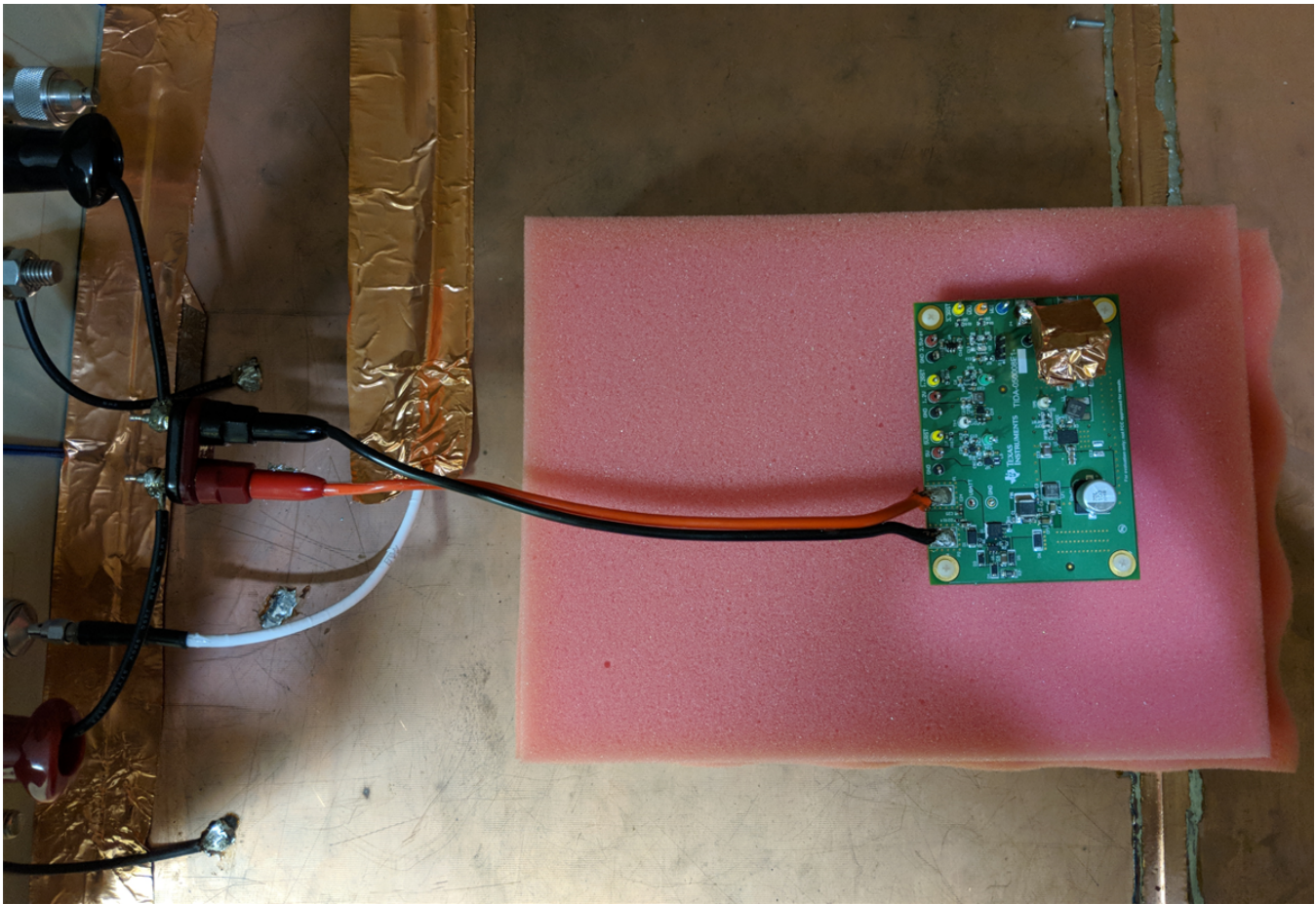


图 60. Setup for EMI Testing

## 4 Design Files

### 4.1 Schematics

To download the schematics for the board, see the design files at [TIDA-050008](#).

### 4.2 Bill of Materials

To download the bill of materials for the board, see the design files at [TIDA-050008](#).

### 4.3 Altium Project

To download the Altium Designer® project for the board, see the design files at [TIDA-050008](#).

### 4.4 Gerber Files

To download the Gerber Files for the board, see the design files at [TIDA-050008](#).

### 4.5 Assembly Drawings

To download the assembly drawings for the board, see the design files at [TIDA-050008](#).

### 4.6 PCB Layout Recommendations

#### 4.6.1 Input Protection Circuitry

Place input protection circuitry as close to the battery terminal inputs as possible, rather than close to the downstream circuit it is protecting, to reduce the inductance of the path. This placement allows the TVS diodes to react as quick as possible to any transients. Close placement provides a tight loop for the return path back to the battery terminals while the TVS diodes shunt a transient event. In the event of a reverse polarity event, the FET Q1 quickly shuts off, possibly causing inductive kicks due to the interrupted current flow. The severity of this kick is a function of the inductance and, therefore, the length and width of the power path.

#### 4.6.2 Input EMI Filter Considerations

The goal of the EMI filter is to minimize emissions, especially conducted emissions. The key to minimizing emissions is providing low impedance paths to quickly ground high-frequency noise, which is typically accomplished by containing high-frequency current loops. 图 61 shows the current flow through the EMI filter. The DC is outlined in red and the high-frequency AC paths are outlined in blue.

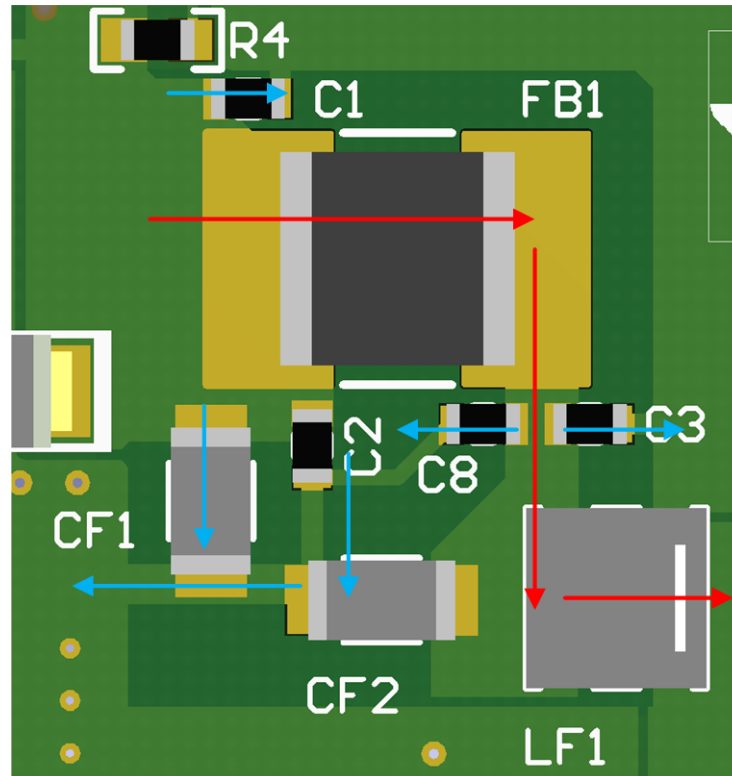


图 61. Input EMI Filter

Conducted emissions are mainly due to high-frequency noise that input capacitors cannot bypass. This noise is conducted onto the input leads of the supply, which drives the convention that the higher-frequency AC flows away from the 3.3-V supply back toward the system supply.

The previous 图 61 shows the smaller 0.1- $\mu\text{F}$  capacitors C3 and C8 close to the 2.2- $\mu\text{H}$  inductor LF1 to filter out the high-frequency noise not attenuated by the inductor. Capacitors C3 and C8 are placed across from each other instead of next to each other to minimize the possibility of inductive coupling during operation due to their close proximity.

Inductors behave capacitively above their resonant frequency; therefore, any frequencies above this are not attenuated. The amount of noise that is injected back onto the supply line directly depends on how much has been filtered out; therefore, the smallest path to ground for high-frequency noise is required.

### 4.6.3 Noise-Sensitive Traces and Components

The feedback (FB) nodes of power supplies are especially high impedance and thus susceptible to picking up noise. These nodes are critical to operate the control loop of the device; therefore, poor placement and routing of these components or traces can affect the performance of the device and system by introducing unwanted parasitic inductances and capacitances.

The switch node of DC-DC converters are typically very noisy. The switch node can radiate a significant amount of energy and can couple noise into sensitive lines. Traces for the switch node must be wide enough for the maximum current but small enough to minimize radiation. Signals like output voltage FB traces for power supplies are high-impedance lines. These signals are quite sensitive to disturbances, especially to noise from switch nodes and high-bandwidth I<sup>2</sup>C lines. The FB line must be routed away from noisy components and traces such as the switch node.

The TIDA-050008 layout in 图 62 shows the current flow and FB for the main 3.3-V supply at the PCB level. The 3.3-V output voltage is sensed and fed back to the supply far enough from the switch node and high-frequency noise path to avoid noise coupling. Note resistor R20 is only populated for supervision test since connecting a floating test point to the FB pin is not ideal.

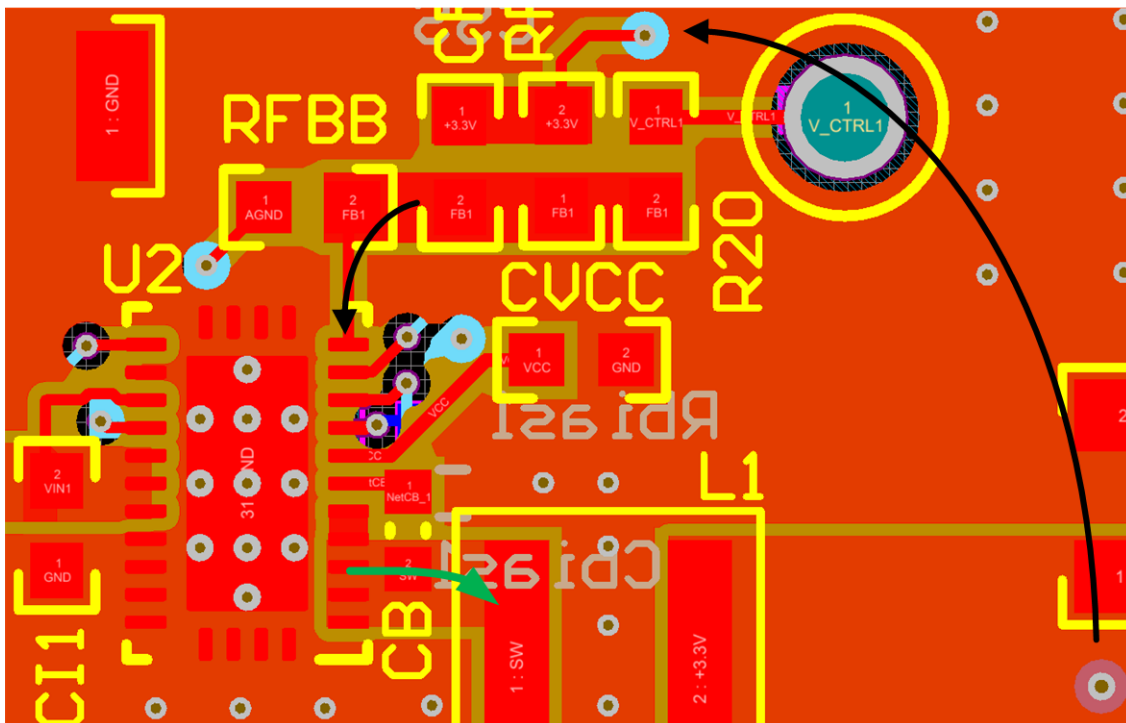


图 62. 3.3-V Supply Component and Node Placement

Create a separate analog ground for the feedback resistor network and net-tie it to the device thermal pad land of the PCB as a star point. Use common power PGND node and a different node for the signal AGND to minimize the effects of ground noise. In 图 63, the red layer is the top layer and the light blue is the third layer, which contains the 3.3-V plane, analog ground plane, and several other signals and nodes. The black arrows show the current flow from the output through the feedback network to the dedicated analog ground plane connected to the GND thermal pad as the star point. The 3.3-V output voltage is sensed in the third layer of the board where the 3.3-V rail is quiet and distributed to the rest of the system.


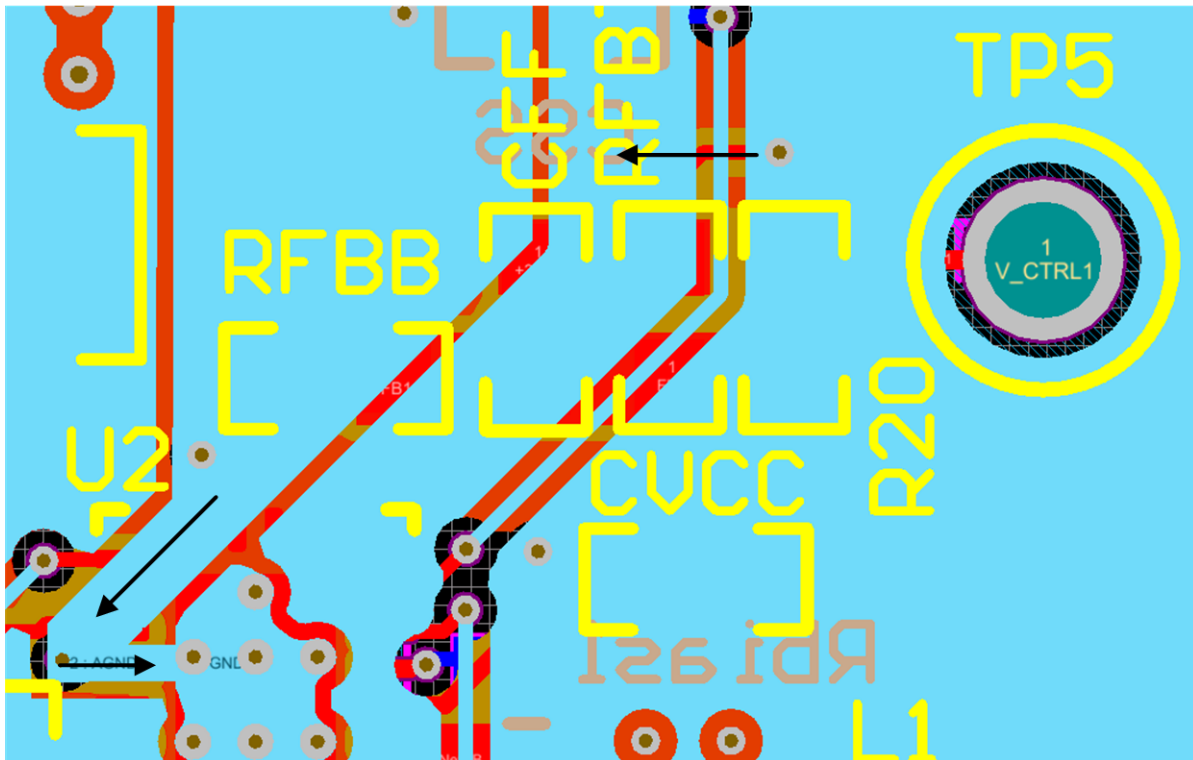


图 63. 3.3-V Output and Feedback Network

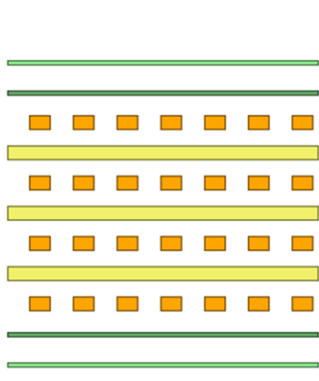

#### 4.6.4 PCB Layering Recommendations

This reference design uses a four-layer board. Layer 2 is used as a dedicated ground plane. Layer 3 is used for the 3.3V power plane to provide power to the rest of the board. It is also used as a signal layer for certain routing circumstances. If using a six-layer board, make layers 2 and 5 ground planes to shield the internal signal layers from outside noise sources as well as the switch nodes found on the top layer. [图 64](#) details the stack-up used in this reference design.



Layer Name	Type	Material	Thickness (mil)	Dielectric Material	Dielectric Constant
Top Overlay	Overlay				
Top Solder	Solder Mask/Co...	Surface Material	0.4	Solder Resist	3.5
Top Layer	Signal	Copper	2.8		
Dielectric 2	Dielectric	Core	10	FR-4	4.2
Signal Layer 1	Signal	Copper	1.4		
Dielectric 3	Dielectric	Core	10	FR-4	4.2
Signal Layer 2	Signal	Copper	1.4		
Dielectric1	Dielectric	Core	10	FR-4	4.2
Bottom Layer	Signal	Copper	2.8		
Bottom Solder	Solder Mask/Co...	Surface Material	0.4	Solder Resist	3.5
Bottom Overlay	Overlay				

**图 64. Layer Stack-Up With GND Planes Separating Signal Layers**

Keep power traces and pours on the same layer as much as routing requirements allow. This grouping minimizes the inductance of the path and reduces noise coupling between planes. Unfortunately, due to the high number of rails in this reference design and the routing requirements required to get signals to the EVM connectors, sticking to this rule is not totally possible.

## 5 Related Documentation

1. Texas Instruments, [LM73605/LM73606 3.5-V to 36-V, 5-A or 6-A Synchronous Step-Down Voltage Converter](#)
2. Texas Instruments, [TLV1805-Q1 Push-Pull High Voltage Comparator](#)
3. Texas Instruments, [TPS3703-Q1 High-Accuracy Window Supervisor](#)
4. Texas Instruments, [TPS3850-Q1 Precision Voltage Supervisor with Programmable Window Watchdog Timer](#)
5. Texas Instruments, [TPS3890-Q1 Low Quiescent Current Precision Supervisor](#)
6. Texas Instruments, [AN-2155 Layout Tips for EMI Reduction in DC/DC Converters](#)

### 5.1 商标

Altium Designer is a registered trademark of Altium LLC.  
All other trademarks are the property of their respective owners.

## 重要声明和免责声明

TI 均以“原样”提供技术性 & 可靠性数据（包括数据表）、设计资源（包括参考设计）、应用或其他设计建议、网络工具、安全信息和其他资源，不保证其中不含任何瑕疵，且不做任何明示或暗示的担保，包括但不限于对适销性、适合某特定用途或不侵犯任何第三方知识产权的暗示担保。

所述资源可供专业开发人员应用 TI 产品进行设计使用。您将对以下行为独自承担全部责任：(1) 针对您的应用选择合适的 TI 产品；(2) 设计、验证并测试您的应用；(3) 确保您的应用满足相应标准以及任何其他安全、安保或其他要求。所述资源如有变更，恕不另行通知。TI 对您使用所述资源的授权仅限于开发资源所涉及 TI 产品的相关应用。除此之外不得复制或展示所述资源，也不提供其它 TI 或任何第三方的知识产权授权许可。如因使用所述资源而产生任何索赔、赔偿、成本、损失及债务等，TI 对此概不负责，并且您须赔偿由此对 TI 及其代表造成的损害。

TI 所提供产品均受 TI 的销售条款 (<http://www.ti.com.cn/zh-cn/legal/termsofsale.html>) 以及 [ti.com.cn](http://www.ti.com.cn) 上或随附 TI 产品提供的其他可适用条款的约束。TI 提供所述资源并不扩展或以其他方式更改 TI 针对 TI 产品所发布的可适用的担保范围或担保免责声明。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2018 德州仪器半导体技术（上海）有限公司

## 重要声明和免责声明

TI 均以“原样”提供技术性 & 可靠性数据（包括数据表）、设计资源（包括参考设计）、应用或其他设计建议、网络工具、安全信息和其他资源，不保证其中不含任何瑕疵，且不做任何明示或暗示的担保，包括但不限于对适销性、适合某特定用途或不侵犯任何第三方知识产权的暗示担保。

所述资源可供专业开发人员应用 TI 产品进行设计使用。您将对以下行为独自承担全部责任：(1) 针对您的应用选择合适的 TI 产品；(2) 设计、验证并测试您的应用；(3) 确保您的应用满足相应标准以及任何其他安全、安保或其他要求。所述资源如有变更，恕不另行通知。TI 对您使用所述资源的授权仅限于开发资源所涉及 TI 产品的相关应用。除此之外不得复制或展示所述资源，也不提供其它 TI 或任何第三方的知识产权授权许可。如因使用所述资源而产生任何索赔、赔偿、成本、损失及债务等，TI 对此概不负责，并且您须赔偿由此对 TI 及其代表造成的损害。

TI 所提供产品均受 TI 的销售条款 (<http://www.ti.com.cn/zh-cn/legal/termsofsale.html>) 以及 [ti.com.cn](http://www.ti.com.cn) 上或随附 TI 产品提供的其他可适用条款的约束。TI 提供所述资源并不扩展或以其他方式更改 TI 针对 TI 产品所发布的可适用的担保范围或担保免责声明。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2018 德州仪器半导体技术（上海）有限公司