

# TI Designs: TIDA-050018

## 多目的センサ用の低消費電力、スタンバイ時電力6μA、単4電池のリファレンス・デザイン



### 概要

このリファレンス・デザインでは、ドアや窓のセンサに使用される、低消費電力の昇圧コンバータ・ソリューションを紹介いたします。このデザインにはアルカリ電池、静止電流の非常に低い昇圧コンバータ、超低消費電力のデジタル・ホール・エフェクト・センサが含まれます。このデザインは、センサのステータスを送信するため使用される、超低消費電力、Sub-1GHzワイヤレス・マイクロコントローラに給電することもできます。

### リソース


<a href="#">TIDA-050018</a>	デザイン・フォルダ
<a href="#">TPS61098</a>	プロダクト・フォルダ
<a href="#">DRV5032</a>	プロダクト・フォルダ
<a href="#">TIDA-01066</a>	デザイン・フォルダ

### 特長



- アルカリ電池から給電
- IQが非常に低い(300nA)昇圧コンバータ
- ノイズに敏感な負荷向けの内蔵LDO
- 磁界検出が常時オンで、継続的な監視が可能
- デュアル・センサ・アーキテクチャで磁気改ざんを検出

### アプリケーション

- ビルディング・オートメーション
- ドアや窓のセンサ
- ホーム・リモート・コントロール



[E2E™ エキスパートに質問](#)

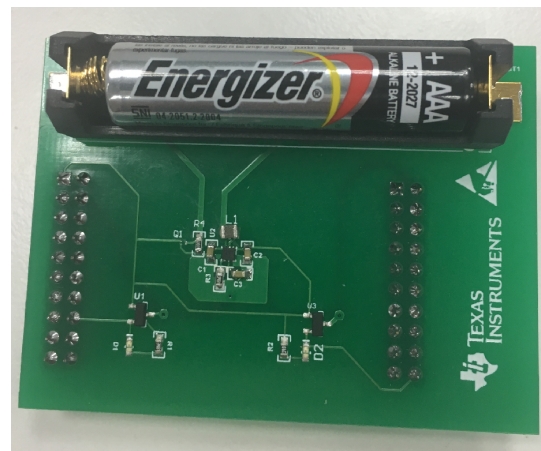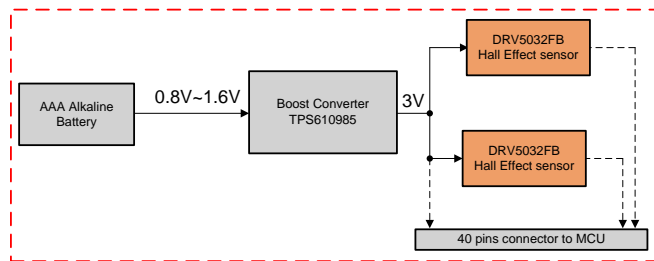

使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE (重要な注意事項)をご参照くださいますようお願いいたします。

# 1 System Description

Many industrial and building automation systems use sensors to monitor whether the doors and windows are opened or closed. A central monitoring device generates alarms based on the information from multiple door and window sensors. These systems require wireless sensor nodes to reduce installation costs and to make the systems more flexible for future expansion. The wireless sensor node is powered by a battery, the voltage of which depends on the battery type and the remaining capacity. For example, the voltage of an alkaline battery varies from 1.5 V to 0.8 V in its operating lifetime. Magnets are commonly used in window and door sensor node to determine if a window or door is opened or closed. In a typical configuration the magnet is embedded in the window or door, and the sensor is attached to the window or door frame. The sensor and magnet are placed so that they are in close proximity when the door or window is closed and away from each other when the window or door is opened. Texas Instruments' ultra-low-power digital Hall effect sensors are designed for such applications. Besides magnets, shock sensors can be also used to detect the motion of the door or window. The power supply for the Hall effect sensors is at least 1.8 V, thus an ultra-low IQ boost converter is required if the system is supplied by an alkaline battery. The output of the boost converter also provides stable voltage to the ultra-low-power wireless microcontroller (MCU). The wireless MCU is required to transmit the sensor status to the central monitoring device.

This reference design includes an alkaline battery, an ultra-low IQ boost converter, and two ultra-low-power digital Hall effect sensors. The reference design can be connected with the CC1310 LaunchPad™ through two receptacles to demonstrate the wireless communication function in the security system.

## 1.1 Key System Specifications


表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Input power source	AAA alkaline battery, voltage from 1.6 V to 0.8 V
Output voltage of the boost	3 V
Output current capability of the boost	90 mA at 1.2-V battery voltage
Sensor sampling frequency	5 Hz
Sensor type	Hall effect
Average standby current consumption	6 $\mu$ A at 25°C room temperature

# 2 System Overview

## 2.1 Block Diagram

図 1. TIDA-050018 Block Diagram

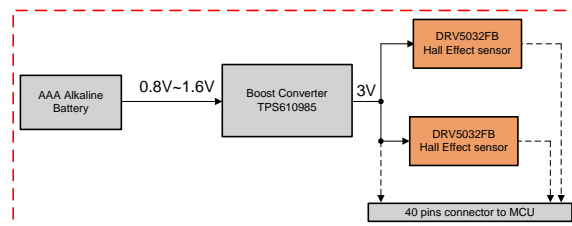

## 2.2 Highlighted Products

This TI Design features the following devices:

- TPS61098 ultra-low quiescent current synchronous boost with integrated LDO or load switch
- DRV5032 ultra-low power digital-switch Hall effect sensor

The 40-pin connector enables the board attaching to a wireless MCU CC1310 launch pad. More information about configuration of the wireless MCU can be found in the reference design [Low Power Door/Window Sensor with Sub-1GHz and 10-Year Battery Life Design Guide](#).

### 2.2.1 TPS610985

TPS610985 is an ultra-low quiescent-current synchronous boost. It integrates a LDO or low switch depend on the version. the device has two operation modes controlled by MODE pin: active mode and low-power mode. In active mode, both outputs are enabled with enhanced response performance. In low-power mode, the LDO or load switch is disabled to disconnect the peripheral components. The TPS61098x consumes only 300-nA quiescent current and can achieve up to 88% efficiency at 10- $\mu$ A load in low-power mode. The TPS61098x can provide up to 50-mA total output current at 0.7-V input to 3.3-V output conversion. The TPS610985 device is based on a hysteretic current controller topology, and it integrates synchronous rectifier to obtain maximum efficiency. The TPS61098x is available in 1.5-mm  $\times$  1.5-mm WSON package to enable small circuit layout size.

### 2.2.2 DRV5032

The DRV5032 is an ultra-low-power digital switch Hall effect sensor, designed for the most compact and battery-sensitive systems. The device is offered in multiple magnetic sensitivities, sampling rates, output drivers, and packages to accommodate various applications.

When the applied magnetic flux density exceeds the  $B_{OP}$  threshold, a device output drives a low voltage. The output stays low until the flux density decreases to less than  $B_{RP}$ , and then the output either becomes high-impedance or drives a high voltage, depending on the device version. By incorporating an internal oscillator, the DRV5032 samples the magnetic field and updates the output at a rate of 20 Hz, or 5 Hz for the lowest current consumption. Both omnipolar and unipolar magnetic responses are available. The features of DRV5032 include:

- Industry-leading ultra-low power consumption
- 1.65-V to 5.5-V operating range
- Omnipolar or unipolar magnetic response
- 20-Hz and 5-Hz sample rate options
- SOT-23 or small SON package

In the DRV5032 product folder, there is a *magnetic field calculator* as shown in [Figure 2](#). For the NdFeB grade-38 6-mm cylinder magnet components, the distance toggling the signal in OUT is approximately 20 mm.

### 図 2. Magnetic Field Calculator

Magnetic Field Calculator


Magnet Material: NdFeB - Grade 38

Remanence (Br): 12400 Gauss

Magnet Shape:  Rectangle  Cylinder

Diameter: 6 mm

Thickness: 6

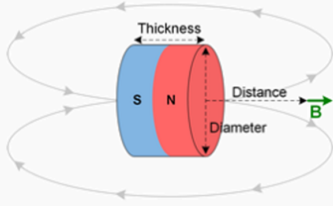

DRV5032 Version	Distance of max-B <sub>OP</sub>	Distance of min-B <sub>RP</sub>
DRV5032DU	17.55 mm	30.38 mm
DRV5032FA	16.17 mm	37.69 mm
DRV5032FB	16.17 mm	37.69 mm


## 2.3 System Design Theory

The designed circuit can be divided into boost converter power solution and the Hall effect sensor circuit.

### 2.3.1 Power Supply Design

The circuit of the boost converter is shown in 図 3. The TPS610985 requires three components to generate 3 V from an alkaline battery input: input capacitor, inductor, and output capacitor. For this application, it is sufficient to have 10- $\mu$ F ceramic capacitor for the input and output. The inductor is 4.7  $\mu$ H with at least 400-mA current capability. For TPS610985, there is a switcher between the VMAIN and VSUB. When MODE pin is logic low, the switcher is off, so there is no voltage in the VSUB. When MODE pin is logic high, the switching is on, so the VSUB voltage follows the voltage of VMAIN. The VSUB can be used to power the loading, which consumes lots of energy but is not frequently powered up. Because the device consumes more quiescent current when MODE is high, the VSUB should be turned off for most of the time.

図 3. Boost Converter Schematic

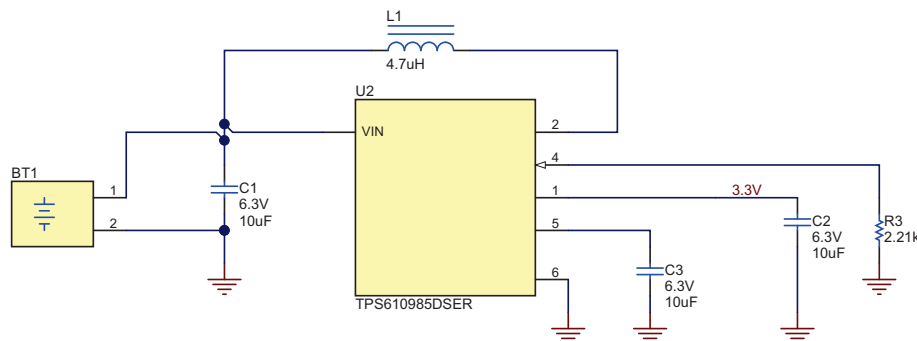




### 2.3.2 Hall Effect Sensor Design

The external circuit is shown in [Figure 4](#). The power supply is 3 V. The LED indicates the changing of the magnetic field. If the magnetic field is higher than typical 3 mT, the OUT pin output logic is low, and the LED D2 turns on. The OUT pin becomes logic high again if the magnetic field is lower than typical 1.5 mT.

**Figure 4. Hall Effect Sensor Circuit**

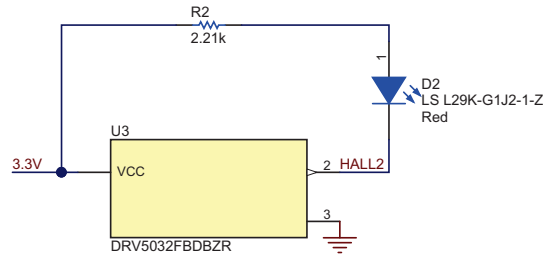

## 3 Test Results

The following shows the test results of this reference design. During the measurement, the power source can be electronic power supply or an alkaline battery.

### 3.1 Standby Current Consumption

[Table 2](#) shows the standby input current of the reference design at different input voltages. The input current is approximately 6  $\mu\text{A}$  from typical 1.2-V battery voltage.

**Table 2. Standby Input Current**

PARAMETER	BATTERY OUTPUT CURRENT AT DIFFERENT VOLTAGE							
Battery voltage (V)	0.8	0.9	1	1.1	1.2	1.3	1.4	1.5
Standby current ( $\mu\text{A}$ )	10	8.4	7.3	6.4	5.7	5.2	4.8	4.3

### 3.2 Boost Converter Operating Waveform

In standby condition, the TPS610981 operates at burst mode as the loading is very small. In the burst mode, the device switches several cycles to ramp up the  $V_{\text{OUT}}$ , and then most of the internal circuit shuts down to reduce power loss. After the output voltage decreases to a threshold, the device starts to switch again. The output ripple is approximately 20 mV shown in

図 5. Boost Converter Output Ripple at Standby Mode

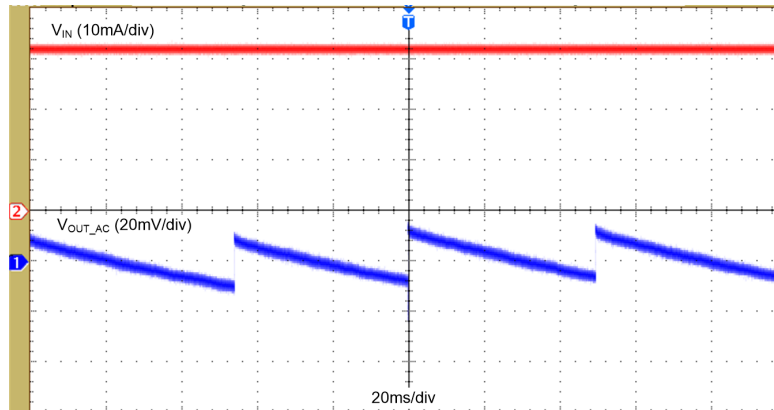


図 6 and 図 7 show the load transient performance of the TPS610981. When the output current is zero, the device operates at burst mode. The average output voltage is approximately 3.1 V at burst mode, which is 100 mV higher than setting 3-V output because the internal circuit of the device needs the extra 100 mV to enter or exit the burst mode. After the loading increases to 10 mA or 50 mA, the device exits the burst mode. The output voltage is regulated at 3 V.

図 6. Boost Load Transient From 0 mA to 10 mA


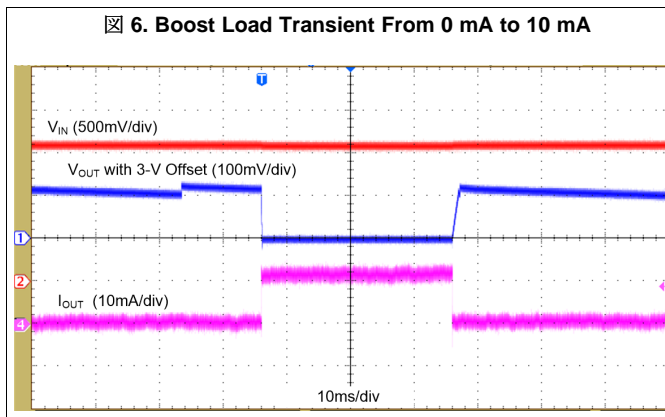



図 7. Boost Load Transient From 0 mA to 50 mA

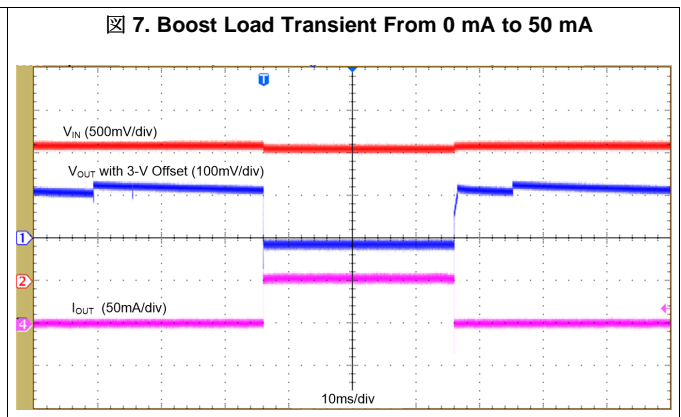


### 3.3 Magnet Response

In 図 8, a cylindrical magnet (6-mm diameter and 6-mm height) is placed on the top of the Hall effect sensor DRV5032. if the distance between the sensor and the magnet is shorter than approximately 16 mm, the sensor outputs logic low and turns on the red LED. if the distance is longer than approximately 22 mm, the sensor outputs high logic and turns off the LED. In 図 9, the magnet is placed closer, so both the sensors output logic low to indicate the tampering magnet.

☒ 8. Magnetic Field Test

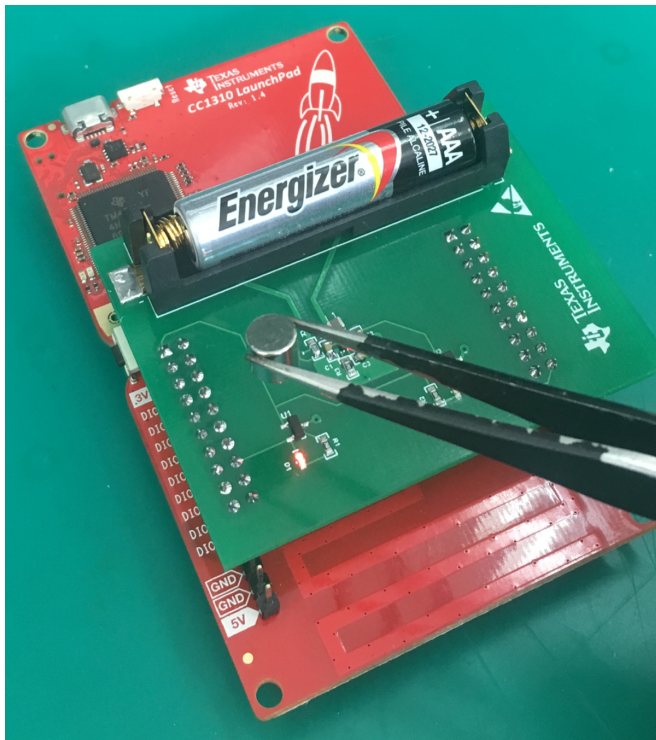

☒ 9. Magnetic Field Test (Close Up)

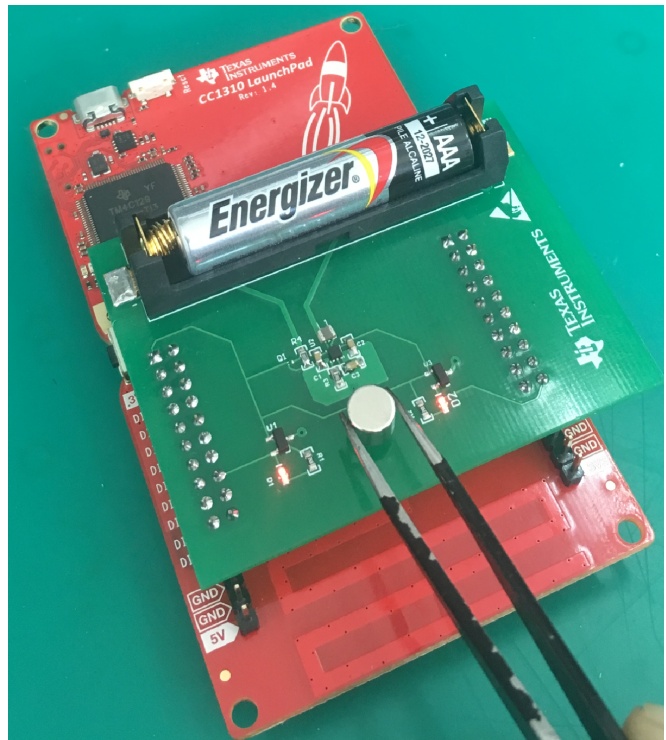

### 3.4 Battery Life Estimation

The battery-life time depends on the energy consumption of the loading as well as the self-discharge of the battery. An alkaline battery loses approximately 3% of its capacity per year when stored at 20°C due to slow electrochemical reactions that continually occur. Warm temperatures increases the reaction. At 40°C, the battery loses 20% of its capacitance after five years of storage.

In this reference design, the alkaline battery is an AAA type. Its typical capacity relates to the discharge current. Using an Energizer alkaline battery as an example, the capacitor is approximately 1100 milliamp-hour at 25-mA discharging current and 900 milliamp-hour at 100-mA discharging current. In this application, the maximum loading current is less than 10 mA caused by the wireless packet transmit. The current out of the battery is less than 30 mA, so 1100 milliamp-hour (mAh) battery capacity can be used to estimate the battery life time.

Considering 5-years lifetime, the total capacity is used by the loading is approximately 880 mAh (0.8 × 1100 mA). Assuming 6-μA standby current, this current sums up to 260 mAh for 5 years, so there will be 520-mAh battery capacity left for the wireless device and other sensors. The average loading current from the output of the boost can then be calculated by 式 1, which is approximately 4 μA.

$$I_{IN} = \frac{\text{Battery Capacity (mAh)}}{n \times 8760 \text{ hours}} \times \frac{V_{IN} \times \eta}{V_{OUT}}$$

where

- n is 5 years
- $V_{IN}$  is the boost input voltage (average is 1.2 V)
- $V_{OUT}$  is 3-V boost output voltage
- $\eta$  is the efficiency of the boost, approximately 0.85

(1)

From the reference design [TIDUC69](#), the power consumption of the wireless communication is only 0.3  $\mu$ A. Thus, there is approximately 3.7  $\mu$ A for other loading, such as temperature sensor or humidity sensor.

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-050018](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-050018](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-050018](#).

### 4.4 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-050018](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-050018](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-050018](#).

## 5 Related Documentation

1. [Low Power Door/Window Sensor with Sub-1GHz and 10-Year Battery Life Design Guide](#)
2. [TPS61098x Ultra-Low Quiescent Current Synchronous Boost with Integrated LDO/Load Switch](#)

### 5.1 商標

E2E, LaunchPad are trademarks of Texas Instruments.  
Altium Designer is a registered trademark of Altium LLC or its affiliated companies.  
すべての商標および登録商標はそれぞれの所有者に帰属します。

### 5.2 Third-Party Products Disclaimer

TI'S PUBLICATION OF INFORMATION REGARDING THIRD-PARTY PRODUCTS OR SERVICES DOES NOT CONSTITUTE AN ENDORSEMENT REGARDING THE SUITABILITY OF SUCH PRODUCTS OR SERVICES OR A WARRANTY, REPRESENTATION OR ENDORSEMENT OF SUCH PRODUCTS OR SERVICES, EITHER ALONE OR IN COMBINATION WITH ANY TI PRODUCT OR SERVICE.

## 重要なお知らせと免責事項

TI は、技術データと信頼性データ(データシートを含みます)、設計リソース(リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Web ツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の黙示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または黙示的にかかわらず拒否します。

これらのリソースは、TI 製品を使用する設計の経験を積んだ開発者への提供を意図したものです。(1) お客様のアプリケーションに適した TI 製品の選定、(2) お客様のアプリケーションの設計、検証、試験、(3) お客様のアプリケーションが適用される各種規格や、その他のあらゆる安全性、セキュリティ、またはその他の要件を満たしていることを確実にする責任を、お客様のみが単独で負うものとします。上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されている TI 製品を使用するアプリケーションの開発の目的でのみ、TI はその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TI や第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TI およびその代理人を完全に補償するものとし、TI は一切の責任を拒否します。

TI の製品は、TI の販売条件 ([www.tij.co.jp/ja-jp/legal/termsofsale.html](http://www.tij.co.jp/ja-jp/legal/termsofsale.html))、または [ti.com](http://ti.com) やかかる TI 製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TI がこれらのリソースを提供することは、適用される TI の保証または他の保証の放棄の拡大や変更を意味するものではありません。

Copyright © 2018, Texas Instruments Incorporated  
日本語版 日本テキサス・インスツルメンツ株式会社

## 重要なお知らせと免責事項

TI は、技術データと信頼性データ(データシートを含みます)、設計リソース(リファレンス・デザインを含みます)、アプリケーションや設計に関する各種アドバイス、Web ツール、安全性情報、その他のリソースを、欠陥が存在する可能性のある「現状のまま」提供しており、商品性および特定目的に対する適合性の黙示保証、第三者の知的財産権の非侵害保証を含むいかなる保証も、明示的または黙示的にかかわらず拒否します。

これらのリソースは、TI 製品を使用する設計の経験を積んだ開発者への提供を意図したものです。(1) お客様のアプリケーションに適した TI 製品の選定、(2) お客様のアプリケーションの設計、検証、試験、(3) お客様のアプリケーションが適用される各種規格や、その他のあらゆる安全性、セキュリティ、またはその他の要件を満たしていることを確実にする責任を、お客様のみが単独で負うものとします。上記の各種リソースは、予告なく変更される可能性があります。これらのリソースは、リソースで説明されている TI 製品を使用するアプリケーションの開発の目的でのみ、TI はその使用をお客様に許諾します。これらのリソースに関して、他の目的で複製することや掲載することは禁止されています。TI や第三者の知的財産権のライセンスが付与されている訳ではありません。お客様は、これらのリソースを自身で使用した結果発生するあらゆる申し立て、損害、費用、損失、責任について、TI およびその代理人を完全に補償するものとし、TI は一切の責任を拒否します。

TI の製品は、TI の販売条件 ([www.tij.co.jp/ja-jp/legal/termsofsale.html](http://www.tij.co.jp/ja-jp/legal/termsofsale.html))、または [ti.com](http://ti.com) やかかる TI 製品の関連資料などのいずれかを通じて提供する適用可能な条項の下で提供されています。TI がこれらのリソースを提供することは、適用される TI の保証または他の保証の放棄の拡大や変更を意味するものではありません。

Copyright © 2018, Texas Instruments Incorporated  
日本語版 日本テキサス・インスツルメンツ株式会社