

THS3001 SPICE Model Performance

Jim Karki
Mixed Signal Products

ABSTRACT

This application report outlines the SPICE model of the THS3001 high-speed monolithic operational amplifier. General information about the model file structure, performance comparison, model listing, and a brief comment about symbols are included. The listing can be copied and pasted into an ASCII editor, or it can be down loaded by visiting the THS3001 product folder at <http://www.ti.com/sc/docs/products/analog/THS3001.html>.

Contents

1	Introduction	3
2	File Structure	3
3	Performance	3
4	Schematic and Subcircuit Listing	12
5	About Building a Symbol	15

List of Figures

1	Output Voltage (pk) vs Temperature	4
2	Output Voltage (pk) vs Temperature	4
3	Supply Current vs Temperature	4
4	Supply Current vs Temperature	4
5	Bias Current vs Temperature	4
6	Bias Current vs Temperature	4
7	Input Offset Voltage vs Temperature	5
8	Input Offset Voltage vs Temperature	5
9	Common-Mode Rejection Ratio vs Frequency	5
10	Common-Mode Rejection Ratio vs Frequency	5
11	Power Supply Rejection Ratio vs Frequency	6
12	Power Supply Rejection Ratio vs Frequency	6
13	Equivalent Input Voltage Noise vs Frequency	6
14	Equivalent Input Current Noise vs Frequency	6
15	Slew Rate vs Output Voltage (pp)	7
16	Slew Rate vs Output Voltage (pp)	7
17	2nd Harmonic vs Frequency	7
18	2nd Harmonic vs Frequency	7
19	3rd Harmonic vs Frequency	8
20	3rd Harmonic vs Frequency	8

21	Differential Gain vs Loads	8
22	Differential Phase vs Loads	8
23	Differential Gain vs Loads	8
24	Differential Phase vs Loads	8
25	Differential Gain vs Loads	9
26	Differential Phase vs Loads	9
27	Differential Gain vs Loads	9
28	Differential Phase vs Loads	9
29	Closed-Loop Gain vs Frequency	9
30	Closed-Loop Gain vs Frequency	9
31	Closed-Loop Gain vs Frequency	10
32	Closed-Loop Gain vs Frequency	10
33	Closed-Loop Gain vs Frequency	10
34	Closed-Loop Gain vs Frequency	10
35	Output Impedance vs Frequency	10
36	Output Voltage vs Time	11
37	Gain and Phase vs Frequency	11
38	Open Loop Transimpedance Gain vs Frequency	11
39	Open Loop Transimpedance Gain vs Frequency	11
40	THS3001 SPICE Model Schematic	12

List of Tables

1	Subcircuit Node to Symbol Pin Summary	15
---	---------------------------------------	----

1 Introduction

SPICE modeling has become commonplace today, especially with the advent of affordable PCs with more computing power than main frames of a few years ago.

A big concern in SPICE modeling is the accuracy of the models. Without a good model, simulation results are little more than verification of rudimentary circuit operation. The Boyle operational amplifier (op amp) model introduced during the mid '70s came from the need for a model that did not use a lot of computing resources, and gave reasonable results for the μ A741. In the years since, people have enhanced the Boyle model to add more accuracy.

Today, full-transistor models simulate with speed and accuracy on modest home systems. The goal, when creating the SPICE model of the THS3001 high-speed monolithic operational amplifier, is to provide a model that will accurately simulate the actual device in a circuit. The model is derived from the full-transistor model used internally by TI design. Simplifications are made to speed simulation time, and various performance parameters are adjusted to match the model to measured device performance.

2 File Structure

The THS3001 SPICE model file, THS3001.lib, is written in ASCII file format and is compatible with a wide variety of computing platforms. The model is written in subcircuit format and has been tested with MicroSim® PSpice® release 8 and OrCAD® PSpice® version 9. It should be compatible with most SPICE2- and SPICE3-based simulation programs.

The THS3001.lib file contains the subcircuit definition for the THS3001. The model begins with a .SUBCKT statement and ends with a .ENDS statement.

3 Performance

Typical performance parameters are modeled, and normal part-to-part variations experienced in real life cannot be expected. At frequencies above a few hundred MHz, performance becomes increasingly dependent on parasitic devices associated with the circuit, and modeling suffers. So, even though the model is very accurate, always verify circuit performance with lab testing. An EVM is available upon request.

The following graphs compare simulation results to measured device data. In all graphs, the simulation results are dashed lines and the measured data are solid lines. Device performance is measured using the THS3001 EVM, or is taken from the data sheet. SPICE simulation was done using MicroSim® PSpice® release 8. Most of the parameters are measured using $V_{cc}=\pm 15$ V, and performance follows at lower voltages.

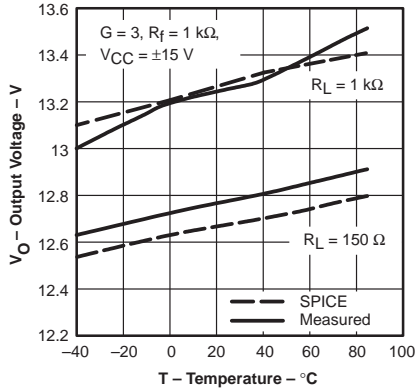


Figure 1. Output Voltage (pk) vs Temperature

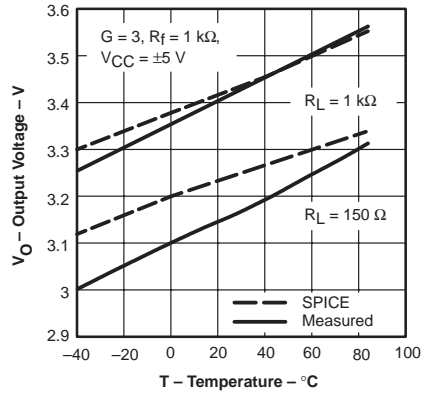


Figure 2. Output Voltage (pk) vs Temperature

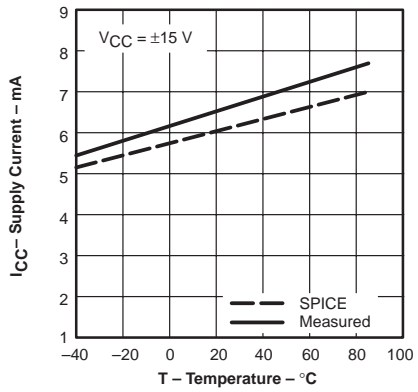
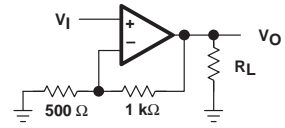


Figure 3. Supply Current vs Temperature

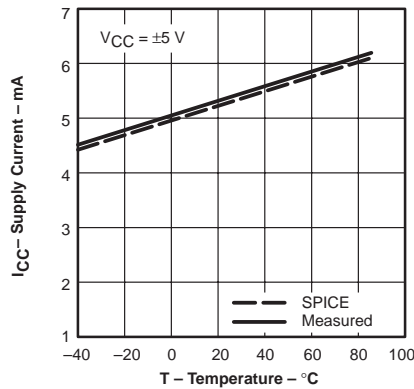


Figure 4. Supply Current vs Temperature

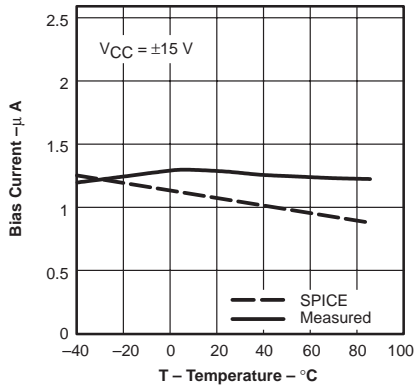


Figure 5. Bias Current vs Temperature

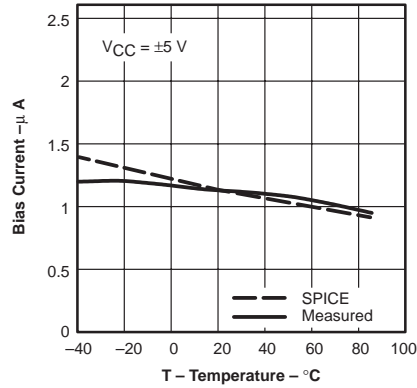


Figure 6. Bias Current vs Temperature

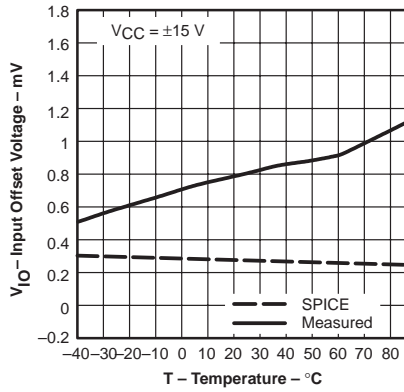


Figure 7. Input Offset Voltage vs Temperature

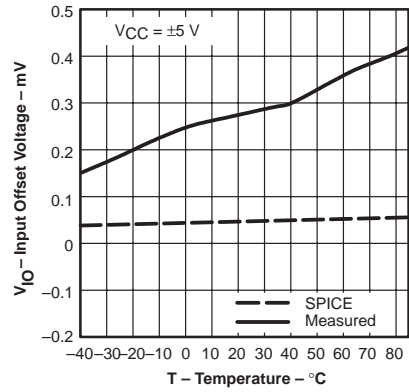


Figure 8. Input Offset Voltage vs Temperature

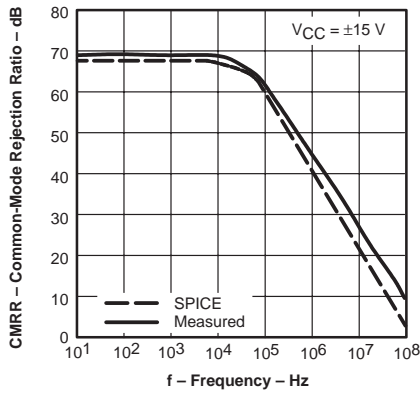


Figure 9. Common-Mode Rejection Ratio vs Frequency

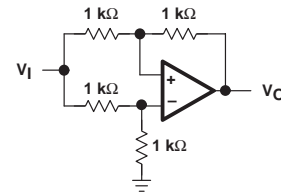
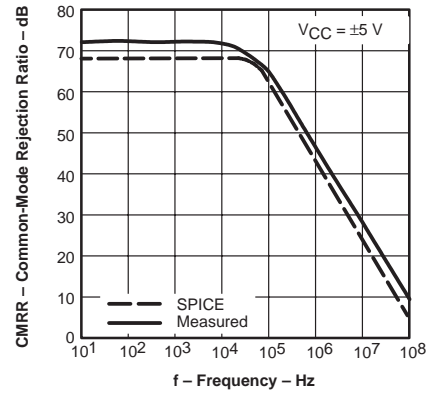


Figure 10. Common-Mode Rejection Ratio vs Frequency

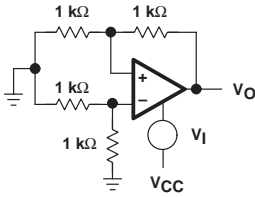
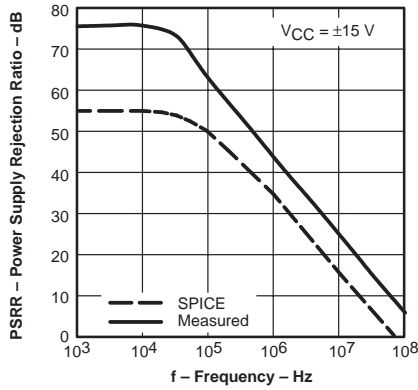


Figure 11. Power Supply Rejection Ratio vs Frequency

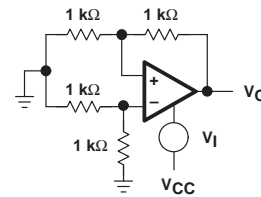
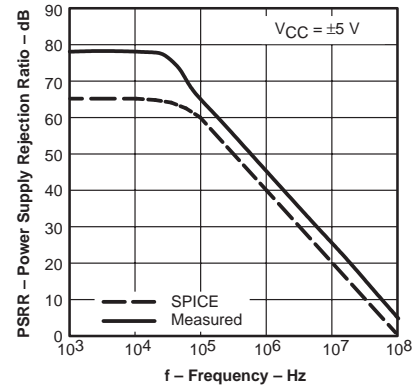


Figure 12. Power Supply Rejection Ratio vs Frequency

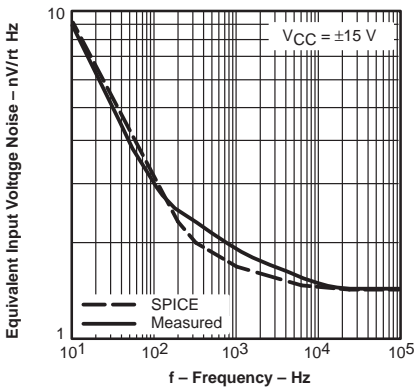


Figure 13. Equivalent Input Voltage Noise vs Frequency

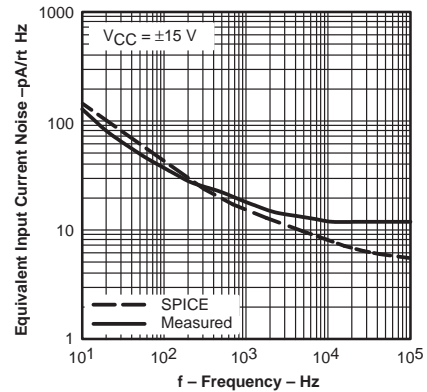


Figure 14. Equivalent Input Current Noise vs Frequency

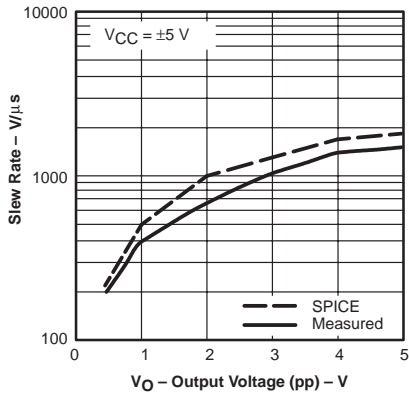


Figure 15. Slew Rate vs Output Voltage (pp)

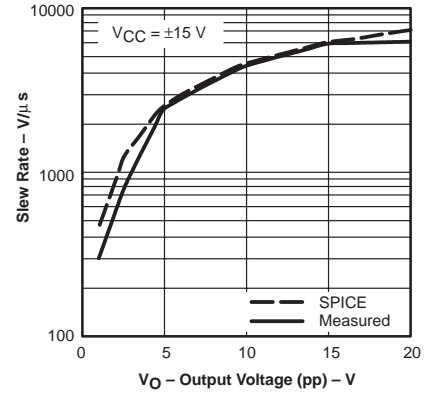


Figure 16. Slew Rate vs Output Voltage (pp)

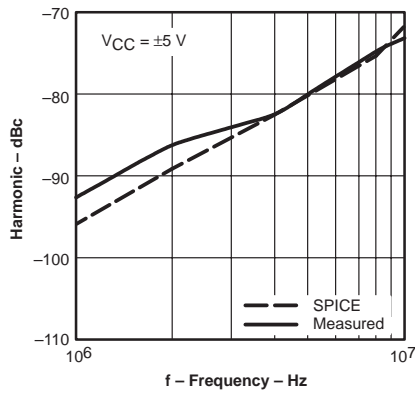


Figure 17. 2nd Harmonic vs Frequency

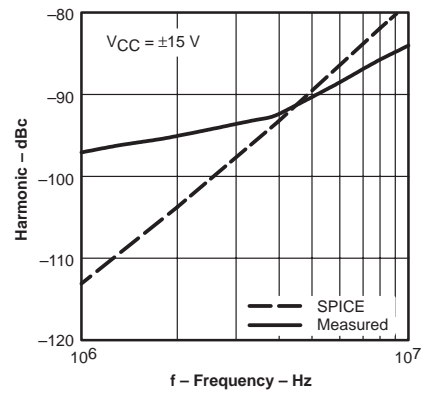


Figure 18. 2nd Harmonic vs Frequency

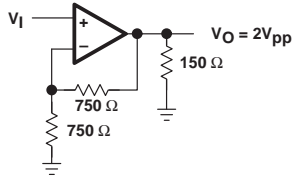
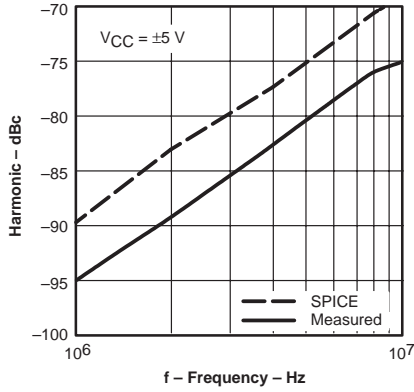


Figure 19. 3rd Harmonic vs Frequency

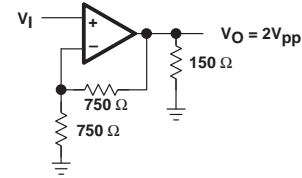
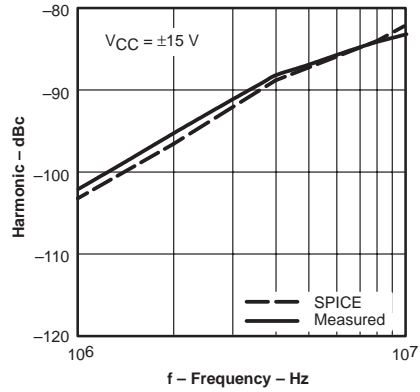


Figure 20. 3rd Harmonic vs Frequency

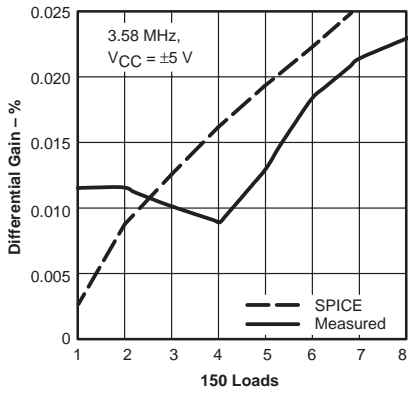


Figure 21. Differential Gain vs Loads

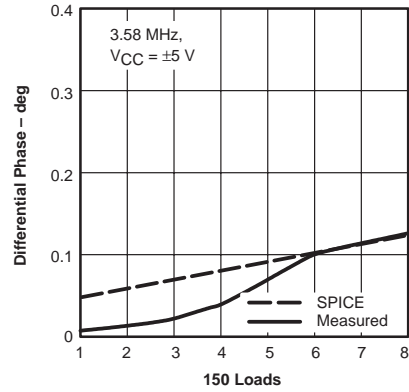


Figure 22. Differential Phase vs Loads

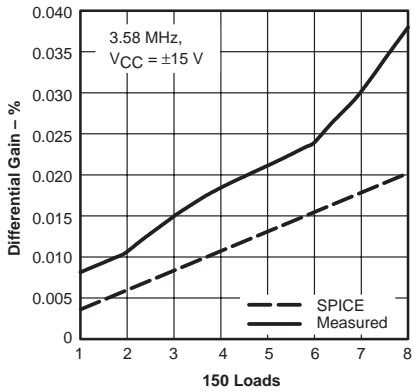


Figure 23. Differential Gain vs Loads

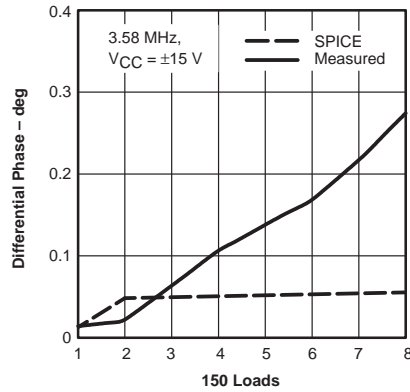


Figure 24. Differential Phase vs Loads

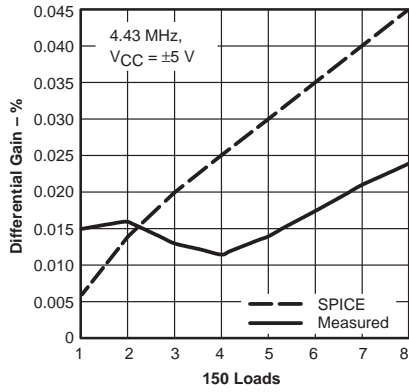


Figure 25. Differential Gain vs Loads

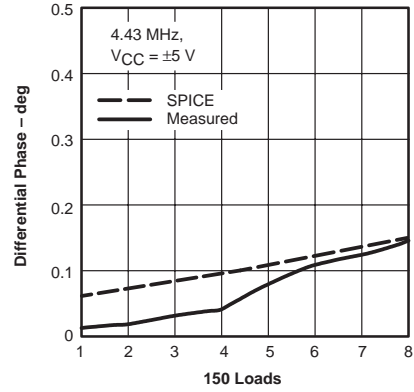


Figure 26. Differential Phase vs Loads

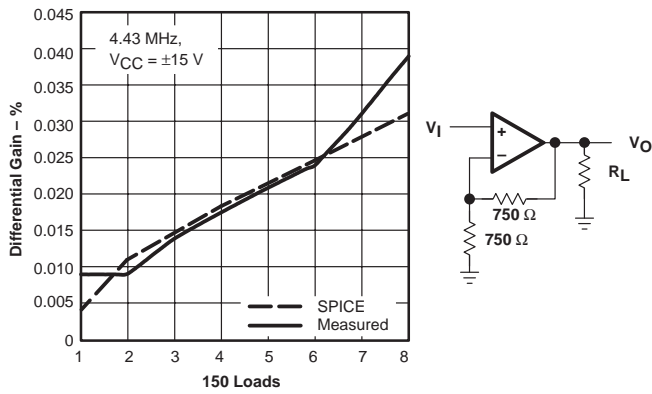


Figure 27. Differential Gain vs Loads

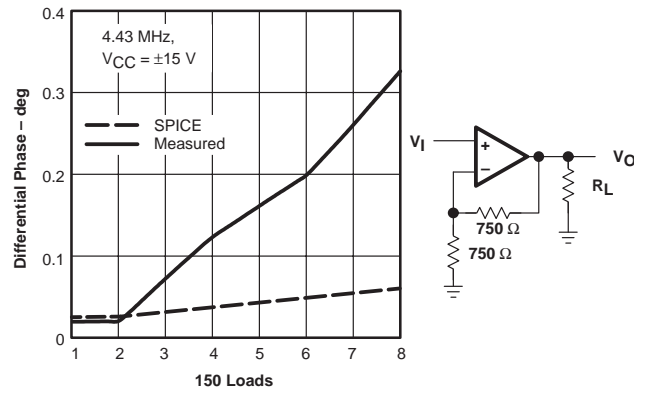


Figure 28. Differential Phase vs Loads

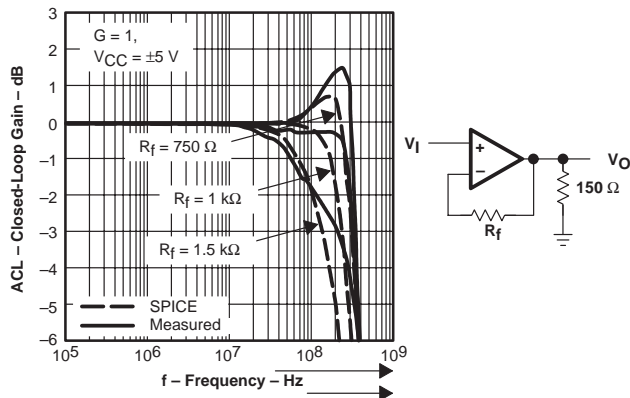


Figure 29. Closed-Loop Gain vs Frequency

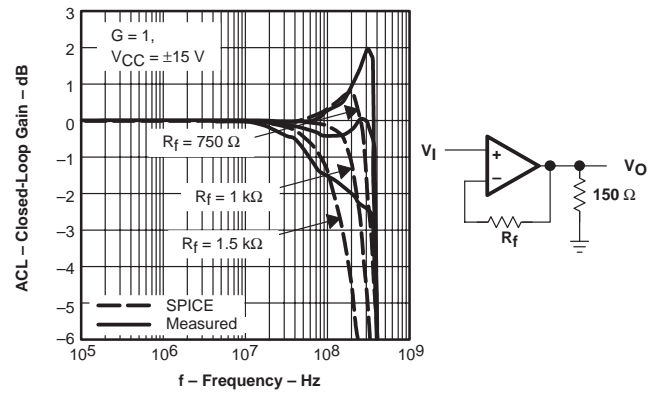


Figure 30. Closed-Loop Gain vs Frequency

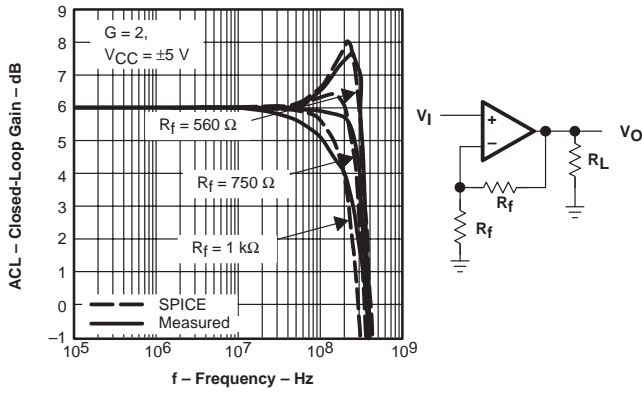


Figure 31. Closed-Loop Gain vs Frequency

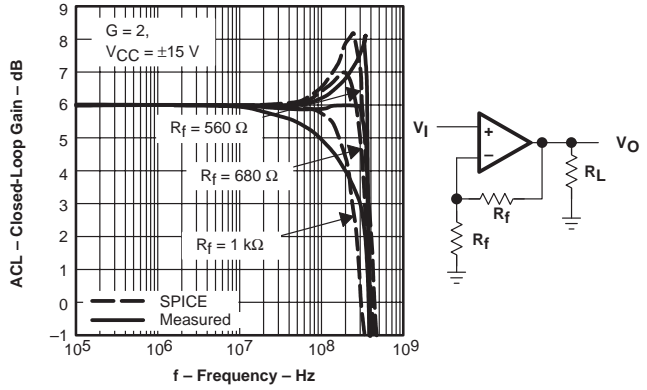


Figure 32. Closed-Loop Gain vs Frequency

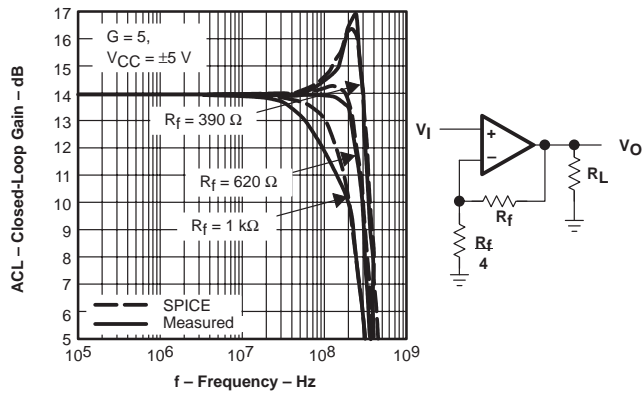


Figure 33. Closed-Loop Gain vs Frequency

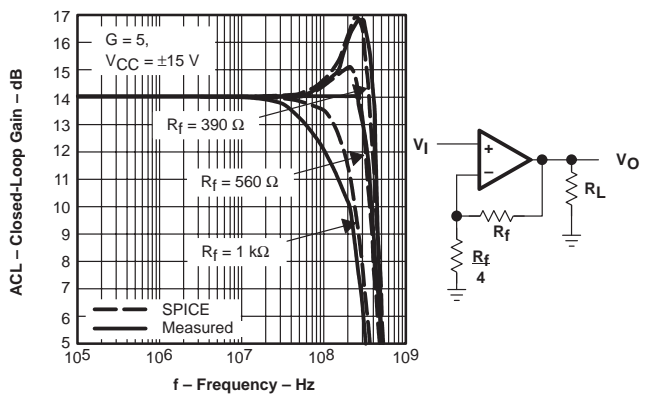


Figure 34. Closed-Loop Gain vs Frequency

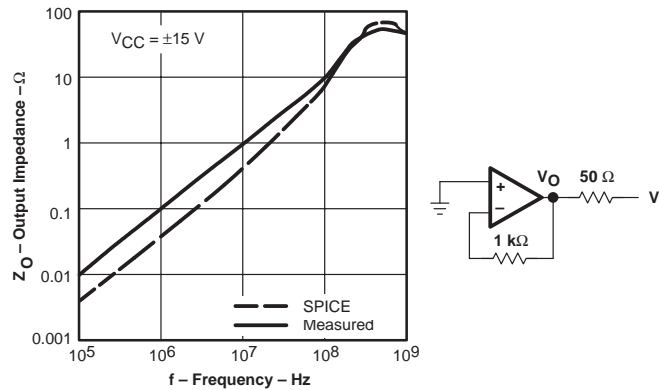


Figure 35. Output Impedance vs Frequency

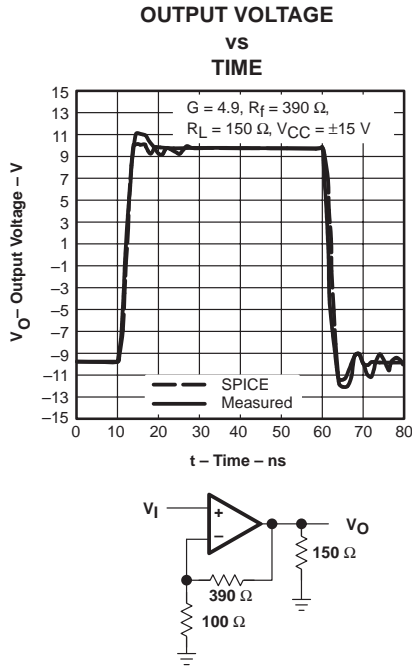


Figure 36. Output Voltage vs Time

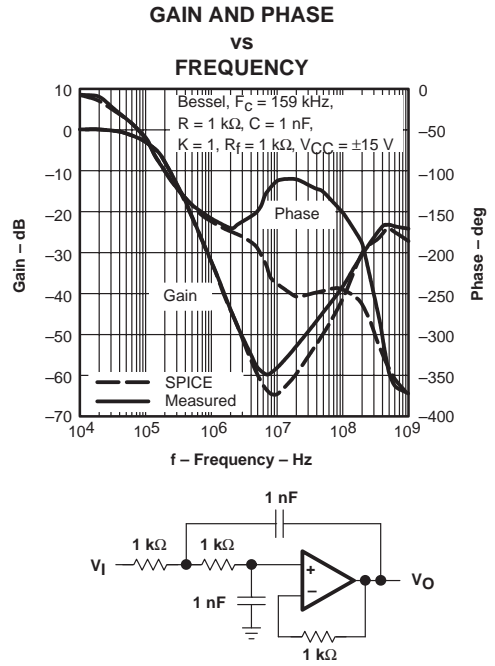


Figure 37. Gain and Phase vs Frequency

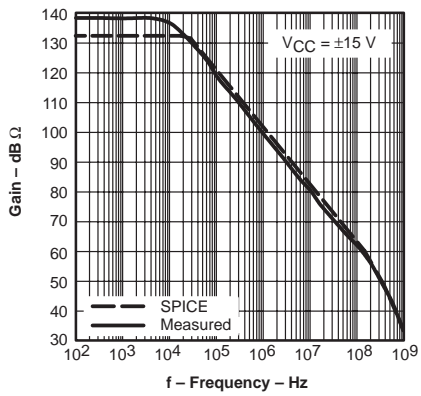


Figure 38. Open Loop Transimpedance Gain vs Frequency

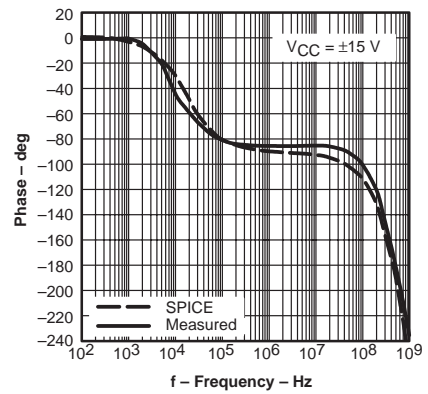


Figure 39. Open Loop Transimpedance Gain vs Frequency


```

* [Disclaimer] (C) Copyright Texas Instruments Incorporated 1999 All rights reserved
* Texas Instruments Incorporated hereby grants the user of this SPICE Macro-model a
* non-exclusive, nontransferable license to use this SPICE Macro-model under the following
* terms. Before using this SPICE Macro-model, the user should read this license. If the
* user does not accept these terms, the SPICE Macro-model should be returned to Texas
* Instruments within 30 days. The user is granted this license only to use the SPICE
* Macro-model and is not granted rights to sell, load, rent, lease or license the SPICE
* Macro-model in whole or in part, or in modified form to anyone other than user. User may
* modify the SPICE Macro-model to suit its specific applications but rights to derivative
* works and such modifications shall belong to Texas Instruments. This SPICE Macro-model is
* provided on an "AS IS" basis and Texas Instruments makes absolutely no warranty with
* respect to the information contained herein. TEXAS INSTRUMENTS DISCLAIMS AND CUSTOMER
* WAIVES ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING WARRANTIES OF MERCHANTABILITY OR
* FITNESS FOR A PARTICULAR PURPOSE. The entire risk as to quality and performance is with
* the Customer. ACCORDINGLY, IN NO EVENT SHALL THE COMPANY BE LIABLE FOR ANY DAMAGES,
* WHETHER IN CONTRACT OR TORT, INCLUDING ANY LOST PROFITS OR OTHER INCIDENTAL, CONSEQUENTIAL,
* EXEMPLARY, OR PUNITIVE DAMAGES ARISING OUT OF THE USE OR APPLICATION OF THE SPICE
* Macro-model provided in this package. Further, Texas Instruments reserves the right to
* discontinue or make changes without notice to any product herein to improve reliability,
* function, or design. Texas Instruments does not convey any license under patent rights or
* any other intellectual property rights, including those of third parties.

```

```

*
* THS3001 SUBCIRCUIT
* HIGH SPEED, CURRENT FEEDBACK, OPERATIONAL AMPLIFIER
* WRITTEN 8/10/99
* TEMPLATE=X^@REFDES %IN+ %IN- %Vcc+ %Vcc- %OUT @MODEL
* CONNECTIONS:      NON-INVERTING INPUT
*                   | INVERTING INPUT
*                   | | POSITIVE POWER SUPPLY
*                   | | | NEGATIVE POWER SUPPLY
*                   | | | | OUTPUT
*                   | | | | |
*                   | | | | |
*                   | | | | |
.SUBCKT THS3001      1 2 3 4 5

```

```

*
* INPUT *
Q1 31 32 2 NPN_IN 4
QD1 32 32 1 NPN 4
Q2 7 15 2 PNP_IN 4
QD2 15 15 1 PNP 4
* PROTECTION DIODES *
D1 1 3 Din_N
D2 4 1 Din_P
D3 5 3 Dout_N
D4 4 5 Dout_P
* SECOND STAGE *
Q3 17 31 11 PNP 2
Q4 16 7 13 NPN 2
QD3 30 30 17 PNP 3

```

```

QD4 30 30 16 NPN 3
C1 30 3 0.4p
C2 4 30 0.4p
F1 3 31 VF1 1
VF1 33 34 0V
F2 7 4 VF2 1
VF2 35 6 0V
F3 3 12 VF3 1
VF3 34 11 0V
F4 14 4 VF4 1
VF4 13 35 0V
* FREQUENCY SHAPING *
E1 18 0 17 0 1
E2 19 0 16 0 1
R1 44 18 25
R2 19 42 25
C3 0 14 9p
C4 0 12 9p
L1 44 14 2.8n
L2 42 12 2.8n
* OUTPUT *
Q5 3 14 28 NPN 128
Q6 4 12 29 PNP 128
C5 28 9 7p
R5 9 5 100
L3 28 10 30n
R7 10 5 8
Re 28 29 Rt 50
C6 29 21 7p
R4 21 5 100
L4 29 22 30n
R6 22 5 8
* BIAS SOURCES *
G1 3 32 VALUE = { 308e-6+1.656e-6*V(3, 4) }
G2 15 4 VALUE = { 307e-6+1.656e-6*V(3, 4) }
V1 3 33 0.83
V2 6 4 0.83
.MODEL Rt RES TC1=-0.006
* DIODE MODELS *
.MODEL Din_N D IS=10E-21 N=1.836 ISR=1.565e-9 IKF=1e-4 BV=30 IBV=100E-6 RS=105 TT=11.54E-9
CJO=2E-12 VJ=.5 M=.3333
.MODEL Din_P D IS=10E-21 N=1.836 ISR=1.565e-9 IKF=1e-4 BV=30 IBV=100E-6 RS=160 TT=11.54E-9
CJO=2E-12 VJ=.5 M=.3333
.MODEL Dout_N D IS=10E-21 N=1.836 ISR=1.565e-9 IKF=1e-4 BV=30 IBV=100E-6 RS=60 TT=11.54E-9
CJO=2E-12 VJ=.5 M=.3333
.MODEL Dout_P D IS=10E-21 N=1.836 ISR=1.565e-9 IKF=1e-4 BV=30 IBV=100E-6 RS=105 TT=11.54E-9
CJO=2E-12 VJ=.5 M=.3333
* TRANSISTOR MODELS *
.MODEL NPN_IN NPN
+ IS=170E-18 BF=100 NF=1 VAF=100 IKF=0.0389 ISE=7.6E-18

```

```

+ NE=1.13489 BR=1.11868 NR=1 VAR=4.46837 IKR=8 ISC=8E-15
+ NC=1.8 RB=251.6 RE=0.1220 RC=197 CJE=120.2E-15 VJE=1.0888 MJE=0.381406
+ VJC=0.589703 MJC=0.265838 FC=0.1 CJC=133.8E-15 XTF=272.204 TF=12.13E-12
+ VTF=10 ITF=0.294 TR=3E-09 XTB=1 XTI=5 KF=25E-15
.MODEL NPN NPN
+ IS=170E-18 BF=100 NF=1 VAF=100 IKF=0.0389 ISE=7.6E-18
+ NE=1.13489 BR=1.11868 NR=1 VAR=4.46837 IKR=8 ISC=8E-15
+ NC=1.8 RB=251.6 RE=0.1220 RC=197 CJE=120.2E-15 VJE=1.0888 MJE=0.381406
+ VJC=0.589703 MJC=0.265838 FC=0.1 CJC=133.8E-15 XTF=272.204 TF=12.13E-12
+ VTF=10 ITF=0.147 TR=3E-09 XTB=1 XTI=5
.MODEL PNP_IN PNP
+ IS=296E-18 BF=100 NF=1 VAF=100 IKF=0.021 ISE=494E-18
+ NE=1.49168 BR=0.491925 NR=1 VAR=2.35634 IKR=8 ISC=8E-15
+ NC=1.8 RB=251.6 RE=0.1220 RC=197 CJE=120.2E-15 VJE=0.940007 MJE=0.55
+ VJC=0.588526 MJC=0.55 FC=0.1 CJC=133.8E-15 XTF=141.135 TF=12.13E-12
+ VTF=6.82756 ITF=0.267 TR=3E-09 XTB=1 XTI=5 KF=25E-15
.MODEL PNP PNP
+ IS=296E-18 BF=100 NF=1 VAF=100 IKF=0.021 ISE=494E-18
+ NE=1.49168 BR=0.491925 NR=1 VAR=2.35634 IKR=8 ISC=8E-15
+ NC=1.8 RB=251.6 RE=0.1220 RC=197 CJE=120.2E-15 VJE=0.940007 MJE=0.55
+ VJC=0.588526 MJC=0.55 FC=0.1 CJC=133.8E-15 XTF=141.135 TF=12.13E-12
+ VTF=6.82756 ITF=0.267 TR=3E-09 XTB=1 XTI=5
.ENDS
*$

```

5 About Building a Symbol

The first line of the subcircuit definition – .SUBCKT THS3001_NN 1 2 3 4 5 – defines the name of the model and the subcircuit nodes available for external connection. When creating a symbol in PSpice®, the subcircuit node assignments need to match the TEMPLATE device property, and the MODEL value must equal the model name. The comment line in the file * TEMPLATE = X^@REFDES %IN+ %IN- %VCC+ %VCC- %OUT @MODEL gives the proper value for the TEMPLATE property. This associates the symbol pin names with subcircuit nodes available for external connections. The symbol pin numbers are used for packaging purposes and are not used for simulation. Using the forgoing results in the following associations:

Table 1. Subcircuit Node to Symbol Pin Summary

Subcircuit Node	THS3001 Symbol Pin Name
2	IN-
3	Vcc+
4	Vcc-
5	OUT

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF TI PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.