

# Schematic Checklist - A Guide to Designing With Fixed or Direction Control Translators

---



Michael Ikwuyum

## ABSTRACT

This application note provides recommendations and a checklist to follow while creating or reviewing schematics for fixed-directional or direction-control level shifters. Examples of such devices are the [TXU](#), [TXV](#), [LXC](#), [LVC](#), [AXC](#), [AVC](#), [AUP](#), [LVxT](#) devices.

---

## Table of Contents

|  |   |
|--|---|
| <b>1 Introduction</b> .....  | 1 |
| 1.1 Device Applicability.....  | 2 |
| 1.2 When to Use or Not Use Fixed Directional Devices.....  | 2 |
| <b>2 Recommendations Specific to Fixed Directional or Direction Control Level Shifters</b> ..... | 3 |
| 2.1 Before You Begin.....  | 3 |
| 2.2 Power Supplies.....  | 3 |
| 2.3 Output Enable and DIR Pins.....  | 3 |
| 2.4 Input or Output Pins.....  | 3 |
| 2.5 Unused Pins.....   | 3 |
| 2.6 Pull-Ups and Pull-Downs.....   | 4 |
| 2.7 Recommended Translator by Interface.....   | 4 |
| <b>3 Summary</b> .....   | 4 |
| <b>4 References</b> .....  | 5 |

## Trademarks

All trademarks are the property of their respective owners.

## 1 Introduction


[TXU](#), [TXV](#), [LXC](#), [LVC](#), [AXC](#), [AVC](#), [AUP](#), [LVxT](#) device families are recommended for unidirectional applications where individual channels are used for a fixed directional signal. [TXS](#), [TXB](#) and [LSF](#) families are recommended for applications that require auto-bidirection signals with individual channels. [Section 1.2](#) shows examples of fixed directional signals and auto-bidirectional signals.

## 1.1 Device Applicability

This application note applies to the following devices:


- TXU, TXV, LXC, LVC, AXC, AVC, AUP, LVxT device families.

## 1.2 When to Use or Not Use Fixed Directional Devices

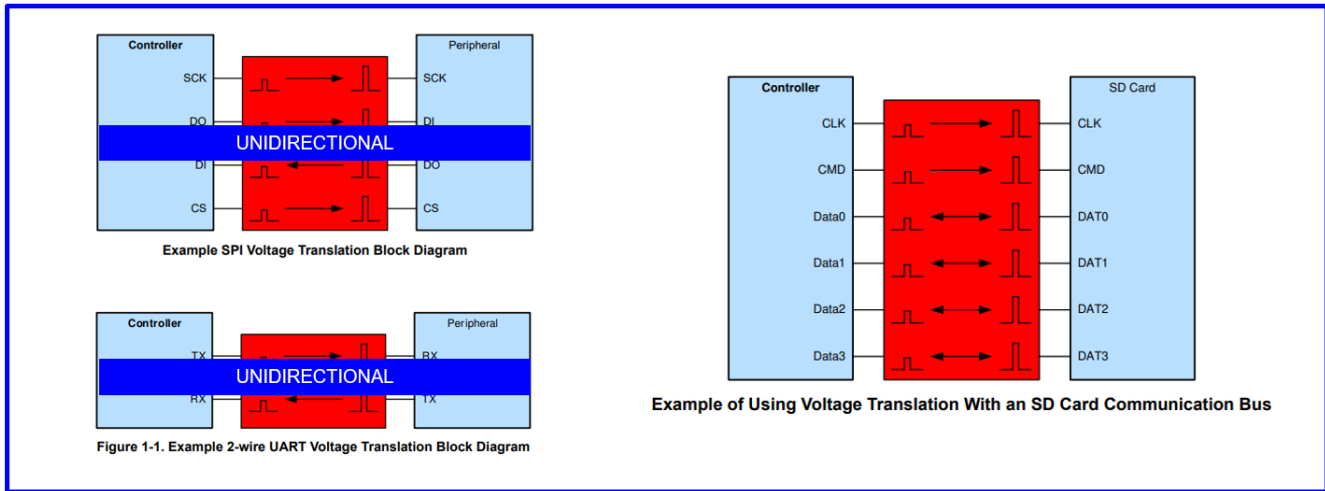


**Figure 1-1. Differences Between Unidirectional and Auto-Bidirectional Signals**

Each channel of unidirectional signals are directed towards a fixed direction while each channel of auto-bidirectional signals can be directed for both directions. Check for the direction of the application's signal or protocol and review this checklist with the latest data sheet documentation. [Figure 1-2](#) and [Figure 1-3](#) are examples showing fixed directional signals. See [Section 2.7](#) for a full list of typical applications with their device recommendations.

 

**Figure 1-2. Example of Using Voltage Translation With an SPI Communication Bus**

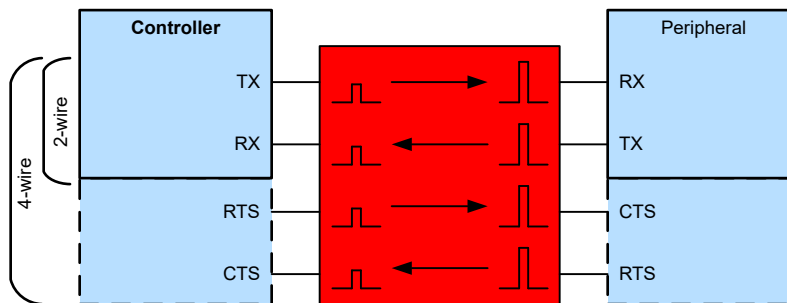

**Figure 1-3. Example of Using Voltage Translation With UART**

## 2 Recommendations Specific to Fixed Directional or Direction Control Level Shifters

### 2.1 Before You Begin

#### 2.1.1 Documentation

Make sure you have the latest version of all documentation and data sheets.

---

#### Note

There is a Notifications button on each [ti.com](https://www.ti.com) device product folder. Registration here enables proactive automatic notification of device errata.

---

### 2.2 Power Supplies

#### 2.2.1 Biasing Requirements

- Make sure supply voltages match data sheet recommendations.

#### 2.2.2 Decoupling Capacitors

During transitions, level-shifters can draw large transient currents from the power supply. Decoupling capacitors prevents voltage droops on the power rails by bypassing the power supply and creating a low-impedance path for high-frequency signals. This makes sure the level-shifter is provided a clean and stable supply voltage.

A typical recommendation is 0.1  $\mu\text{F}$ , to help mitigate noise from power supplies. Place decoupling capacitors as close as possible to  $V_{\text{CC}}$  pins on the printed circuit board layout.

#### 2.2.3 Power Sequencing

- The recommendation is to make sure the OE pin is configured to keep the device disabled until both supplies are stable.
- Devices such as AXC | LXC | TXU are equipped for robust power sequencing and do not recommend any specific power sequence requirement.

### 2.3 Output Enable and DIR Pins

- Never leave floating.
- Connect directly to  $V_{\text{CC}}$  or GND (or drive HIGH or LOW with a control signal).
  - Can use pull-ups or pull-downs when driven by a control signal. 10 k $\Omega$  is typical.

### 2.4 Input or Output Pins

Make sure your input or output pins meet the data sheet recommendations. For example:

- Data rate frequency.
- Load capacitance.
- Double check proper voltage levels for inputs (follow the device-specific  $V_{\text{IH}}$  /  $V_{\text{IL}}$  specification in the data sheet). Devices are over-voltage tolerant and inputs can be  $\geq V_{\text{CC}}$  within the data sheet's recommended operating conditions.
- Series resistors used should be sufficient with the device's output impedance and transmission line used. For more information, see [\[FAQ\] Can I estimate appropriate dampening resistor value for level-shifter outputs?](#)
- Not recommended to have delay (RC) circuitry tied to input pins to avoid violating the data sheet's input transition spec, where applicable. Violations can result to shoot-through currents and oscillations. For more information, see [Implications of Slow or Floating CMOS inputs](#).

### 2.5 Unused Pins

AXC | LXC | TXU devices are equipped with internal pull-downs to prevent floating. Their unused pins can be left disconnected (with the exception of the OE | DIR pins).

Devices not equipped with internal pull-downs can never have unused floating inputs. The recommendation is to tie unused pins to GND.

## 2.6 Pull-Ups and Pull-Downs

- External pull-up (or pull-down) resistors can be used with devices that do not have internal pull-downs (or pull-ups).
- If a device includes internal pull-downs (or pull-ups), external pull-ups (or pull-downs) can be sized properly avoid voltage divider networks.
  - The general rule is to size external pull-ups no larger than 10% of the value of the internal pull-down resistor used. See respective data sheet recommendations for AXC | LXC | TXU.

## 2.7 Recommended Translator by Interface

**Table 2-1. Recommended Translator by Interface**

| Interface                 | Translation Level      |                       |
|---------------------------|------------------------|-----------------------|
|                           | Up to 3.6V             | Up to 5.5V            |
| FET Replacement           | 2N7001T                | SN74LXC1T45 / TXU0101 |
| 1 Bit GPIO / Clock Signal | SN74AXC1T45            | SN74LXC1T45 / TXU0101 |
| 2 Bit GPIO                | SN74AXC2T245           | SN74LXC2T45 / TXU0102 |
| 2-Pin JTAG / UART         | SN74AXC2T45            | SN74LXC2T45 / TXU0202 |
| I2C / MDIO / SMBus        | TXS0102 / LSF0102      | TXS0102 / LSF0102     |
| IC-USB                    | SN74AVC2T872 / TXS0202 | N/A                   |
| 4 Bit GPIO                | SN74AXC4T245           | TXB0104 / TXU0104     |
| UART                      | SN74AXC4T245           | TXB0104 / TXU0204     |
| SPI                       | SN74AXC4T774           | TXU0304               |
| Quad-SPI                  | TXB0106                | TXB0106               |
| JTAG                      | SN74AXC4T774 / TXB0104 | TXB0104 / TXU0304     |
| I2S / PCM                 | SN74AXC4T774 / TXB0104 | TXB0104 / TXU0204     |
| SDIO / SD / MMC           | TXS0206 / TWL1200      | N/A                   |
| 6 Bit RGMII               | TXV0106                | N/A                   |
| 8 Bit GPIO / RGMII        | TXV0108                | SN74LXC8T245          |

For more information on specific interfaces, see [Voltage Translation Application Quick Reference](#).

## 3 Summary

| Step | Checklist   | Comments  |
|------|---|---|
| 1    | Verify the interface  | See <a href="#">Section 2.7</a><br>Fixed directional or direction control devices are used with push-Pull interfaces  |
| 2    | Verify power supplies are biased correctly  | Data sheet guarantees $V_{CC}$ within the respective data sheet's recommended operating conditions<br><b>AXC</b> 0.65V - 3.6V   <b>AVC</b> 1.2V - 3.6V   <b>TXV</b> 1.14V - 3.6V   <b>TXU</b> 1.08V - 5.5V   <b>LXC</b> 1.08V - 5.5V   <b>LVC</b> 1.65V - 5.5V              |
| 3    | Verify decoupling capacitors are used with all power supplies                         | 0.1 $\mu$ F is recommended. Recommended to place cap as close as possible to the $V_{CC}$ supply pin(s).  |
| 4    | Verify the schematic pinout matches the data sheet pinout.                            | Unused I/Os can be left floating only if there is a pull-down internal to the device in cases such as AXC   LXC   TXU<br>Without an internal pull-down, tie all unused pins to GND or use bus-hold alternatives such as AVCH   LVCH.  |
| 5    | Verify output capacitive load is minimal  | Typically, up to 70pF unless specified in data sheets.  |
| 6    | Verify that external pull-up (or pull-down) resistors are consistent with data sheet. | Pull-ups are not recommended for AXC   LXC   TXU. If used, make sure the pull-up used is not larger than 10 % of the internal pull-down.<br>Pull-ups are not recommended with bus-hold devices.<br>Pull ups can be used with all other devices without internal pull-downs. |

## 4 References

- Texas Instruments, [Implications of Slow or Floating CMOS inputs](#), application note.
- Texas Instruments, [Voltage Translation Application Quick Reference](#), product overview.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated