

2.2-W Multi-Output Flyback Reference Design



Description


This reference design is a 2.2-W multi-output flyback design for isolated gate-drive bias supplies. The supply is designed to accept an input from 24-V systems. This design uses the LM36520 synchronous buck converter to generate four isolated outputs. Primary-side regulation maintains each of the four 17-V outputs within $\pm 10\%$.

Features


- Four 17-V isolated outputs
- Achieves $\pm 10\%$ output voltage accuracy on non-regulated outputs
- PSR eliminates need for an optocoupler
- Transformer designed to comply with: IEC61800-5-1

Applications

- [Servo drive power supply module](#)

 

Board Top Photo

 

Bottom Side Photo

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications	Units
Input Voltage	21.6–26.4	V
Output Voltage 1	17	V
Output Current 1	0.1	A
Output Voltage 2	17	V
Output Current 2	0.01	A
Output Voltage 3	17	V
Output Current 3	0.01	A
Output Voltage 4	17	V
Output Current 4	0.01	A

2 Testing and Results


2.1 Efficiency Data

Table 2-1. Efficiency Data

V_{IN} (V)	I_{IN} (A)	P_{IN} (W)	V_{OUT1} (V)	V_{OUT2} (V)	V_{OUT3} (V)	V_{OUT4} (V)	I_{OUT1} (A)	I_{OUT2} (A)	I_{OUT3} (A)	I_{OUT4} (A)	P_{OUT} (W)	Efficiency	Loss (W)
24.00	0.12	2.78	16.85	17.11	17.05	17.14	0.10	0.01	0.01	0.01	2.20	0.79	0.58
24.00	0.02	0.53	18.27	17.65	17.74	17.58	0.00	0.00	0.00	0.00	0.00	0.00	0.53
21.61	0.12	2.66	16.02	16.58	16.38	16.72	0.10	0.01	0.01	0.01	2.09	0.79	0.57
21.60	0.02	0.50	18.14	17.61	17.68	17.55	0.00	0.00	0.00	0.00	0.00	0.00	0.50
26.39	0.11	2.85	17.13	17.29	17.27	17.30	0.10	0.01	0.01	0.01	2.24	0.79	0.61
26.40	0.02	0.58	18.34	17.69	17.79	17.60	0.00	0.00	0.00	0.00	0.00	0.00	0.58

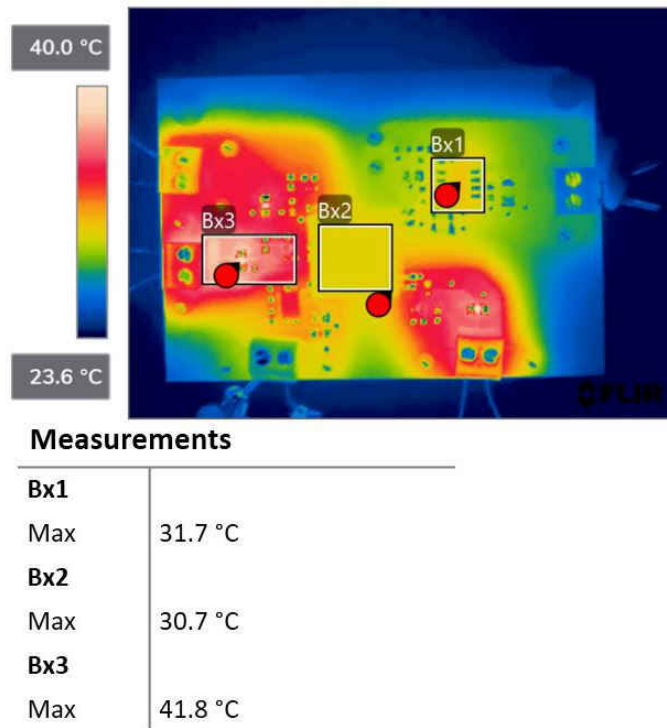2.2 Thermal Images

Thermal image is shown in the following figure.



Bx1 = U1

Bx2 = T1

Bx3 = R4

Figure 2-1. Thermal Image

2.3 Bode Plots

Bode plot is shown in the following figure.

 


Figure 2-2. Bode Plot

3 Waveforms

3.1 Switching

Switching behavior is shown in the following figures.

 


Figure 3-1. Primary FET Vds (U1 Pin 8) – 21.6 V_{IN}, Full Load

 


Figure 3-2. Primary FET Vds (U1 Pin 8) – 26.4 V_{IN}, Full Load

 


Figure 3-3. Diode (D4) – 21.6 V_{IN}, Full Load

 


Figure 3-4. Diode (D4) – 26.4 V_{IN}, Full Load

 


Figure 3-5. Diode (D2) – 21.6 V_{IN}, Full Load

 


Figure 3-6. Diode (D2) – 26.4 V_{IN}, Full Load

3.2 Output Voltage Ripple

Output voltage ripple is shown in the following figures.

 


Figure 3-7. 24-V Input, V_{OUT1} , Maximum Load

 


Figure 3-8. 24-V Input, V_{OUT2} , Maximum Load


 


Figure 3-9. 24-V Input, V_{REG} , Maximum Load

 
3.3 Start-Up Sequence

Start-up behavior is shown in the following figures.




Yellow (C1) = V_{OUT1} ; Pink (C2) = V_{OUT2} ; Blue (C3) = V_{OUT3} ; Green (C4) = V_{OUT4}

Figure 3-10. 24-V Input, No Load

 

Blue (C3) = V_{ds} ; Pink (C2) = V_{REG} ; Green (C4) = V_{OUT4}

Figure 3-11. 24-V Input, No Load

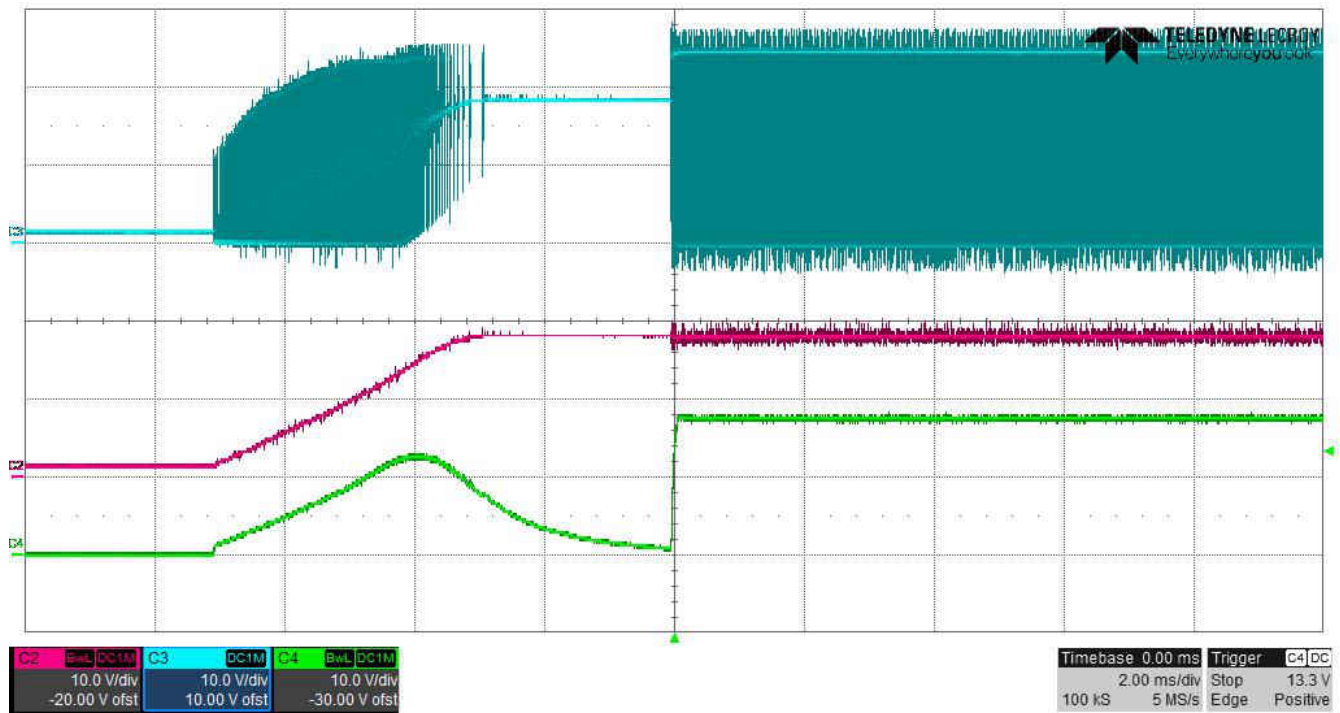

Blue (C3) = V_{ds} ; Pink (C2) = V_{REG} ; Green (C4) = V_{OUT4}

Figure 3-12. 24-V Input, Full Load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated