

GaN-Based Dual-Phase Boost Converter Reference Design for Class H Audio Applications



Description

This design showcases a dual-phase automotive boost converter for Class-H audio applications using LMG2100R026 gallium nitride (GaN) half bridges and offering analog- or digital-output voltage tracking. The output power is 1000W at 11V input voltage (1250W peak at 12V). The converter area measures only 47mm × 48mm, not including the reverse polarity protection and bulk input capacitance.


This test report is based on the LM5125-Q1. The pin-compatible LM51251-Q1 variant offering additional I²C for diagnostics and control can also be used on this design.

Features


- Very high power density
- Low switching losses due to GaN switches
- Digital and analog voltage tracking
- With I²C control (IC variant dependent)
- High efficiency and high peak output power

Applications

- [Premium audio](#)

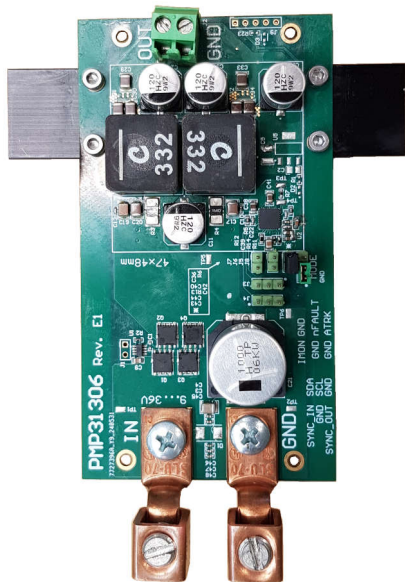

Top of Board

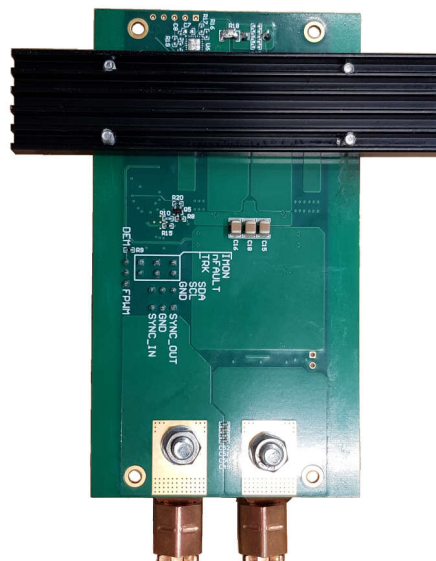

Bottom of Board

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage	9V-18V, 36V peak, full output power at $\geq 11V$
Output Voltage	40.5V
Output Current	31A peak at $12V_{IN}$, 26A at $11V_{IN}$
Switching Frequency	315kHz

1.2 Considerations

- Unless otherwise noted, the input voltage was set to 12V.
- A fan was used to blow air across the board with a heat sink mounted on the GaN switches on the bottom side.
- The 1250W peak output power test was done with 1kW base load and 250W dynamic load set to 2Hz, 20% duty cycle.

1.3 Dimensions

The dimensions of the four-layer board is 115.6mm × 63.6mm × 1.6mm. The thickness of the copper layer is 70 μ m for each layer.

2 Testing and Results

2.1 Efficiency Graph

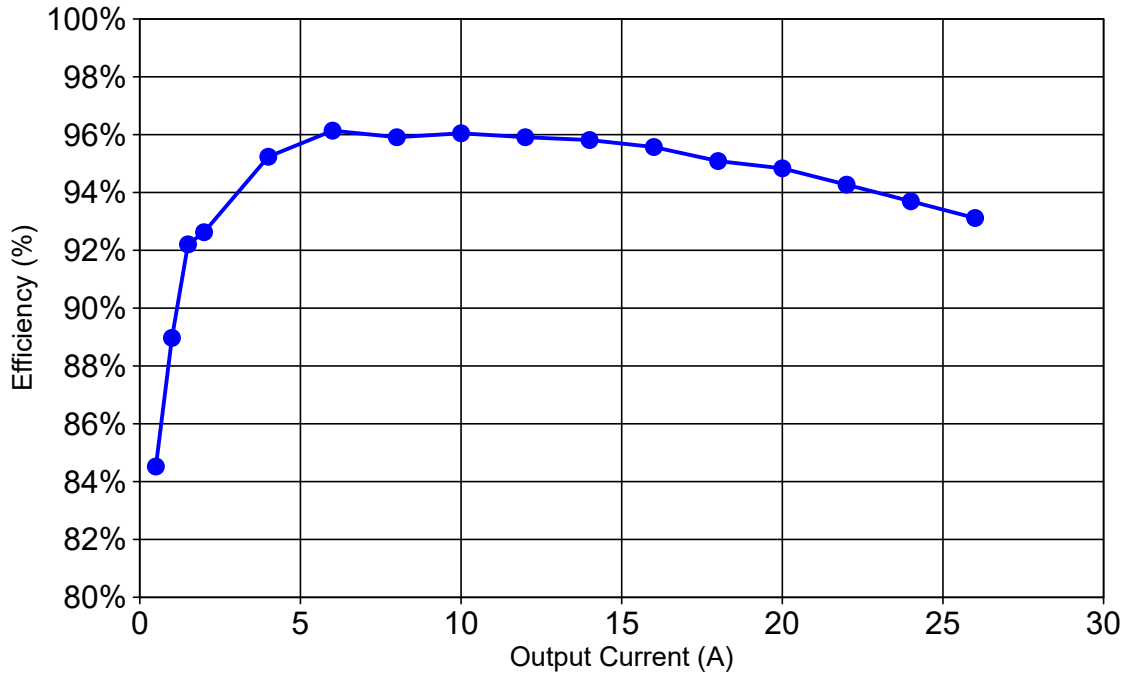


Figure 2-1. Efficiency Graph at 12V Input Voltage

2.2 Efficiency Data

Table 2-1 shows the efficiency data.

Table 2-1. Efficiency Data

OUTPUT CURRENT (A)	EFFICIENCY (%)
0.5	84.5%
1	89.0%
1.5	92.2%
2	92.6%
4	95.2%
6	96.1%
8	95.9%
10	96.0%
12	95.9%
14	95.8%
16	95.6%
18	95.1%
20	94.8%
22	94.3%
24	93.7%
26	93.1%

2.3 Thermal Images

2.3.1 20A Output Current

Figure 2-2 was taken at $12V_{IN}$, 20A output current, after 20 minutes with artificial air flow. The ambient temperature was 25°C . The board image in the [Applications](#) section shows the mounted heat sink.

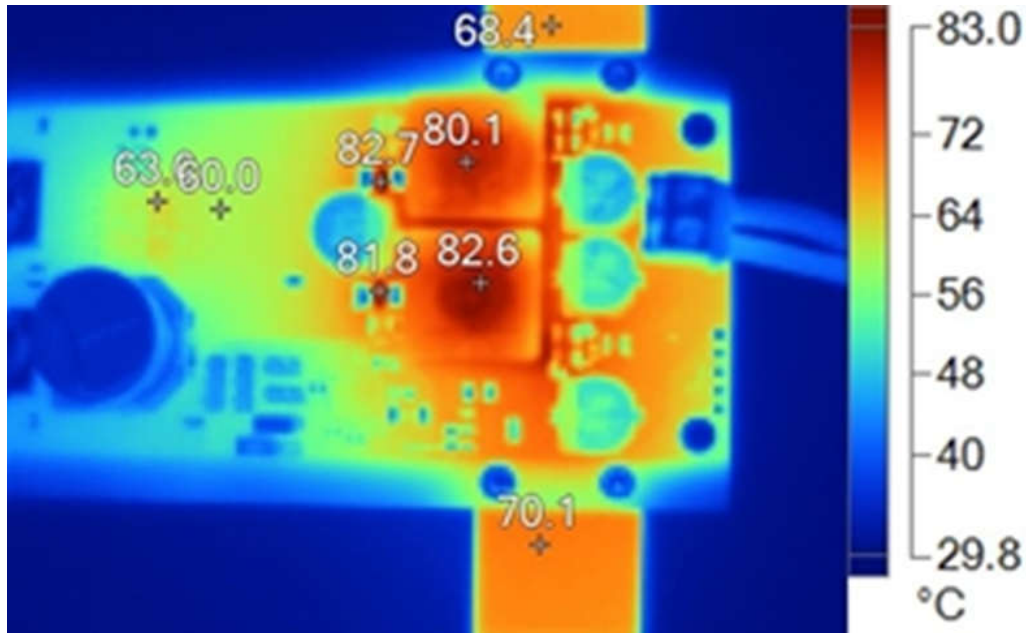


Figure 2-2. Thermal Image at 20A Output Current

2.3.2 26A Output Current

Figure 2-3 was taken at $12V_{IN}$, 26A output current, after 20 minutes with increased artificial air flow. The ambient temperature was 25°C . The board image in the [Applications](#) section shows the mounted heat sink.


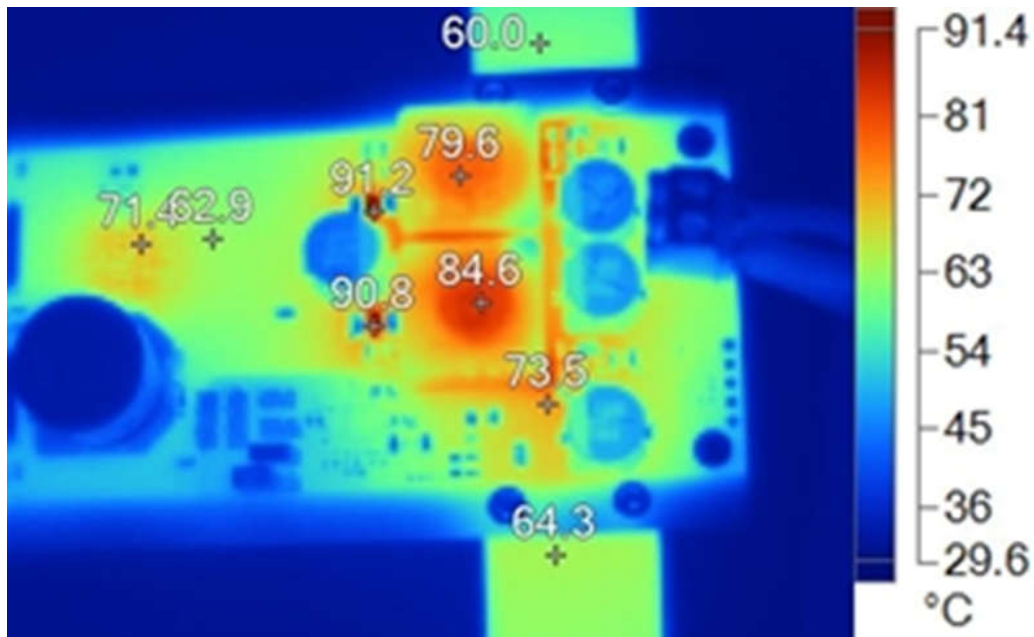


Figure 2-3. Thermal Image at 26A Output Current

2.4 Bode Plots

Figure 2-4 was measured with 11V input voltage and 26A load current.

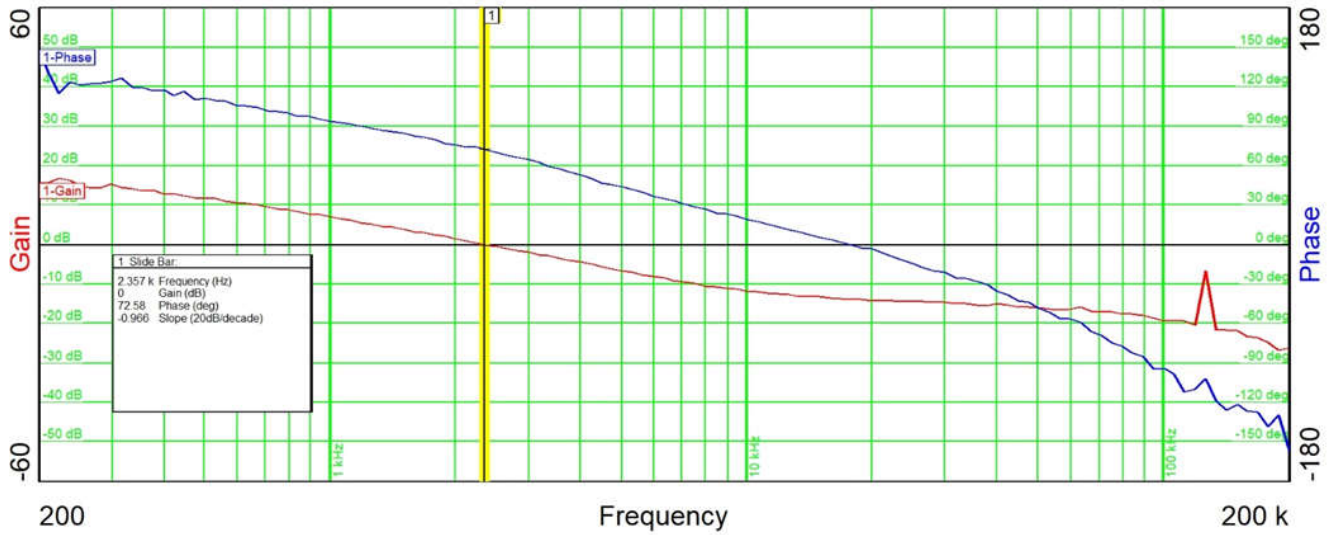


- Crossover frequency = 2.35kHz
- Phase margin = 72°
- Gain margin = 13.9dB

Figure 2-4. Bode Plot

3 Waveforms


3.1 Switching

3.1.1 26A Output Current

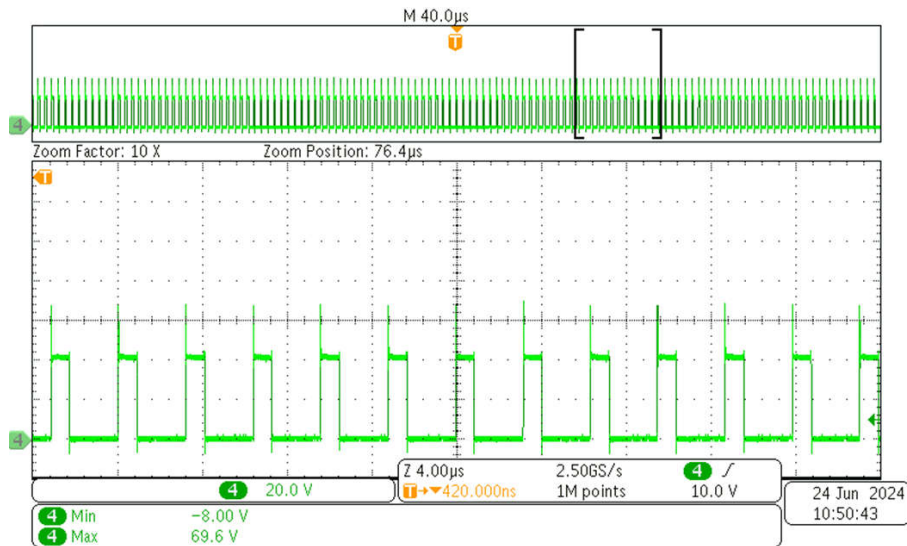

CH4: DC-coupled switch node voltage (scale: 20V/div, 40µs/div, 500MHz bandwidth, 10× zoom)


Figure 3-1. Switching With 12V Input Voltage and 26A Load Current

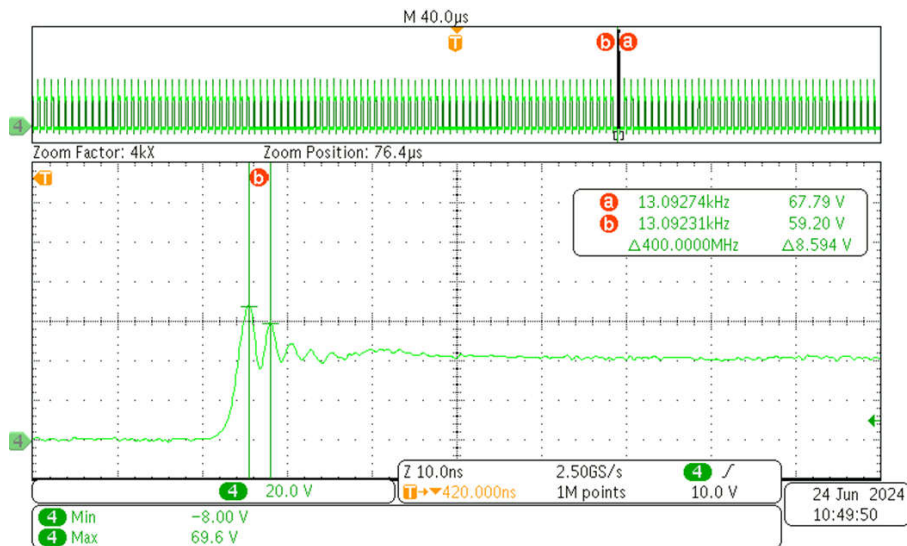

CH4: DC-coupled switch node voltage (scale: 20V/div, 40µs/div, 500MHz bandwidth, 4000× zoom)

Figure 3-2. Switching with 12V Input Voltage and 26A Load Current


3.1.2 4A Output Current

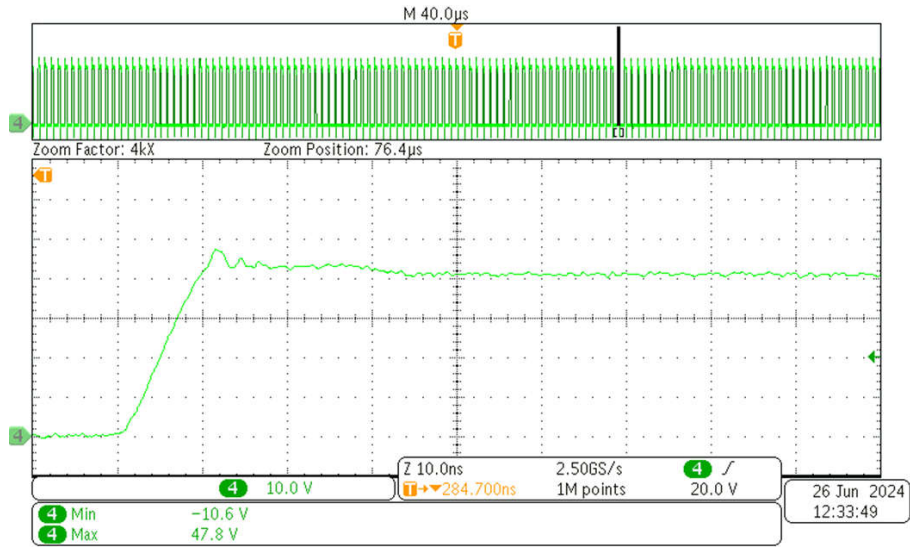

CH4: DC-coupled switch node voltage (scale: 20V/div, 40µs/div, 500MHz bandwidth, 4000× zoom)

Figure 3-3. Switching at 12V Input Voltage and 4A Load Current


3.2 Output Voltage Ripple

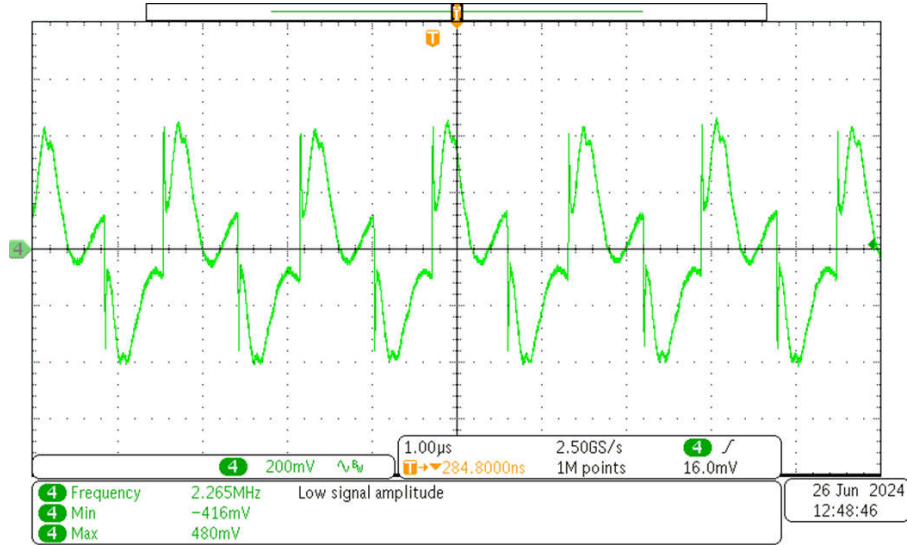

CH4: AC-coupled output voltage (scale: 200mV/div, 1µs/div, 20MHz bandwidth)

Figure 3-4. Output Voltage Ripple at 11V Input and 26A Load Current

3.3 Input Voltage Ripple

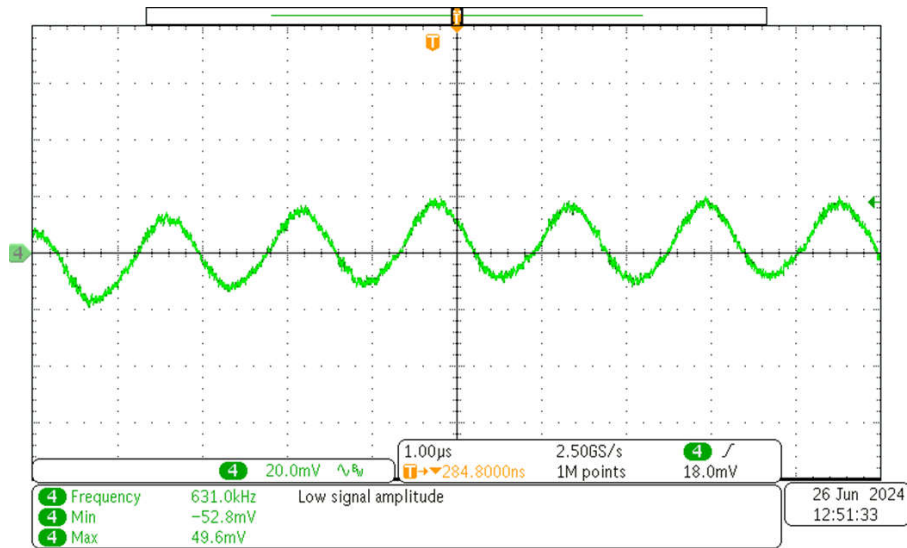


CH4: AC-coupled input voltage (scale: 200mV/div, 1µs/div, 20MHz bandwidth)

Figure 3-5. Input Voltage Ripple at 11V Input Voltage and 26A Load Current

3.4 Load Transients

Figure 3-6 shows the transient behavior with an 8A load step added on top of a 10A DC load (10A DC current not shown).

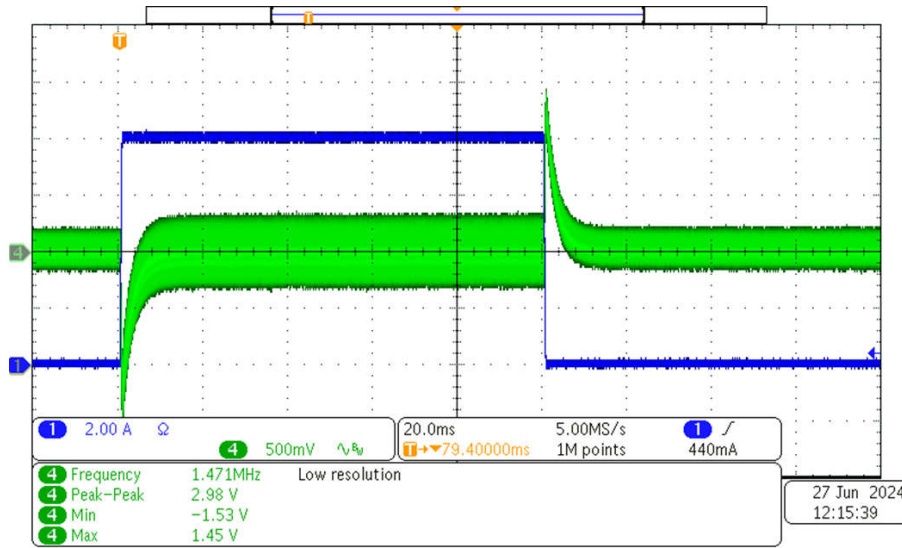


- CH1: Output transient current (scale: 2A/div, 20ms/div)
- CH4: AC coupled output voltage (scale: 500mV/div, 20ms/div, 20MHz bandwidth)

Figure 3-6. Load Transient at 11V Input Voltage

3.5 Start-up Sequence


Figure 3-7 shows the start-up behavior waveform.

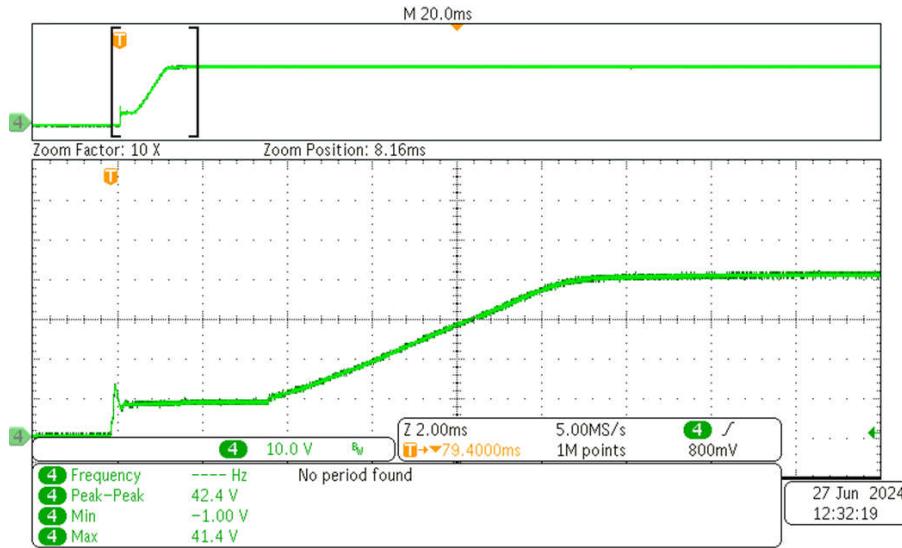

CH4: DC-coupled output voltage (scale: 10V/div, 20ms/div, 20MHz bandwidth, 10× zoom)

Figure 3-7. Start-Up at 11V Input Voltage Into 26A Load Current

3.6 Shutdown Sequence

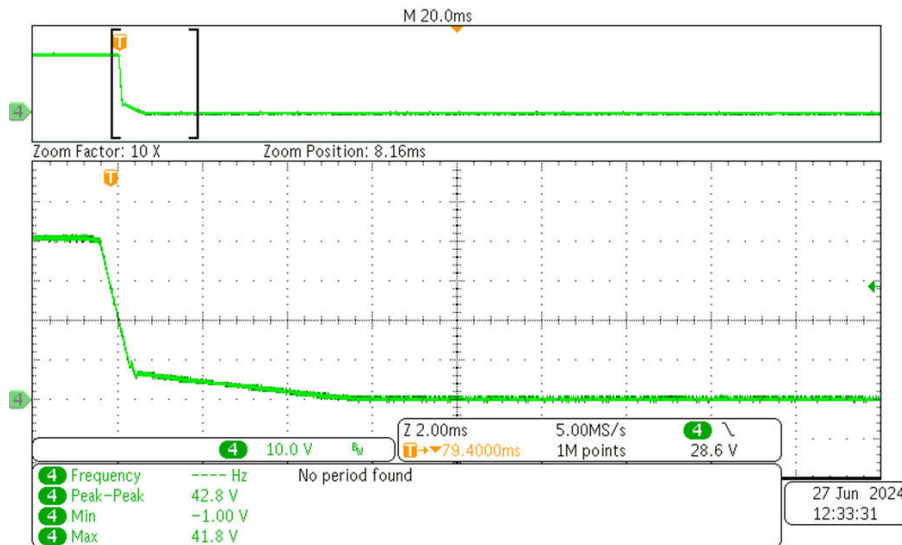

CH4: DC-coupled output voltage (scale: 10V/div, 20ms/div, 20MHz bandwidth, 10× zoom)

Figure 3-8. Shutdown Sequence at 11V Input Voltage with 26A Load Current

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated