

GaN-Based 8kW 3-Phase Totem-Pole PFC and 3-Phase LLC Reference Design



Description

This reference design is a high-density and high efficiency, 8kW power supply. The first stage is a TCM (triangular conduction mode) power factor correction (PFC) converter followed by a delta-delta connected three phase inductor-inductor-capacitor (LLC) converter. Both power stages are implemented with TI high-performance Gallium Nitride (GaN) power switches. The PFC uses a three-phase totem pole PFC in a zero-current detection (ZCD) based control mechanism. The control method operates with variable frequency and maintains zero voltage switching (ZVS) overall operating conditions. The control is implemented with a TMS320F280039C high performance micro-controller and the LMG3527R030 GaN field effect transistor (FET) with integrated


ZCD sensing. The operating frequency range of the converter is approximately between 70kHz and 1.2MHz. The LLC operates between 200kHz and 1.5MHz. The delta-delta resonant tank connection provides reduced root-mean-square (RMS) currents. Control is implemented with a TMS320F28P550SJ high performance micro-controller. The LLC uses LMG3527R030 GaN FETs on the primary and LMG3100R017 GaN FETs on the secondary.

Features

- Peak efficiency at full load: 97.5%
- Dimensions: 700mm × 68.5mm × 32mm

Applications

- [Rack and server power](#)

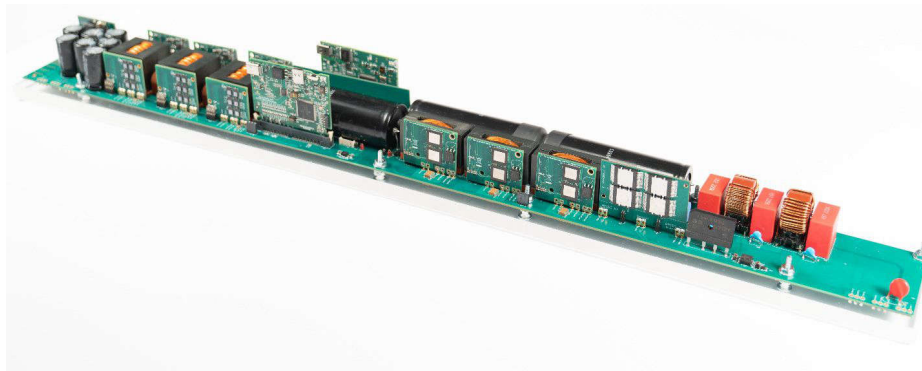

Top Photo

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated