

Analog Engineer's Circuit

Three-Phase Isolated Voltage-Sensing Circuit Using AMC1350




Amplifiers

Design Goals

Voltage Source		AMC1350 Input Voltage		AMC1350 Output Voltage VDD2 / 2 Common Mode ($V_{OUTP} - V_{OUTN}$)		Power Supplies	
V_{MAX}	V_{MIN}	$V_{IN, MAX}$	$V_{IN, MIN}$	$V_{OUT, MAX}$	$V_{OUT, MIN}$	VDD1	VDD2
480V	-480V	5V	5V	4V	-4V	3V-5.5V	3V-5.5V

Design Description

This circuit performs three-phase line-to-neutral, isolated, voltage-sensing measurements utilizing the [AMC1350](#) isolated amplifier and a voltage-divider circuit. The voltage-divider circuit reduces the voltage from $\pm 480V$ to $\pm 5V$ which matches the input range of the AMC1350. The AMC1350 is powered from both a high- and low-side power supply. Typically, the high-side supply is generated using a floating supply or from the low-side using an isolated transformer or isolated DC/DC converter. The AMC1350 can measure differential signals of $\pm 5V$ with a fixed gain of $0.4V/V$. The AMC1350 has a differential input impedance of $1.25M\Omega$ which supports low gain-error and low offset-error signal-sensing in high-voltage applications.

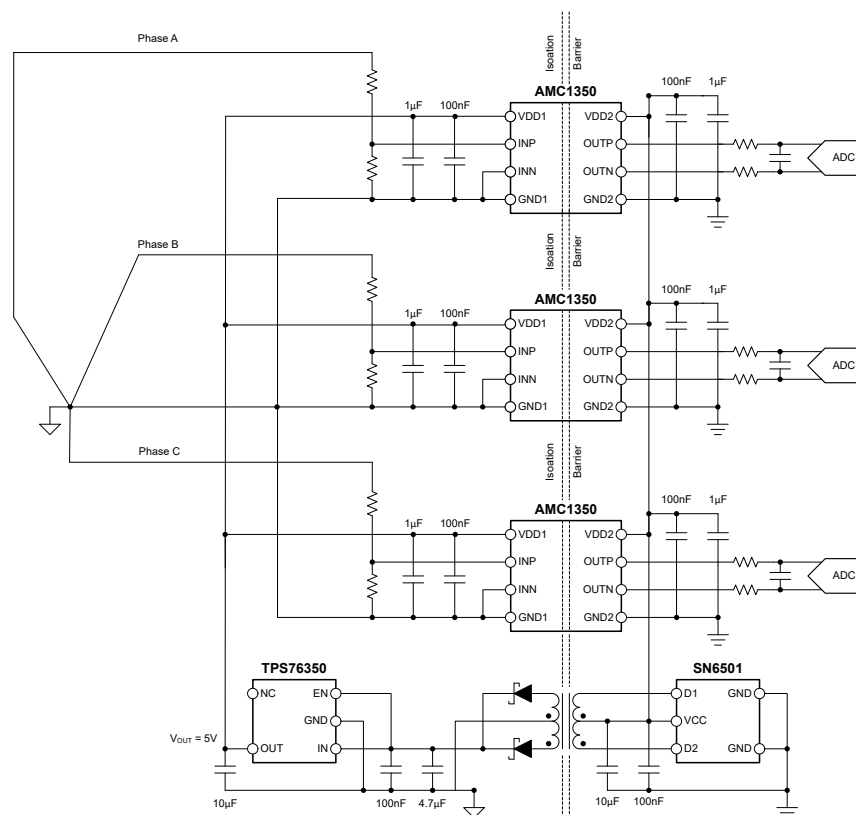

Design Notes

1. The AMC1350 is an excellent choice for voltage-sensing applications due to the high input impedance and low input bias current, both of which minimize the DC errors.
2. Verify the linear operation of the system for the desired input signal range. This is verified using simulation in the [DC Transfer Characteristics](#) section.
3. Make sure the resistors used in the resistor divider circuit are capable of reducing the source input voltage to the AMC1350 input voltage range of $\pm 5V$.
4. Make sure the resistors in the resistor divider circuit have sufficient operating current and voltage ratings.
5. Verify that the AMC1350 input current is less than $\pm 10mA$ as stated in the absolute maximum ratings table of the data sheet.

Design Steps

1. Calculate the ratio from the voltage source to the input of the AMC1350 for the voltage-divider circuit.

$$\frac{5V_{AMC1350, INPUT}}{480V} = 0.010417$$

2. The typical input impedance of the AMC1350 is $1.25M\Omega$. This impedance is in parallel with resistor R_5 and must be considered when designing the voltage-divider circuit. Select $1M\Omega$ resistors for R_1 , R_2 , R_3 , and R_4 . Using the ratio from the previous step and the following voltage-divider equation, solve for the equivalent resistance required for the voltage-divider parallel combination (\parallel) of R_5 and the AMC1350 input impedance.

$$\frac{R_5 \parallel R_{IN, AMC1350}}{R_1 + R_2 + R_3 + R_4 + R_5 \parallel R_{IN, AMC1350}} = 0.010417$$

$$\frac{R_5 \parallel R_{IN, AMC1350}}{4M\Omega + R_5 \parallel R_{IN, AMC1350}} = 0.010417$$

$$R_5 \parallel R_{IN, AMC1350} = 42,736.37\Omega = R_{EQ}$$

3. Substituting $1.25M\Omega$ for the AMC1350 input impedance and using the following equation, solve for R_5 . Use the [analog engineer's calculator](#) to determine the closest standard value for R_5 .

$$R_{EQ} = 42,736.37\Omega = \frac{R_5 \times R_{IN, AMC1350}}{R_5 + R_{IN, AMC1350}} = \frac{R_5 \times 1.25M\Omega}{R_5 + 1.25M\Omega}$$

$$42,736.37\Omega(R_5 + 1.25M\Omega) = R_5 \times 1.25M\Omega$$

$$R_5 = 44.249k\Omega; \text{ closest standard value} = 44k\Omega$$

4. Verify that the equivalent resistance is close to the calculated resistance from step 2.

$$R_{EQ} = \frac{R_5 \times R_{IN, AMC1350}}{R_5 + R_{IN, AMC1350}} = \frac{44k\Omega \times 1.25M\Omega}{44k\Omega + 1.25M\Omega} = 42.503k\Omega$$

5. Verify that the voltage-divider circuit is within a reasonable error tolerance. For the following calculation, the input resistance of the AMC1350 is assumed to be the typical value of $1.25M\Omega$ and this results in an error of 5.1%. However, consider that the input resistance varies from device to device due to variations in manufacturing tolerance. If this error range is unacceptable then either a calibration must be performed or the resistance of the voltage-divider circuit can be scaled down.

$$\frac{42.503k\Omega}{4.042503M\Omega} = 0.01051$$

$$\text{Error}\% = \frac{|\text{Actual} - \text{Calculated}|}{\text{Calculated}} \times 100 = \frac{|0.01051 - 0.010417|}{0.010417} \times 100 = 0.9\%$$

- Calculate the current flowing through the voltage-divider circuit from the voltage source to make sure that the power dissipation does not exceed the ratings of the resistor. For additional details, see [Considerations for High Voltage Measurements](#).


$$V = IR; \frac{V}{R} = \frac{480V}{4M\Omega + 42k\Omega} = 118.69\mu A$$

- Since the gain of the voltage divider is 0.010417 and the gain of the AMC1350 is 0.4V/V, the output voltage can be calculated for an input voltage of 480V using the transfer function equation, $V_{OUT} = \text{Gain} \times V_{IN}$.

$$V_{OUT} = \frac{5}{480} \times 0.4 \times 480 = 2V$$


DC Transfer Characteristics

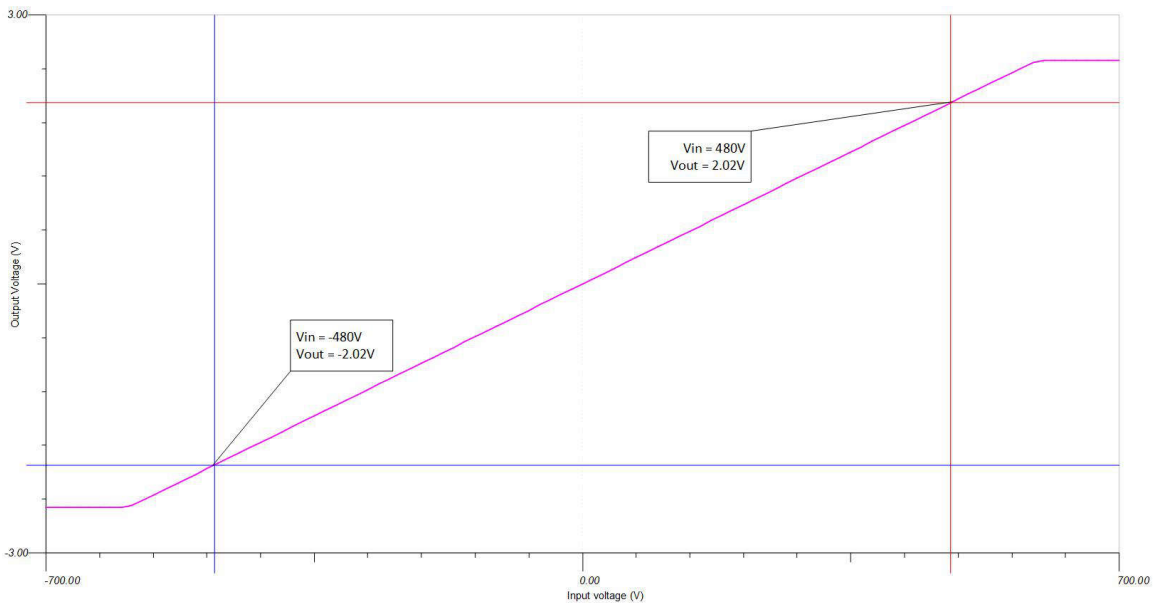The following graph shows the simulated output of the AMC1350 for a $\pm 480V$ input. The output voltage is about 2.02V for an input voltage of 480V, as calculated in [step 7](#).




AC Transfer Characteristics

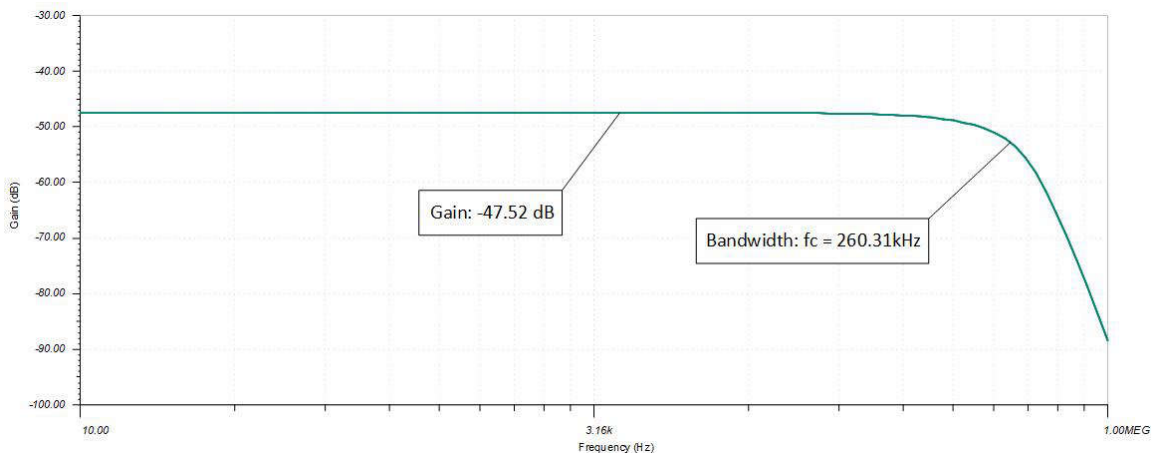The simulated gain is $-47.52dB$ (or $0.0041V/V$) which closely matches the expected gain for the voltage divider and AMC1350.



Transient

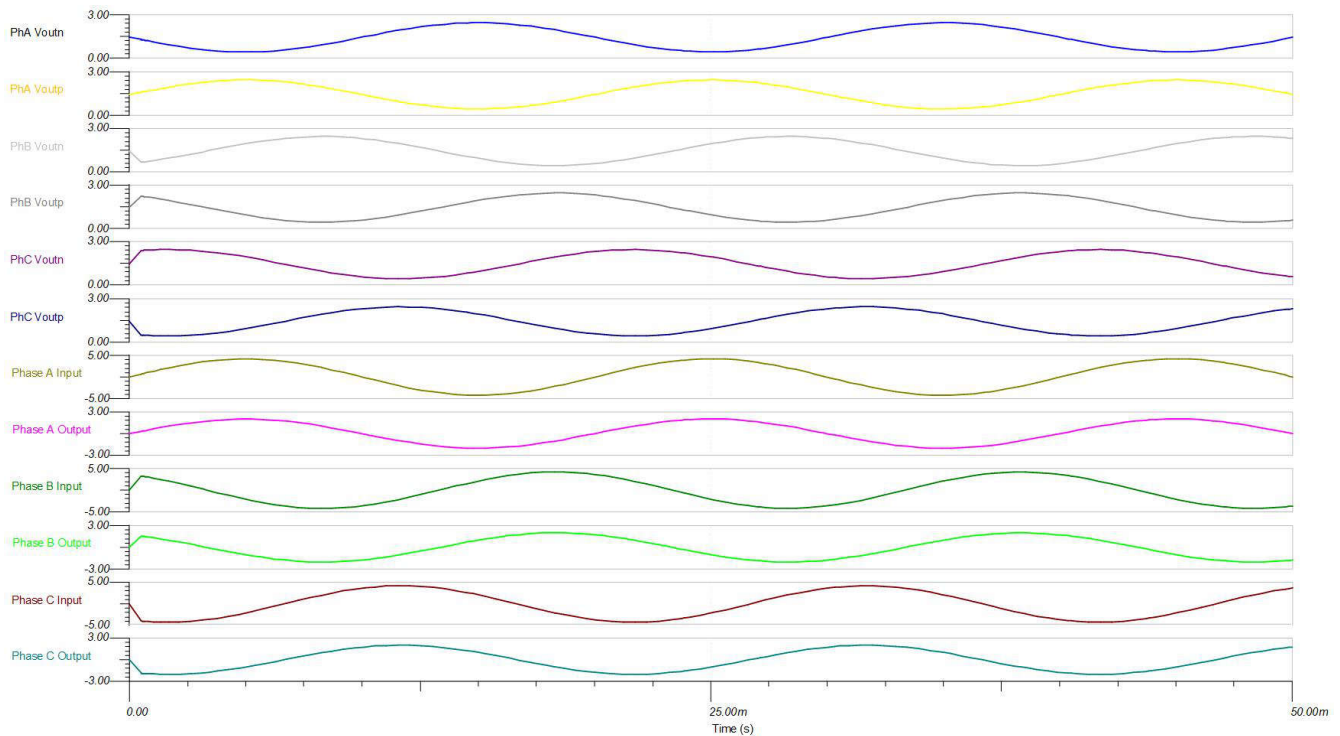The following simulation shows the input and output signals of the AMC1350.



References


1. Texas Instruments, [An Engineer's Guide to Isolated Signal Chain Solutions E-Book](#)
2. Texas Instruments, [Split-Tap Connection for Line-to-Line Isolated Voltage Measurement Using AMC3330 Analog Engineer's Circuit](#)
3. Texas Instruments, [Analog Circuits Design and Development](#)
4. Texas Instruments, [TI Precision Labs](#)

Design Featured AMC0330D, AMC0330R, AMC0330S

AMC0330D	
VDD1	3V to 5.5V
VDD2	3V to 5.5V
Input Voltage Range	$\pm 1V$
Nominal Gain	2
Input Resistance	1G Ω (typical)
Output Bandwidth	110kHz (typical)
Input Offset Voltage and Drift	$\pm 1.5mV$ (maximum), $\pm 10\mu V/^{\circ}C$ (maximum)
Gain Error and Drift	$\pm 0.25\%$ (maximum), $\pm 40ppm/^{\circ}C$ (maximum)
Nonlinearity	0.05% (maximum)
Isolation Transient Overvoltage	7kV _{PEAK}
Working Voltage	1kV _{RMS}
Common-Mode Transient Immunity, CMTI	50V/ns (minimum)
AMC0330D , AMC0330R , AMC0330S	

Design Alternate AMC131M03

The **AMC131M03** is a precision, low-power, isolated, three-channel delta-sigma ($\Delta\Sigma$) analog-to-digital converter (ADC) with reinforced isolation that, in conjunction with a voltage divider, can also be used to perform three-phase, line-to-neutral, isolated, voltage-sensing measurements. Each channel of the AMC131M03 needs to connect to one of the three-phase voltages through a resistor divider to scale down to the input voltage range of the ADC. This device features a fully integrated isolated DC/DC converter that allows single-supply operation of 3.3V or 5V from the low-side of the device. When the measurements are conducted by the device, the ADC converts the three-phase measurements into digital data. The digitized data can be output by the device through serial peripheral interface (SPI) communication, allowing for direct communication to a microcontroller. The dynamic range, size, feature set, and power consumption are optimized for cost-sensitive applications requiring simultaneous sampling.

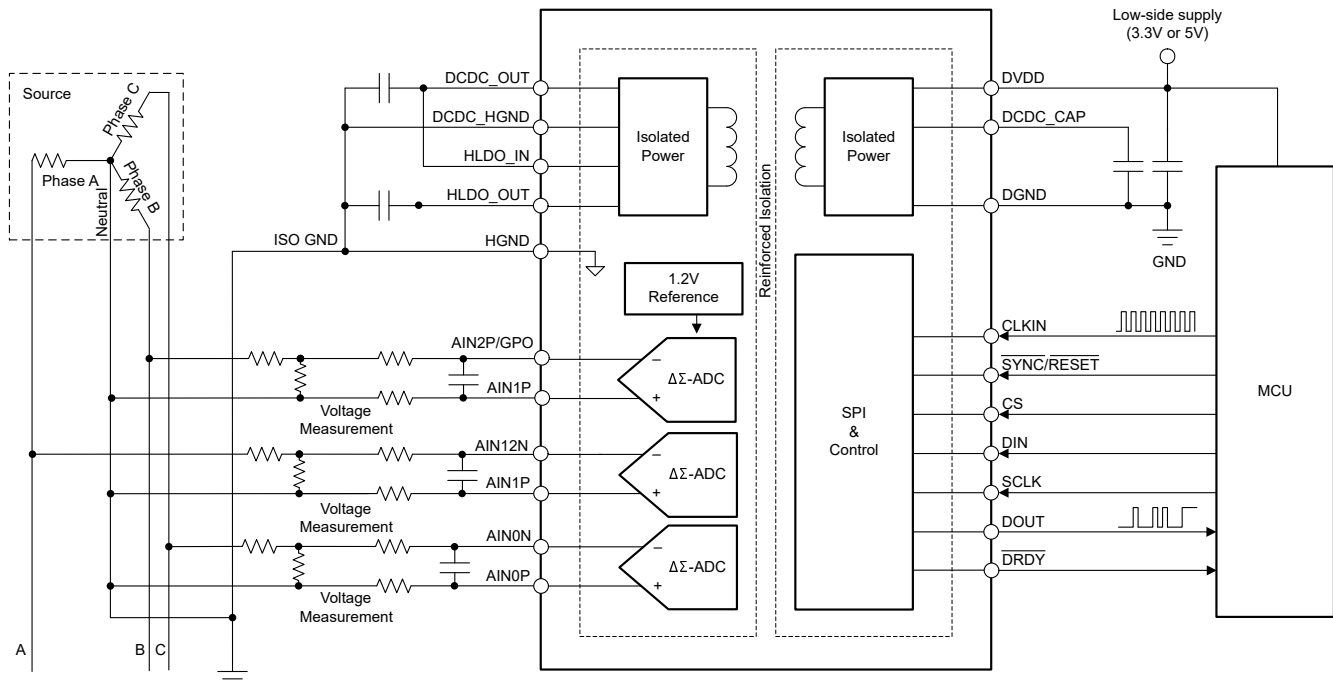

AMC131M03	
V_{DVDD}	3V to 5.5V
Input Voltage Range	V_{ref} / Gain
Gain	Programmable gain up to 128
Input Offset Error and Drift (Channel 0,1)	$\pm 100\mu\text{V}$ (typical), $\pm 0.5\mu\text{V}/^\circ\text{C}$ (maximum)
Input Offset Error and Drift (Channel 2)	$\pm 120\mu\text{V}$ (typical), $\pm 0.5\mu\text{V}/^\circ\text{C}$ (maximum)
Gain Error and Drift (Channel 0)	$\pm 0.2\%$ (maximum), $\pm 25\text{ppm}/^\circ\text{C}$ (maximum)
Gain Error and Drift (Channel 1,2)	$\pm 1\%$ (maximum), $\pm 25\text{ppm}/^\circ\text{C}$ (maximum)
Nonlinearity	6ppm of FSR
Isolation Transient Overvoltage	$7070V_{PEAK}$
Working Voltage	$1.2kV_{RMS}$
Common-Mode Transient Immunity, CMTI	100V/ns (minimum)

AMC131M03

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated