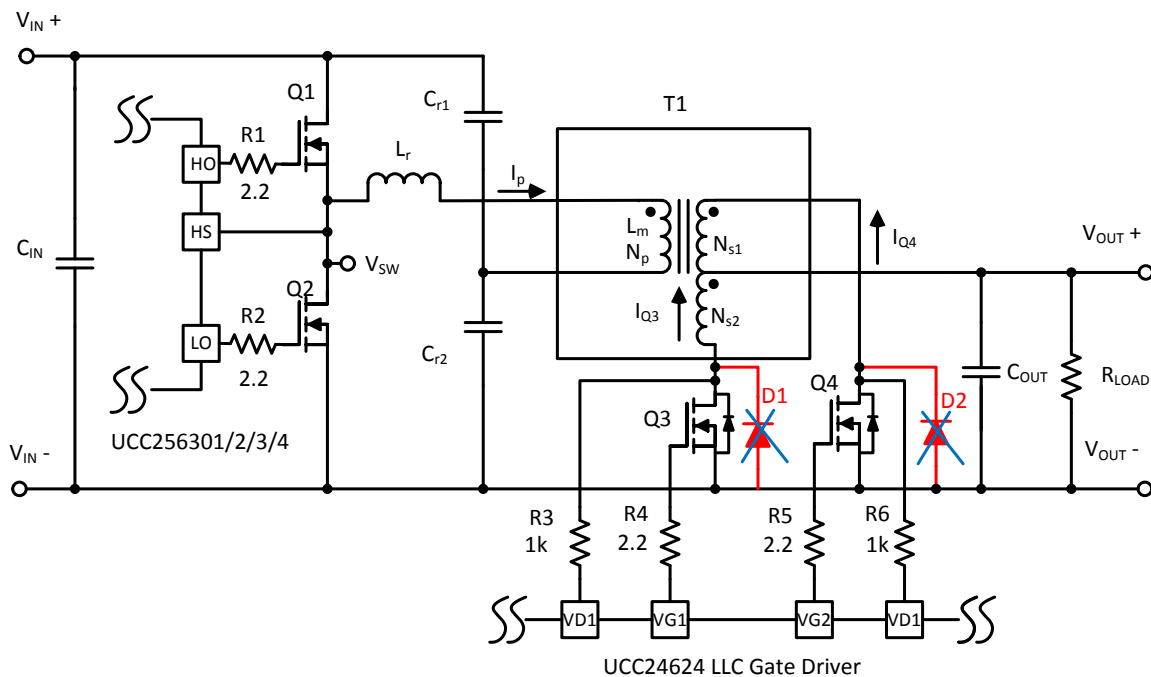


# Improving ZVS and Efficiency in LLC Converters

Michael O'Loughlin

## 1 Introduction

In medium (150 W) to high power (600 W +) high input voltage ( $V_{IN}$ ) DC to DC step down converter applications the resonant LLC topology has become a popular choice, due to its ability to achieve zero voltage switching (ZVS) on the converter's primary switch node ( $V_{sw}$ ) over a wide load range ( $R_{LOAD}$ ). When design correctly the design will achieve zero current switching (ZCS) on the power converter's secondary rectifiers removing secondary side rectifier switching losses. The LLC with ZVS on the primary and ZCS on the secondary removes switching losses power converter and reduces power converter heating allowing the converter to be designed for high switching frequencies and greater power densities. To improve the efficiency of the LLC converter even further output rectifiers can be replaced with synchronous rectifiers (SR) using TI's new dual SR driver the UCC24624 (Fig. 1) to drive these FETs. This application brief will give advice, tips and guidance on how to design an LLC that uses SRs to achieve ZVS on the primary and ZCS on the secondary. Please note that this application brief is supplemental to other Texas Instruments application notes, seminar papers and tech notes referenced at the end of this application brief [1..6].



**Figure 1. LLC Step Down Converter with Synchronous Rectifiers (SR)**

## 2 Quick Review of LLC and System Benefits

The LLC converter (Figure 1) consists of an input filter capacitor ( $C_{IN}$ ) a half bridge power stage drive formed by Q1 and Q2 and driven/controlled by an LLC controller (UCC256301/2/3/4). This converter for galvanic isolation uses transformer (T1) to step down/or up the DC input voltage. This design also requires output rectifiers that consist of two diodes (D1, D2) or two synchronous rectifiers (Q3, Q4) and an output filter capacitor ( $C_{OUT}$ ). To control the output voltage ( $V_{OUT}$ ) Q1 and Q2 are operated at 50% duty cycle and are 180 degrees out of phase with a voltage controlled oscillator. This will put a square wave across an LLC reactance divider network consisting of a resonant inductor ( $L_r$ ), the transformers primary magnetizing inductance ( $L_m$ ) and a resonant capacitor/s ( $C_r = C_{r1} + C_{r2}$ ). When the converter is operating at frequency ( $f_r$ ) where  $L_r$  and  $C_r$  are in resonance. The reactance of  $L_r$  and  $C_r$  at  $f_r$  will be 180 degrees out of phase in resonance and the reactance will cancel each other out in the total reactance of the reactance divider. In this configuration half the input voltage ( $V_{IN}$ ) will be seen across the primary of the transformer and transferred to the secondary across the transformer turns ratio ( $N_{s1/2}$ ) to the output ( $V_{OUT}$ ).

$$V_{OUT} \approx \frac{V_{IN}}{2} \times \frac{N_s}{N_p} \tag{1}$$

When designed correctly and delaying ( $t_d$ ) the turn on of FET Q1 and Q2 this allows time for the energy stored in the magnetizing inductance ( $L_m$ ) to swing the switch node ( $V_{SW}$ ) from rail ( $V_{IN+}$ ) to rail ( $V_{IN-}$ ) and achieve zero voltage switching (ZVS). This reduces switching losses, heating and increases overall system efficiency and power density. Please refer to figure 2 for the LLC's switch node, FETs Q1 and Q2's gates (Q1g, Q2g) and primary transformer (T1) current ( $I_p$ ) operating at the converters resonant frequency and achieving ZVS.



Figure 2. LLC ZVS Oscilloscope Waveforms

Another benefit of using an LLC converter is when the converter is operating at the resonant frequency ( $f_r$ ) or below  $f_r$  the secondary rectifiers achieve ZCS to improve system efficiency. Figure 3 shows the gate drives of the synchronous rectifiers (Q3g and Q4g); as well as, the output rectifiers' drain currents ( $I_{Q3}$  and  $I_{Q4}$ ). From this waveform it can be observed that the SRs are ZCS.



Figure 3. LLC ZVS Oscilloscope Waveforms

The SRs power dissipation ( $P_{Q3}$  and  $P_{Q4}$ ) can be estimated with the following equation at the resonant frequency ( $f_r$ ). Where  $Q_{Q3g}$  and  $Q_{Q4g}$  are the SR's gate charge,  $V_{Q3g}$  is the voltage the gate of the SRs is driven too,  $R_{DS(on)Q3}$  is the on resistance of the SRs and  $I_{OUT}$  is the output current of the power converter.

$$P_{Q3} = P_{Q4} = Q_{Q3g} \times V_{Q3g} \times f_r + R_{DS(on)Q3} \times \left(\frac{\pi}{4} \times I_{OUT}\right)^2 \quad (2)$$

3 Tip 1, Select the FETs for the design before designing your transformer (T1):

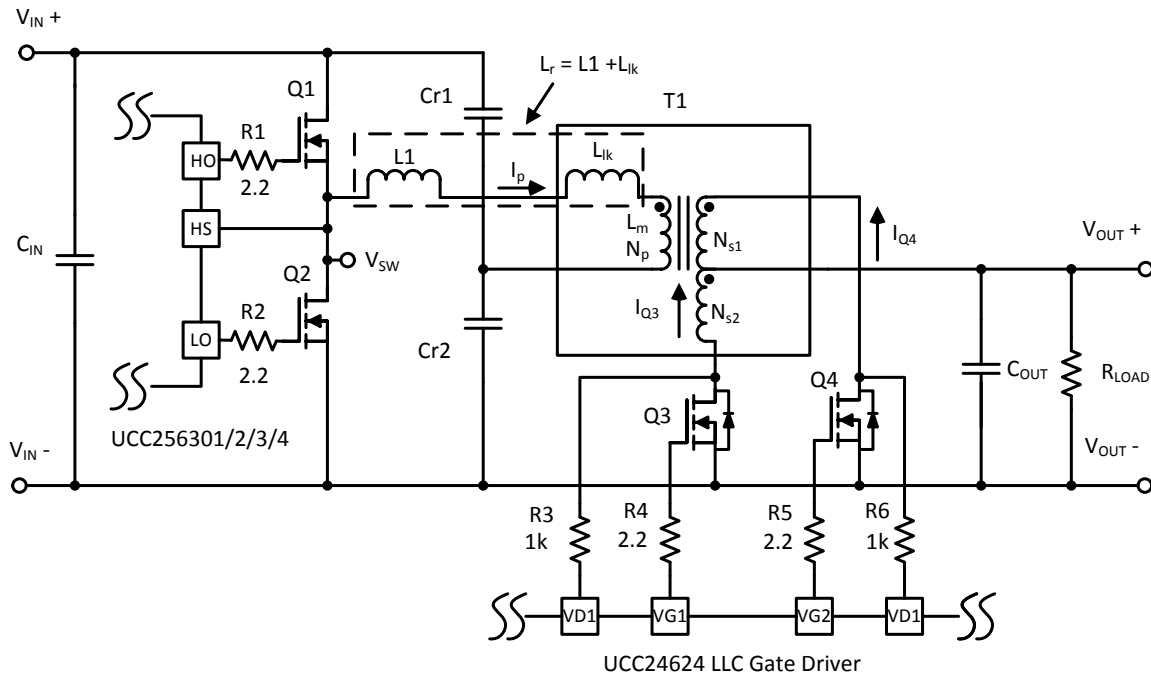


Figure 4. LLC with SRs

To design the transformer it is recommended that the FETs are selected for the design first, to avoid redesigning the transformer later. It is necessary to know Q1 and Q2's approximate switch node capacitance related to time ( $C_{O(tr)}$ ); as well as, these FETs' on resistances  $R_{DS(on)}$ . It will also be necessary to know the output rectifiers' (Q3 and Q4) on resistance to design the transformer as well.

This application brief will review how to calculate the transformer's primary magnetizing inductance ( $L_m$ ) and the transformer primary to secondary turns ratio ( $N_{ps}$ ) based on the input and output requirements and the FETs'  $C_{O(tr)}$  and  $R_{DS(on)}$ . It will also go through a 120 W design example. Table 1, shows the input and output power requirements of a 120 W LLC power converter, as well as, the FET critical parameters that will be required for calculating  $N_{ps}$  and  $L_m$ . It is recommended to keep the input voltage range within +/- 15% of the typical value ( $V_{IN}$ ) for the best LLC performance.

**Table 1. 120W LLC Critical Design Parameter's for T1 Calculations**

	MINIMUM	TYPICAL	MAXIMUM	UNIT S	DESCRIPTION
Input Voltage	340 ( $V_{IN(min)}$ )	390 ( $V_{IN}$ )	410 ( $V_{IN(max)}$ )	V	LLC Input Voltage
$V_{OUT}$		12		V	LLC Output Voltage
$I_{OUT}$		10		A	LLC Output Current
$C_{O(tr)Q1}$		160		pF	Effective FET Output Capacitance Time Related
$C_{O(tr)Q2}$		160		pF	Effective FET Output Capacitance Time Related
$R_{DS(on)Q1}$		220		m $\Omega$	FET on Resistance
$R_{DS(on)Q2}$		220		m $\Omega$	FET on Resistance
$R_{DS(on)Q3}$		2.5		m $\Omega$	FET on Resistance
$R_{DS(on)Q4}$		2.5		m $\Omega$	FET on Resistance
$f_r$		100		kHz	Resonant Frequency

#### 4 Tip 2, Design the Transformer (T1) for ZVS

To select the transformer  $N_{ps}$  requires estimating the transformer primary peak current ( $I_{ppk}$ ) and the output rectifier peak currents ( $I_{Q3pk}$  and  $I_{Q4pk}$ ).

$$I_{ppk} \approx \frac{I_{OUT} \times V_{OUT}}{V_{IN}} \times \frac{\pi}{2} = \frac{10A \times 12V}{390V} \times \frac{\pi}{2} = 483mA \quad (3)$$

$$I_{Q3pk} = I_{Q4pk} \approx I_{OUT} \times \frac{\pi}{2} = 10A \times \frac{\pi}{2} = 15.7A \quad (4)$$

Once the FET peak currents are calculated  $N_{ps}$  can be calculated. For this example based on the design requirements of table 1 this design would require a turn's ratio of 16.2

$$N_{ps} = \frac{N_p}{N_{s1}} = \frac{N_p}{N_{s2}} = \frac{V_{IN} - I_{ppk} \times R_{DS(on)Q1}}{2 \times (V_{OUT} + I_{Q3pk} \times R_{DS(on)Q3})} = \frac{390V - 483mA \times 220m\Omega}{2 \times (12V + 15.7A \times 2.5m\Omega)} = 16.2 \quad (5)$$

Please note that it is understood that fractional turns may be difficult to achieve in a transformer design, just select a turns ratio that is close to the calculated value. For this design we selected and  $N_{ps}$  of 16.

$$N_{ps} = 16 \quad (6)$$

Once the transformer turn's ratio is selected, the transformer's primary magnetizing inductance ( $L_m$ ) should be chosen to insure the design can achieve ZVS over the entire input voltage range of  $V_{IN(min)}$  to  $V_{IN(max)}$ . Start by selecting the delay time ( $t_d$ ) to achieve ZVS to be 1% of the resonant frequency period.

$$t_d = \frac{0.01}{f_r} = \frac{0.01}{100kHz} = 100ns \quad (7)$$

Next calculate  $d_v/d_t$  based on  $V_{IN(max)}$  and  $t_d$ . Please note that some controllers such as the UCC256301/2/3/4 devices have adaptive delays to help achieve ZVS. **However, the UCC256301/2/3/4 devices have a minimum  $d_v/d_t$  requirement of 1 V/ns. To avoid circuit misbehavior it is recommended that the  $d_v/d_t$  that is used to calculate  $I_m$  is at least 4 times this minimum requirement, to exceed this minimum requirement with margin, (Equation 10).**

$$\frac{1V \times 4}{1ns} \geq \frac{d_v}{d_t} = \frac{V_{IN(max)}}{t_d} = \frac{410V}{100ns} = \frac{4.1V}{ns} \quad (8)$$

Once the switch node  $d_v/d_t$  is determined the transformer's magnetizing current ( $I_m$ ) and maximum primary magnetizing inductance ( $L_m$ ) can be calculated.

$$I_m = \frac{d_v}{d_t} \times 2 \times C_{O(tr)Q1} = \frac{4.1V}{1ns} \times 2 \times 160pF \approx 1.3A \quad (9)$$

$$L_m \leq \frac{V_{IN(min)} \times 0.5}{I_m \times 2 \times f_r} = \frac{340V \times 0.5}{1.232A \times 2 \times 100kHz} = 654\mu H \quad (10)$$

For this design example we used a transformer that had a turn's ratio of 16 and a  $L_m$  of 550 $\mu$ H and had a leakage inductance of 27.5  $\mu$ H. Please note that  $L_{lk}$  is part of the resonant inductance and needs to be considered when sizing L1.

$$L_m = 550\mu H \quad (11)$$

$$L_{lk} = 27.5\mu H \quad (12)$$

## 5 Tip 3, Select Resonant Capacitors ( $C_r = C_{r1} + C_{r2}$ ):

To calculate the resonant capacitor ( $C_r$ ) requires calculating the effective reflected impedance ( $R_e$ ) seen by the primary of the transformer.

$$R_e = \frac{8 \times N_{ps}^2 \times V_{OUT}}{\pi^2 \times I_{OUT}} = \frac{8 \times 16^2 \times 12V}{\pi^2 \times 10A} \approx 249\Omega \quad (13)$$

$C_r$  is the sum of  $C_{r1}$  and  $C_{r2}$  and can be calculated based on  $R_e$ ,  $f_r$  and a target  $Q_e$ . For this example we chose a  $Q_e$  of 0.15 to keep the control to output transfer function peaking to a minimum.

$$C_r = \frac{1}{2 \times \pi \times Q_e \times R_e \times f_r} = \frac{1}{2 \times \pi \times 0.15 \times 249\Omega \times 100kHz} \approx 42.6nF \quad (14)$$

For this design example we used two standard 22 nF capacitors for  $C_{r1}$  and  $C_{r2}$ , which resulted in a  $C_r$  of 44 nF.

$$C_r = C_{r1} + C_{r2} = 22nF + 22nF = 44nF \quad (15)$$

## Tip 4, Set $L_r$ by properly selecting L1, but don't forget to include T1's $L_{lk}$ in the calculation:

The resonant inductance ( $L_r$ ) needs to be calculated based on  $C_r$ ,  $Q_e$  and  $R_e$ .

$$L_r = C_r \times Q_e^2 \times R_e^2 = 44nF \times (249\Omega)^2 \times (0.145)^2 \approx 57.4\mu H \quad (16)$$

With  $L_r$  and  $L_{lk}$  inductor L1 can be calculated.

$$L1 = L_r - L_{lk} = 57.4\mu H - 27.5\mu H = 29.9\mu H \quad (17)$$

In this example we used a high current, high voltage, 33  $\mu$ H inductor for L1.

$$L1 = 33\mu H \quad (18)$$

## 6 Tip 5, Double check to make sure the transformer with $L_r$ , $C_r$ and $N_{ps}$ meets the design requirements

Calculate the designs minimum gain required  $Mg_{min}$ :

$$Mg_{min} = \frac{N_{ps} \times (V_{OUT} + I_{Q3pk} \times R_{DS(on)Q3})}{\frac{(V_{IN(max)} - I_{Q1pk} \times R_{DS(on)Q1})}{2}} = \frac{16 \times (12V + 15.7A \times 2.5m\Omega)}{\frac{(410V - 483mA \times 220m\Omega)}{2}} \approx 0.94 \quad (19)$$

Calculate the designs maximum gain required  $Mg_{max}$ :

$$Mg_{max} = \frac{N_{ps} \times (V_{OUT} + I_{Q3pk} \times R_{DS(on)Q3})}{\frac{(V_{IN(min)} - I_{Q1pk} \times R_{DS(on)Q1})}{2}} = \frac{16 \times (12V + 15.7A \times 2.5m\Omega)}{\frac{(340V - 483mA \times 220m\Omega)}{2}} \approx 1.133 \quad (20)$$

Plot Gain vs Frequency ( $Mg(f)$ ):

$$L_n = \frac{L_m}{L_1 + L_{lk}} = \frac{550\mu H}{33\mu H + 27.5\mu H} \approx 9.09 \quad (21)$$

$$M_{g(f)} = \left| \frac{L_n \times \left(\frac{f}{f_r}\right)^2}{\left[ (L_n + 1) \times \left(\frac{f}{f_r}\right)^2 - 1 \right] + j \times \left[ \left(\left(\frac{f}{f_r}\right)^2 - 1\right) \times \left(\frac{f}{f_r}\right) \times Q_e \times L_n \right]} \right| \quad (22)$$

From the  $M_{g(f)}$  curve in figure 6 it can be observed that the transformer's turns ratio and resonant components will meet the systems gain requirements of  $M_{g\_min}$  to  $M_{g\_max}$ . Please note when using a PFC pre-regulator the converter will be operating at  $f_r$  nominally and will only vary the switching frequency ( $f$ ) during large signal transients.

 


Figure 5. Plot of  $M_{g(f)}$  vs frequency ( $f_{sw}$ )

## 7 Tip 6, Avoid ZCS on primary switch node ( $V_{sw}$ )

Please note that ZCS on the output rectifiers will not cause issues with circuit performance. However, when using an LLC, ZCS on the primary switch node ( $V_{sw}$ ) can lead to feedback control misbehavior or latch up if older LLC controllers are used; such as, the UCC25600 that do not have primary ZCS detection/correction.

If an older LLC controller, such as the UCC25600, to avoid operating in the ZCS frequency range just requires setting the minimum frequency ( $f_{min}$ ) to greater than the  $f_{pp}$  frequency (fig 6).

$$f_{min} > f_{pp} = \frac{f_r}{\sqrt{L_n + 1}} = \frac{100kHz}{\sqrt{9.00 + 1}} \approx 31.5kHz \quad (23)$$

In this example, I would suggest setting  $f_{min}$  to 40 kHz. This is generally done by selecting a resistor to program this frequency. Refer to the UCC25600 data sheet for details on how to set  $f_{min}$ .

$$f_{min} = 40kHz \quad (24)$$

**If the design is using newer LLC controllers, UCC256301/2/3/4, there is no need to worry about programing  $f_{min}$  or operating in the ZCS frequency range. These devices have internal circuitry that has primary ZCS detection and frequency correction to avoid feedback control latch up and does not require an external resistor for programing  $f_{min}$ . If ZCS is detected these LLC controller will automatically increase the switching frequency ( $f_{sw}$ ) so the converter will operate above  $f_{pp}$  and operate in the ZVS frequency range.**



## 8 Evaluating Design Performance

A 120W LLC prototype was constructed based on the design example, table 1. The design used a UCC256302 LLC controller; as well as, the UCC24624 LCC SR driver.

The  $N_{ps}$ ,  $L_m$ ,  $L_r$  and  $C_r$  that were selected for an  $f_r$  of 100 kHz that would occur at a  $V_{IN}$  of 385 V. In the prototype circuit an  $f_r$  of roughly 100.9 kHz was achieved at  $V_{IN}$  of 380 V. These values were very close to the design target and achieved ZVS quite easily. Please refer to figure 7 for circuit performance at  $V_{IN}$  of 385 V.



Figure 6.  $V_{IN} = 380\text{ V}$ ,  $I_{OUT} = 10\text{ A}$ , ZVS at  $f_r$

Please note that using this design technique ZVS was maintained at minimum and maximum input voltages as well to handle large signal transients. Please refer to Figure 7 and Figure 8 for ZVS circuit performance.

 


Figure 7. ZVS @  $V_{IN} = 340\text{ V}$ ,  $I_{OUT} = 10\text{ A}$

 


Figure 8. ZVS @  $V_{IN} = 400\text{ V}$ ,  $I_{OUT} = 10\text{ A}$

## 9 Summary

As this application brief discussed when designing an LLC converter (UCC256301/2/3/4) for off line applications using SRs (UCC24624) to get the highest efficiency and best performance possible, we recommend the following.

1. Select FETs for the primary and SRs before designing the transformer.
2. Transformer design considerations to ensure ZVS.
  - Select  $N_{ps}$  at the nominal LLC input voltage and include the effect of the voltage drops across the FETs used in the design.
  - Select  $L_m$  to achieve ZVS based on input and output power requirements, Q1 and Q2's  $C_{o(tr)}$ , and  $d_v/d_t$  requirements. **Please note that when using the UCC256301/2/3/4 devices the  $d_v/d_t$  needs to be set greater than 4 V/ns to avoid control misbehavior.**
3. After the preliminary transformer calculations are done  $C_r$  can be calculated/selected based on  $Q_e$ ,  $R_e$  and  $f_r$ .
4. When selecting  $L_r$  and L1 don't forget to include the effects of the transformer's  $L_{lk}$ .
5. Avoid operating the LLC when the primary switch node is operating in ZCS to avoid feedback control latch up.
  - In older controllers this just requires setting  $f_{min}$  to greater than  $f_{pp}$  (UCC25600).
  - Newer LLC controllers (UCC285601/2/3/4) have ZCS detection and frequency adjustment to avoid latch up. So there is no need to worry about switch node ZCS feedback latch up issues in these devices.

## 10 References

1. Hong Huang, "Designing an LLC Resonant Half-Bridge Power Converter," Texas Instruments (TI) Power Supply Design Seminar, SEM1900, 2010, TI Literature No. SLUP263, <https://www.ti.com/seclit/ml/slup263/slup263.pdf>
2. Benjamin Lough, "AC Ripple Rejection in AC/DC Systems Using LLC," Texas Instruments Application Report, October 2018, TI Literature No. SLUA850, <http://www.ti.com/lit/an/slua850/slua850.pdf>
3. Brent McDonald and Dave Freemand, "Design and Optimization of a High-Performance LLC Converter," Texas Instruments (TI) Power Supply Design Seminar, SEM2000, 2012, TI Literature No, SLUP306, <https://www.ti.com/seclit/ml/slup306/slup306.pdf>
4. "Exceeding Modern Energy Standards with Always on PFC and LLC Controllers" TI TechnNotes, February 2018, TI Literature No. SLUA867A, <http://www.ti.com/lit/an/slua867a/slua867a.pdf>



5. "Improving Transient Response in LLC Converters Using Hybrid Hysteretic Control," Texas Instruments Applications Report, August 2017, TI Literature No. SLUA834, <http://www.ti.com/lit/an/sl原因834/sl原因834.pdf>
6. "UCC25630x Practical Design Guidelines," Texas Instruments Applications Report, August 2017, TI Literature No. SLUA836A, <http://www.ti.com/lit/an/sl原因836a/sl原因836a.pdf>

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2018, Texas Instruments Incorporated