

Extend LM5067 Applications With an External Auxiliary Source



Zichen Liu

ABSTRACT

In everyday life, there are many hot-swap scenarios. One of the hazards of hot-swap is that the transient rush currents and voltages generated by hot-swap can damage the post-stage circuitry. Hot-swap protection chips limit the transient power and transient current generated during hot-swap to protect the post-stage circuit. Hot-swap protection chips sometimes need to adapt to large dynamic range voltage swing, which can cause overstress on certain parameters of the chip during use. This paper proposes a method to add an auxiliary source. Theory and experimental verification can be used to extend the dynamic voltage operating range of this chip.

Table of Contents

1 Introduction.....	2
2 The External Auxiliary Power Supply and Op Amp Follows and Changes the UVLO Swing Amplitude of LM5067.....	4
3 Testing and Verification.....	5
4 Summary.....	7
5 References.....	8

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

In real life, we often have such a scenario, when we connect the computer through the USB or HDMI interface to connect external devices, hard disks or monitors, we do not cut off the power supply of the PC, the external device is directly unplugged or plugged in, which is called hot-swap with power for this type of use scenario. Hot-swap allows users to remove and replace damaged hard drives, power supplies, or boards without shutting down the system or cutting off the power supply, thereby improving the system's timely disaster recovery ability, scalability, and flexibility. However, in the process of hot-swap, transient peak current and voltage occurrence is likely, if not protected, this causes the rear circuit to be damaged by the impact of transient high power. As shown in [Figure 1-1](#), this is a typical application scenario for hot-swappable protection chips.

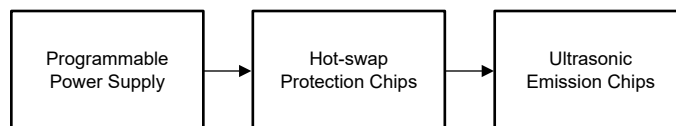


Figure 1-1. Ultrasonic Emission Link

Because the ultrasonic equipment needs to select different probes according to different detection objects, there are hot-swap scenarios, in this application, to maintain the stability and reliability of the entire ultrasonic system in the application process, hot-swap protection chips are necessary. LM5067 is a negative voltage hot-swap protection chip launched by TI in 2020. The voltage operating range of LM5067 is -9V to -80V, while the negative voltage range of conventional ultrasonic emission systems is typically -9V to -64V. In terms of specifications, LM5067 meets the current application scenario. The internal block diagram of the LM5067 is shown in [Figure 1-2](#), which can set the UVLO (Undervoltage lockout) and OVLO (Overvoltage lockout) to protect the post stage circuit. The specification of the LM5067 indicates the absolute maximum voltage value of the UVLO pin can not exceed $V_{EE}+17V$. If exceeded, permanent damage can occur.

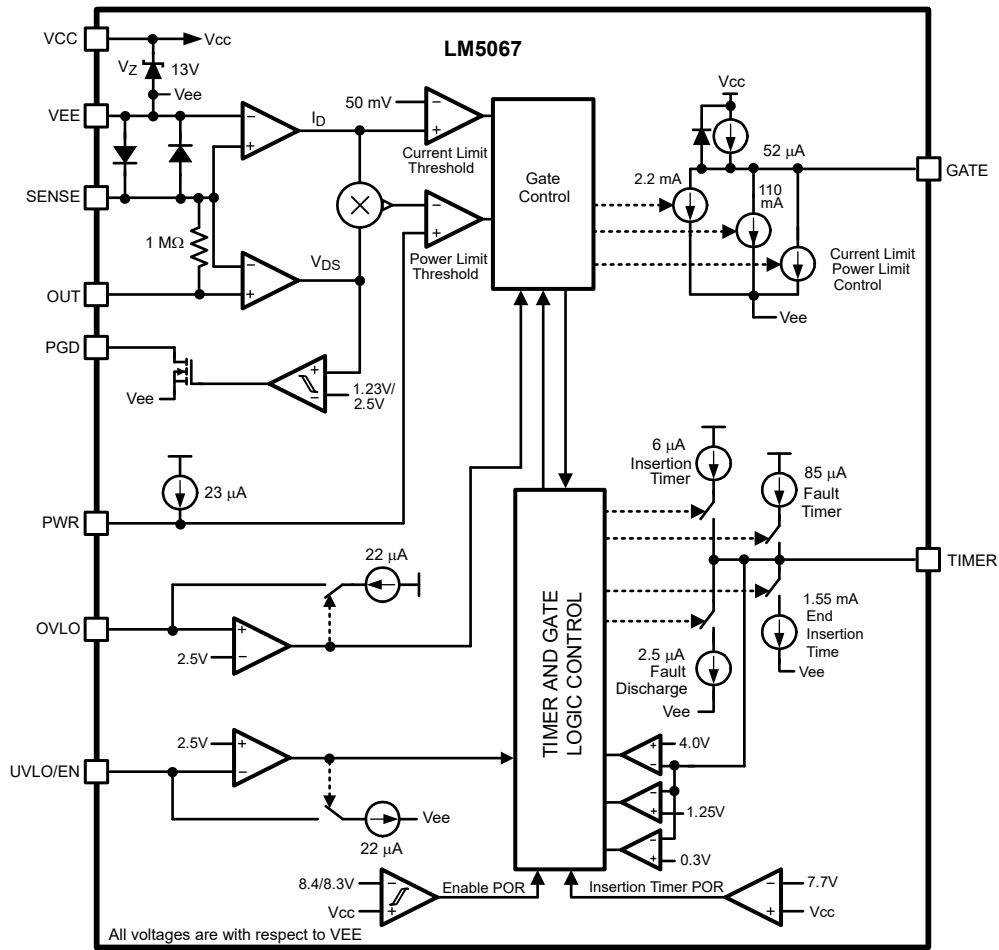


Figure 1-2. LM5067 System Block Diagram

In a practical application, the system needs to have a dynamic change in the operating voltage, ranging from -9V to -64V. The LM5067 can be set with the voltage thresholds of UVLO and OVLO using the external resistor divider ratio as shown in Figure 1-3. UVLO pin voltage can be expressed as Equation 1.

$$UVLO = \frac{(R2 + R3)}{(R2 + R3 + R1)} \times (VCC - VEE) \quad (1)$$

When $VCC = 0V$, $VEE = -9V$, the resistor-to-voltage ratio must be at least 9:2.5 to meet the voltage of the UVLO pin minimum voltage greater than 2.5V, according to the calculation, when $VCC=0V$, $VEE=-64V$, the voltage of the UVLO pin can reach 17.7V, which is beyond the normal voltage working range of the chip. To solve this problem, we can change the voltage of the UVLO pin through the external circuit.

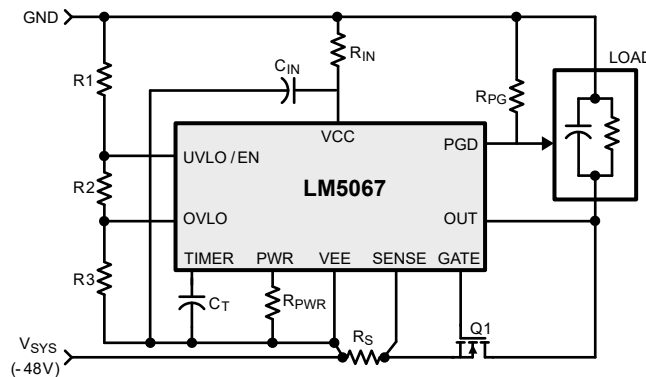


Figure 1-3. Typical Application of LM5067

2 The External Auxiliary Power Supply and Op Amp Follows and Changes the UVLO Swing Amplitude of LM5067

As shown in [Figure 2-1](#), [Figure 2-2](#), and [Figure 2-3](#), the external auxiliary power supply can use a regulated diode, an external DAC, LDO, and other available power supplies and follow through the op amp, you can output an adjustable power supply VS, and the adjustable power supply VS is added to the voltage divider resistor. The voltage setpoint of the UVLO Pin can be expressed as [Equation 2](#).

$$UVLO = \frac{(R2 + R3)}{(R2 + R3 + R1)} \times (VS - VEE) \quad (2)$$

For the LM5067 to work properly, set the LM5067 to 2.5V. UVLO_{MIN} when the voltage dynamic range of VS-VEE is R. The voltage swing range of UVLO Pin can be expressed as [Equation 3](#).

$$UVLO_{MAX} = \frac{VS + R}{VS + 0} \times UVLO_{MIN} \quad (UVLO_{MIN} = 2.5V) \quad (3)$$

Taking VS as the independent variable, the derivative of [Equation 3](#) can be obtained and expressed as [Equation 4](#).

$$\frac{dUVLO_{MAX}}{dvs} = \frac{-R}{(vs)^2} \times UVLO_{MIN} < 0, \text{ Monotonically decreasing} \quad (4)$$

Therefore, if the resistor-to-voltage ratio is a fixed value, the maximum voltage of the UVLO pin can be reduced by increasing the VS.

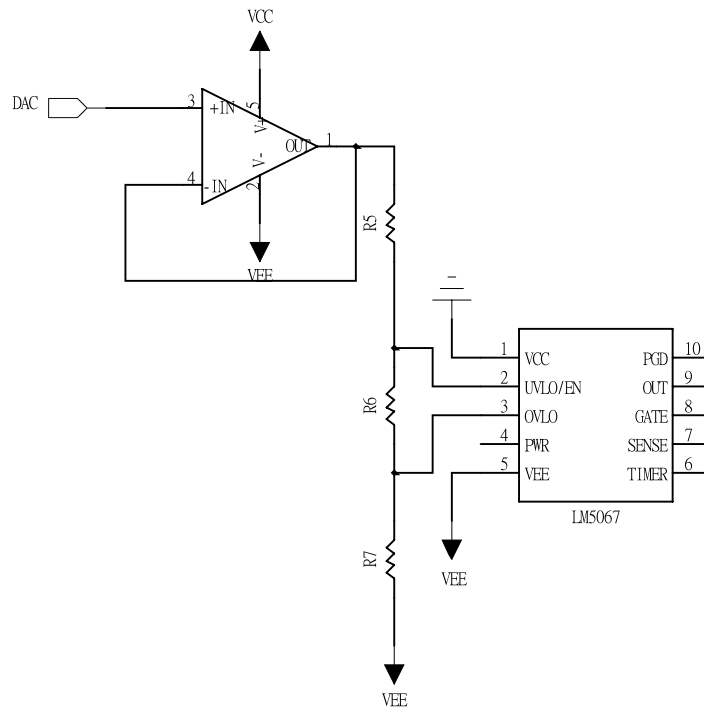


Figure 2-1. Set LM5067 UVLO With External DAC

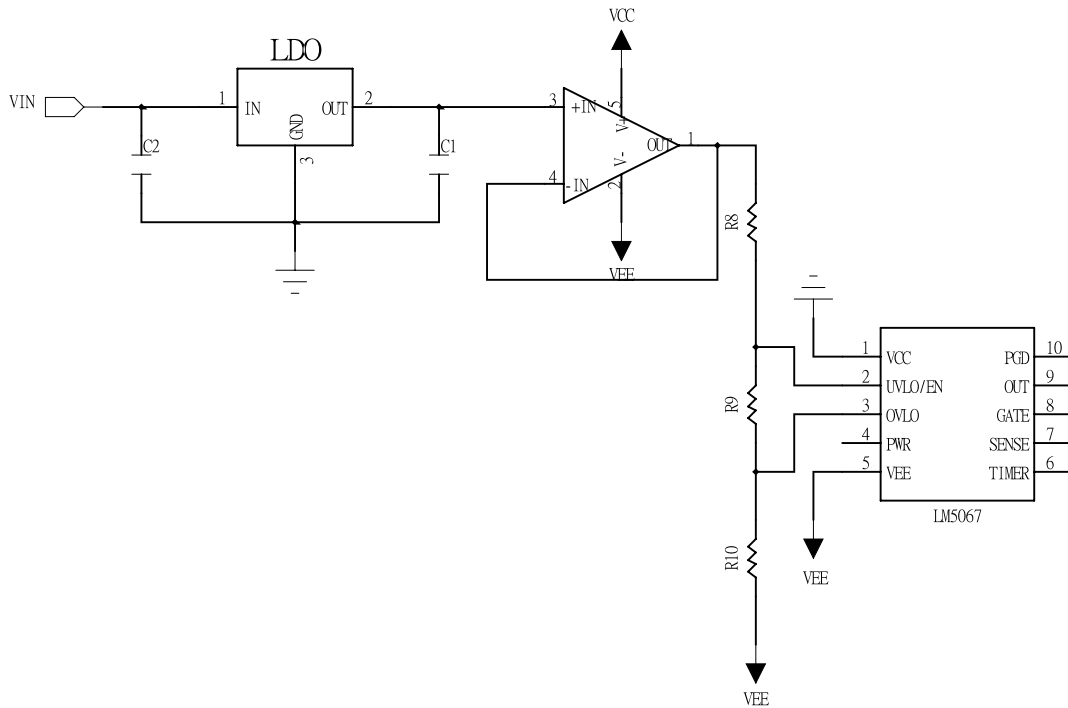


Figure 2-2. Set the LM5067 UVLO With External LDO

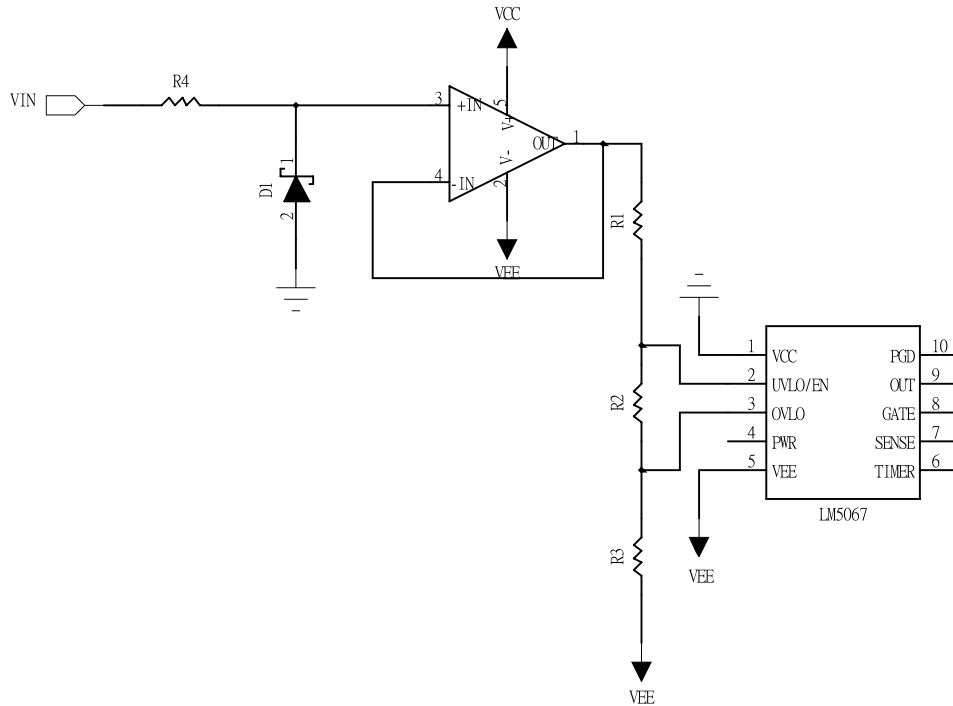


Figure 2-3. Set the LM5067 UVLO With External Zener Diode

3 Testing and Verification

When the dynamic variation range of $V_S - V_{EE}$ is -9V to -63.5V, the voltage swing of UVLO Pin can be expressed as Equation 5.

$$UVLO_{MAX} = \frac{VS + 63.5}{VS + 9.0} \times UVLO_{MIN} \quad (UVLO_{MIN} = 2.5V) \quad (5)$$

When $V_S = 5V$, the theoretical values of the $UVLO_{MAX}$ is 12.39V.

$$UVLO_{MAX} = 12.39V < 17V \tag{6}$$

The actual test conditions are shown in Figure 3-1, and the setting is $V_S = 4.9V$ and $V_{EE} = 63.5V$.

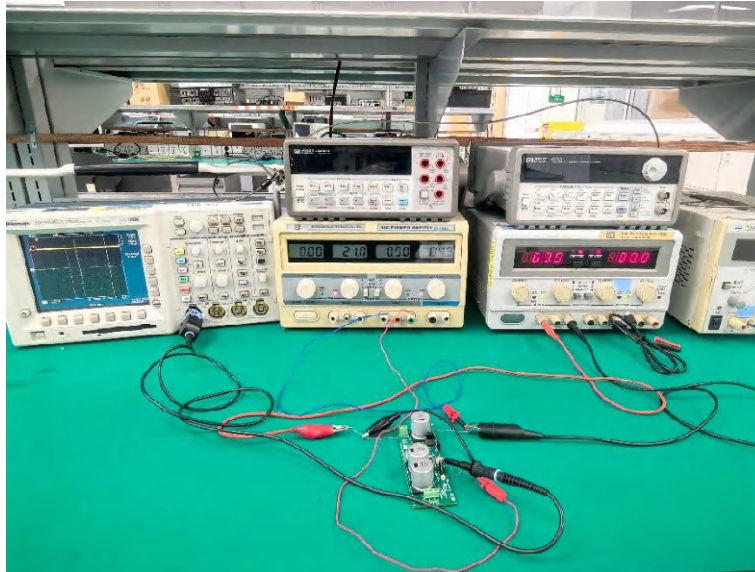


Figure 3-1. Actual Test Conditions

The test results are shown in Figure 3-2, and the measured UVLO is 12.3V, which is in line with the theoretical expectation.

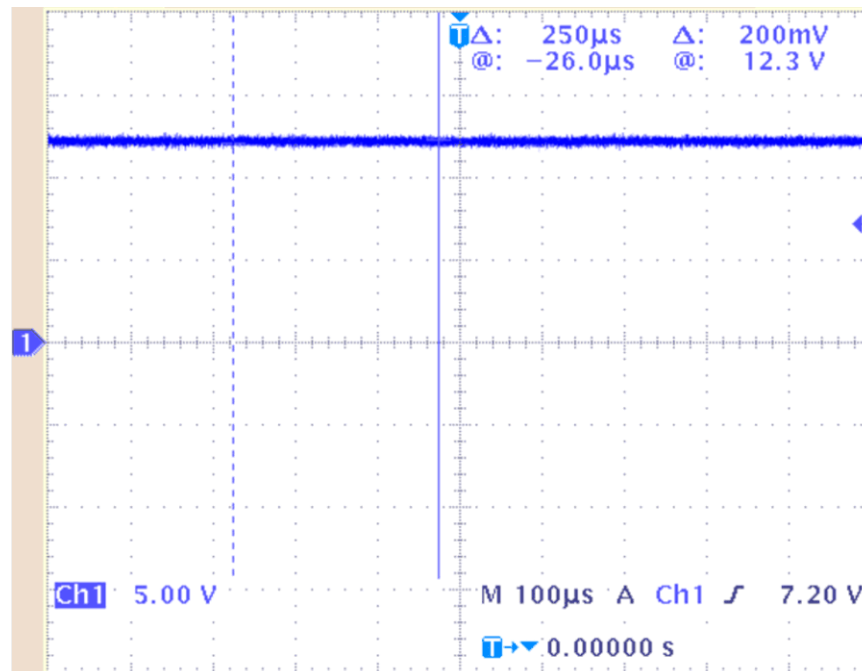


Figure 3-2. Measured Voltage at UVLO Pin

According to this method, the LM5067 can be made to work normally in a larger dynamic voltage range by applying an external power supply V_S , which solves the problem of the LM5067 under the traditional single negative power supply, eliminates the limit of the dynamic output voltage range of the chip caused by UVLO pin

voltage limit. For further protection of the UVLO Pin pin, A TVS or Zener diode can be added between VEE pin and VIN pin for voltage clamping.

4 Summary

According to this method, the LM5067 can be made to work normally in a larger dynamic voltage range by applying an external power supply VS, which solves the problem of the LM5067 under the traditional single negative power supply, eliminates the limit of the dynamic output voltage range of the chip caused by UVLO pin voltage limit. For further protection of the UVLO Pin pin, A TVS or Zener diode can be added between VEE pin and VIN pin for voltage clamping.

5 References

- Texas Instruments, [LM5067 Negative Hot Swap / Inrush Current Controller with Power Limiting](#) data sheet.
- Texas Instruments, [Basics of Power Switches](#) application report.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated