

AN-1533 Over Voltage Protection Circuit for Automotive Load Dump

ABSTRACT

This application report discusses an over voltage protection circuit for automotive load dump.

Contents

1	Introduction	2
2	The Circuit	2
3	Response Time Measurement	5
4	Load Limits	6

List of Figures

1	Over Voltage Protection.....	2
2	Adjustable Reference Concept.....	3
3	Circuit Function.....	4
4	Normal 12V Operation	5
5	Response to 60V Step Input, $C_{load} = 1 \mu\text{F}$	5
6	Raw Response to 60V Input, $C_{load} = 0 \mu\text{F}$	6

1 Introduction

Transient bus voltages are a serious danger to integrated circuits. The maximum voltage that an integrated circuit can handle depends upon its design process and can be particularly low for small geometry CMOS devices. Transient or persistent over voltage conditions that exceed an IC's absolute maximum voltage rating will permanently damage a device. The need for over voltage protection is particularly common in automotive 12V and 24V systems where peak "load dump" transients can be as high as 60V. Some load protection approaches shunt input transient to ground using devices like avalanche diodes and MOVs. The difficulty with the shunt approach is that large amounts of energy may have to be absorbed. Shunt approaches can also be unattractive if there is a requirement to provide continuous protection while in an over voltage condition (as occurs with double battery).

2 The Circuit

The circuit shown in [Figure 1](#) is a precision series disconnect that was designed to protect a switching regulator load that had an absolute maximum input voltage of 24V. The circuit is designed from low cost discrete devices and uses a single Texas Instruments LMV431AIMF. Since this circuit uses a PFET pass device (Q_1), there is little forward voltage drop or associated power loss.

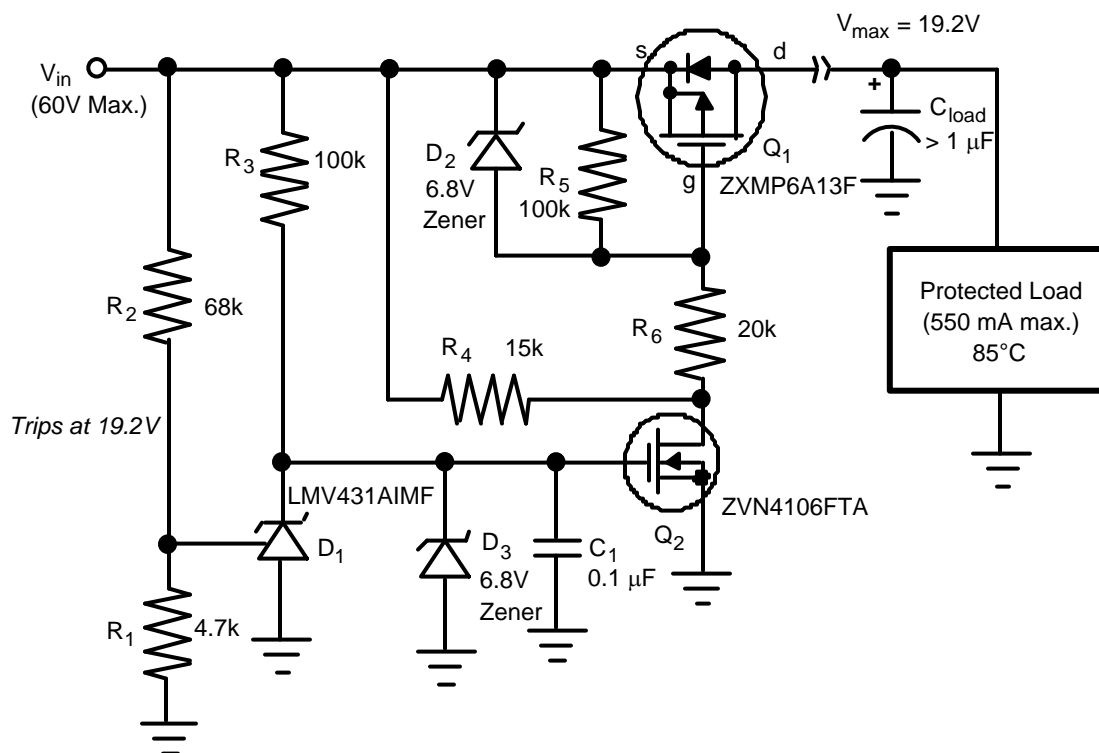


Figure 1. Over Voltage Protection

The LMV431AIMF (D_1) adjustable reference is ideal for this problem because it provides a low cost means to determine a precision trip point and maintain temperature stability that is not possible with a zener diode or with other approaches (1% for the A version, 0.5% for the B version). In order to preserve this precision, resistors R_1 and R_2 should be 1% tolerance or better.

Adjustable references are often misunderstood. As in: "What's that third wire coming out of that diode?" There are many flavors of adjustable reference. Some have different internal reference voltage and some have different gain polarity. They all have two basic (and very useful) components: A temperature stable, precision band gap reference, and a high gain error amplifier (used as a comparator in this circuit). Most devices have uni-polar output in the form of an open collector or emitter. [Figure 2](#) shows conceptually what is inside Texas Instruments LMV431AIMF.

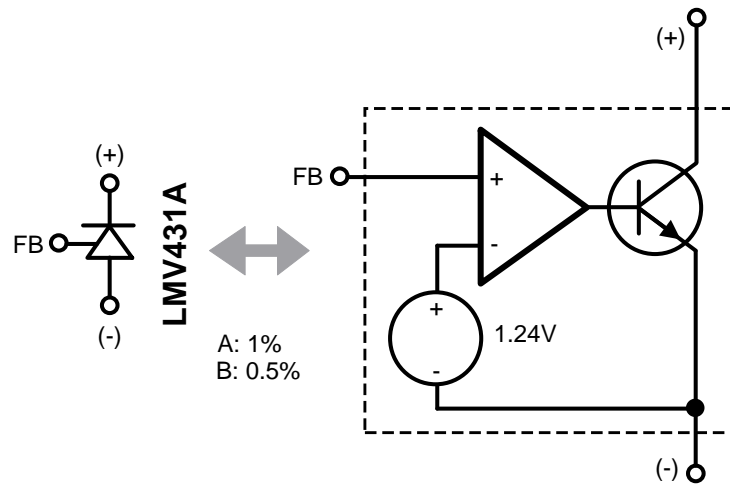


Figure 2. Adjustable Reference Concept

The input voltage is monitored by the LMV431 through voltage divider R_1 and R_2 . The circuit shown in Figure 1 is set to trip at 19.2V but an arbitrary trip point can be selected and is determined with these equations:

$$V_{\text{trip}} = 1.24 \times \frac{R_1 + R_2}{R_1}$$

$$R_2 = R_1 \times \left(\frac{V_{\text{trip}}}{1.24} - 1 \right) \tag{1}$$

The output of the LMV431 pulls down when the reference pin exceeds 1.24V. The cathode of an LMV431 can pull down to a saturation point of about 1.2V. This is sufficient to turn Q_2 off. Q_2 was specifically selected to have a high gate threshold ($>1.3V$). Do not make substitution for Q_2 without taking this into account.

The device states for D_1 , Q_2 , and Q_1 are shown in Table 1 for the case of a 19.2V trip point.

Table 1. Truth Table

	LM431 Q1	NFET Q2	PFET Q1
<2.7 V	OFF	?	OFF
2.7V to 19.2	OFF	ON	ON
>19.2 V	ON	OFF	OFF

The circuit's function is shown in Figure 3. The trip point can be anywhere in the 2.7V to 60V range. Below about 2.7V the circuit will enter the off state. This is because there is no longer sufficient input voltage to satisfy the gate to source thresholds of Q_1 and Q_2 .

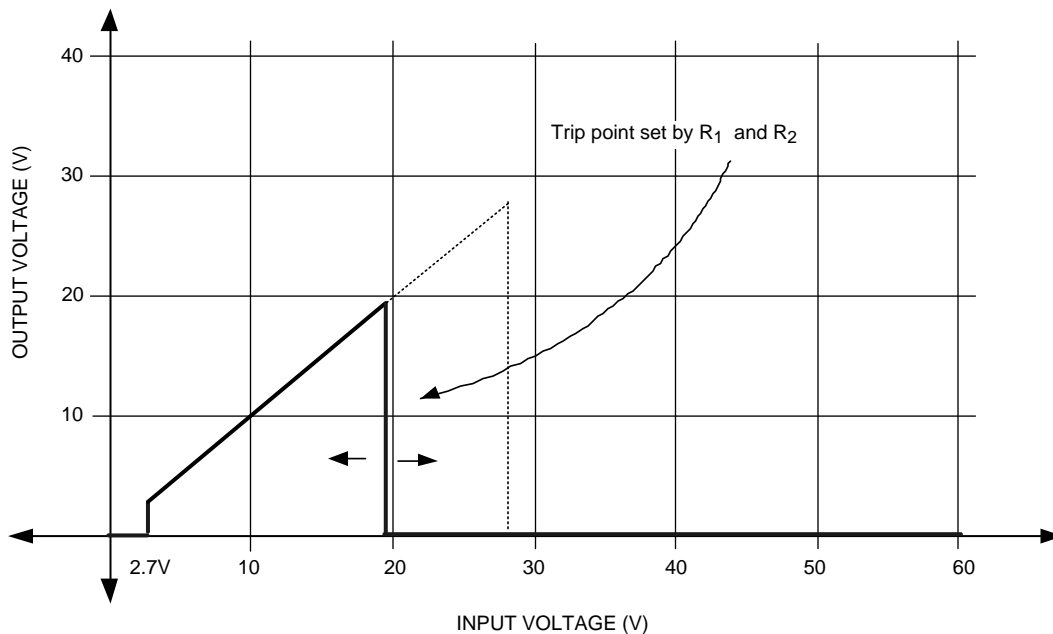


Figure 3. Circuit Function

When in the off state, the circuit presents about 42 k Ω to the input (off state quiescent load). Zener diodes D_2 and D_3 are necessary to limit the maximum gate to source voltages seen by Q_1 and Q_2 (which cannot exceed 20V). D_3 also prevents the cathode of D_1 from exceeding its maximum of 35V. Resistor R_4 provides a small amount of bias to Q_2 in order to satisfy Q_2 's drain leakage in the off state. Note that the body diode in Q_1 means that there is no protection to the load for reverse battery (negative input voltages). In order to protect against reverse battery, either a blocking diode or a second (back to back) PFET is required.

The circuit is designed to actuate quickly but reconnect more slowly. Capacitor C_1 rapidly discharges to ground through the LMV431 when over voltage is detected. When conditions return to normal, reconnect is delayed by the $R_3 \cdot C_1$ time constant. Most loads (usually regulators) contain large input capacitors which provide time for the disconnect circuit to engage by limiting the transient slew rate. The nature of the expected transient along with the available capacitance will determine the required response time. The shut off action of this circuit occurs in about 12 μ sec. Maximum transient rise times are limited in proportion to this time interval by C_{load} . This circuit was tested with a C_{load} of 1 μ F. Larger C_{load} is allowed and recommended if fast rising, low source impedance transients are expected.

3 Response Time Measurement

The response to a normal 12V ON and OFF cycle is shown in Figure 4. The off portion decays slowly because of the 1 μ F Cloud dissipating into the 1 k Ω test load. The driving waveform also shows this decay because the test source used could not sink current.

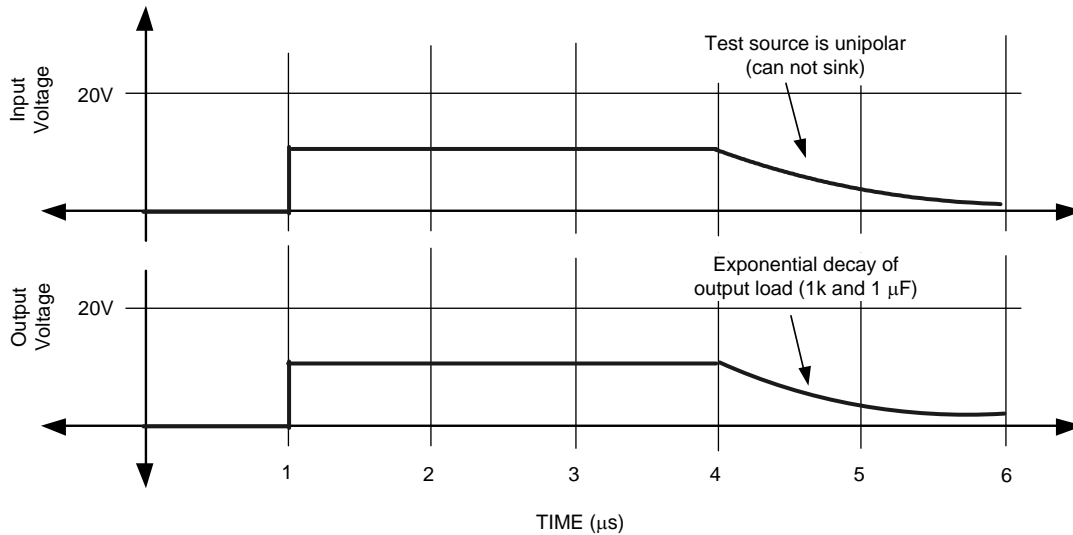


Figure 4. Normal 12V Operation

The response to an over voltage is shown in Figure 5. Note that the fast rising over voltage event has time to charge the output to 19.2V where the circuit disconnects. After this, the disconnected output voltage decays into the 1 k Ω load.

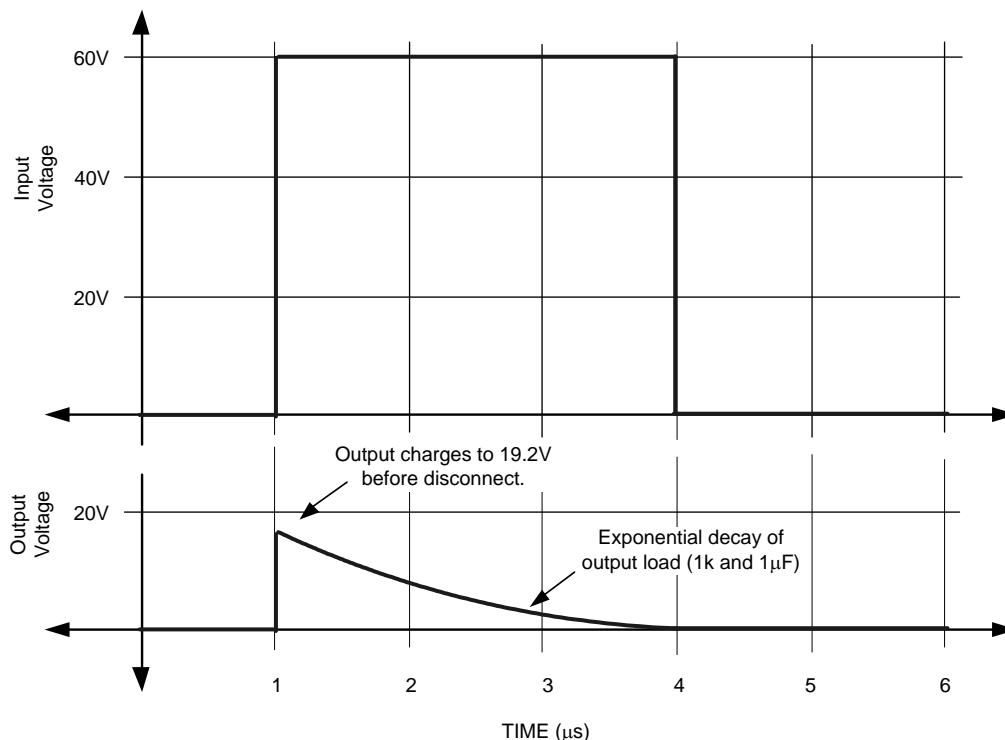


Figure 5. Response to 60V Step Input, $C_{load} = 1 \mu F$

If the $1\mu\text{F}$ C_{load} capacitor is removed the actuation speed of the disconnect can be observed. This is shown in Figure 6. Since the rise time of the input transient isn't limited by any capacitance the output voltage is charged to the full 60V before action is taken. For this reason, C_{load} should be sized appropriately for the expected transient rise time and expected transient source impedance.

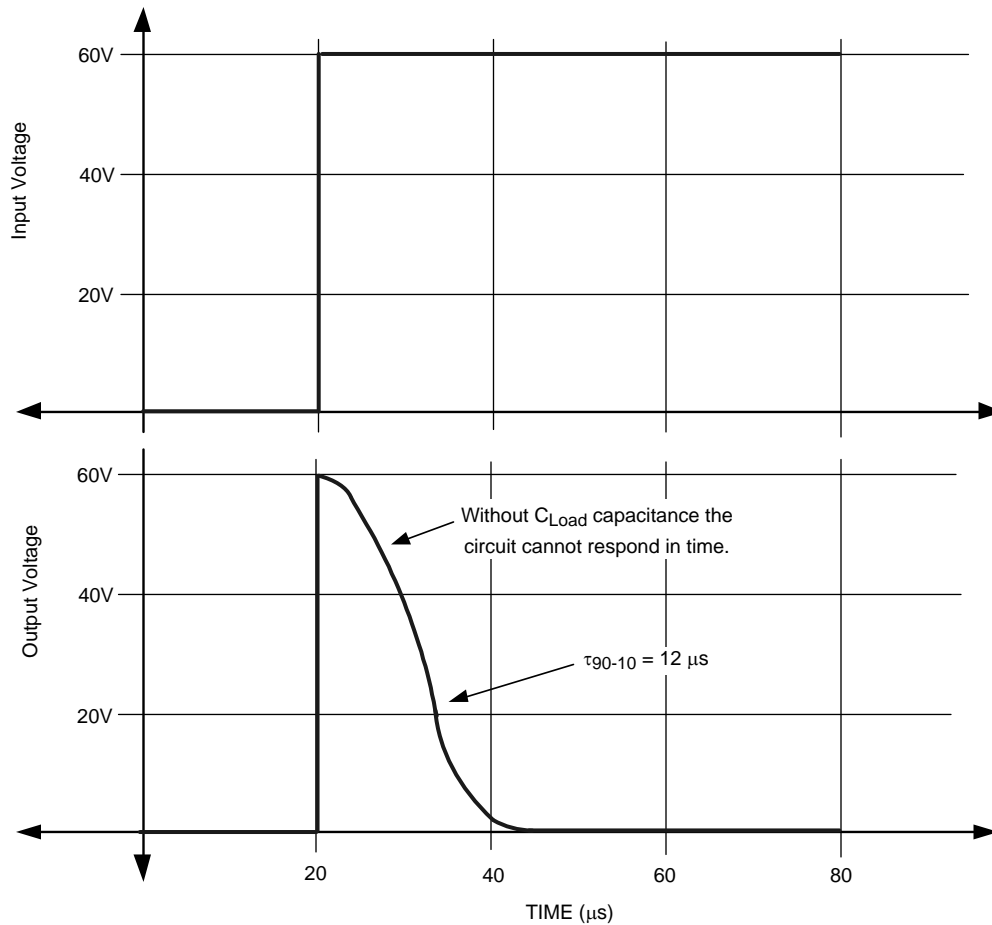


Figure 6. Raw Response to 60V Input, Cload = 0 μF

4 Load Limits

The 550 mA maximum allowed load is set by the thermal limits of Q1 at 85°C. When making this calculation, remember that $R_{\text{DS(ON)}}$ is highest when the gate to source voltage is low. For larger loads replace Q1 with a 60V PFET with more thermal capacity (smaller θ_{JA}) or lower $R_{\text{DS(ON)}}$.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com