

# Schematic Checklist - A Guide to Designing with Auto-Bidirectional Translators



Michael Ikwuyum

## ABSTRACT

This application note provides recommendations and a checklist to follow while creating or reviewing schematics for auto-bidirectional level shifters. Examples of such devices are the [TXS, TXB and LSF device families](#). These devices are typically designed with limited drive strength, allowing their hosts to overdrive them for any direction. Such auto-bidirectional devices can be very sensitive to many factors when used in applications that are not auto-bidirectional. Intentional considerations should be ensured when designing with auto-bidirectional devices. [Section 1.2](#) shows examples of auto-bidirectional use-cases.

## Table of Contents

<b>1 Introduction</b> .....	1
1.1 Device Applicability.....	1
1.2 When to Use or Not Use Auto-Bidirectional Devices.....	2
<b>2 Recommendations Specific to TXB, TXS, LSF</b> .....	3
2.1 Before You Begin.....	3
2.2 Power Supplies.....	3
2.3 Output Enable Pins.....	3
2.4 Input or Output Pins.....	3
2.5 Unused Pins.....	4
2.6 Pull-Ups and Pull-Downs.....	4
2.7 Recommended Translator by Interface.....	4
<b>3 Summary</b> .....	5
<b>4 References</b> .....	5

## Trademarks

All trademarks are the property of their respective owners.

## 1 Introduction


TXB, TXS, and LSF device families are recommended for auto-bidirectional applications and TXU, TXV, LXC, LVC, AXC, AVC, AUP, LVxT families are recommended for applications where individual channels are used for a fixed directional signal.

### 1.1 Device Applicability

This application note applies to the following devices:


- [TXS, TXB and LSF device families](#)

## 1.2 When to Use or Not Use Auto-Bidirectional Devices

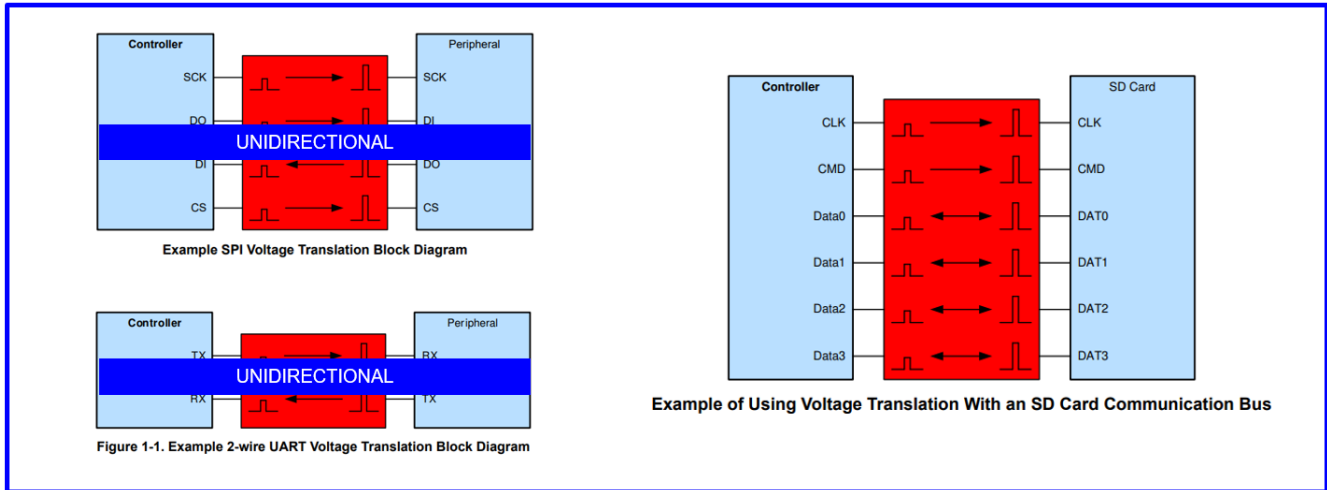


**Figure 1-1. Differences Between Unidirectional and Auto-Bidirectional Signals**

Each channel of unidirectional signals are directed towards a fixed direction while each channel of auto-bidirectional signals can be directed for both directions. Check for the direction of the application's signal or protocol and review this checklist with the latest data sheet documentation. Below are examples showing auto-bidirectional signals. See [Section 2.7](#) for a full list of typical applications with their device recommendations.

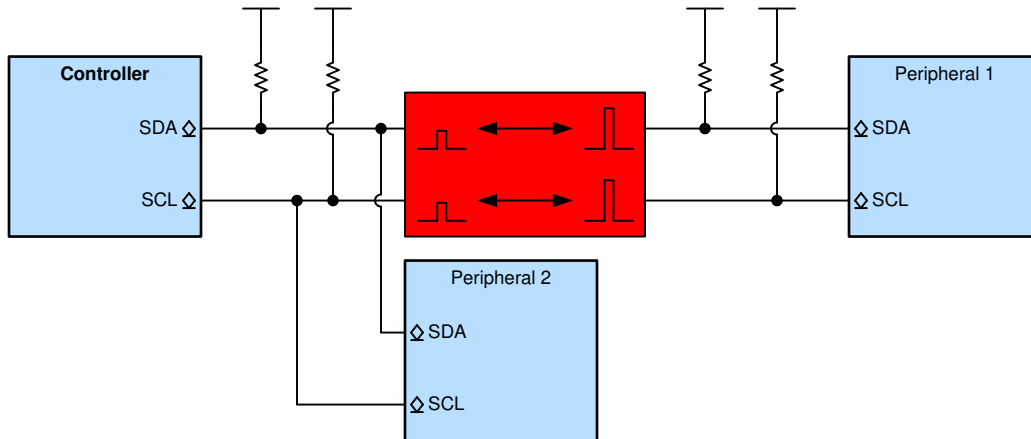

**Figure 1-2. Example of Using Voltage Translation With an I2C Communication Bus**

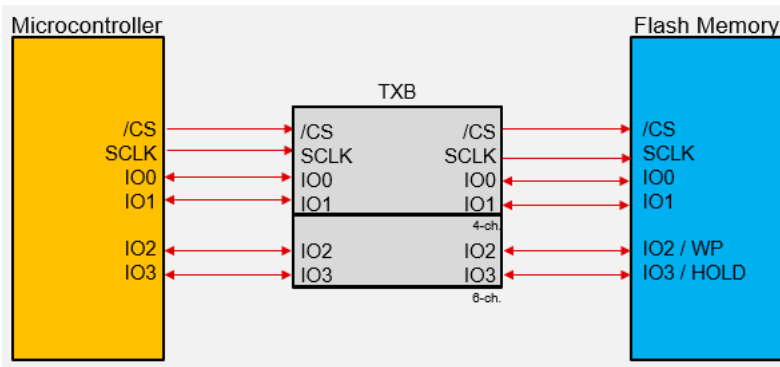

**Figure 1-3. Example of Using Voltage Translation With Quad-SPI**

## 2 Recommendations Specific to TXB, TXS, LSF

### 2.1 Before You Begin

#### 2.1.1 Documentation

Make sure you have the latest version of all documentation and data sheets.

---

#### Note

There is a Notifications button on each [ti.com](https://www.ti.com) device product folder. Registration here enables proactive automatic notification of device errata.

---

### 2.2 Power Supplies

#### 2.2.1 Biasing Requirements

- **TXB or TXS:** Make sure supply voltages match data sheet recommendations for  $V_{CCA} \leq V_{CCB}$ .
- **LSF:** Make sure supply voltages match data sheet recommendations for  $V_{ref\_B} \geq V_{ref\_A} + 0.8V$ .
  - If level-shifting voltage levels conflicting with the above for LSF, pull-ups to voltage supplies different from  $V_{ref}$  can be populated on the inputs or outputs.
  - If LDOs are used, make sure LDO used can sink current flowing from  $V_{ref\_B}$  into  $V_{ref\_A}$ . With the recommended LSF 200k $\Omega$  bias resistor, current =  $(V_{ref\_B} - V_{ref\_A} - 0.8V) / 200k\Omega$ .
    - Or, a 100k $\Omega$  weak pull-down resistor on  $V_{ref\_A}$  to the output of the regulator is recommended.

#### 2.2.2 Decoupling Capacitors

During transitions, level-shifters can draw large transient currents from the power supply. Decoupling capacitors prevents voltage droops on the power rails by bypassing the power supply and creating a low-impedance path for high-frequency signals. This makes sure the level-shifter is provided a clean and stable supply voltage.

A typical recommendation is 0.1 $\mu$ F, to help mitigate noise from power supplies. Place decoupling capacitors as close as possible to  $V_{CC}$  pins on the printed circuit board layout.

#### 2.2.3 Power Sequencing

- TXB, TXS and LSF devices do not have any specific power sequence requirement.
- Make sure the OE pin is configured to keep the device disabled until both supplies are stable.

### 2.3 Output Enable Pins

- Never leave floating.
- Connect directly to  $V_{CC}$  or GND (or drive HIGH or LOW with a control signal).
  - Can use pull-ups or pull-downs when driven by a control signal. 10 k $\Omega$  is typical.
  - Pull-down is only required if LOW is needed on start-up, then driven HIGH with an MCU or other signals.
- **For LSF:** Make sure the EN pin is shorted to  $V_{ref\_B}$  with 200 k $\Omega$  (internally done for LSF0204 and needs to be done externally for LSF010x).

### 2.4 Input or Output Pins

Make sure your input or output pins meet the data sheet recommendations. For example:

- Data rate frequency.
- Load capacitance.
- Recommended to keep trace lengths and loading as minimal as possible. Note, connectors add to the lumped capacitive loading.
- Double check proper voltage levels for inputs (follow the device-specific  $V_{IH}$  /  $V_{IL}$  specification in the data sheet). Devices are over-voltage tolerant and inputs can be  $\geq V_{CC}$  within the data sheet's recommended operating conditions.
- Series resistors used should be sufficient with the device's output impedance and transmission line used. For more information, see [\[FAQ\] Can I estimate appropriate dampening resistor value for level-shifter outputs?](#)
- Not recommended to have delay (RC) circuitry tied to input pins to avoid violating the data sheet's input transition spec. Violations can result to shoot-through currents and oscillations. For more information,

see section 3 of [Do's and Don'ts for TXB and TXS Voltage Level-Shifters with Edge Rate Accelerators](#), application note and [Implications of Slow or Floating CMOS inputs](#).

## 2.5 Unused Pins

Unused pins for the TXB, TXS and LSF devices can be left disconnected (with the exception of the OE pin).

## 2.6 Pull-Ups and Pull-Downs

- TXB and TXS devices are sensitive to external pull-up or pull-down resistors due to the internal pull-up resistors present in the TXS device and the internal serial resistors present in the TXB device.
  - $V_{OL}$  and  $V_{OH}$  levels are impacted with external pull-up and pull-down resistors.
  - Pull-up or pull-down resistor greater than 50 k $\Omega$  is recommended.
- LSF family is recommended for auto-bidirectional applications where external pull-up resistors are required. Pull-downs are not recommended as they create a voltage divider network with the pull-ups used.
  - **LSF Up translate with pull-ups:**
    - Required on the higher voltage side (B-side).
    - Required on the lower voltage side (A-Side) only if outputs are open-drain or with leakage > 1  $\mu$ A.
  - **LSF Down translate with pull-ups:**
    - Not required if leakage into the receiver is < 1  $\mu$ A.

## 2.7 Recommended Translator by Interface

**Table 2-1. Recommended Translator by Interface**

Interface	Translation Level	
	Up to 3.6V	Up to 5.5V
FET Replacement	<a href="#">2N7001T</a>	<a href="#">SN74LXC1T45</a> / <a href="#">TXU0101</a>
1 Bit GPIO / Clock Signal	<a href="#">SN74AXC1T45</a>	<a href="#">SN74LXC1T45</a> / <a href="#">TXU0101</a>
2 Bit GPIO	<a href="#">SN74AXC2T245</a>	<a href="#">SN74LXC2T45</a> / <a href="#">TXU0102</a>
2-Pin JTAG / UART	<a href="#">SN74AXC2T45</a>	<a href="#">SN74LXC2T45</a> / <a href="#">TXU0202</a>
I2C / MDIO / SMBus	<a href="#">TXS0102</a> / <a href="#">LSF0102</a>	<a href="#">TXS0102</a> / <a href="#">LSF0102</a>
IC-USB	<a href="#">SN74AVC2T872</a> / <a href="#">TXS0202</a>	N/A
4 Bit GPIO	<a href="#">SN74AXC4T245</a>	<a href="#">TXB0104</a> / <a href="#">TXU0104</a>
UART	<a href="#">SN74AXC4T245</a>	<a href="#">TXB0104</a> / <a href="#">TXU0204</a>
SPI	<a href="#">SN74AXC4T774</a>	<a href="#">TXU0304</a>
Quad-SPI	<a href="#">TXB0106</a>	<a href="#">TXB0106</a>
JTAG	<a href="#">SN74AXC4T774</a> / <a href="#">TXB0104</a>	<a href="#">TXB0104</a> / <a href="#">TXU0304</a>
I2S / PCM	<a href="#">SN74AXC4T774</a> / <a href="#">TXB0104</a>	<a href="#">TXB0104</a> / <a href="#">TXU0204</a>
SDIO / SD / MMC	<a href="#">TXS0206</a> / <a href="#">TWL1200</a>	N/A
6 Bit RGMII	<a href="#">TXV0106</a>	N/A
8 Bit GPIO / RGMII	<a href="#">TXV0108</a>	<a href="#">SN74LXC8T245</a>

For more information on specific interfaces, see [Voltage Translation Application Quick Reference](#)

### 3 Summary

Step	Checklist	Comments
1	Verify the interface	See <a href="#">Section 2.7</a> Open-drain interfaces – TXS or LSF devices. Push-Pull interfaces – TXB or TXS or LSF devices.
2	Verify power supplies are biased correctly	TXB and TXS: $V_{CCA} \leq V_{CCB}$ is recommended LSF: $V_{ref\_A} + 0.8V \leq V_{ref\_B}$ is recommended
3	Verify decoupling capacitors are used with all power supplies	0.1 $\mu$ F is recommended. Recommended to place cap as close as possible to the $V_{CC}$ supply pin.
4	Verify the schematic pinout matches the data sheet pinout.	Unused I/Os can be left floating. Traces with used I/Os can be kept as short as possible.
5	Verify output capacitive load is minimal	Typically, up to 70pF unless specified in data sheets.
6	Verify that external pull-up or pull-down resistors are consistent with data sheet.	Pull-ups or pull-downs are not recommended for TXB and TXS. LSF can use pull-ups. Pull-downs not recommended.

### 4 References

- Texas Instruments, [A Guide to Voltage Translation with TXB-Type Translators](#), application note.
- Texas Instruments, [A Guide to Voltage Translation with TXS-Type Translators](#), application note.
- Texas Instruments, [Do's and Don'ts for TXB and TXS Voltage Level-Shifters with Edge Rate Accelerators](#), application note.
- Texas Instruments, [Effects of External Pullup and Pulldown Resistors on TXS and TXB Devices](#), application note.
- Texas Instruments, [Voltage-Level Translation with the LSF Family](#), application note.
- Texas Instruments, [Factors Affecting VOL for TXS and LSF Auto-Bidirectional Translators](#), application note.
- Texas Instruments, [Implications of Slow or Floating CMOS inputs](#), application note.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated