

# Low-side Current Sensing for High-performance Cost-sensitive Applications




Tim Claycomb

Other Parts Discussed in Post: [TLV906X](#)

Applications that require the control of a motor typically involve some type of current-sensing circuitry. Being able to sense the current through the motor allows adjustments, such as speed, to the motor’s current state if needed.

For example, in [drones](#), each of the motors that control the propellers typically use a low-side current-sensing circuit to steer, stabilize and lift the drone through the air. In [power tools](#) like drills and reciprocating saws, low-side current sensing controls the speed of the tool based on how hard users pull the trigger. These products typically require a cost-sensitive design because they are sold in the consumer market space. In this blog post, I’ll discuss how to design a low-side current-sensing circuit for cost-sensitive applications.

One cost-effective option when designing a low-side current-sensing circuit is to use an [operational amplifier](#) (op amp) in a noninverting configuration. [Figure 1](#) is a schematic of a typical low-side current-sensing circuit using an op amp.

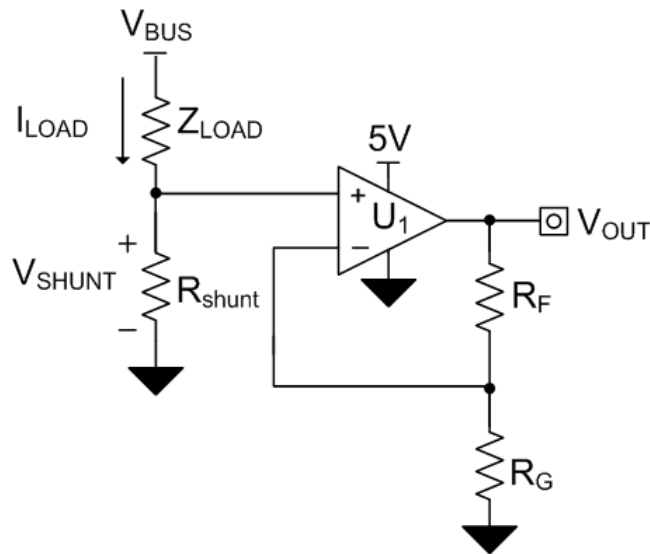

**Figure 1. Low-side Current-sensing Schematic**

Equation 1 gives the transfer function of the circuit shown in [Figure 1](#) as:

$$V_{out} = I_{LOAD} \times R_{SHUNT} \times Gain \quad (1)$$

where  $Gain = 1 + \frac{R_F}{R_G}$ .

The design process for the low-side current-sensing circuit shown in [Figure 1](#) breaks down into three simple steps:

1. **Calculate the maximum shunt resistance.** When current from the load ( $I_{LOAD}$ ) flows through the shunt resistor ( $R_{SHUNT}$ ), a voltage potential ( $V_{SHUNT}$ ) develops across  $R_{SHUNT}$ .  $V_{SHUNT}$  is seen as the “ground” for the system load. Therefore, I recommend keeping  $V_{SHUNT}$  below 100mV at the maximum load current to avoid issues when interfacing with other systems that have a true 0V ground. Equation 2 calculates the

$$R_{SHUNT\_MAX} = \frac{V_{SHUNT\_MAX}}{I_{LOAD\_MAX}} \quad (2)$$

maximum  $R_{SHUNT}$  value as:

2. **Calculate the gain of the amplifier.** The op amp amplifies  $V_{SHUNT}$  in order to produce an output voltage swing of  $V_{OUT\_MIN}$  to  $V_{OUT\_MAX}$ , where  $V_{OUT\_MIN}$  and  $V_{OUT\_MAX}$  are the minimum and maximum output swing limits of the amplifier, respectively. Equation 3 calculates the gain of the amplifier to produce the desired

$$Gain = \frac{V_{OUT\_MAX} - V_{OUT\_MIN}}{V_{SHUNT\_MAX} - V_{SHUNT\_MIN}} \quad (3)$$

output swing:

Equation 4 calculates the size of the resistors,  $R_F$  and  $R_G$ , in the feedback network of the amplifier in order to set the gain calculated in Equation 3:


$$Gain = 1 + \frac{R_F}{R_G} \quad (4)$$

3. **Choose your amplifier.** In low-side current-sensing applications, the common-mode voltage can be at or below ground if the current is bidirectional; therefore, the amplifier must have an input common-mode voltage range specified at or below ground. One device with an input common-mode voltage range that extends below ground is the [TLV9062](#), a high-performance, general purpose amplifier designed for cost-sensitive applications.

The TLV906x high-performance general-purpose amplifier family is designed for cost-sensitive low-side current-sensing applications due to its gain bandwidth (10MHz), slew rate (6.5V/μs), offset voltage (0.3mV) and input common-mode voltage range, which is specified at 100mV below the negative supply voltage. Table 1 highlights a few of the TLV906x family’s typical specifications.

Parameter	Specification
Supply voltage range ((V+)-(V-))	1.8V to 5.5V
Quiescent current	538μA
Gain bandwidth product (GBP)	10MHz
Input voltage noise	10nV/√Hz
Slew rate	6.5V/μs
Offset voltage	0.3mV
Input bias current	0.5pA
Input common-mode voltage	(V-)-100mV to (V+)+100mV

The design in [Figure 2](#) shows the final component values for a 0A to 0.5A low-side current-sensing circuit, with component values calculated by following steps 1 through 3.

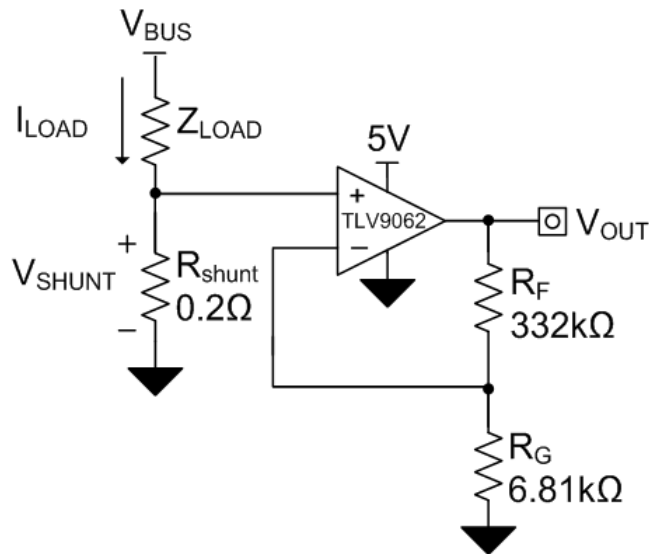

**Figure 2. 0A to 0.5A Low-side Current-sensing Schematic**

Popular applications such as drones and power tools require cost-sensitive low-side current-sensing solutions for motor control. In this post, I simplified circuit design into three simple steps: determine the maximum shunt resistor, calculate the gain of the amplifier that produces the largest output swing and choose your amplifier. In my [next post](#), I discuss how to properly lay out a printed circuit board (PCB) for a low-side current-sensing circuit.

#### Additional Resources

- Start designing quickly with the [0-1A, Single-Supply, Low-Side, Current Sensing Solution](#).
- Watch the video, “[TI Precision Labs – Op Amps: Input and Output Limitations](#).”

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated