


# Four-switch Buck-boost Layout Tip No. 1: Identifying the Critical Parts for Layout



Vijay Choudhary

Layout is very critical to the successful operation of a buck-boost converter. A good layout begins by identifying these critical components, as shown in [Figure 1](#):

- High di/dt loops or hot loops.
- High dv/dt nodes.
- Sensitive traces.

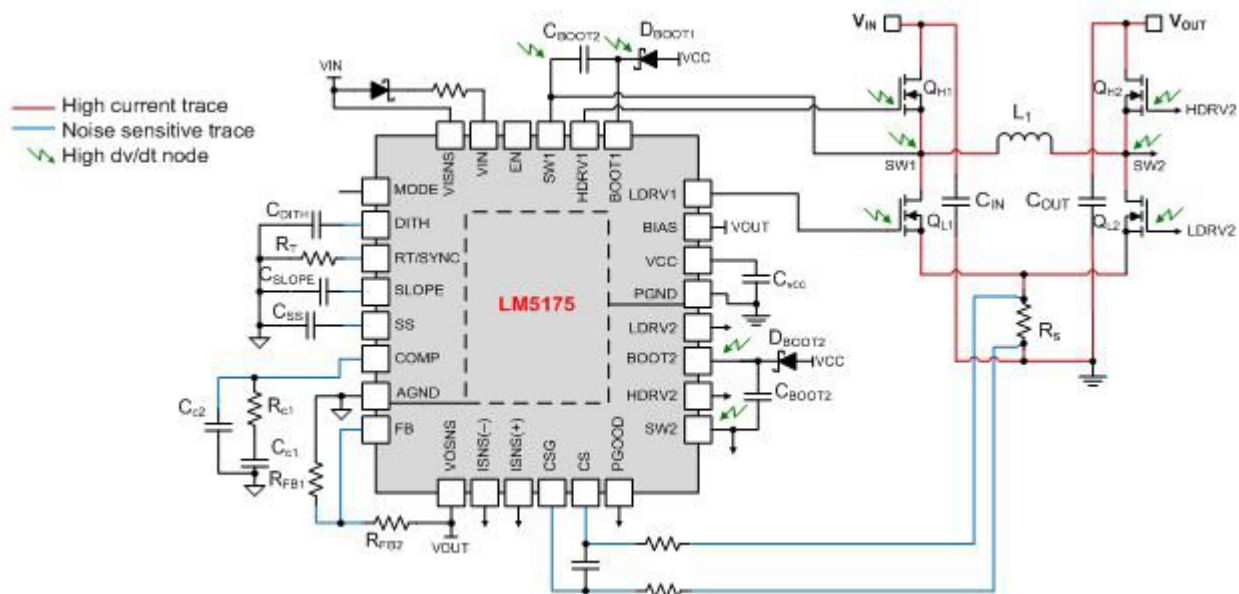

**Figure 1. Identifying High Di/dt Loops, High Dv/dt Nodes and Sensitive Traces**

[Figure 1](#) shows the high di/dt paths in the LM5175 four-switch buck-boost converter. The most dominant high di/dt loops are the input-switching current loop and output-switching current loop. The input loop consists of an input capacitor ( $C_{IN}$ ), MOSFETs ( $Q_{H1}$  and  $Q_{L1}$ ), and a sense resistor ( $R_s$ ). The output loop consists of an output capacitor ( $C_{OUT}$ ), MOSFETs ( $Q_{H2}$  and  $Q_{L2}$ ), and a sense resistor ( $R_s$ ).

The high dv/dt nodes are those with fast voltage transition. These nodes are switch nodes (SW1 and SW2), boot nodes (BOOT1 and BOOT2), and gate-drive traces (HDRV1, LDRV1, HDRV2 and LDRV2), along with their return paths.

The current-sense traces from resistor  $R_s$  to the integrated circuit (IC) pins (CS and CSG), the input and output sense traces (VISNS, VOSNS, FB), and the controller components (SLOPE,  $R_{c1}$ ,  $C_{c1}$ ,  $C_{c2}$ ) form the noise-sensitive traces. They are shown in blue in [Figure 1](#).

For good layout performance, minimize the loop areas of high di/dt paths, minimize the surface areas of high dv/dt nodes, and keep the noise-sensitive traces from the noisy (high di/dt and high dv/dt) portions of the circuit. In the other two installments of this series, I'll look at each of these in detail in the context of the four-switch buck-boost converter. My next topic will include an example for [optimizing hot loops](#).

---

### Additional Resources

- Check out my 2016-2017 Power Supply Design Seminar topic, "[Under the hood of a non-inverting buck-boost converter.](#)"

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated