

John Betten

The many virtues of flyback converters include being the lowest-cost isolated power converter, easily supplying multiple output voltages, a simple primary-side controller and power delivery of up to 300W. Flyback converters are used in many offline applications from televisions to phone chargers as well telecommunications and industrial applications. Their basic operation can appear intimidating and the design choices are many, especially for those who have not designed one before. Let’s look at some of the key design considerations for a 53 VDC to 12V at 5A continuous-conduction mode (CCM) flyback.

Figure 1 shows a detailed 60W flyback schematic, operating at 250 kHz. When FET Q2 turns on, the input voltage is applied across the transformer’s primary winding. Current in the winding now ramps up, allowing energy to be stored in the transformer. Since output rectifier D1 is reverse-biased, current flow to the output is blocked. When Q2 turns off, primary current is interrupted, forcing the winding’s voltage polarities to reverse. Current now flows out of the secondary winding, reversing the polarity of the winding voltage with the dot-voltage positive. D1 conducts, delivering current to the output load and recharging the output capacitors.


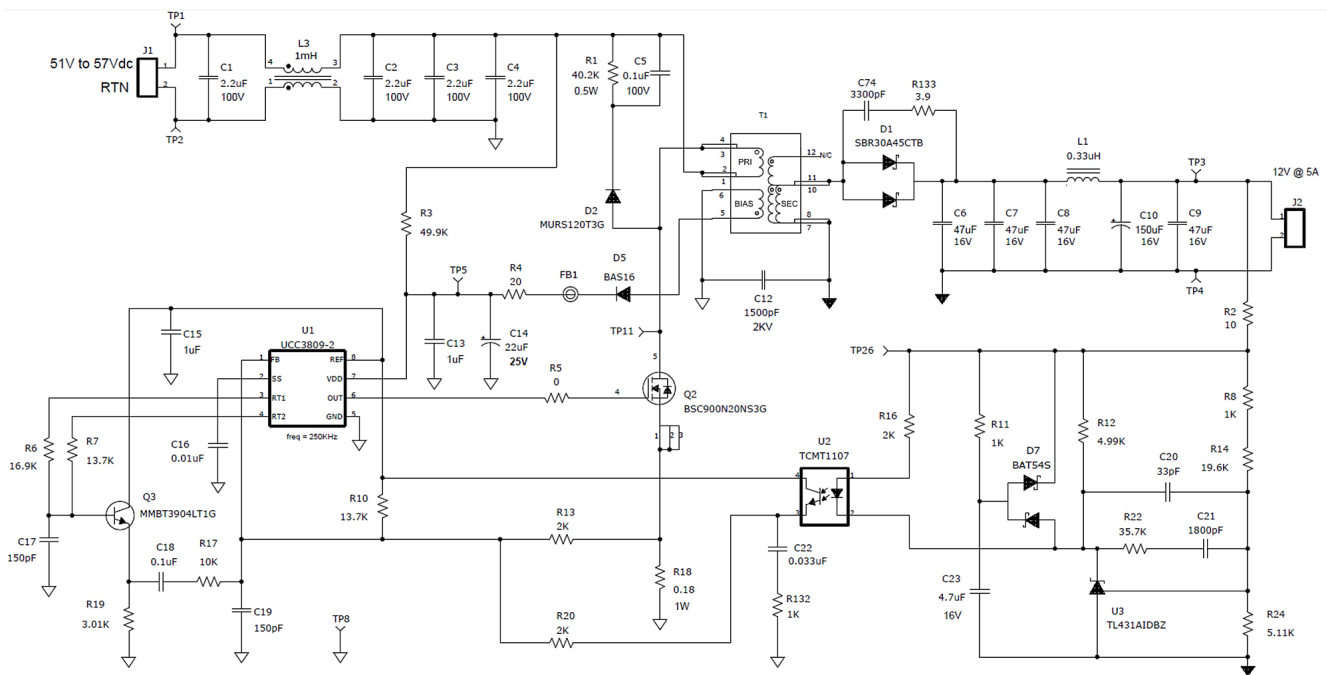


Figure 1. 60 W CCM flyback converter schematic.

Additional transformer windings can be added, or even stacked on top of other windings, to obtain additional outputs. However, the more outputs added, the worse their regulation will be. This is because of the imperfect magnetic flux linkages between the windings and the core (coupling) and the physical separation of the windings, creating leakage inductance. Leakage inductance acts as stray inductance in series with the primary and the output windings. This creates an unintended voltage drop in series with the windings, effectively decreasing output voltage regulation accuracy. A general rule of thumb is to expect non-regulated outputs to vary +/-5 to 10%, over cross-loading, with a properly wound transformer. Additionally, a heavy-loaded regulated output can cause a large increase in an unloaded secondary output’s voltage by peak-detecting leakage-induced voltage spikes. In this case, a preload or soft clamp can help limit the voltage.

CCM and discontinuous-conduction mode (DCM) operation each have their own merits. By definition, DCM operation occurs when the output rectifier current decreases to 0A before the next cycle starts. DCM operation benefits include a lower primary inductance typically resulting in a smaller power transformer, elimination of the rectifier’s reverse-recovery losses and FET turn on losses, and no right-half-plane-zero. However, these advantages are offset by higher peak currents in the primary and secondary, increased input and output capacitances, increased electromagnetic interference (EMI), and decreased duty-cycle operation at light-load compared to CCM.

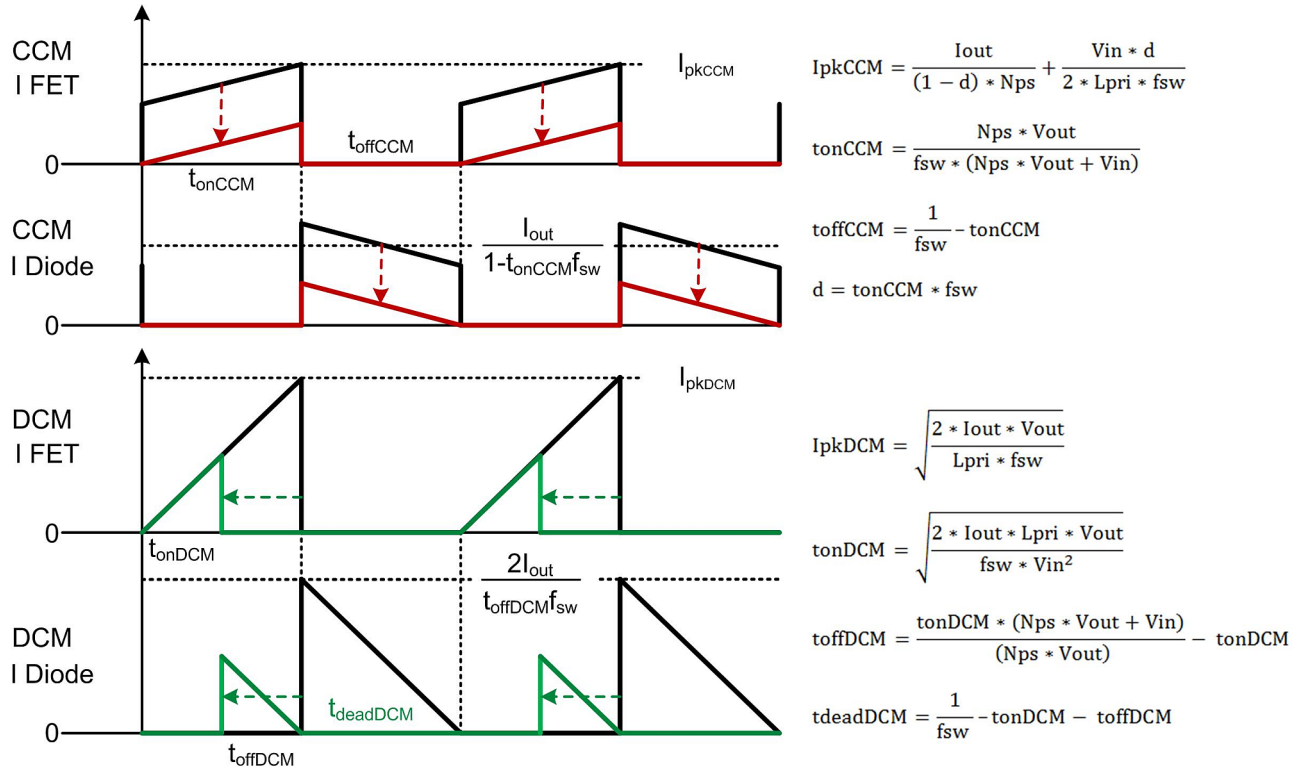

**Figure 2. Comparison of CCM and DCM flyback FET and rectifier currents,**

Figure 2 illustrates how currents in Q2 and D1 change while at minimum  $V_{IN}$ , and the load decreases from the maximum to ~25% in both CCM and DCM. In CCM, the duty cycle is constant for a fixed-input voltage and when the load is between its maximum and minimum design level (~25%). The current “pedestal” levels decrease with reduced loading until DCM is reached, at which point the duty-cycle decreases. In DCM, maximum duty-cycle only occurs at minimum  $V_{IN}$  and maximum load. The duty cycle decreases for increased input voltage or reduced load.

This can make the duty-cycle small at high-line and minimum load, so be sure your controller can operate properly at this minimum on-time. DCM operation introduces a dead-time for duty cycles below 50% after the rectifier current reaches 0A. It’s characterized by a sinusoidal voltage on the FET drain and set by residual current, parasitic capacitances, and leakage inductance, but is generally benign. For this design, CCM operation was chosen because higher efficiency can be achieved from reduced switching and transformer losses.


This design uses a primary referenced 14V bias winding to power the controller after the 12V output reaches regulation, reducing losses versus being directly powered from the input. I chose a two-stage output filter for low-ripple voltage. The first-stage ceramic capacitors handle the high RMS current from the pulsating currents in D1. Their ripple voltage is reduced by filter L1 and C9/C10, providing about 10 times the ripple reduction along with reduced RMS currents in C9/C10. If a higher output ripple voltage is acceptable, the inductor-capacitor filter can be eliminated, but the output capacitors must be capable of handling the full RMS current.

The [UCC3809-1](#) or [UCC3809-2](#) controller is designed to interface directly with the U2 optocoupler for an isolated application. In non-isolation designs, U2 and U3 can be eliminated along with the voltage-feedback resistor-divider connected directly to a controller, such as the [UCC3813-x](#) series with internal error amplifier.

Switching voltages on Q2 and D1 create high-frequency common-mode currents in the transformer interwinding and component parasitic capacitances. Without the EMI capacitor C12 providing a return path, these currents would flow into the input and/or output, increasing noise or possibly erratic operation.

The combination of Q3/R19/C18/R17 provides slope-compensation by summing the oscillator’s voltage-ramp into the primary current-sense voltage of R18, which is used for current-mode control. Slope-compensation eliminates sub-harmonic oscillation, a phenomena characterized by a wide duty-cycle pulse followed by a narrow one. Since this converter is designed to not exceed 50% operation, instead I added slope compensation to reduce switch-jitter susceptibility. However, excessive voltage-slope can push the control loop towards voltage-mode control and possible instability. Finally, the optocoupler transfers the error-signal from the secondary-side to keep the output voltage regulated. The feedback (FB) signal comprises the current-ramp, slope-compensation, output error signal, and DC offset to reduce the over-current threshold.

Figure 3 shows the voltage waveforms for Q2 and D1, displaying some leakage inductance and diode reverse-recovery induced ringing.

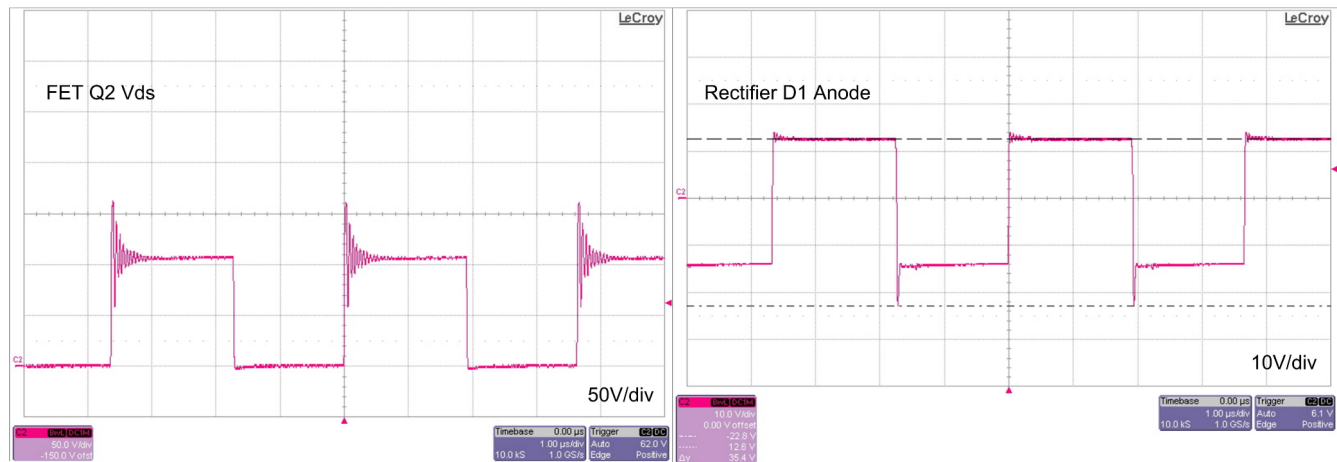

**Figure 3. FET and rectifier ringing are limited with a clamp and snubber (57 V<sub>IN</sub>, 12 V at 5 A).**

Flybacks are considered the standard in applications requiring a low-cost, isolated converter. This design example covers basic design considerations for a CCM flyback design.

Check out TI's Power Tips blog series on Power House.

**Also see :**

- [Power Tips #75: USB Power Delivery for automotive systems](#)
- [How to design a flyback converter as a front-end for a two-stage LED driver](#)
- [LTC Design Note: 560V Input, no-opto isolated flyback converter](#)
- [Quasiresonant flyback converter easily charges energy-storage capacitors](#)
- [Why use a BJT in a flyback converter?](#)

Previously published on [EDN.com](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated