

TI Designs: TIDA-01374 EMC-Compliant, Automotive Stop Light and Tail Light Reference Design



Description

This automotive reference design details a solution for a stop light and a tail light. The automotive battery directly supplies the TPS92830-Q1 linear light-emitting-diode (LED) controller of the TPS92830-Q1 used in this design, which allows the designer to use the same LEDs for both functions. This reference design also features robust electromagnetic compatibility (EMC) performance, full protection, and diagnostics.

Resources

[TIDA-01374](#)

[Design Folder](#)

[TPS92830-Q1](#)

[Product Folder](#)





[ASK Our E2E Experts](#)

Features

- Automotive Battery Supply
- Meets CISPR 25 Conducted and Radiated Emission Standards and Passes ISO11452-4 Bulk Current Injection (BCI) Test
- Stop Light and Tail Light LED Reuse Using Device Internal Pulse Width Modulation (PWM) Generator
- LED-String Open-Circuit, Short-to-Ground, and Short-to-Battery Diagnostics With Auto Recovery
- Fault Bus Configurable as One-Fails-All-Fail or Only-Failed-Channel-Off
- LED Binning Function Using Analog Dimming Input Pin

Applications

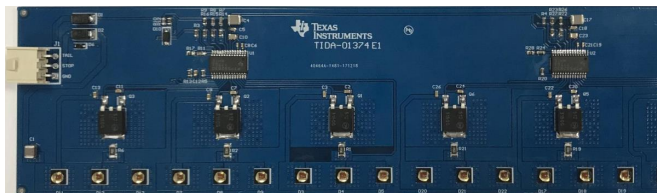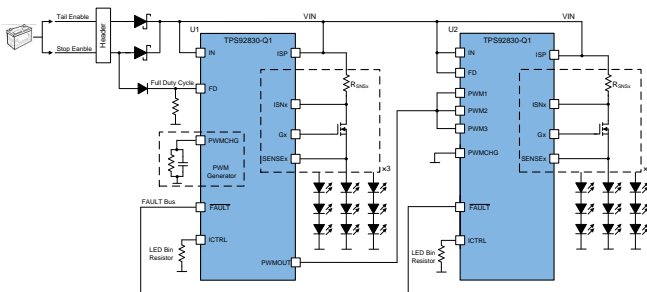- [Automotive Rear Light \(Stop and Tail Light\)](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Description

Automotive stop lights and tail lights often reuse the same LEDs with two levels of brightness. This reference design offers a dual-brightness solution for stop- and tail-light reuse applications, using the integrated PWM generator of the TPS92830-Q1 controller. Two devices are cascaded by a synchronization PWMOUT output.

Using linear devices, this design has a satisfactory EMC performance that meets CISPR 25 Class-5 conducted emission and radiated emission standards and passes the ISO11452-4 BCI test.

This design provides the LEDs and devices with protection from LED string short-to-ground and open-circuit faults, with auto recovery. The LED open-circuit detection is disabled to avoid false diagnostics on an output channel resulting from a low supply voltage. By using different FAULT bus configurations, the designer can configure the system as one-fails-all-fail or only-failed-channel-off.

In the design, by using bin-setting resistors for analog dimming, the device can realize LED-bin brightness correction. In addition, the LED current can be reduced when the input voltage is higher than 18 V, to protect the MOSFETs from overheating.

1.1 Key System Specifications

Table 1. Key System Specifications

| PARAMETER | SPECIFICATION |
|-----------------------------|-------------------------------|
| Input voltage range | 9 V to 16 V |
| Output current (tail light) | 150 mA/CH with 20% duty cycle |
| Output current (stop light) | 150 mA/CH |
| LED number | 3s6p |
| LED type | LR H9GP, OSRAM |

2 System Overview

2.1 Block Diagram

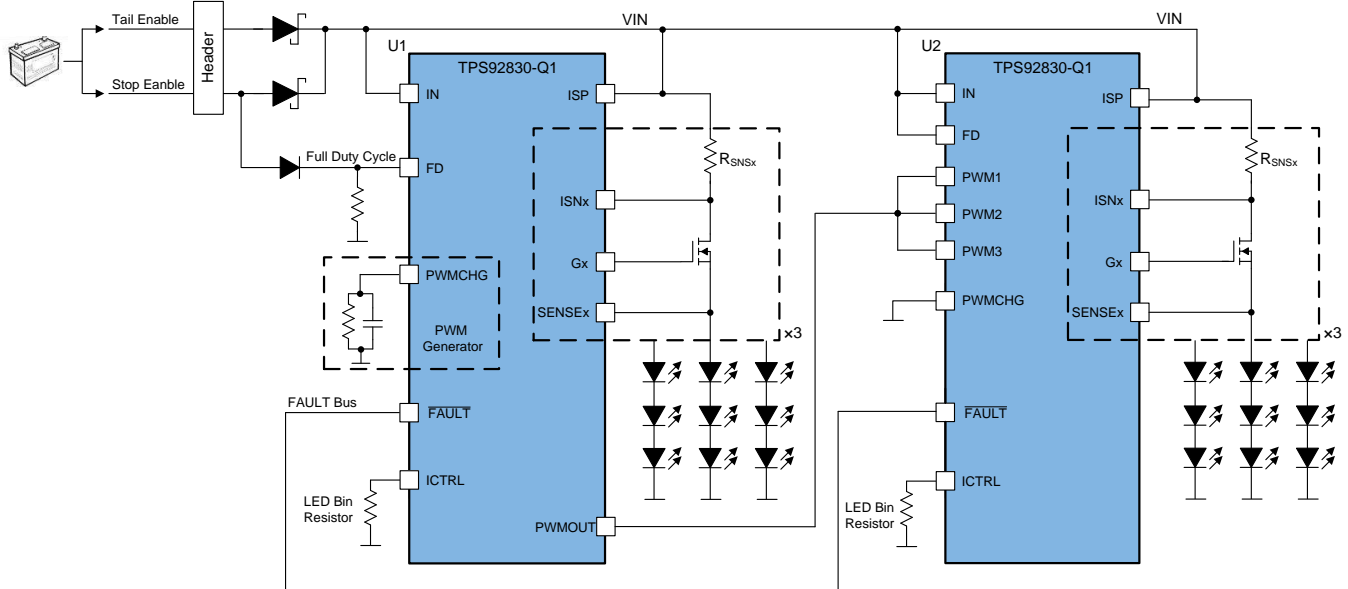


Figure 1. TIDA-01374 Block Diagram

2.2 Highlighted Products

2.2.1 TPS92830-Q1

The TPS92830-Q1 device is an advanced, automotive-grade, high-side, constant-current, linear LED controller, which delivers high current using external N-channel MOSFETs. The device has a full set of features for automotive applications. Each channel of the TPS92830-Q1 device independently sets the channel current using the sense resistor value. An internal, precision, constant-current, regulation loop senses the channel current by the voltage across the sense resistor and controls the gate voltage of the N-channel MOSFET accordingly. The device also integrates a two-stage charge pump for low-dropout operation. The charge-pump voltage is high enough to support a wide selection of N-channel MOSFETs. PWM dimming allows multiple sources for flexibility: internal PWM generator, external PWM inputs, or power-supply dimming. Various diagnostic and protection features specially designed for automotive applications help to improve the system robustness and ease of use. A one-fails-all-fail FAULT bus supports TPS92830-Q1 operation, together with the TPS92630-Q1, TPS92638-Q1, and TPS9261x-Q1 family of devices, to fulfill various fault-handling requirements.

For more information on the TPS92830-Q1 device used in this reference design, see the [TPS92830-Q1 product folder](#).

3 System Design Theory

This reference design uses two TPS92830-Q1, linear LED controllers to drive six red LED strings. The TPS92830-Q1 device provides a precision PWM generator to realize the dual-brightness output control for automotive stop and tail light applications. Two devices are cascaded by a synchronization PWMOUT output. With a full set of features from the TPS92830-Q1, the design can realize various functions with simple external circuits. Figure 2 shows the schematic of the design. The following subsections provide details on the design.

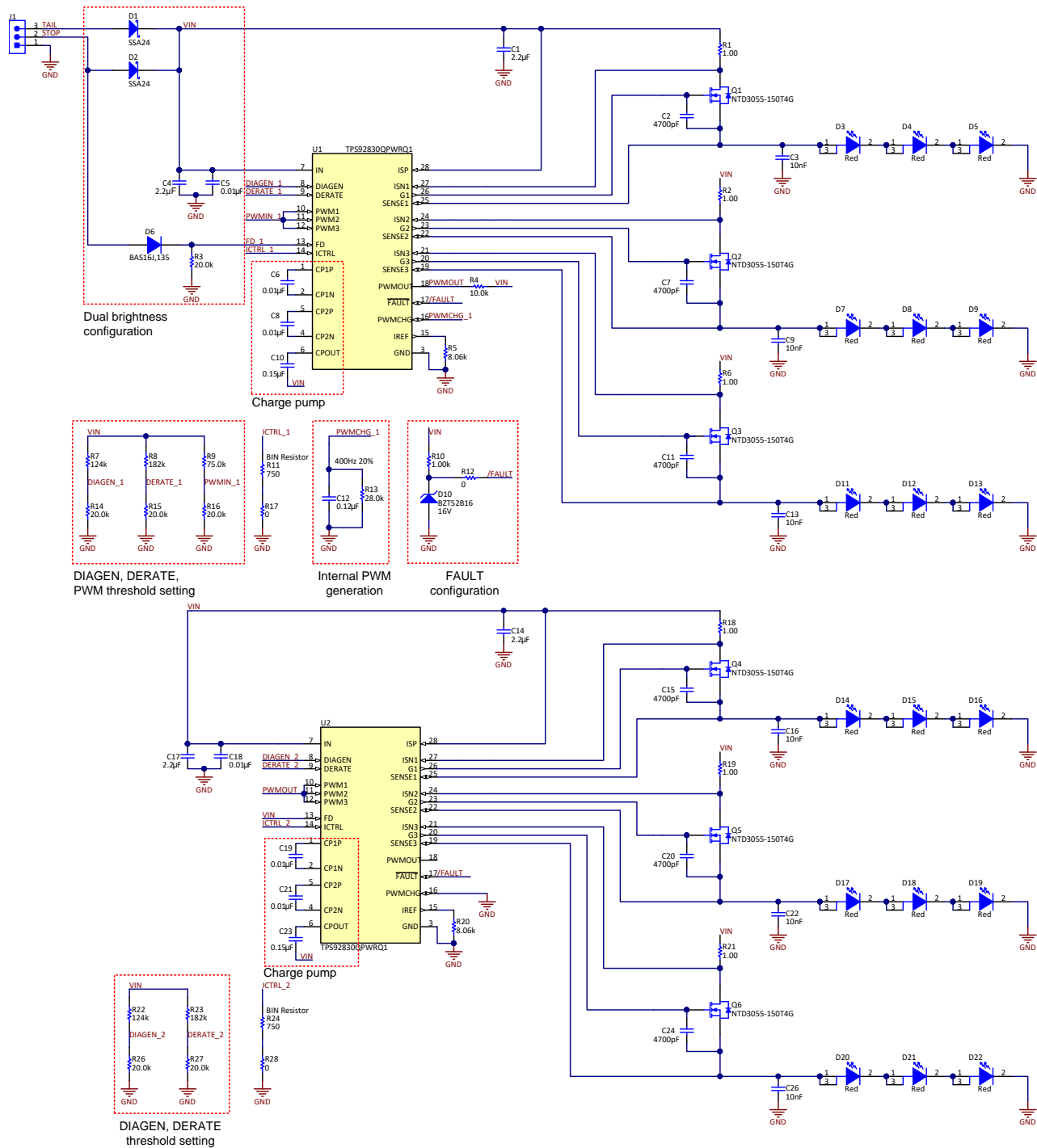


Figure 2. TIDA-01374 Schematic

3.1 Dual-Brightness Design

3.1.1 Dual-Brightness Control

This reference design uses the same set of LEDs to illuminate both automotive stop and tail lights. The LEDs can operate at two different brightness levels. One way to set the brightness level is through analog dimming, which means the LEDs always operate at a 100% duty cycle, and the maximum current through the LEDs varies to the required level of brightness. However, differing levels of LED current may affect the LED color temperature. The other option is to use PWM dimming, which can achieve the desired dimming ratio with the same color temperature.

The TPS92830-Q1 device provides an integrated precision-PWM generator for on-chip PWM dimming. An external RC circuit sets the duty cycle and frequency of the PWM signal, as shown in Figure 2. The device can flexibly switch between the internal PWM modulation mode and the 100% duty cycle mode by using the FD input. When the FD pin is low, the channel PWM depends on the internal PWM generator. When the FD pin is high, the internal PWM generator is bypassed, and the PWM inputs take complete control of the output. Moreover, the device supports open-drain PWMOUT for synchronization between devices. Each device can be connected as a master, which generates PWM, or as a slave, which relies on external PWM sources.

In this design, by connecting PWMOUT of U1 (TPS92830-Q1) to three PWM inputs of U2 (TPS92830-Q1), the two devices are in a master-slave configuration. When the STOP terminal is connected to the battery, the FD input of U1 is high. The output current of U1 is 150 mA per channel at a 100% duty cycle. Also, PWMOUT of U1 is high, so the output current of U2 is also at full duty cycle. The LED strings work in stop mode. When the TAIL terminal is connected to the battery, the FD input of U1 is low. The output current of U1 and U2 is at a 20% duty cycle and 400 Hz, as the external RC circuit sets. The LED strings work in tail light mode.

3.1.2 LED Current Design

The TPS92830-Q1 device has three independent, constant, current-driving channels. Each channel sets the channel current with an external, high-side, current-sense resistor, R_{SNSx} . The channel current is set as $V_{(CS_REG)} / R_{SNSx}$.

Considering the analog dimming pin, ICTRL, is used for LED-bin brightness correction, the current-sense voltage, $V_{(CS_REG)}$, is reduced using a dimming ratio, $k_{(ICTRL_DIM)}$. The voltage across the sense resistor and the output current are reduced if the ICTRL voltage, $V_{(ICTRL)}$, decreases. Figure 3 shows the analog dimming ratio versus the $V_{(ICTRL)}$ voltage. In the linear region, the analog dimming ratio can be calculated using Equation 1.

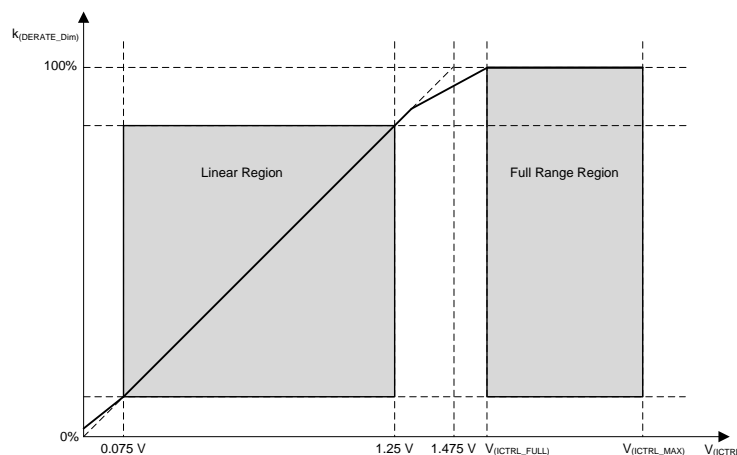


Figure 3. Analog Dimming Ratio

$$k_{(\text{ICTRL_DIM})} = \frac{V_{(\text{ICTRL})}}{1.475 \text{ V}} \times 100\% = \frac{I_{(\text{ICTRL_pullup})} \times R_{\text{Bin}}}{1.475 \text{ V}} \times 100\%$$

where

- $I_{(\text{ICTRL_pullup})}$ is the ICTRL, internal pull-up current (typically 0.985 mA).
 - R_{Bin} is the bin-setting resistor connected between ICTRL and GND.
- (1)

In this design, the current for each LED string is set at 150 mA, so the current-sense resistors can be calculated using [Equation 2](#).

$$R1(\text{R18}) = R2(\text{R19}) = R6(\text{R21}) = \frac{V_{(\text{CS_REG})} \times k_{(\text{ICTRL_DIM})}}{I_{(\text{CH})}} = \frac{0.295 \times 0.985 \times R_{\text{Bin}}}{150 \times 1.475}$$

where

- $V_{(\text{CS_REG})}$ is the current-sense resistor-regulation voltage (typically 295 mV).
 - $I_{(\text{CH})}$ is the channel current.
- (2)

In this design, use 750- Ω resistors for R_{Bin} , R11 and R24. Use 1.0- Ω resistors for R1 (R18), R2 (R19) and R6 (R21). Designers can use bin-setting resistors of different value to adjust the output current if using LEDs from different bins, while the current-sense resistors can remain unchanged.

3.1.3 PWM Generator Design

As [Section 3.1.1](#) describes, the designer must generate a 20% duty cycle and 400-Hz frequency PWM output to implement the tail light function. The PWM generator uses reference current $2 \times I_{(\text{IREF})}$ as the internal charge current, $I_{(\text{PWMCHG})}$. The recommended value of the reference resistors R5 and R20 in [Figure 2](#) is 8 k Ω . Select 8.06-k Ω resistors in this design.

Use external resistor R13 and C12 to set the PWM cycle time and duty cycle as required (see [Equation 3](#) and [Equation 4](#)).

$$D_{(\text{Tail})} = \frac{\ln \left(\frac{V_{(\text{PWMCHG_th_falling})} - I_{(\text{PWMCHG})} \times R13}{V_{(\text{PWMCHG_th_rising})} - I_{(\text{PWMCHG})} \times R13} \right)}{\ln \left(\frac{V_{(\text{PWMCHG_th_falling})} - I_{(\text{PWMCHG})} \times R13}{V_{(\text{PWMCHG_th_rising})} - I_{(\text{PWMCHG})} \times R13} \right) + \ln \left(\frac{V_{(\text{PWMCHG_th_rising})}}{V_{(\text{PWMCHG_th_falling})}} \right)}$$
(3)

$$f_{(\text{Tail})} = \frac{1}{R13 \times C12 \times \left[\ln \left(\frac{V_{(\text{PWMCHG_th_falling})} - I_{(\text{PWMCHG})} \times R13}{V_{(\text{PWMCHG_th_rising})} - I_{(\text{PWMCHG})} \times R13} \right) + \ln \left(\frac{V_{(\text{PWMCHG_th_rising})}}{V_{(\text{PWMCHG_th_falling})}} \right) \right]}$$
(4)

R13 can be derived as follows in Equation 5.

$$R13 = \frac{V_{(PWMCHG_th_falling)} \times \left(\frac{V_{(PWMCHG_th_falling)}}{V_{(PWMCHG_th_rising)}} \right)^{\frac{D_{(Tail)}}{1-D_{(Tail)}}} - V_{(PWMCHG_th_rising)}}{I_{(PWMCHG)} \left[\left(\frac{V_{(PWMCHG_th_falling)}}{V_{(PWMCHG_th_rising)}} \right)^{\frac{D_{(Tail)}}{1-D_{(Tail)}}} - 1 \right]}$$

where

- $D_{(Tail)} = 0.2$
- $f_{(Tail)} = 400$
- $V_{(PWMCHG_th_rising)}$ is typically 1.48 V.
- $V_{(PWMCHG_th_falling)}$ is typically 0.8 V (1).
- $I_{(PWMCHG)}$ is typically 200 μ A (1).

(1) Data sheet value; see the data sheet for a detailed calculation description.

(5)

C12 can be derived as follows in Equation 6.

$$C12 = \frac{1 - D_{(Tail)}}{R13 \times f_{(Tail)} \times \ln \left(\frac{V_{(PWMCHG_th_rising)}}{V_{(PWMCHG_th_falling)}} \right)}$$

(6)

Equation 3 shows that the duty cycle is only dependent on R13 and has nothing to do with C12, so the capacitance variation of C12 has no impact on the precision of the duty cycle.

According to the calculation, use $R13 = 28 \text{ k}\Omega$ and $C12 = 0.12 \text{ }\mu\text{F}$ in the design.

Because U2 is connected as a slave, the PWM input of U2 is connected to PWMOUT of U1 for synchronization. FD of U2 is pulled up to VIN and the PWM-generator oscillation stops. PWMCHG of U2 is connected to ground directly.

3.2 Charge Pump Design

The TPS92830-Q1 device uses a two-stage charge pump to generate the high-side gate-drive voltage, as shown in Figure 2. The charge pump is a voltage tripler using external flying capacitors C6 (C19) and C8 (C21) and storage capacitor C10 (C23). The charge-pump voltage is high enough to support a wide selection of N-channel MOSFETs. Recommended capacitance for C6 (C19) and C8 (C21) and C10 (C23) is 10 nF, 10 nF and 150 nF.

3.3 MOSFET Driving Circuits

To ensure control-loop stability, the drive circuit requires sufficient gate-to-source capacitance (C_{GS}) on the MOSFETs. TI recommends the minimum total gate-to-source capacitance on the MOSFETs is 4 nF. For the NVD3055-150 MOSFET, TI recommends placing additional capacitors across the gate and source terminals, because C_{GS} is smaller than 1 nF. Use $C2 (C15) = C7 (C20) = C11 (C24) = 4.7 \text{ nF}$.

3.4 LED Fault Design

The TPS92830-Q1 device provides advanced diagnostics and fault protection methods for this design. The device can detect and protect the system from LED output short-to-GND, LED output open-circuit, and device overtemperature scenarios.

The TPS92830-Q1 supports flexible, FAULT bus diagnostic, which can be configured as one-fails-all-fail or only-failed-channel-off, based on legislative requirements and application conditions. Setting resistor R12 enables and disables the one-fails-all-fail function.

In Figure 4, when R12 is not mounted, the $\overline{\text{FAULT}}$ pin is floating. During normal operation, an internal pull-up current source weakly pulls up the $\overline{\text{FAULT}}$ pin. If any fault scenario occurs, an internal pulldown current source strongly pulls the $\overline{\text{FAULT}}$ pin low. All outputs shut down for protection, which effectively realizes the one-fails-all-fail function. The faulty channel continually retries until the fault condition is removed. The designer can also connect the FAULT bus to an MCU for fault reporting.

If R12 is mounted, the $\overline{\text{FAULT}}$ pin is externally pulled up. The one-fails-all-fail function is disabled and only the faulty channel is turned off. A 16-V Zener diode (D10) is used to prevent the $\overline{\text{FAULT}}$ pin from overvoltage, because the recommended maximum operating voltage for the $\overline{\text{FAULT}}$ pin is 20 V.

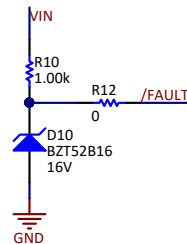


Figure 4. Fault Bus Configuration of TPS92830-Q1

3.5 DIAGEN, DERATE, and PWM Threshold Setting

Figure 5 shows a schematic of the DIAGEN, DERATE, and PWM threshold setting.

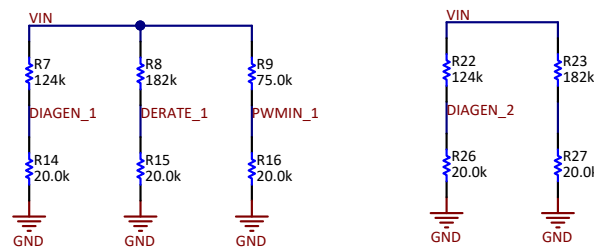


Figure 5. DIAGEN, DERATE, and PWM Threshold Setting

3.5.1 DIAGEN Setting

When the input voltage is not high enough to keep the external N-channel MOSFET in the constant-current saturation region, the TPS92830-Q1 device works in low-dropout mode. In low-dropout mode, the LED open-circuit detection must be disabled through the DIAGEN input. Otherwise, the dropout mode would be treated as an LED open-circuit fault.

In this design, LED open detection is enabled when $V_{IN} > 9$ V. Use Equation 7 to set the resistor dividers R7 (R22) and R14 (R26).

$$K_{(\text{RES_DIAGEN})} = \frac{R14(\text{R26})}{R7(\text{R22}) + R14(\text{R26})} = \frac{V_{IH}(\text{DIAGEN, max})}{9}$$

where

- $V_{IH}(\text{DIAGEN, max})$ is the maximum-input logic-high voltage for the DIAGEN pin in the data sheet (1.255 V). (7)

Set R7 (R22) = 124 k Ω and R14 (R26) = 20 k Ω .

3.5.2 DERATE Setting

The TPS92830-Q1 device has an integrated output-current derating function. Voltage across the sense resistor is reduced if the DERATE pin voltage ($V_{(\text{DERATE})}$) increases, so that the output current is reduced as well. Figure 6 shows the output-current derating profile.

With an external resistor divider, R8 (R23) and R15 (R27), connected from V_{IN} to set the $V_{(DERATE)}$ voltage, as shown in Figure 5, the current is reduced when V_{IN} rises above the set level. Therefore, the current derating function can be used to limit power dissipation in external MOSFETs and LEDs, to prevent thermal damage at a high-input voltage.

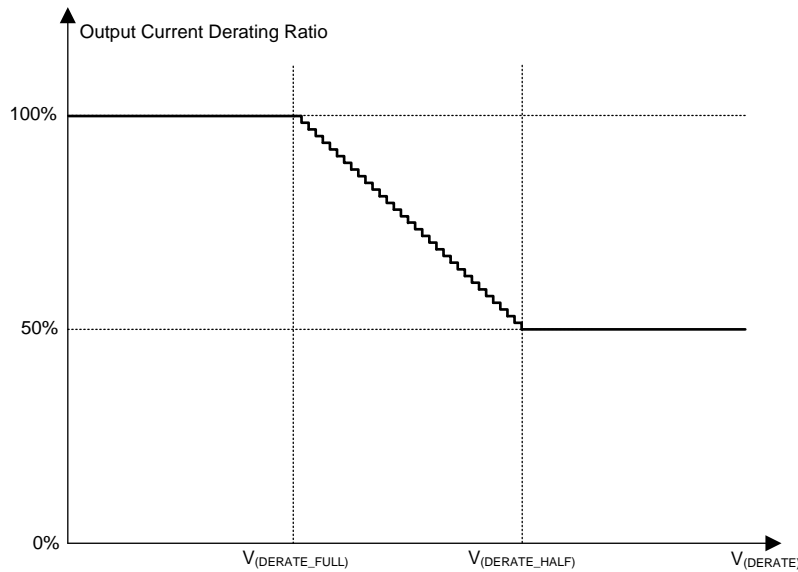


Figure 6. Output-Current Derating Profile

In this design, the output current is configured to be reduced when $V_{IN} > 18$ V, with the output-current derating feature. Use Equation 8 to set the resistor divider ratio.

$$K_{(RES_DERATE)} = \frac{R15(R27)}{R8(R23) + R15(R27)} = \frac{V_{(DERATE_FULL)}}{18}$$

where

- $V_{(DERATE_FULL)}$ is the full-range DERATE voltage in the data sheet (1.83 V). (8)

Set R8 (R23) = 182 k Ω and R15 (R27) = 20 k Ω .

3.5.3 PWM Threshold Setting

With the wide range of battery voltages in modern automotive systems, a common requirement among car OEMs is to turn LEDs off when the battery voltage is below the minimal voltage threshold. In this design, the three channels are designed to be enabled when $V_{IN} > 6$ V. PWM1 to PWM3 are connected together with a resistor divider, R9 and R16. Use Equation 9 to set the resistor-divider ratio.

$$K_{(RES_PWM)} = \frac{R16}{R9 + R16} = \frac{V_{IH(PWMx, \max)}}{6}$$

where

- $V_{IH(PWMx, \max)}$ is the maximum-input logic-high voltage for PWM in the data sheet (1.248 V). (9)

Set R9 = 75 k Ω and R16 = 20 k Ω .

4 Getting Started Hardware

The following steps outline the hardware setup (see [Figure 7](#)).

1. Connect a 12-V DC power supply across terminals TAIL and GND, to enable the tail-light function.
2. Connect a 12-V DC power supply across terminals STOP and GND, to enable the stop-light function.



Figure 7. TIDA-01374 Board

5 Testing and Results

5.1 System-Input Current Tested Under Different Brightness Levels

With supply voltage applied to stop light input and tail light input, the device operates at 100% duty cycle and 20% duty cycle, respectively, achieving different brightness levels. [Table 2](#) lists the system-input currents tested under two different brightness levels.

Table 2. System Input Current

| FUNCTION | BRIGHTNESS | INPUT VOLTAGE | INPUT AVERAGE CURRENT |
|------------|------------|---------------|-----------------------|
| Stop light | 100% | 9 V | 903 mA |
| | | 12 V | 903 mA |
| | | 16 V | 902 mA |
| Tail light | 20% | 9 V | 188 mA |
| | | 12 V | 188 mA |
| | | 16 V | 188 mA |

5.2 Waveforms

Figure 8 and Figure 9 show the input voltage and input-current waveforms for the stop and tail light function, respectively.

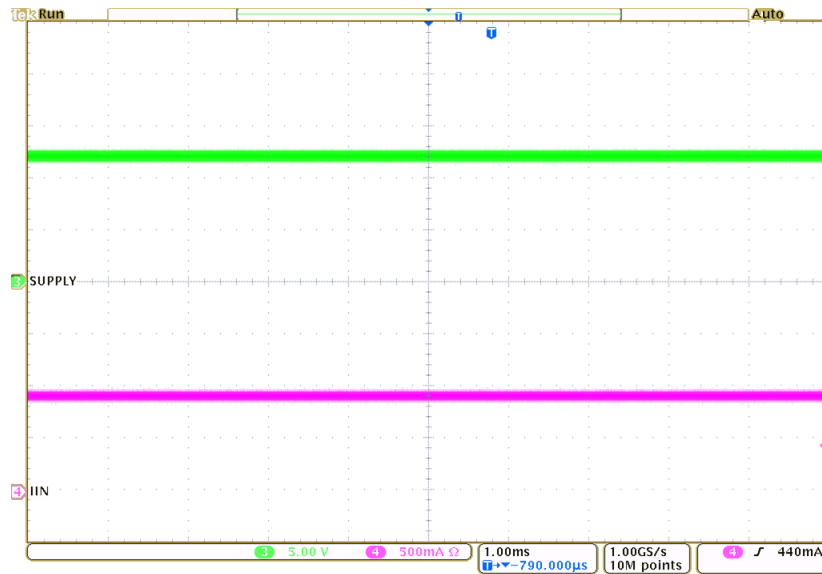


Figure 8. Stop-Function Waveform
CH3: Supply Voltage and CH4: Input Current

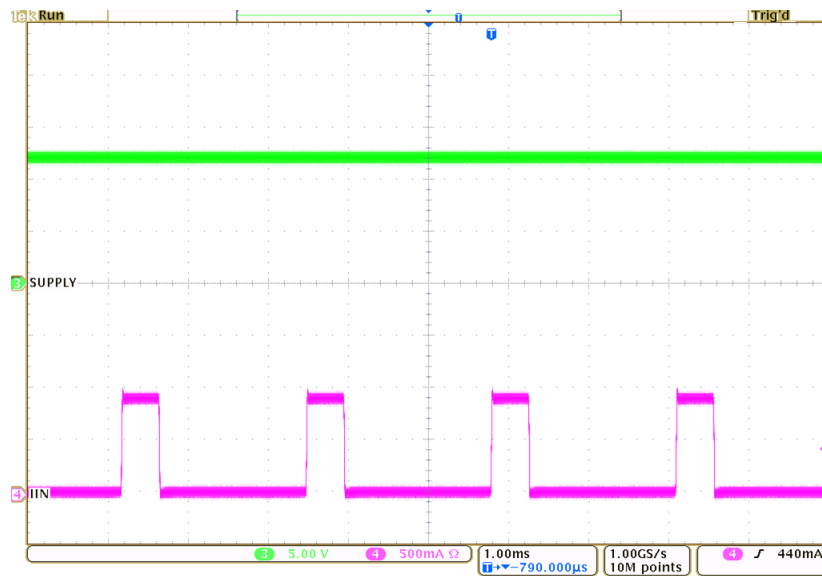


Figure 9. Tail-Light Function Waveform
CH3: Supply Voltage and CH4: Input Current

5.3 Thermal Results

Figure 10 and Figure 11 show the infrared thermal images of the design when operating as a stop and tail light, respectively. The input voltage is 12 V. The ambient temperature is 25°C.

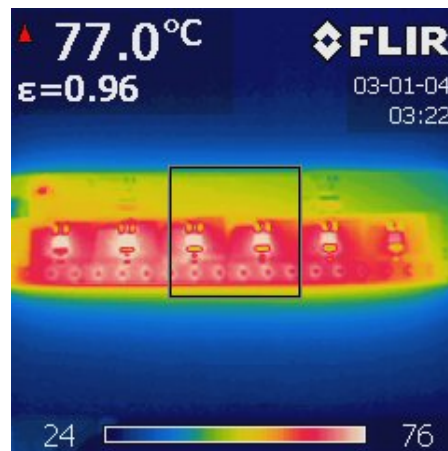


Figure 10. Thermal Image of Stop-Light Function at 25°C, 12-V Input Voltage



Figure 11. Thermal Image of Tail-Light Function at 25°C, 12-V Input Voltage

5.4 EMC Test Results

This reference design is compliant with several EMC standards that are important for automotive applications. The design has been tested against the CISPR 25 conducted and radiated emissions standard and ISO11452-4 BCI standard at a qualified third-party facility. The following subsections provide the test results.

5.4.1 Conducted and Radiated Emissions Test

CISPR 25 is the automotive EMI standard that most OEMs reference for requirements. Both conducted and radiated emissions tests for this design were completed against the CISPR 25 standards. The test was conducted at 13.5 V input when operating at the stop function mode.

[Table 3](#) lists the summarized results of both the conducted and radiated portions of the tests across different operating points and test conditions. For the test setup, test equipment, limits, and detailed test results, see the official test report at [TIDA-01374](#).

Table 3. Conducted and Radiated Emissions Test Results Summary

| RADIATED EMISSION (ALSE METHOD) - CISPR25: 2008 | | | | | |
|---|----------------------|------------------------------|------------------|--------------------------|--------------------------|
| FREQUENCY BAND (MHz) | ANTENNA POLARIZATION | MEASUREMENT SYSTEM BANDWIDTH | DETECTION SCHEME | TEST LIMIT | TEST RESULT DESCRIPTION |
| 0.15 to 30 | V | 9 kHz | PK/QP/AV | CISPR25: 2008 Class 5 | Meets requirement |
| 30 to 200 | V | 120 kHz | PK/QP/AV | | Meets requirement |
| | H | 120 kHz | PK/QP/AV | | Meets requirement |
| 200 to 1000 | V | 120 kHz | PK/QP/AV | | Meets requirement |
| | H | 120 kHz | PK/QP/AV | | Meets requirement |
| 1000 to 2500 | V | 9/120 kHz | PK/AV | | Meets requirement |
| | H | 9/120 kHz | PK/AV | | Meets requirement |
| CONDUCTED EMISSION (VOLTAGE MODE) - CISPR25: 2008 | | | | | |
| FREQUENCY BAND (MHz) | SUPPLY LINE POLARITY | MEASUREMENT SYSTEM BANDWIDTH | DETECTION SCHEME | TEST LIMIT | TEST RESULTS DESCRIPTION |
| 0.15 to approximately 108 | Positive | 9/120 kHz | PK/QP/AV | CISPR25: 2008 Class 5 | Meets requirement |
| | Negative | 9/120 kHz | PK/QP/AV | | Meets requirement |

5.4.2 BCI Test

The BCI test for this design was conducted against the ISO11452-4 standard and at a 13.5-V input when operating in stop mode. [Table 4](#) and [Table 5](#) list the test requirement and acceptance criteria of the BCI test. [Table 6](#) summarizes the test results. For the test setup, test equipment, limits, and detailed test results, see the official test report at [TIDA-01374](#).

Table 4. BCI Test Requirement

| BULK CURRENT INJECTION-ISO11452-4: 2011 | | | |
|---|---------------------------|------------------|-----------------|
| FREQUENCY (MHz) | FREQUENCY STEP SIZE (MHz) | DWELL TIME (sec) | TEST LEVEL (mA) |
| 1 to 10 | 1 | 2 | 200 |
| 10 to 200 | 5 | 2 | 200 |
| 200 to 400 | 10 | 2 | 200 |

Table 5. BCI Test Acceptance Criteria

| WORKING MODE | MONITORING PARAMETERS | ACCEPTANCE | TEST LEVEL | STATUS |
|--------------|-----------------------|-----------------------|------------|---------|
| Mode 1 | Brightness of light | No obvious phenomenon | 200 mA | Class A |

Table 6. BCI Test Results Summary

| FREQUENCY BAND (MHz) | INJECTION MODE | POSITION (mm) | MODULATION | TEST LEVEL | TEST RESULTS DESCRIPTION |
|----------------------|----------------|---------------|------------|------------|--------------------------|
| 1 to 400 | CBCI | 150 | CW | 200 mA | No obvious phenomenon |
| | | | AM | | No obvious phenomenon |
| | | 450 | CW | | No obvious phenomenon |
| | | | AM | | No obvious phenomenon |
| | | 750 | CW | | No obvious phenomenon |
| | | | AM | | No obvious phenomenon |

6 Design Files

6.1 Schematics

To download the schematics, see the design files at [TIDA-01374](#).

6.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01374](#).

6.3 PCB Layout Recommendations

This design relies on external MOSFETs to dissipate heat. The thermal performance of the design is highly dependent on the cooling conditions of the MOSFETs and LEDs. A good printed-circuit board (PCB) design can optimize heat transfer, which is essential for long-term reliability. Consider the following PCB layout recommendations:

- Increase copper thickness or use metal-based boards if possible. Maximize the copper coverage on the PCB to increase the thermal conductivity of the board. Place thermal vias on the thermal dissipation area to further improve the thermal dissipation capability.
- The current path starts from IN through the sense-resistors, MOSFETs, and LEDs to GND. Wide traces are helpful to reduce parasitic resistance along the current path.
- Place capacitors, especially charge-pump capacitors, close to the device to make the current path as short as possible.

6.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01374](#).

6.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01374](#).

6.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01374](#).

6.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01374](#).

7 Related Documentation

1. CISPR 25, Edition 3.0, 2008-03, *Vehicles, Boats and Internal Combustion Engines – Radio Disturbance Characteristics – Limits and Methods of Measurement for the Protection of On-Board Receivers*
2. ISO11452-4, Edition 4, 2011-12, *Road vehicles — Component test methods for electrical disturbances from narrowband radiated electromagnetic energy — Part 4: Harness excitation methods*
3. Texas Instruments, [TPS92830-Q1 3-Channel High-Current Linear LED Controller](#), data sheet

7.1 Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated