



说明

此参考设计演示了如何在具有集成保护功能和 RTD 传感器前端并且 PCB 宽度为 6mm 的小型器件中进行 IO-Link 通信。高度集成的微型 IO-Link PHY 可提供 ESD、EFT 和浪涌保护以及反极性保护。内置的 LDO 和可配置的输出电流可提供简单灵活的系统实现方案，同时还由于超低的残余电压而实现低功耗。24 位  $\Sigma$ - $\Delta$  模数转换器 (ADC) 可捕获 RTD 值 (PT100 温度传感器)，该值在 MCU 中经过转换并经由 IO-Link 发送到 IO-Link 主站。

资源

<a href="#">TIDA-01335</a>	设计文件夹
<a href="#">TIOL111</a>	产品文件夹
<a href="#">MSP430FR5738</a>	产品文件夹
<a href="#">ADS1220</a>	产品文件夹




咨询我们的 E2E 专家

特性

- IO-Link PHY 具有以下集成特性：
  - 3.3V 或 5V LDO
  - 反极性保护
  - 符合 IEC 61000-4 标准的 ESD、EFT 和浪涌保护
- 50 至 350mA 可配置输出电流限制
- IO-Link V1.1 和 V1.0 (TMG 堆栈)
- 宽度仅为 6mm 的小型 PCB 板
- RTD 性能: 0.17°C

应用

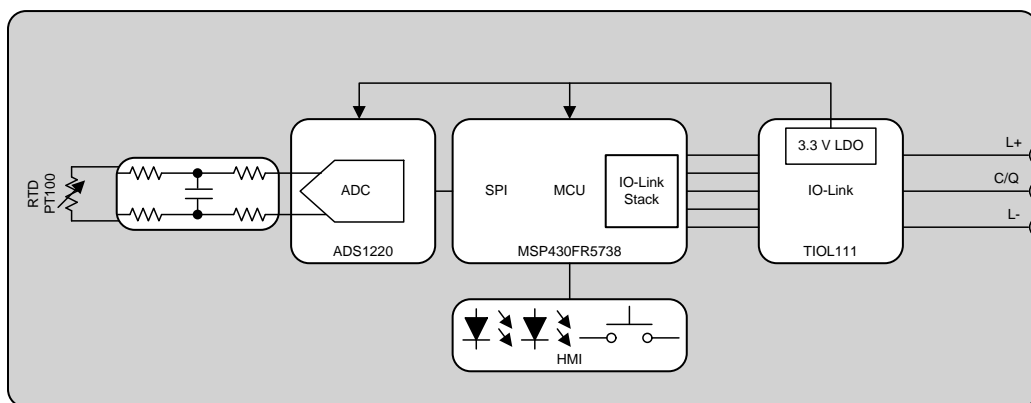- 工厂自动化与控制
- 位移变送器
- 温度变送器
- 流量变送器
- 液位变送器
- 压力变送器



Copyright © 2017, Texas Instruments Incorporated



该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

## 1 System Description

In Factory Automation and Control systems, the IO-Link interface is becoming more and more popular. Applications that usually have a switching output, either NPN or PNP, are upgraded with the IO-Link standard. With this upgrade, two possible scenarios can be addressed:

1. Extend the switching output with the capability to program and configure the field transmitter with IO-Link.
2. Completely communicate with the IO-Link protocol between the field transmitter and PLC.

For the IO-Link communication, a stack is implemented in the MCU, which is also part of this system design. To easily showcase the functionality, a resistance temperature detector (RTD) sensor (in particular, a PT100 element) is connected to the 24-bit ADC, so the sensor data is sent through the IO-Link interface. When the system is connected to an IO-Link master system, the temperature information is shown in the master software.

In addition, this reference design allows one to set a temperature threshold level either with the switch button or configured using IO-Link through the IO-Link master. Two LEDs indicating the status of the system, whether the IO-Link communication is established or in case an error occurs.

The highly integrated IO-Link PHY with a size of only 2.5 mm × 3 mm provides reverse polarity protection and helps designers meet system compliance with the International Electrotechnical Commission (IEC) 61000-4 standard. The built-in EMC protection allows for:

- ±16-kV IEC 61000-4-2 ESD Contact Discharge
- ±4-kV IEC 61000-4-4 Electrical Fast Transient (EFT)
- ±1.2-kV/500-Ω IEC 61000-4-5 Surge

With the capability of using the onboard LDO with either a 3.3-V or 5-V output, the remaining system can be supplied with up to 20 mA. In this reference design, the integrated 3.3-V LDO supplies the MCU and the 24-bit ADC with power from the voltage input, which covers a range from 7 to 36 V with a ±65-V tolerant transient.


This feature set is key for very small field transmitters, like the 6-mm wide PCB in this reference design, which easily fits in a M12-sized tube.

## 1.1 Key System Specifications

PARAMETER	SPECIFICATIONS / COMMENTS
<b>ANALOG FRONT-END</b>	
PT100	3-wire mode
Current excitation	Programmable (10, 50, 100, 250, 500, 1000, 1500 $\mu$ A)
Reference resistor	3.24 k $\Omega$ , Tol = 0.1 %, TC = 10 ppm/C
Resolution	24-bit ADC
<b>DIGITAL PROCESSING</b>	
Temperature calculation	Look up table, based on the Callendar-Van Dusen equation
IO-Link stack	TMG
	V1.1 and V1.0
	Supports COM3
<b>INTERFACE</b>	
Communication	IO-Link
SIO	NPN, PNP
	50- to 350-mA configurable current limit
<b>ALARM</b>	
Fault indicator (open drain)	Overcurrent
	Temperature
	Power supply
<b>POWER SUPPLY</b>	
Operating voltage	7- to 36-V DC
	$\pm$ 65-V transients < 100 $\mu$ s
LDO	3.3-V output voltage
	20-mA output current

## 2 System Overview

### 2.1 Block Diagram

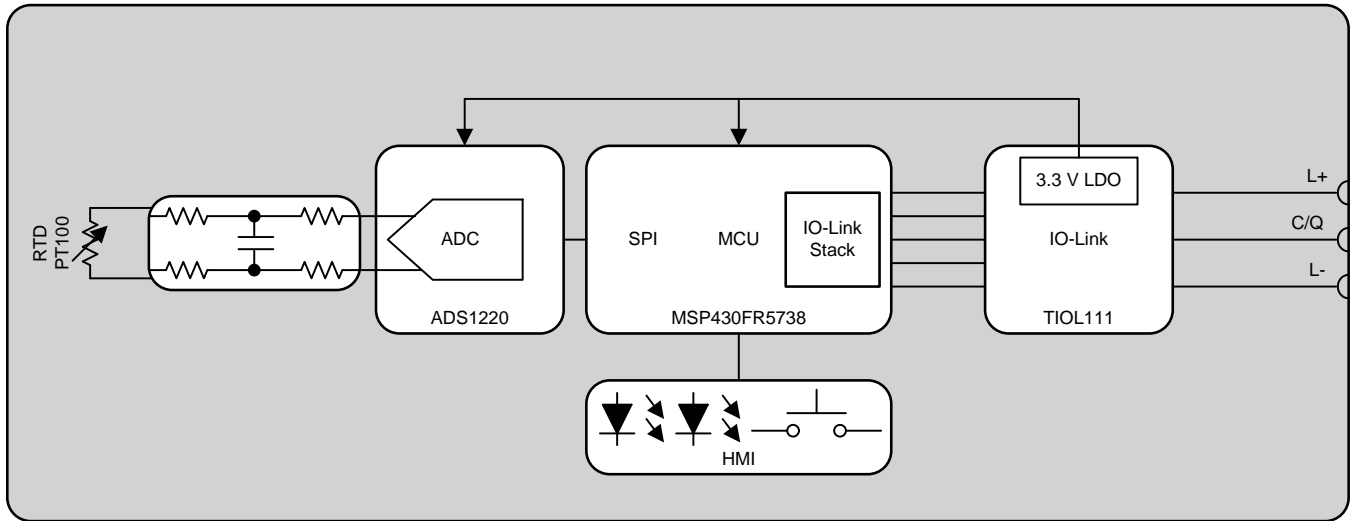

Copyright © 2017, Texas Instruments Incorporated


图 1. TIDA-01335 Block Diagram

## 2.2 Design Considerations

### 2.2.1 IO-Link Interface

The highly integrated IO-Link PHY TIOL111 requires only a small amount of external components. In this reference design, C10, C11, and C13 are placed at the inputs. C9 is the output capacitor of the integrated LDO, and R16 is the resistor setting the maximum output current. The two output signals WAKE and FAULT are open-drain outputs. The needed pullup resistors are inside the MSP430™.

图 2 shows the schematic of the IO-Link interface. J2 is the M12 connector.

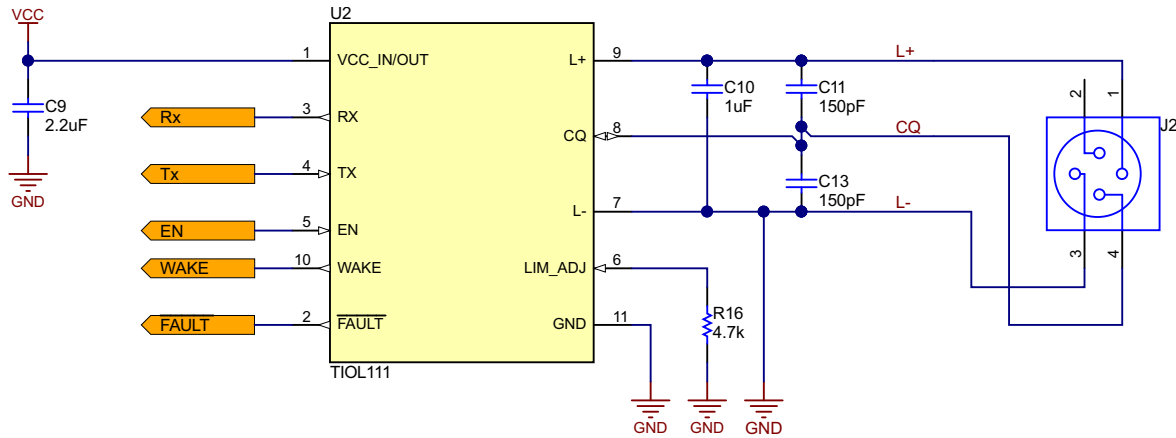

Copyright © 2017, Texas Instruments Incorporated

图 2. IO-Link Interface and 3.3-V Output

The TIOL111 device comes in three different versions:


- TIOL111-3: IO-Link PHY with an integrated LDO, providing 3.3 V
- TIOL111-5: IO-Link PHY with an integrated LDO, providing 5 V
- TIOL111: IO-Link PHY without an integrated LDO

This reference design uses the 3.3-V LDO version, which is capable of providing up to a 20-mA output current. This current is sufficient to power the MCU and ADC as well as to supply the LEDs.
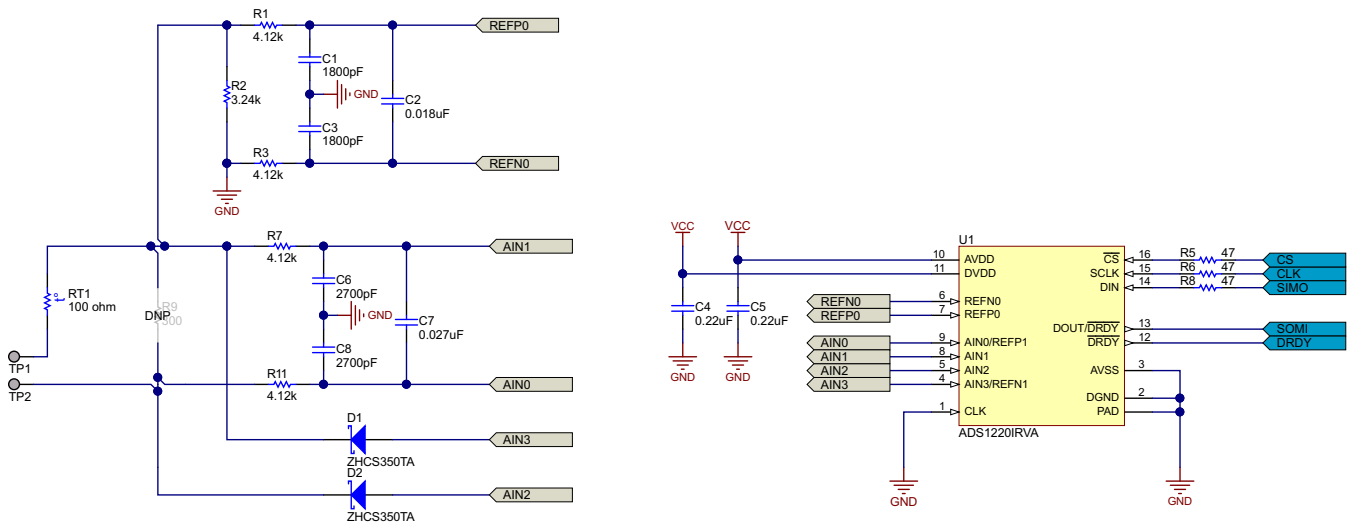
## 2.2.2 RTD Front End

The main focus of this reference design is the realization of the IO-Link interface including the IO-Link stack. To have real world sensor data to transmit using the IO-Link interface, a temperature sensor is also part of this design. The board contains a PT100 element as the temperature sensor.

For the excitation current and to measure the RTD resistance value, this reference design uses the ADS1220. With two integrated, programmable excitation current sources and a programmable PGA, the 24-bit ADC is a perfect fit in this application.



Copyright © 2017, Texas Instruments Incorporated

图 3. Analog Front-End Circuitry


图 3 shows the circuitry of the analog front end. Resistor R9 is only needed for calibration purposes. With  $R9 = 300 \Omega$ , it is used to run a gain calibration. For this purpose, the PT100 element has to be disconnected. This can be realized by removing the short between TP1 and TP2 once calibration is done or not needed. R9 has to be removed and TP1 shorted with TP2.

The excitation current from the ADS1220 is provided through the two diodes D1 and D2, developing a reference voltage across R2. This 3.24-k $\Omega$  precision resistor has a 0.1% tolerance with a temperature coefficient of 10 ppm/C and generates the reference voltage for the ADC, enabling a ratiometric measurement.
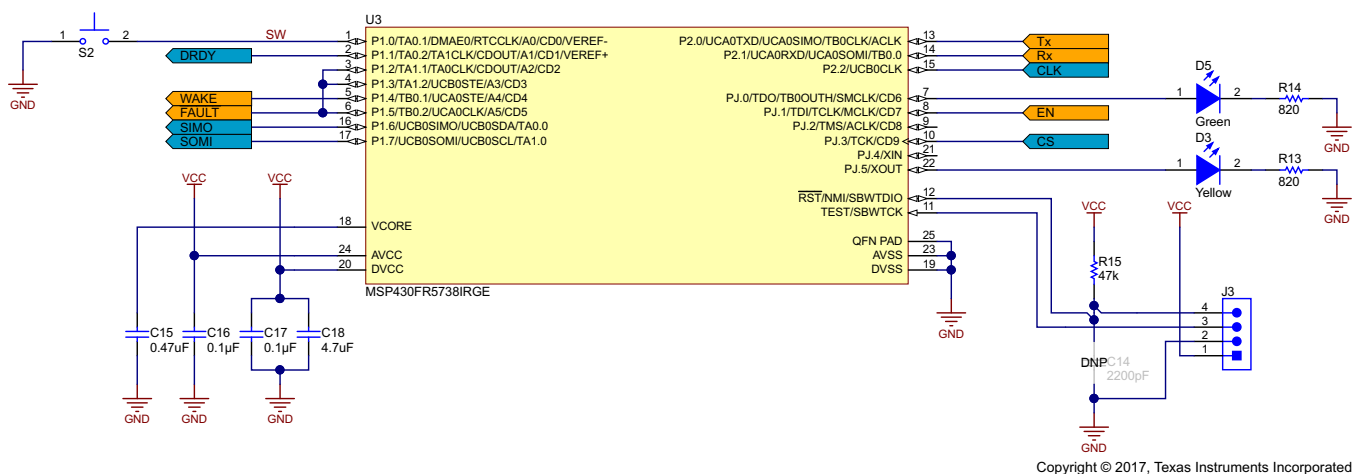
### 2.2.3 Digital Processing

For calculating the temperature, based on the measured RTD resistance, the MSP430FR5738 is part of the design. A look-up table (LUT) translates the measured voltage levels into the respective temperature values according to Calendar-Van Dusen equations. For this, the MCU gets a data set once the ADC provides the data ready (DRDY) information. Once calculated, the temperature data is transmitted through the IO-Link interface.

Also in the MSP430FR5738, the IO-Link stack is running. Once an IO-Link connection is established between the TIDA-01335 reference design and an IO-Link master, the green LED D5 is blinking. With the pushbutton S1, it is possible to set a temperature threshold. Once this threshold is reached, the information is also sent through IO-Link to the master. With the IO-Link master GUI, it is possible to read out this temperature threshold and overwrite the temperature threshold with the GUI. 图 4 shows the schematic of the digital processing section.



Copyright © 2017, Texas Instruments Incorporated

图 4. Digital Processing Section

## 2.3 Highlighted Products

The following subsections detail each circuit block in the TIDA-00559 block diagram. For more information on each of these devices, see their respective product folders at [TI.com](http://ti.com).

### 2.3.1 TIOL111: IO-Link Device Transceiver With Integrated Surge Protection


The TIOL111 family of transceivers implements the IO-Link interface for industrial bidirectional, point-to-point communication. When the device is connected to an IO-Link master through a three-wire interface, the master can initiate communication and exchange data with the remote node while the TIOL111 acts as a complete physical layer for the communication.

These devices are capable of withstanding up to 1.2 kV (500  $\Omega$ ) of IEC 61000-4-5 surge and feature integrated reverse polarity protection. A simple pin-programmable interface allows easy interfacing to the controller circuits. The output current limit can be configured using an external resistor. Fault reporting and internal protection functions are provided for undervoltage, overcurrent, and overtemperature conditions.

Key features of this device include:

- 7- to 36-V supply voltage
- PNP, NPN, or IO-Link configurable output
  - IEC 61131-9 COM1, COM2, and COM3 data rate support
- Low residual voltage of 1.75 V at 250 mA
- 50- to 350-mA configurable current limit
- Tolerant to  $\pm 65$ -V transients  $< 100 \mu\text{s}$
- Reverse polarity protection of up to 55 V on L+, CQ, and L–
- Integrated EMC protection on L+ and CQ:
  - $\pm 16$ -kV IEC 61000-4-2 ESD Contact Discharge
  - $\pm 4$ -kV IEC 61000-4-4 EFT
  - $\pm 1.2$ -kV/500- $\Omega$  IEC 61000-4-5 Surge
- Fast demagnetization of inductive loads up to 1.5 H
- Large capacitive load driving capability
- $< 2$ - $\mu\text{A}$  CQ leakage current
- $< 1.5$ -mA quiescent supply current
- Integrated LDO options for up to 20-mA current:
  - TIOL111: No LDO
  - TIOL111-3: 3.3-V LDO
  - TIOL111-5: 5-V LDO
- Overtemperature warning and thermal protection
- Remote wake-up indicator
- Fault indicator
- Extended ambient temperature:  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$
- 2.5-mm $\times$ 3-mm 10-pin VSON package



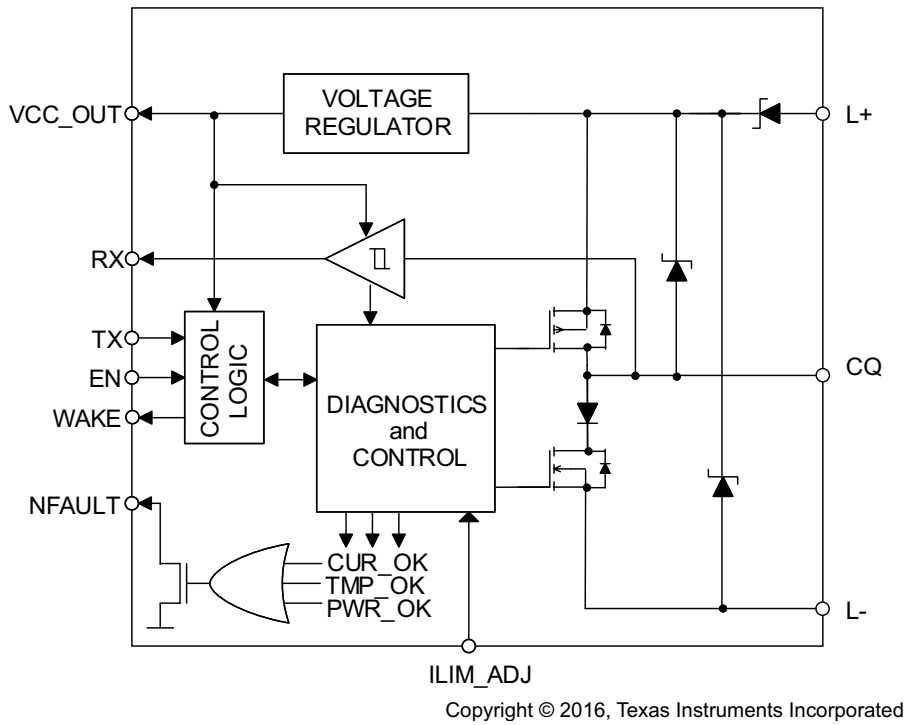

Copyright © 2016, Texas Instruments Incorporated


图 5. TIOL111-3 With 3.3-V Voltage Regulator

### 2.3.2 MSP430FR5738

The TI MSP430FR573x family of ultra-low-power microcontrollers consists of multiple devices that feature embedded FRAM nonvolatile memory, an ultra-low-power 16-bit MSP430 CPU, and different peripherals targeted for various applications. The architecture, FRAM, and peripherals, combined with seven low-power modes, are optimized to achieve extended battery life in portable and wireless sensing applications. FRAM is a new nonvolatile memory that combines the speed, flexibility, and endurance of SRAM with the stability and reliability of flash, all at lower total power consumption. Peripherals include a 10-bit ADC, a 16-channel comparator with voltage reference generation and hysteresis capabilities, three enhanced serial channels capable of I<sup>2</sup>C, SPI, or UART protocols, an internal DMA, a hardware multiplier, an RTC, five 16-bit timers, and digital I/Os.

Key features of this device include:

- Embedded MCU 16-bit RISC architecture up to 24-MHz clock:
  - Wide supply voltage range (2 to 3.6 V)
  - Optimized ultra-low-power modes (81.4  $\mu$ A/MHz in active and 320 nA in shutdown (LPM4.5))
  - Ultra-low-power ferroelectric RAM
  - 16-KB nonvolatile memory
  - Ultra-low-power writes
  - Fast write at 125 ns per word (16kB in 1 ms)
  - Built-in error coding and correction (ECC) and MPU
  - Universal memory = program + data + storage
  - 10<sup>15</sup> write cycle endurance
- Intelligent digital peripherals:
  - 32-bit hardware multiplier (MPY)
  - Three-channel internal DMA
  - RTC with calendar and alarm functions
  - 16-bit Cyclic redundancy checker (CRC)
  - High-performance analog
  - Enhanced serial communication

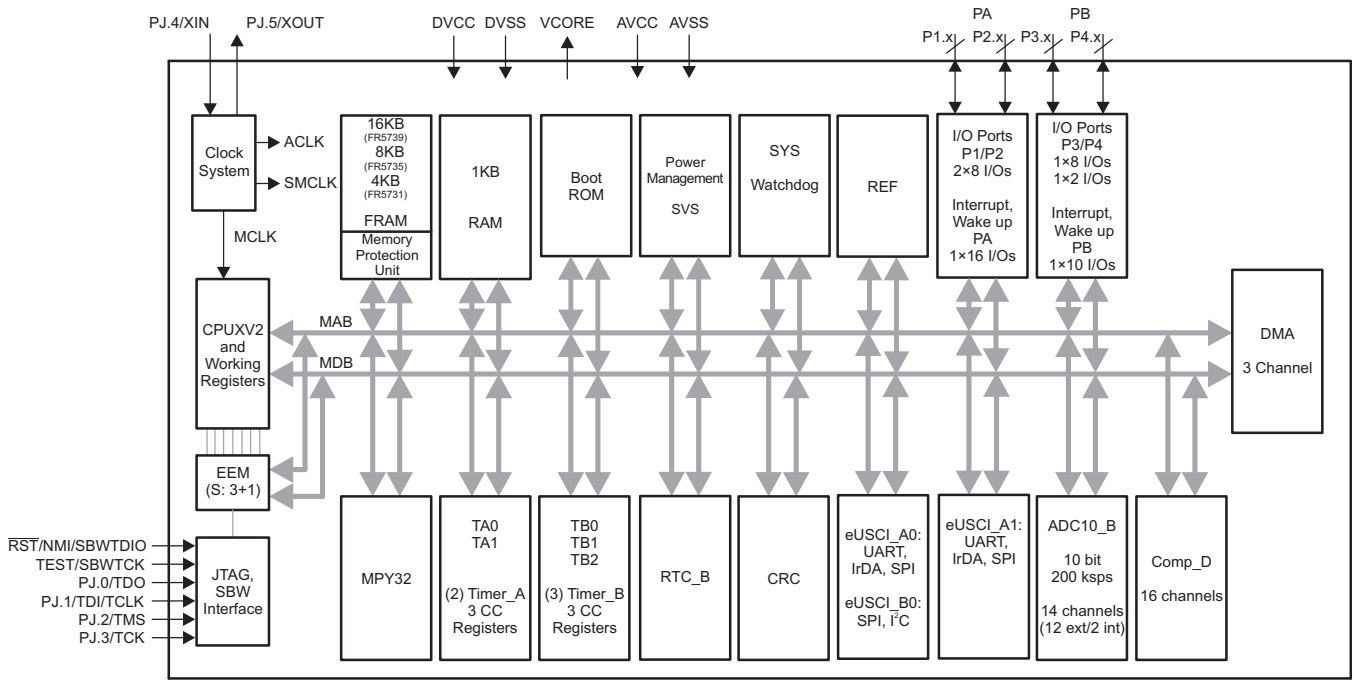

Copyright © 2016, Texas Instruments Incorporated

图 6. Functional Block Diagram MSP430FR5738

### 2.3.3 ADS1220: 24-Bit, 2kSPS, Four-Channel, Low-Power Delta-Sigma ADC With PGA and $V_{REF}$ for Small Signal Sensors


The ADS1220 is a precision, 24-bit, ADC that offers many integrated features to reduce system cost and component count in applications measuring small sensor signals. The device features two differential or four single-ended inputs through a flexible input multiplexer (MUX), a low-noise, programmable gain amplifier (PGA), two programmable excitation current sources, a voltage reference, an oscillator, a low-side switch, and a precision temperature sensor.

The device can perform conversions at data rates up to 2000 samples-per-second (SPS) with single-cycle settling. At 20 SPS, the digital filter offers simultaneous 50-Hz and 60-Hz rejection for noisy industrial applications. The internal PGA offers gains up to 128 V/V. This PGA makes the ADS1220 ideally-suited for applications measuring small sensor signals, such as RTDs, thermocouples, thermistors, and resistive bridge sensors. The device supports measurements of pseudo- or fully-differential signals when using the PGA. Alternatively, the device can be configured to bypass the internal PGA while still providing high input impedance and gains up to 4 V/V, allowing for single-ended measurements.

Power consumption is as low as 120  $\mu$ A when operating in duty-cycle mode with the PGA disabled. The ADS1220 is offered in a leadless VQFN-16 or a TSSOP-16 package and is specified over a temperature range of  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$ .

Key features of this device include:

- Low current consumption:
  - Duty-cycle mode: 120  $\mu$ A
  - Normal mode: 415  $\mu$ A
- Wide supply range: 2.3 to 5.5 V
- Programmable gain: 1 to 128 V/V
- Programmable data rates: up to 2 kSPS
- Simultaneous 50-Hz and 60-Hz rejection at 20 SPS with a single-cycle settling digital filter
- Low-noise PGA: 90 nV<sub>RMS</sub> at 20 SPS
- Dual-matched programmable current-sources: 10 to 1500  $\mu$ A
- Internal 2.048-V reference: 5 ppm/ $^{\circ}\text{C}$  (typical) drift
- Internal oscillator: 2% (maximum) accuracy
- Internal temperature sensor
- Two differential or four single-ended inputs
- SPI-compatible interface
- Package: 3.5 mm  $\times$  3.5 mm  $\times$  0.9 mm QFN

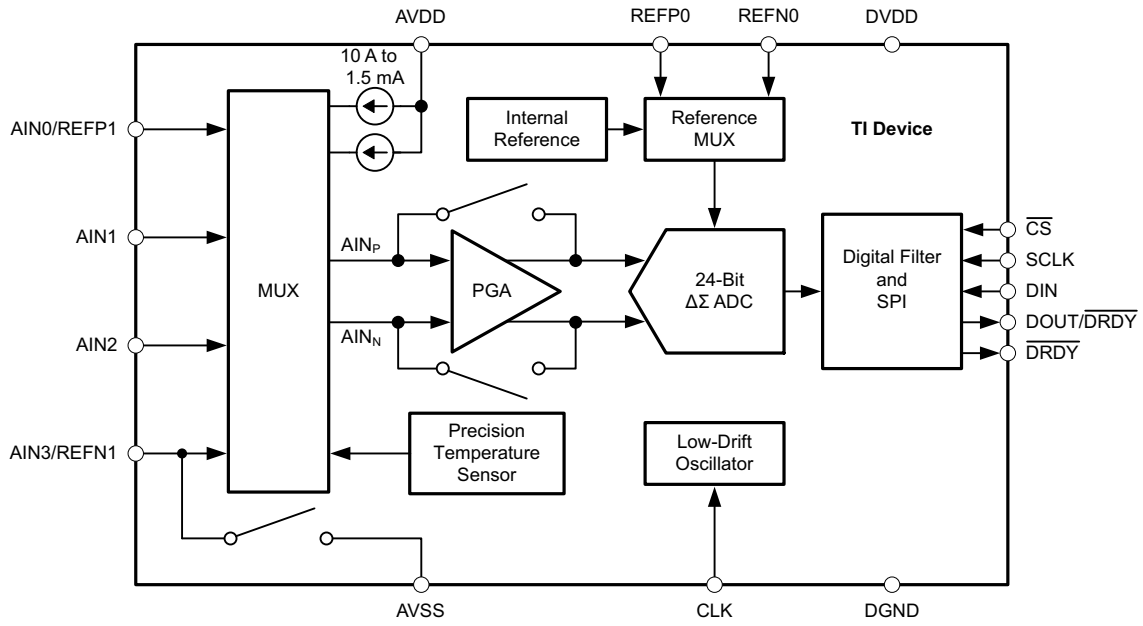


Copyright © 2016, Texas Instruments Incorporated

图 7. Functional Block Diagram of ADS1220
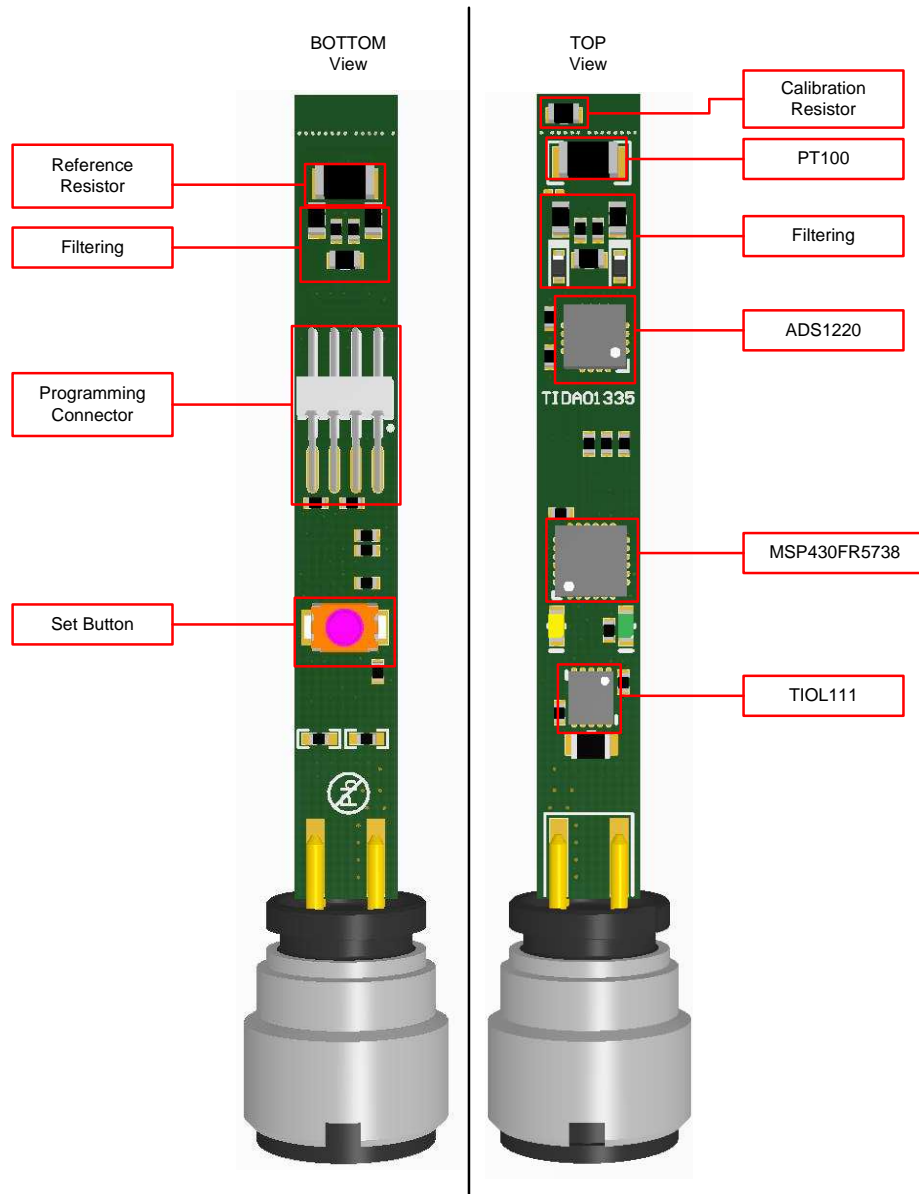
### 3 Hardware, Software, Testing Requirements, and Test Results

In 图 8, the different building blocks of TIDA-01335 are highlighted.




Copyright © 2017, Texas Instruments Incorporated

图 8. TIDA-01335 Board Description


In the bottom view:

- Reference resistor (see 图 9): The resistor R2 is a precise reference resistor. The excitation current develops a voltage across R2, which is used as a reference voltage for the ADC. This approach allows for a ratiometric measurement. It is important to have a stable resistor because the resistor value of the RTD is a ratio to R2. In this reference design, R2 has a tolerance of 0.1% with a temperature coefficient of 10ppm/C.
- Filtering (see 图 9)
- Programming connector (see 图 10)
- Set button: When pressing this button, the current temperature is used as a temperature threshold. The value can also be read out using IO-Link.

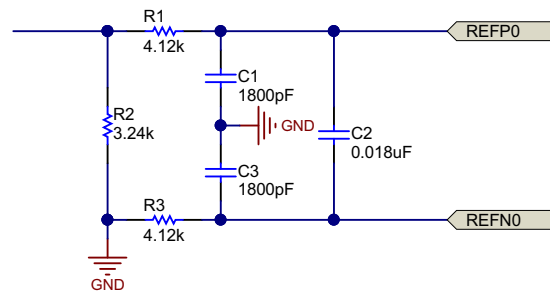

Copyright © 2017, Texas Instruments Incorporated

图 9. Reference Resistor and Filtering

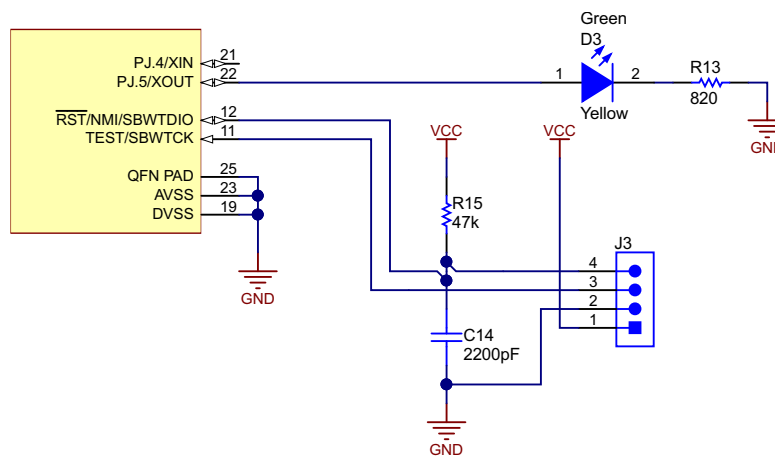

Copyright © 2017, Texas Instruments Incorporated

图 10. Programming Connector

In the top view:

- Calibration resistor: Resistor R9 is not populated per default. The resistor can be used for gain calibration of the ADC.
- PT100: The PT100 is the temperature sensing element.
- ADS1220: ADC to capture the voltage across the RTD
- MSP430FR5738: The MCU calculates the temperature based on the voltage across the RTD and the look-up table. The MSP430 also has the IO-Link stack for the IO-Link communication.

- TIOL111: This is the IO-Link PHY



### 3.1 Required Hardware and Software

To get the TIDA-01335 reference design up and running, the following hardware and software is needed:

- TIDA-01335 reference design
- IO-Link master:
  - Example: TMG USB IO-Link Master V2
  - Software for IO-Link master
- M12 cable to connect the reference design and IO-Link master
- MSP430 programmer
  - Example: [MSP-FET](#)
- PC
- IO-Link stack
- IO-Link IODD files
- Optional:
  - Precision reference resistor for calibrating the analog front end
  - Precision digital multimeter (DMM)

### 3.2 Testing and Results

#### 3.2.1 Test Setup

图 11 shows how to connect the reference design. The MSP-FET is only required for programming or debugging the MSP430. The M12 cable connects the reference design with the IO-Link master, which is also connected through USB to the PC. The PC has the IO-Link master software installed. For details on the installation of the GUI, see the user manual of the IO-Link master software.

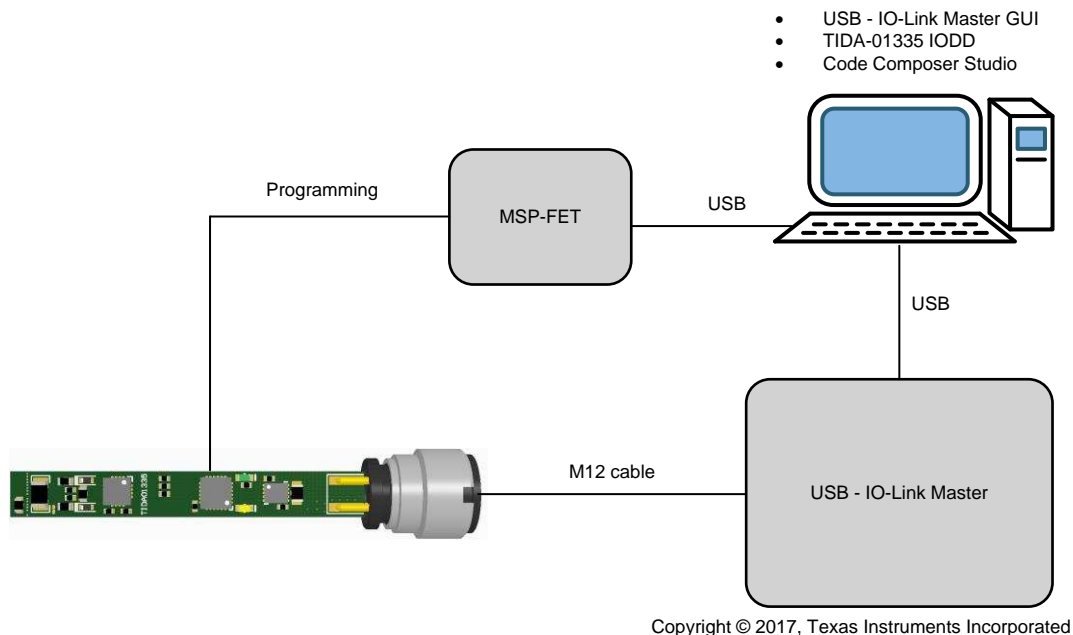


图 11. Test Setup of Reference Design

### 3.2.2 Test Results

图 12 through 图 18 show the different steps to configure the IO-Link master GUI. Note that these steps are only valid for the IO-Link master used here. When the reference design is connected as per 图 11, launch the GUI and follow these steps:

1. Click the "Search Master" button (see 图 12).
2. Double-click in the pop-up window on the IO-Link master, which is connected to the system. Typically, this is only one entry as long as only one IO-Link master is connected to the PC (see 图 13).
3. Drag the "TIDA-01335" IODD file and drop it in the "IO-Link" row. See the manual on how to load the specific IODD files (see 图 14).
4. Go to the Vendor and Device information in the IO-Link row. Click on the "Go Online" button to establish a connection between the PC and the IO-Link master. If successful, the color of the button turns green (see 图 15).
5. Double-click in the "Topology" window on "TI Design TIDA-01335" to open the details of this reference design (see 图 16).
6. The green button in the upper left corner indicates a proper connection between the IO-Link master and IO-Link device (see 图 17).
7. By clicking on the "Process Data" tab, the information of the reference design are shown. For this design, the temperature of the RTD sensor is shown, as well as the threshold of the low and high temperature limits (see 图 18).

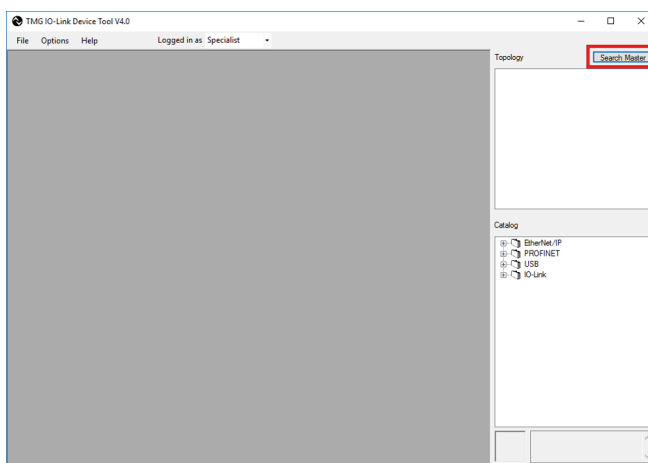


图 12. IO-Link Master GUI 1

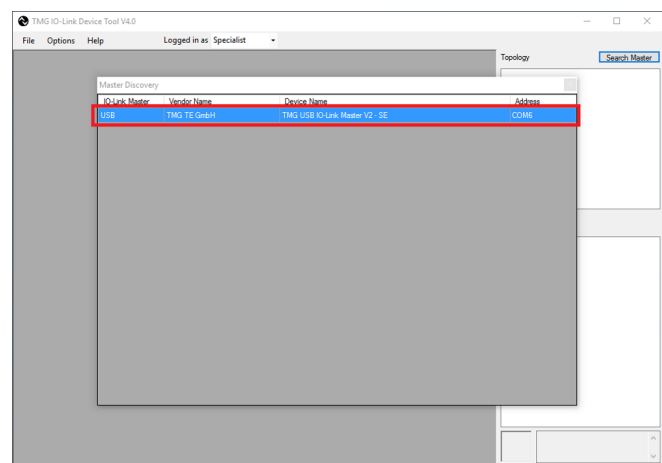


图 13. IO-Link Master GUI 2

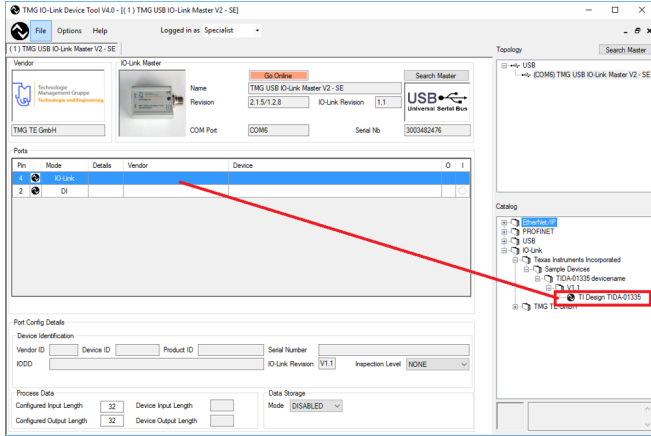


图 14. IO-Link Master GUI 3

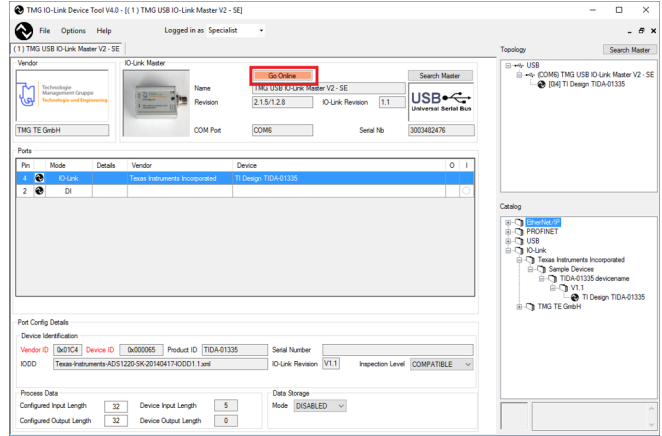


图 15. IO-Link Master GUI 4

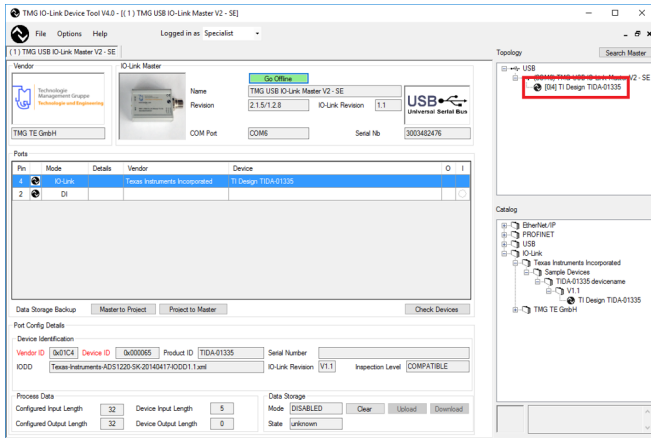


图 16. IO-Link Master GUI 5

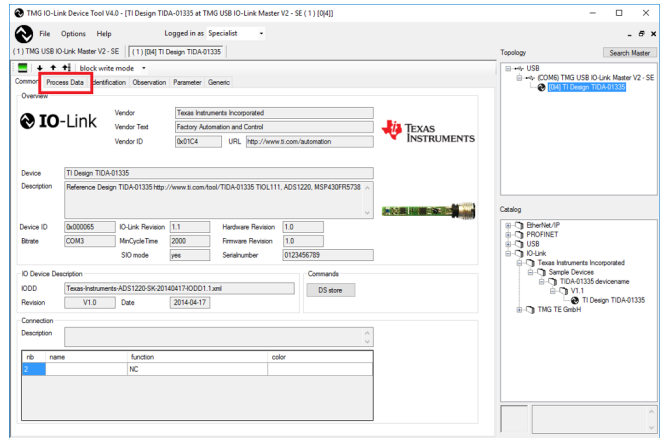


图 17. IO-Link Master GUI 6

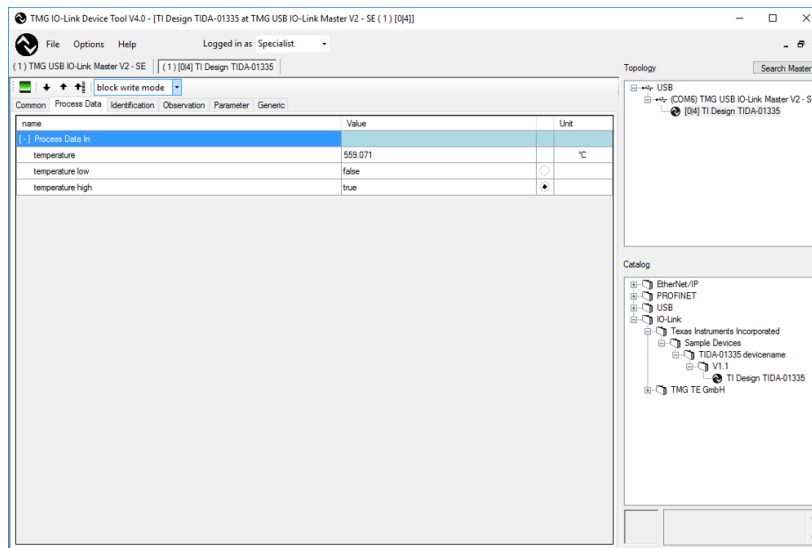


图 18. IO-Link Master GUI 7

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-01335](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01335](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01335](#).

### 4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01335](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01335](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01335](#).

## 5 Software Files

To download the software files, see the design files at [TIDA-01335](#).

## 6 Related Documentation

This design did not use any documentation.

### 6.1 商标

MSP430 is a trademark of Texas Instruments.

All other trademarks are the property of their respective owners.

## 7 About the Author

**ALEXANDER WEILER** is a systems engineer at Texas Instruments, where he is responsible for developing reference design solutions for the industrial segment. Alexander brings to this role his extensive experience in high-speed digital, low-noise analog, and RF system-level design expertise. Alexander earned his diploma in electrical engineering (Dipl.-Ing.(FH)) from the University of Applied Science in Karlsruhe, Germany.

## 有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。您就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等产权包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默示的保证或陈述，包括但不限于对准确性或完整性、产权保证、无复发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、[评估模块](http://www.ti.com/sc/docs/sampters.htm)和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122  
Copyright © 2017 德州仪器半导体技术（上海）有限公司