

Product Overview

Voltage Translating Gates



Hannah Bludau, Albert Xu

Systems that require logic gates can have mismatched logic voltage levels resulting in the need for a voltage translating gate to enable communication between devices. For example, a singular LVxT device can be used instead of both a translator and gate, resulting in a decrease of board space and easier integration.

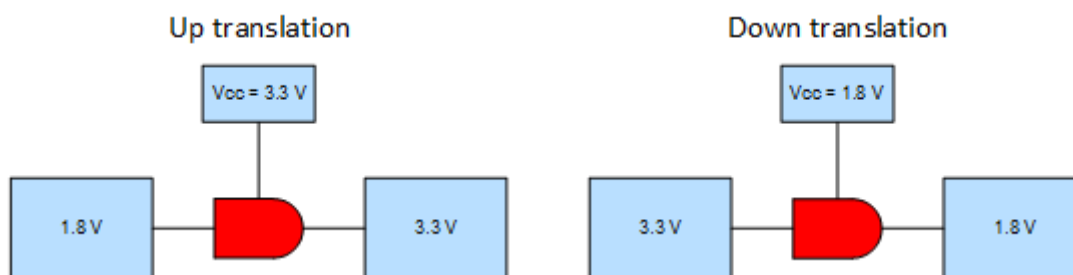


Figure 1. Voltage Translation Using an AND Gate

Left: block diagram for up translation Right: block diagram for down translation

Design Considerations

- Voltage translation is capable of performing both up and down translation with a single supply
- Ability to reduce the number of parts for qualification and assembly
- Board design is streamlined by obtaining the functionality of two devices in one
- Wide voltage range support systems with varied levels of logic coexisting including 1.8V, 2.5V, 3.3V and 5.0V
- For traces longer than 12cm (4760 mil), see [Drive Transmission Lines With Logic](#)
- [\[FAQ\] How does a slow or floating input affect a CMOS device?](#)
- [\[FAQ\] Where do I find maximum power dissipation for a device?](#)
- Ask a question on TI's [E2E™](#) forums

Recommended Parts

Part Number	AEC-Q100	V _{CC} Range	Channels	Features
SN74AUP1T02		2.3V to 3.6V	1	Single 2-input Schmitt-trigger NOR gate
SN74AUP1T08		2.3V to 3.6V	1	Single 2-input Schmitt-trigger AND gate
SN74AUP1T32		2.3V to 3.6V	1	Single 2-input Schmitt-trigger OR gate
SN74LV1T08		1.65V to 5.5V	1	Single 2-input AND gate
SN74LV1T08-Q1	✓			
SN74LV1T32		1.65V to 5.5V	1	Single 2-input OR gate
SN74LV1T32-Q1	✓			
SN74LV4T08		1.65V to 5.5V	4	Quad 2-input AND gates
SN74LV4T08-Q1	✓			
SN74LV4T00				
SN74LV4T00-Q1	✓	1.65V to 5.5V	4	Quad 2-input NAND gates

For more devices, browse through the [online parametric tool](#) where you can sort by desired voltage, channel numbers, and other features.

Trademarks

E2E™ is a trademark of Texas Instruments.

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated