

# Realizing Low-power and High-scalability OBC Wake-up Design with MSPM0 MCU

---



## Introduction

Electric vehicles are becoming more and more popular. On-board chargers (OBC) are important to charge the vehicle battery safely and smartly. Most of the time, OBC is in sleep mode. The OBC wakes up and functions after detecting signals from the charging gun. Based on the GB/T 18487.1-2015 standard, there are two types of required signals for AC charging gun detection. The CC signal determines the connection status between the OBC and the charging gun, and the CP signal determines the valid voltage and duty cycle status of the AC power supply.


To detect the CC and CP signals, determine the normal status, and wake up the host MCU to control the charging process, some designs leverage discrete designs with transistors, resistors and capacitors. However, it can be difficult to make changes for different project requirements and can require different PCB sizes. Now, a user can leverage a MSPM0 MCU to design a lower-power and higher-scalability integrated OBC wake-up design.



Figure 1. OBC Charging Gun

## Why build an integrated design with MSPM0?


- Low power: MSPM0 supports less than 1µA of standby current.
- High scalability: satisfies different requirements of wake-up delay time, condition, and source with flexible software design compared to fixed discrete hardware design.

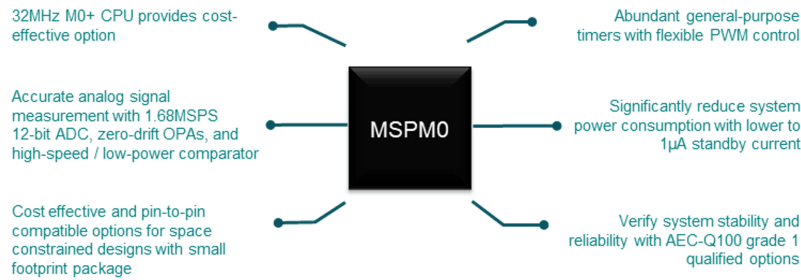

**Figure 2. MSPM0L Series Overview**

## What can MSPM0 do in an OBC wake-up design?

- Detect the resistance value of the CC port to check the connection status between the OBC and the charging gun by using an ADC or comparator module.
  - 12-bit SAR ADC with 11.2ENOB and 1.68MSPS sampling rate.
  - Two mode (low power and high speed) comparator with an 8-bit reference DAC.
- Detect the voltage and duty cycle values of the CP port to find the valid wake-up status by using ADC and timer modules.
  - Four 16-bit timers that support low-power operation in standby mode.
- Enable the LDO for the host MCU and wake the MCU up to control the charging process by using a GPIO.
- More functions such as controlling PWM indicators, and conducting protocol translations with multiple enhanced communication interfaces.
  - Two UART interfaces that support low-power operation in standby mode.
  - Two I2C interfaces that support wakeup from stop mode.
  - One SPI supports up to 16Mbit/s.

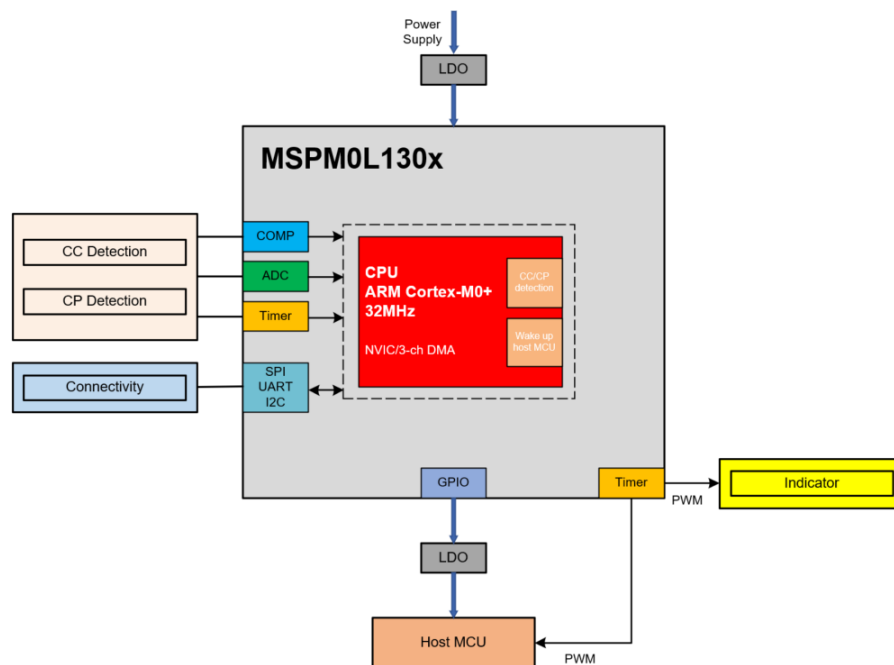

**Figure 3. Block Diagram of OBC Wake-up Design Based on MSPM0L130x**

## Resources

Order a low-cost development kit [LP-MSPM0L1306](#) to start designing an integrated OBC wake-up design. Jump-start coding with a [MSPM0-SDK](#) software development kit and the [SysConfig](#) graphical code generation tool. The following links show additional MSPM0 resources.

- Texas Instruments, [MSPM0 overview page](#), product page.
- Texas Instruments, [MSPM0L130x-Q1 Automotive Mixed-Signal Microcontrollers](#), data sheet.
- Texas Instruments, [MSPM0 L-Series 32-MHz Microcontrollers Technical Reference Manual](#), technical reference manual.
- Texas Instruments, [MSPM0 L-Series Hardware Development Guide](#), application note.
- Texas Instruments, [MSPM0 Academy](#), training.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated