

User's Guide

# LMZ21700 and LMZ21701 Power Module Evaluation Module User's Guide



## Table of Contents

1 Introduction.....	2
2 Board Specifications.....	2
3 Schematic, Bill of Materials, and PCB Layout.....	3
4 Typical Performance.....	6
5 Revision History.....	8

### Trademarks

SIMPLE SWITCHER® is a registered trademark of Texas Instruments.  
All trademarks are the property of their respective owners.

## 1 Introduction

The LMZ21701 and LMZ21700 SIMPLE SWITCHER® nano modules are easy-to-use DC-DC solutions optimized for space constrained applications. The LMZ21701 is capable of driving up to 1-A load with excellent power conversion efficiency, output voltage accuracy, line and load regulation, and load transient response. The LMZ21700 is a 650-mA load current version module, pin-to-pin compatible with the LMZ21701. The evaluation board is configured for 3.3-V output voltage from 5-V to 17-V input. The resistor voltage dividers,  $R_{FBT}$  and  $R_{FBB}$ , set the output voltage. The external capacitor  $C_{SS}$  sets the soft-start time for  $V_{OUT}$ . See the [LMZ21701 1-A Nano Module With 17-V Maximum Input Voltage](#) or [LMZ21700 650-mA Nano Module With 17-V Maximum Input Voltage](#) data sheets for component selection and device details. The board features turret terminals for easy connection to input supply, load, EN input, as well as soft start voltage and power-good flag monitoring.

## 2 Board Specifications

- $V_{IN}$  = 5 V to 17 V
- $V_{OUT}$  = 3.3 V
- 1-A max load (LMZ21701)
- 650-mA max load (LMZ21700)
- 4-layer PCB
- 4.2-cm × 4.2-cm PCB size

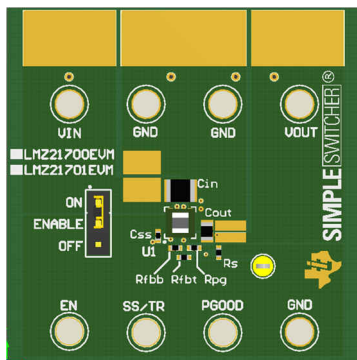


Figure 2-1. Board Top View

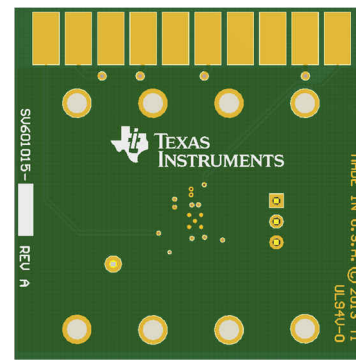


Figure 2-2. Board Top View

### 3 Schematic, Bill of Materials, and PCB Layout

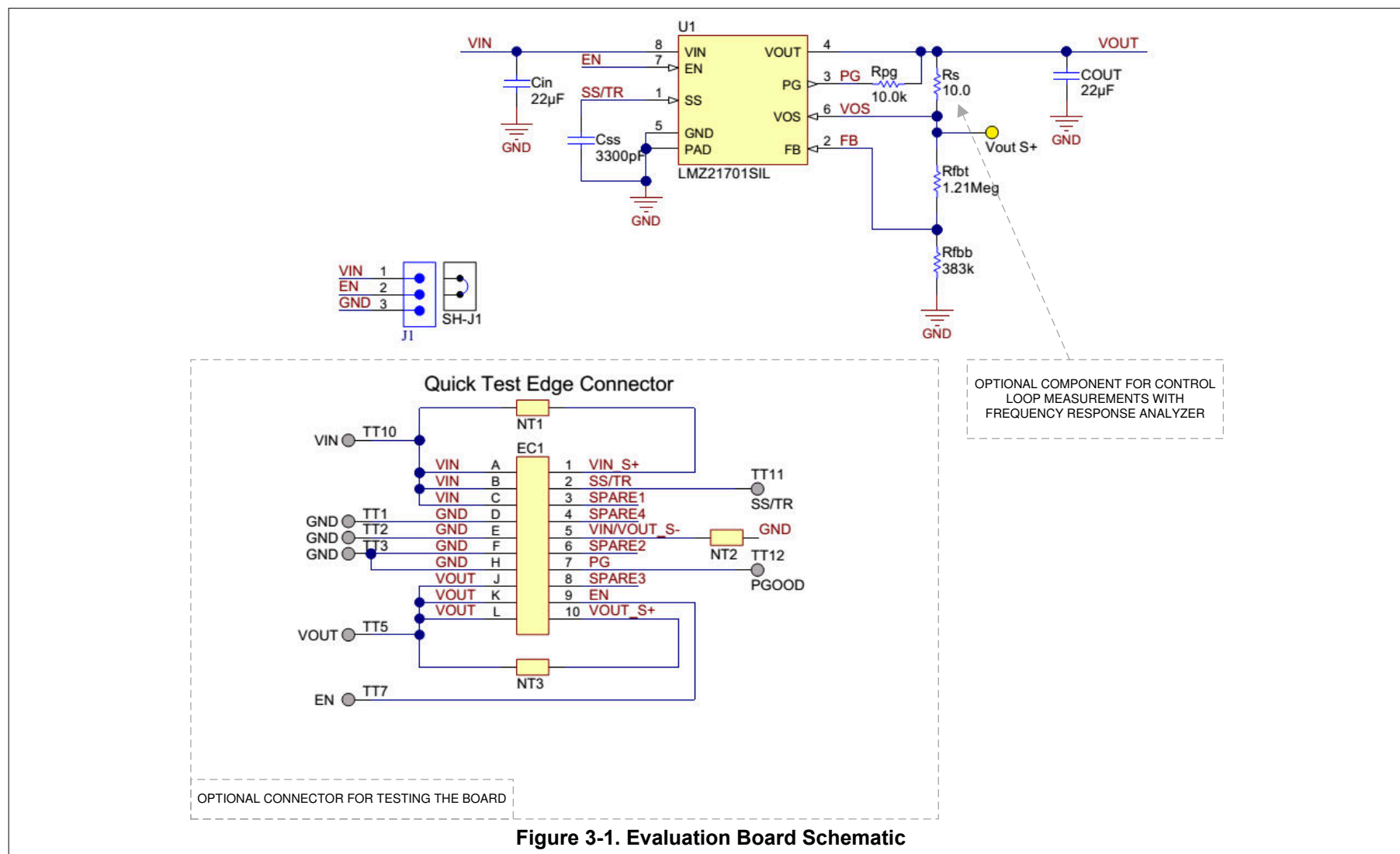



Figure 3-1. Evaluation Board Schematic


Table 3-1. Bill of Materials,  $V_{IN} = 5\text{ V to }17\text{ V}$ ,  $V_{OUT} = 3.3\text{ V}$ ,  
 $I_{OUT (MAX)} = 1000\text{ mA (LMZ21701), }650\text{ mA (LMZ21700)}$

Designator	Description	Case Size	Manufacturer	Manufacturer P/N	Quantity
U1	SIMPLE SWITCHER Nano Module	SIL0008E	Texas Instruments	LMZ21701SIL / LMZ21700SIL	1


**Table 3-1. Bill of Materials,  $V_{IN} = 5\text{ V}$  to  $17\text{ V}$ ,  $V_{OUT} = 3.3\text{ V}$ ,  
 $I_{OUT (MAX)} = 1000\text{ mA}$  (LMZ21701),  $650\text{ mA}$  (LMZ21700) (continued)**

Designator	Description	Case Size	Manufacturer	Manufacturer P/N	Quantity
C <sub>IN</sub>	CAP, CERM, 22 $\mu\text{F}$ , 25 V, $\pm 10\%$ , X7R	1210	MuRata	GRM32ER71E226KE15L	1
C <sub>OUT</sub>	CAP, CERM, 22 $\mu\text{F}$ , 10 V, $\pm 20\%$ , X5R	0805	Taiyo Yuden	LMK212BJ226MG-T	1
C <sub>SS</sub>	CAP, CERM, 3300 pF, 50 V, $\pm 10\%$ , X7R	0402	MuRata	GRM155R71H332KA01D	1
J1	Header, TH, 100 mil, 1x3, Gold plated		Samtec, Inc	TSW-103-07-G-S	1
R <sub>fb</sub>	RES, 383 k $\Omega$ , 1%, 0.063 W	0402	Vishay-Dale	CRCW0402383KFKED	1
R <sub>fbt</sub>	RES, 1.21 M $\Omega$ , 1%, 0.063 W	0402	Vishay-Dale	CRCW04021M21FKED	1
R <sub>pg</sub>	RES, 10.0 k $\Omega$ , 1%, 0.063 W	0402	Vishay-Dale	CRCW040210K0FKED	1
R <sub>s</sub>	RES, 10.0 $\Omega$ , 1%, 0.063 W	0402	Vishay-Dale	CRCW040210R0FKED	1
SH-J1	Shunt, 100 mil, Gold plated, Black		Samtec, Inc	SNT-100-BK-G	1
TT1-12	Terminal, Turret, TH, Double		Keystone Electronics	1502-2	8
Vout S+	Test Point, TH, Miniature, Yellow		Keystone Electronics	5004	1

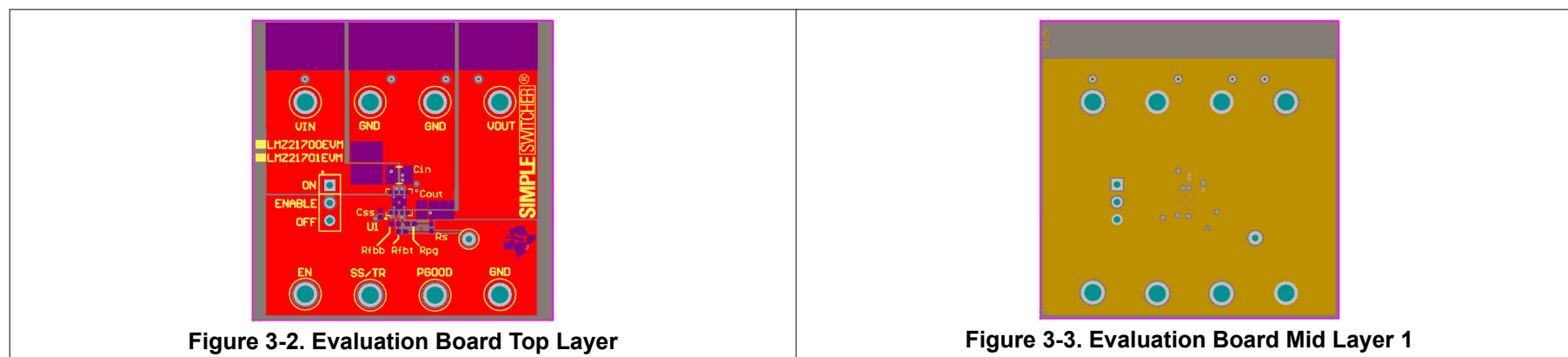

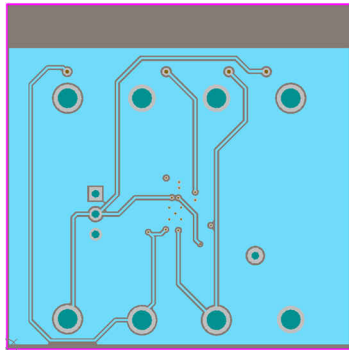

**Figure 3-4. Evaluation Board Mid Layer 2**

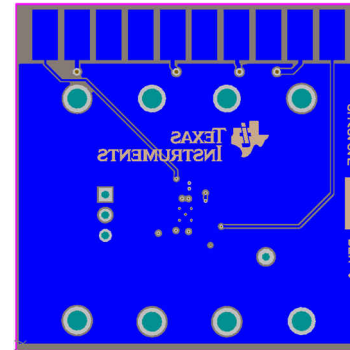

**Figure 3-5. Evaluation Board Bottom Layer**

## 4 Typical Performance

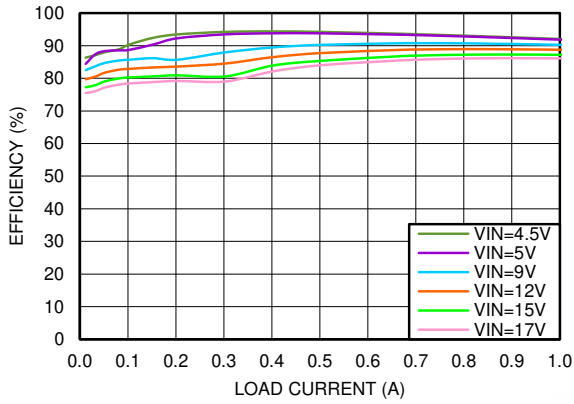


Figure 4-1. Efficiency

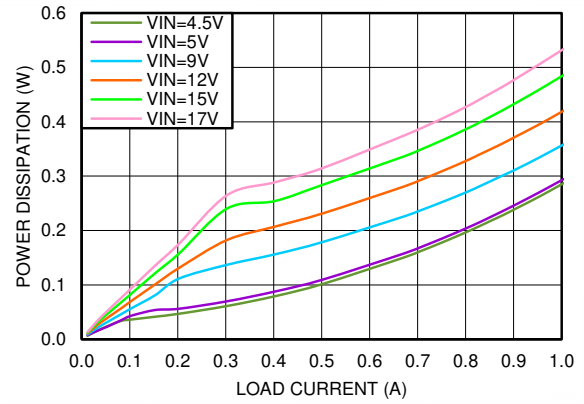


Figure 4-2. Power Dissipation

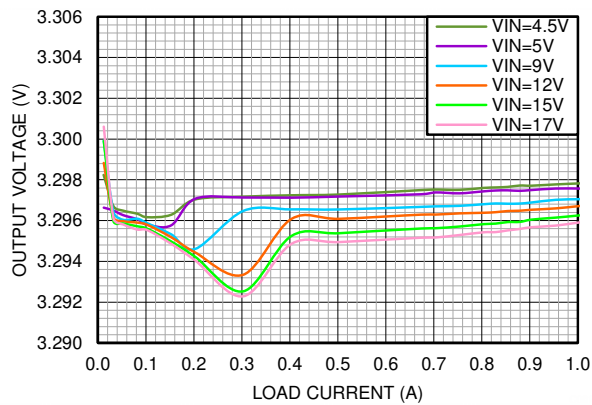


Figure 4-3. Line and Load Regulation

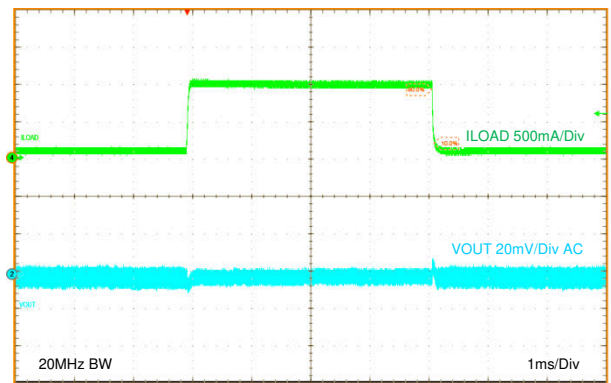


Figure 4-4. Load Transient

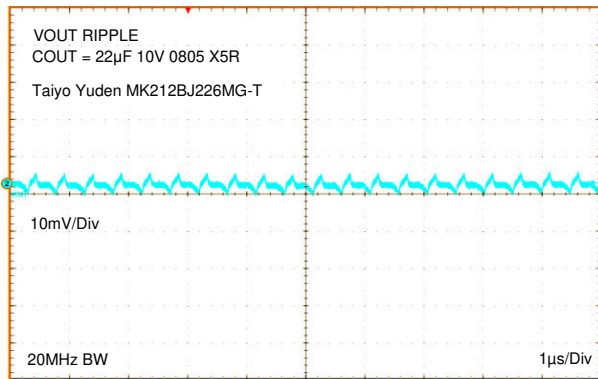


Figure 4-5. Output Voltage Ripple (20-MHz Scope BW)

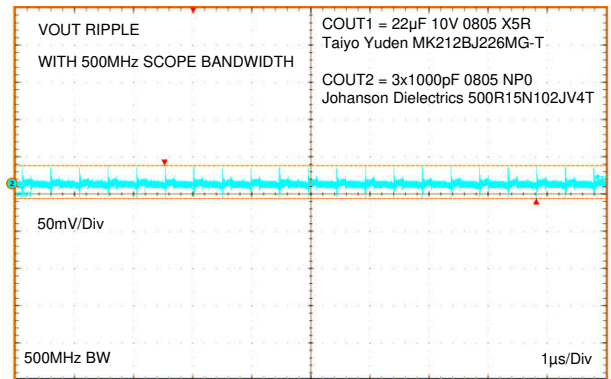


Figure 4-6. Output Voltage Ripple and HF Noise (500-MHz Scope BW)

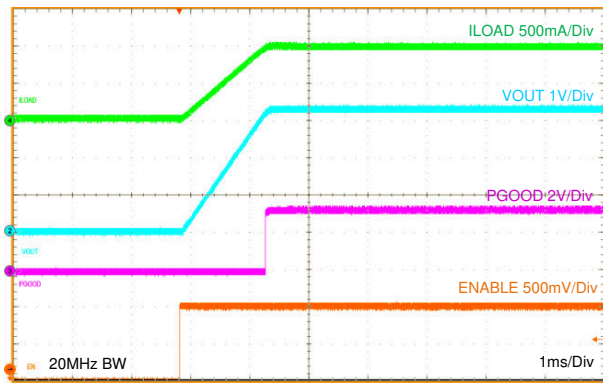


Figure 4-7. Start-Up

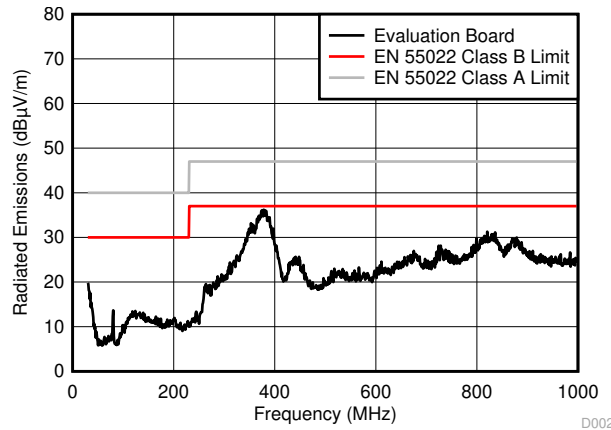


Figure 4-8. LMZ21700 Radiated EMI (Default BOM),  $V_{IN} = 12\text{ V}$ ,  $V_{OUT} = 3.3\text{ V}$ ,  $I_{OUT} = 650\text{ mA}$

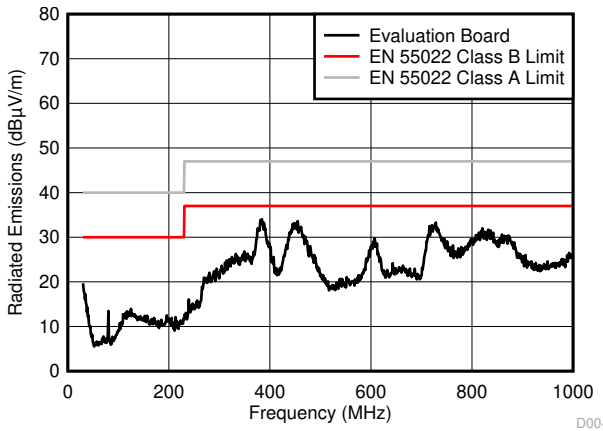


Figure 4-9. LMZ21701 Radiated EMI (Default BOM),  $V_{IN} = 12\text{ V}$ ,  $V_{OUT} = 3.3\text{ V}$ ,  $I_{OUT} = 1000\text{ mA}$

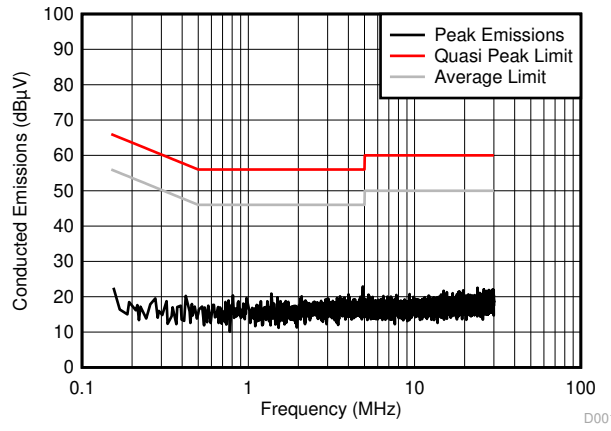


Figure 4-10. LMZ21700 Conducted EMI (1  $\mu\text{F}$ , 2.2  $\mu\text{H}$  Input Filter),  $V_{IN} = 12\text{ V}$ ,  $V_{OUT} = 3.3\text{ V}$ ,  $I_{OUT} = 650\text{ mA}$

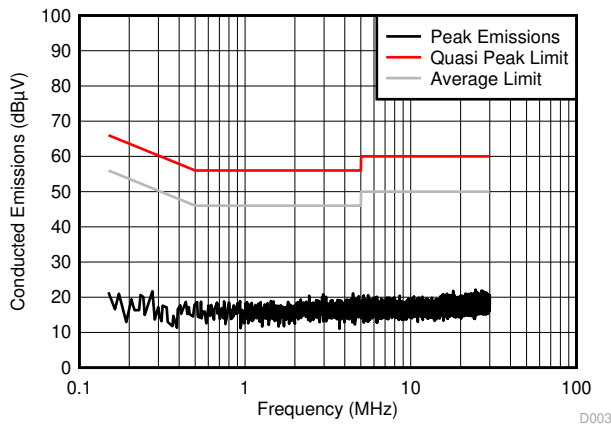


Figure 4-11. LMZ21701 Conducted EMI (1  $\mu\text{F}$ , 2.2  $\mu\text{H}$  Additional Input Filter),  $V_{IN} = 12\text{ V}$ ,  $V_{OUT} = 3.3\text{ V}$ ,  $I_{OUT} = 1000\text{ mA}$

## 5 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Revision A (October 2014) to Revision B (January 2022)</b>	<b>Page</b>
• Updated the numbering format for tables, figures, and cross-references throughout the document. ....	2
• Updated the user's guide title .....	2
<hr/>	
<b>Changes from Revision * (April 2014) to Revision A (October 2014)</b>	<b>Page</b>
• Added SVA cleanup and editing.....	6

---



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated