

10-VDC to 30-VDC Input PSR Flyback Converter With Dual-Output Reference Design



1 Description

This reference design provides two isolated voltages (6 V at 200 mA, 12 V at 200 mA) from a DC input supply (10 V–30 V). By means of 0- Ω resistors, a flexible transformer can be configured to change the turns ratio and output voltages without any layout change. The converter enables an isolated DC/DC solution with high density and low component count. No auxiliary transformer winding is required and a 100-V rated primary-side switch is integrated.

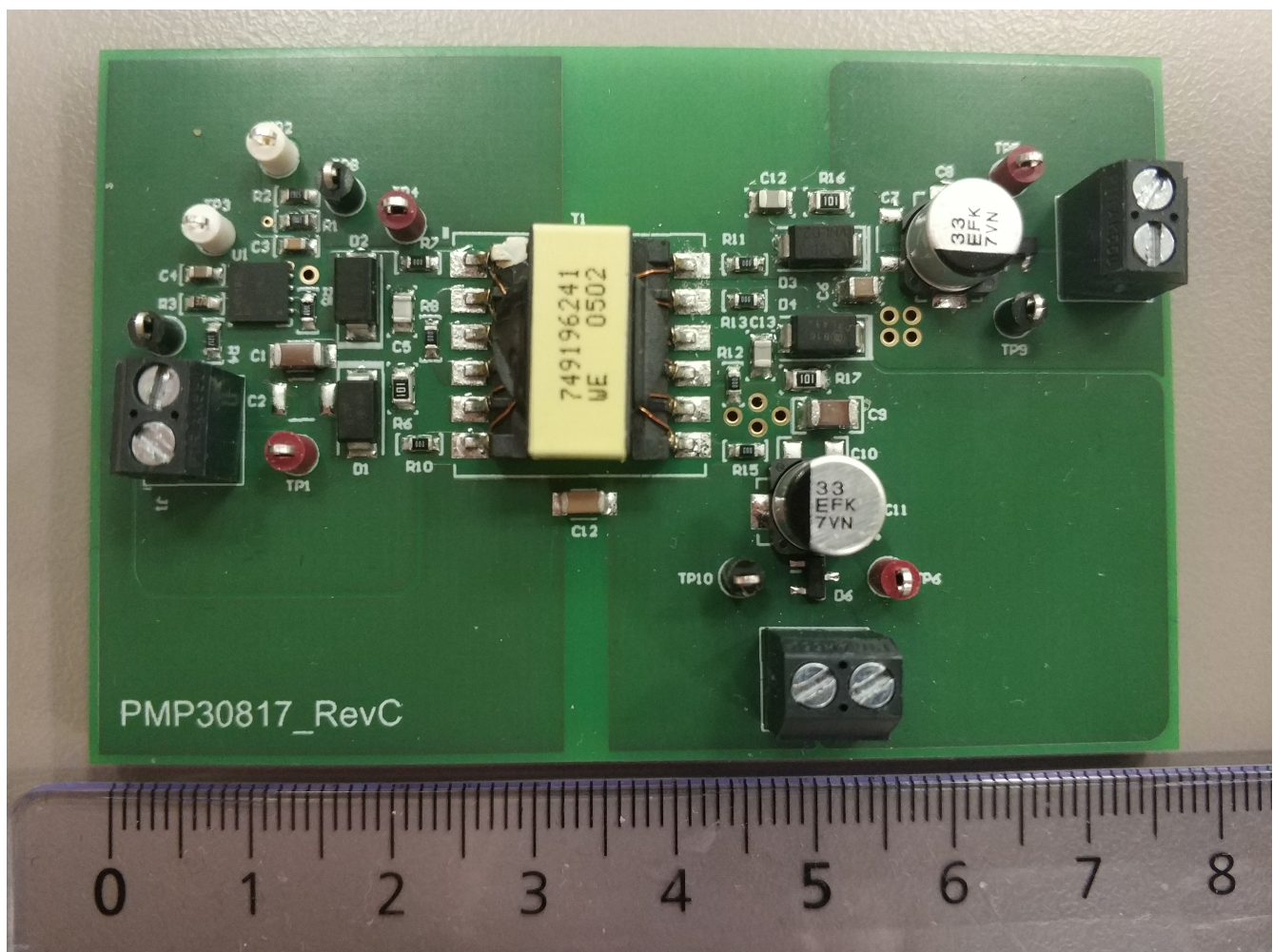


Figure 1-1. PMP30817_RevC Board Top

2 Testing and Results

2.1 Efficiency Graphs

Efficiency is shown in the following figure.

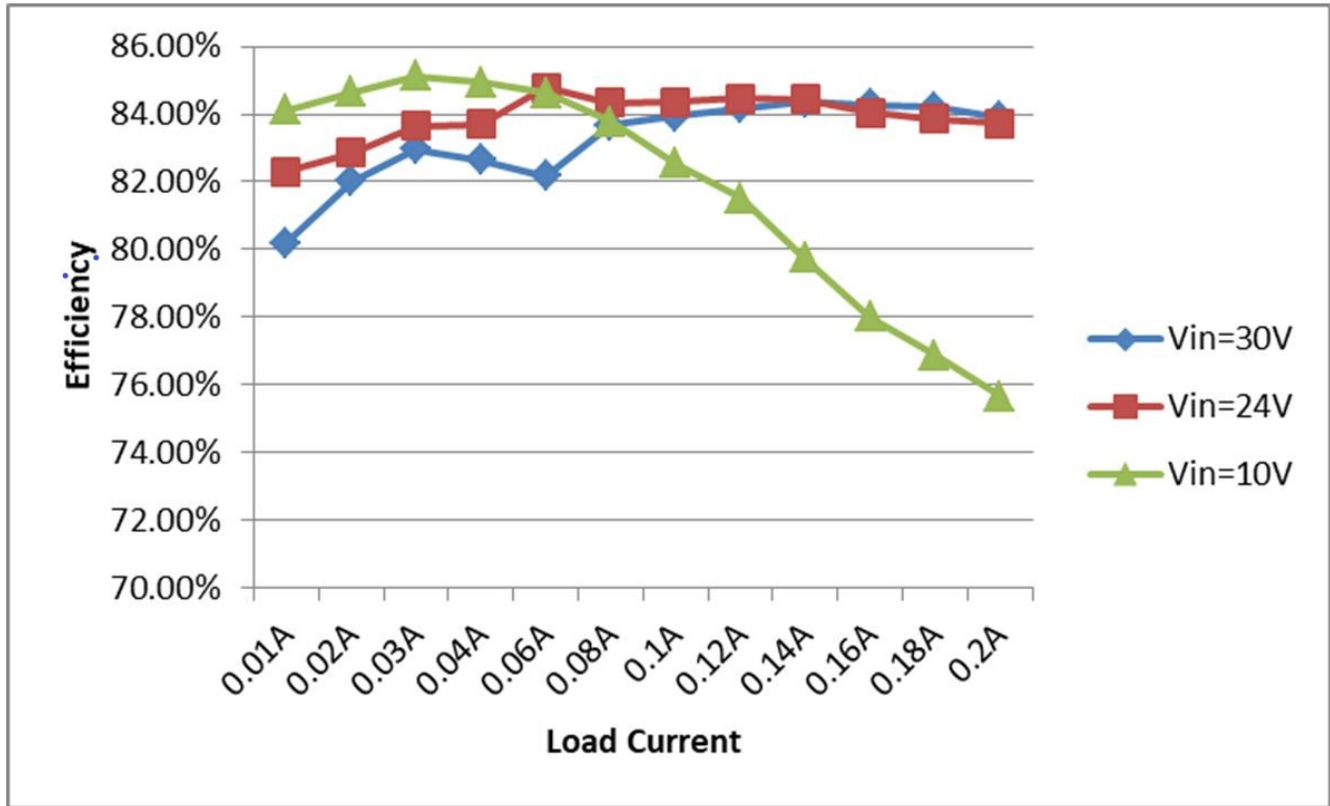


Figure 2-1. Efficiency Graph

2.2 Load Regulation

The load regulations of the two outputs is shown in the following figures.

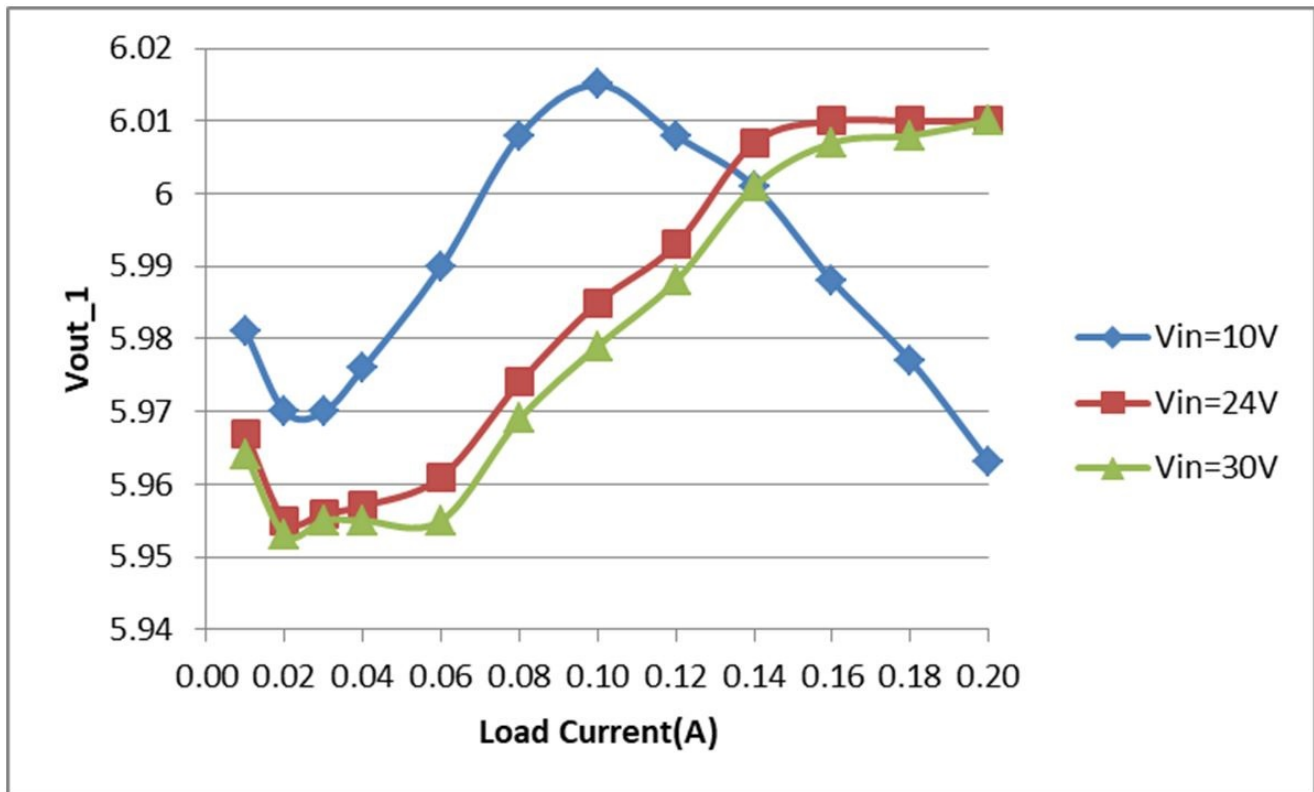


Figure 2-2. Load Regulation Output1

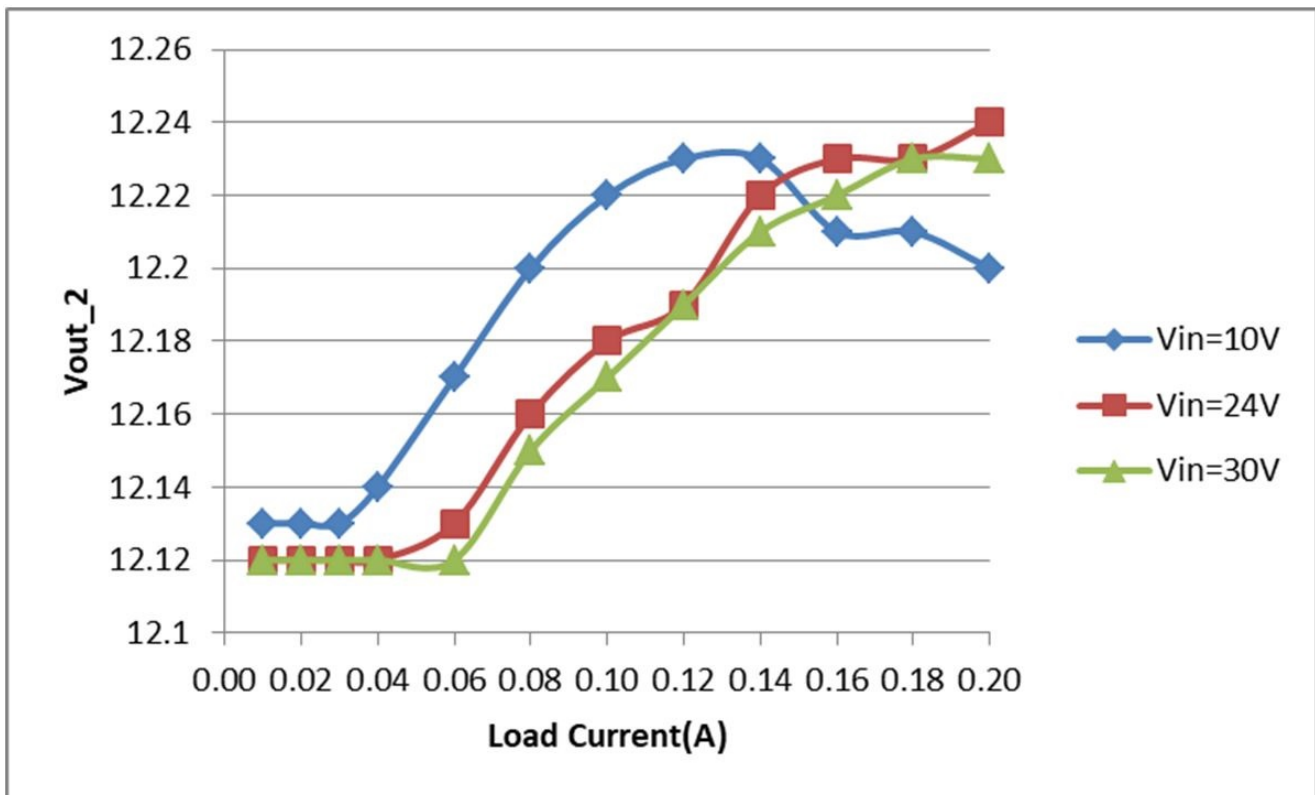


Figure 2-3. Load Regulation Output2

2.3 Thermal Image

The thermal image is shown in the following figure.

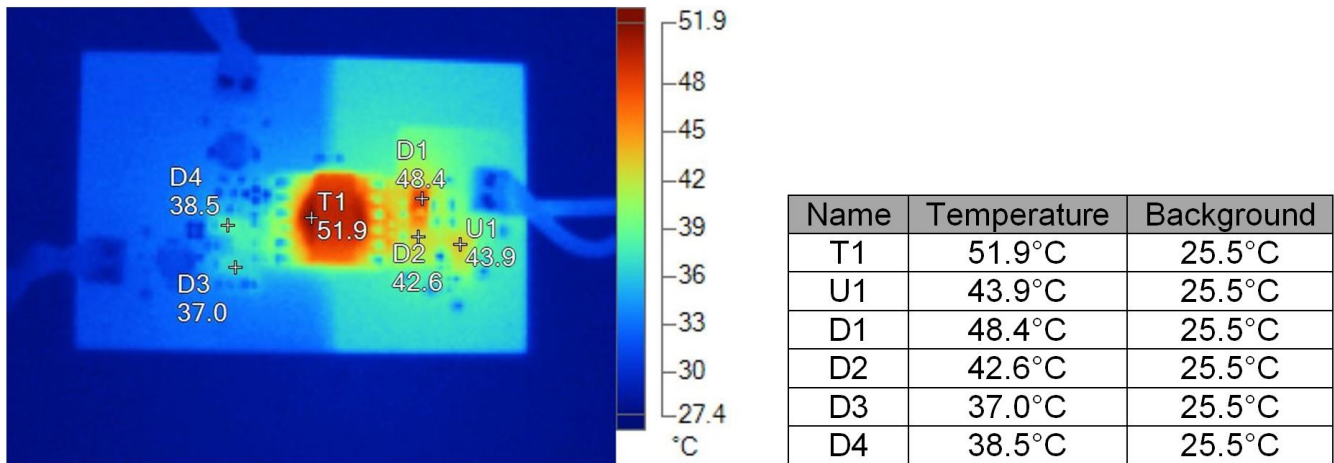


Figure 2-4. Input Voltage = 10 V; Load Current = Full Load

3 Waveforms

3.1 Switch Node Voltage

Switching behavior is shown in the following figures.

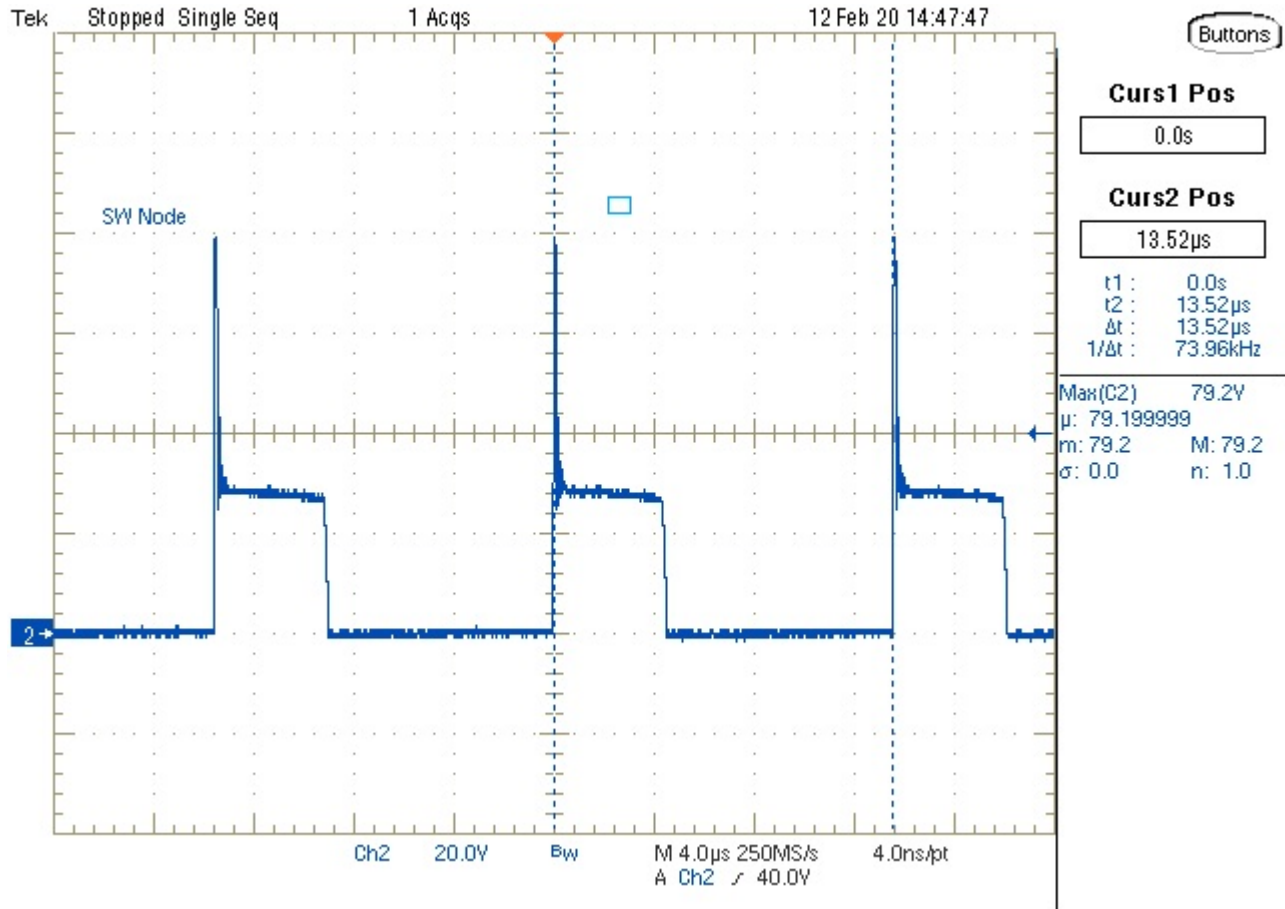


Figure 3-1. Input Voltage = 10 V; Load Current = Full Load

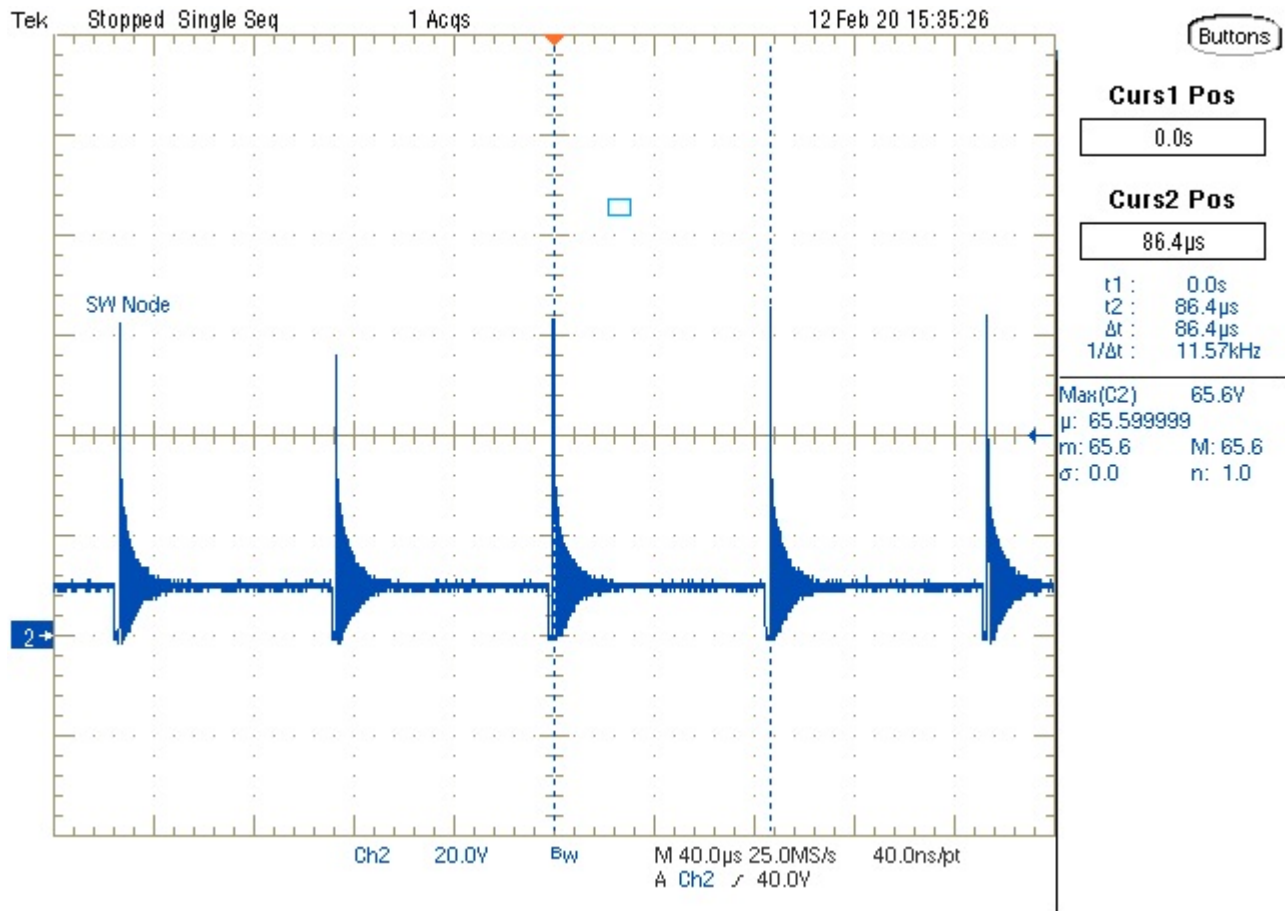


Figure 3-2. Input Voltage = 10 V; Load Current = No Load

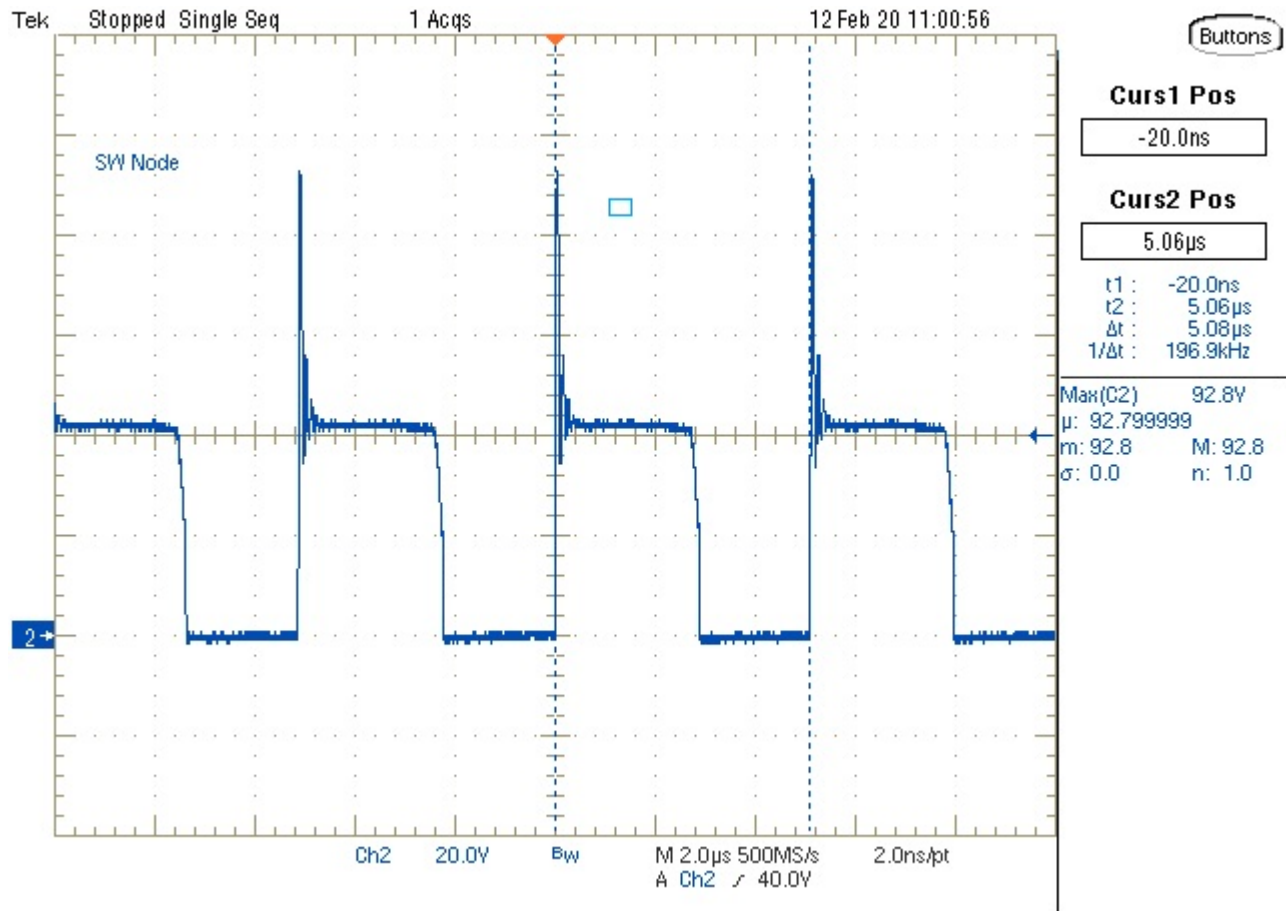


Figure 3-3. Input Voltage = 24 V; Load Current = Full Load

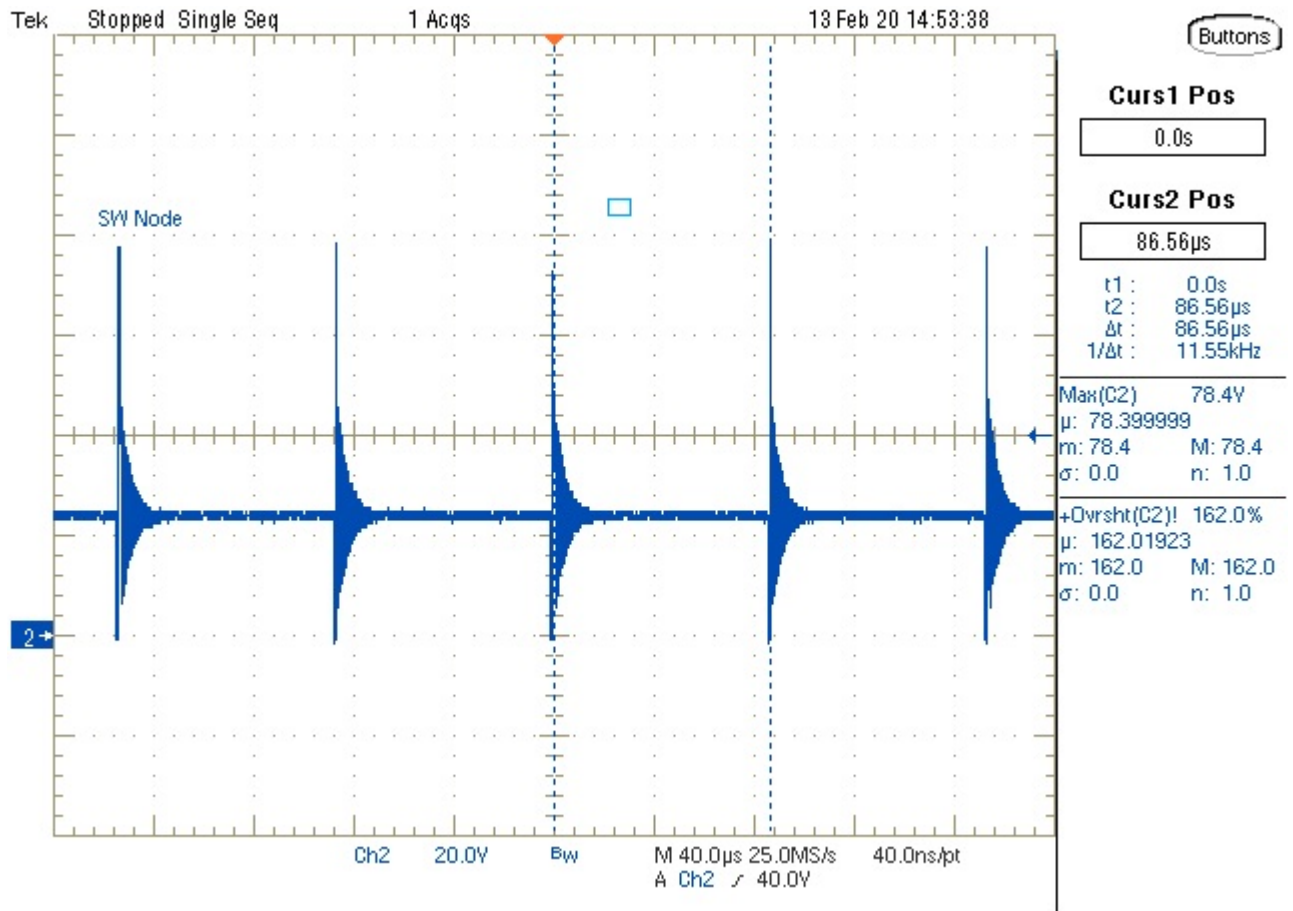


Figure 3-4. Input Voltage = 24 V; Load Current = No Load

3.2 Output Voltage Ripple

Output voltage ripple is shown in the following figures.

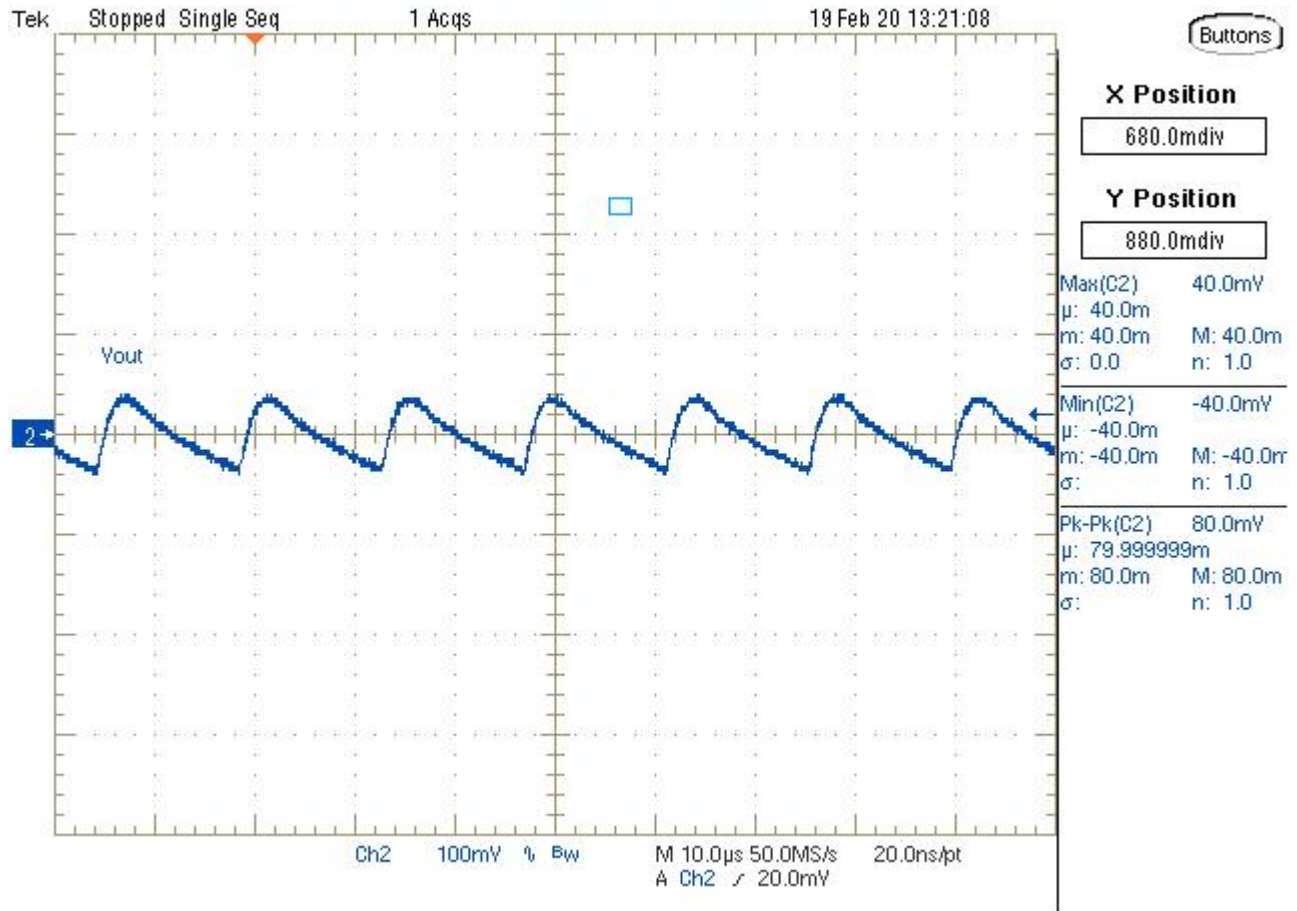


Figure 3-5. Output1: Input Voltage = 10 V; Load Current = Full Load

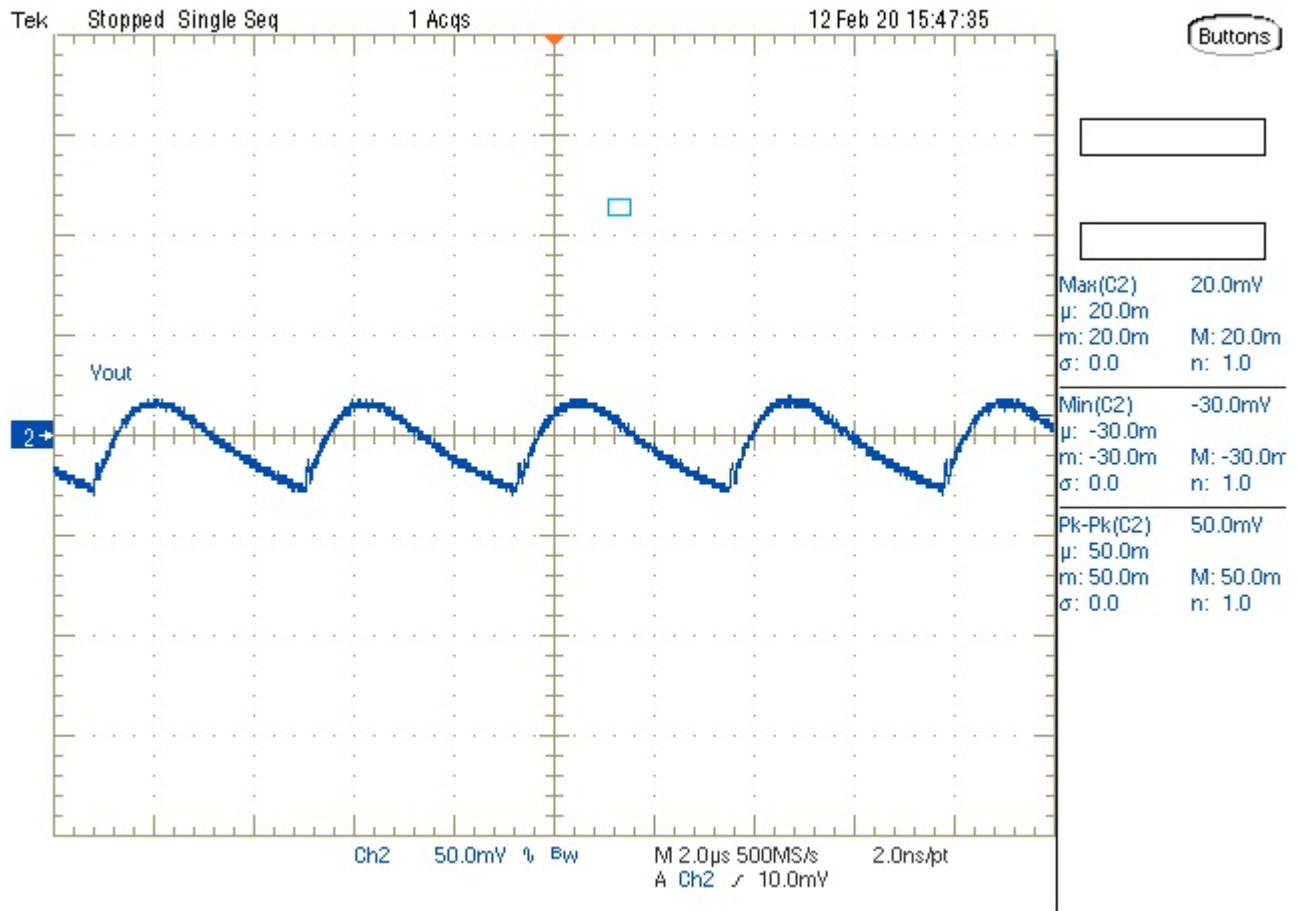


Figure 3-6. Output1: Input Voltage = 30 V; Load Current = Full Load

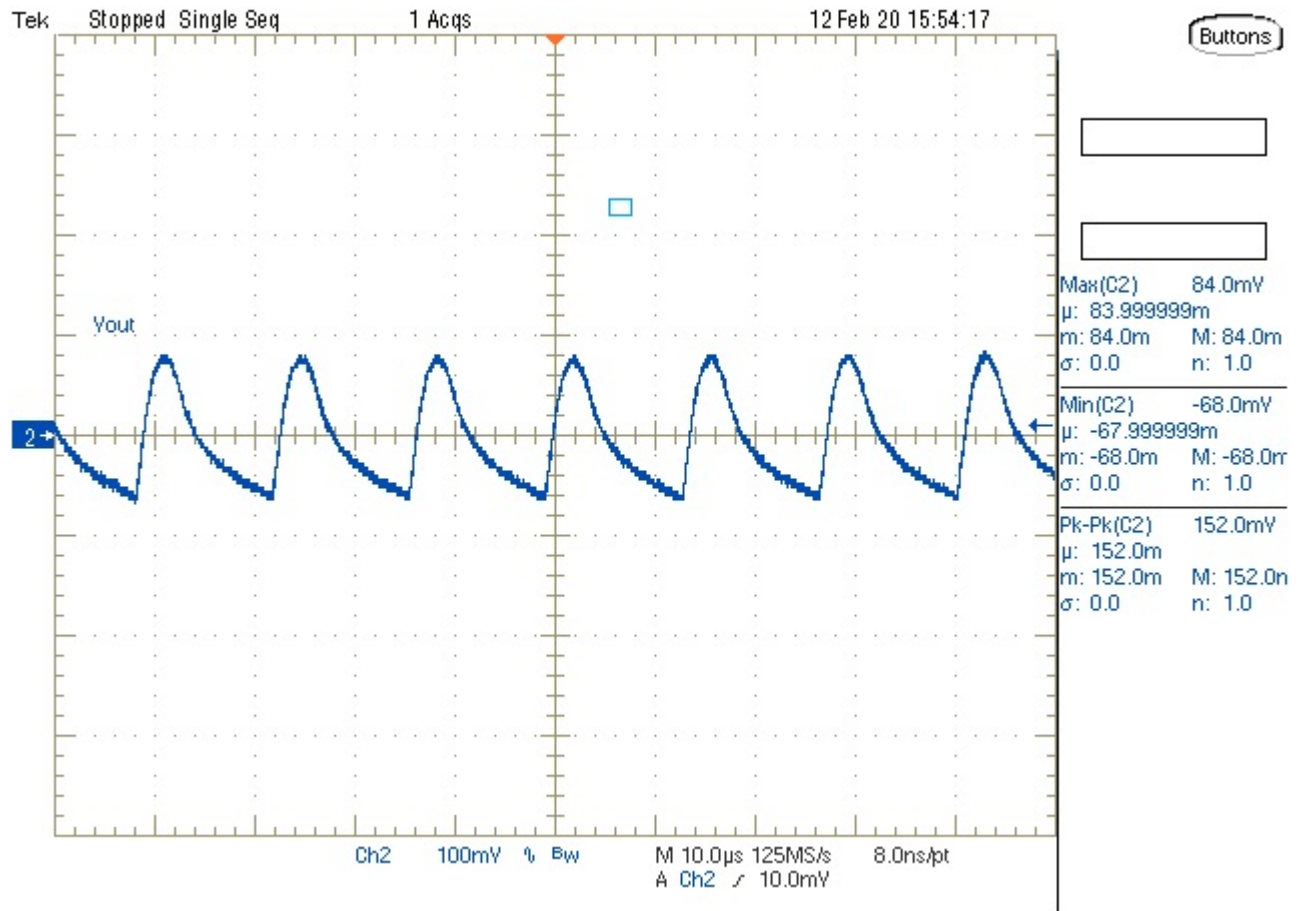


Figure 3-7. Output2: Input Voltage = 10 V; Load Current = Full Load

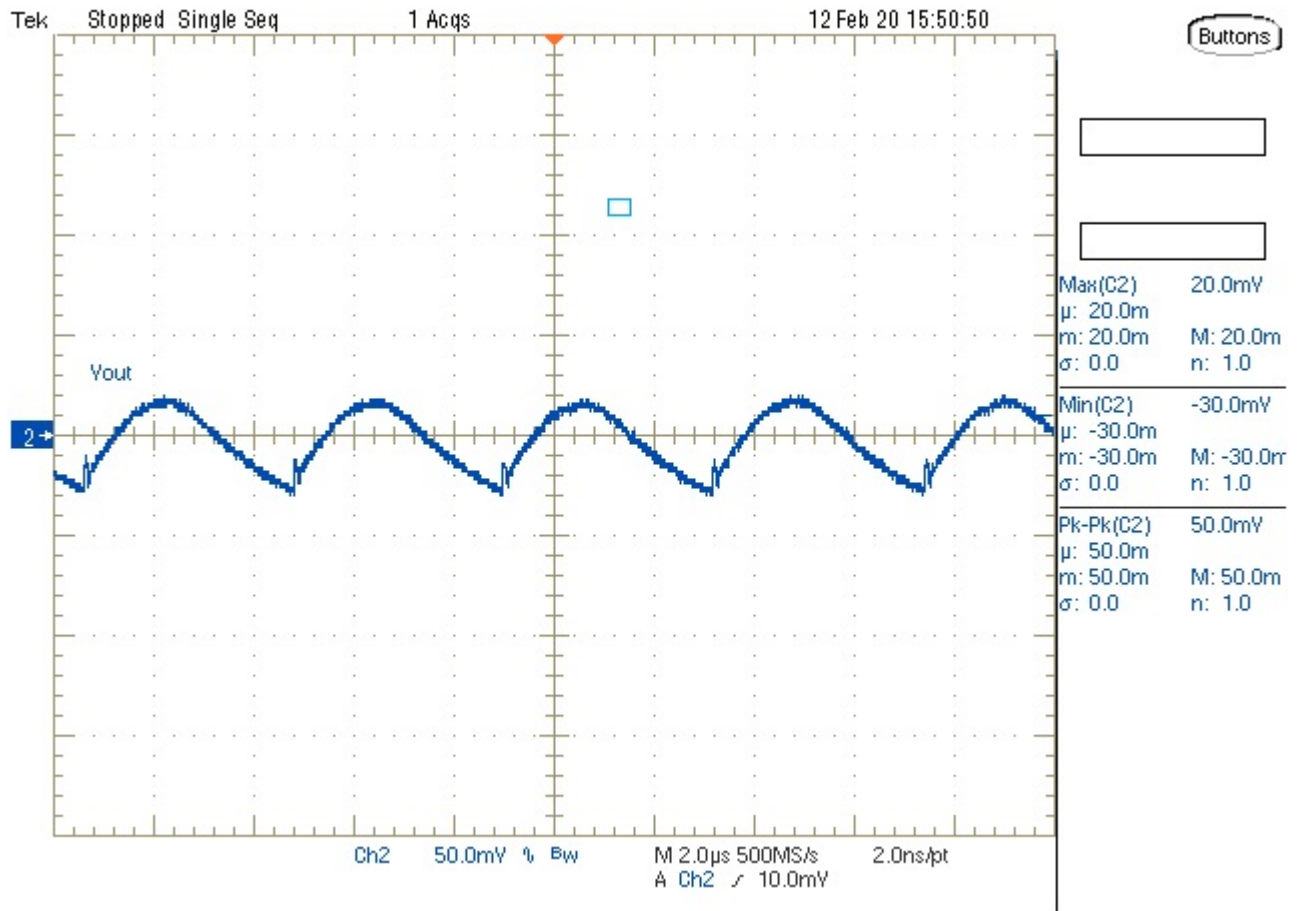


Figure 3-8. Output2: Input Voltage = 30 V; Load Current = Full Load

3.3 Load Transients

Load transient response is shown in the following figures.

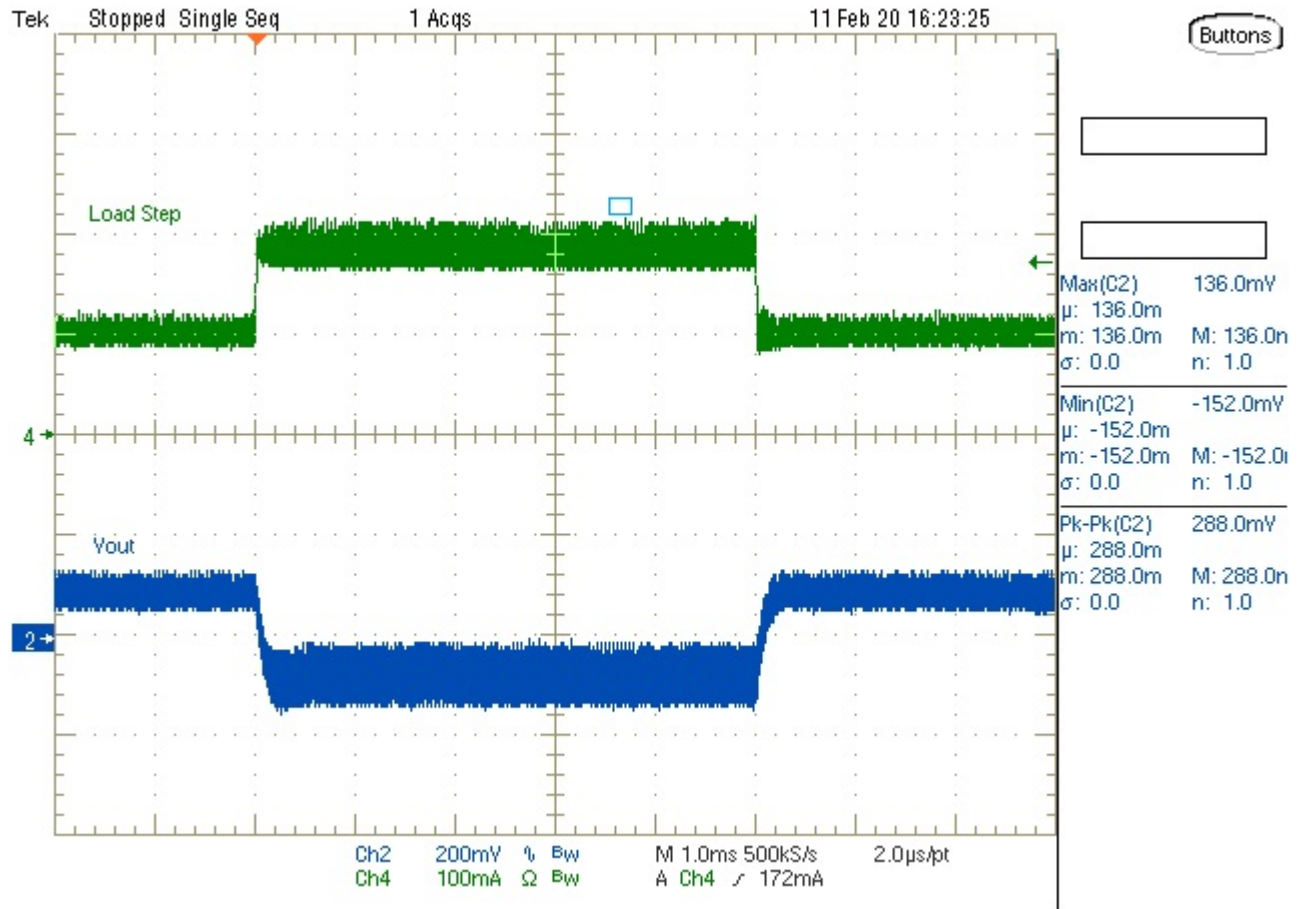


Figure 3-9. Output1: Input Voltage = 10 V; Load Current = 0.1 A to 0.2 A

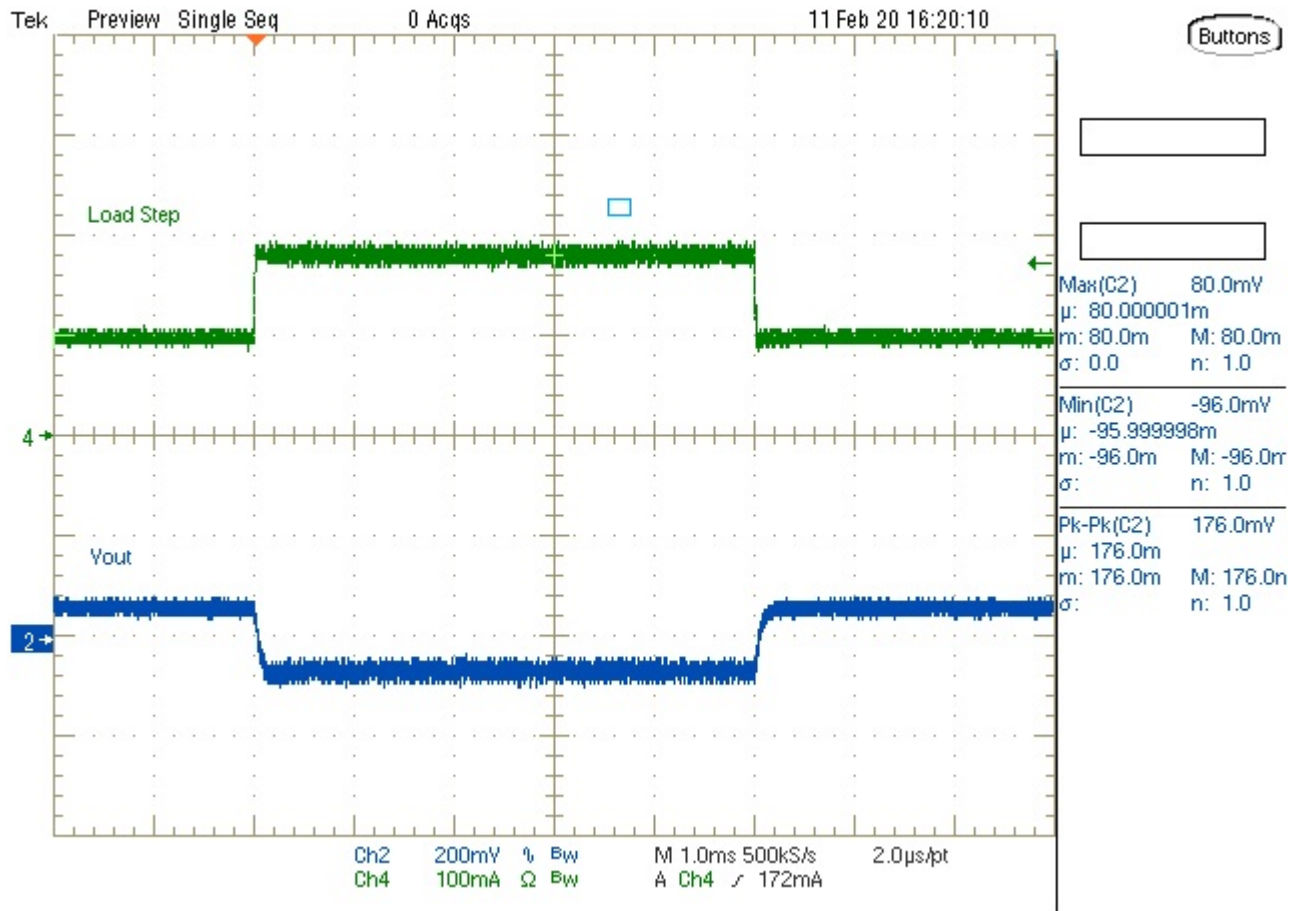


Figure 3-10. Output1: Input Voltage = 30 V; Load Current = 0.1 A to 0.2 A

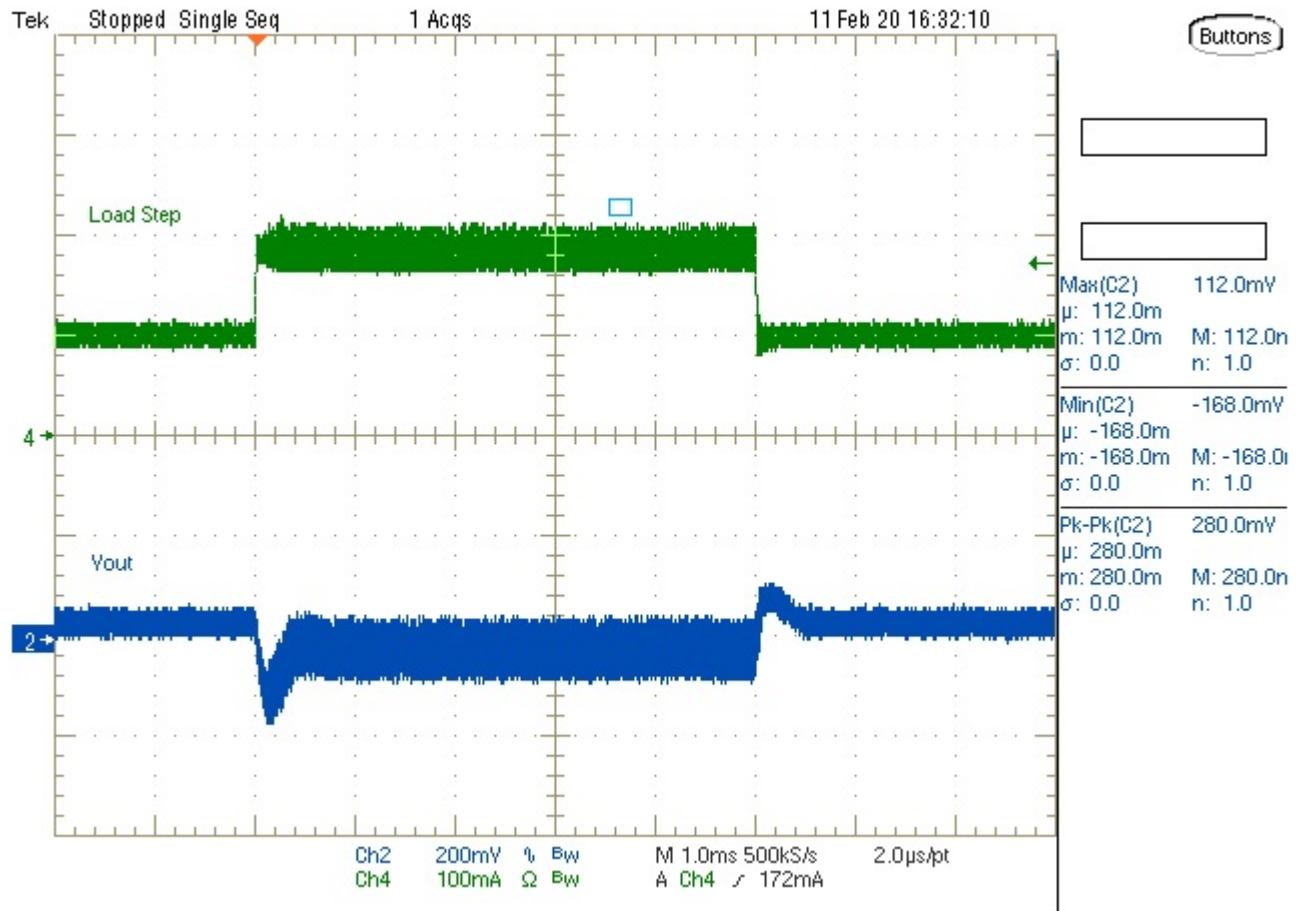


Figure 3-11. Output2: Input Voltage = 10 V; Load Current = 0.1 A to 0.2 A

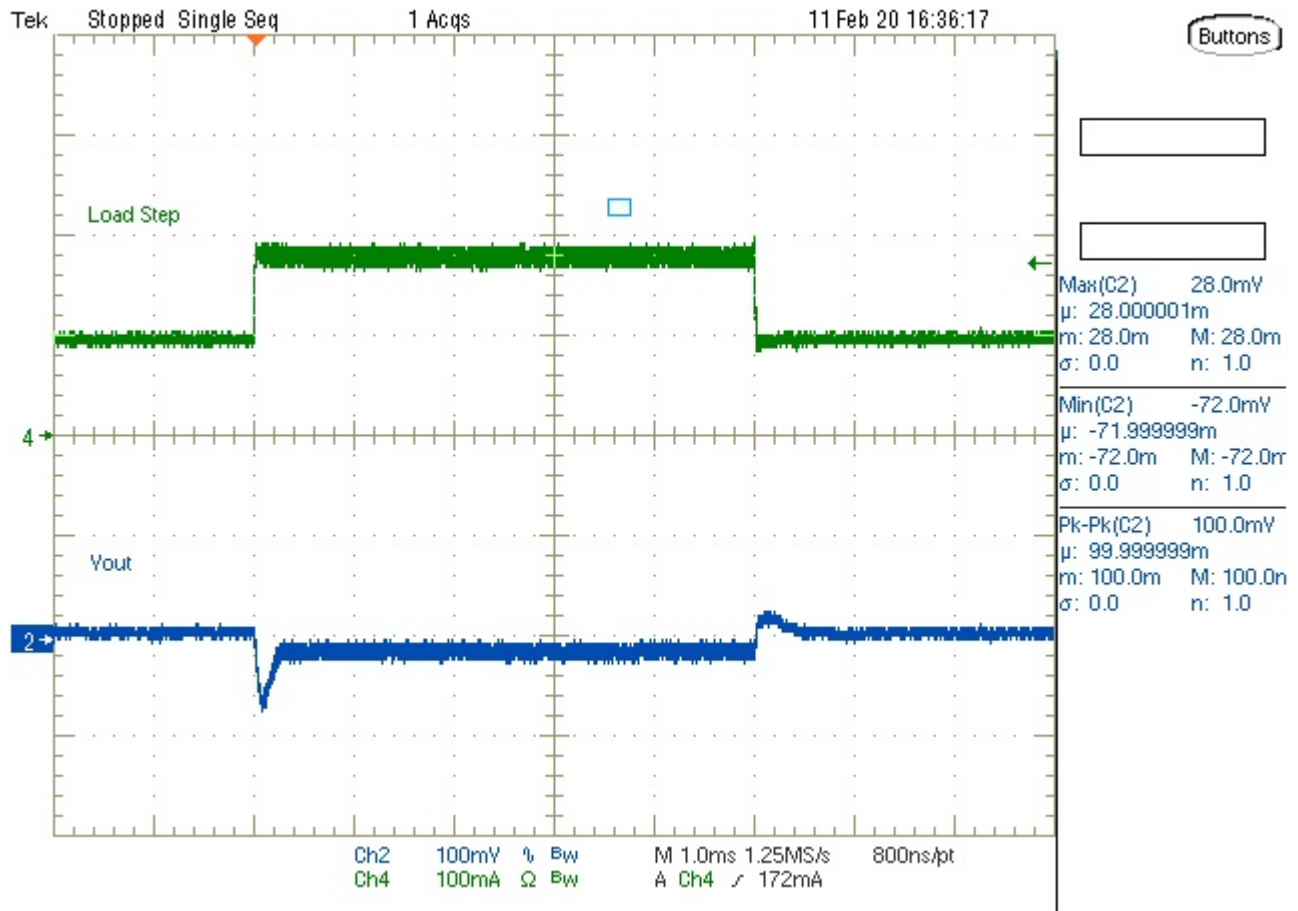


Figure 3-12. Output2: Input Voltage = 30 V; Load Current = 0.1 A to 0.2 A

3.4 Start-up Sequence

Start-up behavior is shown in the following figures.

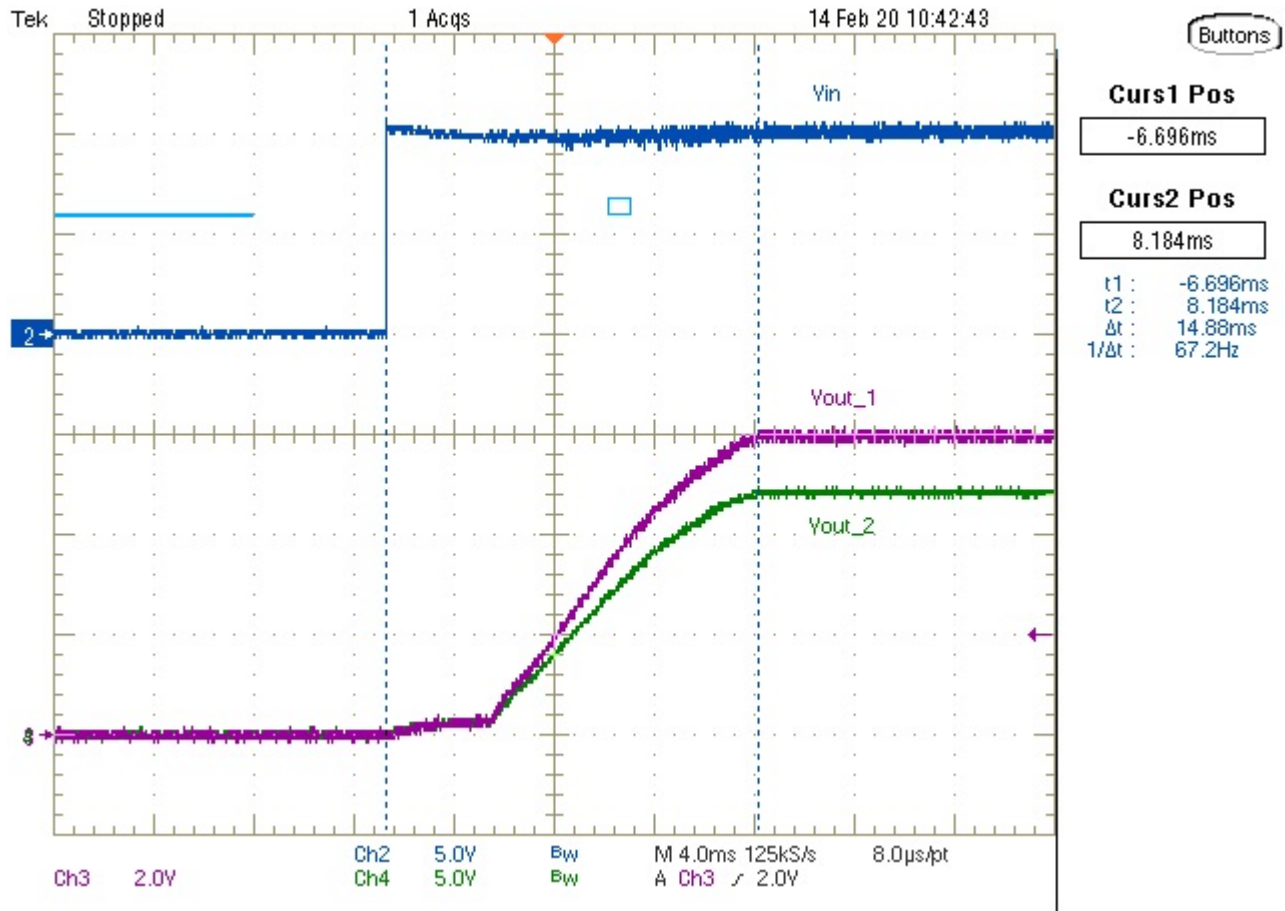


Figure 3-13. Input Voltage = 10 V; Load Current = Full Load

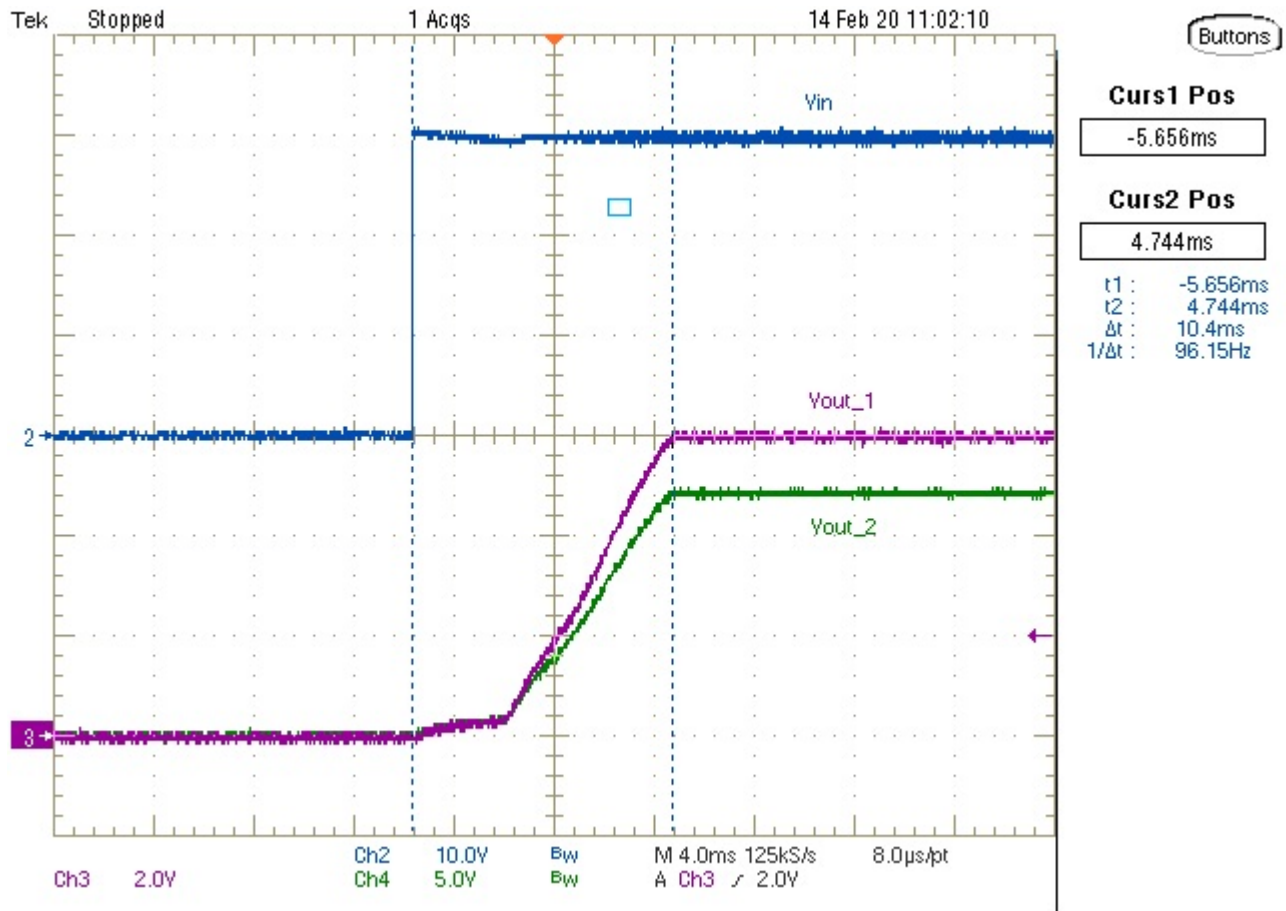


Figure 3-14. Input Voltage = 30 V; Load Current = Full Load

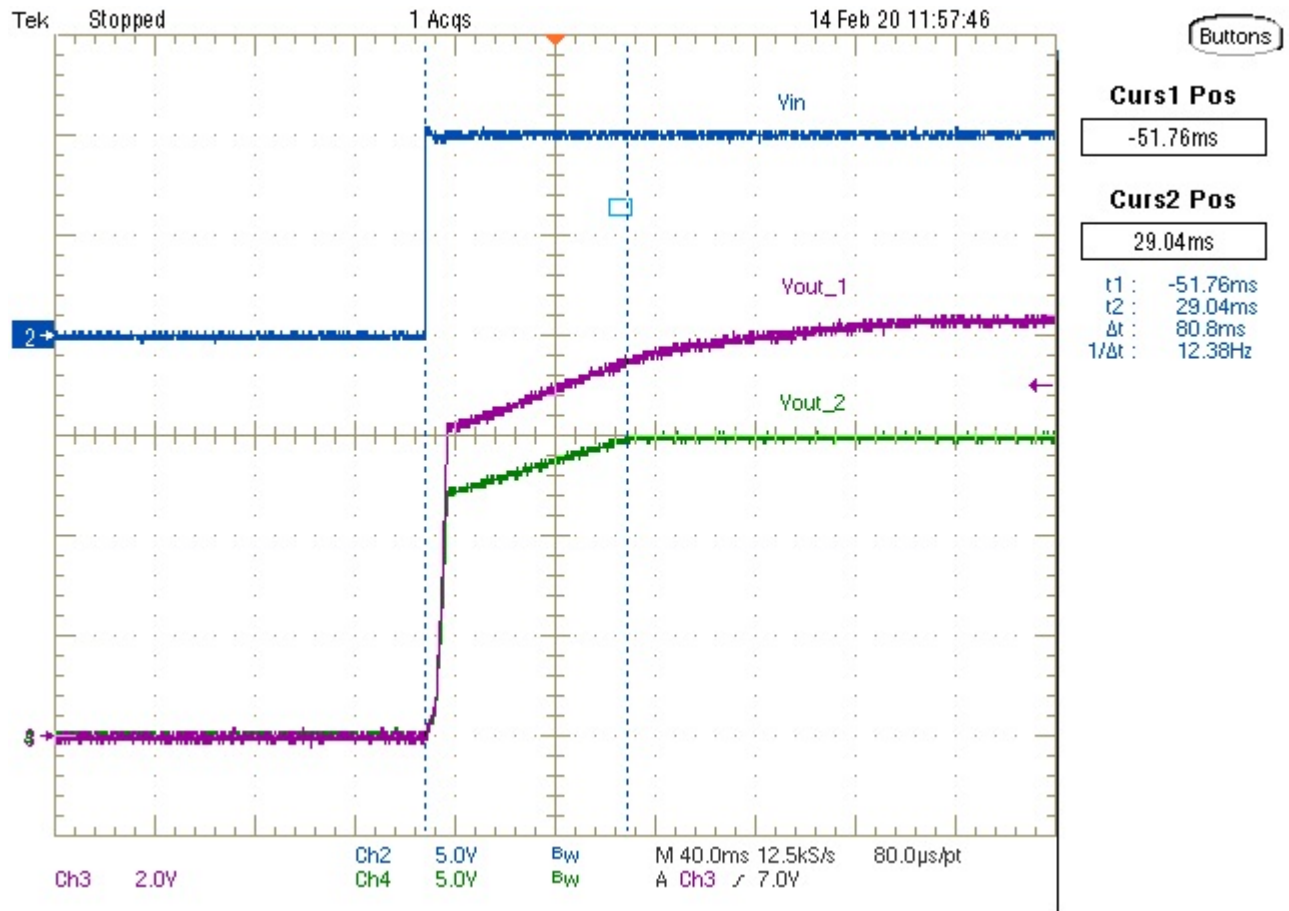


Figure 3-15. Input Voltage = 10 V; Load Current = No Load

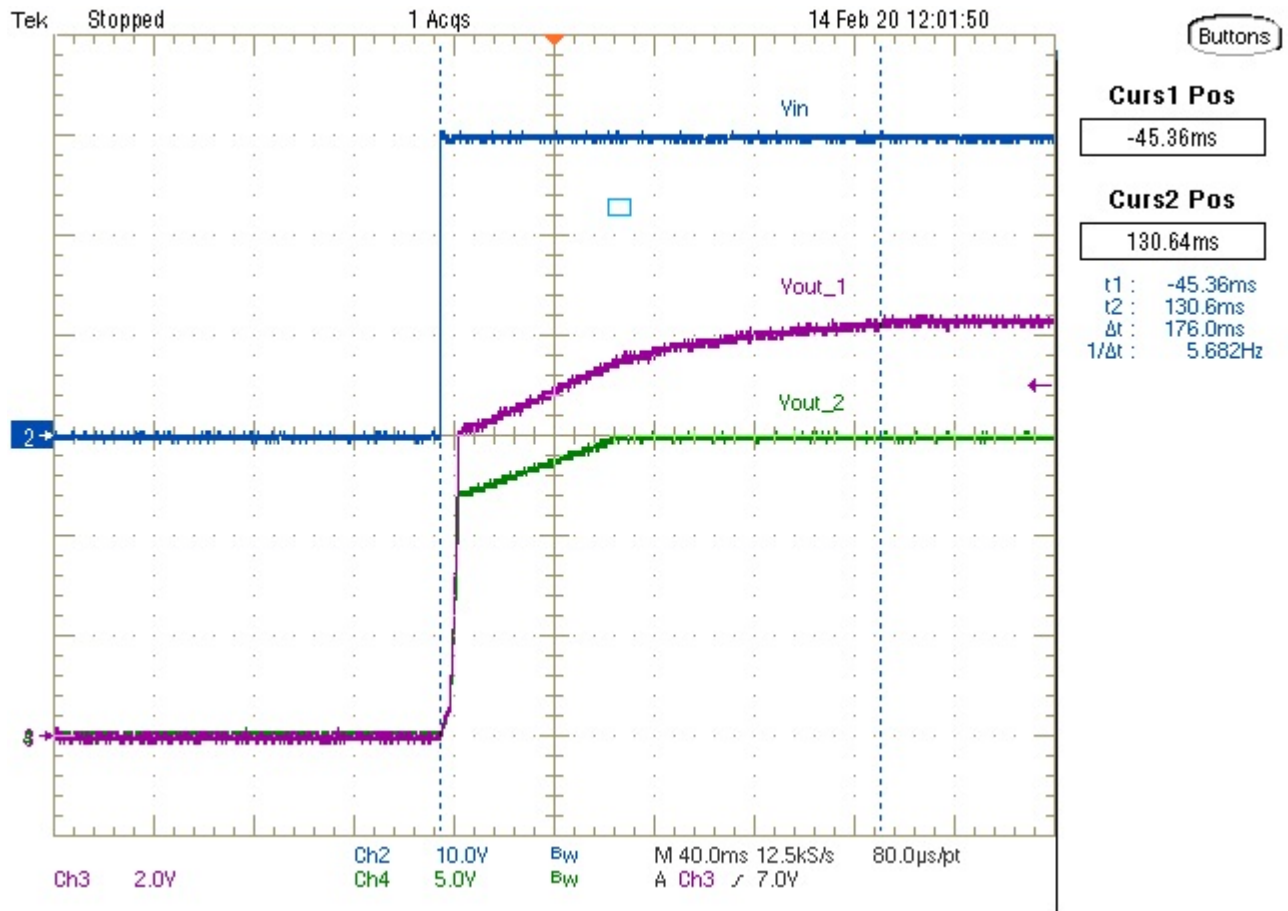


Figure 3-16. Input Voltage = 30 V; Load Current = No Load

3.5 Shut-down Sequence

Shut-down sequence is shown in the following figures.

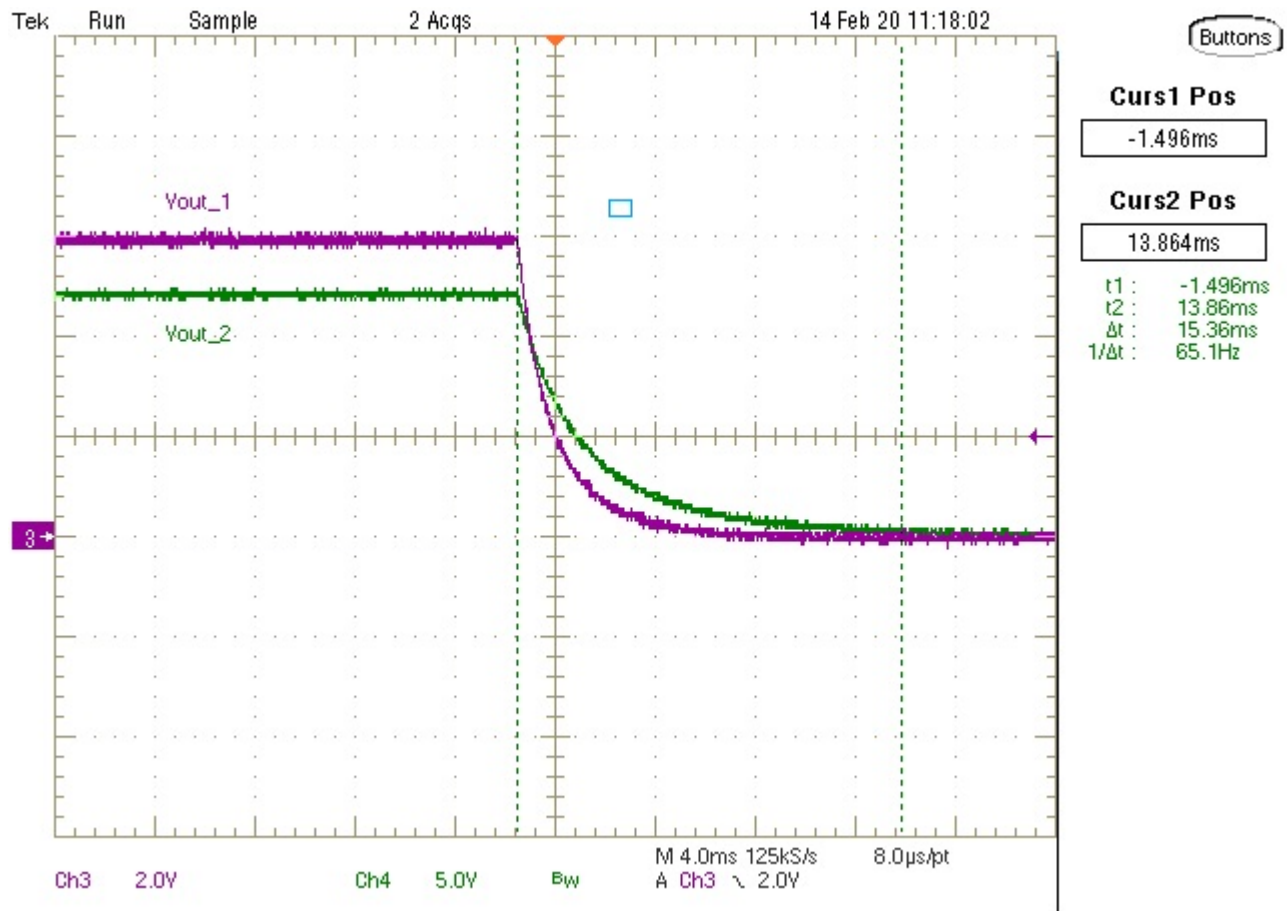


Figure 3-17. Input Voltage = 10 V; Load Current = Full Load

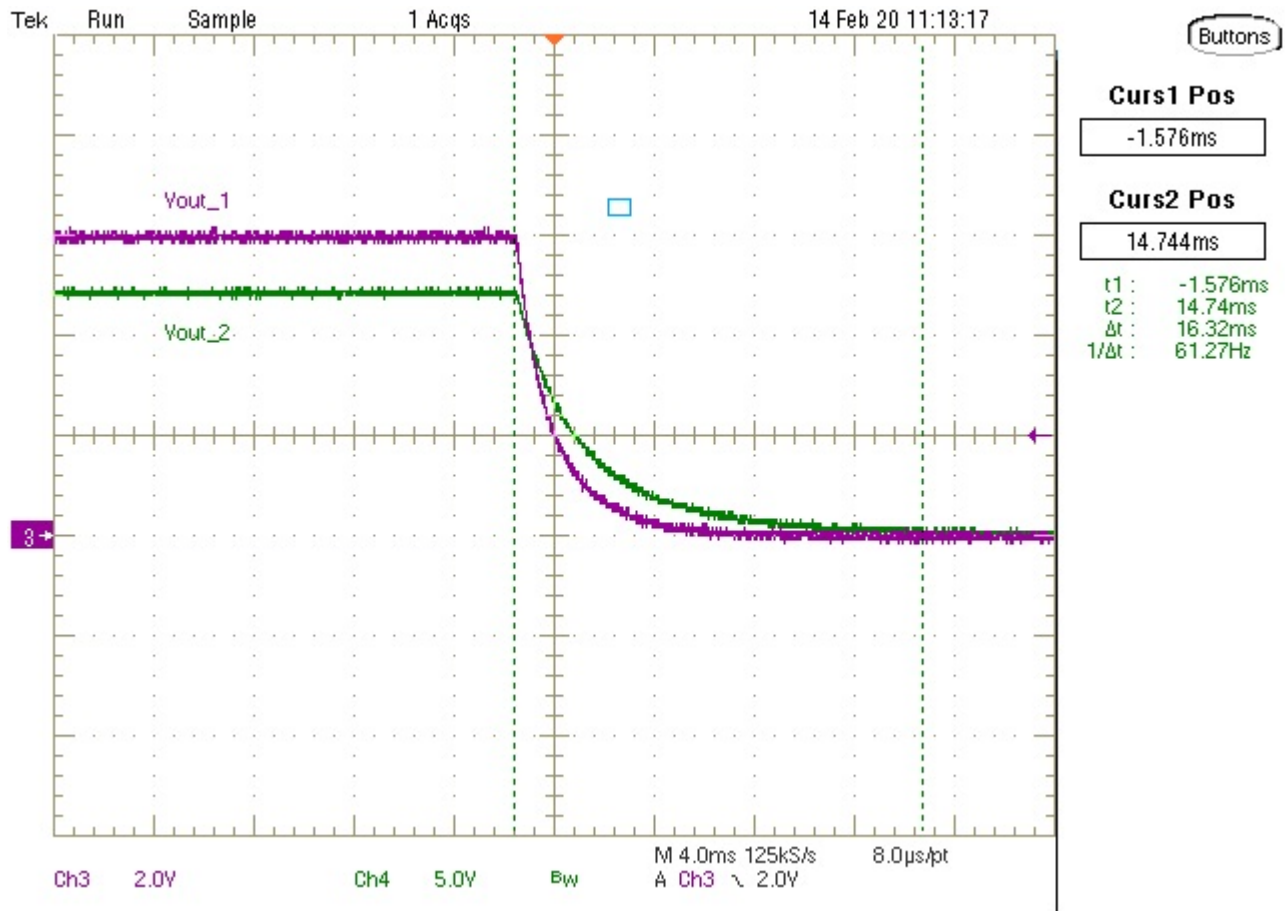


Figure 3-18. Input Voltage = 30 V; Load Current = Full Load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated